

Electrical Circuits

R.J. Marks II Lecture Notes

Texas Tech University (1976)

- PRELIMINARY CLASS ROLLS -

RR001

DEPARTMENT 590 (E E) COURSE 233 SECTION 002

INSTRUCTOR NO INSTRUCTOR

SECRET

STUDENT NUMBER	LAST NAME	FIRST NAME	MI	SCHOOL	CLASS	SEX
460 76 9213	STARK	JOHN	R	04	3	1
453 78 3617	SUGAREK	RICHARD	H	04	4	1
528 11 1482	TAI	HSU-CHEN	J	02	2	1
467 86 9902	WISCHNEWSKY	GLENN	R	04	3	1
460 06 9345	WORSHAM	MICHAEL	H	02	4	1
TOTAL NUMBER OF STUDENTS						28

HINTS FOR LAB INSTRUCTORS

Fall 1976

1. Be prepared to discuss in detail the homework which has already been taken up in lecture. Homework assignments will be posted on the blackboard in Room 154.
2. Be prepared with a lecture on the theory, and with typical example problems. To do a good job, prepare well. You're there to help them learn the material. Spend the allotted time.
3. Have problems for students to work in class. Send them to the board to do problems.
4. Pass out lab experiment sheets one week in advance.
5. Get together with the other lab instructors at a convenient time (ex. on Friday before the students do an experiment) and perform the experiment to be done the next week. Check out the necessary equipment for the week. Equipment should be checked into the stock room at the end of the week by the instructor who has the last lab of the week.
6. Explain purpose of the experiment and measuring techniques to be used.
7. Give frequent quizzes on lab experiments and lecture material.
8. The laboratory grade will count 20% of the student's total grade for the course. Keep a record of absences. Turn in a numerical grade at the end of the semester as follows:
 - a. Record each student's full name, number of absences, the final numerical grade and class average on a ditto master which you get from the departmental secretary. Indicate how final grades are determined.
 - b. Make a copy for each instructor in the lecturer sections, and turn them in to Tom Stenis by the first day of final exams.

1976 Lab Schedule, EE 233 & 234

Date	EE233	EE234
Sept. 7-10	*P	Rectifiers
Sept. 13-17	P	P
20-24	P	BJT & FET Amplifiers
27-Oct. 1	P	P
Oct. 4-8	P	Freq. Response
11-15	Meters	P
18-22	P	Recording Instruments
25-29	Resonance	P
Nov. 1-5	P	Op Amp
8-12	Power & 3 phase	P
15-18	P	Transducers
29-Dec. 3	Transformers	P
Dec. 6-10	P	Machines

* Problem session.

Lecture and Lab

Instructors in EE233, 4.

Fall 1976

EE233

Lecture Sections	001	7:30	MW	E156	Stenis
	002	11:30	MF	E156	Marks
	003	8:30	MF	E251	Brock
	004	7:30	TT	E251	Stenis
	005	9:00	TT	E215	Gordon

Lab Sections A, J	1:30 - 3:30	F	E 202	Trotter ✓
B	Arrange			Trotter)
C	1:30 - 3:30	Th	E156	Hubbard ✓
D	3:00 - 5:00	Th	*	Hubbard X
E	1:30 - 3:30	M	E202	Kirbie ✓
F	3:30 - 5:30	M	E67	Note ✓
G	3:30 - 5:30	W	E67	Note ✓
<u>H</u>	1:30 - 3:30	Tue	E67	<u>Hiang</u>

EE234

Lecture Sections:	001	10:30 - 12:00	TT		Stenis
	002	9:00	TT	E251	Stenis

Lab Sections:	A	3:30 - 5:30	F	E202	Yao
	B	10:30 - 12:30	Tu	*	Yocum

*These are scheduled for E157, which is not available. Meet in E67 until a suitable class room is found.

1. A point charge $Q_1 = +1.6 \times 10^{-18}$ coulombs, is separated from another point charge $Q_2 = -3.2 \times 10^{-17}$ coulombs, by a distance of 10^{-3} meters. The charges are in a vacuum.


- a) Sketch a diagram of the physical layout.
- b) Find the force on each charge and indicate the direction on the sketch.

2. A $+1.6 \times 10^{-19}$ coulombs charge (Q_3) is brought into the vicinity of the charges of problem 1. If $Q_1 + Q_2$ remains fixed in position, find at least one point where Q_3 could be located and the net force on it be zero. How many such points are there?

3. In the glass tube of fig. 2, the density of free electron is equal to the density of free ions, and is 1.6×10^{12} coulombs per cubic meter. If the electrons are travelling at 10^4 m/sec. and the ions at 10^6 m/sec., calculate the current from plate (a) to (b), assuming plate (a) is positively charged.

4. A copper wire, 0.01 meters in diameter, has a density of free electrons equal to 84×10^{20} electrons/m³. If a current in the wire is 2 amperes what is the average velocity of the electrons?

5.

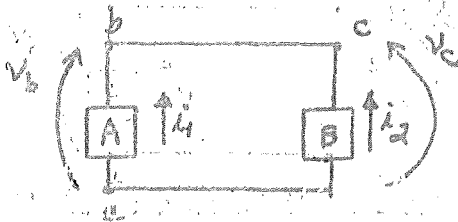

In the circuit shown,
 $i_1 = 1$ ampere $= -i_2$, $v_b = v_c$
 $= 5t$.

1) Sketch curves of i_1 , v_b and power supplied by box A vs. time, from zero to 10 seconds.

2) Calculate the power supplied by box A at time = 1, 2, and 5 seconds.

3) Calculate the power absorbed by box B at 1, 2 and 5 seconds.

4) Calculate the energy supplied by box A from 0 to 5 seconds.

6. In the circuit of problem 5, $v_b = 10 - 5t$, $i_1 = -i_2 = 10t$.


a) Sketch the curve of p_s of box A vs t , from 0 to 5 seconds.

b) Calculate p_s of box A at $t = 0, 1, 2, 3, 4$ seconds.

c) Calculate energy supplied by box A from 0 to 5 seconds.


7. Some problem, number of 10^{-12} C .
8. For problem 7, find the power absorbed by box B at $t = 0, .5, 1$ and 2 seconds.

9. Omit

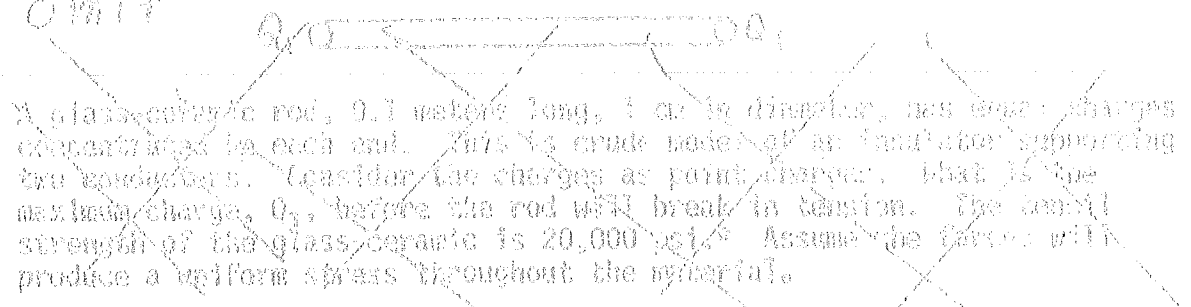

*P.132 CRC Handbook of Tables for Applied Engineering Science.

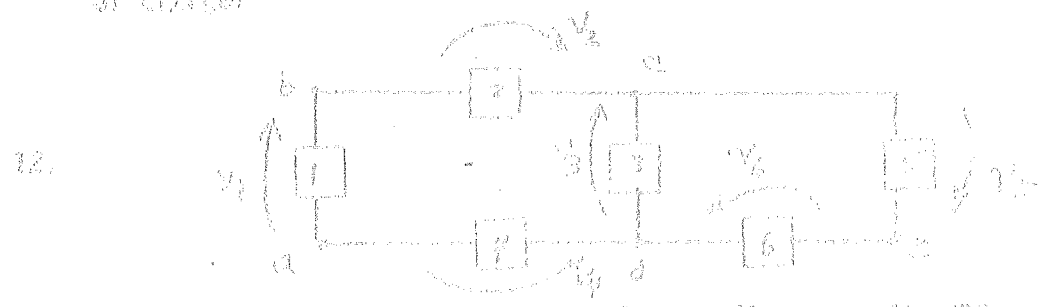10. A consumer of electrical energy requires 100 ampere of steady current over an 8 hour period, from a steady voltage source at 110 volts.
- What power is the customer using?
 - How much energy in joules and watt-sec. is he using in the 8 hr. period?
 - If he is paying 3 ¢ per kilowatt-hr. for the energy, what is the cost for the 8 hrs?
11. How many electrons make up a coulomb? If a gas ion is doubly ionized (loses 2 orbital electrons), how many such ions are there in a coulomb of charge?



Using the defined voltages shown in the figure, write KVL around the following loops:

- 1) A b c d a 2) d c e d 3) a b c d a
- 4) d e c d 5) e d c b a

7) 13. For the circuit of problem 12:

- a) Define element currents.
- b) Write KCL, using the currents of part (a), for the following nodes:
 1) b 2) c 3) d 4) e 5) a
- c) What elements (boxes) are in series in this circuit?
- d) Define the branch currents. Write KCL, using these currents, for nodes c and d.

14. The voltages in the circuit of problem 12, are as follows:
 $V_1 = 10V$, $V_2 = -2V$, $V_3 = 4V$, $V_5 = -2$ volts







- a) Find V_4 , V_6 , V_{cd} , V_{eb} .
- b) If the loop current circulating around a b c d a is 2 amperes, and the loop current circulating around d c e d is 3 amperes, find the following:
 - 1) Power supplied by : (a) element 1 (b) element 3.
 - 2) Power absorbed by : (a) element 2 (b) element 5.
 - 3) Which elements in the circuit are sources?
 - 4) Is the sum of power supplied by the sources equal to the sum of all the absorbed power?

Marks

LAD Problems for EE 235



1. For each circuit assigned by the instructor, do the following:

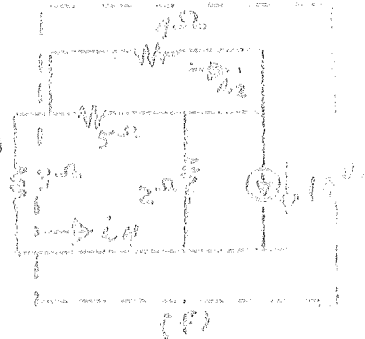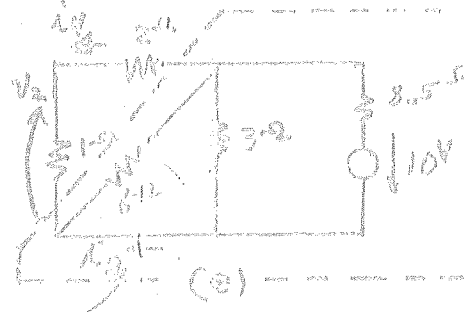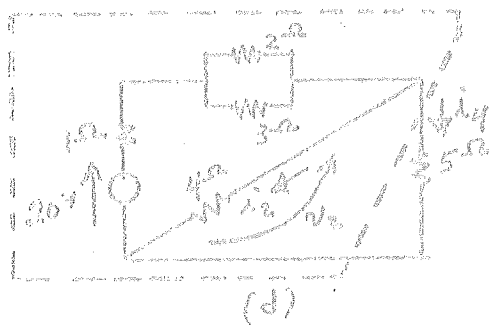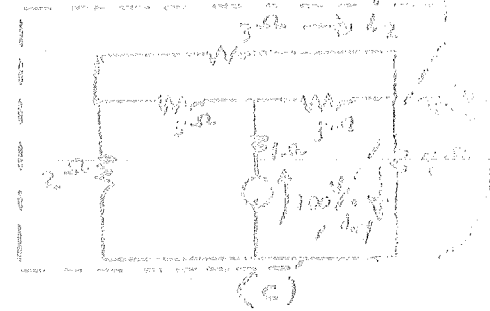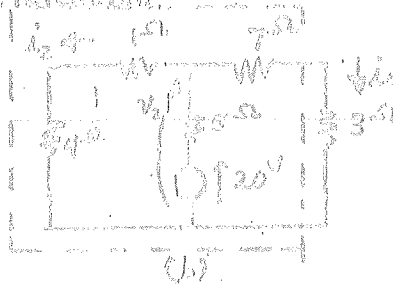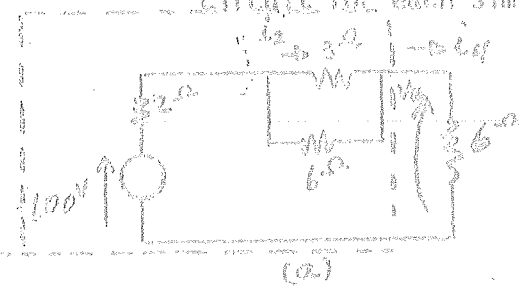A) Reduce each to one resistor in series with the source. Draw a new circuit for each simplification.




- b) Find the power supplied by each ideal source.
- c) Find V_2 .
- d) Find i_2 .

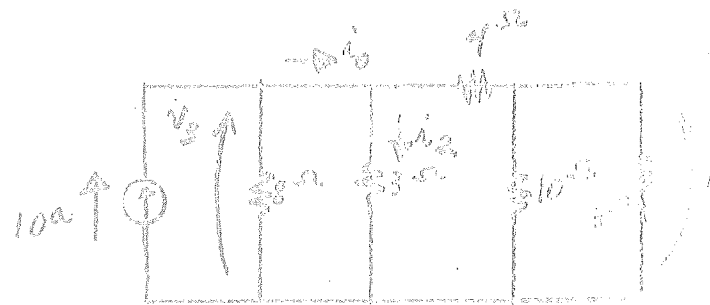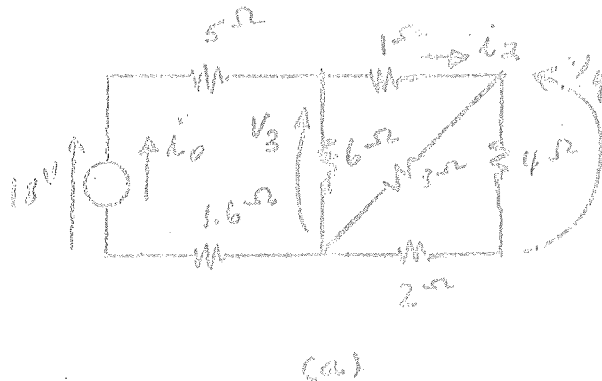2. Simplify the following circuits to one resistor in series with the source. Draw a new circuit for each simplification.



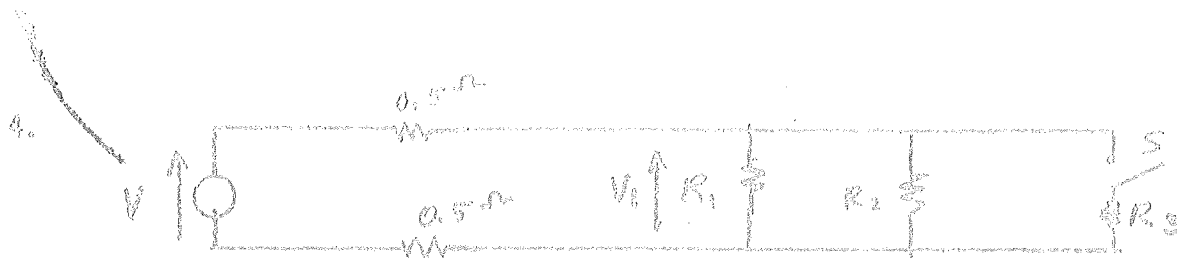3. In each of the circuits above, calculate the following: i_0 , V_3 , i_2 , V_4 .



A 1000 volt source is providing power to resistive loads $R_1 = R_2 = R_3 = 33$ ohms., through a transmission line having 0.5 ohms resistance per wire.

a) With switch S open, find the following:

V_1 , power loss in the transmission line, power absorbed by the loads, current in R_1 or R_2 .

b) Repeat part (a) with switch S closed.

5. Refer to problem one for the circuits assigned by your instructor:


a) Reduce the active portion of the circuits which are enclosed in boxes, to a single ^{voltage} source and resistor in series.

b) Convert each active portion enclosed by a box, to a constant current source and parallel resistor.

c) Find the current i_4 for each circuit assigned.

6. a) Reduce the active portion of the circuit which is enclosed in a box, to one resistor and one ideal source.

b) Calculate i_2 and i_3 .

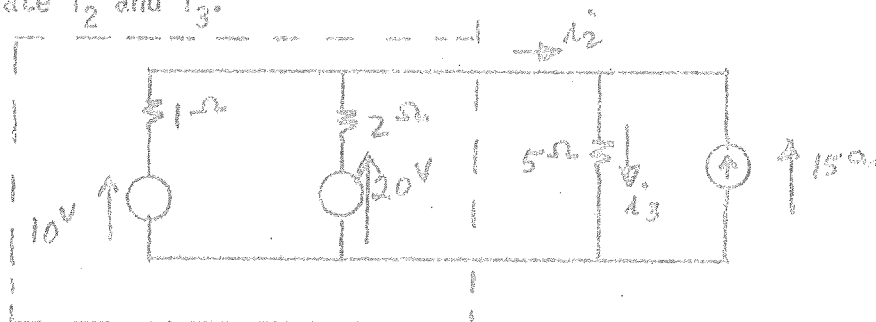


7. A manufacturer's specification on a power supply is as follows: No load (open circuited) voltage is 100 volts, full load current is 10 amperes, full load voltage is 99.99 volts.

a) What is the full load resistance?

b) What is the internal resistance (R_T) of the power supply?

c) If a 20 ohm resistor is connected to this power supply, what is the terminal voltage?

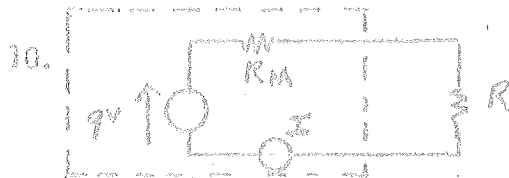8. Draw a diagram and explain the operation of a D'Arsonval type permanent-magnet moving-coil meter.
9. A D'Arsonval type meter is used as a basic movement for constructing D.C. ammeters or voltmeters. In a particular movement, full scale deflection occurs with 1 ma of current in the meter and a 50 mV voltage across the meter.
- What parallel resistor (shunt) should be provided with this movement, to make an ammeter with a 10 ampere full scale reading?
 - What shunt is needed to make a 100 ampere full-scale reading ammeter?
 - What series resistor is needed to make a voltmeter with 5 volt full scale reading?
 - Repeat (c) for a 100 volt full scale reading.




The circuit in the box represents an ohmmeter (used to measure resistance). The meter is a D'Arsonval type having full scale reading with 50 μ a current and a voltage across it of 50 m volts.

R represents the unknown resistance.

- What resistive value should R_m have if full scale deflection is desired when $R = 0$?
 - If R_m is 100K ohms, what value of R would produce full scale deflection?
 - What value should R_m have if a full scale reading is desired when $R = 50K$ ohms?
11. These resistors are connected in series, to a source which provides 100 volts open circuit, and has 9 ohms of internal resistance. The resistors have the following ohmic values: $R_1 = 8900$, $R_2 = 1001$, $R_3 = 90$.
- Draw the circuit diagram.
 - Find the voltage across each resistor.
 - A voltmeter having a full scale reading of 100 volts and a sensitivity of 200 ohms/volt, is used to measure the voltage across each of the three resistors. Calculate the voltage which the meter will measure, as it is connected across each resistor. Compare these readings with part (b) calculations.

12. A power supply has 8 ohms of internal resistance and supplies 800 volts when open circuited. A 2 ohm resistor is connected across the supply terminals.
- Draw the circuit diagram.
 - Calculate the current in the 2 ohm resistor and the voltage across it.
 - An ammeter with 0.5 ohms resistance is connected in series with the 2 ohm resistor. Calculate the current which the meter will measure and the voltage across the 2 ohms with the meter in the circuit.

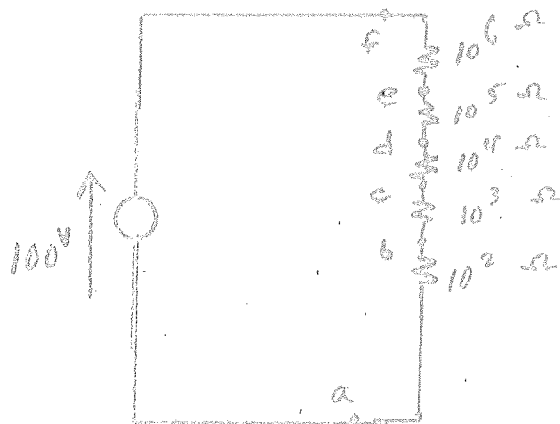
13. An electronic d.c. voltmeter has a switch with which the following full-scale ranges are available:
 0- .01 volts, 0- .1 volts, 0-1. volt, 0-10 volts, 0-100 volts.
 The meter resistance is 1 M ohm for each range. The meter is used to measure the following voltages, as indicated in the circuit shown:



$$V_{af}, V_{ab}, V_{bc}, V_{cd}, V_{de}, V_{ef}$$

- For each of the voltages, indicate the following:
 - Which range should be selected? (The upper half of the meter range is best).
 - What value does the meter indicate in each case? Compare each voltage with the value before the meter was added.


14.

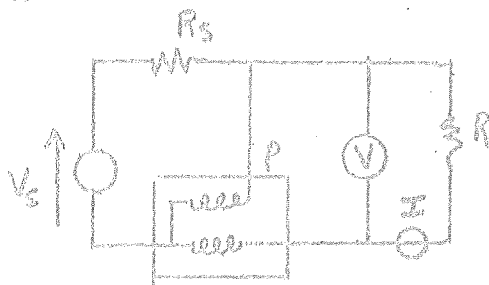

The wattmeter and ammeter shown connected in the accompanying circuit diagram, read the following values: $P = 200$ watts, $I = 2$ amperes.

Find the value of R and the voltage across it. Neglect the voltage across the ammeter.

15.

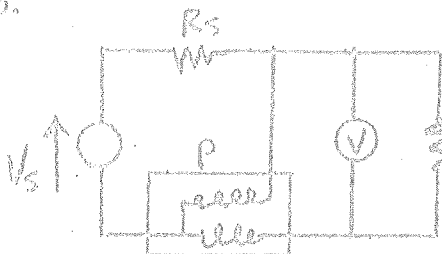

The wattmeter in the accompanying circuit reads 4 K watts and the voltmeter reads 0.5 K volts. Find the value of R and the current through R . Neglect any circuit changes which the meter produces.

16. A d.c. generator supplies 1 KW open circuited, and has 1 ohm of internal resistance. It is connected to a pair of wires (transmission line) each one being 200 feet long and having 0.01 ohms/ft. resistance. A 20 ohm load resistor is connected at the end of the line:

- a) Draw a circuit diagram and include meters for measuring the power, current and voltage at the generator and load ends of the line.
- b) Calculate each of the meter readings, neglecting any effect the meters have on the circuit.

17. The load resistor of problem 16 is changed so that the voltmeter and ammeter at the generator end read, respectively: 900 volts and 100 amperes.


- a) Find the readings of the rest of the meters in the circuit of problem 16.
- b) Find the value of load resistance.

18. A 400 KV d.c. transmission system is capable of supplying 100 M watts at the generator end. A 50 mile transmission line from the generator to a load center uses number 00 AWG copper wire. Assume 400 KV at the generator end, and the generator is supplying rated power.

- a) What is the full-load current at the generator end?
- b) What is the voltage at the receiving end?
- c) What is the power delivered to the load and power loss in the transmission line?


19. Describe a double-pole, single throw switch; a double-pole, double throw switch.

20.

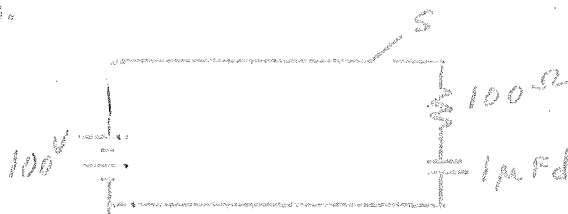


The switch S is closed at $t = 0$, and the capacitor has no charge on it at that time.

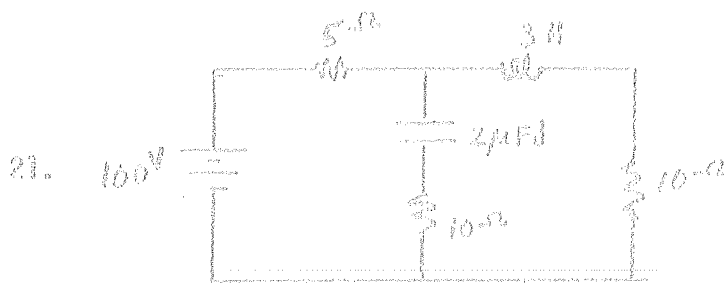- a) Determine the equation for the current.
- b) What value does the current have in one time constant? Two time constants?



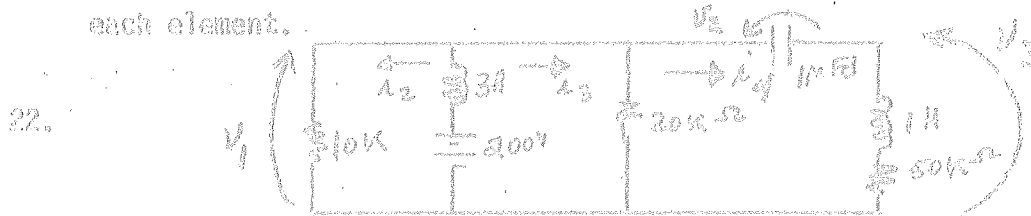Find the steady-state current in each element and the voltage across each element.



Find the steady-state values of the following:

- Current in the source
- i_2 , i_3 , i_4
- V_1 , V_2 , V_3

Works

Here is a set of problems suitable
for lab. work. When you finish with little
set # II, and don't wish to keep it, return
it to me (put it in my box). If you
have solutions to any of the problems in
that set, I would appreciate a copy.

T Stennis

I'll be out of town Fri., so
check my blackboard before then.

45

marks


1. A size AWG (American Wire Gauge) 14 copper conductor with RWI insulation has an allowable current carrying capacity of 20 amperes. This is based on a room temperature of 36°F , using open wiring.

Reference:

Bolz, Ray E., and George L. Tava, "Handbook of Tables for Applied Engineering Science", Ohio: The Chemical Rubber Company, 1970.


- a) What is the resistance of 20 feet of AWG 14 copper wire?
 - b) What is RWI insulation?
 - c) What is the diameter in mils, of this wire?
 - d) What is the power absorbed by 20 feet of the wire when carrying its maximum allowable current?
 - e) What is the voltage across the 20 feet of wire when carrying maximum allowable current?
2. Repeat problem 1 for AWG 00 wire which has 225 amperes allowable current.
 3. The resistivity of nichrome is 100×10^{-8} ohm - meters at 20°C , and its temperature coefficient is 4.4×10^{-4} $(\%/^{\circ}\text{C})$. A 100 ohm wire wound resistor is to be made from #22 size nichrome wire (6.44×10^{-2} cm. diameter).
 - a) What length of wire is needed (20°C)?
 - b) When the voltage across the resistor is 10 volts, how much power is it absorbing?
 - c) If the temperature rises to 60°C , what is the resistance?
 4. A cable 20 meters long is used to connect a 400 volt source to a 5 ohm load. The cable has two copper conductors, each of size AWG 10.
 - a) What is the voltage across the load?
 - b) Repeat part (a) if aluminum is substituted for the copper.
 5. A 1000 ohm resistor is rated for 25 watts.
 - a) What is the maximum ^{possible} current through it and ~~maximum voltage across it~~ without exceeding its rating? *What is the voltage in this case?*
 - b) *What is the maximum possible voltage across it, without exceeding its rating? What is the current in this case?*

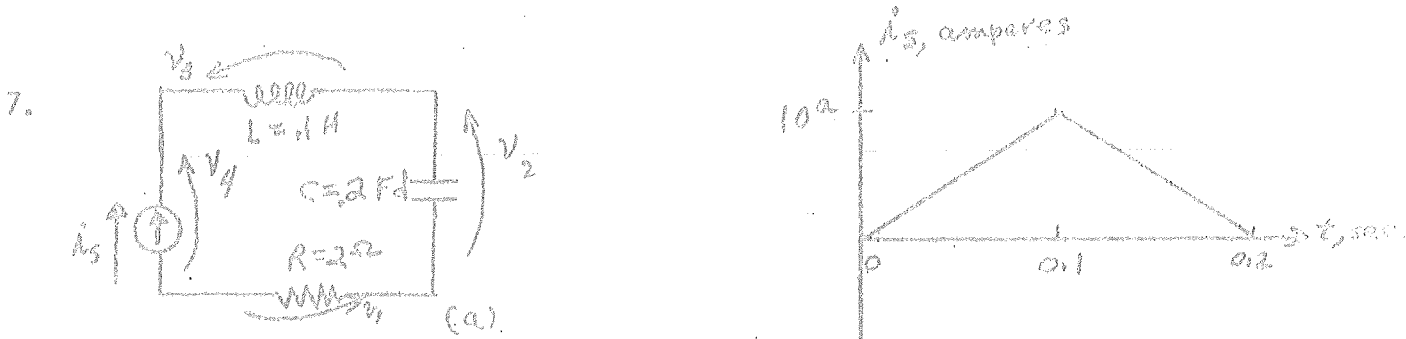6. a) A 10,000 ohm resistor in an electronic circuit will have 100 volts across it. What should be its power-rating?
 b) If two 5000 ohm resistors in series are substituted for the 10,000 ohm resistor, what should be the power-rating of each one?




The circuit shown in fig. (a) has a source supplying current as shown in figure (b). There is zero energy stored in L and C at $t = 0$.

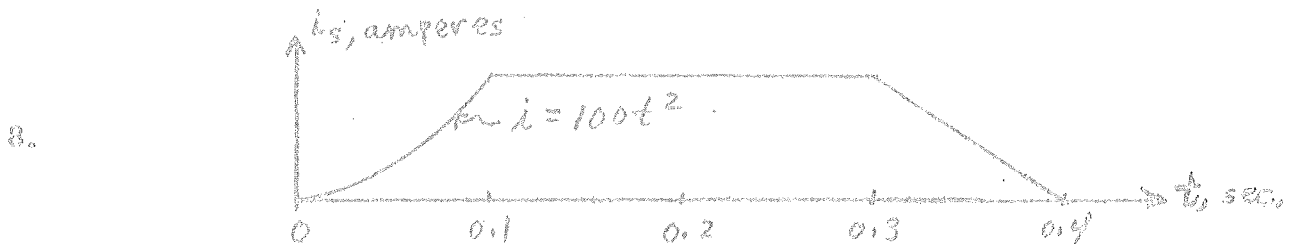- a) Sketch curves of v_1 , v_2 , and v_3 vs. t , showing values at $t = 0, .1$ and $.2$ seconds, $.3$ and $.4$ sec. for prob. 8.
 b) Sketch curves of energy stored in L and energy stored in C vs t , showing values at $t = 0, .1$ and $.2$ seconds, $.3$ and $.4$ seconds for prob. 8.
 c) What is the instantaneous power absorbed by R at $t = 0.05$ and 0.15 seconds?
 d) Repeat (c) for the inductor, and for the capacitor.



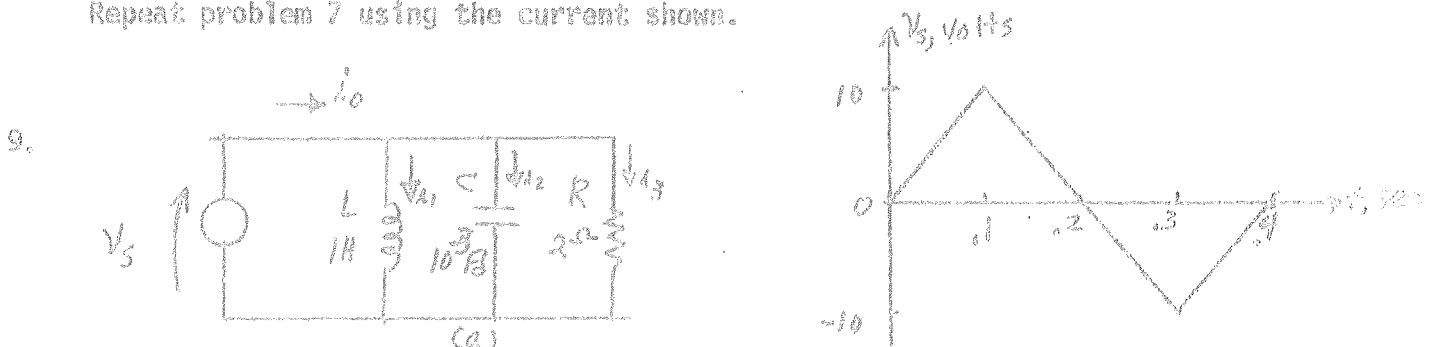Repeat problem 7 using the current shown.



The source voltage waveform for circuit (a) is given in fig. (b). No energy is stored in L or C at $t = 0$.

- a) Sketch i_1 , i_2 and i_3 vs t . Show values at $t = .1, .2, .3, .4$ and $.5$ seconds.
 b) Sketch a curve of i_0 vs t .
 c) What energy is stored in L and in C at $t = .3$ seconds?
 d) What instantaneous power is the source supplying at $t = 0.2$ seconds?

- e) How much energy has each of the elements absorbed by time $t = 0.5$ seconds?
 d) Find the energy supplied by the source, by time $t = 0.5$ seconds.

11.

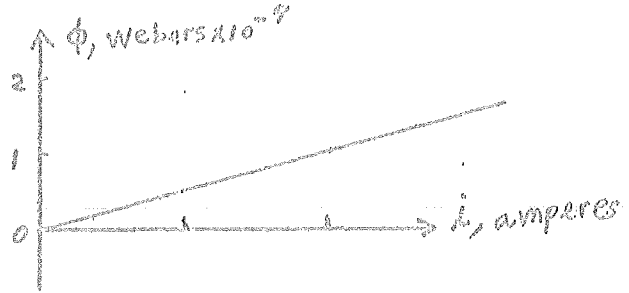
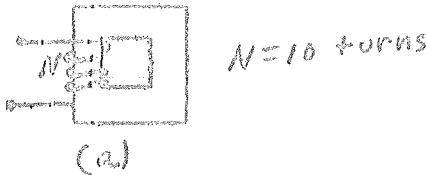



Figure (a) shows a coil with a closed iron core. The ϕ - i curve for this coil without the iron core is shown in fig. (b).

- a) What is the inductance of the coil without the iron core?
 b) If the iron core increases the slope of curve fig. (a) by 2000 times, what is the inductance of the coil with the iron core?
 c) If the number of turns for coil of part (b) is doubled, find the new value of inductance.

12. A parallel plate condenser with an air dielectric has a value of capacitance of 10^{-6} Fd.

- a) What is the new value of c if the distance between plates is doubled? How much is c increased by changing the dielectric to polystyrene?


13.

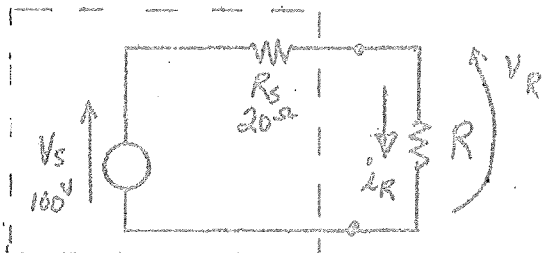

The model for a practical source connected to a load is shown in the figure.


- a) Find v_R and i_R for the following values of R (in ohms).
 $R = 0.5, 10, 20, 100, 200$ and infinity.
 b) Plot a curve of v_R vs i_R .
 c) On one set of axes, plot a curve of power absorbed by R and power absorbed by R_s vs R .
 d) What is the relative values of the two resistors (R, R_s) for the case of maximum power absorbed by R ?

14.

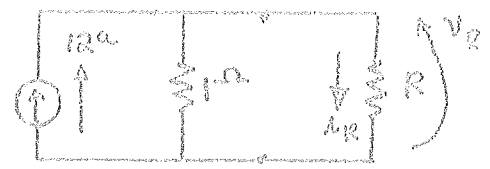

Plot curves of v_R and i_R vs R , using these values of R (ohms): 0, 50, 1, 2, 10, 100, infinity.


15.

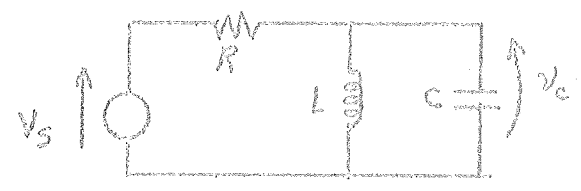


$v_c(0) = -2$ volts

- a) Define loop currents.
- b) Write the voltage equations in terms of the defined currents and circuit elements.

16.

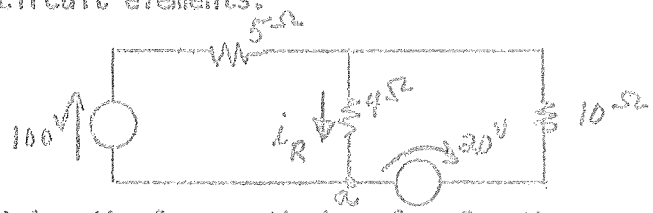

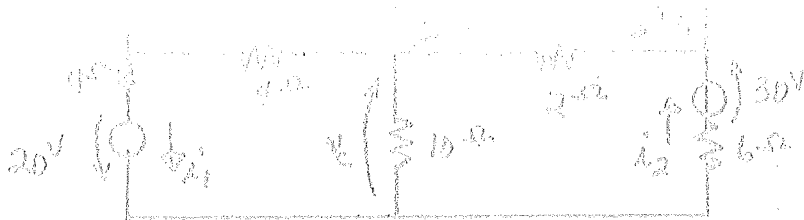- a) Using the loop method, solve for the currents in each source.
 - b) Find the power supplied by each source
 - c) Find the power absorbed by each resistor.
17. a) For the circuit in problem 16, define branch currents and solve for the current in the 20 volt source.
- b) Find the power supplied by the 20 volt source.
18. a) For the circuit of problem 16, define the minimum number of unknown voltages, using node 'a' as a reference.
- b) Solve for the voltage(s) of part (a).
- c) Find i_R .




- Solve for current i_1 using the loop method.
- Solve for voltage v_c using the node method.

20. For the circuit of problem 19:

- Solve for current i_2 using the loop method.
- Solve for voltage v_b using the node method.

21.

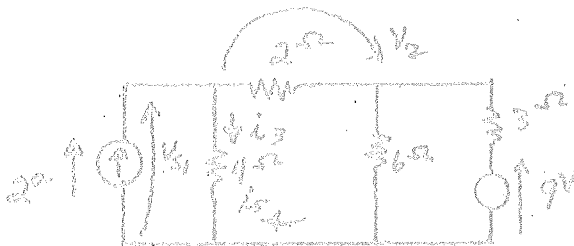

Find the current in the 4 ohm resistor.
Find v_2 , power supplied by the 7 volt source.

22. For the circuit of problem 21, find the voltage across the 6 ohm resistor.
Find i_3 , v_{s1} , power supplied by the 2ampere source.

23. For the circuit of problem 21, find the current in the 2 ohm resistor, and i_1 .

24.

When maximum detail is desirable, and a digital computer is available for a solution, circuit analysis can be done using the following procedure:

- Define branch voltages $v_1, v_2, v_3, v_4, v_5, v_6$.
- Define branch currents $i_1, i_2, i_3, i_4, i_5, i_6$.
- Write KVL in terms of voltages defined in step 1.


$$v_1 + v_2 - v_4 = 0$$

$$v_4 - v_5 - v_6 = 0$$

$$v_3 - v_5 - v_2 = 0$$
- Write ohms law relations for each branch voltage

$$v_1 = v_s + i_1 R_1 \quad v_3 = i_3 R_3 \quad v_5 = i_5 R_5$$
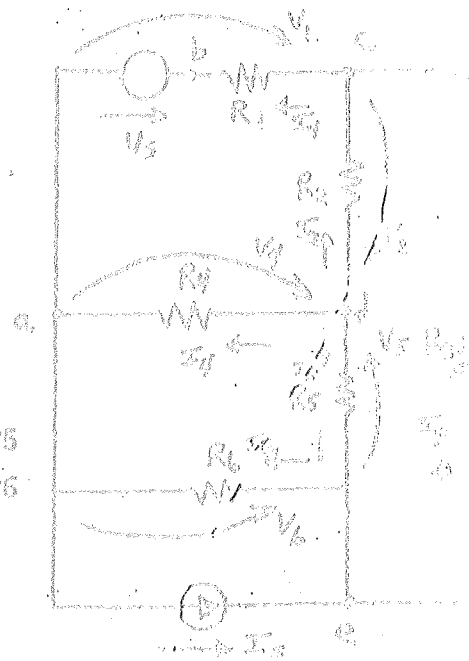
$$v_2 = i_2 R_2 \quad v_4 = i_4 R_4 \quad v_6 = i_6 R_6$$



5. Write KCL for each major node

Node C: $-I_1 + I_2 + I_3 = 0$

Node D: $I_2 + I_4 + I_5 = 0$


Node E: $I_5 + I_5 - I_6 - I_3 = 0$

6. Solve the above 12 equations for the particular unknowns of interest.

PROBLEM

- a) Write the determinant for the voltage V_4 .
- b) Write the determinant for the current I_1
- c) What computer language is best suited for the solution of equations of part (a) or (b)?

25.

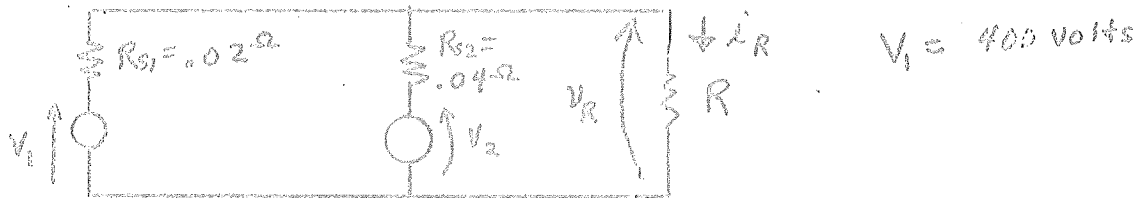

Two generators are supplying power to an industrial plant, represented by $R = 0.5$ ohms. The voltage v_R is to be 392 volts.

- a) Find the value of v_2 needed to provide the required v_R .
 - b) Find the power supplied by each source. (Subtract the loss in R_{s1} or R_{s2}).
 - c) Express the power loss in each generator as a percent of the power absorbed by the load.
 - d) ^{Find} Efficiency.
26. Generator $\mathcal{E}(V_2)$ in problem 24, is removed from the circuit, (open circuited).
- a) Find V_1 needed to provide 392 volts to the load.
 - b) If the maximum voltage for V_1 is 410 volts, what will be the maximum value of v_R ?

27. In the circuit of problem 26, $V_2 = 400$ volts.

- What value will V_R have?
- What power will each generator be supplying?
(subtract power loss in R_{s1} or R_{s2} .)

28. A 12 battery is discharged when its terminal voltage is 10.3 volts. It has internal resistance of 0.01 ohms. A source is connected in series with the battery in order to charge it.

- Draw the circuit and indicate the polarity of the battery and charging source.
- What charging voltage is needed to provide 5 amperes of charging current?
- After one hours time, the battery voltage has risen to 13.2 volts. What charging voltage is needed to maintain the 10 amperes charging current?

29.



(a)



(b)

Several power supplies of each type available in a laboratory.

depicted in the figures are

- How should two supplies of the Fig. (a) type be connected to provide simultaneous voltages of 0, +10, and +20 volts? Indicate the reference node in the connection: Draw the connections.
- Show how to connect two supplies of Fig. (b) to provide simultaneous voltages of: 0, +20, +40, -20, -40 volts.
- Show the connections required to provide simultaneous voltages of -40, -20, 0, +10 volts.

marks

EE 233 Lecture instructors

This experiment will be done, beginning
on Oct 25. When you finish
Ch. I, go to p 180 in Ch. VII
and discuss Resonance, to
prepare them for lab.


T Stenis

Lab 10

Series and Parallel Resonance

The instruments of interest in this experiment are the variable frequency audio oscillator, the HP 400 vacuum tube voltmeter (VTVM), and the oscilloscope. The VTVM is a high impedance voltmeter with reasonable accuracy over the audio frequency range. The oscilloscope is particularly useful as a voltmeter and observing the actual waveforms. Current resonance in the series circuit and voltage resonance in the parallel circuit are to be observed as the source frequency is varied.

Series Resonance

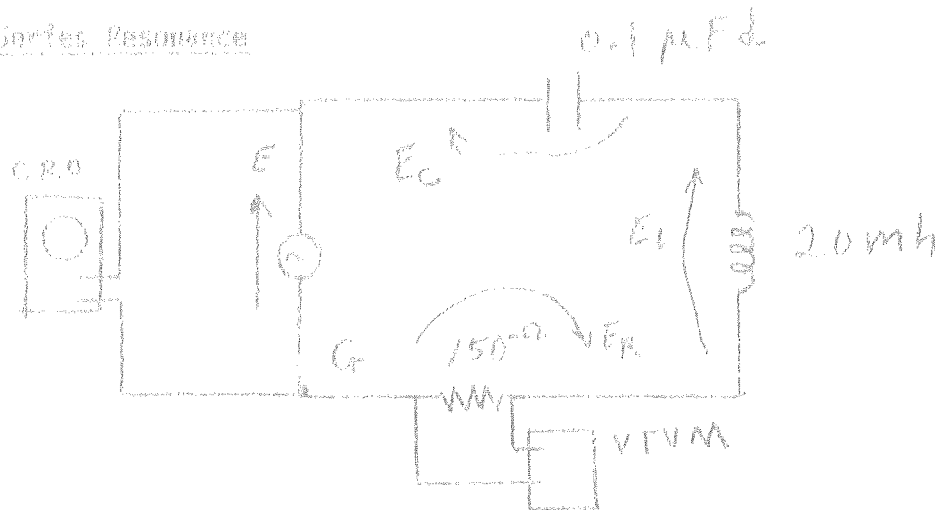

A) Connect the circuit shown. (Caution) Since the CRO and VTVM are each grounded through the a.c. line, be sure the ground terminal of each is connected to point G of the circuit. E is the audio oscillator with the amplitude dial set on about 1/5 maximum. Use the oscilloscope to measure E and the VTVM to measure E_R .

B) Vary the frequency until resonance occurs. (Maximum $E_R = E_{R0}$). At resonance record the frequency, E_R , and E . Keep E constant for parts B, C, D, and E. Measure the frequency using CRO.


C) Disconnect the CRO (both terminals), and measure E_L and E_C at resonance with VTVM.

D) Reconnect the meters as in part (A), and with f set at each half power point ($70\% E_{R0}$), record the reading of part (B).

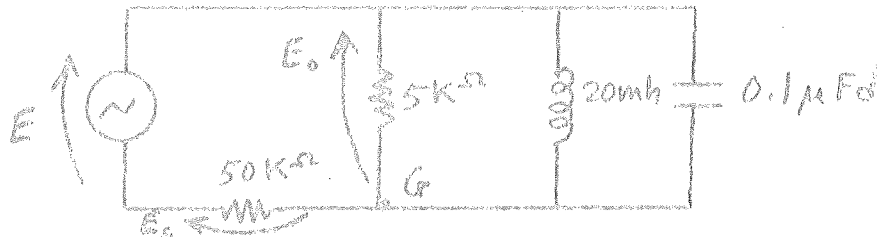E) Take additional data so you can plot a resonant curve (E_R vs f).

Parallel Resonance

An RLC parallel circuit supplied by a constant current source has a resonant effect because the voltage across it maximizes at a particular source frequency. Connect the circuit shown, simulating a constant current source by using a large (100 K Ω) resistor in series with the audio oscillator.



Set the amplitude of the oscillator dial to 0.9 maximum for this part of the experiment. Use the VTVM to measure E_s and the CRO to measure E_o . (Common ground at G).

A) Confirm that I_s remains constant over the frequency range of 2 to 5 KHz. Do this by measuring E_s ($I_s = E_s / 50 \text{ K}$) at several frequencies. While doing this, observe E_o with an oscilloscope and note the frequency where E_o maximizes.

B) Take data to plot a resonant curve (E_o vs f). Be sure to include the resonant point and the half power points.

Report


A) Record the type of VTVM used, the ranges of voltages it can read, and its input impedance (see instruction manual).

B) Record the type of oscilloscope used, the minimum and maximum voltage sensitivity, minimum and maximum sweep speed and input impedance (see Manual).

C) Include a sketch of the front of the oscilloscope in your report.

D) Plot the two resonant curves and calculate the band width and Q (ω_o / BW) in each case, from the curves. Check by calculating Q and bandwidth from circuit parameters.

Power Measurements

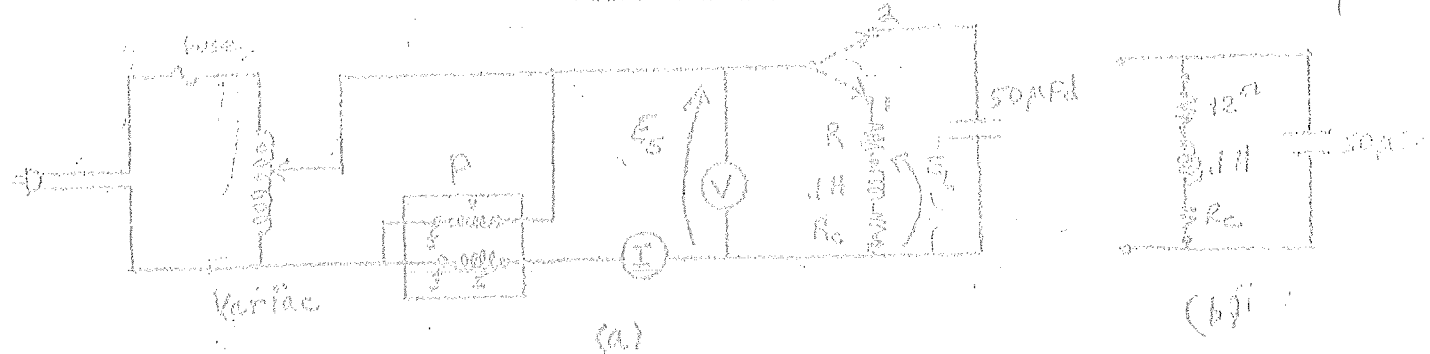


This experiment shows how to use a wattmeter, voltmeter and ammeter to determine real and apparent power and power factor. Learn how to connect a wattmeter into a circuit. Measure R_C using a bridge.

- Connect the circuit shown in Fig. (a), S in position 1, and $R = 0$. Gradually increase E_S to 72 V RMS. (Watch the meters as E_S rises. If any meter reads unusually high, recheck the circuit and correct any bad connections). Record meter readings of I , P and E_S .
- Increase R to 12 ohms. Gradually raise E_S until $E_L = 72$ volts. Record readings of E_L , E_S , P and I .
- With S in position 2, increase E_S to the same reading it showed in part b). Record readings of E_S , P and I .
- Connect the circuits of parts b) and c) in parallel (Fig. b) and increase E_S to the same value as in parts b) or c). Record readings of E_S , P and I .

Report

- Do the following calculations, for each part of the experiment:
 - Calculate the real power using $I^2 R$, and reactive power using $I^2 X$ (use the measured value for I).
 - Draw the power triangle to scale, using the calculations of part a). Determine the apparent power and the power factor using the triangle.
 - Find power factor using the measured values of E_S , I and P .
- How close does the real power, as calculated above compare with the wattmeter reading (calculate the % error);
- Calculate the error between apparent power as determined from the triangle, with apparent power calculated from the meter readings ($E_S I$).
- Calculate the error between the P.F. calculated from parts b) and c).

Power Measurements

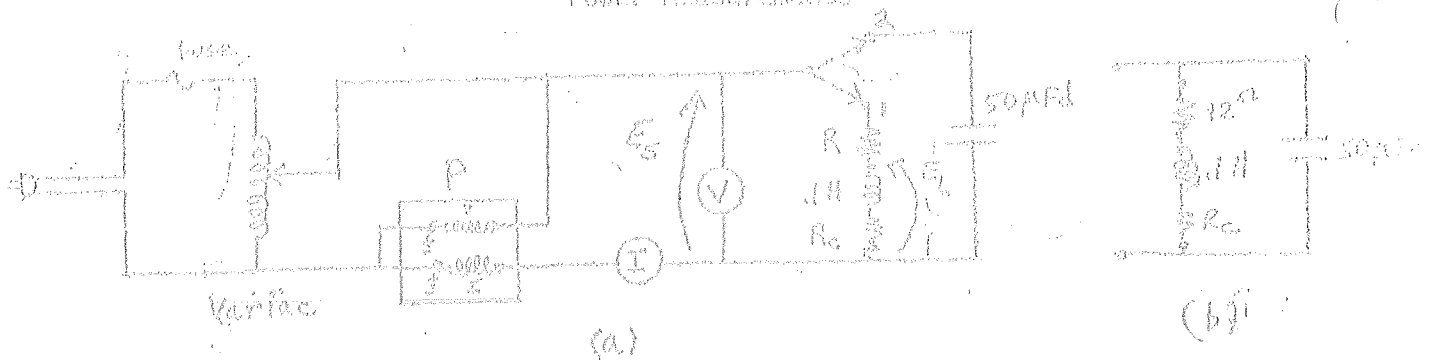

This experiment shows how to use a wattmeter, voltmeter and ammeter to determine real and apparent power and power factor. Learn how to connect a wattmeter into a circuit. Measure R_C using a bridge.

- a) Connect the circuit shown in Fig. (a), S in position 1, and $R = 0$. Gradually increase E_S to 72 V RMS. (Watch the meters as E_S rises. If any meter reads unusually high, recheck the circuit and correct any bad connections). Record meter readings of I, P and E_S .
- b) Increase R to 12 ohms. Gradually raise E_S until $E_L = 72$ volts. Record readings of E_L , E_S , P and I.
- c) With S in position 2, increase E_S to the same reading it showed in part b). Record readings of E_S , P and I.
- d) Connect the circuits of parts b) and c) in parallel (Fig. b) and increase E_S to the same value as in parts b) or c). Record readings of E_S , P and I.

Report


- 1.) Do the following calculations, for each part of the experiment:
 - a) Calculate the real power using I^2R , and reactive power using i^2X (use the measured value for I).
 - b) Draw the power triangle to scale, using the calculations of part a). Determine the apparent power and the power factor using the triangle.
 - c) Find power factor using the measured values of E_S , I and P.
- 2.) How close does the real power, as calculated above compare with the wattmeter reading (calculate the % error);
- 3.) Calculate the error between apparent power as determined from the triangle, with apparent power calculated from the meter readings ($E_S I$).
- 4.) Calculate the error between the P.F. calculated from parts b) and c).

marks

Experiment 25 Transformer, 3 phase

This experiment illustrates the current and voltage transformations according to the primary and secondary of a transformer. It also shows how the secondary voltage changes as the transformer is loaded. A current transformer is used to extend the current range of the meter. The wattmeter is also used to measure power into a load, when energized with a source providing an available (variable) voltage.

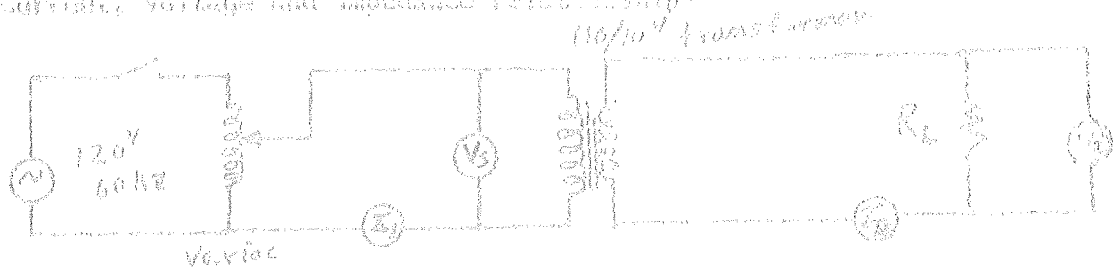A. Current, voltage and impedance relationships



Connect the circuit shown, and have the instructor check before energizing it.

- 1) With the secondary open circuited ($R_L = \text{infinity}$) gradually increase the variac, setting V_s to 105 volts. Watch the ammeters for any excess readings. Read V_{s1} and V_2 .
- 2) For each of the following values of R_L , read V_2 , I_1 and I_2 (setting $V_s = 105$ volts): $R_L = \infty, 8, 7, 6$ and 5 ohms.
- 3) Replace meter I_2 with a current transformer, connecting the meter to the secondary of the current transformer. Set the current transformer ratio to 10/5.

Repeat part (2) for values of $R_L = 5, 4, 3$ and 2 ohms.

- a) Calculate the open circuited voltage ratio and assume it is the turns ratio.
- b) Plot a curve of V_2 vs I_2 .
- c) From the meter readings, calculate the current ratio I_2/I_1 , and compare to the turns ratio. Use the values for $R_L = 2$ ohms only.
- d) Calculate the input impedance of the transformer using metered values V_s and I_1 ($R_L = 2$ ohms). Compare to the input impedance calculated using the turns ratio and $R_L = 2$ ohms.

Part B

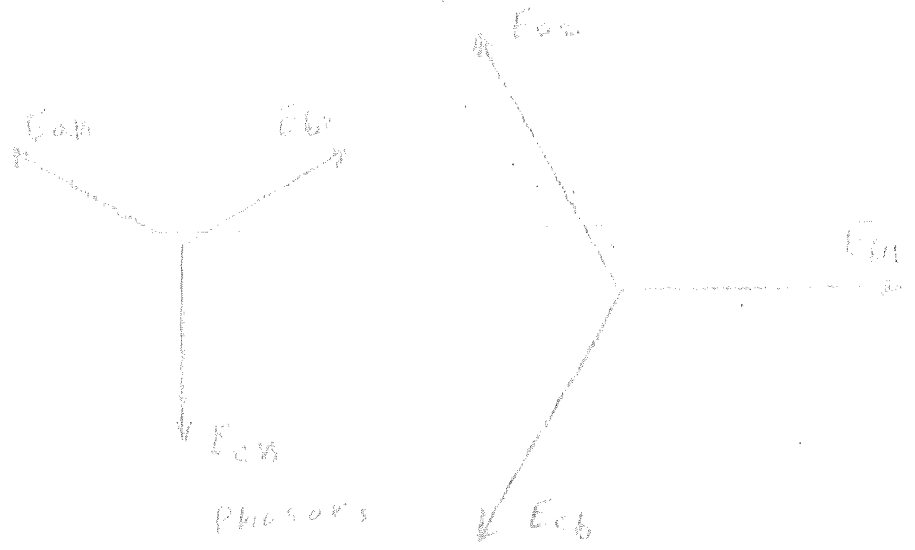
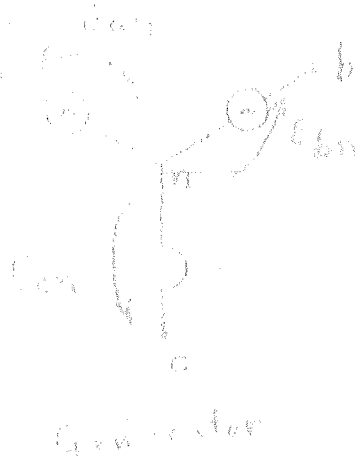


FIGURE 2

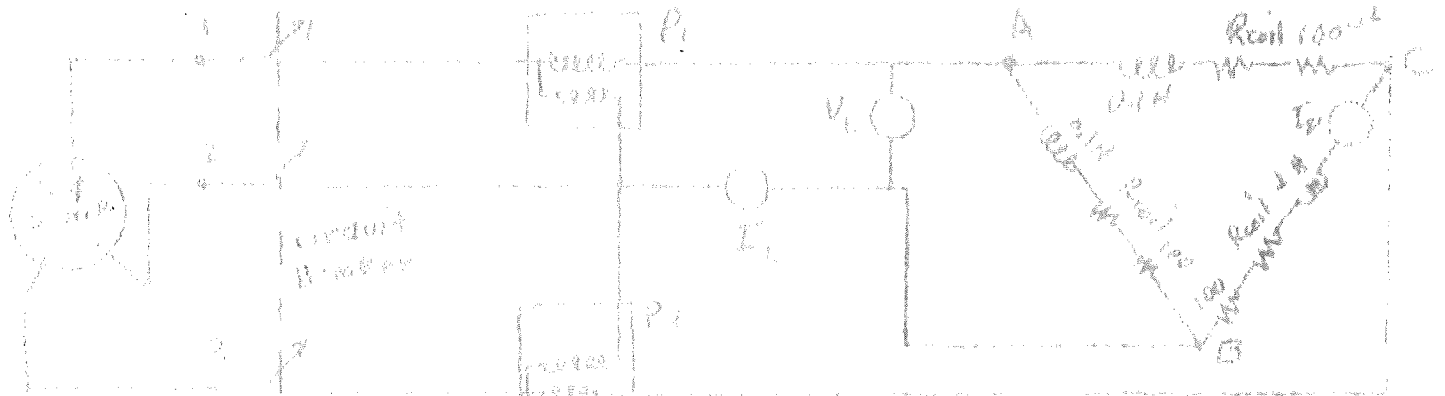


FIG. 2

Let us first consider the circuit, note the connections given in Fig. 2. The line-to-line voltage is $\sqrt{3}$ times the line-to-neutral voltage. The line current is $1/\sqrt{3}$ times the line-to-neutral current. The transformer is a three-phase transformer with a delta primary and a star secondary. The load is a three-phase load with a delta connection. The transformer is labeled 'Transformer' and the load is labeled 'Load'.

Part B

The line-to-line voltage is $\sqrt{3}$ times the line-to-neutral voltage. The line current is $1/\sqrt{3}$ times the line-to-neutral current. The transformer is a three-phase transformer with a delta primary and a star secondary. The load is a three-phase load with a delta connection. The transformer is labeled 'Transformer' and the load is labeled 'Load'.

TOPICS	CH	PAGES
Charge, current, voltage, power, energy	1 (2)	3-16 (10-14)
Circuit elements, stored energy, energy sources	1 (2)	16-24 (14-27)
Circuit laws, solution for currents	2 (7)	29-37 (27-36)
Solution for voltages	2 (7)	38-40 (36-38)
Passive network reduction, current and voltage	2 (6)	42-44 (210-211)
Active network reduction, superposition theorem Quiz #1	2 (1)	44-51 (211-217)
Exponential and sinusoidal waveforms, complex numbers ✓	3 (3)	51-75 (49-50) 77-79 (77-79)
Phasors, effective values, meters, Wattmeter ✓	3 (3, 7)	75-87 (60-68, 163-165) 579 (543), 606 (570)
Natural response, first order system ✓	4 (6)	87-93 (73-79)
→ Forced response for D.C. ✓	5 (5)	109-123 (109-111)
Forced response to sinusoids	5 (5)	126-129 (111-118)
Series and parallel circuits ✓	5 (6)	129-132 (118-123)
Power calculations ✓ ←	7 (7)	169-177 (167-175)
○ Frequency response and resonance ✓	7 (7)	177-191 (175-190)
Three phase circuits ✓ Quiz #2	7 (7)	192-201 (190-198)
One port networks, maximum power transfer ✓	8 (8)	209-215 (209-217, 231-224)
Transformer coupling ✓	8 (11)	216-229 (260-261)
Cathode Ray Tube and oscilloscope ✓	10 (9, 27)	236-267 (247-252, 267-268)
Diode characteristics ✓	10 (9) 11 (9)	271 (262-263, 299-303 (277-281))
Diode Models and application ✓	12 (10, 12)	311-319 (271-275, 391-395)
Bipolar Junction Transistor (BJT) curves & amplification	13 (9)	340-347 (289-293)

2012

Quiz #3
 QUIZ 40 ✓
 LAB 20
 FINAL 30
 HW 10

FUNDAMENTAL ELECTRIC QUANTITIES

[CHARGE, (COULOMB'S LAW), ^{CURRENT} VOLTAGE, POWER, ENERGY]

1. CHARGE: A FUNDAMENTAL ELECTROSTATIC UNIT. S.I. UNITS ARE "COULOMBS"

1 COULOMB \Rightarrow 6.24×10^{18} ELECTRONS

COULOMB'S LAW

$$q_1 \leftarrow r \rightarrow q_2$$

$$\vec{F} = \frac{q_1 q_2}{4\pi\epsilon r^2} \vec{a}_r$$

ϵ = PERMITTIVITY

ϵ_0 = " OF FREE SPACE = 8.854×10^{-12} FARAD/METE.

\vec{a}_r = UNIT VECTOR

FOR $q_1 > 0$ AND $q_2 > 0$, CHARGES REPEL

" $q_1 < 0$ " $q_2 < 0$, " "

" $q_1 > 0$ " $q_2 < 0$, " ATTRACT

" $q_1 < 0$ " $q_2 > 0$, " ATTRACT

2. CURRENT: RATE OF CHANGE OF CHARGE WITH RESPECT TO TIME:

$$i = \frac{dq}{dt} \quad (\text{AMPS} = \frac{\text{COULOMBS}}{\text{SEC}})$$

→ $q^+ > 0$ (HOLES, POSITRONS)

← $q^- < 0$ (ELECTRONS)

→ RESULTING CURRENT

$$i = \frac{dq^+}{dt} + \frac{dq^-}{dt}$$

3. ENERGY: THE ABILITY TO DO WORK
- MEASURED IN JOULES

4. VOLTAGE (POTENTIAL - EMF) THE ENERGY TRANSFER CAPABILITY OF A FLOW OF ELECTRIC CHARGE.

$$V = \frac{dw}{dq} \quad (\text{VOLTS} = \frac{\text{JOULES}}{\text{COULOMB}})$$

TO SPECIFY A VOLTAGE, WE NEED TO DESIGNATE TWO REFERENCE POINTS (AS IN A GRAVITATIONAL POTENTIAL)

5. POWER - THE RATE AT WHICH ENERGY IS TRANSFERRED:

$$P = \frac{dw}{dt} \quad (\text{WATTS} = \frac{\text{JOULES}}{\text{SEC}})$$

NOTE THAT


$$P = \frac{dw}{dt} = dq \frac{dw}{dq} \frac{dq}{dt} = V i$$

$$\text{THUS, } W = \text{TOTAL ENERGY} = \int P dt = \int V i dt$$

THE FUNDAMENTAL (PASSIVE) CIRCUIT ELEMENTS

1. RESISTANCE

a. CIRCUIT

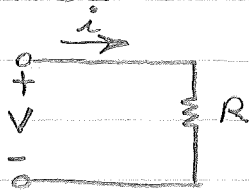

IDEAL RESISTOR

$$V = iR \quad (\text{OHM'S LAW})$$

R IS IN "OHMS"

$$G = \frac{1}{R} = \text{"CONDUCTANCE"} \quad \text{IN "MHOS" OR "SIEMENS"}$$

b. AN EXAMPLE OF A PHYSICAL RESISTOR

ρ = RESISTIVITY (PROPERTY OF MATERIAL)

IN OHM-METERS

CONSIDER A TUBE:



ρ = UNIFORM RESISTIVITY


A = CROSS SECTION OF TUBE

l = LENGTH OF TUBE


THEN $R = \rho l / A$ (INTUITIVE)

(WE ARE ASSUMING UNIFORM CURRENT DENSITY)

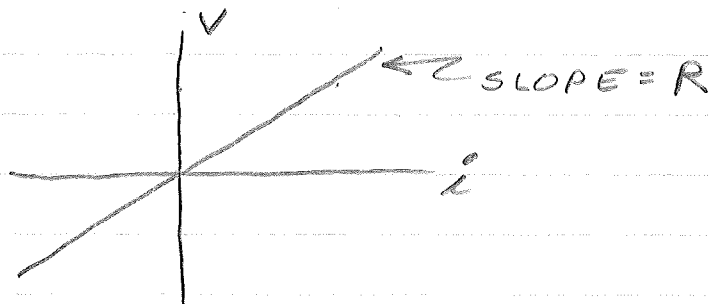c. NOTE THAT WE CAN EXPRESS A RESISTOR ON A $V-i$ CURVE



2. CAPACITANCE (CONDENSOR)

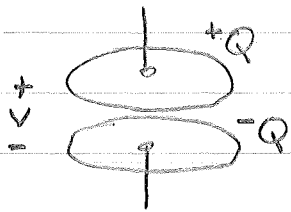

THE CHARGE OF THE CAPACITOR IS PROP. TO VOLTAGE:

$$q = CV$$

C = CAPACITANCE (IN FARADS)

DIFFERENTIATING:

$$\frac{dq}{dt} = \frac{d}{dt}(CV) = C \frac{dV}{dt}$$

OR


$$i = C \frac{dV}{dt}$$

NOTE THAT

$$V = \frac{1}{C} \int_{-\infty}^t i dt$$


THUS, PAST CURRENT HISTORY IS STORED. THE CAPACITOR STORES ENERGY IN AN ELECTRIC FIELD.

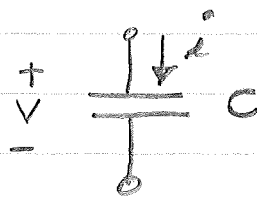THE CAPACITOR IS SYMBOLIZED BY THE FIGURE



SCHEMATIC

3. INDUCTANCE (COIL, CHOKE)

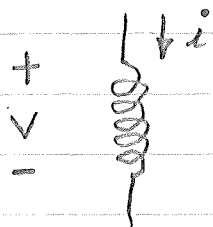


THE VOLTAGE IS PROP.
TO RATE OF CHANGE
OF CURRENT

$$V = L \frac{di}{dt}$$

L = INDUCTANCE (IN HENRYS)


INDUCTORS STORE ENERGY IN
A MAGNETIC FIELD.

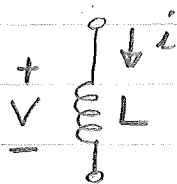THE INDUCTOR IS SYMBOLIZED
BY THE FIGURE:




SUMMARY OF THE THREE BASIC (PASSIVE) CIRCUIT ELEMENTS


RESISTOR

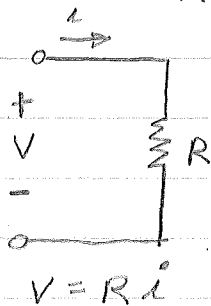

INDUCTOR

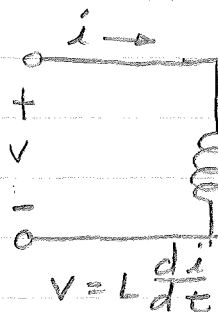

CAPACITOR

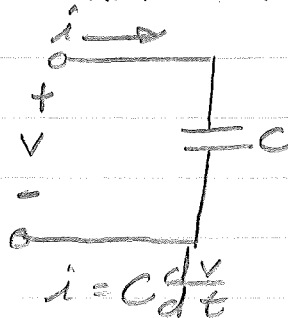

amw

ENERGY STORAGE AND DISSIPATION IN THE LINEAR PASSIVE ELEMENTS

(1) LINEARITY, FOR R, L, $\frac{1}{s}C$, WE HAVE $v = f(i)$

BY LINEARITY, WE MEAN

$$f(ai_1 + bi_2) = af(i_1) + bf(i_2)$$

$\exists a \neq b$ ARE CONSTANT. SIMILARLY

$$i = g(v) (= f^{-1}(v))$$

THE R, L, $\frac{1}{s}C$ ARE ALSO LINEAR IN THE SENSE THAT

$$g(av_1 + bv_2) = ag(v_1) + bg(v_2)$$

(2) ENERGY CONSIDERATIONS

RECALL THAT WE SHOWED

$$W = \text{ENERGY} = \int v i dt$$

(a) FOR AN INDUCTOR : $v = L \frac{di}{dt}$

$$\Rightarrow W_L = \int L \frac{di}{dt} i dt = \int L i di$$

LET'S LOOK AT THE ENERGY OVER A TIME INTERVAL $0 < t < T$ AND

ASSUME $i(t=0) = 0$ AND $i(t=T) = I$

$$\text{THEN } W_L = \int_0^T L i \frac{di}{dt} dt = \int_0^I L i di = \frac{1}{2} LI^2$$

\Rightarrow INDUCTANCE IS A MEASURE OF THE ABILITY OF A DEVICE TO STORE ENERGY IN THE FORM OF A MAGNETIC FIELD.

(b) FOR A CAPACITOR ; $i = C \frac{dv}{dt}$

LET'S LOOK AT THE ENERGY OVER
A TIME INTERVAL $0 < t < T$

AND ASSUME $V(0) = 0$ AND $V(T) = V$

$$\text{THEN } W_L = \int_0^T V C \frac{dv}{dt} dt = \int_0^V C V dV = \frac{1}{2} C V^2$$

\Rightarrow CAPACITANCE IS A MEASURE
OF THE ABILITY OF A DEVICE
TO STORE ENERGY IN AN
ELECTRIC FIELD.

(c) FOR A RESISTOR ; $V = R i$

LET'S LOOK AT THE ENERGY OVER
A TIME INTERVAL $0 < t < T$ AND

ASSUME A CONSTANT CURRENT

$$i(t) = I \text{ FOR } 0 < t < T$$

$$\text{THEN } W_L = \int_0^T R i^2(t) dt \\ = R I^2 T =$$

\Rightarrow RESISTANCE IS A MEASURE OF
THE ABILITY OF A DEVICE
TO DISSIPATE ENERGY (IRREVERSIBLY
AS HEAT)

THE POWER OF A RESISTOR HAS
BEEN SHOWN TO BE

$$p = v i$$

USING OHM'S LAW : $V = R i$

WE MAY WRITE THIS AS

$$p = i^2 R$$

$$p = V^2 / R$$

ENERGY CONTINUITY

ENERGY CANNOT BE CHANGED INSTANTLY

(FOR EXAMPLE, CONSIDER THE INERTIA OF A MASS)

1. FOR A CAPACITOR:

$$W_C = \frac{1}{2} C V^2$$

SINCE W_C CANNOT CHANGE INSTANTLY, AND

C IS FIXED $\Rightarrow V$ CANNOT CHANGE

INSTANTANEOUSLY ACROSS A CAPACITOR.

2. FOR AN INDUCTOR

$$W_L = \frac{1}{2} L I^2$$

$\Rightarrow I$ CANNOT CHANGE INSTANTLY ACROSS
AN INDUCTOR.

3. FOR A RESISTOR

$$W_R = I R^2 T = (IR) I T = V I T$$

VOLTAGE (CURRENT) CAN CHANGE
INSTANTLY ACROSS (THRU) A RESISTOR.

IT IS ACCOMPANIED, HOWEVER, BY
AN INVERSE CHANGE IN CURRENT

(VOLTAGE) IN SUCH A MANNER TO
ALLOW NO INSTANTANEOUS CHANGE
IN ENERGY.

SINCE THE RESISTOR CANNOT
STORE ENERGY, THERE IS

NO LIMITATION ON THE
RAPIDITY WITH WHICH V $\frac{1}{I}$


I CHANGES CAN OCCUR.

ENERGY (VOLTAGE & CURRENT) SOURCES

$R, L, \frac{1}{C}$ ARE "PASSIVE"


VOLTAGE & CURRENT SOURCES ARE "ACTIVE"

1. CURRENT SOURCE (GENERATOR)

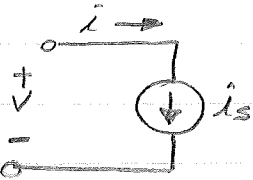


$$i = i_s \quad \forall v$$


$v-i$ CURVE \Rightarrow

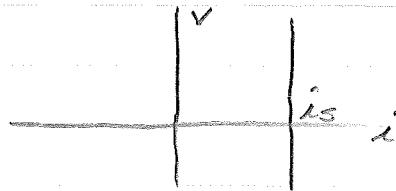

FOR $i_s = 0$, WE HAVE AN "OPEN CIRCUIT"

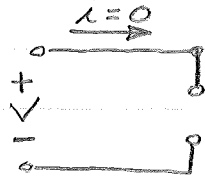


2. VOLTAGE SOURCE (GENERATOR)

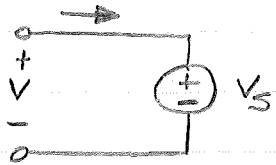


$$v = v_s \quad \forall i$$

$v-i$ CURVE \Rightarrow

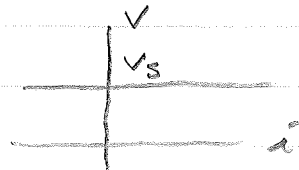

FOR $v_s = 0$, WE HAVE A "SHORT CIRCUIT"

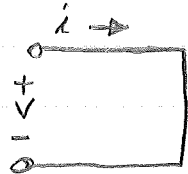

$$v = 0 \quad \forall i$$

THESE MODELS ARE "IDEAL"

NOTE ON SCHEMATIC REPRESENTATION

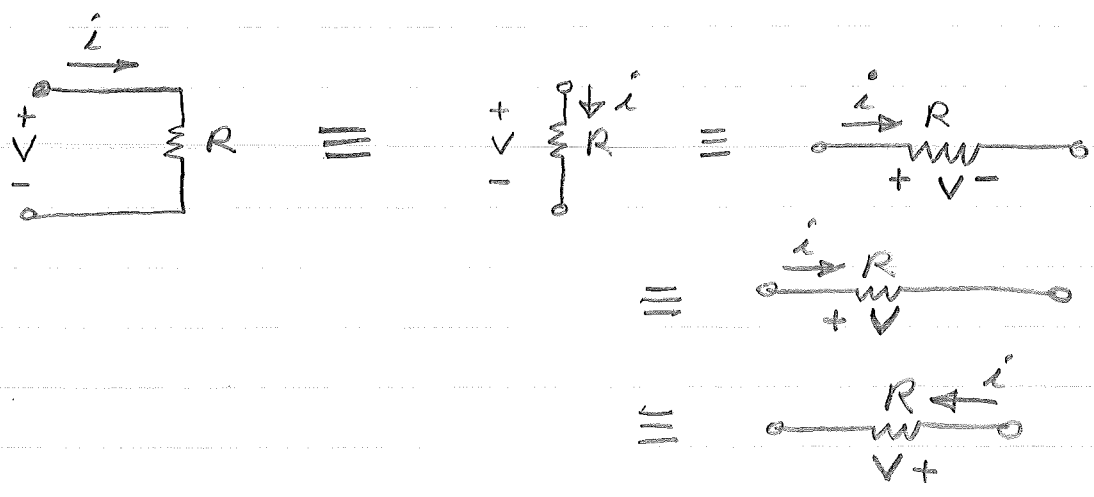



TABLE 1-4 IN TEXT GIVES GOOD SUMMARY OF ACTIVE & PASSIVE CIRCUIT ELEMENTS
($R, G, I, C, SC, OS, V_{SOURCE}, I_{SOURCE}$)
(MEMORIZATION ADVISED)


SOME CIRCUIT ANALYSIS NOMENCLATURE

1. LUMPED CIRCUIT ELEMENT - A REGION IN SPACE IN WHICH AT LEAST TWO POINTS ARE DEFINED: "SCHEMATIC \Rightarrow "  "

EX: L, R, C, V_s , I_s


2. LUMPED CIRCUIT: A COLLECTION OF LUMPED CIRCUIT ELEMENTS WHOSE METHOD OF CONNECTION IS SPECIFIED

EX:

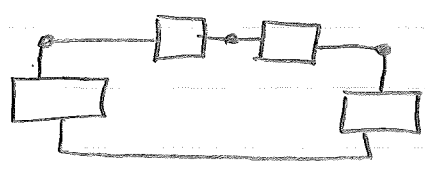


3. NODE: A POINT AT WHICH TWO OR MORE CIRCUIT ELEMENTS HAVE A COMMON CONNECTION


EX:

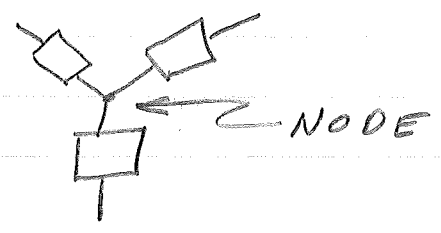


EX.

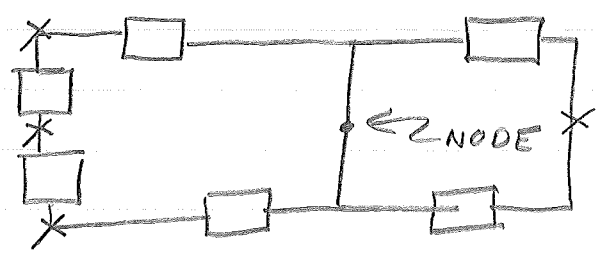

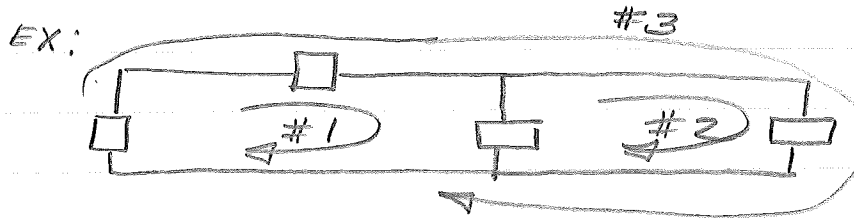4. LOOP: ANY SEQUENCE OF CIRCUIT ELEMENTS FORMING A CLOSED PATH WHICH DOES NOT PASS THRU A NODE MORE THAN ONCE.



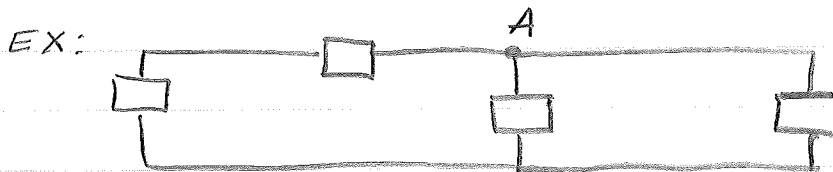BRANCH: A PART OF A NETWORK EXTENDING FROM ONE NODE TO ANOTHER.





NODE A HAS 3 CORRESPONDING BRANCHES



5. MESH: ANY LOOP CONTAINS NO CIRCUIT ELEMENT IN ITS INTERIOR. ALL MESHES ARE LOOPS. ALL LOOPS ARE NOT MESHES (#1 & #2 ABOVE, ARE MESHES. LOOP #3 IS NOT)

KIRCHHOFF'S LAWS

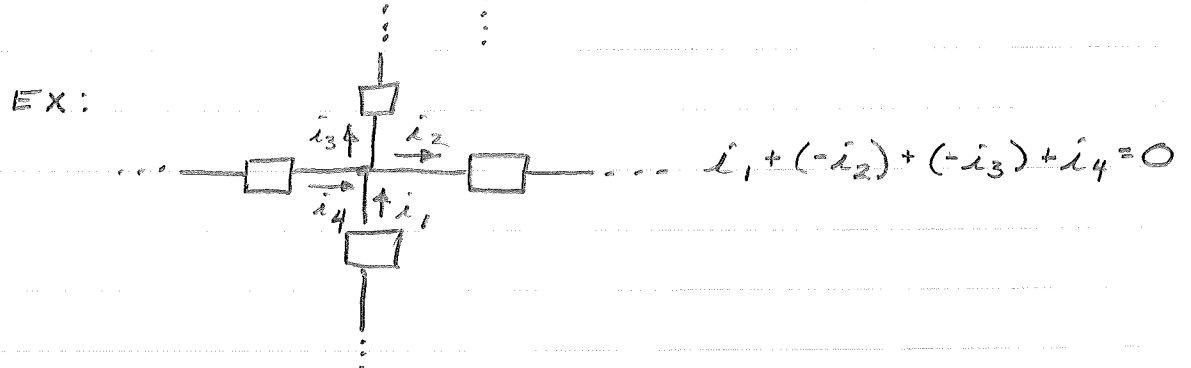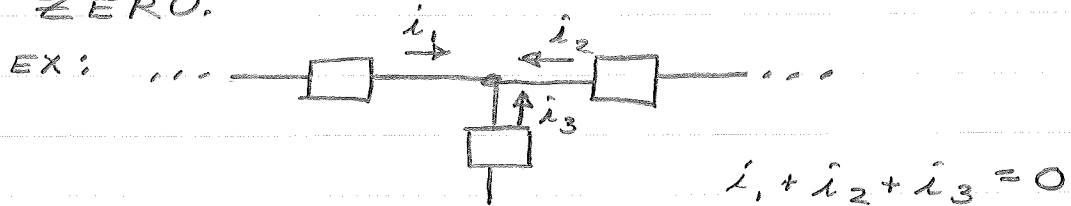1. KIRCHHOFF'S CURRENT LAW: THE ALGEBRAIC SUM OF THE CURRENTS INTO A NODE AT ANY INSTANT IS ZERO.



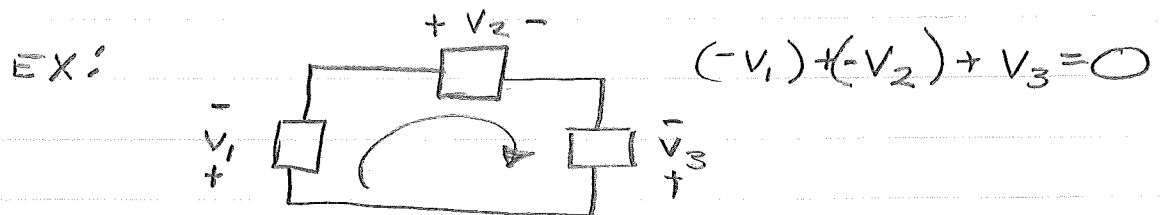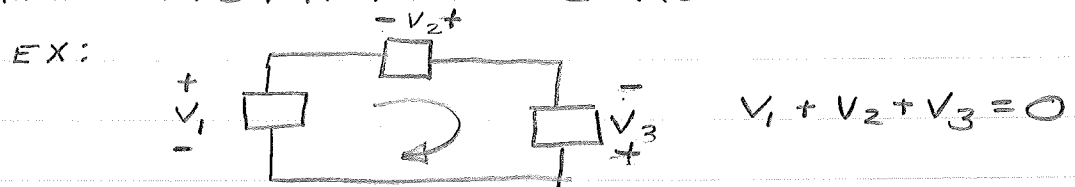2. KIRCHHOFF'S VOLTAGE LAW: THE ALGEBRAIC SUM OF THE VOLTAGES AROUND A LOOP AT ANY INSTANT IS ZERO




APPLICATION OF KIRCHHOFF'S LAWS

1. LOOP CURRENT METHOD (USING KIRCHHOFF'S VOLTAGE LAW)

STEPS:

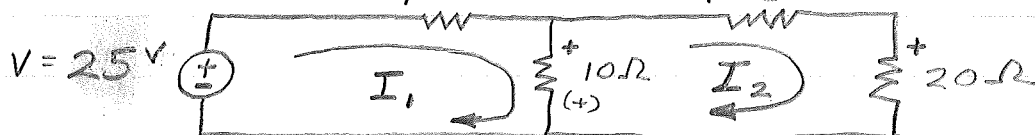1. DRAW "LOOP CURRENTS" IN THE CIRCUIT (USING "MESH"

CURRENTS ASSURES NO REDUNDANCY) FOR CONSISTANCY, USE SAME CURRENT SENSE (CW)



2. FOR EACH LOOP, SUM THE VOLTAGES

AND SET TO ZERO

(a) IF A ^{LOOP} CURRENT ENTERS A POSITIVE TERMINAL, THE VOLTAGE IS DESIGNATED AS POS

(b) IF A ^{LOOP} CURRENT ENTERS A PASSIVE ELEMENT, DENOTE THE

POINT OF ENTRY AS A POSITIVE V

3. USE OHM'S LAW: $V = IR$

FOR I_1

$$-25 + 5I_1 + 10I_1 - 10I_2 = 0$$

$$\text{OR } 15I_1 - 10I_2 = 25$$

FOR I_2

$$15I_2 + 20I_2 + 10I_2 - 10I_1 = 0$$

$$\text{OR } -10I_1 + 45I_2 = 0$$

IN SUMMARY

$$15I_1 - 10I_2 = 25$$

$$-10I_1 + 45I_2 = 0$$


TWO EQUATIONS / TWO UNKNOWNNS

SOLVING GIVES

$$I_1 = \frac{45}{23} \text{ AMPS}$$


$$I_2 = \frac{10}{23} \text{ AMPS}$$

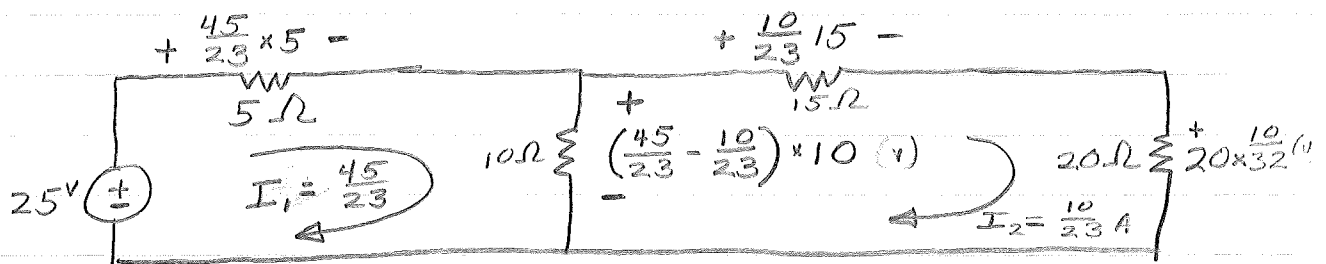WE CAN NOW ASSIGN VOLTAGES TO ALL THE CIRCUIT'S RESISTORS.



NOTE THAT THE 10Ω RES. IS SHARED BY BOTH I_1 & I_2 . IT IS THE "MUTUAL RESISTANCE" BETWEEN THE TWO LOOPS. LOOP 1 HAS 5Ω OF "SELF-RESISTANCE". LOOP 2 HAS $15\Omega + 20\Omega = 35\Omega$ OF "SELF-RESISTANCE"

EXAMPLE (SKIP)

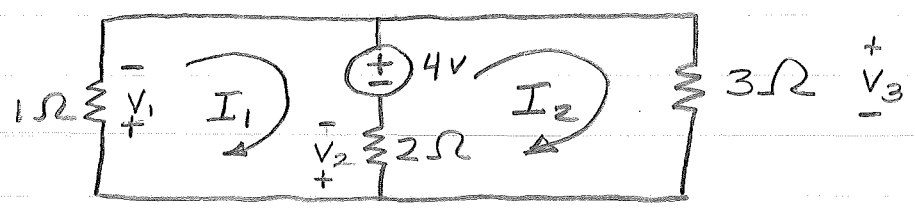

$$1 I_1 + 4 + 2 I_1 - 2 I_2 = 0$$

$$\text{OR } 3 I_1 - 2 I_2 = -4$$

$$3 I_2 + 2 I_2 - 2 I_1 - 4 = 0$$

$$\text{OR } -2 I_1 + 5 I_2 = 4$$

$$\text{SOLVING: } I_2 = \frac{4}{11} \quad I_1 = -\frac{12}{11}$$


$$V_1 = (1 \Omega) \left(-\frac{12}{11} \text{ A} \right) = -\frac{12}{11} \text{ VOLTS}$$

$$V_2 = (2 \Omega) \left(\frac{4}{11} - \left(-\frac{12}{11} \right) \right) \text{ AMPS}$$

$$= \frac{32}{11} \text{ V}$$

$$V_3 = (3 \Omega) \left(\frac{4}{11} \text{ A} \right) = \frac{12}{11} \text{ V}$$

EXAMPLE

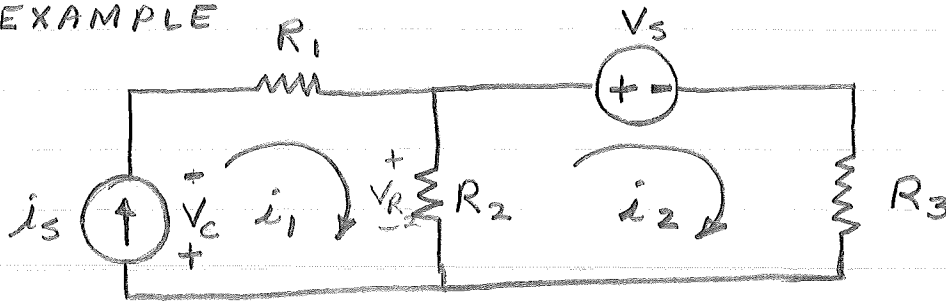

$$i_1 = i_s$$

$$\begin{cases} V_c + (R_1 + R_2)i_1 - R_2 i_2 = 0 \\ V_s + (R_2 + R_3)i_2 - R_2 i_1 = 0 \end{cases}$$

OR

$$\begin{cases} V_c + (R_1 + R_2)i_s - R_2 i_2 = 0 \\ V_s + (R_2 + R_3)i_2 - R_2 i_s = 0 \end{cases}$$

TWO EQUATIONS - TWO UNKNOWNNS

$$i_2 = \frac{R_2 i_s - V_s}{R_2 + R_3}$$

$$\begin{aligned} V_c &= R_2 i_2 - (R_1 + R_2) i_s \\ &= R_2 \left[\frac{R_2 i_s - V_s}{R_2 + R_3} \right] - (R_1 + R_2) i_s \end{aligned}$$


$$V_{R_1} = R_1 i_1 = R_1 i_s$$

$$\begin{aligned} V_{R_2} &= R_2 (i_1 - i_2) = R_2 \left[i_s - \frac{R_2 i_s}{R_2 + R_3} + \frac{V_s}{R_2 + R_3} \right] \\ &= R_2 \left[\left(1 - \frac{R_2}{R_2 + R_3} \right) i_s + \frac{V_s}{R_2 + R_3} \right] \end{aligned}$$

2. NODE-VOLTAGE METHOD (USING KIRCHHOFF'S CURRENT LAW)

STEPS

1. SPECIFY A VOLTAGE AT EVERY NODE

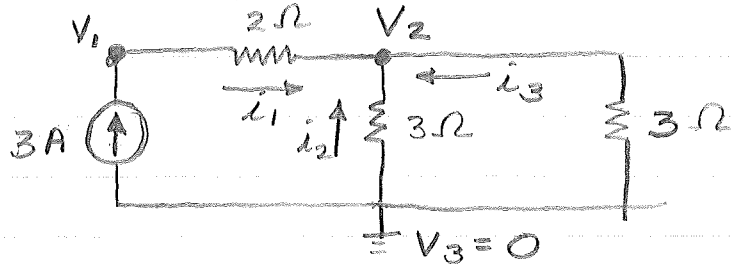

SET ONE OF THE NODES TO ZERO VOLTS
DEFINE A CURRENT THRU ANY V SOURCE.

2. FOR EACH NODE, SUM THE INCOMING CURRENT AND SET TO ZERO. THE CURRENT OF A BRANCH IS THE DIFFERENCE IN POTENTIAL \div RESISTANCE

$$V = iR \Rightarrow i = V/R$$

FOR NODE 2 :

$$\begin{aligned} i_1 + i_2 + i_3 &= \frac{V_1 - V_2}{2} + \frac{V_3 - V_2}{3} + \frac{V_3 - V_2}{3} \\ &= \frac{V_1 - V_2}{2} - \frac{2}{3} V_2 = -\frac{7}{6} V_2 + \frac{V_1}{2} \end{aligned}$$

FOR NODE 1 :

$$3A - i_1 = 3A - \frac{V_1 - V_2}{2} = 0$$


WE THUS HAVE EQUATIONS

$$-\frac{7}{6} V_2 + \frac{V_1}{2} = 0 \quad \Bigg| \quad 3 - \frac{V_1}{2} + \frac{V_2}{2} = 0$$

$$V_1 = 9/2 \text{ VOLTS} \quad V_2 = 27/14 \text{ VOLTS}$$

NOTE: WE CAN SOLVE FOR ALL CURRENTS

EXAMPLE:

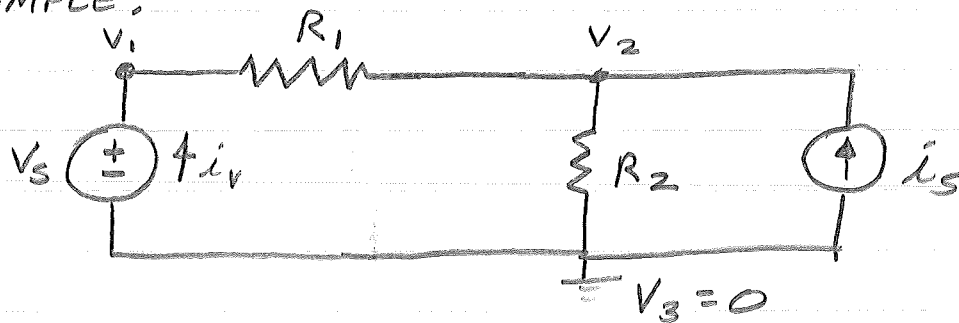

AT NODE 1:

$$i_V + \frac{V_2 - V_1}{R_1} = 0$$

$$\text{BUT } V_S = V_1 - V_3 = V_1$$

$$\Rightarrow i_V + \frac{V_2 - V_S}{R_1} = 0$$

$$i_V R_1 + V_2 - V_S = 0 \quad (1)$$

AT NODE 2:


$$\frac{V_1 - V_2}{R_1} + \frac{V_3 - V_2}{R_2} + i_S = 0$$

$$\frac{V_S}{R_1} - \left(\frac{1}{R_1} + \frac{1}{R_2}\right)V_2 + i_S = 0 \quad (2)$$

TWO EQUATIONS, TWO UNKNOWNS

SOLVE FOR V_S AND i_V

EXAMPLE:

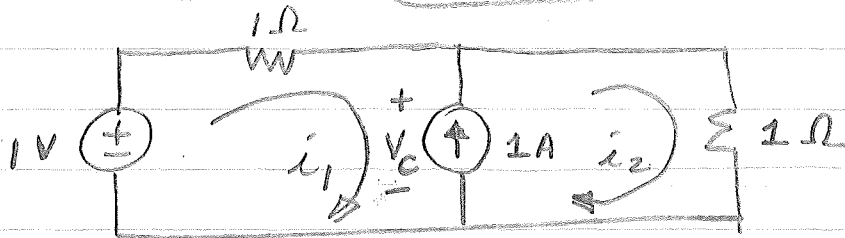USING LOOPS

$$\begin{cases} -1 + i_1 + V_c = 0 & \textcircled{1} \\ -V_c + i_2 = 0 & \textcircled{2} \\ i_2 - i_1 = 1 & \textcircled{3} \end{cases}$$

UNKNOWN S: i_1, V_c, i_2

FROM $\textcircled{2}$ $V_c = i_2$

FROM $\textcircled{3}$ $i_2 = 1 + i_1$

$$\Rightarrow V_c = 1 + i_1$$


SUBSTITUTING INTO $\textcircled{1}$

$$-1 + i_1 + (1 + i_1) = 0$$

$$2i_1 = 0 \Rightarrow i_1 = 0$$

FROM $\textcircled{3}$ $\Rightarrow i_2 = 1 \text{ AMP}$

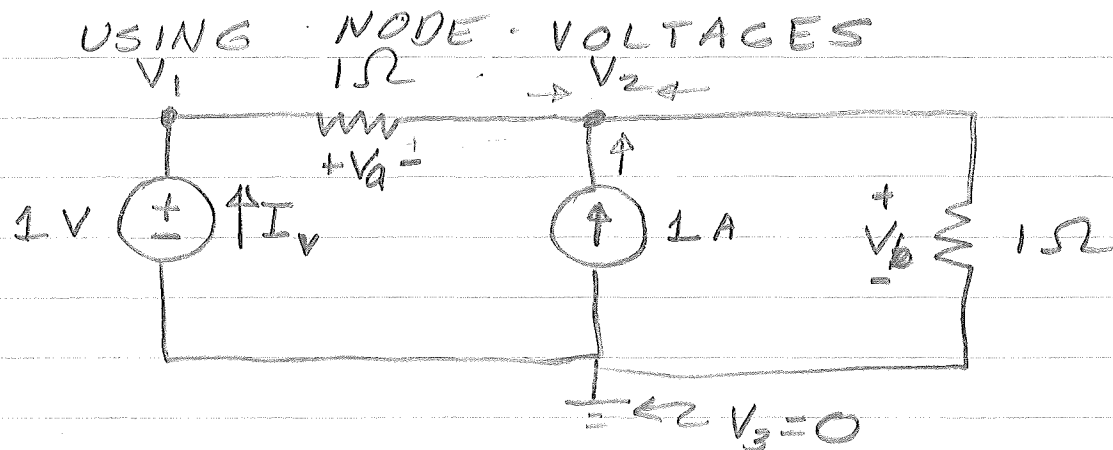FROM $\textcircled{1}$ $V_c = 1 \text{ V}$



$$I_V + \frac{V_2 - V_1}{1} = 0 \Rightarrow I_V + V_2 - V_1 = 0 \quad (1)$$

$$1 + \frac{V_1 - V_2}{1} + \frac{0 - V_2}{1} = 0 \Rightarrow 1 + V_1 - 2V_2 = 0 \quad (2)$$

$$V_1 = 1 \quad (3)$$

(3) INTO (2)

$$1 + 1 - 2V_2 = 0 \Rightarrow V_2 = 1$$

THIS AND (3) INTO (1)

$$I_V + 1 - 1 = 0 \Rightarrow I_V = 0$$

$$V_a = I_V (1\Omega) = 0$$

$$V_b = \frac{V_2 - V_3}{1\Omega} (1\Omega) = +1V$$

ENERGY STORAGE ELEMENTS IN KIRCHHOFF'S LAWS

(SOLUTIONS RATHER DIFFICULT)


1. LOOP CURRENTS (USE VOLTAGE RELATION)

a. $R \Rightarrow V_R(t) = R i(t)$

b. $L \Rightarrow V_L(t) = L \frac{d}{dt} i_L(t)$

c. $C \Rightarrow$ RECALL $i_C(t) = C \frac{dV_C(t)}{dt}$
 $\Rightarrow V_C(t) = V_0 + \frac{1}{C} \int_0^t i_C(t) dt$

EXAMPLE:

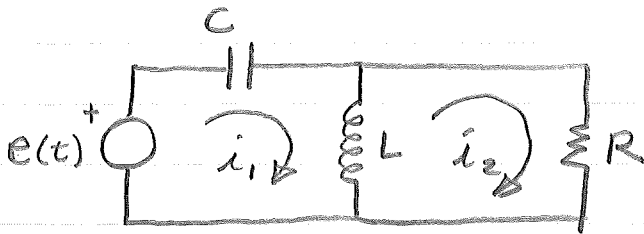

$$-e(t) + \left[V_0 + \frac{1}{C} \int_0^t i_1(t) dt \right] + L \frac{d}{dt} (i_1 - i_2) = 0$$

$$L \frac{d}{dt} (i_2 - i_1) + R i_2 = 0$$


2. NODE VOLTAGE (USE CURRENT RELATION)

(a) $R = 1/G \Rightarrow i_R(t) = G V_R(t)$

(b) $C \Rightarrow i_C(t) = C \frac{dV_C(t)}{dt}$

(c) L RECALL: $V_L(t) = L \frac{di_L(t)}{dt}$
 $\Rightarrow i_L(t) = I_0 + \frac{1}{L} \int_0^t V_L(t) dt$

EXAMPLE:

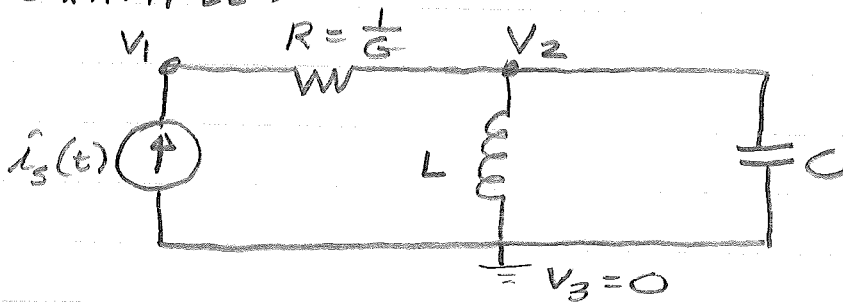


$$i_s(t) + G(V_2 - V_1) = 0$$

$$G(V_1 - V_2) + \left[I_0 + \frac{1}{L} \int_0^t (0 - V_2) dt \right] + C \frac{d(0 - V_2)}{dt} = 0$$

PASSIVE NETWORK REDUCTION


(1) PRELIMINARIES

(a) V-i CHARACTERISTICS

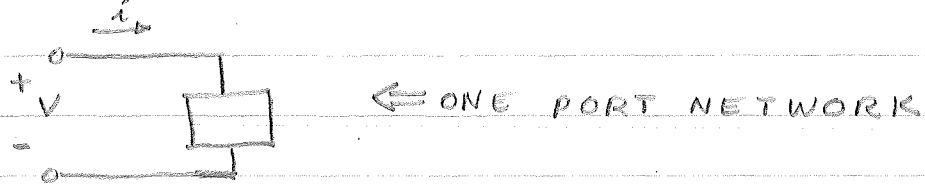


A LUMPED ELEMENT IS COMPLETELY DETERMINED BY IT'S V-i RELATION


EX: $R \Rightarrow V = iR$

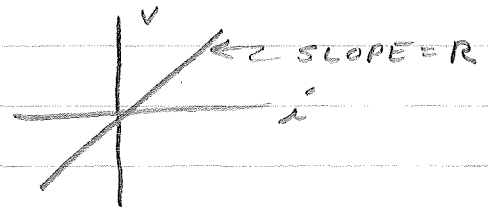

$L \Rightarrow V = L \frac{di}{dt}$

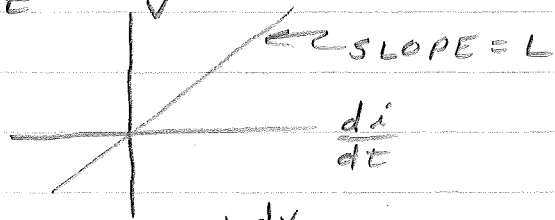


$C \Rightarrow i = C \frac{dv}{dt}$

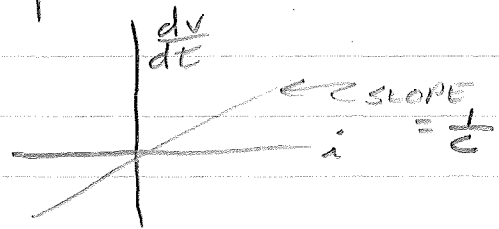

TWO ONE-PORTS ARE EQUIVALENT IF THEY HAVE SAME V-i RELATION

(b) CONNECTION DEFINITIONS

(i) PARALLEL:

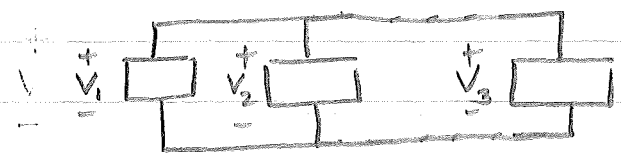

TWO OR MORE CIRCUIT ELEMENTS ARE CONNECTED IN PARALLEL IF IDENTICAL (NOT JUST EQUAL) VOLTAGES APPEAR ACROSS EACH ONE:

$$V_1 = V_2 = V_3$$

(ii) SERIES



TWO OR MORE CIRCUIT ELEMENTS ARE CONNECTED IN SERIES IF IDENTICAL (NOT JUST EQUAL) CURRENT FLOWS THRU EACH ONE:

$$i_1 = i_2$$

(2) PASSIVE ELEMENT CONNECTIONS

(a) RESISTOR

(i) PARALLEL




$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \quad (\text{OR } G_{eq} = G_1 + G_2)$$

(ii) SERIES




$$R_{eq} = R_1 + R_2$$

EXAMPLE:

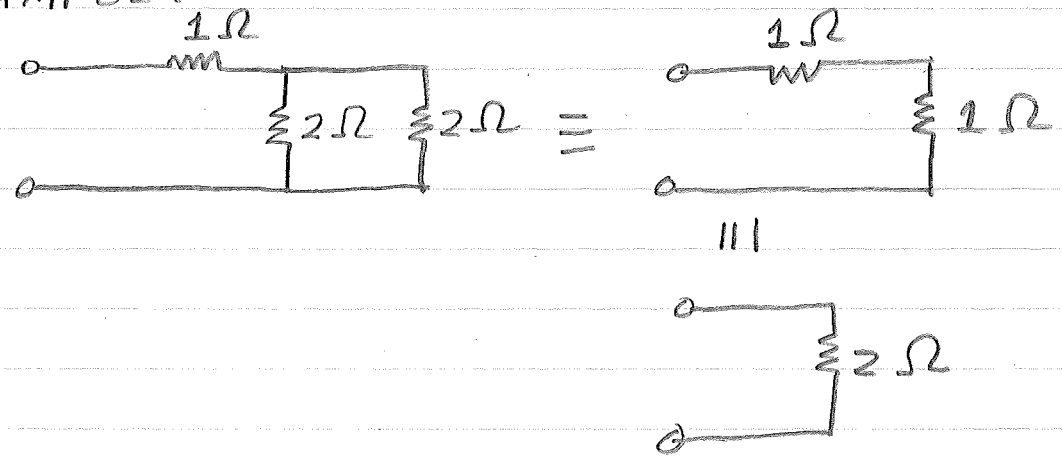



PROOF:

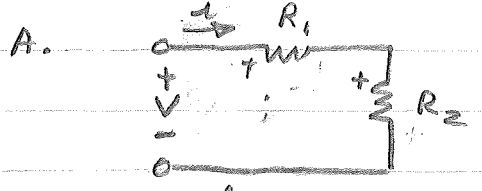

$$-V + R_1 i + R_2 i = 0$$

$$V = (R_1 + R_2) i$$

$$= R_{eq} i$$

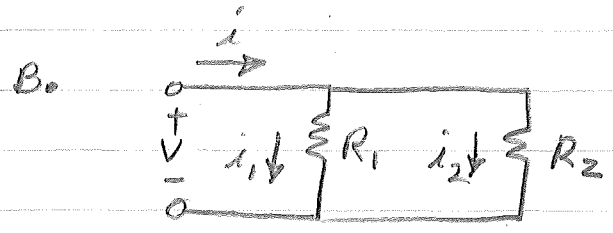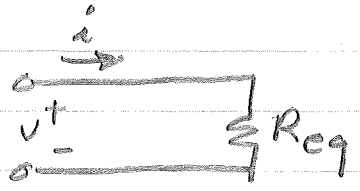

$$i_1 = \frac{V}{R_1}, \quad i_2 = \frac{V}{R_2}$$

$$i - i_1 - i_2 = 0$$


OR

$$i = \left(\frac{1}{R_1} + \frac{1}{R_2} \right) V$$

$$V = \left[\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \right] i$$


$$= R_{eq} i$$
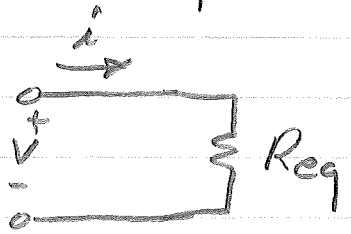
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$



(b) INDUCTOR

(i) PARALLEL

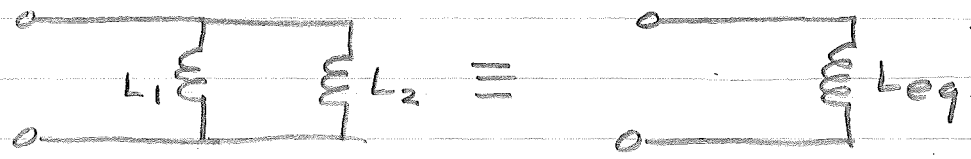


$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

(ii) SERIES




$$L_{eq} = L_1 + L_2$$

(EX)

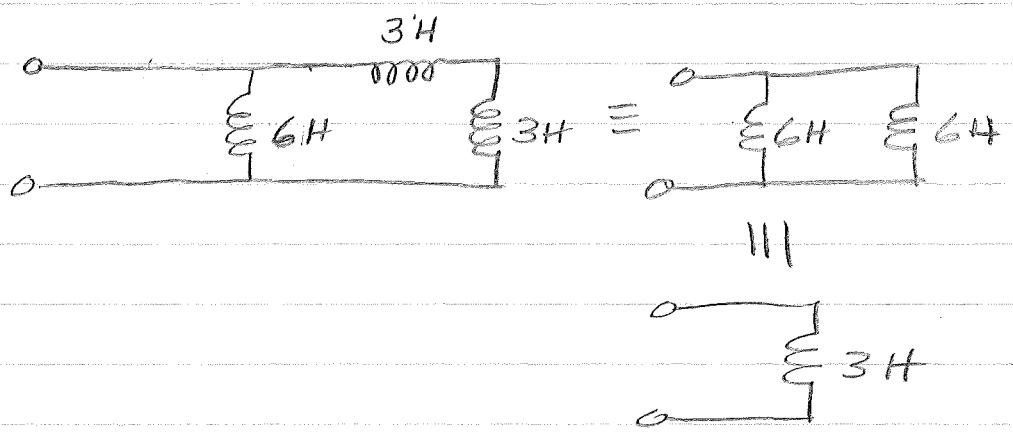

(C) CAPACITOR

(i) PARALLEL

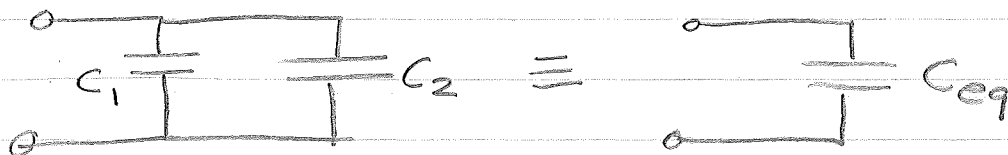


$$C_{eq} = C_1 + C_2$$

(ii) SERIES




$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

EXAMPLE

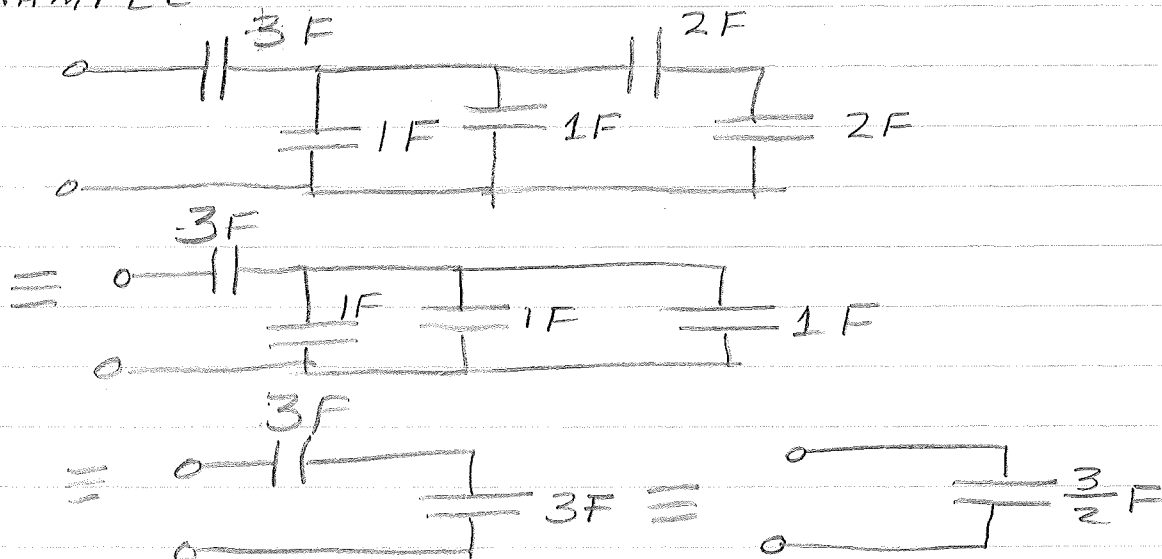

CURRENT AND VOLTAGE DIVIDERS

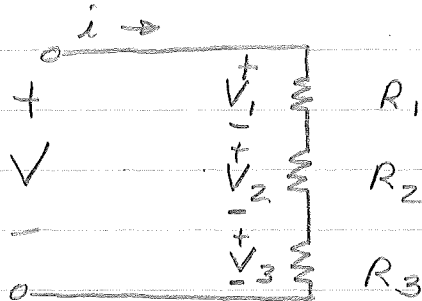1. VOLTAGE DIVIDER - TWO OR MORE RESISTORS IN SERIES DIVIDES THE APPLIED VOLTAGE PROPORTIONALLY



FROM KVL: $V = V_1 + V_2 + V_3$
 $V = (R_1 + R_2 + R_3) i$


$$i = \frac{V}{R_1 + R_2 + R_3}$$

$$V_1 = i R_1 = \frac{R_1}{R_1 + R_2 + R_3} V$$

$$V_2 = i R_2 = \frac{R_2}{R_1 + R_2 + R_3} V$$

$$V_3 = i R_3 = \frac{R_3}{R_1 + R_2 + R_3} V$$

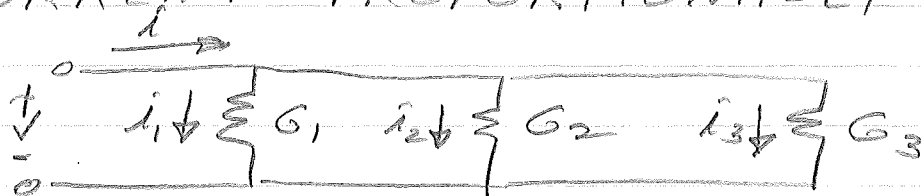2. CURRENT DIVIDER - TWO OR MORE CONDUCTANCES IN PARALLEL DIVIDES THE APPLIED CURRENT PROPORTIONALLY





$$i_1 = \frac{G_1}{G_1 + G_2 + G_3} i$$

$$i_2 = \frac{G_2}{G_1 + G_2 + G_3} i$$


$$i_3 = \frac{G_3}{G_1 + G_2 + G_3} i$$

ACTIVE NETWORK REDUCTION


1. SOURCE REDUCTION

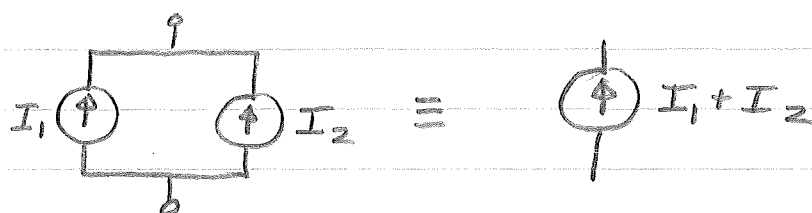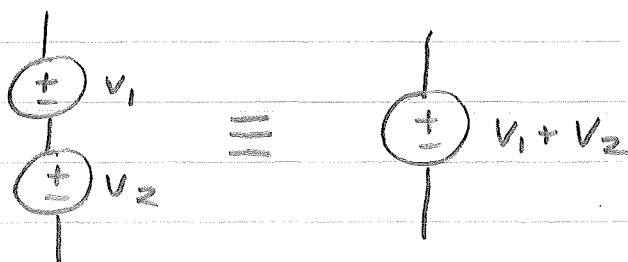


NOT ALLOWED (WILL BLOW UP)

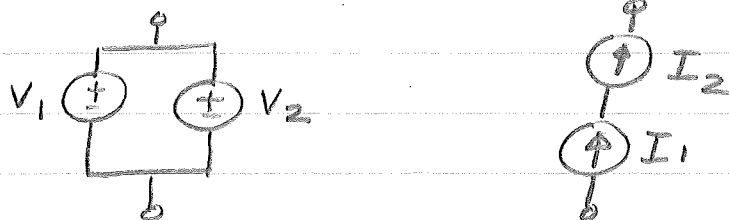

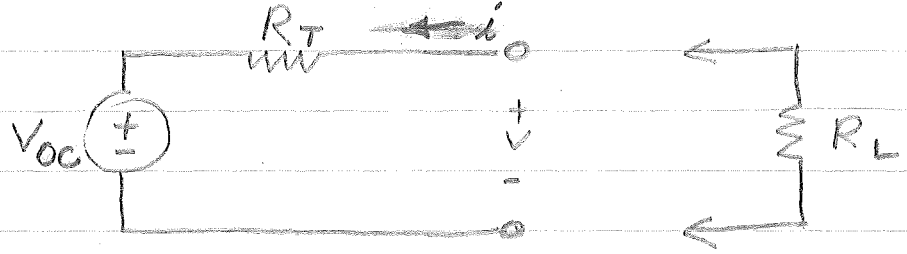2. THEVENIN'S THEOREM: IN SO FAR AS A LOAD IS CONCERNED, ANY ONE-PORT NETWORK OF RESISTORS AND ENERGY SOURCES CAN BE REPLACED BY:



V-i CURVE

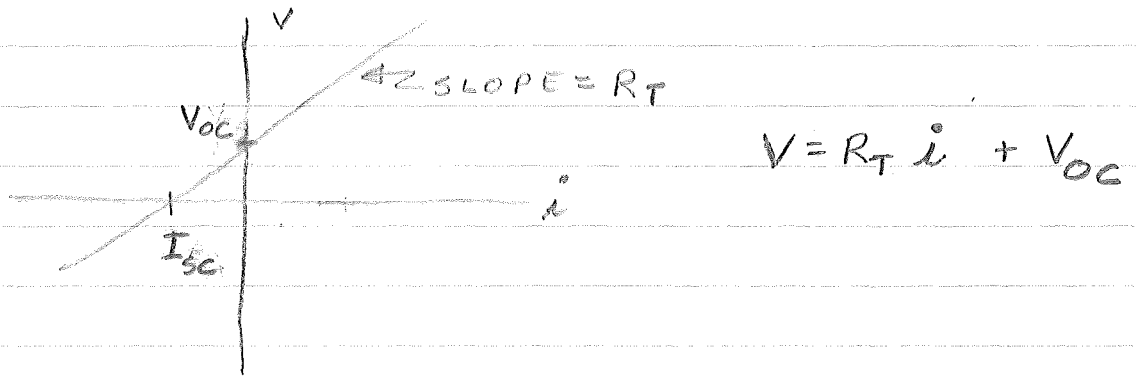



V_{OC} = OPEN CIRCUIT VOLTAGE ($i=0, R_L = \infty$)

LET I_{SC} = SHORT CIRCUIT CURRENT


($V=0, R_L=0$)

THEN $R_T = -V_{OC} / I_{SC}$

EXAMPLE

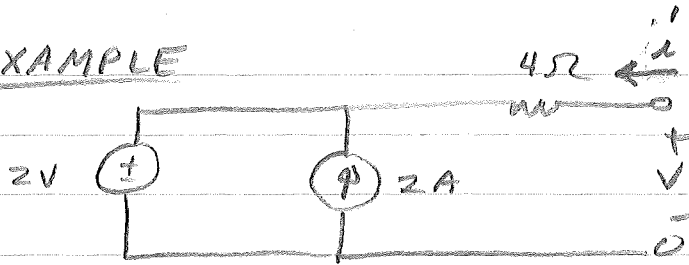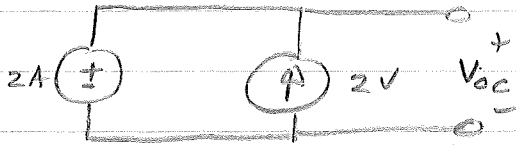 V_{oc} ($i=0$)

$$V_{oc} = 2V$$

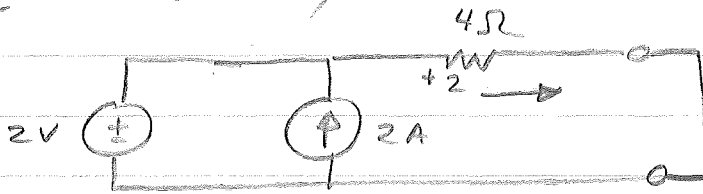
 I_{sc} ($V=0$)

$$V_{4\Omega} = 2V \Rightarrow -i_{4\Omega} = I_{sc} = -\frac{1}{2} \text{ AMP}$$


$$R_T = -V_{oc} / I_{sc} = 4\Omega$$

$$V = 4i + 2$$

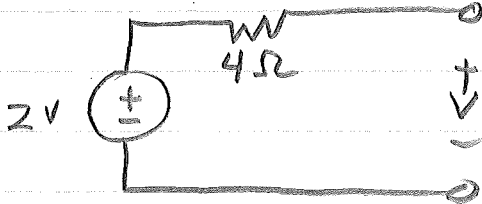\uparrow \uparrow
 R_T V_{oc}
 $\leftarrow i \rightarrow$




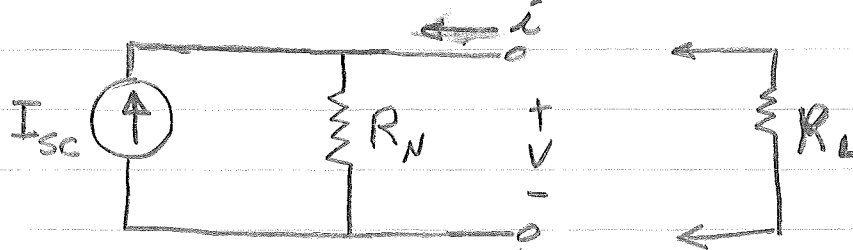3. NORTON'S THEOREM: IN SO FAR AS A LOAD IS CONCERNED, ANY ONE-PORT NETWORK OF RESISTORS AND ENERGY SOURCES CAN BE REPLACED BY




$$R_N = V_{oc} / I_{sc} (= R_T)$$


EQUIVALENT TO THEVENIN'S:

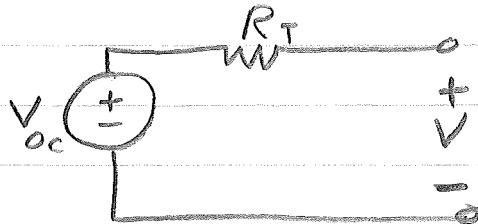

IN LAST EXAMPLE, WE HAD

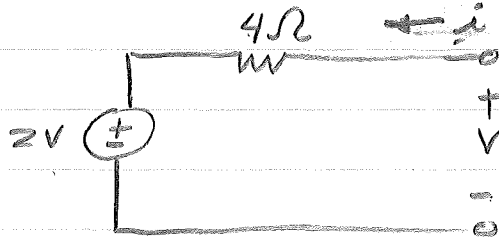

THE NORTON EQUIVALENT IS

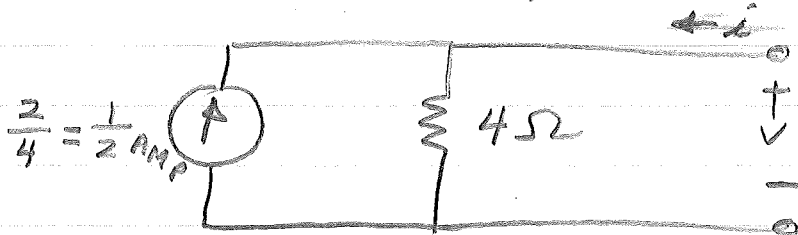


SUPERPOSITION THEOREM


IN CIRCUITS WITH ONLY R 's, L 's, C 's, V_s 's, AND I_s 's, THE CURRENT (VOLTAGE) THRU (ACROSS) AN ELEMENT IS THE SUM OF THE CURRENTS (VOLTAGES) INDUCED ON THAT ELEMENT BY THE CIRCUIT'S ENERGY SOURCES.

IMPLEMENTATION: WHEN VIEWING EFFECTS OF AN ENERGY SOURCE, SHORT CIRCUIT ALL V_s 's AND OPEN CIRCUIT ALL I_s 's NOT UNDER CONSIDERATION.

EXAMPLE

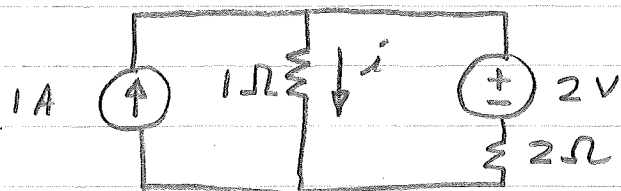FIND i


① FROM 1A SOURCE:

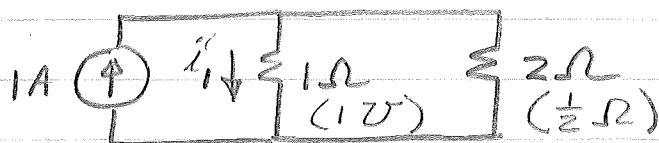

CURRENT DIVIDER

$$i_1 = \frac{1}{1 + \frac{1}{2}} (1 \text{ AMP}) = \frac{2}{3} \text{ AMP}$$

② FROM 2V SOURCE

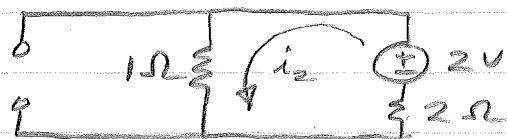
 ΣV AROUND LOOP

$$3i_2 = 2 \Rightarrow i_2 = \frac{2}{3} \text{ A}$$




THUS

$$i = i_1 + i_2 = \frac{4}{3} \text{ A}$$

A FEW FINAL NOTES

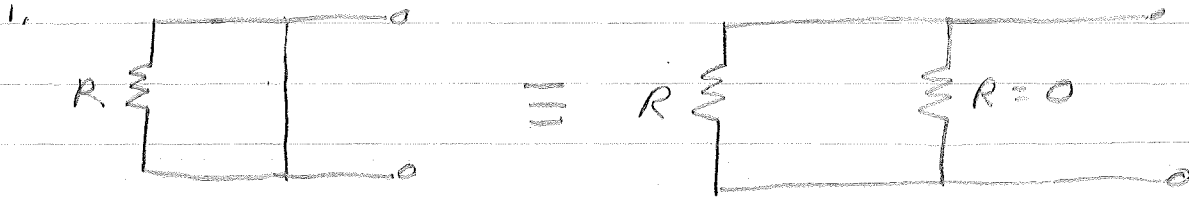
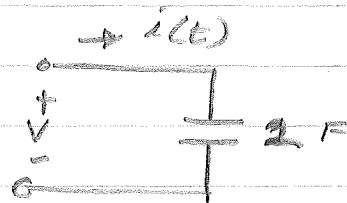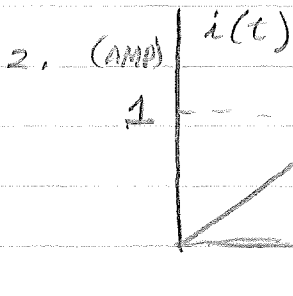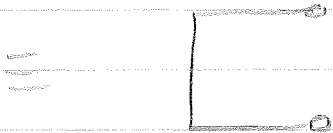
$$\frac{1}{0} + \frac{1}{R} = \frac{1}{R_{eq}} = \infty \Rightarrow R_{eq} = 0$$



$$v(t=2) = v(0) + \frac{1}{C} \int_0^2 i(t) dt$$

$$= \frac{1}{2} [1] = \frac{1}{2} v$$

TEST I

KNOW HOMEWORK & CLASS LECTURE EXAMPLES

1. V-I RELATIONS OF L.C.E.
2. CONCEPT OF ENERGY CONTINUITY
3. PASSIVE & ACTIVE ELEMENT COMBINATIONS
4. KIRCHHOFF'S LOOP AND VOLTAGE-NODE METHODS
5. CURRENT AND VOLTAGE DIVIDERS
6. THEVININ'S & NORTON EQUIVALENTS &
HOW TO FIND THEM
7. SUPERPOSITION THEOREM

TEST MONDAY

OPEN BOOK (TEXT, NOTES, H.W, HANDOUTS, CALC)

7 PROBLEM \Rightarrow 125 POINTS

B.Y.O.P. TEST

HOMEWORK GRADING

m = NUMBER OF PROBLEMS ASSIGNED

q = " " " NOT ATTEMPTED

n = " " " GRADED $\geq m/2$

$I(d)$ = NEXT HIGHEST INTEGER $\geq d$


P_i = POINTS ON i^{TH} GRADED PROBLEM

SCORE = $I(d)$ WHERE

$$d = \left(\sum_{i=1}^n P_i \right) \left(\frac{m-q}{n} \right)$$

$$d_{\text{MAX}} = I_{\text{MAX}} = 10m$$

COMPLEX NUMBERS

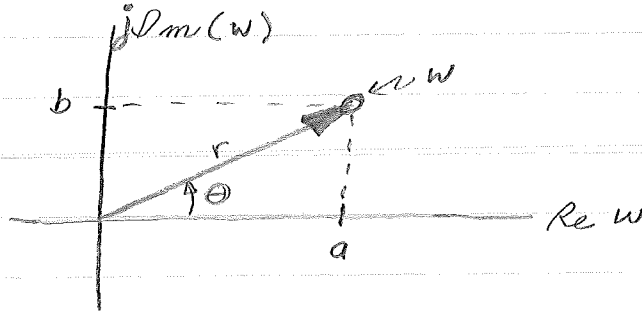

$$\begin{aligned} W &= \text{Re } W + j \text{Im } W \\ &= a + jb \end{aligned}$$

WE MAY SPECIFY THE POINT W
IN TWO WAYS

(1) RECTANGULAR COORDINATES

$$W = a + jb$$

(2) POLAR COORDINATES

$$W = r \angle \theta$$

" \angle " IS READ "AT THE ANGLE"

θ IS ALWAYS MEASURED CCW
FROM THE $\text{Re } W$ AXIS

WE MAY EQUIVALENTLY WRITE

$$W = r e^{j\theta} = a + jb; \quad j$$

(WILL SHOW THIS LATER)

FROM GEOMETRY

$$a = r \cos \theta$$

$$b = r \sin \theta$$

$$r = \sqrt{a^2 + b^2}$$

$$\theta = \text{atan} \frac{a}{b}$$

PROPERTIES AND NOMENCLATURE

COMPLEX CONJUGATE

$$W = a + jb = r e^{j\theta}$$

$$W^* = a - jb = r e^{-j\theta}$$

ABSOLUTE VALUE & COMPONENTS

$$|W| = |a + jb| = r = \sqrt{a^2 + b^2}$$


$$\text{Arg } W = \theta$$

$$\text{Re } W = a$$

$$\text{Im } W = b$$

EULER'S FORMULA
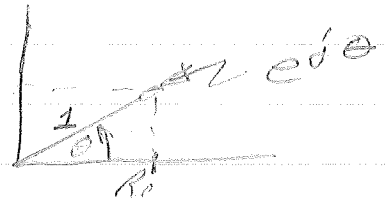
$$e^{\pm j\theta} = \cos \theta \pm j \sin \theta$$



$$\text{Re}[e^{j\theta}] = a = \cos \theta$$

$$\text{Im}[e^{j\theta}] = b = \sin \theta$$

HOMEWORK

SHOW THAT

$$|e^{j\theta}| = 1$$

$$\cos \theta = \frac{1}{2} [e^{j\theta} + e^{-j\theta}]$$

$$\sin \theta = \frac{j}{2} [e^{j\theta} - e^{-j\theta}]$$

$$|W| = |W^*|$$

$$\text{arg } W = -\text{arg } W^*$$

ALWAYS VIEW $e^{j\theta}$ AS
1 AT AN ANGLE OF θ ,

COMPLEX ARITHMETIC

(a) X AND \div

ALWAYS USE POLAR FORM

$$\frac{W_1}{W_2} = \frac{r_1 e^{j\theta_1}}{r_2 e^{j\theta_2}} = \frac{r_1}{r_2} e^{j(\theta_1 - \theta_2)}$$

$$= \frac{r_1}{r_2} \angle \theta_1 - \theta_2$$

$$W_1 W_2 = (r_1 e^{j\theta_1})(r_2 e^{j\theta_2}) = r_1 r_2 e^{j(\theta_1 + \theta_2)}$$

$$= r_1 r_2 \angle \theta_1 + \theta_2$$

(b) + and -

ALWAYS USE RECTANGULAR FORM

$$W_1 \pm W_2 = (a_1 + jb_1) \pm (a_2 + jb_2)$$

$$= (a_1 \pm a_2) + j(b_1 \pm b_2)$$

(c) IF $W_1 = W_2$

THEN

$$a_1 = a_2$$

$$b_1 = b_2$$

OR


$$r_1 = r_2$$

$$\theta_1 = \theta_2$$

EXPONENTIALS

(A) REAL ARGUMENTS

(1) CAPACITOR

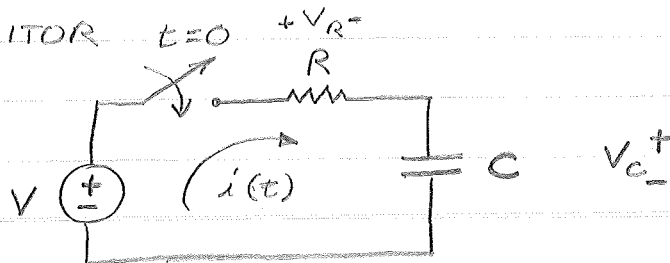

ASSUME $V_C(0) = 0$, $t < 0$

FOR $t > 0$

$$-V + R i(t) + \left[\frac{1}{C} \int_{t_0}^t i(t) d\tau + V_C(t_0) \right] = 0$$

DIFFERENTIATING

$$R \frac{di}{dt} + \frac{1}{C} i = 0 \Rightarrow \frac{di}{dt} = -\frac{1}{RC} i(t)$$

SOLUTION IS

$$i(t) = a e^{-\frac{t}{RC}} ; t > 0$$

(HW: CONFIRM THIS IS A SOLUTION)

AT $t=0^+$, $V_C(0^+) = 0$

\Rightarrow ALL VOLTAGE IS ACROSS R AND


$$i(0^+) = \frac{V}{R} = a e^0$$

OR $a = \frac{V}{R}$ AND

$$i(t) = \frac{V}{R} e^{-t/RC}$$

$\tau = RC \Rightarrow$ TIME CONSTANT
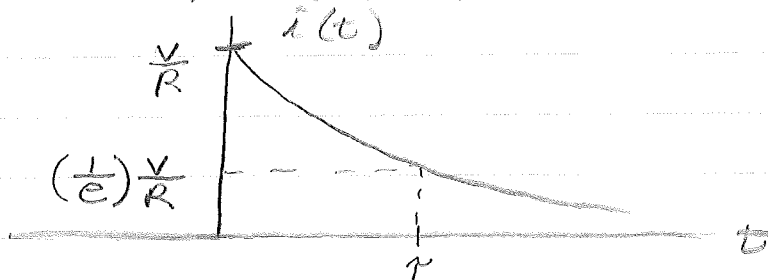
$$\frac{1}{\tau} i(t) = \frac{V}{R} e^{-t/\tau}$$




WHAT IS $V_R(t)$?

$$\begin{aligned} V_R(t) &= R i(t) \\ &= v e^{-t/\tau} \end{aligned}$$

WHAT IS $V_C(t)$?

$$\begin{aligned} V &= V_R(t) + V_C(t) \\ &= v e^{-t/\tau} + V_C(t) \end{aligned}$$

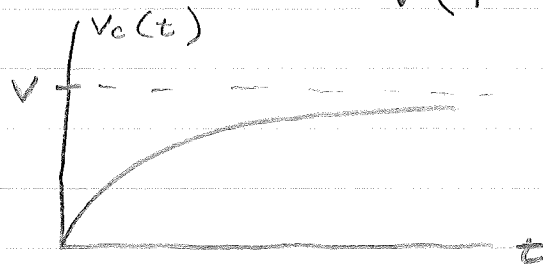
$$\begin{aligned} \Rightarrow V_C(t) &= v - v e^{-t/\tau} \\ &= v(1 - e^{-t/\tau}) \end{aligned}$$



$$V_C(0) = 0$$

$$V_C(\infty) = V$$

(2) INDUCTOR

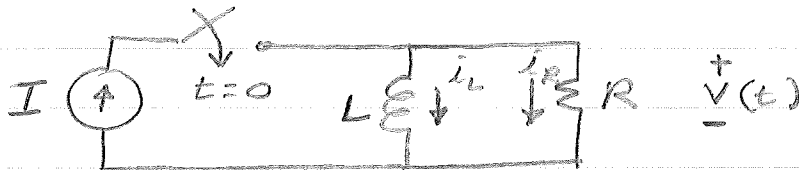

ASSUME $i_L(0^-) = 0$

$$\begin{aligned} I &= i_L + i_R \\ &= \left[\frac{1}{L} \int_{t_0}^t v(t) dt + v(t_0) \right] + \frac{1}{R} v(t) \end{aligned}$$

DIFFERENTIATE

$$0 = \frac{1}{L} v(t) + \frac{1}{R} \frac{d}{dt} v(t) \Rightarrow \frac{dv}{dt} = -\frac{R}{L} v(t)$$

SOLUTION IS: $v(t) = a e^{-\frac{R}{L}t}$

$\tau = L/R = \text{TIME CONSTANT}$

$$\Rightarrow v(t) = a \cdot e^{-t/\tau}$$


FIND a

$$i_L(0^+) = i_L(0^-) = 0$$

$$\Rightarrow i_R(0^+) = I$$

$$v(0^+) = RI$$

$$\Rightarrow v(t) = RI e^{-t/\tau}$$

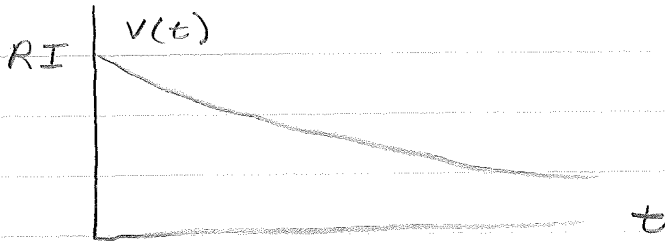


[H.W: FIND $i_L(t)$ AND $i_R(t)$]


(3) INTERPRETATION OF EXPONENTIALS

CAPACITOR $\rightarrow \tau = RC$

INDUCTOR $\rightarrow \tau = L/R (= LG)$

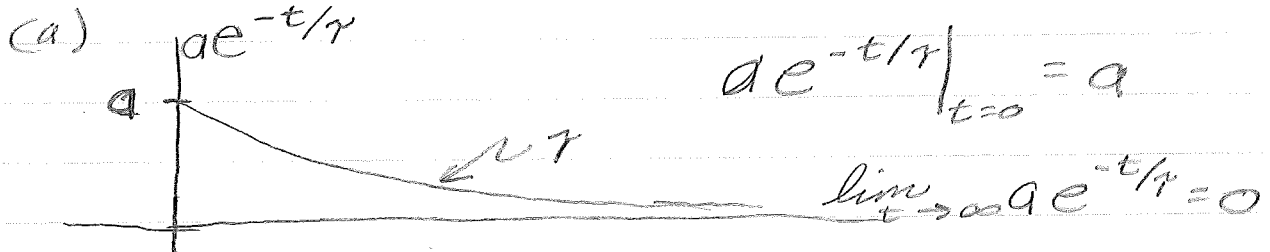

(b) $a [1 - e^{-t/\tau}]$

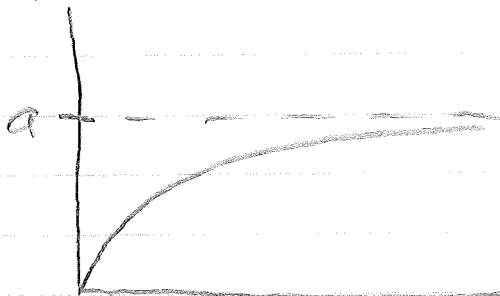

$$@ t=0 \Rightarrow 0$$


$$t \rightarrow \infty \Rightarrow a$$

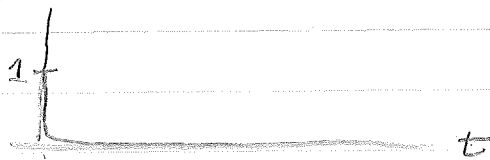(C) TIME CONSTANT




$$\lim_{\tau \rightarrow \infty} e^{-t/\tau} = e^{-0} = 1$$



$$\lim_{\tau \rightarrow 0} e^{-t/\tau} = e^{-\infty} = \frac{1}{e^{\infty}} = \frac{1}{\infty} = 0$$




THUS

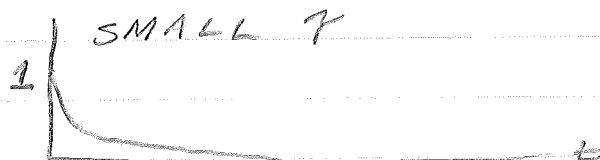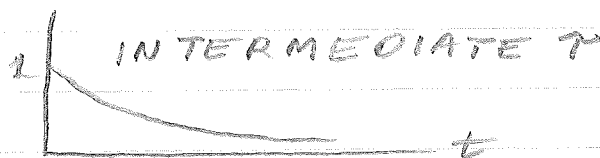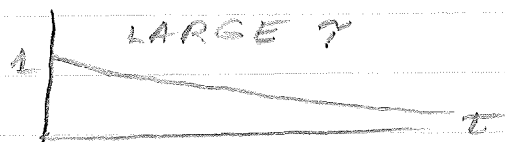

PHASORS

$$w(t) = M e^{j(\omega t + \phi)} = \text{Re}[M \cos(\omega t + \phi)]$$

$$w(\omega) = M e^{j\phi}$$

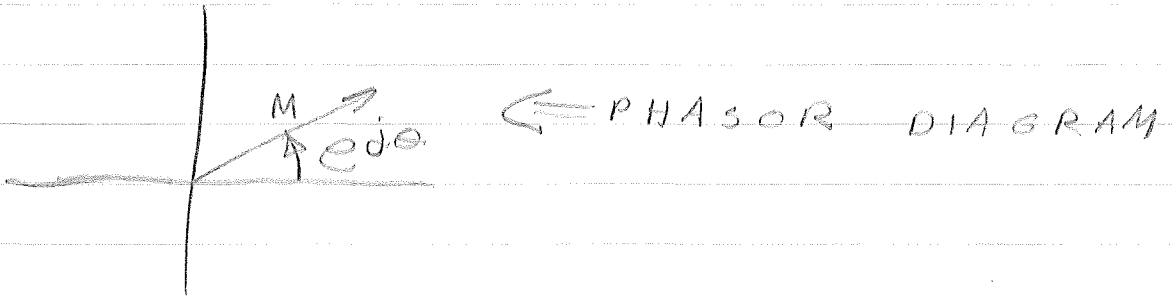


(B) IMAGINARY ARGUMENTS

(SINUSOIDS)

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$\text{LET } \theta = \omega t = 2\pi f t$$
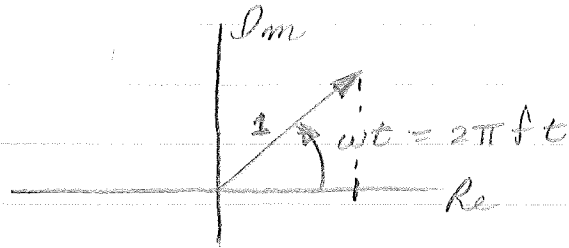
$$e^{j\omega t} = \cos \omega t + j \sin \omega t$$



THE PROJECTION OF THIS PHASOR ON
THE REAL AXIS IS

$$\text{Re } e^{j\omega t} = \cos \omega t = \cos 2\pi f t$$

IDENTIFICATION AND MEASUREMENT OF PERIODIC WAVEFORMS


(A) SINUSOIDS

$$V(t) = V_0 \cos(2\pi ft + \phi)$$

$V_0 =$ AMPLITUDE

$f =$ FREQUENCY (HZ) } COMPLETELY SPECIFIES

$\phi =$ PHASE (RADIAN) } SINUSOID

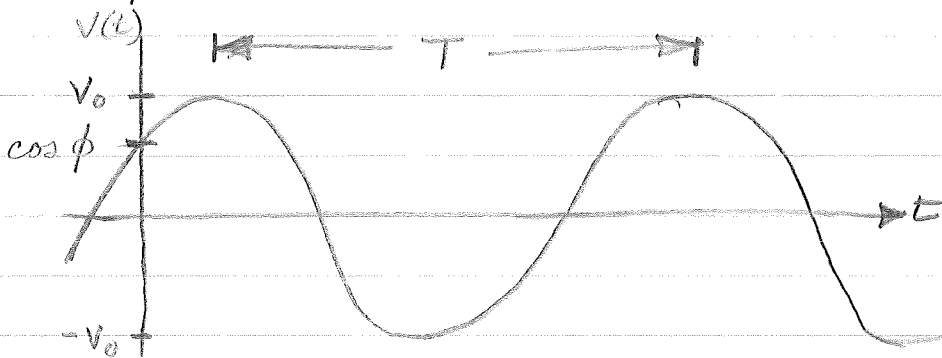

RELATION TO OTHER PARAMETERS:


$$T = \text{PERIOD} = 1/f$$

$$\omega = \text{ANGULAR FREQUENCY} = 2\pi f$$

$$\begin{cases} \cos(\theta - \pi/2) = \sin \theta \\ \sin(\theta + \pi/2) = \cos \theta \end{cases}$$

~~RELATION TO PHASOR~~

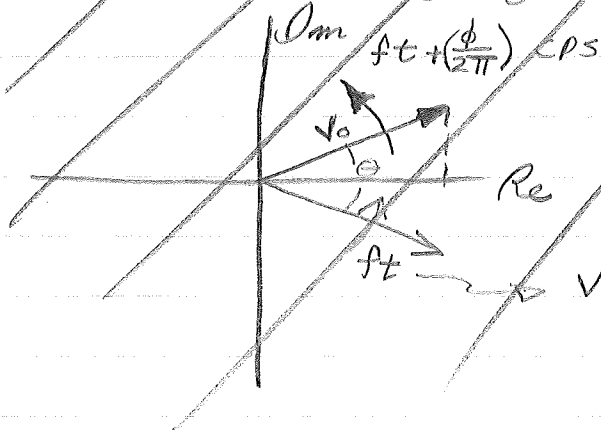~~$$V(t) = V_0 \cos\{2\pi ft + \phi\}$$~~
~~$$= \text{Re } V_0 e^{j(2\pi ft + \phi)}$$~~




NOTE: WE'VE SPECIFIED

$f, \phi,$ AND V_0

~~$$V_0 \cos 2\pi ft$$~~


(B) GENERAL PERIODIC WAVEFORMS

$f(t)$ IS PERIODIC IF $\exists T$
 $\Rightarrow f(t+T) = f(t) \forall t$

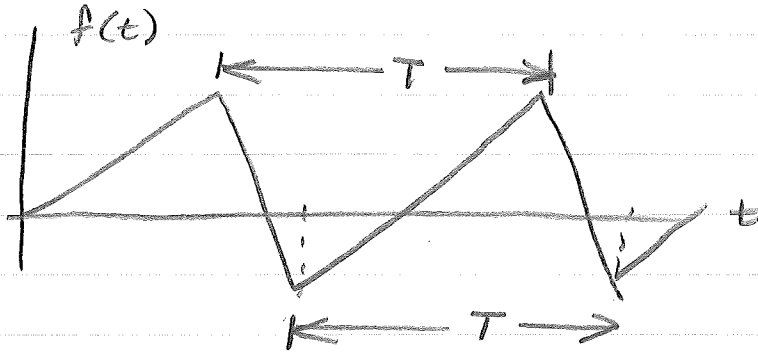MEASURES OF PERIODIC FUNCTIONS

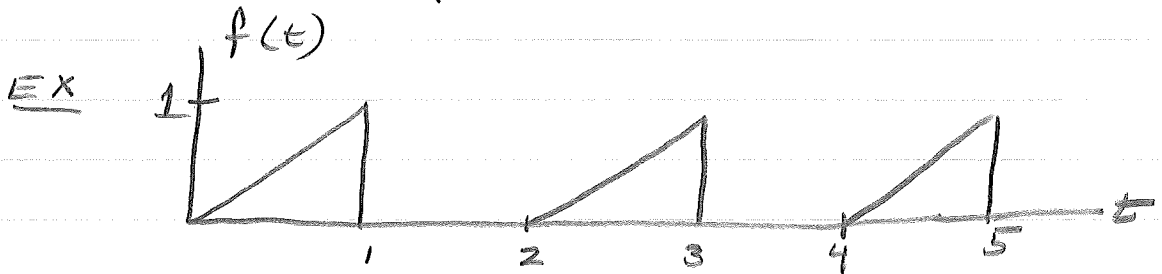(1) AVERAGE VALUE

$$f_{AVE} \triangleq \frac{1}{T} \int_T f(t) dt = \frac{1}{T} \int_{t_0}^{t_0+T} f(t) dt$$



$$f(t) = \begin{cases} t & ; 0 < t \leq 1 \\ 0 & ; 1 < t \leq 2 \end{cases}$$

$$f(t) = f(t+2) \Rightarrow T = 2$$

$$\begin{aligned} f_{AVE} &= \frac{1}{2} \left[\int_0^1 t dt + \int_1^2 (0) dt \right] \\ &= \frac{1}{2} \left. \frac{1}{2} t^2 \right|_0^1 \\ &= \frac{1}{4} \end{aligned}$$

(2) RMS (ROOT MEAN SQUARE) OR EFFECTIVE VALUE

$$f_{\text{RMS}} = f_{\text{EFF}} \triangleq \sqrt{\frac{1}{T} \int_T f^2(t) dt}$$

EX) FOR PREVIOUS EXAMPLE

$$\begin{aligned} f_{\text{RMS}} &= \left[\frac{1}{2} \int_0^1 t^2 dt + \frac{1}{2} \int_1^2 (0)^2 dt \right]^{1/2} \\ &= \left[\frac{1}{2} \left. \frac{1}{3} t^3 \right|_0^1 \right]^{1/2} \\ &= 1/\sqrt{6} \end{aligned}$$

NOTE: IN GENERAL

$$f_{\text{RMS}} \neq f_{\text{AVE}}$$

(3) PEAK TO PEAK VALUE

$$f_{\text{PTP}} = f_{\text{MAX}} - f_{\text{MIN}}$$

HOMEWORK (1) FIND f_{RMS} AND f_{EFF} WHEN, FOR $a \neq \phi$ CONSTANT,

$$f(t) = a \cos(2\pi f t + \phi)$$

HINTS:



$$T = 1/f$$

$$\cos^2 \theta = \frac{1}{2} [1 + \cos 2\theta]$$


(b) SHOW THAT $f(t) = a = \text{CONSTANT}$ IS "PERIODIC". COMPUTE f_{AVE} AND f_{RMS} AND COMMENT.

(3) METERS

(a) AMMETER

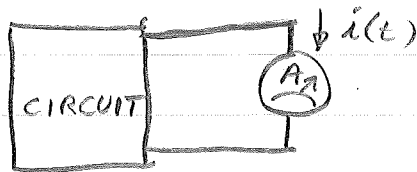
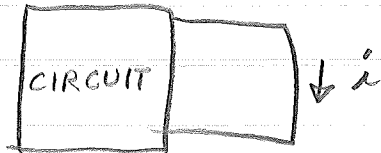


(b) VOLTMETER

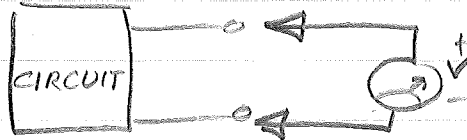

IF THE CURRENT, (VOLTAGE) IS PERIODIC, THEN THE AMMETER (VOLTMETER) REGISTERS THE RMS VALUE.

(3) WATTMETER (COMMON)

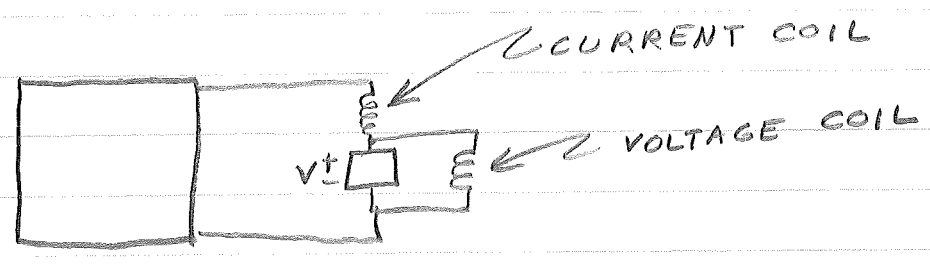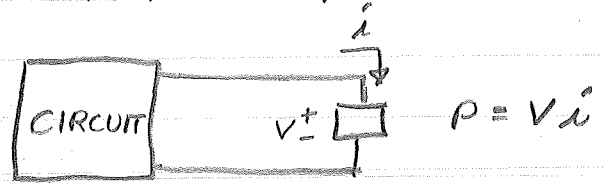


COIL'S MAGNETIC FIELDS INTERACT TO GIVE A NEEDLE DEFLECTION PROPORTIONAL TO THE AVERAGE POWER.

ENERGY STORAGE ^{D.C.}
~~CIRCUIT~~ ELEMENT RESPONSES

A₀. TRANSIENT RESPONSE - THE EFFECT OF AN ACTION (SUCH AS THROWING A SWITCH) ON THE V OR i OF AN ELEMENT


1. CAPACITOR $t=0$

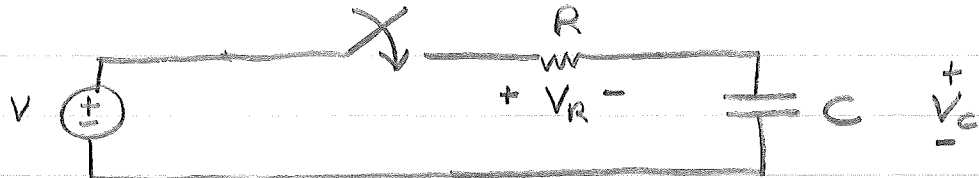

$$V_C(0^+) = V_C(0^-)$$

VOLTAGE CAN'T CHANGE INSTANTANEOUSLY ACROSS A CAPACITOR

2. INDUCTOR

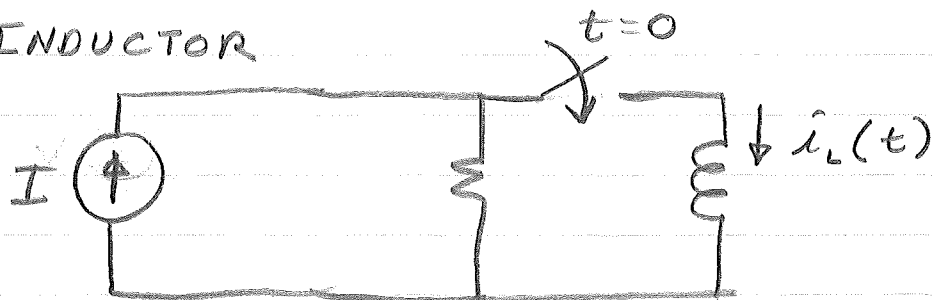


$$\hat{i}_L(0^+) = \hat{i}_L(0^-)$$

CURRENT CAN'T CHANGE INSTANTANEOUSLY ACROSS AN INDUCTOR

B. STEADY STATE RESPONSE - THE V OR i OF AN ELEMENT AFTER THE CIRCUIT HAS BEEN CONNECTED FOR A "LONG TIME"

(1) CAPAC.

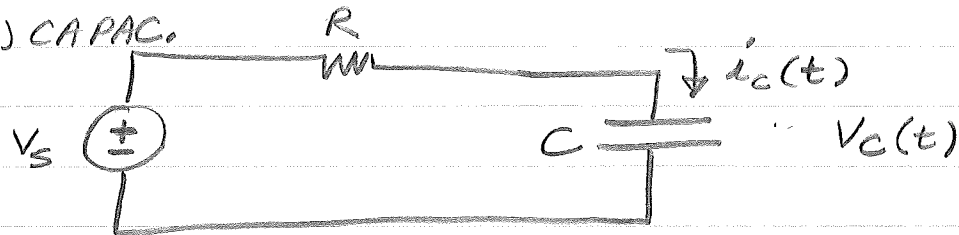


$$V_c(\infty) = V_s$$

$$i_c(\infty) = C \frac{dV}{dt} = 0$$

\therefore AFTER A "LONG TIME", A CAPACITOR UNDER D.C. CONDITIONS ACTS AS AN OPEN CIRCUIT.


(2) INDUCTOR

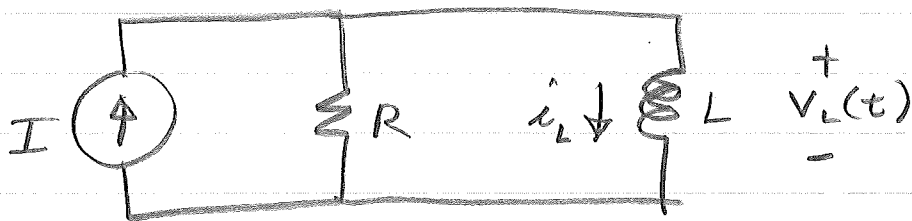

$$i_L(\infty) = I$$


$$V_L(\infty) = L \frac{di}{dt} = 0$$

\therefore AFTER A "LONG TIME", AN INDUCTOR UNDER D.C. CONDITIONS, ACTS AS A SHORT CIRCUIT.

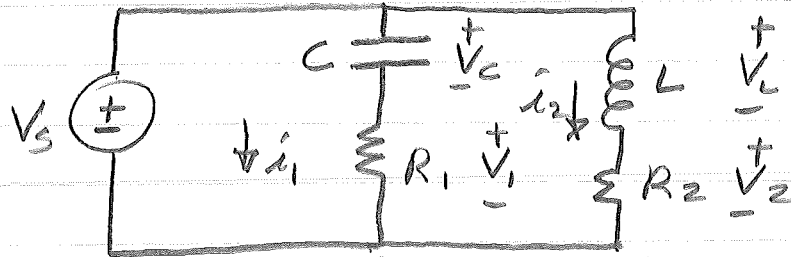
EX

(b) AFTER "A LONG TIME", WHAT ARE ALL OF THE ABOVE i 'S AND V 'S?

ANS:

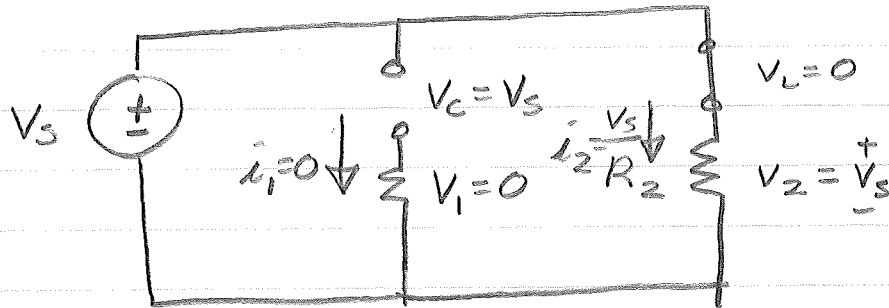

(a)

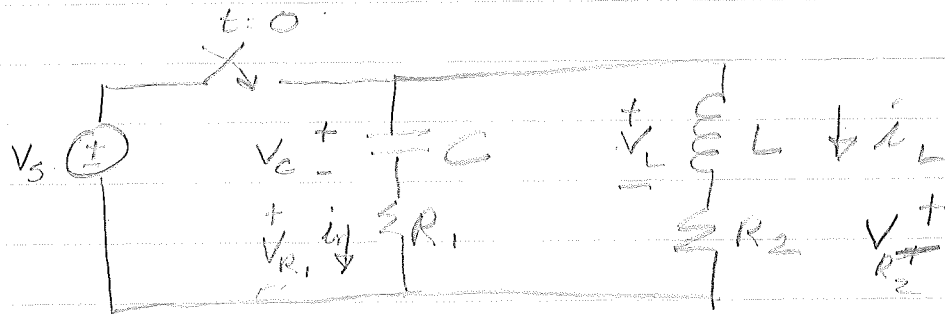

$$V_C(0^+) = V_C(0^-) = 0 \Rightarrow V_{R_1} = V_s$$

$$\Rightarrow i_{R_1}(0^+) = V_s / R_1$$

$$i_L(0^+) = i_L(0^-) = 0$$

$$\Rightarrow V_{R_2} = 0$$

$$\Rightarrow V_L = 0$$


NATURAL RESPONSE TO FIRST ORDER SYSTEM

DEF: FIRST ORDER SYSTEM: CONTAINS R'S, V'S, I'S AND ONE ENERGY STORAGE DEVICE (C OR L).

WE WILL CLOSE (OR OPEN) SWITCHES IN 1st ORD. SYS.

1. SOLUTION TOOLS

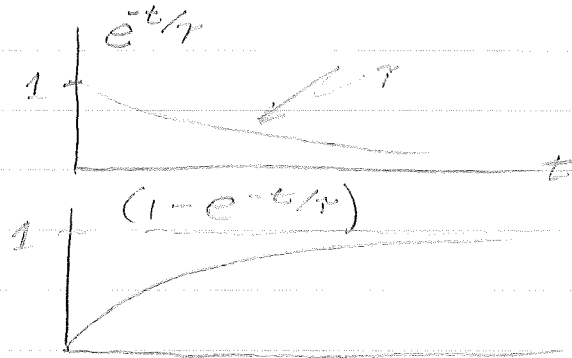1. TRANSIENT & STEADY STATE RESPONSES.
2. EXPONENTIAL CURVES (CONNECTS 0 & ∞)




2. FOUR NUGGETS OF KNOWLEDGE

1. $V(0^-)$ = VOLTAGE RIGHT BEFORE SWITCH IS CLOSED (D.C. ANALYSIS)
2. $V(0^+)$ = VOLTAGE RIGHT AFTER SWITCH IS CLOSED (TRANSIENT RESP)
3. $V(\infty)$ = STEADY STATE VOLTAGE
4. τ = TIME CONSTANT
= $R_{eq}C$ OR L/R_{eq}

WE CAN USE THE ABOVE FOR CURRENT TOO.


(Ex)

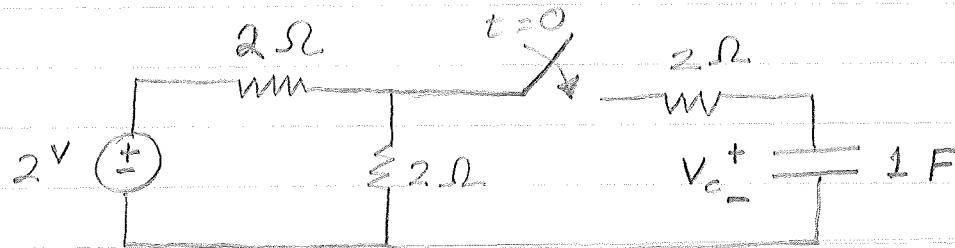

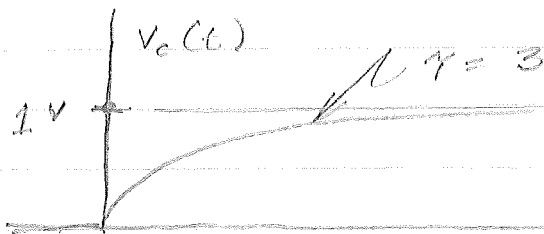
1. $V_c(0^-) = 0$
2. $V_c(0^+) = 0$
3. $V_c(\infty) = \frac{2}{2+2} \cdot 2 = 1 \text{ VOLT}$
4. $\tau = R_{eq} C$

$$R_{eq} = 2\Omega + 2\Omega // 2\Omega = 3\Omega$$


$$\Rightarrow \tau = (1F)(3\Omega) = 3 \text{ SEC}$$


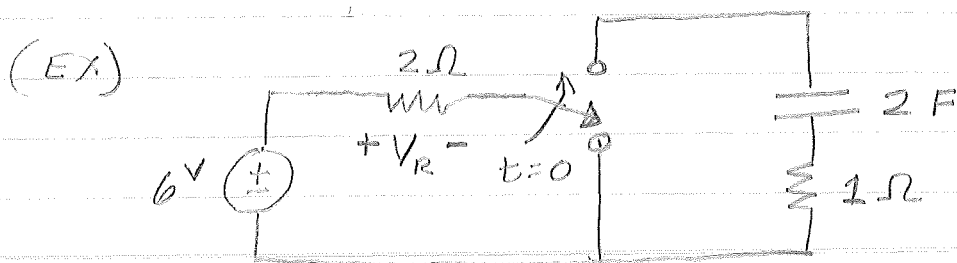
$$V_c(t) = \begin{cases} 1 - e^{-t/3} & ; t \geq 0 \\ 0 & ; t \leq 0 \end{cases}$$



$$(1) V_R(0^-) = 6V$$

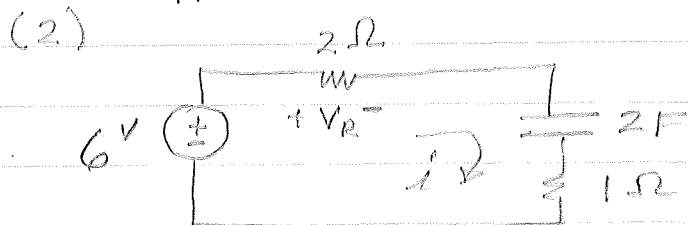

C ACTS AS SHORT

VOLTAGE DIVIDER

$$V_R(0^+) = \frac{2}{2+1} 6 = 4V$$


$$(3) @ t = \infty, C \text{ ACTS "OPEN"}$$

$$\Rightarrow i = 0 \Rightarrow V_R(\infty) = 0$$


$$(4) \tau = R_{eq} C$$

$$R_{eq} = 2 + 1 = 3\Omega$$

$$\tau = (3\Omega)(2F) = 6 \text{ SEC}$$

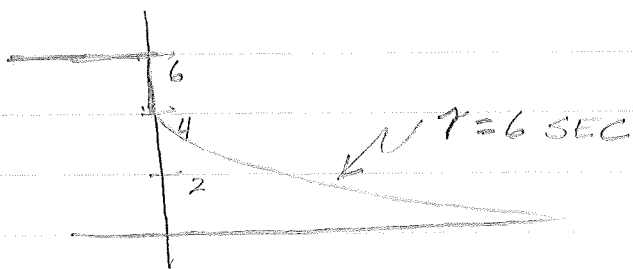
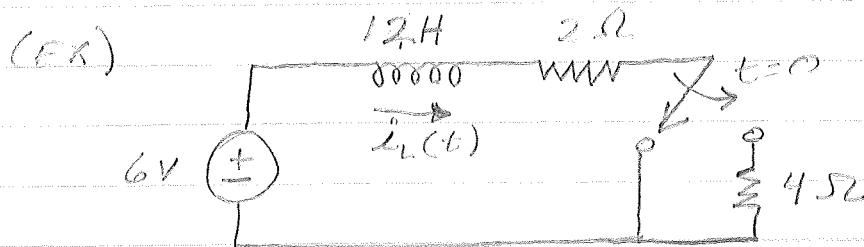
$$V_R(t) = \begin{cases} 6V & ; t < 0 \\ 4e^{-t/6} & ; t > 0 \end{cases}$$



(1) @ $t=0^-$, L ACTS SHORTED

$$i_L(0^-) = \frac{6V}{2\Omega} = 3 \text{ AMPS}$$

(2) @ $t=0^+$


$$i_L(0^+) = 3 \text{ AMPS}$$

$$(3) i_L(\infty) = \frac{6V}{(2+4)\Omega} = 1 \text{ AMP}$$

$$(4) \tau = L/R_{eq}$$

$$R_{eq} = 2 + 4 = 6 \Omega$$
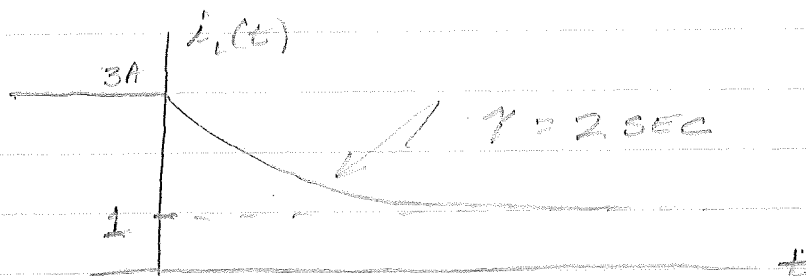
$$\Rightarrow \tau = 12/6 = 2 \text{ SEC}$$



$$i_L(t) = \begin{cases} 3 & ; t < 0 \\ 1 + 2e^{-t/2} & ; t > 0 \end{cases}$$

IMPEDENCE (SINUSOIDAL STEADY STATE RELATIONS)

A. PASSIVE ELEMENTS

1. RESISTOR

$$V(t) = V_s e^{j2\pi ft} \quad \begin{array}{|c|} \hline \oplus \quad \quad \quad \ominus \\ \hline \end{array} \quad \begin{array}{|c|} \hline i(t) \\ \hline \end{array} \quad \begin{array}{|c|} \hline R \\ \hline \end{array}$$

$$V_s e^{j2\pi ft} = R i(t)$$

$$\Rightarrow i(t) = \frac{V_s}{R} e^{j2\pi ft}$$

$$\text{OR } V(t) = R i(t)$$

2. INDUCTOR

$$V(t) = V_s e^{j2\pi ft} \quad \begin{array}{|c|} \hline \oplus \quad \quad \quad \ominus \\ \hline \end{array} \quad \begin{array}{|c|} \hline i(t) \\ \hline \end{array} \quad \begin{array}{|c|} \hline L \\ \hline \end{array}$$

$$V_s e^{j2\pi ft} = L \frac{di(t)}{dt}$$

$$di(t) = \frac{V_s}{L} \int e^{j2\pi ft} dt$$


$$= \frac{V_s}{j2\pi fL} e^{j2\pi ft}$$

$$\Rightarrow V(t) = V_s e^{j2\pi ft} = j2\pi fL i(t)$$

$$j2\pi f = j\omega$$

$$\Rightarrow V(t) = j\omega L i(t)$$

3. CAPACITOR

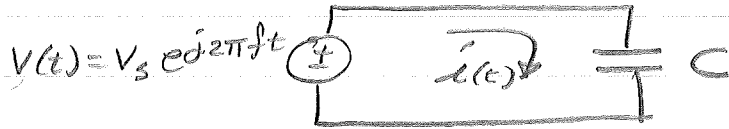

$$\begin{aligned} i(t) &= C \frac{dv(t)}{dt} \\ &= C V_s \frac{d}{dt} e^{j2\pi ft} \\ &= j2\pi f C V_s e^{j2\pi ft} \\ &= (j\omega C) v(t) \end{aligned}$$

OR
$$v(t) = \frac{1}{j\omega C} i(t)$$

WE HAVE GENERALIZED OHM'S LAW FOR SINUSOIDAL STEADY STATE:

$$V = Z \dot{I}$$




$Z = \text{IMPEDANCE}$

$$R \Rightarrow Z = R$$

$$C \Rightarrow Z = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$


$$L \Rightarrow Z = j\omega L$$

EQUIVALENT CIRCUITS

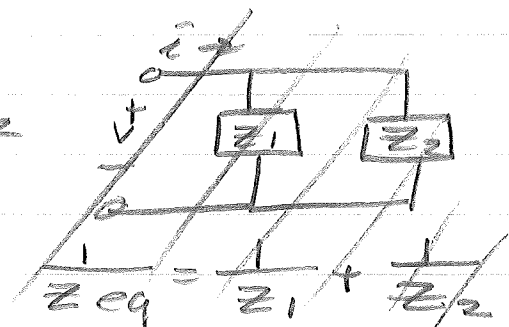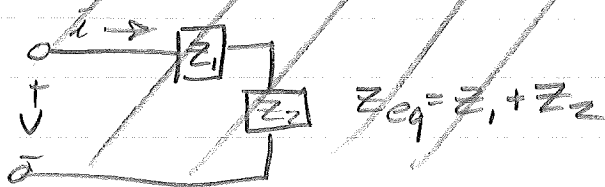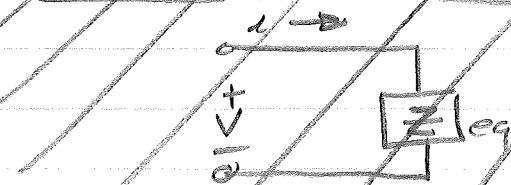

SERIES & PARALLEL COMBINATION OF IMPEDENCE

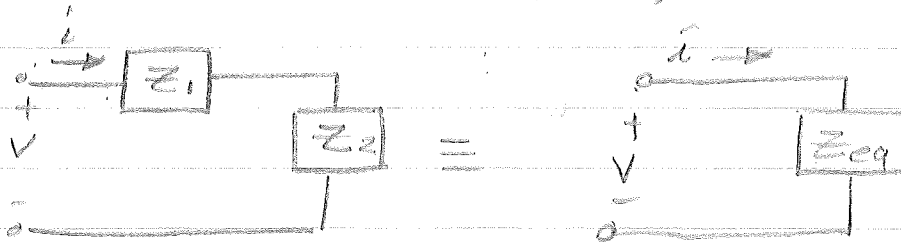1. SERIES CONNECTION (SAME i THRU ALL COMPONENTS)




$$Z_{eq} = Z_1 + Z_2$$

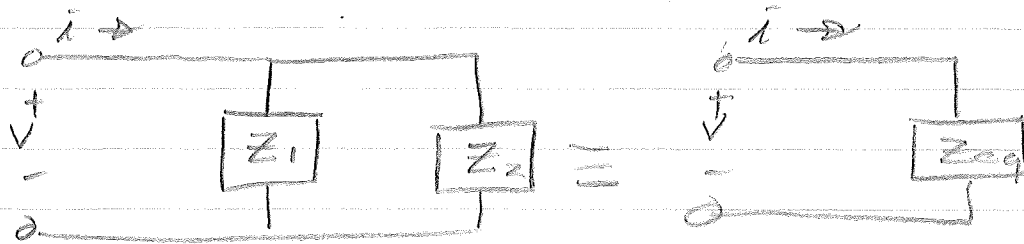2. PARALLEL CONNECTION (SAME V ACROSS ELEMENTS)

$$Y = 1/Z = \text{ADMITTANCE}$$

{ IMPEDANCE IN OHMS (Ω)
{ ADMITTANCE IN MHOS (\mathcal{U})





$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2}$$



OR

$$Y_{eq} = Y_1 + Y_2$$

EXAMPLE : $\omega = 10$

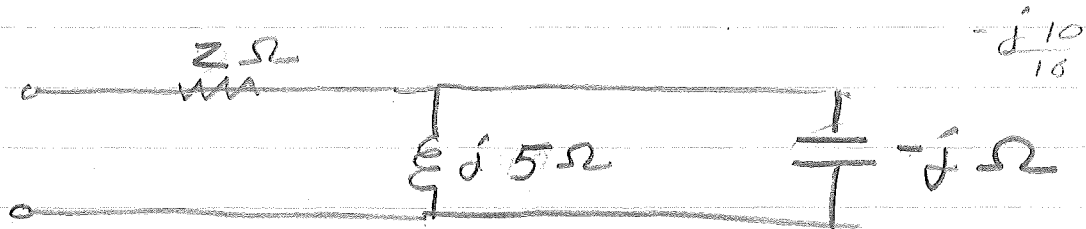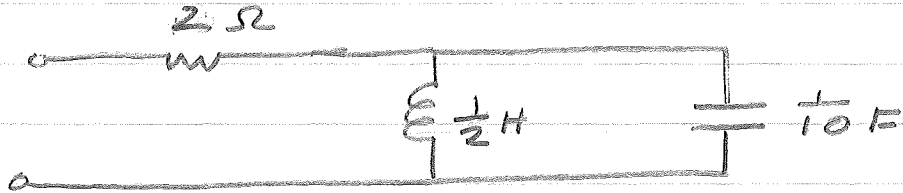

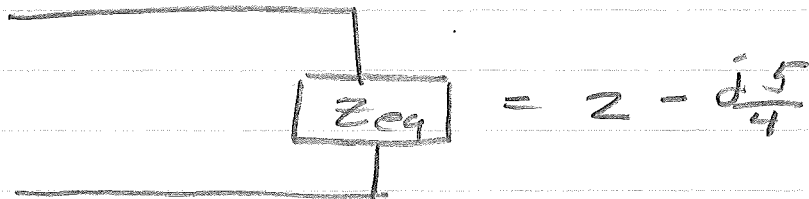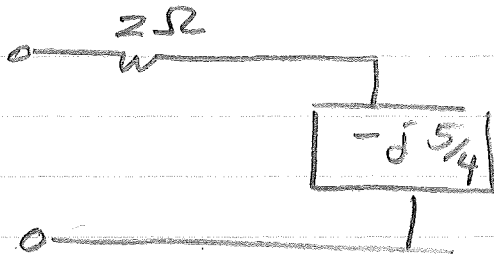
$$\begin{aligned} \frac{1}{Z_{eq}} &= \frac{1}{j5} + \frac{1}{-j} \\ &= \frac{1-j5}{j5} = \frac{-4}{j5} \Rightarrow Z_{eq} = \frac{-j5}{4} \end{aligned}$$




B. INTERPRETATION

1. COMPLEX PLANE INTERPRETATION

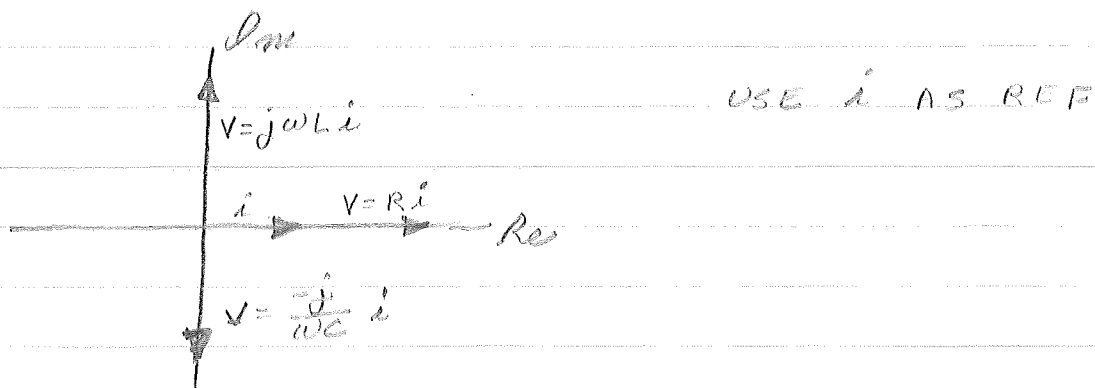


THE VOLTAGE THRU A CAPACITOR
 "LAGS" THE CURRENT BY $\frac{\pi}{2} = 90^\circ$, AND
 THAT THRU AN INDUCTOR "LEADS" BY $\frac{\pi}{2}$
 (NOTE 'V LEADS i ' \equiv ' i LAGS V')

2. PHYSICAL INTERPRETATION

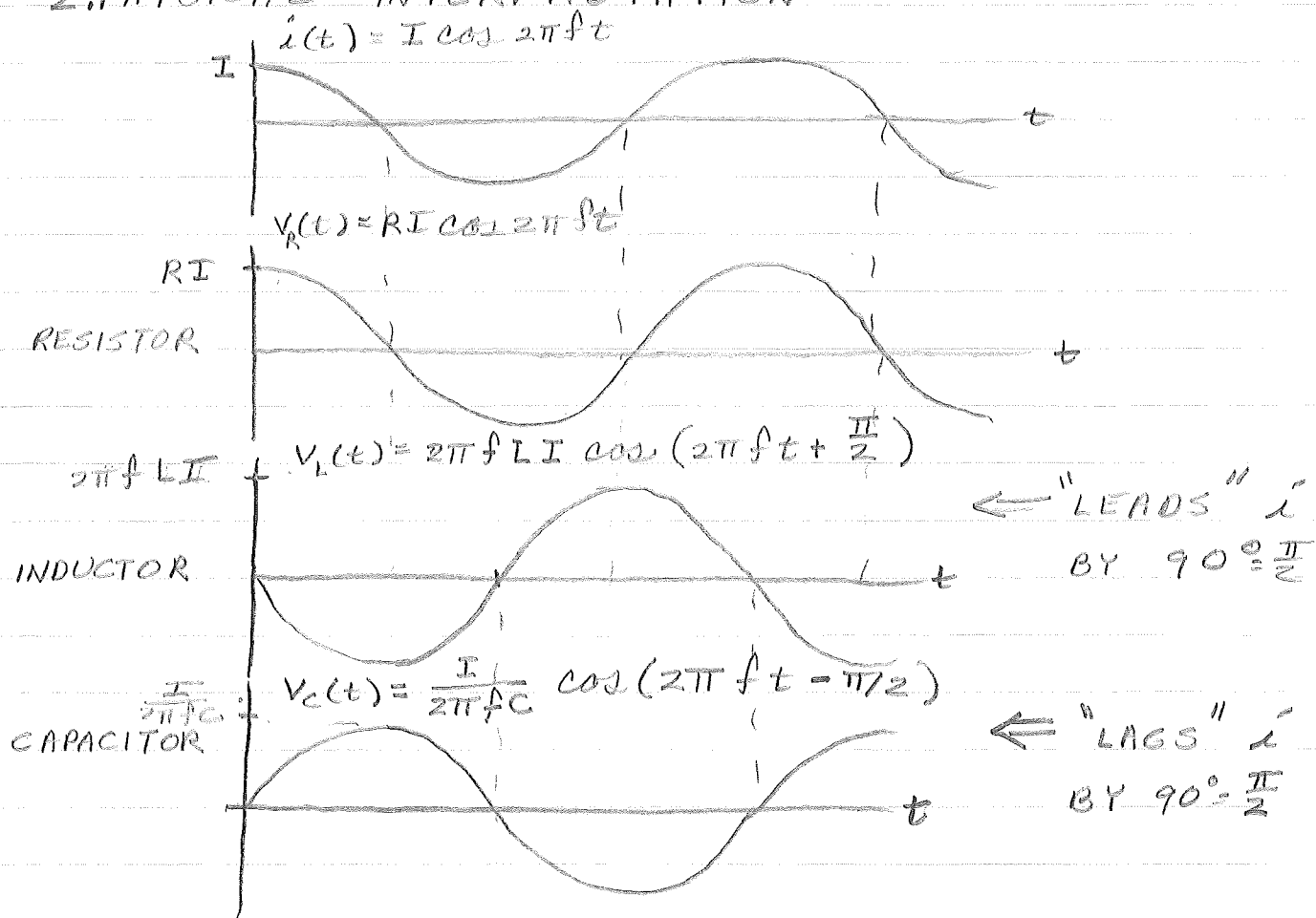


(C) EXAMPLES

(1)

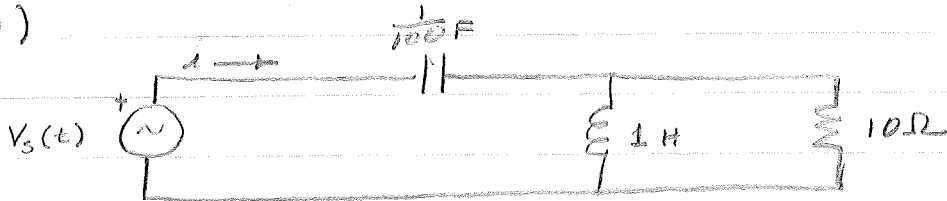

$$V_s(t) = V_0 \cos 10t \quad \Rightarrow \quad \omega = 2\pi f = 10$$

$$V_s(t) = V_0 \angle 0$$

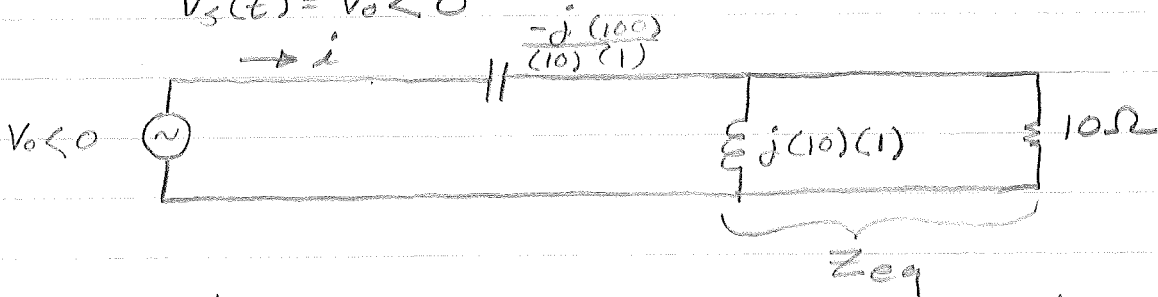


$$\frac{1}{Z_{eq}} = \frac{1}{j10} + \frac{1}{10} = \frac{1+j}{j10} = \frac{1-j}{10}$$

$$Z_{eq} = \frac{10}{1-j} \quad (\text{USE COMPLEX CONJ. TRICK})$$

Leave
in

NOTE: TO REMOVE A COMPLEX # FROM THE DEN, MULTIPLY BOTH NUM. & DEN BY COMPLEX CONJUGATE OF DENOM.
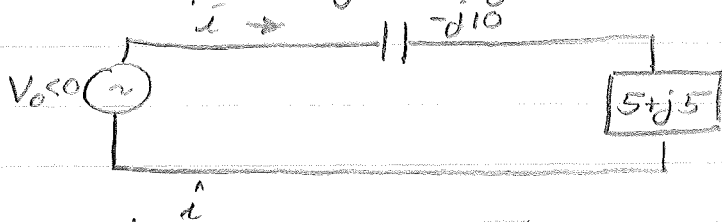
$$Z_{eq} = \frac{10}{1-j} \cdot \frac{1+j}{1+j} = \frac{10+j10}{2} = (5+j5) \Omega$$




$$V = ZI$$

$$V_0 \angle 0 = (5-j5) i = \sqrt{2} e^{-j\frac{\pi}{4}} i$$


OR
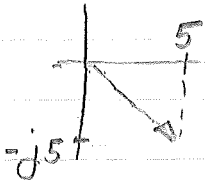
$$i = \frac{1}{\sqrt{2}} e^{j\frac{\pi}{4}} V$$




FIND i_R IN THE FOLLOWING CIRCUIT

(2)

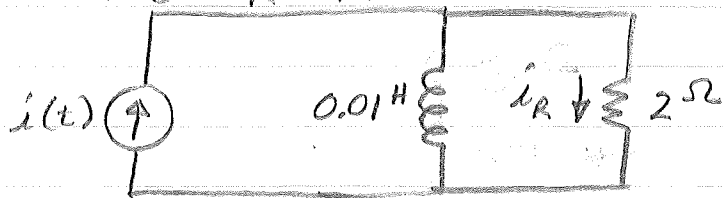

$$i(t) = I_0 \cos 100t \Rightarrow \omega = 2\pi f = 100$$

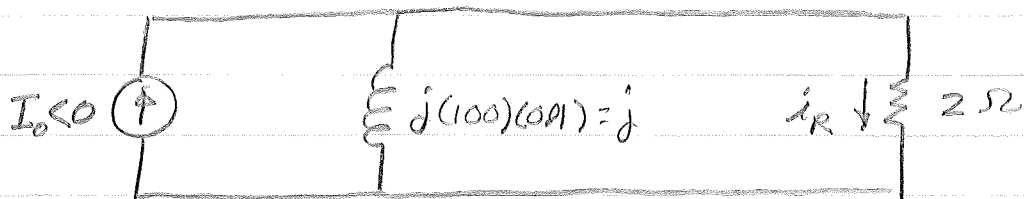IN PHASOR FORM $\Rightarrow i(t) = I_0 \angle 0 = I_0$




USE CURRENT DIVIDER

$$i_R = \frac{\frac{1}{2}}{\frac{1}{j} + \frac{1}{2}} I_0 = \frac{j}{2+j} (I_0)$$

USE COMPLEX CONJ. "TRICK"

$$i_R = \frac{j}{2+j} \frac{2-j}{2-j} (I_0)$$
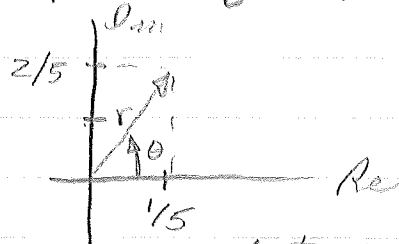
$$= \frac{1+j^2}{4+1} I_0 = \left(\frac{1}{5} + j \frac{2}{5}\right) I_0$$




$$\theta = \text{atan} \frac{2/5}{1/5}$$

$$= \text{atan} 2 = 63.4^\circ = 1.11 \text{ rad}$$


$$r = \sqrt{5}/5 = 1/\sqrt{5}$$

$$\Rightarrow i_R = \frac{1}{\sqrt{5}} e^{+j \text{atan} 2} I_0$$

PHASOR DIAGRAM

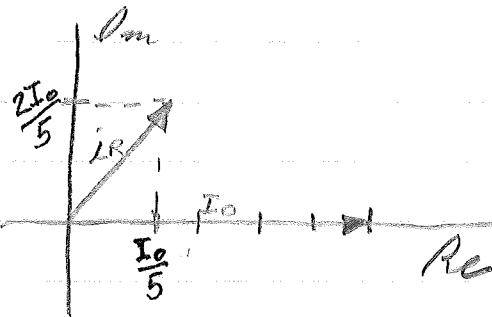


i_R "LEADS" i
BY $\text{atan} 2$ RADIANS

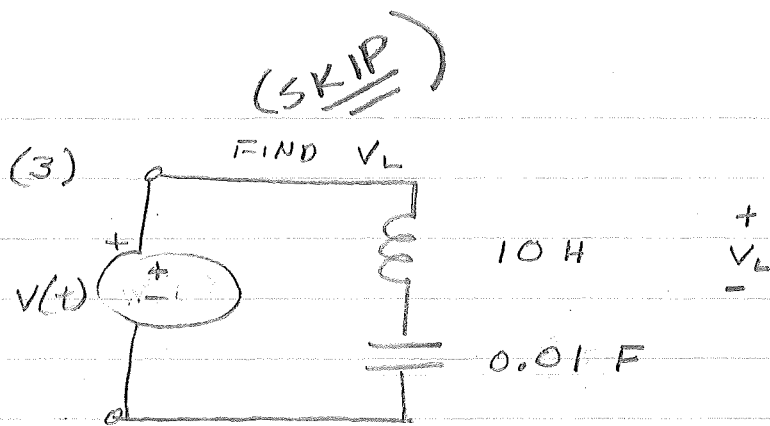

$$v(t) = V_0 \cos 5t \quad ; \quad \omega = 2\pi f = 5$$

$$V = V_0 < 0$$

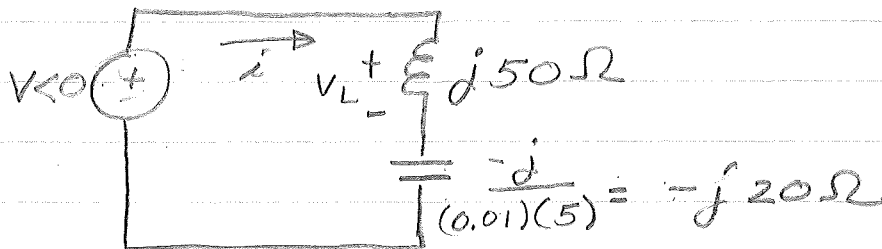

USE VOLTAGE DIVIDER:

$$V_L = \frac{j50}{j50 - j20} V_0 = \frac{j50}{j30} V_0$$


$$= \frac{5}{3} V_0$$

$$\Rightarrow V_L = \frac{5}{3} V_0 < 0$$

$$= \frac{5}{3} V_0 \cos 5t$$

WHAT IS i ?
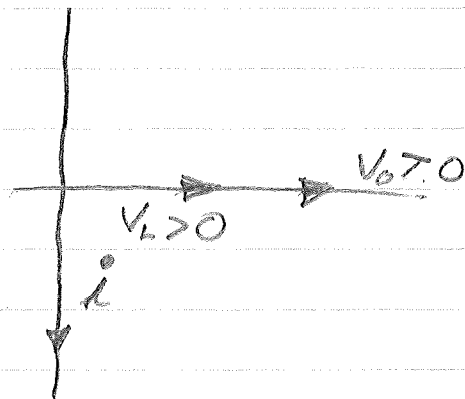
$$i = \frac{V_L}{j50} = \frac{\frac{5}{3} V_0}{j50} = \frac{-j}{30} V_0$$



IMPEDANCE COMPONENTS

- ① REACTANCE - THE IMAGINARY COMPONENT OF IMPEDANCE

THUS

$$\text{IMPEDANCE} = \text{RESISTANCE} + j \text{ REACTANCE}$$

$$Z = R + jX$$

- ② SUSCEPTANCE - THE IMAGINARY PART OF ADMITTANCE

THUS

$$\text{ADMITTANCE} = \text{CONDUCTANCE} + j \text{ SUSCEPTANCE}$$


$$= \frac{1}{\text{IMPEDANCE}}$$

OR

$$Y = \frac{1}{Z} = G + jB$$

$$\text{NOTE: } G \neq \frac{1}{R} \text{ AND } B \neq \frac{1}{X}$$


HOMEWORK: THE IMPEDANCE OF

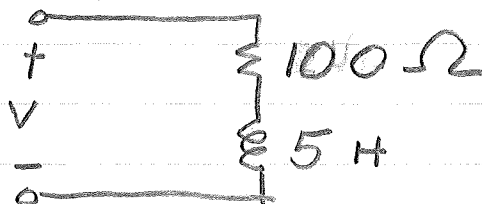

IS, AT $\omega = 10$, $Z = 100 + j50$.
 WHAT IS THE ^{CORRESPONDING} ADMITTANCE,
 AND CONDUCTANCE, AND
 SUSCEPTANCE?

RESONANCE

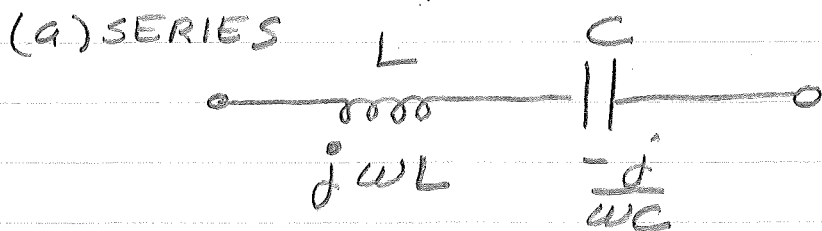AN $L \neq C$ ARE IN RESONANCE AT RESONANCE IF THEIR REACTANCES ARE OPPOSITE AND EQUAL. THAT IS, $X_L + X_C = 0$



$$X_L + X_C = 0$$

$$\omega L - \frac{1}{\omega C} = 0$$


$$\omega^2 L - \frac{1}{C} = 0$$

$$\omega^2 = \frac{1}{LC}$$


$$\omega = 2\pi f = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow f = \frac{1}{2\pi\sqrt{LC}} \leftarrow \text{RESONANT FREQUENCY}$$

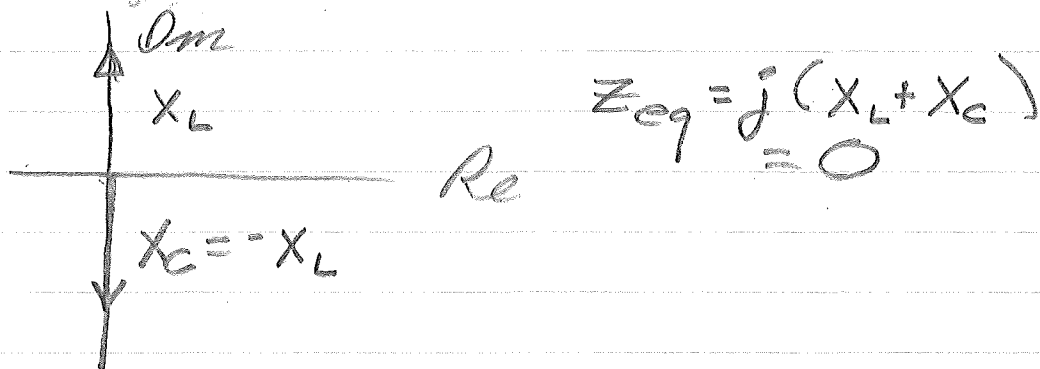\therefore @ $f = \frac{1}{2\pi\sqrt{LC}}$, $X_C + X_L = 0$ AND THE SERIES COMBINATION ACTS AS A SHORT CIRCUIT:



2. PARALLEL

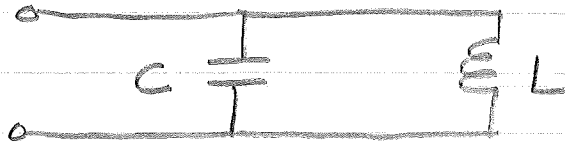

$$j\omega L + \frac{-j}{\omega C} = 0 \Rightarrow f = \frac{1}{2\pi\sqrt{LC}}$$


@ $f = \frac{1}{2\pi\sqrt{LC}}$, $X_L = X_C$ AND THE PARALLEL COMBINATION ACTS AS AN OPEN CIRCUIT:

$$\frac{1}{Z_{eq}} = \frac{1}{jX_L} + \frac{1}{jX_C} = 0$$

$$\Rightarrow Z_{eq} = \frac{1}{0} = \infty$$

~~\therefore @ $f = \frac{1}{2\pi\sqrt{LC}}$, THE PARALLEL COMBINATION OF AN L & C ACTS LIKE AN OPEN CIRCUIT.~~


EXAMPLE


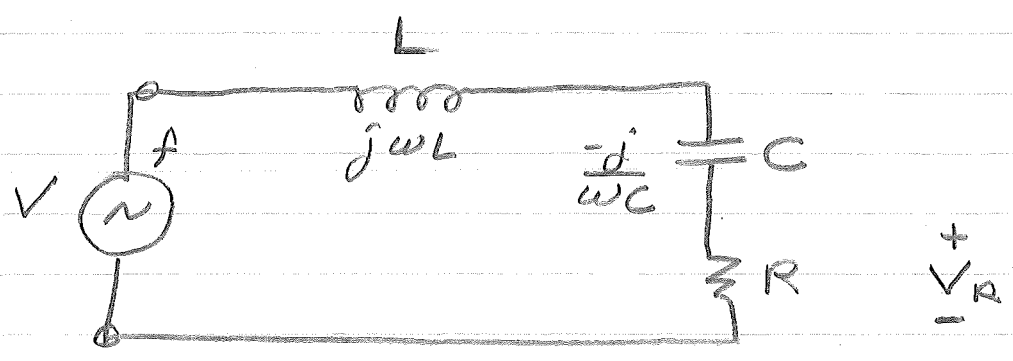


FIND V_R
 USING VOLTAGE DIVIDER


$$V_R = \frac{R}{R + j(\omega L - \frac{1}{\omega C})} V_0$$

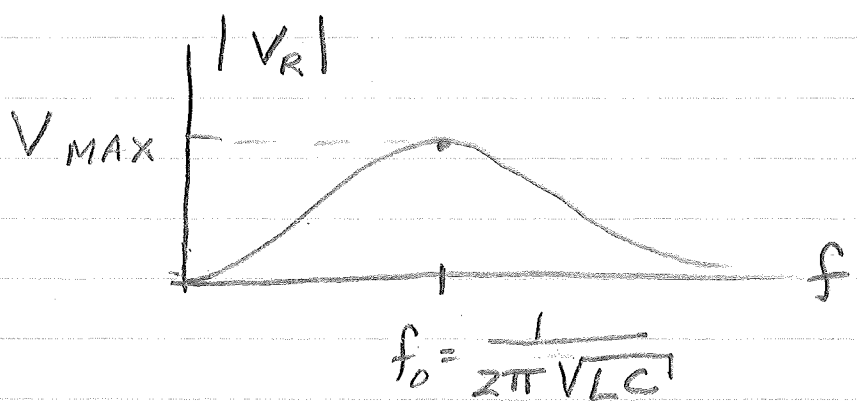INTUITIVELY, V_R SHOULD BE
 MAXIMUM WHEN $L \frac{1}{C}$ ARE
 AT RESONANCE



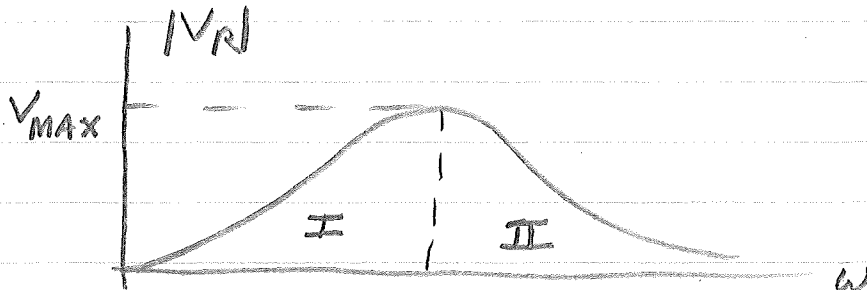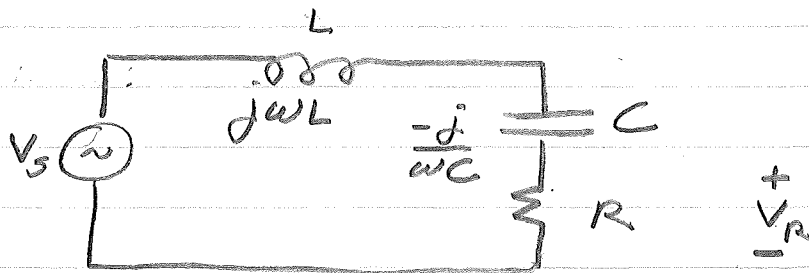


@ f_0 , $V_R = V_{MAX} = V_s$
 IN REGION I, $X_C > X_L$
 $X = X_C + X_L < 0$

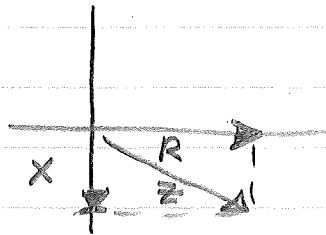

CIRCUIT IS
"CAPACITIVE"

IN REGION II, $X_C < X_L$
 $X = X_C + X_L > 0$

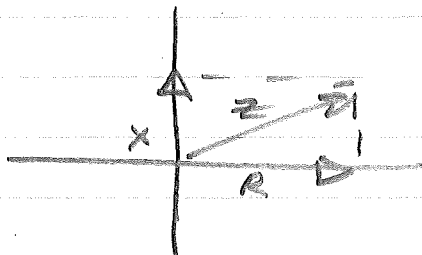

CIRCUIT IS
"INDUCTIVE"

POWER CALCULATIONS

A. ACTIVE & REACTIVE POWER

1. RESISTOR

$$\Rightarrow P = Vi$$

$$V = iR \Rightarrow P_R = i^2 R = \frac{V^2}{R}$$

FOR PERIODIC i , V IS ALSO PERIODIC, AS IS P . CONSIDER AVERAGE POWER FROM PERIODIC CURRENT:

$$\begin{aligned} P_R &= \frac{1}{T} \int_T P(t) dt \\ &= \frac{R}{T} \int_T i^2(t) dt \\ &= R \left[\sqrt{\frac{1}{T} \int_T i^2(t) dt} \right]^2 \\ &= R i_{RMS}^2 \end{aligned}$$

NOTE: AVERAGE POWER IS GIVEN BY RMS VOLTAGE.

FOR $i(t) = I_0 \cos(2\pi ft + \phi)$, WE SHOWED IN HOMEWORK THAT

$$\begin{aligned} i_{RMS} &= \frac{I_0}{\sqrt{2}} \\ \Rightarrow P_R &= \frac{1}{2} R I_0^2 \end{aligned}$$

SINCE $V_{RMS} = R i_{RMS}$
 $P_R = \frac{V_{RMS}^2}{R}$

FOR SINUSOIDAL VOLTAGE, $V_{RMS} = \frac{V_0}{\sqrt{2}}$
 $\Rightarrow P_R = \frac{V_0^2}{2R} = \frac{1}{2} G V_0^2$

P_R MEASURED IN WATTS

2. REACTIVE POWER (AVERAGE)

$$P_x = I_{RMS}^2 X = \frac{V_{RMS}^2}{X} \quad (\text{VOLT-AMPS-REACTIVE})$$

$$\text{FOR CAPACITOR: } X_C = \frac{1}{\omega C}$$

$$\text{" INDUCTOR: } X_L = \omega L$$

REACTIVE POWER MEASURED IN

B. POWER COMPUTATION

$$\begin{aligned} P_{AVE} &= V i = P_R + j P_x \Rightarrow \text{VOLT-AMPS} = \text{WATTS} + j \\ &= [V_{RMS} e^{j\phi_v}] [I_{RMS} e^{j\phi_i}] \\ &= V_{RMS} I_{RMS} e^{j(\phi_v + \phi_i)} \end{aligned}$$


$$\text{LET } \theta = \phi_v + \phi_i$$

$$\Rightarrow P_R + j P_x = V_{RMS} I_{RMS} e^{j\theta}$$

THUS

$$P_R = V_{RMS} I_{RMS} \cos \theta$$

$$P_x = V_{RMS} I_{RMS} \sin \theta$$

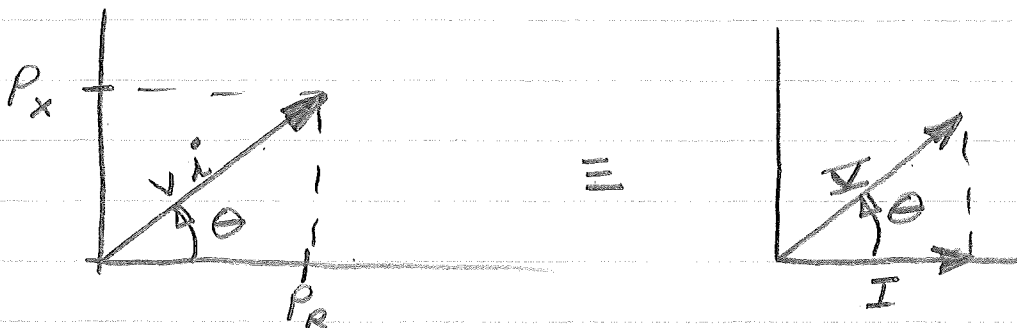

$\cos \theta \equiv \text{POWER FACTOR}$

$\sin \theta \equiv \text{REACTIVE FACTOR}$


Note: SINCE $V = Z i = [|Z| \angle \theta] I$,
THE "ANGLE" OF THE IMPEDANCE
CAN ALSO GIVE THE POWER
FACTOR.

C. POWER FACTOR CORRECTION

FOR A GIVEN VI , THE MAXIMUM ACTIVE (USEFUL) POWER IS

$P_{X_{MAX}} = VI$. IT COSTS MONEY TO MAKE V & I , THUS, WE'D LIKE TO MAXIMIZE OUR USEFUL POWER. WE MAY DO THIS BY MAKING ALL REACTANCES CANCEL (ie, IMPOSE RESONANCE)

EXAMPLE:

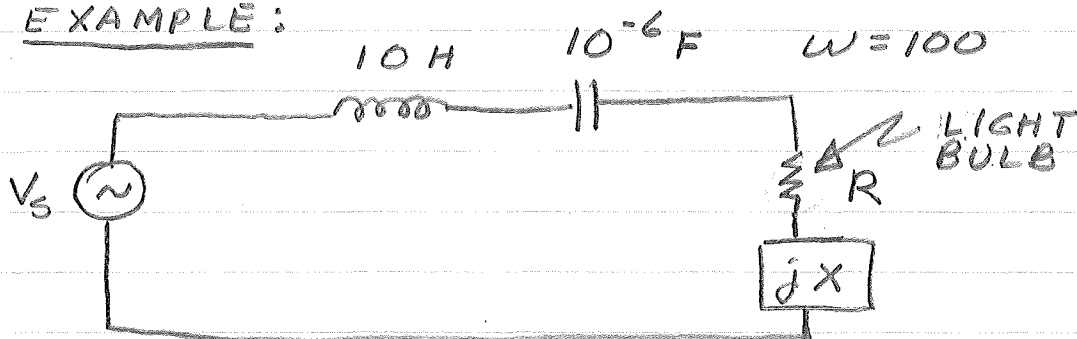

FIND jX TO MAXIMIZE PWR. TO LITE BULB.

WHAT VALUE OF L OR C IS REQUIRED?

SOLN:

SET THE TOTAL CIRCUIT REACTANCE TO 0:


$$0 = X_L + X_C + X = (10)(100) - \frac{(100)(10^{-6})}{X} + X$$

$$= 10^3 - 10^4 + X = -9000 + X$$

THUS: $X = 9000$

SINCE $X > 0$, WE USE INDUCTOR:
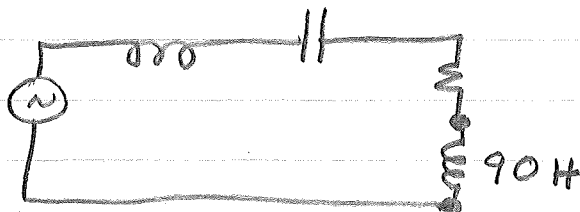
$$X = \omega L \Rightarrow 9000 = 100 L \Rightarrow L = 90 H$$




- 72
- (15) COMPLEX ARITHMETIC
 - (15) SINUSOIDS, EXPONENTIALS, PHASORS
 - (20) RMS, AVG, AND PEAK TO PEAK
 - MEASURES OF PERIODIC WAVEFORMS
 - (20) 4 NUCCAL PROBLEMS
 - (20) RESONANCE
 - (20) PHASOR PROBLEM
 - IMPEDANCE REDUCTION


FREQUENCY RESPONSE

THE MANNER IN WHICH A CIRCUIT IN S.S.S. PERFORMS IS DEPENDENT ON THE CIRCUIT'S FREQUENCY. "FREQUENCY RESPONSE" REFERS TO A CIRCUIT'S PERFORMANCE AS A FUNCTION OF FREQUENCY.

A SIMPLE "FILTER"

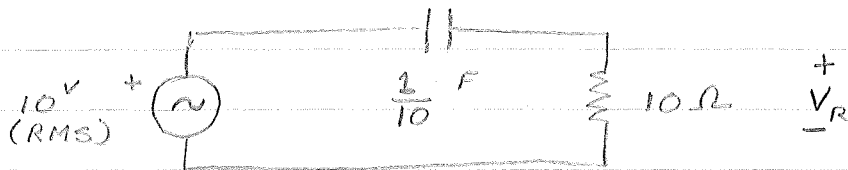

FIND V_R AS A FUNCTION OF FREQ

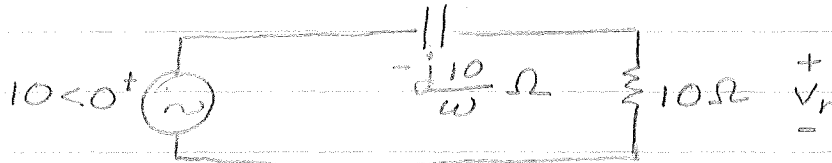

USE VOLTAGE DIVIDER:


$$V_r = \frac{10 \angle 0^\circ}{-j\frac{10}{\omega} + 10} \cdot 10 = \frac{10}{1 - (j/\omega)}$$

$$|V_r| = \frac{10}{\sqrt{1 + 1/\omega^2}}$$

LET'S SKETCH THE CURVE;

$$D.C. \Rightarrow |V_r|_{\omega=0} = \frac{10}{\sqrt{1+1/0^2}} = \frac{10}{\sqrt{\infty}} = 0$$



$$|V_r|_{\omega=\infty} = \frac{10}{\sqrt{1+1/\infty^2}} = 10 \text{ V}$$

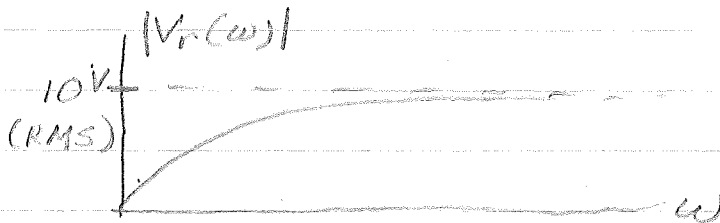

THE CIRCUIT IS A
"HIGH PASS FILTER"

SINCE HI FREQ'S ARE
PASSED BETTER THAN
LOW FREQUENCIES

CONSIDER MORE GENERAL CIRCUIT;

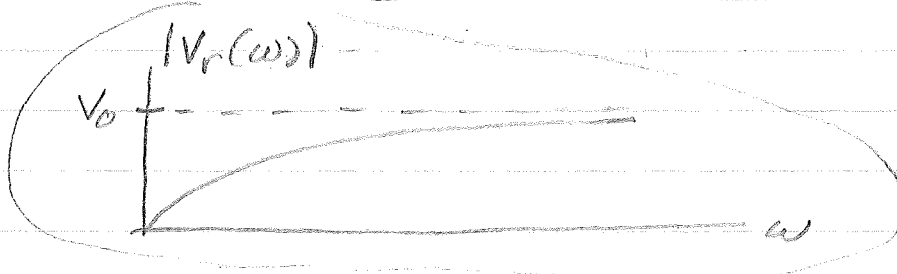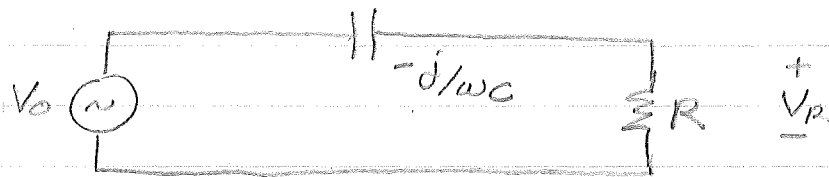

HOMEWORK: SHOW THAT

$$|V_r(\omega)| = \frac{V_0}{\sqrt{1 + (\omega RC)^2}}$$

OBVIOUSLY, $|V_r(0)| = 0$ AND $|V_r(\infty)| = V_0$
THE MANNER IN WHICH $|V_r(\omega)|$
GOES FROM 0 TO V_0 IS DETER.
BY THE PRODUCT, RC .

NOW

$$P_{AVE} = \frac{|V_r|^2}{R}$$

THE MAXIMUM POWER IS WHEN $|V_r|$ IS MAX, WHICH IS @ $\omega = \infty$

$$P_{MAX} = \frac{|V_{RMAX}|^2}{R} = \frac{|V_0|^2}{R}$$

CONSIDER HALF POWER POINT:



$$P_{1/2} = \frac{1}{2} P_{MAX} = \frac{|V_0|^2}{2R} = \frac{1}{R} \left| \frac{V_0}{\sqrt{2}} \right|^2$$

NOW


$$|V_r(\omega)| = \frac{V_0}{\sqrt{1 + (\frac{1}{\omega RC})^2}}$$

$$|V_r(\frac{1}{RC})| = \frac{V_0}{\sqrt{2}}$$

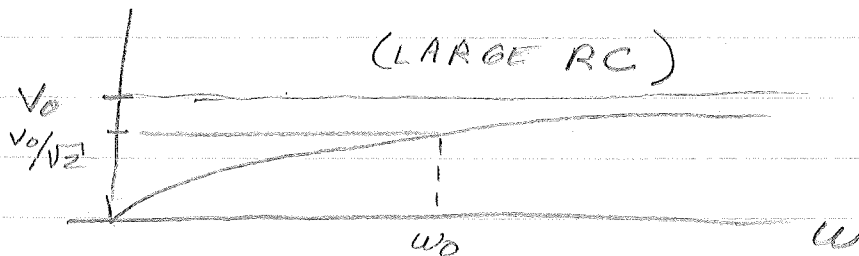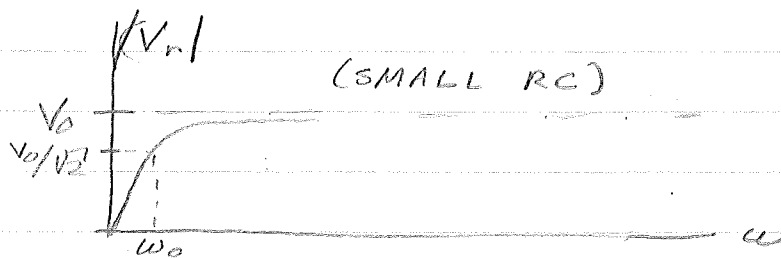
THUS, AT $\omega_0 = \frac{1}{RC}$, WE ARE AT THE "HALF POWER" POINT



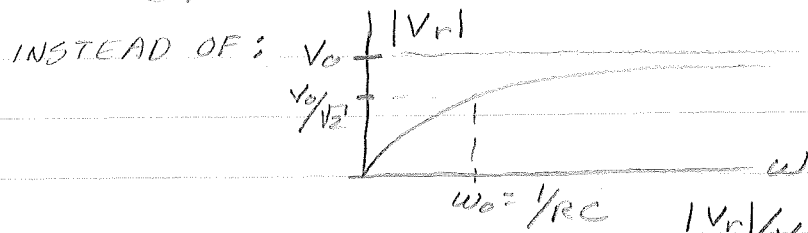
NORMALLY, FREQUENCY RESPONSES ARE EXPRESSED IN UNITLESS QUANTITIES BY NORMALIZING THE VARIABLE MEASURED QUANTITY BY THE MAXIMUM MEASURED QUANTITY:



WE SKETCH:

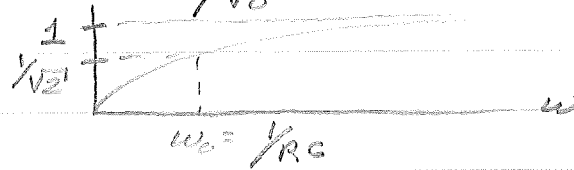

EXAMPLE:

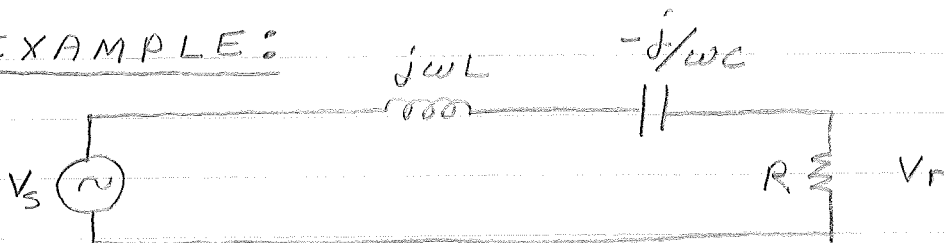

BY VOLTAGE DIVIDER:

$$V_r = \frac{R V_s}{j\omega L - j/\omega C + R} = \frac{V_s}{1 + \frac{j}{R}(\omega L - \frac{1}{\omega C})}$$

THUS:


$$\frac{V_r}{V_s} = \frac{1}{1 + \frac{j}{R}(\omega L - \frac{1}{\omega C})}$$

$$\frac{|V_r|}{V_s} = \frac{1}{\sqrt{1 + \frac{(\omega L - 1/\omega C)^2}{R^2}}}$$

LET'S SKETCH THE CURVE:

$$|V_r|/V_s \Big|_{\omega=0} = 0 = |V_r|/V_s \Big|_{\omega=\infty}$$

FROM PREVIOUS CONSIDERATIONS,
 $|V_r|$ WILL BE MAXIMUM WHEN $L \frac{1}{C}$
 ARE IN RESONANCE, ^($\omega = \frac{1}{\sqrt{LC}}$) AT WHICH
 TIME, $V_r = V_0 \Rightarrow |V_r|/V_0 = 1$

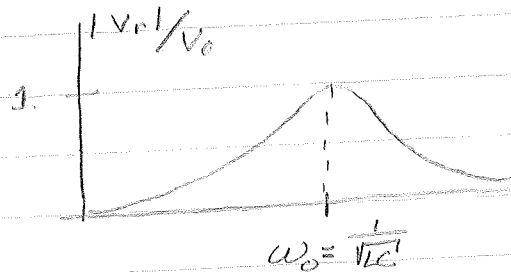

THIS IS A "BAND-PASS"

FILTER \Rightarrow IT PASSES
 FREQUENCIES BEST
 AROUND THE BAND
 OF FREQUENCIES
 ABOUT ω_0

HALF POWER POINTS ARE AT
 $|V_r|/V_0 = \frac{1}{\sqrt{2}}$. FROM FORMULA, THIS
 OCCURS WHEN

$$\left(\omega L - \frac{1}{\omega C}\right)^2 = R^2$$

$$\omega L - R = \frac{1}{\omega C}$$


$$CL\omega^2 - CR\omega - 1 = 0$$

USE QUADRATIC FORMULA:


$$\frac{CR \pm \sqrt{R^2 C^2 + 4LC}}{2LC}$$

$$\omega = \frac{1}{2}$$

$$2LC$$

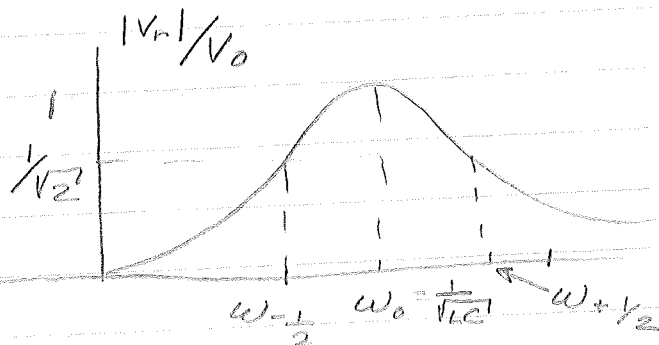

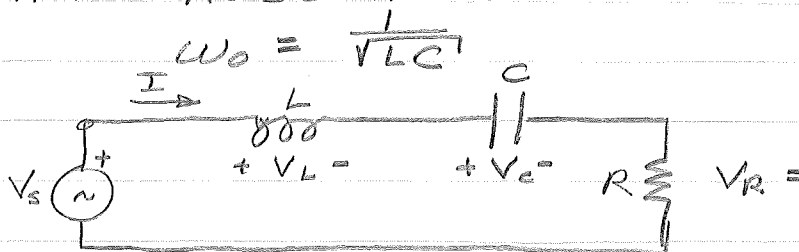THE QUALITY FACTOR
IN OUR SERIES RLC CIRCUIT, IT
IS POSSIBLE TO OBTAIN VOLTAGES
GREATER THAN THE SOURCE VOLTAGE.
AT RESONANCE




THEN, @ RESONANCE, $V_R = V_s$

$$I = I_0 = \frac{V}{R}$$

$$\Rightarrow V_L = j\omega_0 L I_0$$

$$V_C = \frac{-j I_0}{\omega_0 C}$$

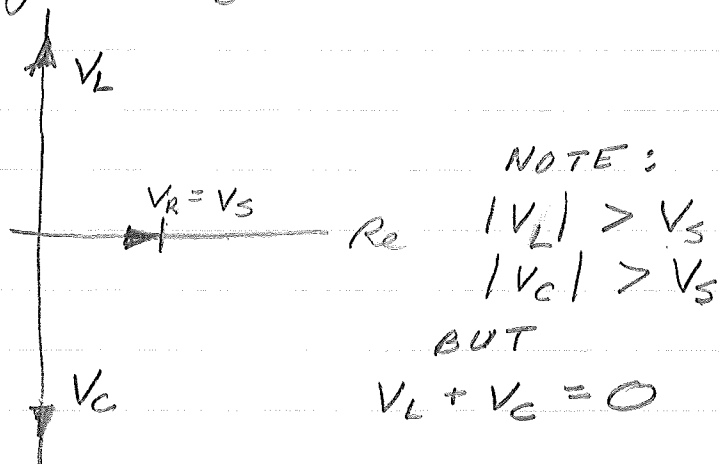

A MEASURE OF HOW MUCH HIGHER THE
C & L VOLTAGES CAN GO IS THE
QUALITY FACTOR, Q_0 AT RESONANCE

$$|V_L| = \omega_0 L I_0 = \omega_0 L |V| / R$$

$$\Rightarrow |V_L| / |V_s| = \omega_0 L / R$$

$$|V_C| = |I_0| / \omega_0 C = |V_s| / \omega_0 R C$$

$$\Rightarrow |V_C| / |V_s| = 1 / \omega_0 R C$$

BUT, AT RESONANCE, $|V_L| = |V_C|$


$$\Rightarrow \frac{|V_L|}{|V_S|} = \frac{|V_C|}{|V_S|}$$

OR

$$\frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R} = Q$$


NOTE: THIS IS Q ONLY FOR
THE SERIES RLC CIRCUIT
UNDER INSPECTION.

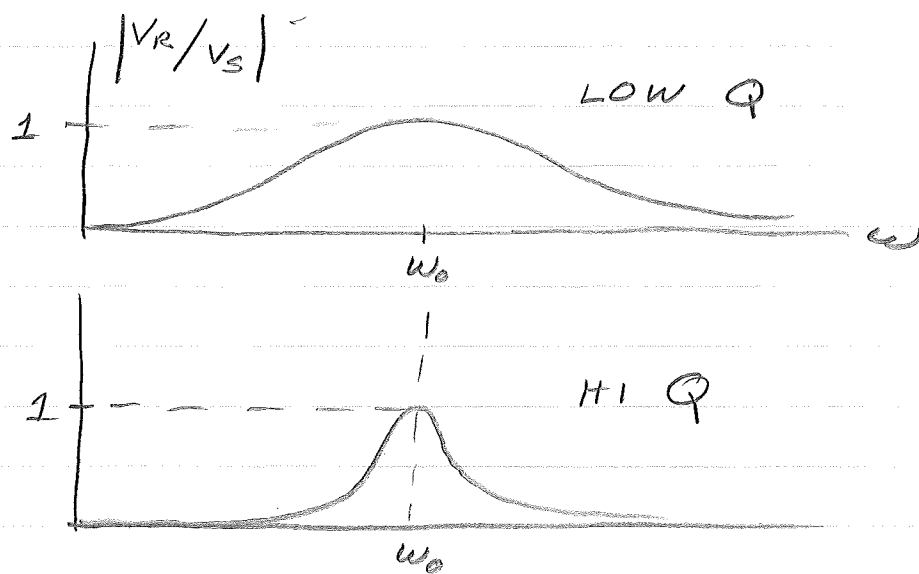THE Q ALSO IS A MEASURE
OF THE DISPERSION OF THE
FREQUENCY RESPONSE CURVES





A GENERAL VIEW OF FILTERS


1. LOW PASS

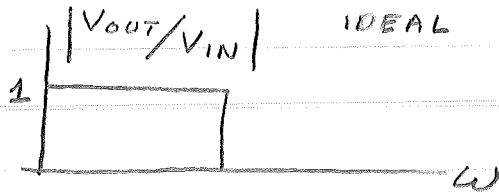



EXAMPLE

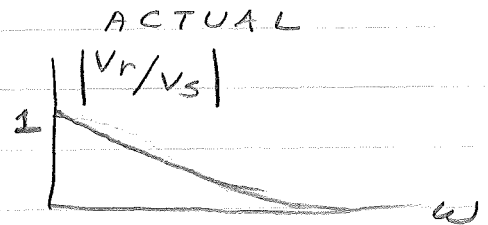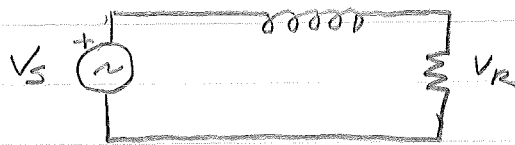

2. HI PASS

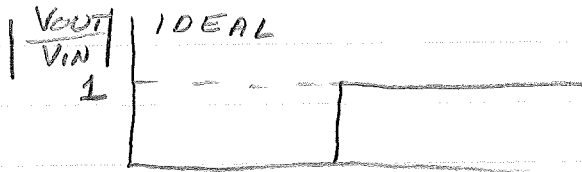



EXAMPLE

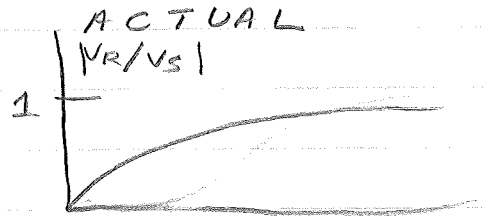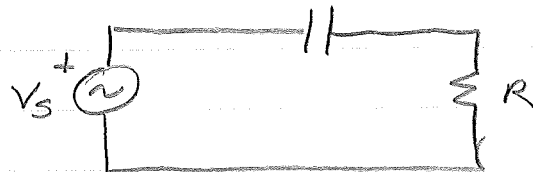


3. BAND PASS




EXAMPLE

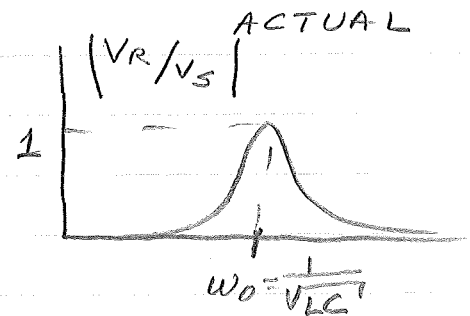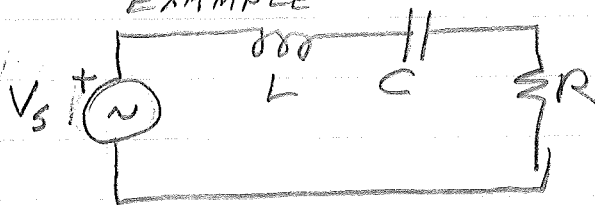


4. BAND STOP

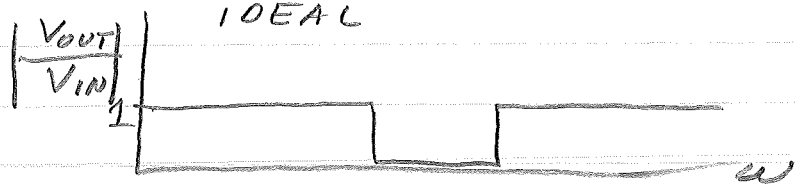

EXAMPLE

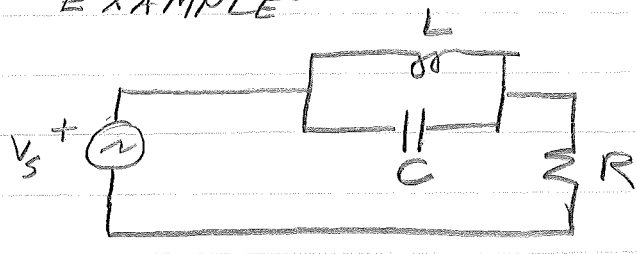

ACTUAL

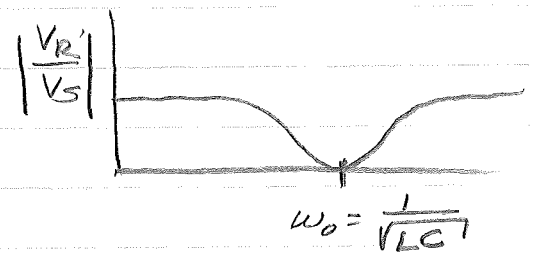

GENERALIZED THEVININ & NORTON THEOREMS

THEVININ: INsofar AS A LOAD IS CONCERNED, ANY ONE PORT NETWORK^{IN 555} CONSISTING OF OF LINEAR PASSIVE ELEMENTS MAY BE REPRESENTED BY A VOLTAGE SOURCE AND IN SERIES WITH AN IMPEDANCE:




AS BEFORE:

V_{OC} = OPEN CIRCUIT VOLTAGE

I_{SC} = SHORT CIRCUIT CURRENT

$$Z_{eq} = V_{OC} / -I_{SC}$$

EXAMPLE:

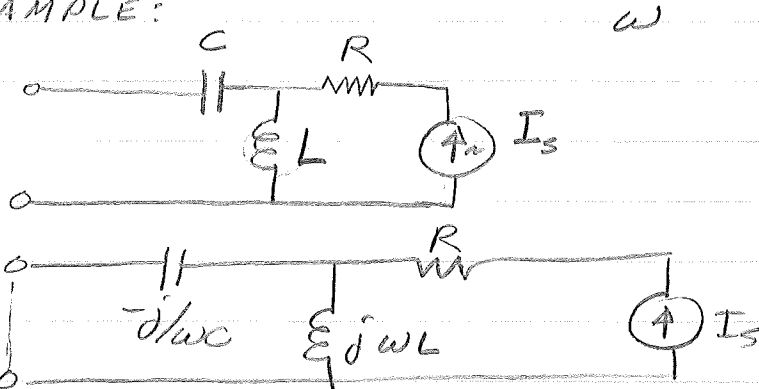


USE CURRENT DIVIDER:


$$I_{SC} = \frac{jwC}{jwC - j/wL} I_S = \frac{wC I_S}{wC - 1/wL} = \frac{w^2 LC I_S}{w^2 LC - 1}$$

$$\text{NOW } V_{OC} = jwL I_S \quad \text{OR} \quad \frac{-jwL I_S}{\left(\frac{w^2 LC I_S}{w^2 LC - 1} \right)} = \frac{-j(w^2 LC - 1)}{wC}$$

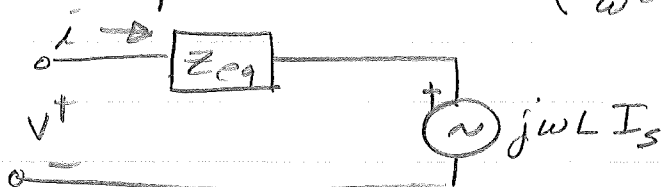
$$\Rightarrow Z_{eq} = V_{OC} / -I_{SC} = \frac{-j(w^2 LC - 1)}{wC}$$



NORTON'S EQUIVALENT FOLLOWS AS

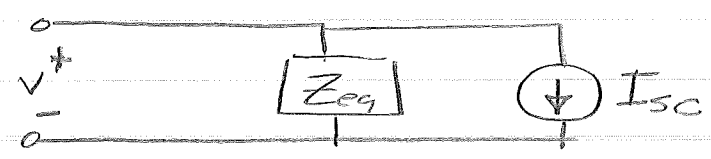


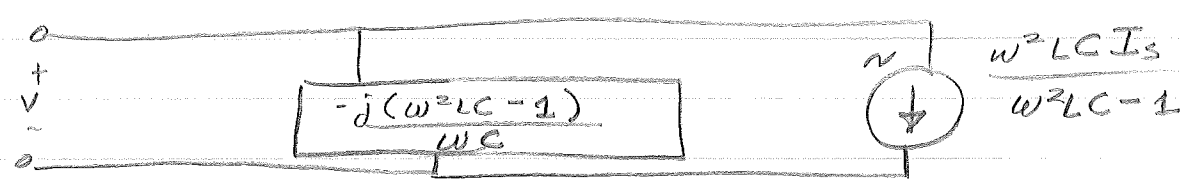
FOR PREVIOUS EXAMPLE, THE NORTON EQUIVALENT IS:



GENERALIZED SUPERPOSITION

BY FINDING THE VOLTAGE OR CURRENT DUE TO AN INDIVIDUAL SOURCE (SHORTING ALL OTHER V SUPPLIES & OPENING ALL OTHER I SUPPLIES), WE MAY FIND ^{THE} RESULTING ~~V~~ VOLTAGE OR CURRENT MAY BE FOUND FROM THE PHASER SUMS OF THE COMPONENTS.


EXAMPLE

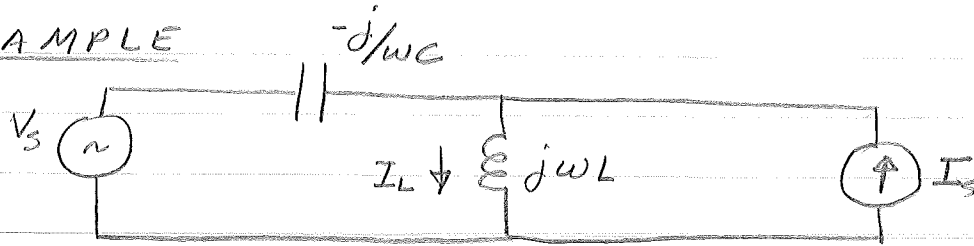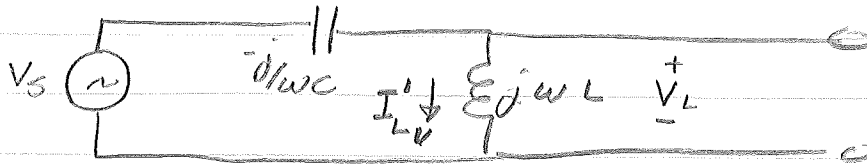FIND EFFECT OF V_s (OPEN I_s):

BY VOLTAGE DIVIDER

$$V_L = \frac{jwL}{jwL - j/wc} V_s = \frac{wL V_s}{wL - \frac{1}{wc}} = \frac{w^2 LC V_s}{w^2 LC - 1}$$

$$I_{L_V} = \frac{V_L}{jwL} = \frac{\frac{w^2 LC V_s}{w^2 LC - 1}}{jwL} = \frac{-jwC V_s}{w^2 LC - 1}$$

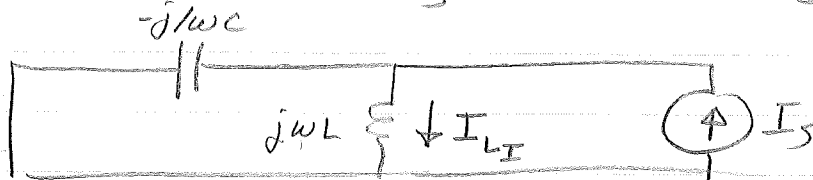FIND EFFECT OF I_s (SHORT V_s):


BY CURRENT DIVIDER

$$I_{L_I} = \frac{-j/wL I_s}{jwC - j/wL} = \frac{-1/wL I_s}{wC - 1/wL}$$

$$= \frac{-I_s}{w^2 LC - 1}$$

TOTAL CURRENT IS THEN

$$I_L = I_{L_V} + I_{L_I} = \frac{-1}{w^2 LC - 1} [+ I_s + jwC V_s]$$

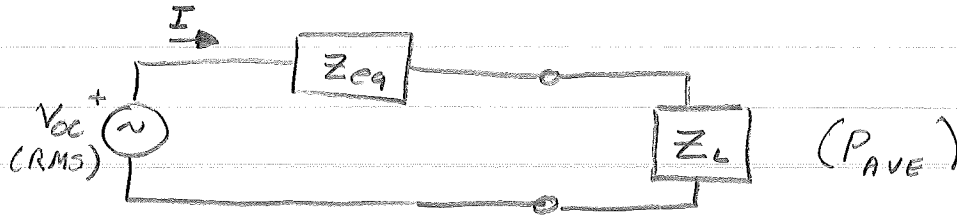MAXIMUM POWER TRANSFER

PROBLEM: GIVEN THE THEVININ EQUIVALENT CIRCUIT WITH V_{oc} AND Z_{eq} , FIND Z_L SUCH THAT THERE IS MAXIMUM ^(ACTIVE) POWER IS ASSOCIATED WITH THE LOAD.

SOLUTION: MAXIMIZE $P = |I|_{RMS}^2 R_{AVE}$ WHERE

$$Z_{eq} = R_{eq} + jX_{eq}$$

$$Z_L = R_L + jX_L$$

NOW
$$I = \frac{V_{oc}}{Z_{eq} + Z_L}$$

$$|I| = \frac{|V_{oc}|}{|Z_{eq} + Z_L|}$$

$$= \frac{|V_{oc}|}{|(R_{eq} + R_L) + j(X_{eq} + X_L)|}$$

$$= \frac{|V_{oc}|}{\sqrt{(R_{eq} + R_L)^2 + (X_{eq} + X_L)^2}}$$

THEN

$$P_{AVE} = |I|^2 R_L$$

$$= \frac{|V_{oc}|^2 R_L}{(R_{eq} + R_L)^2 + (X_{eq} + X_L)^2}$$

IN TERMS OF REACTANCE, P_{AVE} IS MAXIMUM WHEN $X_{eq} + X_L = 0$

$$\Rightarrow P_{AVE} = \frac{|V_o|^2 R_L}{(R_{eq} + R_L)^2}$$

NOTE: BY SETTING $X_{eq} + X_L = 0$, WE ARE SETTING CIRCUIT @ RESONANCE.

NOW:

$$\frac{d}{dR_L} P_{AVE} = \frac{(R_{eq} + R_L)^2 - 2(R_{eq} + R_L)R_L}{(R_{eq} + R_L)^4} |V_o|^2 = 0$$

SET NUM = 0 :


$$(R_{eq} + R_L)^2 - 2(R_{eq} + R_L)R_L = 0$$

SOLVING GIVES $R_L = R_{eq}$

SUMMARY: MAXIMUM POWER IS TRANSFERRED WHEN $R_L = R_{eq}$ AND $X_L = -X_{eq}$ OR

$$Z_L = R_{eq} - jX_{eq} = Z_{eq}^*$$

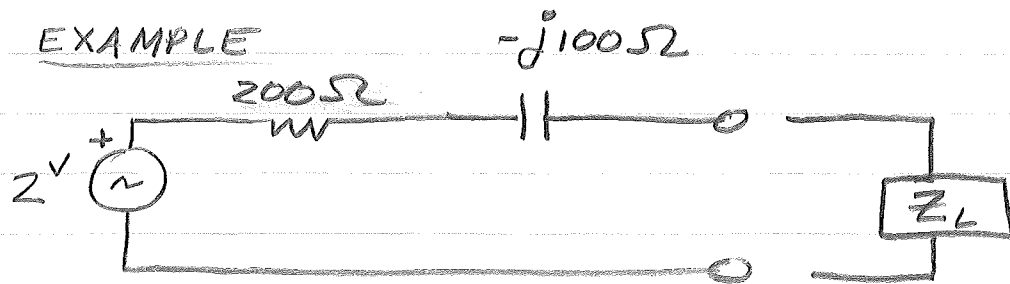(i.e., ^{WHEN} Z_L AND Z_{eq} ARE COMPLEX CONJUGATES)



$$Z_{eq} = 200 - j100$$

MAXIMUM POWER IS XFERED WHEN

$$Z_L = 200 + j100$$


TRANSFORMER (INDUCTIVE) COUPLING

FOR INDUCTOR: $V = L \frac{di}{dt}$

L IS "SELF INDUCTANCE"


ANOTHER TYPE OF INDUCTANCE IS

M = "MUTUAL INDUCTANCE"

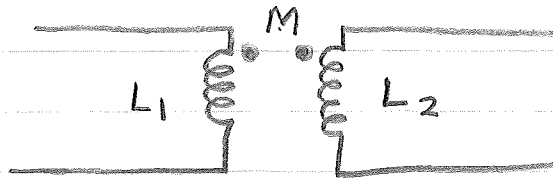


M IS DUE TO INTERACTION OF
MAGNETIC FIELD OF L_1 ON L_2
AND VISA VERSA.

"T" EQUIVALENT


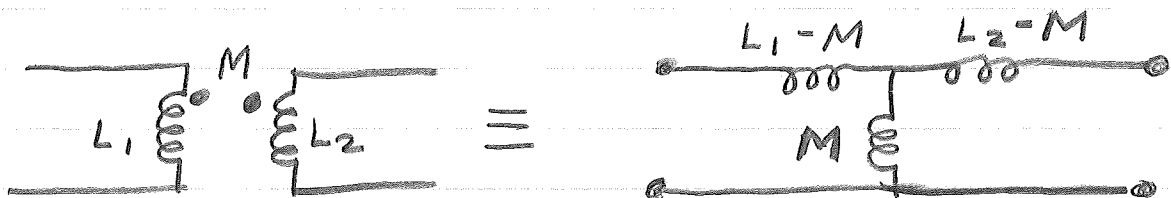


CIRCUITS OF THIS TYPE ARE
"TRANSFORMERS"


EXAMPLE

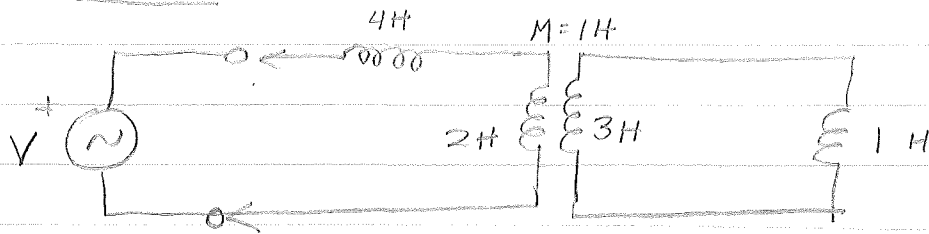

USE T EQUIVALENT

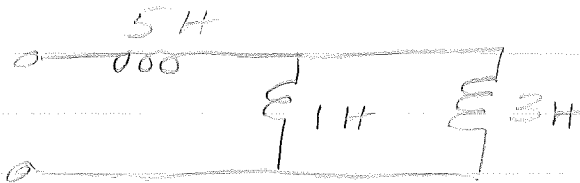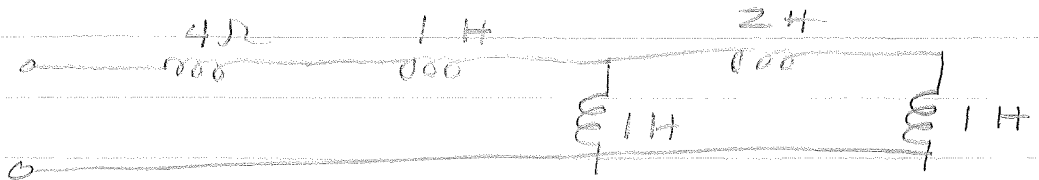
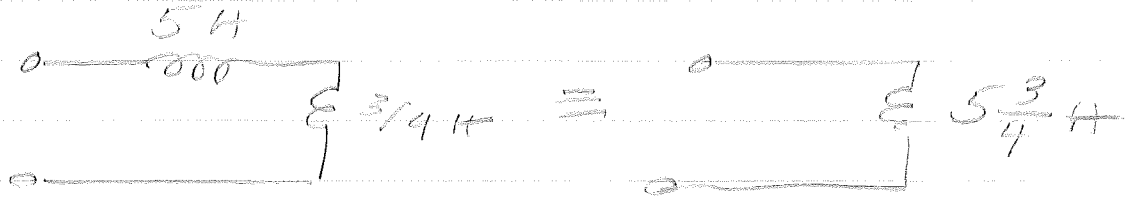
$$\frac{1}{L_{eq}} = \frac{1}{1} + \frac{1}{3} = \frac{4}{3} \Rightarrow L_{eq} = \frac{3}{4} H$$



k = COEFFICIENT OF COUPLING

= A MEASURE OF HOW WELL THE MAGNETIC FIELDS OF THE AN INDUCTOR INTERACT WITH THE OTHER INDUCTOR


$$-1 \leq k \leq 1$$

RELATION OF M & k :

$$M = k \sqrt{L_1 L_2}$$

NOTE THAT $|M| \leq \sqrt{L_1 L_2}$


EXAMPLE

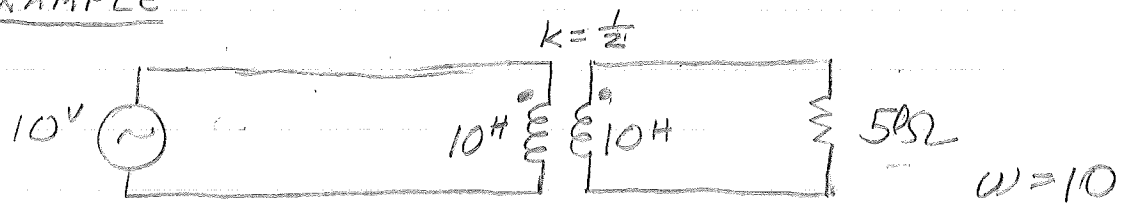


(a) FIND M

$$M = k \sqrt{L_1 L_2} = \frac{1}{2} \sqrt{10 \cdot 10} = 5 \text{ H}$$

(b) DRAW EQUIVALENT T CIRCUIT

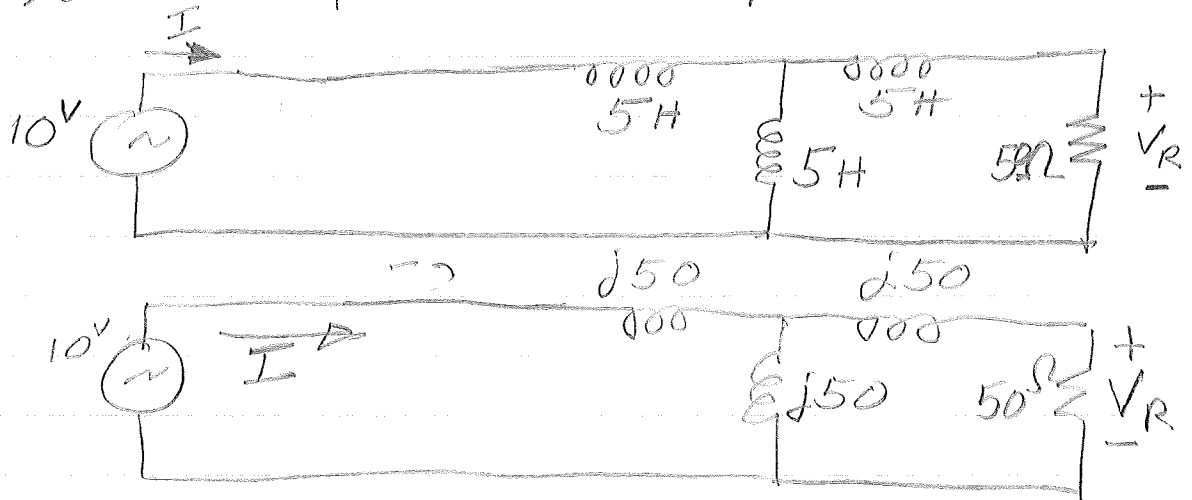

BACK TO ORIGINAL CIRCUIT

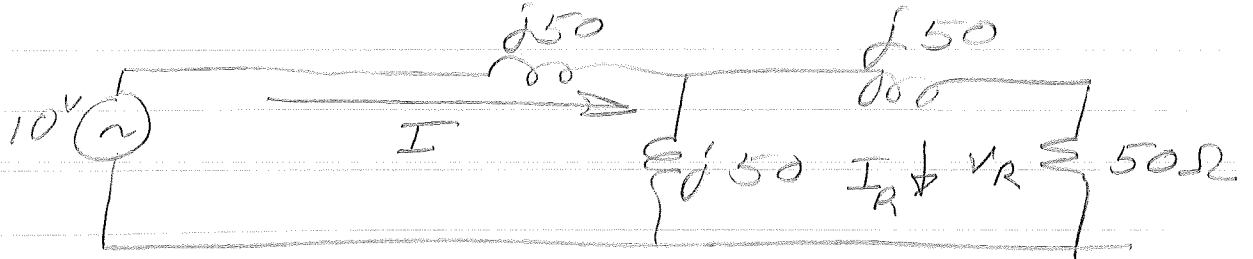

$$I = \frac{1-j8}{65}$$

USE CURRENT DIVIDER



$$\begin{aligned}
 I_R &= \frac{\frac{1}{50+j50}}{\frac{1}{50+j50} + \frac{1}{j50}} I \\
 &= \frac{j50}{j50 + (50+j50)} \frac{1-j8}{65} \\
 &= \frac{j50}{50+j100} \frac{1-j8}{65} \\
 &= \frac{j}{1+j2} \frac{1-j8}{65} \\
 &= \frac{8+j}{65} \frac{1}{1+j2} \frac{1-j2}{1-j2} \\
 &= \frac{8-j16+j+2}{5 \cdot 65} = \frac{10-j15}{5 \cdot 65}
 \end{aligned}$$

$$V_R = 50 I_R = \frac{100-j150}{65} \text{ VOLTS}$$

FIND I BY REDUCING Z


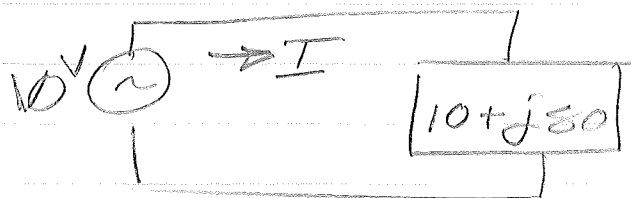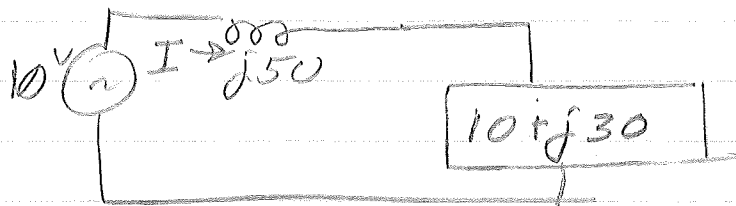
$$\begin{aligned} \frac{1}{Z_{eq}} &= \frac{1}{j50} + \frac{1}{50(1+j)} \\ &= \frac{1}{50} \left[\frac{1}{j} + \frac{1}{1+j} \right] \\ &= \frac{1}{50} \frac{1+2j}{j(1+j)} \\ \Rightarrow Z_{eq} &= 50 \frac{j(1+j)}{1+2j} \\ &= 50 \frac{-1+j}{1+j} \frac{(1-2j)}{(1-2j)} \\ &= \frac{50(-1+j^2+j+2)}{5} \\ &= 10(1+j3) \end{aligned}$$




$$I = \frac{V}{Z}$$

$$= \frac{10}{10(1+j8)} \cdot \frac{1-j8}{1-j8}$$

$$= \frac{1-j8}{65}$$

THE IDEAL TRANSFORMER: $k=1$

$$M = \sqrt{L_1 L_2}$$

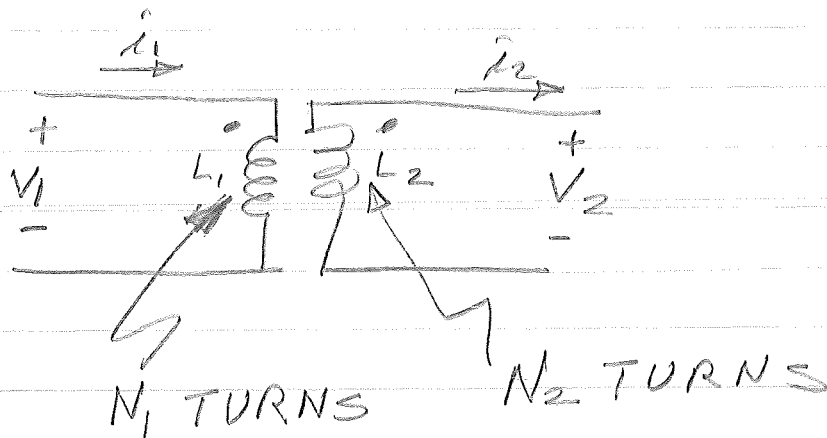


$$\frac{N_1}{N_2} = \text{TURNS RATIO}$$

$$\frac{L_1}{L_2} = \left(\frac{N_1}{N_2}\right)^2$$

$$\frac{V_1}{V_2} = \left(\frac{N_1}{N_2}\right)$$


$$\frac{i_1}{i_2} = \frac{1}{\left(\frac{N_1}{N_2}\right)} = \left(\frac{N_2}{N_1}\right)$$

EXAMPLE

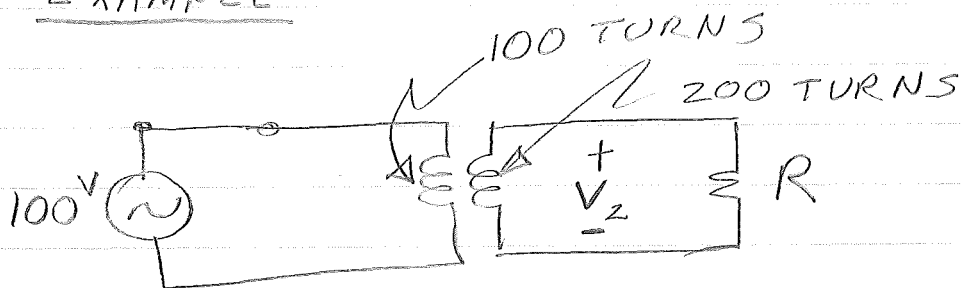


$$V_2 = \frac{N_2}{N_1} V_1 = \frac{200}{100} \times 100 = 200V$$

THE CATHODE RAY TUBE (CRT)

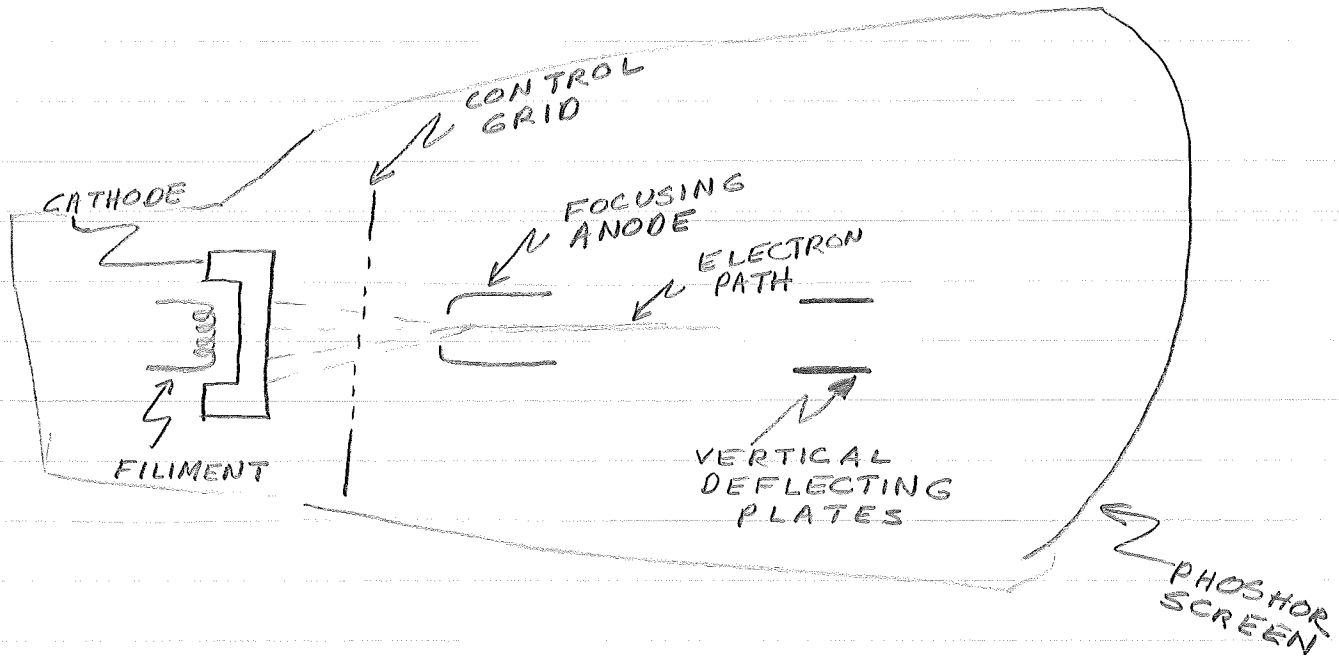

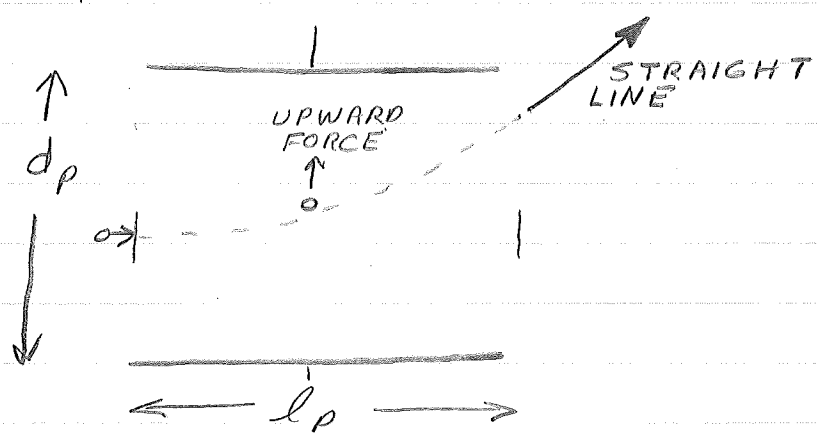ANODE - ACCERATES & FOCUSES BEAM
 HORIZONTAL DEFLECTION PLATES NOT SHOWN
 CONSIDER VERTICAL DEFL. PLATES



POTENTIAL ON PLATES
 BY CHANGING VOLTAGE ON PLATES,
 WE CAN CHOOSE THE POSITION OF
 THE DOT ON THE SCREEN.

USES OF CRT

1. VOLTAGE DISPLACEMENT: DISPLACEMENT ON SCREEN IS PROPORTIONAL TO APPLIED VOLTAGE




2. TIME MEASUREMENT

(APPLY SAWTOOTH)

3. WAVEFORM PLOTTING

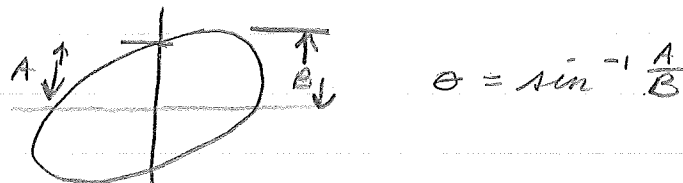
4. PHASE MEASUREMENTS (LISSAJOUS PATTERN)



5. FREQ. MEASUREMENTS


IDEAL DIODES

V-i CHARACTERISTIC

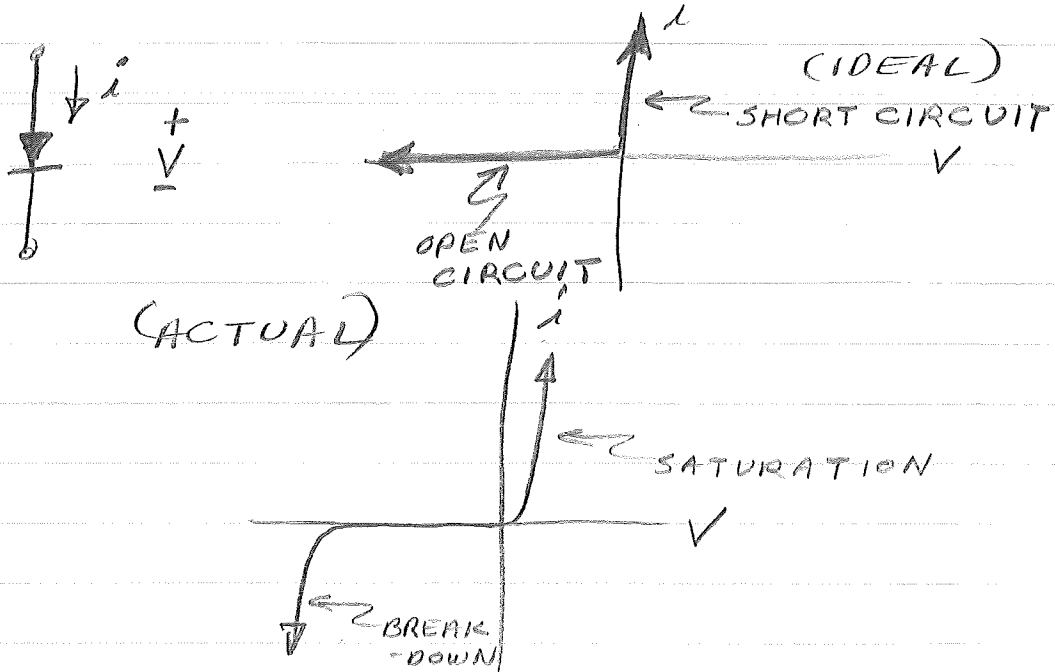

PHYSICAL DIODES

1. TUBE TYPES

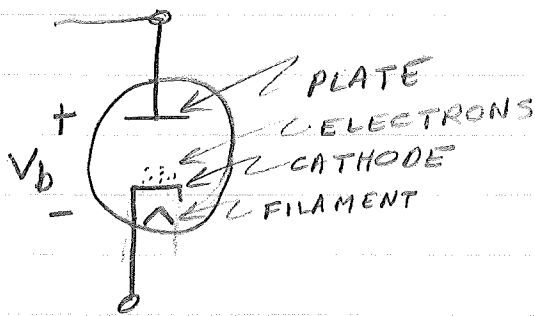


FILAMENT "BOILS OFF" ELECTRONS

IF $V_b > 0$, THE VOLTAGE OF THE PLATE IS $>$ THE CATHODE, AND

EL e^- ARE ATTRACTED. THUS, CONDUCTION, IF $V_b < 0$, EA PLATE WILL REPEL ELECTRONS \Rightarrow NO CONDUCTION.

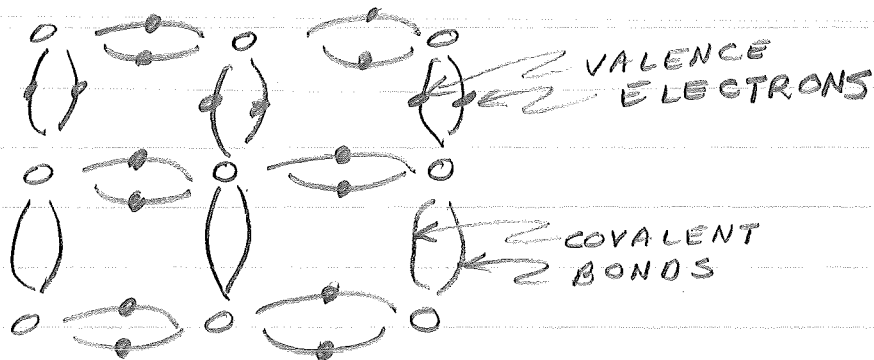
2. SEMICONDUCTOR DIODES

(USUALLY SILICON & GERMANIUM)
SILICON CRYSTAL (VALENCE = 4)



DOPED SEMICONDUCTORS (IMPURITY ATOMS ARE ADDED)

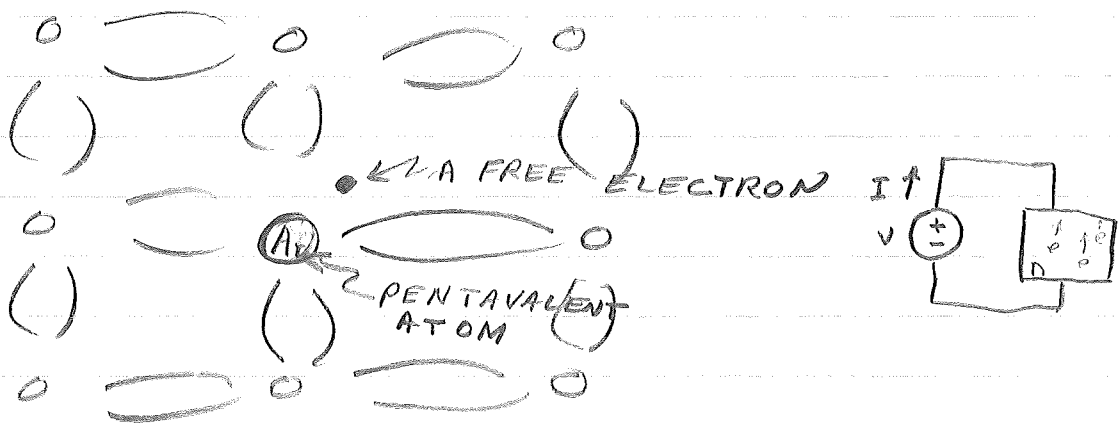
a. n -DOPING - THE IMPURITY HAS MORE VALENCE ELECTRONS
($5e \Rightarrow$ ANTIMONY, PHOSPHORUS, ARSENIC)



PENTAVALENT ATOMS ARE "DONORS"
THEY HAVE AN EXTRA ELECTRON
TO GIVE.

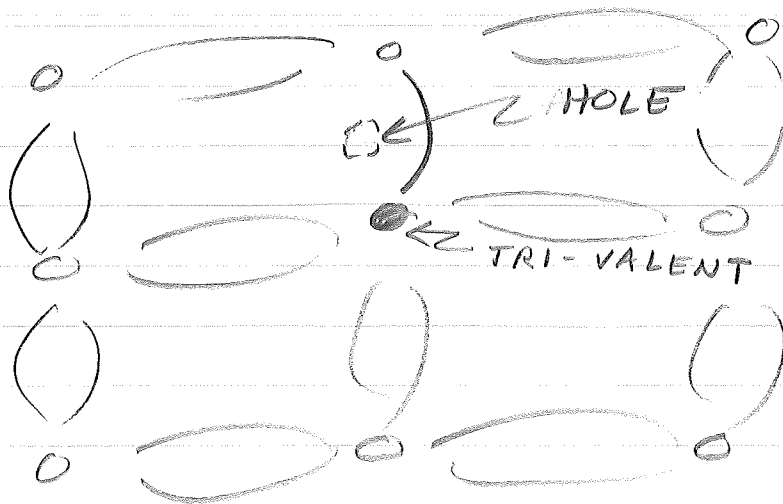b. p-DOPED SEMICONDUCTORS

TRI-VALENT ATOM \rightarrow 3 VALENCE e^-
(BORON, ALUMINUM, & GALLIUM)



A "HOLE" IS AN ABSENCE OF A BOND.
TRI-VALENT ATOMS ARE "ACCEPTORS"
SINCE THEY HAVE A HOLE
TO "ACCEPT" AN ELECTRON.





CONCEPT: JUST AS FREE ELECTRONS
CAN PRODUCE CURRENT, SO
CAN "FREE HOLES". THAT IS,
WE CAN SPEAK OF A "HOLE
CURRENT" JUST AS WE CAN
AN "ELECTRON" CURRENT



- 20 1. DOPED SEMICOND. AND/OR TUBE DIODES
- 20 2. MAXIMUM POWER XFER/ LOAD MATCHING
- 25 3. TRANSFORMERS
- 20 4. FREQUENCY RESPONSE
- 25 5. THREE PHASE

APPLIED VOLTAGE TO DOPED SEMICONDUCTORS


n DOPPED

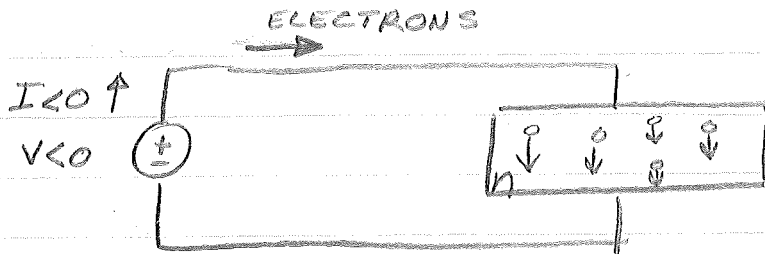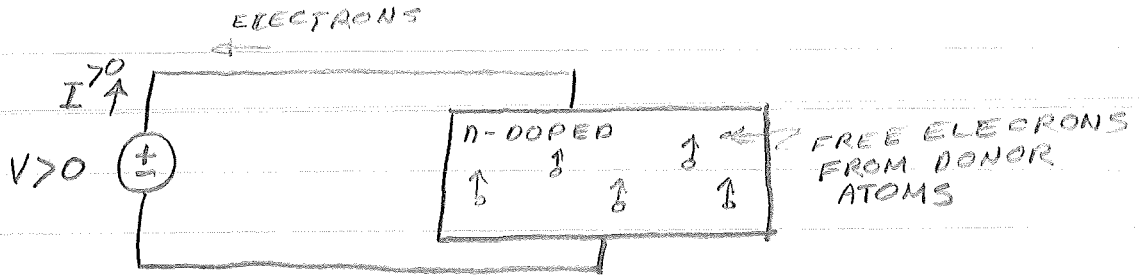


p DOPPED

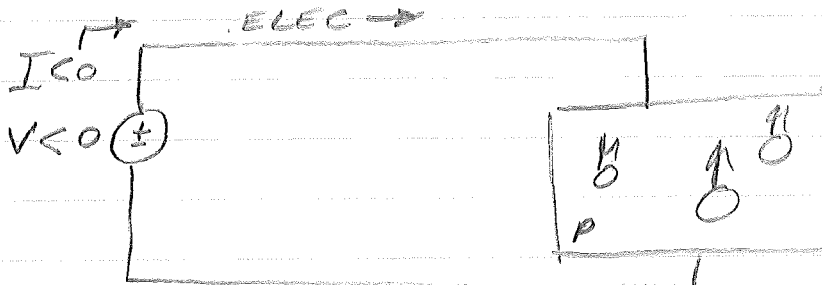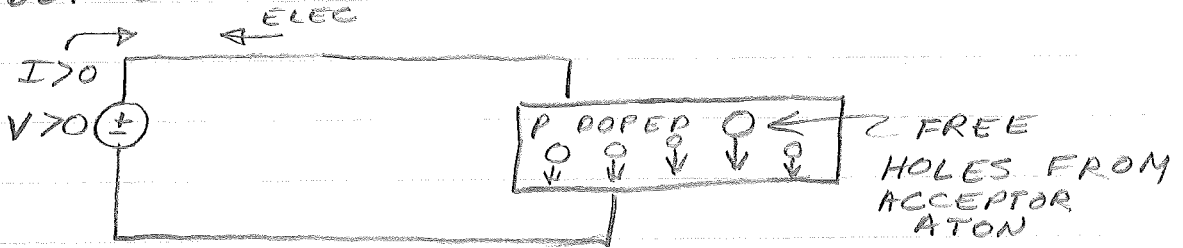

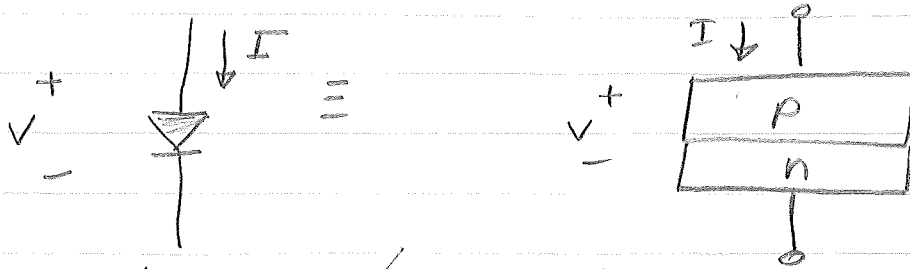A SEMICONDUCTOR DIODE IS FORMED WHEN A P-DOPED AND N DOPED SEMICONDUCTOR ARE PLACED BACK TO BACK, CALLED "P.N" JUNCTION




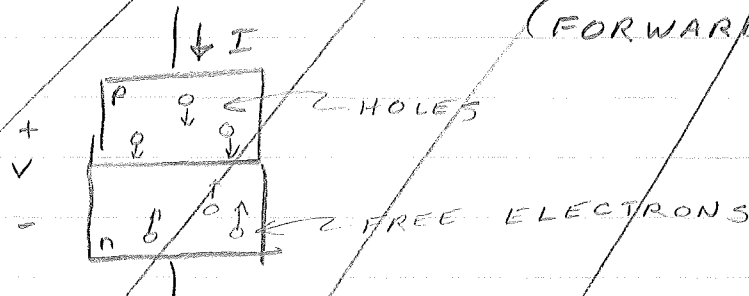SUPPOSE WE TRY TO MAKE $V > 0$ (FORWARD BIASED)



WE HAVE CONDUCTION AND THE DIODE ACTS AS A SHORT CIRCUIT


SUPPOSE $V < 0$ (REVERSE BIAS)

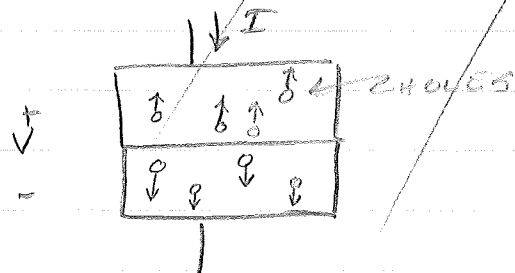


DIODE ACTS LIKE OPEN CIRCUIT

()

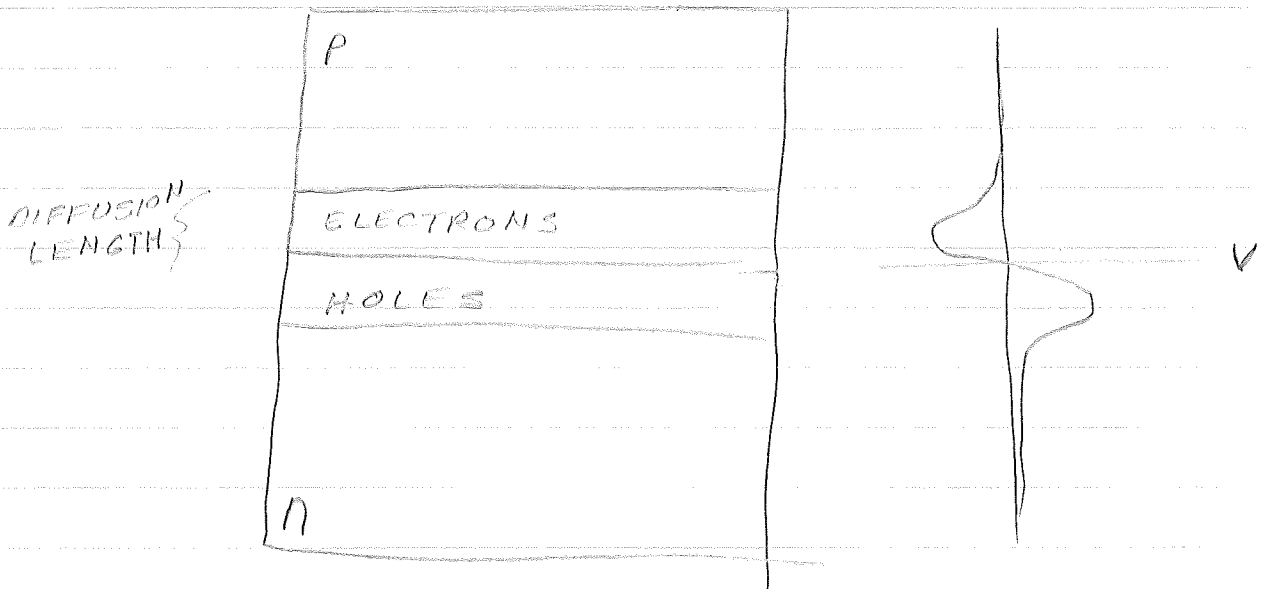AT ZERO VOLTS
AT A P-N JUNCTION, ^vSOME
OF THE FREE e'S FROM
THE N MATERIAL DIFFUSE
INTO P MATERIAL & SOME
HOLES INTO N MATERIAL:




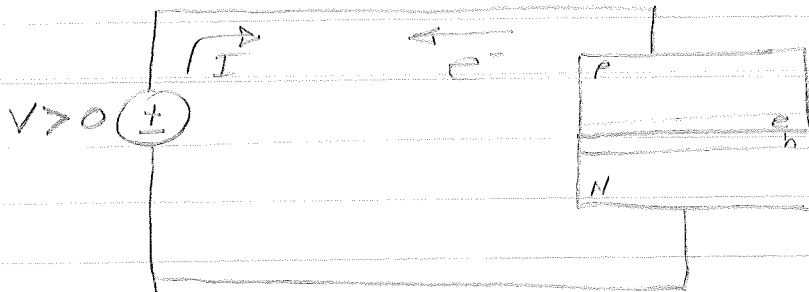(a) IF WE "FORWARD BIAS" THE DIODE, IT CONDUCTS (SHORT CIRCUIT)



THE ELECTRONS ARE "SUCKED" FROM THE DEPLETION REGION (AS ARE HOLES) AND WE HAVE CONDUCTION. NOTE THE DIFFUSION LENGTH DECREASES

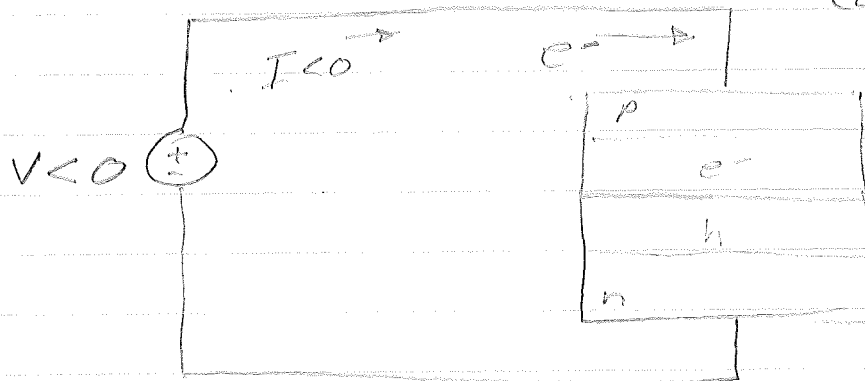
(b) IF WE "REVERSE BIAS" THE DIODE, IT DOESN'T CONDUCT (OPEN CIRCUIT)



MORE e^- 'S ARE SUPPLIED TO DEPLETION REGION IN P MATERIAL & MORE HOLES TO N REGION. DIFFUSION LENGTH INCREASES




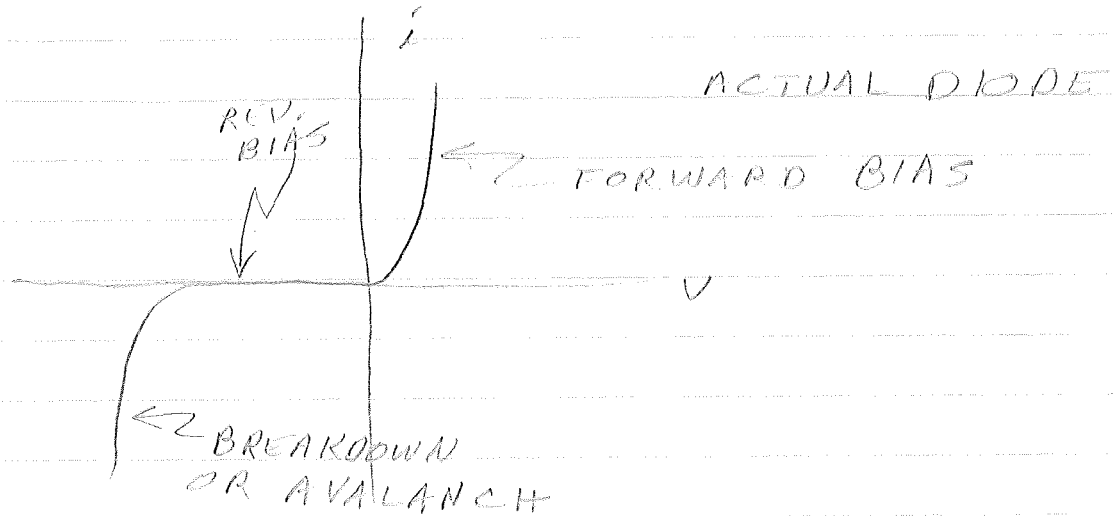IF WE REVERSE BIAS BIG ENOUGH, THE DIODE NO LONGER HAS BIG ENOUGH DEPLETION REGION AND WE AGAIN HAVE CONDUCTION. THIS IS CALLED "BREAKDOWN" OR "AVALANCH" EFFECT



DIODES IN CIRCUITS


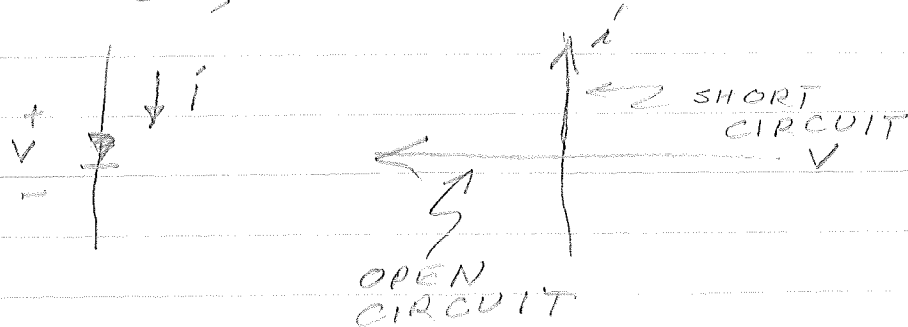
FOR (FIRST ORDER) CIRCUIT ANALYSIS, WE USE IDEAL DIODES:



THE DIODE IS NON-LINEAR, THUS, ALL LINEAR LAWS NO LONGER APPLY (SUPERPOSITION, THEV & NORTON) LAWS WHICH STILL APPLY ARE KIRCHHOFFS LOOP AND NODE LAWS.

DIODES IN CIRCUITS

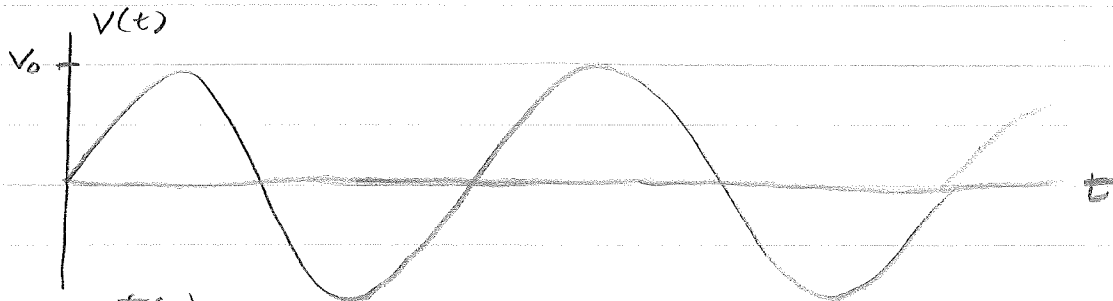
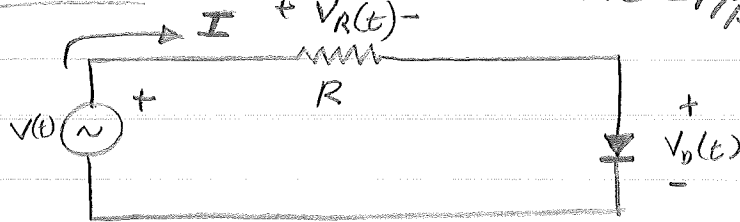
~~OHM'S LAWS STILL APPLY,~~
~~KIRCHHOFF'S LAWS STILL APPLY,~~ ~~THEY & NOT, DON'T~~
 CAN NO LONGER USE IMPEDANCE IDEAS
 EXAMPLE: HALF WAVE RECTIFIER




FIND $I(t)$

EITHER THE DIODE CONDUCTS OR IT DOESN'T.

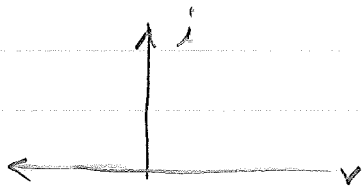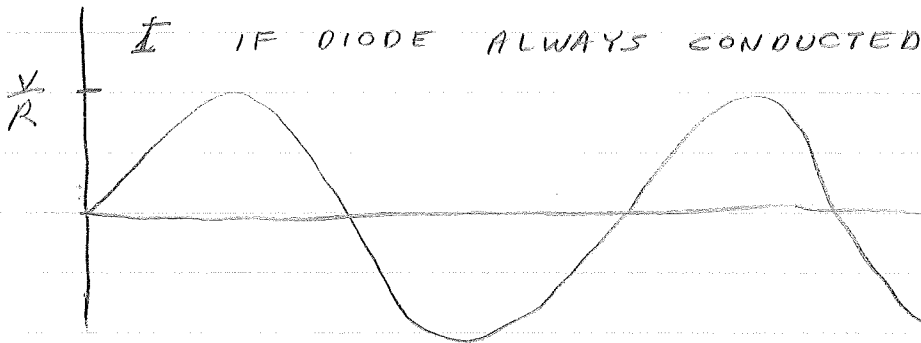IF IT DID CONDUCT ALWAYS, THEN $I = \frac{v}{R}$.




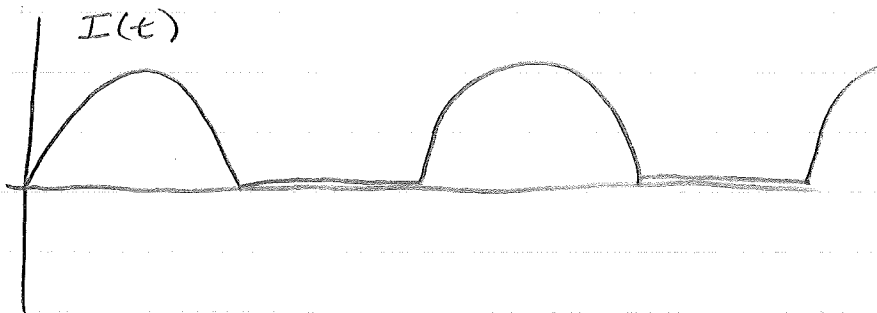BUT, FROM $v-i$ CURVE,
 i CANNOT BE NEGATIVE
 SO, OUR ANSWER IS




WHAT IS $V_D(t)$?

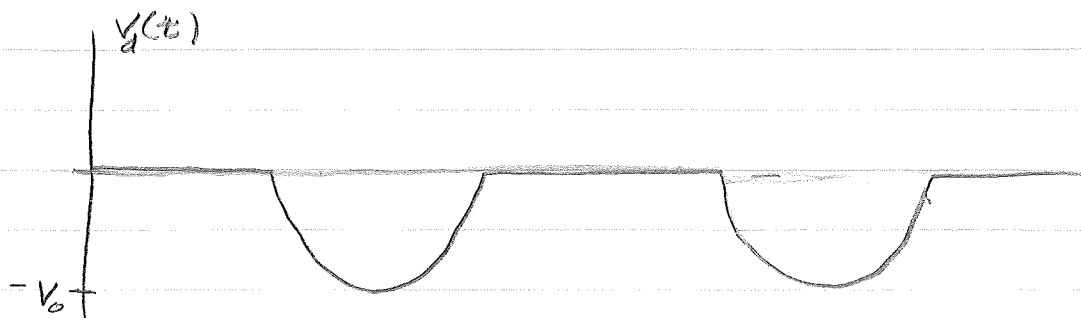WHEN DIODE CONDUCTS, IT IS A SHORT CIRCUIT, AND $V_D(t) = 0$. WHEN IT DOESN'T CONDUCT, THERE IS NO VOLTAGE ACROSS R. THUS, USING K'S LOOP RULE, $V_D(t) = V(t)$ WHEN DIODE ISN'T CONDUCTING:




WHAT IS $V_R(t)$? $V_R = V - V_D$

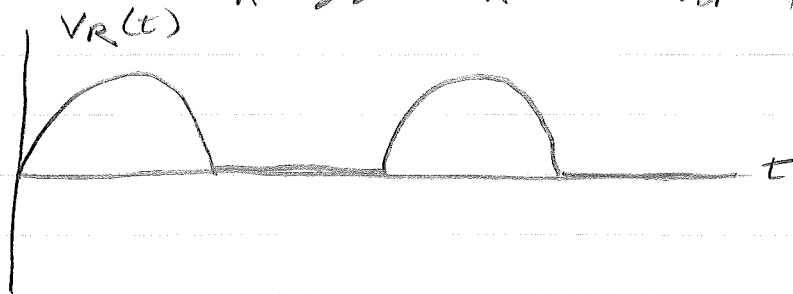


NOTE THAT $V(t) = V_D(t) + V_R(t)$

EXAMPLE

THE DIODE LIMITER

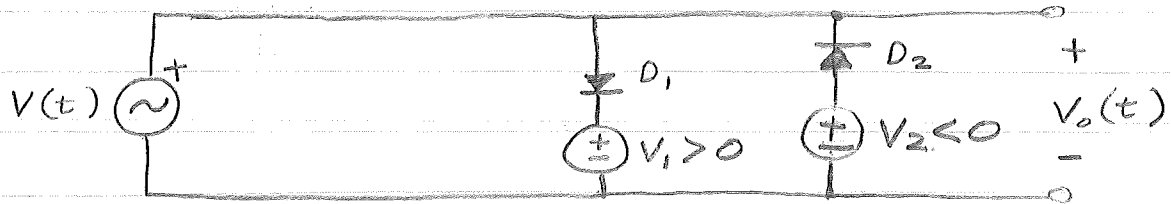


FIND $V_0(t)$

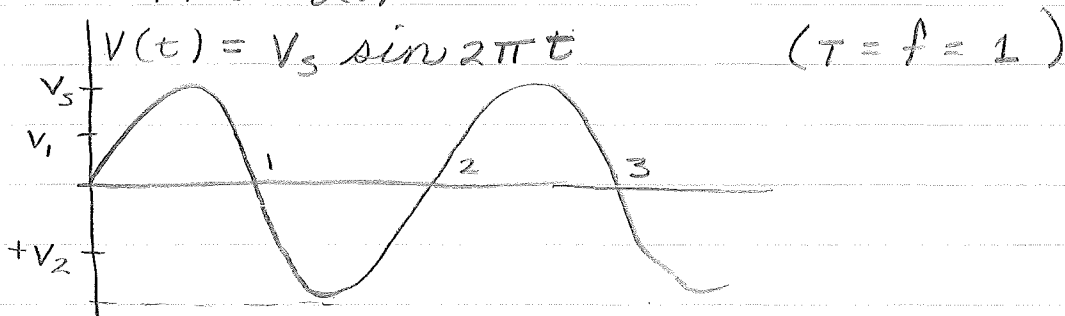

ASSUME $V_s > V_1$; $-V_s < V_2$

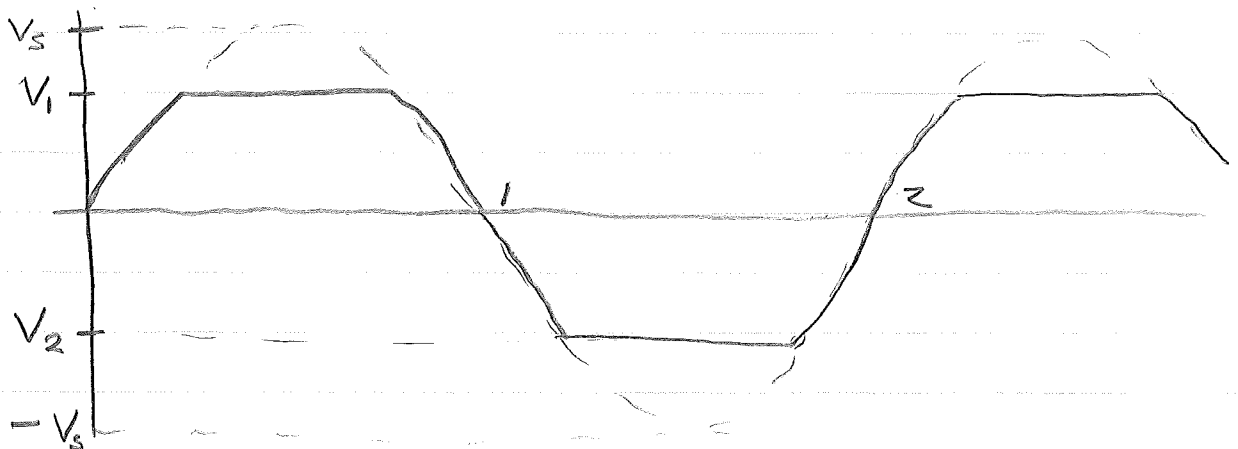- (a) WHEN $V(t) > V_1$, D_1 IS FORWARD BIASED (A SHORT CIRCUIT) AND $V_0(t) = V_1$
- (b) WHEN $V(t) < -V_2$, D_2 IS FORWARD BIASED AND $V_0(t) = V_2$
- (c) IN ALL OTHER CASES, D_1 AND D_2 ARE REVERSED BIASED (OPEN CIRCUITS) AND $V_0(t) = V(t)$



GRADING

40% 1. QUIZES

$$Q = \frac{\text{TOTAL POINTS ON THE THREE QUIZES}}{300}$$

20% 2. LAB

$$L = \text{LAB GRADE} \quad 0 < L < 1$$

10% 3. HOMEWORK

HW = TOTAL POINTS ON ALL REGULAR HOMEWORK

EC = EXTRA CREDIT POINTS

LHW = NUMBER OF LATE HOMEWORK PROBLEMS

THW = TOTAL HOMEWORK POINTS = 375

HWC = HOMEWORK COEFFICIENT

$$HWC = \frac{HW + \frac{5LHW}{THW}(THW - HW) + EC}{THW}$$

$$0 < HWC < 1 +$$

30% 4. FINAL

$$F = \frac{\text{TOTAL POINTS}}{250}$$

FINAL GRADE WILL BE DETERMINED BY

$$G = (0.4)Q + (0.2)L + (0.1)HW + (0.3)F$$

$$0 < G < 1 +$$

FINAL GRADES WILL BE ANALYTICALLY
(NOT SUBJECTIVELY) CURVED, BUT
WILL BE "CLOSE" TO

.9	1.0	A
.8	.9	B
.7	.8	C
.6	.7	D
<.6		F

FINAL (OPEN BOOK, PAPER SUPPLIED)

250 POINTS

(60PTS) 30 TRUE/FALSE QUESTIONS

(WITH A PENALTY FOR GUESSING)

7 PROBLEMS IN CIRCUIT ANALYSIS



(190 PTS)

SOME PROBLEMS WILL HAVE
EXTRANEIOUS UNNECESSARY INFO.

- DIODES

NO 3-PHASE

4 NUGGETS PROBLEM

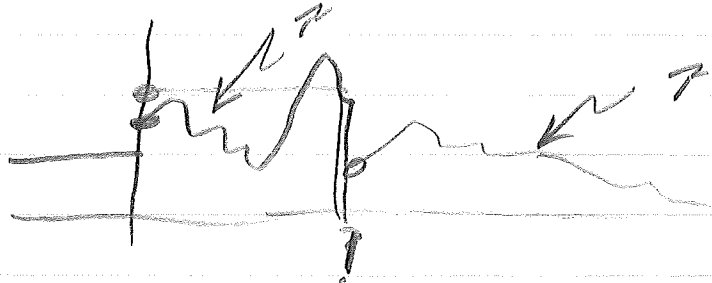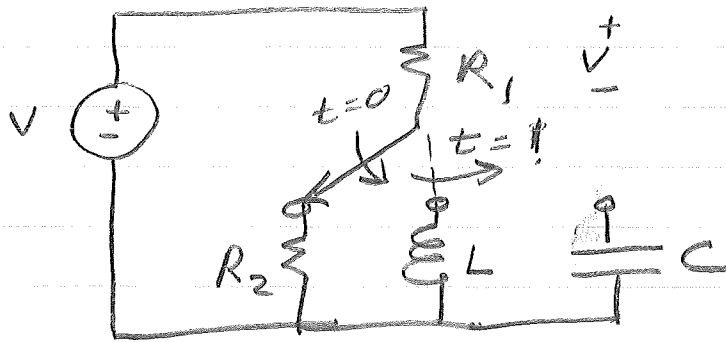


HOMEWORK

PROBLEMS	ASSIGNED	DUE
26: 2, 3, 5abcd	9/3/76	9/8/76
27: 12, 13, 15, 16	9/10/76	9/17/76

PROB. 7 & 57 ADD 5Ω & 4Ω

FIND i_2 USING BR. CURRENTS

FIND i_2 USING BRANCH CURRENTS

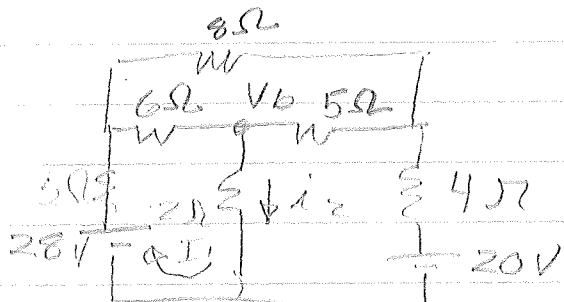



SOLVE CIRCUIT FOR i_2 BY LOOPS

V_D BY NODES

- 5. 57-58 # 12, 16, 17
- 58 18, ~~20~~, 24
- 84 11ace, 17, 18(a)
- 94 19(a,b) BY PHASORS
- 141 4b, ~~also find V_D~~
- 142 11, 16
- 143 24
- 144 #5 (SET UP METER) Nov. 1-2
- 204 # 25
- 202 202-3 #1, 4, 6 (11-9)
- PT 203- 11, 13
- 206- 38

0.27.

2)

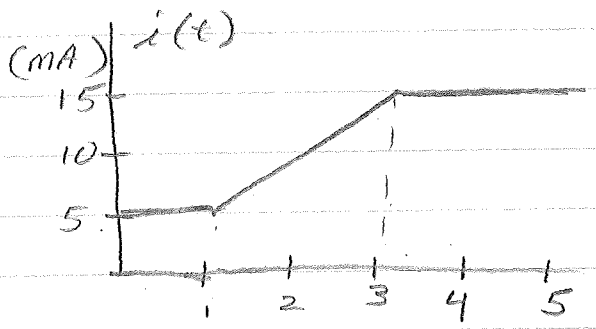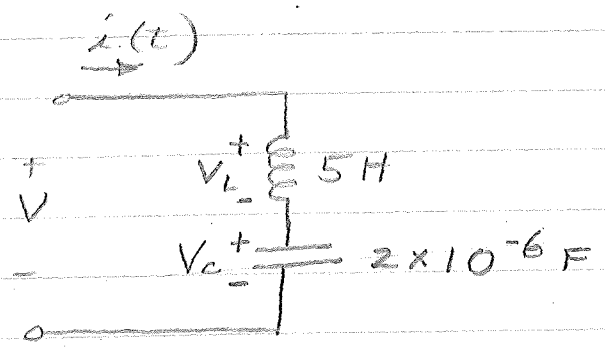


$$i(t) = \begin{cases} 0 & ; t < 0 \\ 5 \times 10^{-3} \text{ A} & ; 0 < t < 10^{-3} \\ 5t & ; 10^{-3} < t < 3 \times 10^{-3} \\ 15 \times 10^{-3} & ; t > 3 \times 10^{-3} \end{cases}$$

(NOTE: IN THIS EXPRESSION, WE ARE MEASURING t IN SECONDS AND i IN AMPS)

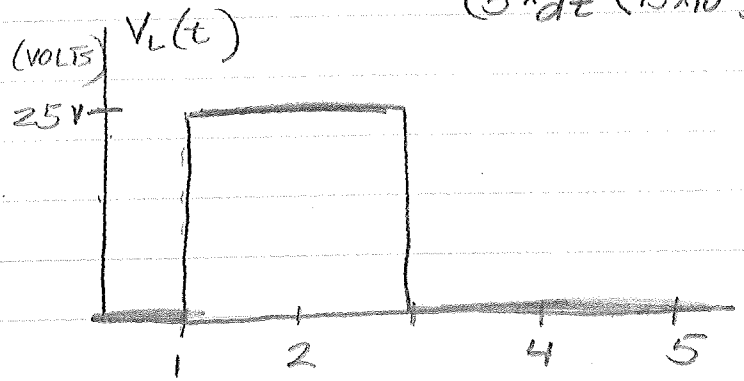1) FOR THE INDUCTOR

$$V_L = L \frac{di}{dt} = 5 \frac{di}{dt} = \begin{cases} 5 \times \frac{d}{dt}(0) = 0 & ; t < 0 \\ 5 \times \frac{d}{dt}(5 \times 10^{-3}) = 0 & ; 0 < t < 10^{-3} \\ 5 \times \frac{d}{dt}(5t) = 25 & ; 10^{-3} < t < 3 \times 10^{-3} \\ 5 \times \frac{d}{dt}(15 \times 10^{-3}) = 0 & ; t > 3 \times 10^{-3} \end{cases}$$



(b) FOR THE CAPACITOR

$$V_c = \frac{1}{t} \int_{-\infty}^t i dt = V(t_0) + \frac{1}{t} \int_{t_0}^t i dt$$
$$= V(t_0) + 5 \times 10^5 \int_{t_0}^t i dt$$

→ $0 < t < 10^{-3}$

WE ARE GIVEN THAT THE CAPACITOR IS

INITIALLY UNCHARGED $\Rightarrow V_c(t=0) = 0$

$$\Rightarrow V_c(t) = V_c(0) + 5 \times 10^5 \int_0^t (5 \times 10^{-3}) dt$$
$$= 2.5 \times 10^3 t$$

NOTE: $V_c(t = 10^{-3}) = 2.5$ VOLTS


→ $10^{-3} < t < 3 \times 10^{-3}$

$$V_c(t) = V_c(t = 10^{-3}) + 5 \times 10^5 \int_{10^{-3}}^t (5t) dt$$
$$= 2.5 + 2.5 \times 10^5 \cdot \frac{1}{2} t^2 \Big|_{10^{-3}}^t$$
$$= 2.5 + 12.5 \times 10^5 (t^2 - 10^{-6})$$
$$= 2.5 - 1.25 + 12.5 \times 10^5 t^2$$
$$= 1.25 + 12.5 \times 10^5 t^2$$

NOTE: $V_c(t = 3 \times 10^{-3}) = 12.5$ V

→ $t > 3 \times 10^{-3}$
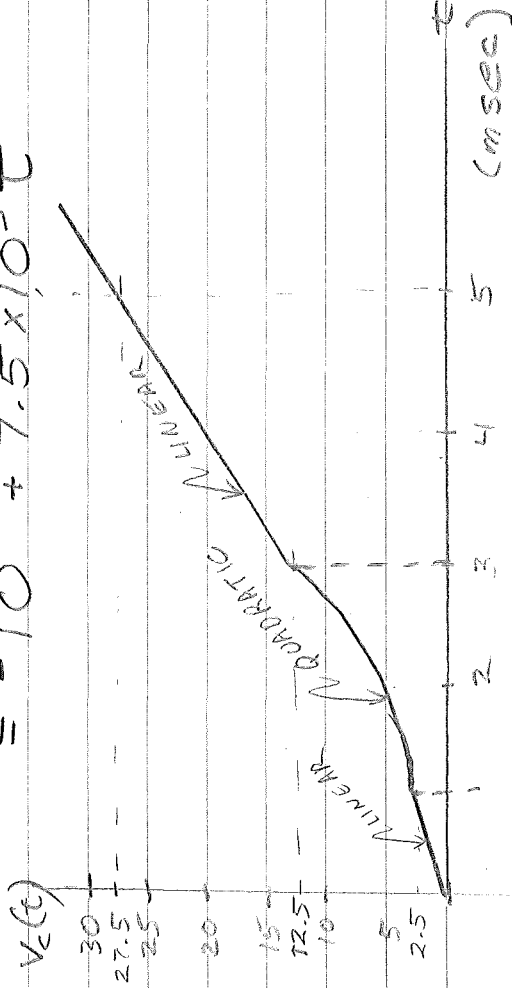
$$V_c(t) = V_c(t = 3 \times 10^{-3}) + 5 \times 10^5 \int_{3 \times 10^{-3}}^t (15 \times 10^{-3}) dt$$
$$= 12.5 + 75 \times 10^2 (t - 3 \times 10^{-3})$$
$$= 12.5 - 22.5 + 75 \times 10^3 t$$
$$= -10 + 7.5 \times 10^3 t$$



(b) FOR THE CAPACITOR

$$V_c = \frac{1}{C} \int_{-\infty}^t i dt = V(t_0) + \frac{1}{C} \int_{t_0}^t i dt$$

$$= V(t_0) + 5 \times 10^5 \int_{t_0}^t i dt$$

$$\rightarrow 0 < t < 10^{-3}$$

WE ARE GIVEN THAT THE CAPACITOR IS INITIALLY UNCHARGED $\Rightarrow V_c(t=0) = 0$

$$\Rightarrow V_c(t) = V_c(0) + 5 \times 10^5 \int_0^t (5 \times 10^{-3}) dt$$

$$= 2.5 \times 10^3 t$$

NOTE: $V_c(t = 10^{-3}) = 2.5$ VOLTS

$$\rightarrow 10^{-3} < t < 3 \times 10^{-3}$$

$$V_c(t) = V_c(t = 10^{-3}) + 5 \times 10^5 \int_{10^{-3}}^t (5t) dt$$

$$= 2.5 + 25 \times 10^5 \frac{1}{2} t^2 \Big|_{10^{-3}}^t$$

$$= 2.5 + 12.5 \times 10^5 (t^2 - 10^{-6})$$

$$= 2.5 - 1.25 + 12.5 \times 10^5 t^2$$

$$= 1.25 + 12.5 \times 10^6 t^2$$

NOTE: $V_c(t = 3 \times 10^{-3}) = 12.5$ V


$$\rightarrow t > 3 \times 10^{-3}$$

$$V_c(t) = V_c(t = 3 \times 10^{-3}) + 5 \times 10^5 \int_{3 \times 10^{-3}}^t (15 \times 10^{-3}) dt$$



$$= 12.5 + 75 \times 10^2 (t - 3 \times 10^{-3})$$

$$= 12.5 - 22.5 + 7.5 \times 10^3 t$$

$$= -10 + 7.5 \times 10^3 t$$

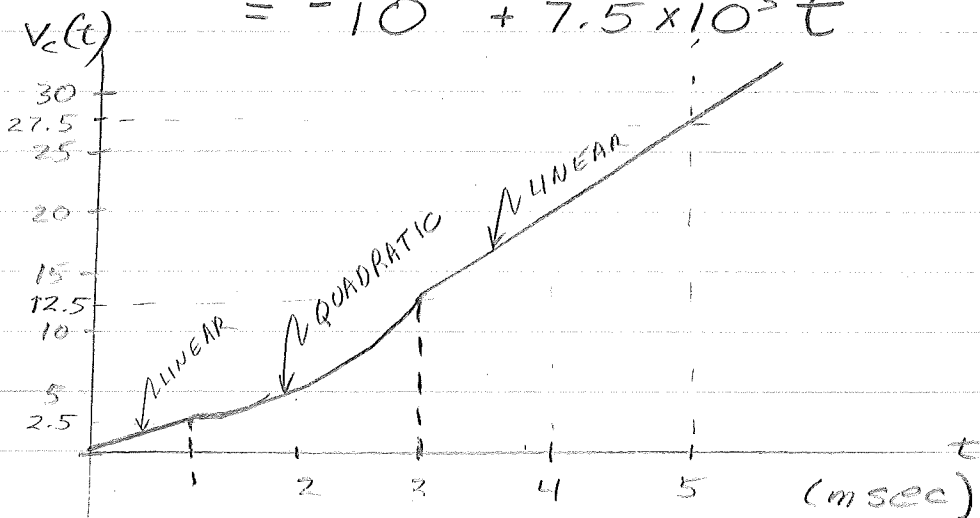

pg. 27
(13)

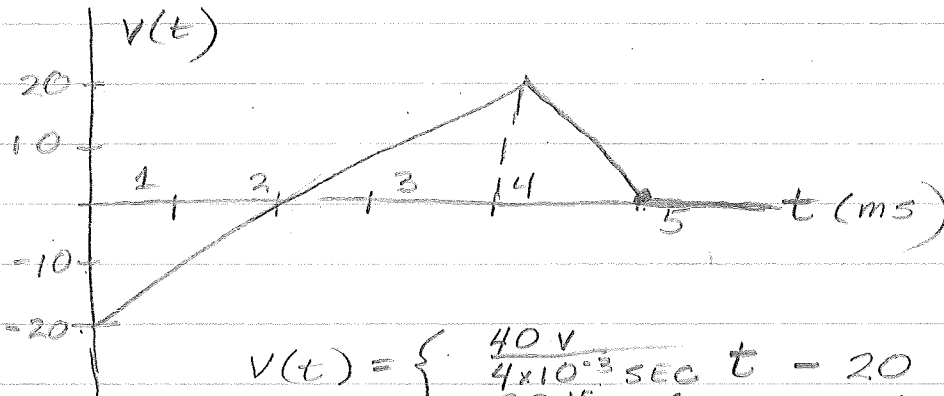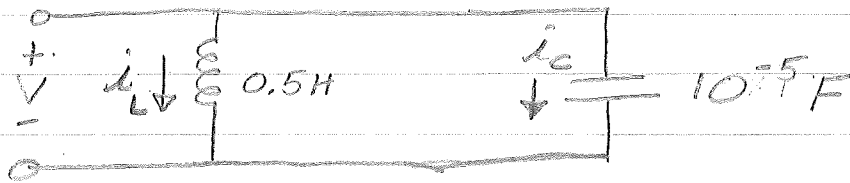

$$V(t) = \begin{cases} \frac{40V}{4 \times 10^{-3} \text{ sec}} t - 20 & ; 0 < t < 4 \text{ ms} \\ -\frac{20V}{10^{-3} \text{ sec}} (t - 5 \times 10^{-3}) & ; 4 < t < 5 \text{ ms} \\ 0 & ; t > 5 \text{ ms} \end{cases}$$


$$= \begin{cases} 10^4 t - 20 & ; 0 < t < 4 \text{ ms} \\ -2 \times 10^4 t + 10^2 & ; 4 < t < 5 \text{ ms} \\ 0 & ; t > 5 \text{ ms} \end{cases}$$

FOR CAPACITOR:

$$i_C = C \frac{dV}{dt} = 10^{-5} \frac{dV}{dt}$$

$$= \begin{cases} 10^{-5} (10^4) & ; 0 < t < 4 \text{ ms} \\ 10^{-5} (-2 \times 10^4) & ; 4 < t < 5 \text{ ms} \\ 0 & ; t > 5 \text{ ms} \end{cases}$$
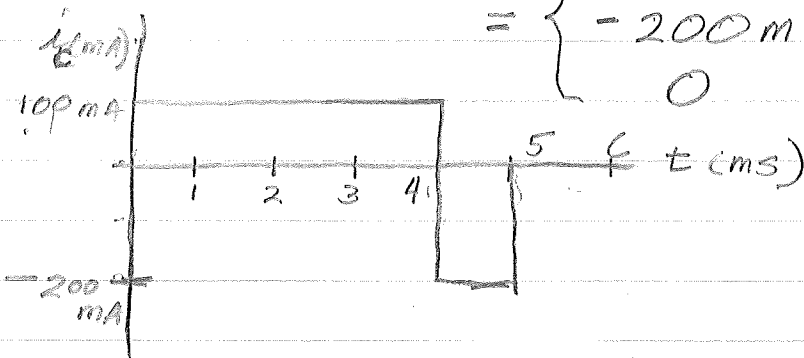
$$= \begin{cases} 100 \text{ mA} & 0 < t < 4 \text{ ms} \\ -200 \text{ mA} & 4 < t < 5 \text{ ms} \\ 0 & t > 5 \text{ ms} \end{cases}$$



$$w(t) = \int_{-\infty}^t P(t) dt$$

$$= W(t_0) + \int_{t_0}^t P(t) dt$$

$$0 < t < 4 \text{ ms}$$

$$w(t) = w(0) + \int_0^t [10^3 t - 2] dt$$

$$= 0.5 \times 10^3 t^2 - 2t$$

$$w(4 \times 10^{-3}) = 8 \times 10^{-3} - 8 \times 10^{-3} = 0$$

$$4 \text{ ms} < t < 5 \text{ ms}$$

$$w(t) = w(4 \text{ ms}) + \int_{4 \times 10^{-3}}^t (4 \times 10^3 t - 20) dt$$

$$= [2 \times 10^3 t^2 - 20t]_{4 \times 10^{-3}}^t$$

$$= [(2 \times 10^3 t^2 - 20t) - (32 \times 10^{-3} - 80 \times 10^{-3})]$$


$$= 2 \times 10^3 t^2 - 20t + 48 \times 10^{-3}$$

$$w(t=5 \times 10^{-3}) = 50 \times 10^{-3} - 100 \times 10^{-3} + 48 \times 10^{-3}$$

$$= -2 \times 10^{-3} = -2 \text{ mJ}$$

MINIMUM @ $t = 2 \times 10^{-3} \text{ SEC}$
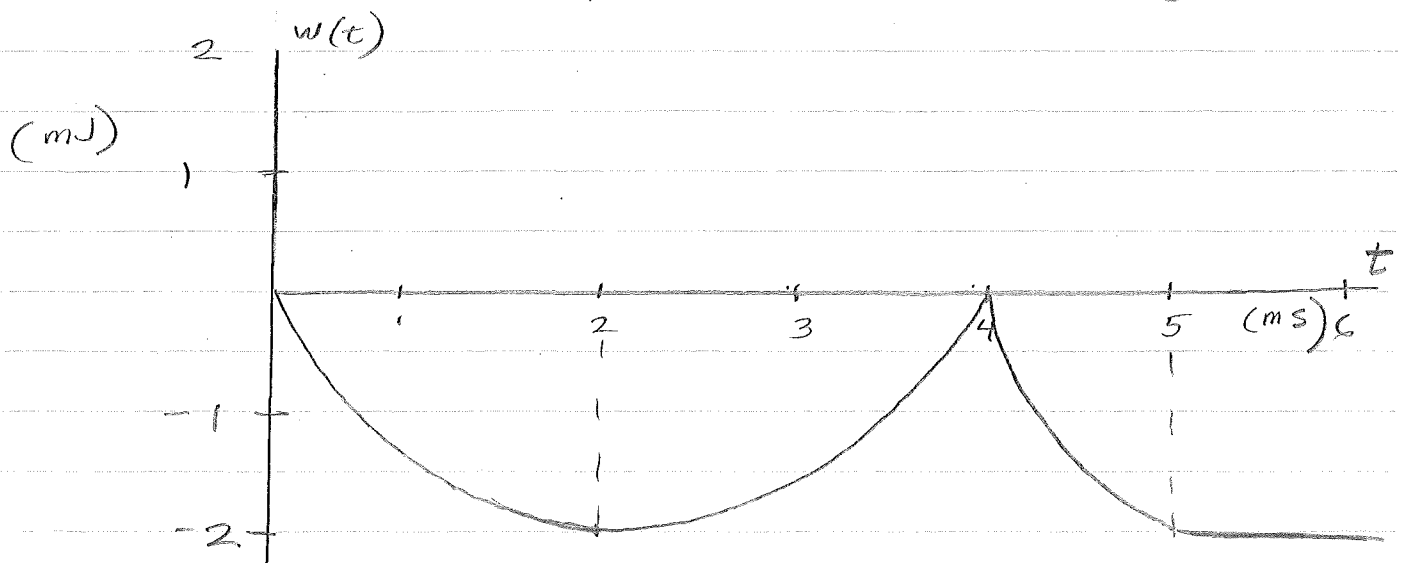
$$w(t=2 \times 10^{-3} \text{ SEC}) = -2 \times 10^{-3} = -2 \text{ mJ}$$



FOR INDUCTOR

$$i_L = i(t_0) + \frac{1}{L} \int_{t_0}^t i(t) dt$$
$$= i(t_0) + 2 \int_{t_0}^t i(t) dt$$

WE ARE GIVEN THAT $i_L(0) = 0$

FOR $0 < t < 4 \text{ ms}$

$$i_L(t) = i(0) + 2 \int_0^t [10^4 t - 20] dt$$
$$= 10^4 t^2 - 40t \Big|_0^t$$
$$= 10^4 t^2 - 40t$$

MINIMUM @ $t = 2 \times 10^{-3}$

$$i_L(2 \times 10^{-3}) = -0.04 \text{ AMPS} = -40 \text{ mA}$$


ALSO $i_L(4 \text{ ms}) = 0$

FOR $4 \text{ ms} < t < 5 \text{ ms}$

$$i_L(t) = i_L(4 \text{ ms}) + 2 \int_{4 \times 10^{-3}}^t [-2 \times 10^4 t + 10^2] dt$$
$$= \int_{4 \times 10^{-3}}^t [-4 \times 10^4 t + 2 \times 10^2] dt$$
$$= -2 \times 10^4 t^2 + 2 \times 10^2 t \Big|_{4 \times 10^{-3}}^t$$
$$= (-2 \times 10^4 t^2 + 2 \times 10^2 t) - (-0.32 + 0.8)$$
$$= -2 \times 10^4 t^2 + 2 \times 10^2 t - 0.48$$



NOTE $i_L(t = 5 \times 10^{-3}) = -0.5 + 1 - 0.48 = 0.02 \text{ AM}$

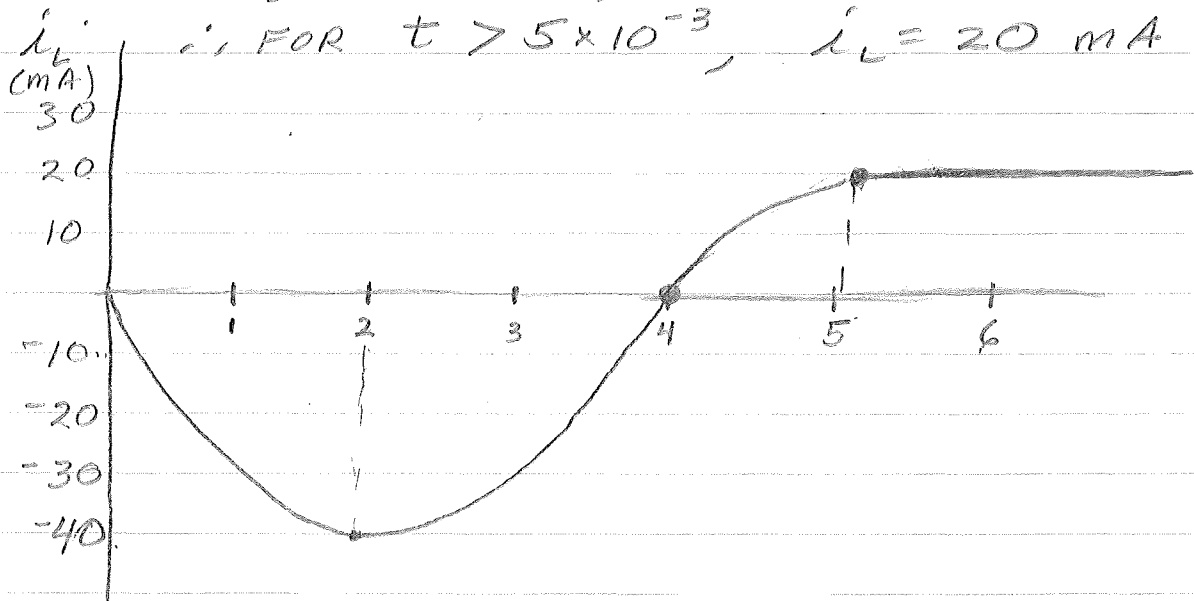FOR $t > 5 \times 10^{-3}$, $i_L = 20 \text{ mA}$



p. 27

(16) $P = V i$

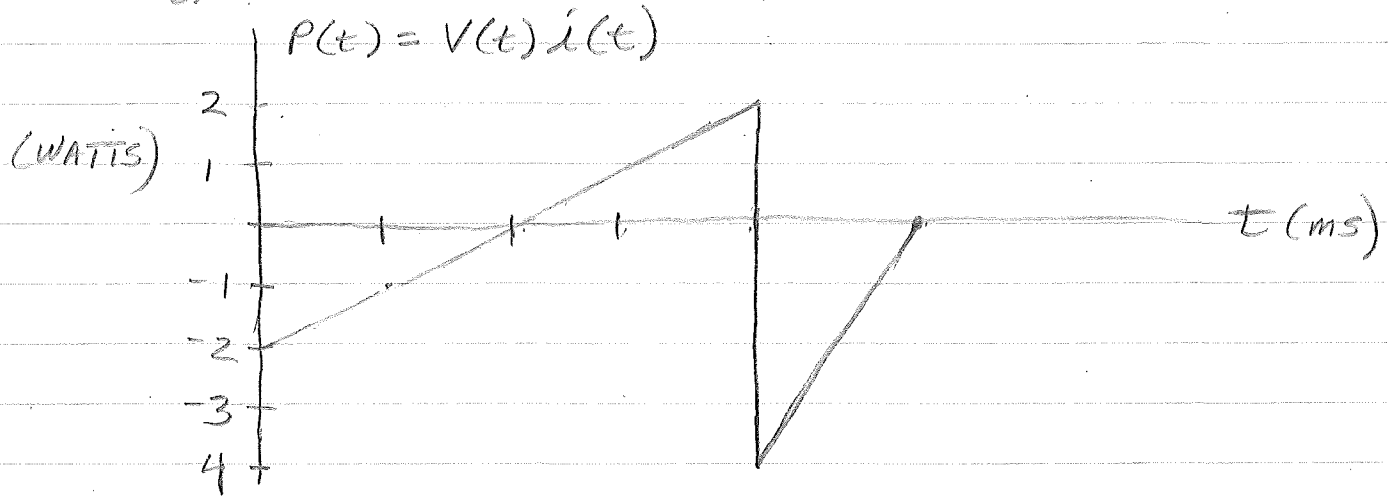
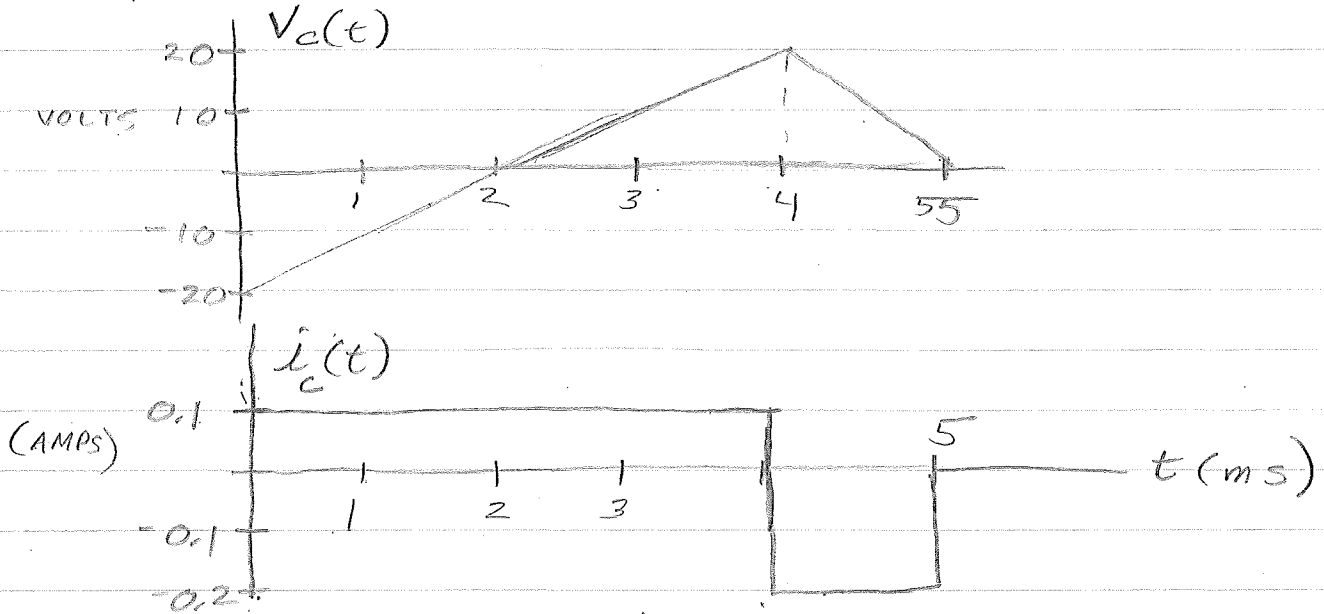


$$P(t) = \begin{cases} 10^3 t - 2 & ; 0 < t < 4 \text{ ms} \\ 4 \times 10^3 t - 20 & ; 4 \text{ ms} < t < 5 \text{ ms} \\ 0 & ; \text{OTHERWISE} \end{cases}$$

pg. 27


(15) $P = Vi$

WE HAVE SHOWN IN PROBLEM 12:

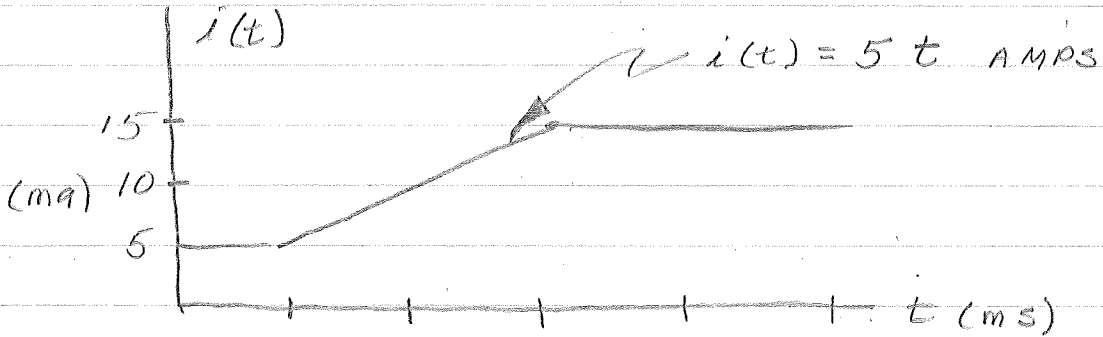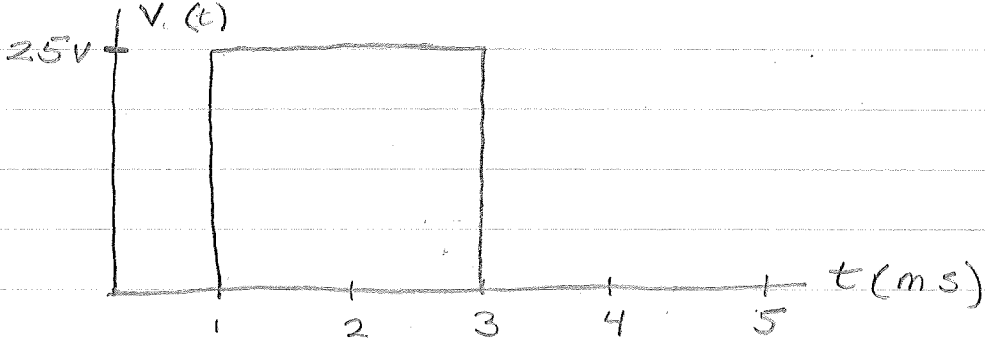


MULTIPLYING THESE TWO CURVES GIVES:
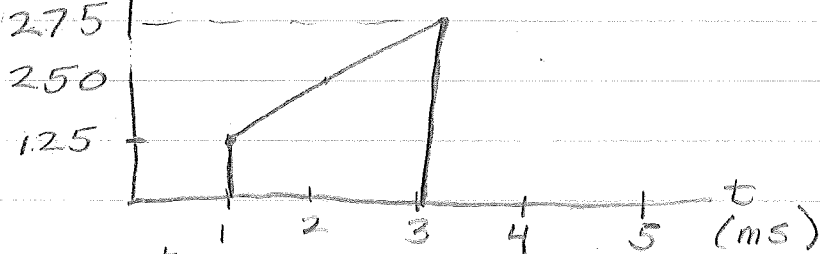
$$P(t) = \begin{cases} 125t & ; 1 \text{ ms} < t < 3 \text{ msec} \\ 0 & ; \text{ OTHERWISE} \end{cases}$$



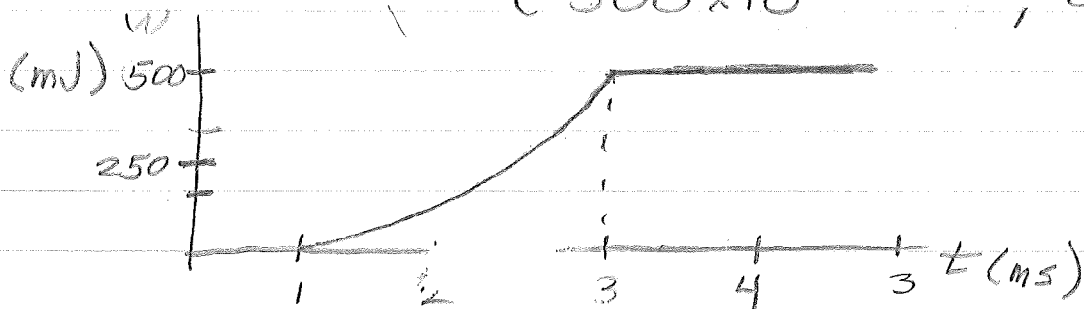
$$W = \int_{-\infty}^t P(t) dt = \begin{cases} 62.5t^2 - 62.5 \times 10^{-6} & ; 1 < t < 3 \text{ ms} \\ 500 \times 10^{-6} & ; t > 3 \end{cases}$$



P 2.6.

2.

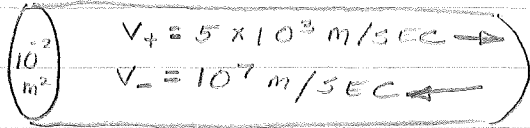

$$\rho_p = 10^{+13} \frac{10NS}{m^3}$$
$$\rho_e = 10^{11} \frac{e^-}{m^3}$$

$$I_p = \left(10^{+13} \frac{CH}{m^3}\right) (10^{-2} m^2) (5 \times 10^3 \frac{m}{SEC}) \left(\frac{1.602 \times 10^{-19} C}{CH}\right)$$


$$= 8.01 \times 10^{-5} \text{ AMP} = 0.0801 \times 10^{-3} \text{ AMP}$$

$$I_e = \left(10^{11} \frac{CH}{m^3}\right) (10^{-2} m^2) (10^7 \frac{m}{SEC}) \left(\frac{1.602 \times 10^{-19} C}{CH}\right)$$

$$= 1.602 \times 10^{-3} \text{ AMP}$$

$$I = I_p + I_e = \dots \text{ (IN DIRECTION OF } + \text{)}$$

3.

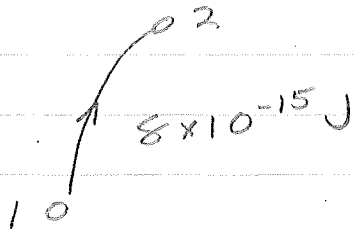

5. $V = 12 \text{ V}$ $P = 30 \text{ W}$

$$I = P/V = 30/12 = 15/6 = 5/2 \text{ AMP}$$

a. $q = It = \frac{5}{2} \times 60 \text{ SEC} = 5 \times 30 = 150 \text{ COUL}$

b. $1e = 1.602 \times 10^{-19} \text{ C}$

OR $6.24 \times 10^{18} \text{ elec} = 1 \text{ COUL}$

$$\Rightarrow 150 \text{ COUL} = 9.36 \times 10^{20} \text{ elec}$$

c. $30 \text{ W} \times 24 \text{ HR} = 720 \text{ WAT HR}$


$$= .72 \text{ KWH}$$

$$.72 \text{ KWH} \times \frac{6\text{¢}}{\text{KWH}} = 4.32\text{¢}$$

d. $P = I^2 R = \frac{V^2}{R}$

$$\Rightarrow R = (12)^2 / 30 = 4.80 \Omega$$

(2-7) (a) LOOP METHODS

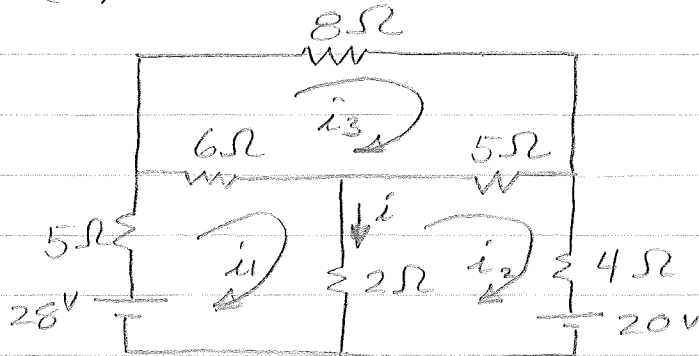

MESH EQUATIONS ARE

$$13i_1 - 2i_2 - 6i_3 = 28$$

$$-2i_2 + 11i_2 - 5i_3 = -20$$

$$-6i_1 - 5i_2 + 19i_3 = 0$$

SOLUTIONS ARE *

$$i_1 = 2.106 \text{ AMPS}$$

$$i_2 = -1.286 \text{ AMPS}$$



$$i_3 = 0.3266 \text{ AMPS}$$

OBVIOUSLY

$$i = i_1 - i_2$$

$$= 2.106 + 1.286 = 3.392 \text{ AMPS}$$


pg 57
(12)

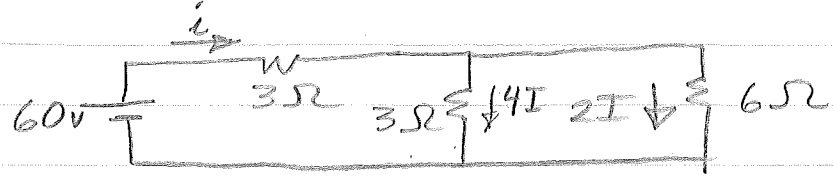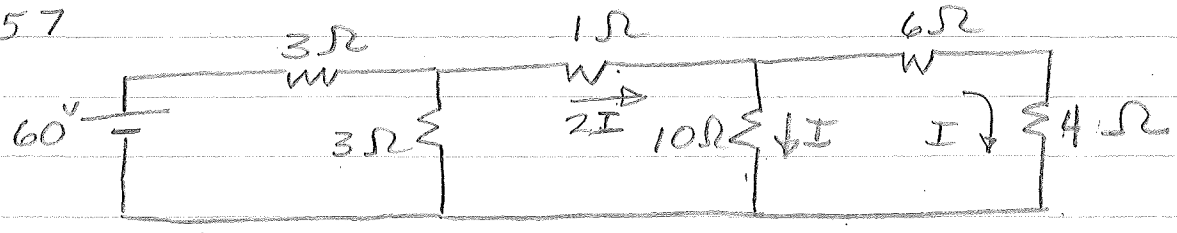

$$\frac{1}{R} = \frac{1}{3} + \frac{1}{6} = \frac{3}{6} \Rightarrow R_{eq} = 2$$


$$i = \frac{60}{5} = 12 \text{ AMPS} = 6I \Rightarrow I = 2 \text{ AMPS}$$

(16).

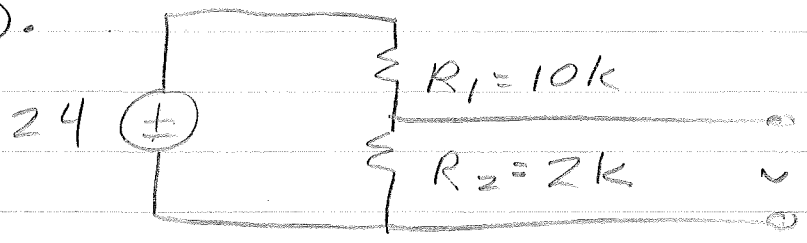

$$(a) V = \frac{2}{2+10} 24 = \frac{2}{12} 24 = 4 \text{ V}$$

(b)

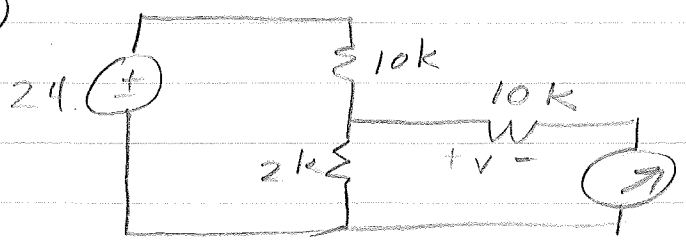

$$\frac{1}{2} + \frac{1}{10} = \frac{10+2}{20} = \frac{12}{20} \Rightarrow R_{eq} = \frac{20}{12} = \frac{5}{3} \text{ k}\Omega$$

$$V = \frac{5/3}{5/3 + 10} 24 = \frac{5}{35} 24 = \frac{24}{7} \text{ V}$$

$$\begin{array}{r} 3.43 \\ 7 \overline{) 24} \\ \underline{21} \\ 30 \\ \underline{28} \\ 20 \end{array}$$

SEMESTER _____ SESSION 19.....19.....
 SUBJECT _____
 SECTION _____ CLASS PERIOD _____ ROOM _____
 ASSISTANT _____

<190 F (6)
 <140 D (8)
 <190 C (1)
 <240 B (5)
 <285 A (3)

2 A+
 10 A
 5 B
 1 J
 2 F

0.9-1.0 3
 0.8-0.9 4
 0.7-0.8 4
 0.6-0.7 4
 0.5-0.6 3
 0.4-0.5 4
 0.3-0.4 3
 0.2-0.3 4
 0.1-0.2 3

DATE	HOMEWORK										MID	HW	LHW	EC	HWC.	POINTS MAXIMUM EARNED
	30	40	50	20	40	35	50	285	10	15						
1	19	23	40	15	7	14	12	115	C	63	178	10	0.501			
2	30	20	40	15	16	34	28	213	A	83	296		0.789			
3	30	8	34	13	10	9	17	121	A-	60	181		0.483			
4	23	-	50	12	5	20	5	115	D+	69	284	8 5	0.558			
5	30	19	49	17	20	20	12	206	B+	85	291	15	0.816			
6	30	15	47	20	9	20	9	150	B+	85	203	11 10	0.635			
7	30	25	50	20	32			157	C+	87	244	16	0.697			
8	21	24	12					57	A	81	57		0.152			
9	24	24	50	20	20	38	35	234	A	67	315	339	0.904			
10	28	19	49	19	20	20	28	222	A	87	289	15	0.811			
11	29	30	47	12	19	38	13	176	A	87	263	10	0.728			
12	29	29	37	10	19	38		162	A	65	227	5 5	0.645			
13	30	29	45	20	20	10	23	269	A+	80	349	15	0.971			
14	-	-	-	-	-	-	-	0								
15	-	-	-	-	-	-	-	0								
16	27	32	50	17	29	20	28	218	B-	72	290	10	0.808	L 4		
17	26	16	39	9	20	20	9	148	C-	76	224	15	0.637	+ CL 2		
18	24	28	49	20	20	38	35	258	A-	83	341		0.909	+ CL 2		
19	30	25	30	18	14	26	14	186	A	72	258	10	0.715	+ CL 1		
20	29	21						50	D	60	110	8 10	0.395	CL 1		
21	29	33	49	17	14	20	9	175	C	87	262		0.699	TO 00		
22	30	17	47	11	15	20	12	182	B	76	258		0.688			
23	-	2	42					44	D		44		0.117			
24	23	8	122			10		63		51	114		0.304			
25	-	-	40			20	23	125	C		125		0.333			
26	26	-	35	16	20	10	9	116	B-	15	203		0.541			
27	28	32	50	20	20	38	35	273	A+	90	263	5	0.981			
28	27	17	40	15		20	25	176	A	78	254	15	0.717			
29	26	15	20			8	1	84	C	80	164		0.437			
30	17	15	32	13		20		132	B+	69	201		0.536			
31	18	22	50	10				100	C		100	11	0.374			
32	26	15	32		15	16	13	145	A	13	158		0.421			
33	-	-	-					0			0					
34	30	14	10	39	13			118			118		0.315			
35	27	-	42					69	C		69		0.184			
36	13	21	45			10	11	145	F	67	67	10	0.205			

POINTS MAXIMUM EARNED
 K PROBLEMS POINTS
 $\frac{(LHW-HW)}{2} + E.C.$

L 4
 + CL 2
 + CL 1
 TO 00

.....SEMESTER
 SUBJECT.....
 SECTION.....CLASS
 ASSISTANT.....

TEXT BOOKS

100-110	1	40-50	2	10	100-110	1
90-100						
80-90	3	30-40	0	1	90	100
70-80	1	20-30	2	6	80	90
60-70	7			3	70	80
50-60	13				60	70
					50	60
					40	50

TESTS

DATE	115 PTS	110	110	110
1	77	77	54	210
2	99	101	97	297
3	92	92	65	249
4	70	89	65	155
5	110	89	65	264
6	76	109	29	190
7	81	109	63	253
8	76	106	50	232
9	98	101	67	266
10	110	103	53	266
11	110	107	83	300
12	92	92	58	252
13	98	104	51	253
14	30	WP	WP	WP
15		83	50	211
16	78	50	60	201
17	91	82	58	236
18	96	97	83	281
19	101	58	51	203
20	87	85	58	211
21	68	95	68	233
22	70	79	51	201
23	79	70	23	177
24	80	74	50	206
25	82	75	56	224
26	83	108	101	310
27	101	101	80	286
28	105	73	52	214
29	89	86	50	216
30	80	86	47	208
31	75	100	74	274
32	100			
33				
34	77			
35	89	60	69	215
36	51	50	47	148

GRADE COMPUTATION

L HOMEWORK
 THW = TOTAL HOMEWORK POINTS MAXIMUM
 HW = HOMEWORK POINTS EARNED
 LHW = # LATE HOMEWORK PROBLEMS
 EC = # EXTRA CREDIT POINTS


$$HW\% = \frac{HW + \frac{10LHW}{THW} \left(\frac{THW - HW}{2} \right) + E.C.}{THW}$$

THW = 375 STO → 1

STO 2 (HW)	RCL 4
STOP	+ RCL 2
STO 3 (LHW)	+ RCL 1
STO 4 (EC)	÷
RCL 1	GTO 00
RCL 2	
-	
2	
÷	
RCL 3	
X	
1	
0	
X	
RCL 1	
÷	


SEMESTER _____ SESSION 19.....19..... *EDDIE HUANG
 SUBJECT _____ *HUBBARD
 SECTION _____ CLASS PERIOD _____ ROOM TROTTER
 ASSISTANT _____ *NOTE
 _____ *KIRBY
 .2 LAB
 +HWQ+.3FINAL

NAMES (0.1)HWQ+(6.4)Q	MONTH DATE	LAB	HW+Q	FINAL	GRADE	
0.330 D	1-2	0	.88	.330	0.70	C
0.475 A	0-3	3 F	.97	.475	0.99	A
0.380 C	3-35	9 D	*89.5	.380	0.75	B
	35-4	5 C	*59	0.29	0.54	B
0.434 B	4-45	9 B	*91.7	.434	0.78	B
0.317 D	45-5	3 A	*86	.317	0.45	D
0.407 B	5-5	1 A	93.2	.407	1.02	B
0.325 D			*87.5	.325	0.74	D
0.445 B			*82.4	.445	.92	B
0.436 B			*90	.436	.81	B
0.473 A			*90	.473	0.93	A
0.409 B			*96	.409	0.92	B
0.434 B			*93	.434	1.04	B
-		26	-	-	-	
0.361 C			*70.5	.361	0.90	B
			76+	0.68 0.33	0.54	C
0.406 B			86	.406	0.82	B
0.446 B			96	.446	0.97	B
0.310 D			*79	.310	0.69	D
0.351 C			*93.1	.351	0.87	C
0.379 C			*84.7	.379	0.80	C
0.312 D			100	.312	0.69	D
0.266 F			*37.7	.266	0.67	F
0.308 D			*99	.308	0.75	D
0.353 C			*91	.353	0.69	C
0.511 A			*89	.511	1.00	A
0.453 A			*86.5	.453	0.96	A
0.329 D			*88	.329	0.68	D
0.342 D			*73.5	.342	0.80	D
0.307,314 D			40.3	.374	0.57	D
0.407 B			*89	.407	0.90	B
-			*70.4	-	-	
			*21.2	-	-	
0.312 D			*72	.312	0.68	D
0.218 F			*49	.218	0.32	F

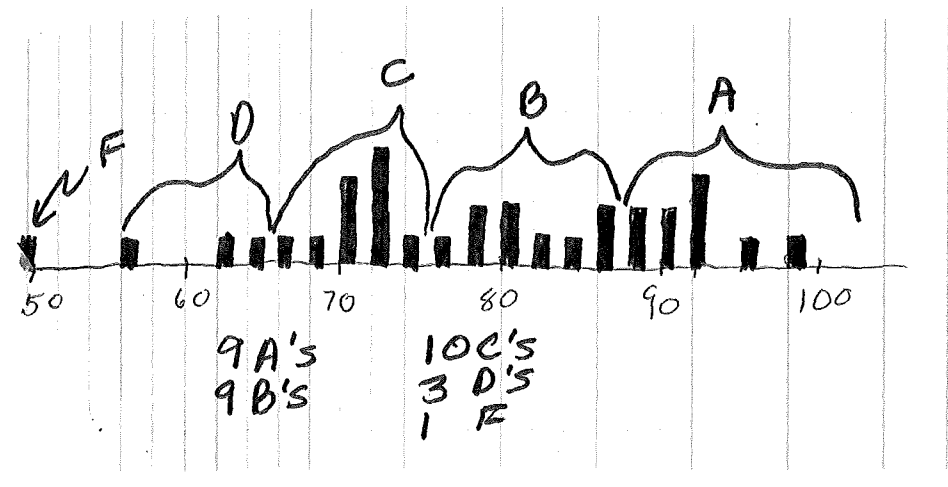


EE 332 - 5068

7.27.76

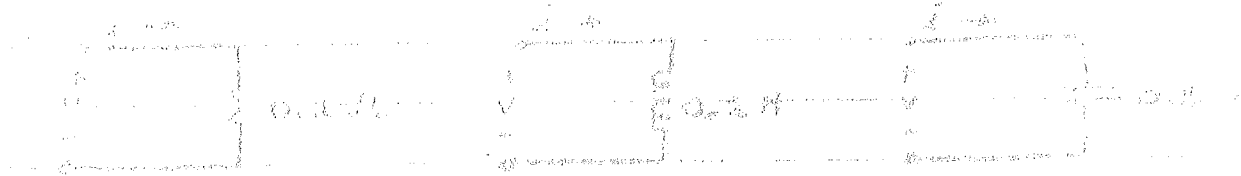


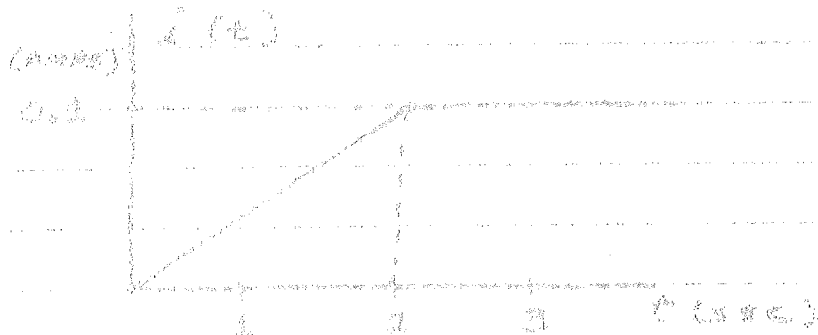(1) GIVEN THE FOLLOWING $i(t)$, COMPUTE AND SKETCH $v(t)$, $P(t) = v(t)i(t)$, AND $W(t) = \int_{-\infty}^t P(t) dt$ AND $W(t_0) = \int_{-\infty}^{t_0} P(t) dt$ FOR (a) R (b) L AND (c) C



(ASSUME $v_c(t=0) = 0$)

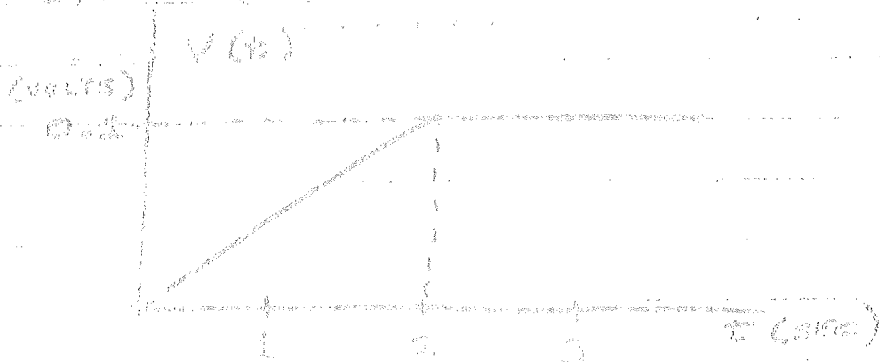(2) GIVEN THE FOLLOWING $v(t)$, COMPUTE AND SKETCH $i(t)$, $P(t)$, AND $W(t)$ FOR (a) R (b) L AND (c) C




(3) COMPARE THE RESULTS IN (1) AND (2) AND COMMENT.

EXTRA CREDIT PROBLEM - EE 233 (MATH)

DUE: 10/1/76


SOLUTIONS

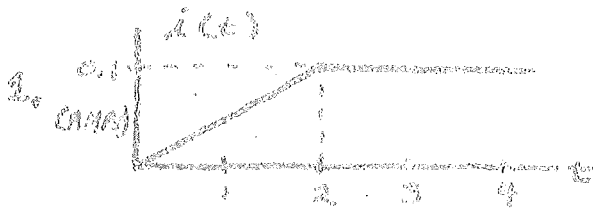

$$i(t) = \begin{cases} 0.05t & ; 0 \leq t < 2 \\ 0.1 & ; t \geq 2 \end{cases}$$

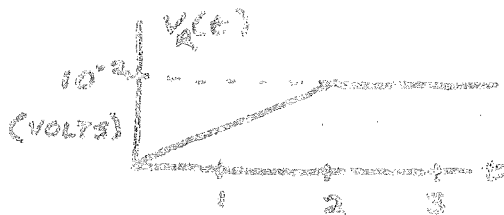
(a) FOR RESISTOR

$$V_R(t) = Ri(t) = 0.1 i(t) = \begin{cases} 5 \times 10^{-3} t & ; 0 \leq t < 2 \\ 10^{-2} & ; t \geq 2 \end{cases}$$



$$P_R(t) = i(t) V_R(t) = \begin{cases} (0.05t)(5 \times 10^{-3} t) & ; 0 \leq t < 2 \\ 10^{-3} & ; t \geq 2 \end{cases}$$
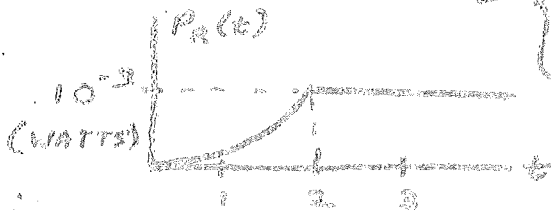
$$= \begin{cases} 2.5 \times 10^{-4} t^2 & ; 0 \leq t < 2 \\ 10^{-3} & ; t \geq 2 \end{cases}$$



$$W_R(t) = W_R(t_0) + \int_{t_0}^t P(t) dt$$


$$= 0 + \int_0^t 2.5 \times 10^{-4} t^2 dt \quad ; 0 \leq t < 2$$

$$= 2.5 \times 10^{-4} \frac{1}{3} t^3$$

$$= 8.33 \times 10^{-5} t^3 \quad ; 0 \leq t < 2$$


$$W_R(2) = 8(8.33 \times 10^{-5}) = 50.67 \times 10^{-5} = 5.07 \times 10^{-4}$$
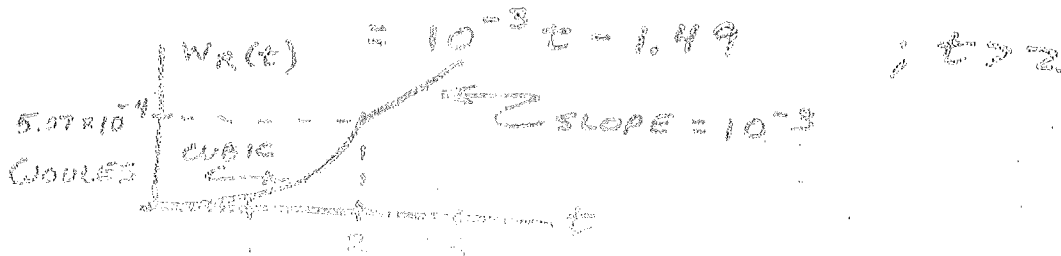
$$W_R(t) = W_R(2) + \int_2^t 10^{-3} dt = 5.07 \times 10^{-4} + 10^{-3}(t-2)$$



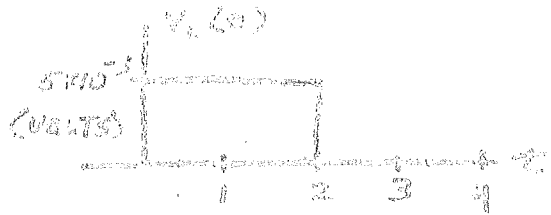
(b) FOR INDUCTOR

$$V_L(t) = -L \frac{di}{dt} = 2.1 \frac{di}{dt} = \begin{cases} 10^{-3} \times 5 & ; 0 \leq t < 2 \\ 0 & ; t > 2 \end{cases}$$



$$P_L(t) = i(t) V_L(t) = \begin{cases} (5 \times 10^{-3})(5 \times 10^{-3} t) & ; 0 \leq t < 2 \\ 0 & ; t > 2 \end{cases}$$
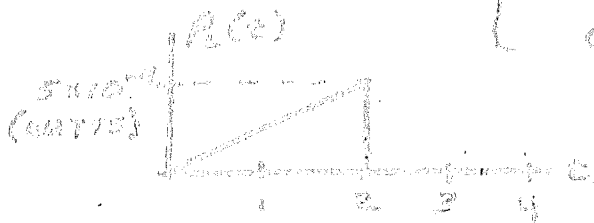
$$= \begin{cases} 2.5 \times 10^{-5} t & ; 0 \leq t < 2 \\ 0 & ; t > 2 \end{cases}$$



$$w_L(t) = w(t_0) + \int_{t_0}^t P(t) dt$$


$$= w(0) + \int_0^t (2.5 \times 10^{-5} t) dt \quad ; 0 \leq t < 2$$

$$= 0 + 1.25 \times 10^{-4} t^2 \quad ; 0 \leq t < 2$$

$$w_L(2) = 5 \times 10^{-4}$$

$$w_L(t) = w_L(2) + \int_2^t (0) dt \quad ; t > 2$$

$$= 5 \times 10^{-4}$$

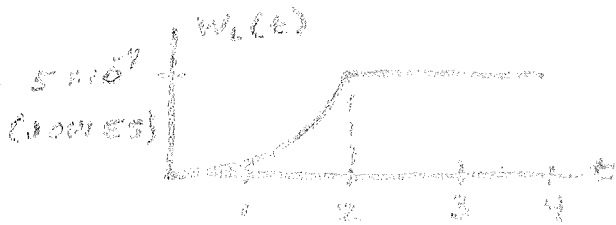


(c) FOR CAPACITOR

$$\begin{aligned}
 V_c(t) &= V_c(t_0) + \frac{1}{C} \int_{t_0}^t i(t) dt \\
 &= V_c(t_0) + 10 \int_{t_0}^t i(t) dt \\
 &= V_c(0) + 10 \int_0^t 5 \times 10^{-2} t dt \quad ; 0 \leq t < 2 \\
 &= 0 + 0.25 t^2 \quad ; 0 \leq t < 2
 \end{aligned}$$


$$V_c(2) = 1 \text{ volt}$$
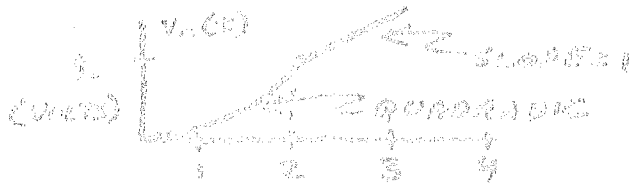
$$\begin{aligned}
 V_c(t) &= V_c(2) + 10 \int_2^t (0.1) dt \quad ; t > 2 \\
 &= 1 + (t-2) = t - 1 \quad ; t > 2
 \end{aligned}$$



$$\begin{aligned}
 P_c(t) = V_c(t) i(t) &= \begin{cases} (0.25 t^2)(0.05 t) & ; 0 \leq t < 2 \\ 0.1 (t-1) & ; t \geq 2 \end{cases} \\
 &= \begin{cases} 1.25 \times 10^{-2} t^3 & ; 0 \leq t < 2 \\ 0.1 t - 0.1 & ; t \geq 2 \end{cases}
 \end{aligned}$$

$$P_c(2) = 0.1$$

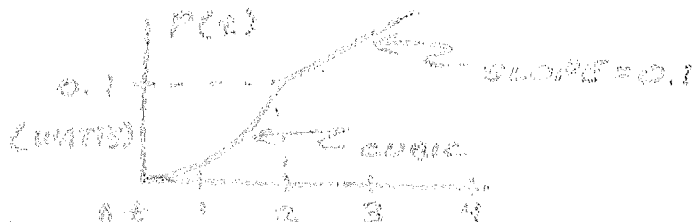


$$W_c(t) = W_c(t_0) + \int_{t_0}^t P_c(t) dt$$


$$= 0 + 1.25 \times 10^{-2} \int_0^t t^3 dt \quad ; 0 \leq t < 2$$

$$= 0.31 t^4 \quad ; 0 \leq t < 2 \Rightarrow W_c(2) = 4.96$$

$$W_c(t) = 4.96 + \int_2^t (0.1 t - 0.1) dt \quad t \geq 2$$

$$= 0.05 t^2 - 0.1 t + 4.96$$

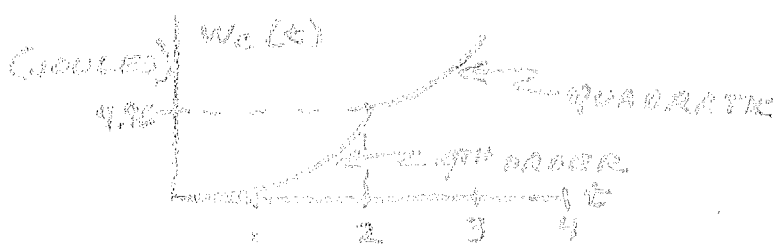


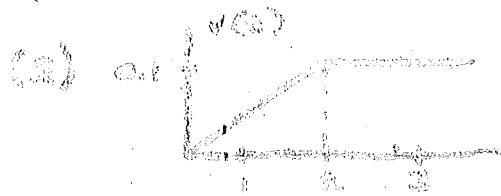


$$v(t) = \begin{cases} 0.05t & ; 0 \leq t < 2 \\ 0.1 & ; t \geq 2 \end{cases}$$

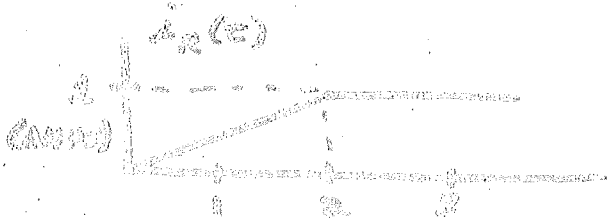(a) RESISTOR

$$i_R(t) = \frac{1}{R} v(t) = 10v(t) = \begin{cases} 0.5t & ; 0 \leq t < 2 \\ 1.0 & ; t \geq 2 \end{cases}$$


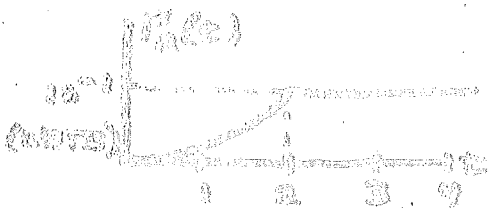
$$p_R(t) = v(t) \cdot i_R(t) = \begin{cases} 2.5 \times 10^{-2} t^2 & ; 0 \leq t < 2 \\ 0.1 & ; t \geq 2 \end{cases}$$



$$w_R(t) = w_R(t_0) + \int_{t_0}^t p_R(t) dt$$

$$= 0 + 2.5 \times 10^{-2} \int_0^t t^2 dt \quad ; 0 \leq t < 2$$

$$= 8.33 \times 10^{-3} t^3 \quad ; 0 \leq t < 2$$

$$w_R(2) = 6.67 \times 10^{-2}$$

$$w_R(t) = 6.67 \times 10^{-2} + \int_2^t (0.1) dt$$

$$= 0.067 + 0.1t - 0.2 = 0.1t - 1.33$$



(2) (b) FOR INDUCTOR

$$i_L(t) = i(t) + \frac{1}{L} \int_{-\infty}^t v(t) dt$$

THIS IS THE SAME MATN AS WE WENT THROUGH IN PROBLEM 31 PART C. FOR ANSWERS SEE

$$i_L(t) = \begin{cases} 0.15 e^{-2t} & ; 0 < t < 2 \\ t^{-1} & ; t > 2 \end{cases}$$




$P_L(t)$ = THE SAME AS $P_L(t)$ IN PROB. 16
 $w_L(t)$ = " " " " $w_L(t)$ " " "

(2) (c) FOR CAPACITOR

$$i_C(t) = C \frac{dv}{dt}$$

THIS IS THE SAME MATN AS IN PROB. 16.
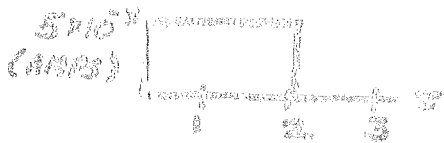
$$\Rightarrow i_C(t) = \begin{cases} 5 \times 10^{-3} & ; 0 < t < 2 \\ 0 & ; t > 2 \end{cases}$$




$P_C(t)$ = THE SAME AS $P_C(t)$ IN PROB. 16
 $w_C(t)$ = " " " " $w_C(t)$ " " "

(3) BY NOTING THE SIMILARITIES (OR "DUALITY") OF THE PROBLEMS, WE'VE SAVED SOME WORK.


E 232 - sec A (800 MARKS)
 TEST 1, 9/27/26 (55 MINUTES)

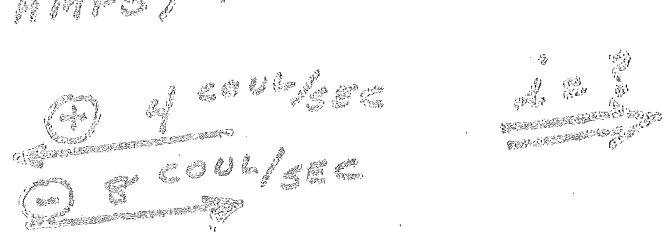(15)(a) A TOTAL OF 4 COULOMBS DUE TO POSITIVE IONS ARE FLOWING FROM RIGHT TO LEFT. EIGHT COULOMBS PER SECOND DUE TO (NEGATIVELY CHARGED) ELECTRONS ARE FLOWING FROM LEFT TO RIGHT. WHAT IS THE TOTAL CURRENT (IN AMPS) FLOWING FROM LEFT TO RIGHT







- (a) 4 AMPS
- (b) -4 AMPS
- (c) 12 AMPS
- (d) -12 AMPS



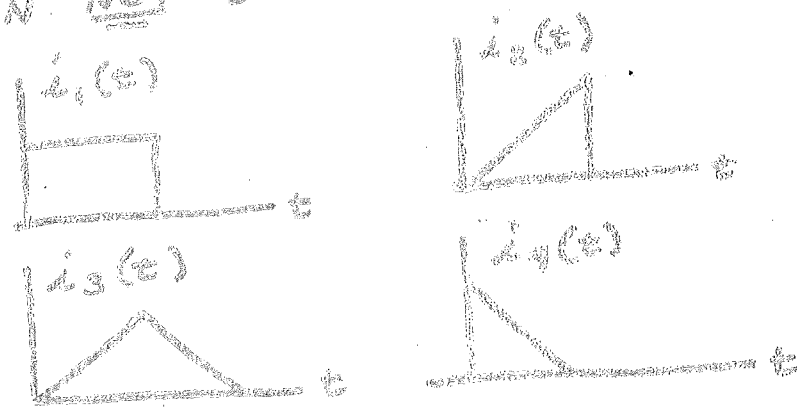
(b) WHICH OF THE FOLLOWING CURRENTS CAN NOT GO THRU AN (IDEAL) INDUCTOR



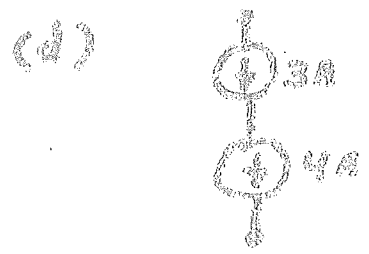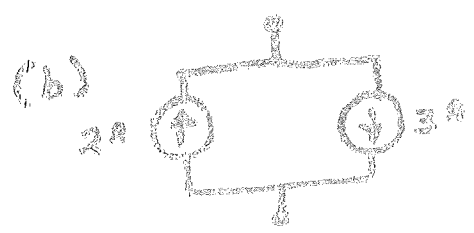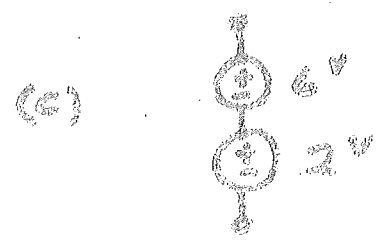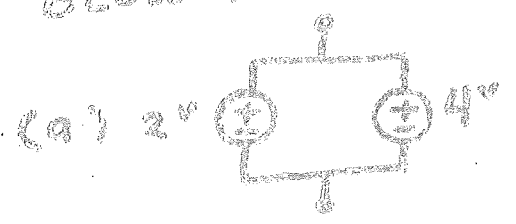(c) WHICH OF THE FOLLOWING CIRCUITS WILL "BLOW UP" (OR AT LEAST BLOW A FUSE)




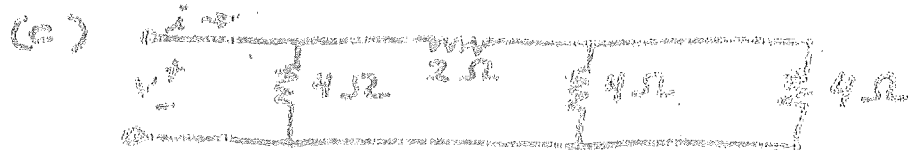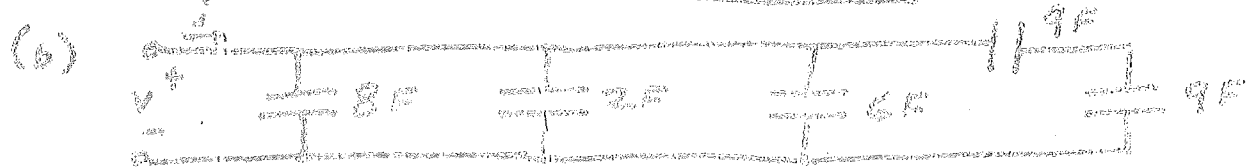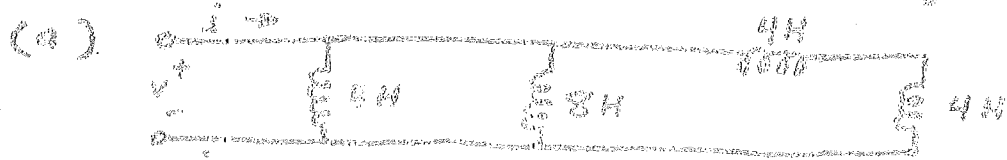2. (15) REDUCE THE FOLLOWING TO A SINGLE PASSIVE ELEMENT:




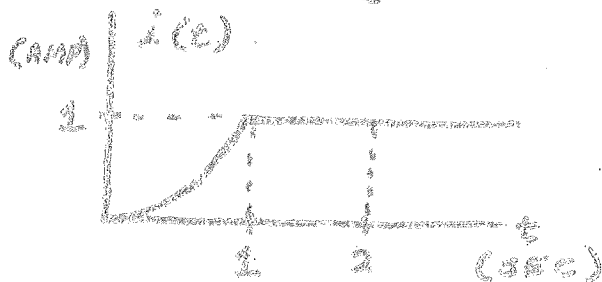3. (15) GIVEN THE CURRENT

$$i(t) = \begin{cases} t^2 \text{ AMP} & ; 0 \leq t \leq 1 \text{ SEC} \\ 1 \text{ AMP} & ; t \geq 1 \text{ SEC} \end{cases}$$



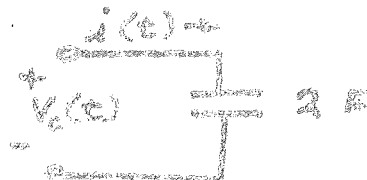(a) FIND THE VOLTAGE ACROSS A 2 FARAD CAPACITOR AT TIME $t = 2 \text{ SEC}$ (ASSUME THE CAPACITOR IS INITIALLY UNCHARGED $\Rightarrow V_c(t=0) = 0$)




(b) WHAT IS THE CORRESPONDING POWER AT TIME $t = 2 \text{ SEC}$?

(c) WHAT IS $V_c(t = 2 \text{ SEC})$ IF

$V_c(t=0) = 1 \text{ VOLT}$? (i.e., REWORK (b) FOR $V_c(t=0) = 1 \text{ VOLT}$)


4. (5) FOR THE CIRCUIT:

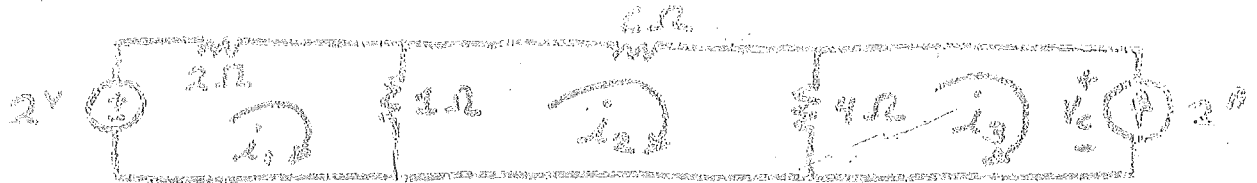

(a) WHAT IS i_3 ? (HINT: JUST LOOK AT THE CIRCUIT)

(b) WRITE THE LOOP (MESH) EQUATIONS FOR THE CIRCUIT. ASSUME A VOLTAGE V_c ACROSS THE CURRENT SOURCE. DO NOT SOLVE


5. (15) FOR THE CIRCUIT

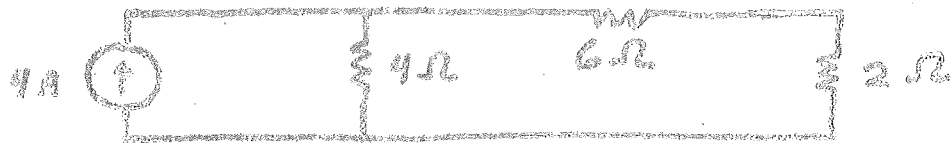


(a) SPECIFY ALL NODES

(b) WRITE THE CORRESPONDING NODE-VOLTAGE EQUATIONS. DO NOT SOLVE

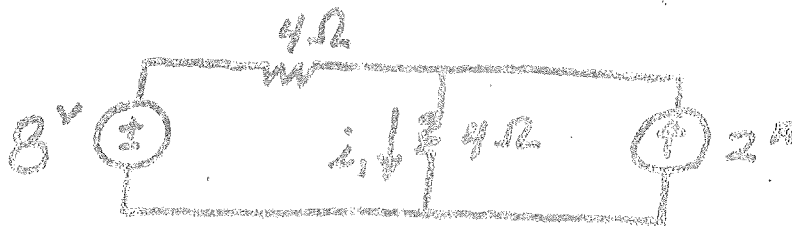6. (20) BY SUPERPOSITION, DETERMINE i_1 IN THE CIRCUIT BELOW. USE CURRENT AND VOLTAGE DIVIDER PRINCIPLES:



7. (20) FOR THE CIRCUIT

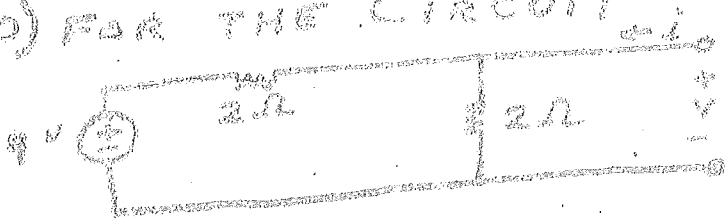

- (a) FIND THE OPEN CIRCUIT VOLTAGE, V_{oc} .
- (b) FIND THE SHORT CIRCUIT CURRENT, I_{sc} .
- (c) DRAW THE CIRCUIT'S $v-i$ CURVE
- (d) SKETCH THÉVENIN'S & NORTON'S EQUIVALENT CIRCUITS.

THE
END

"Wisdom is the principal thing; therefore,
get wisdom; and with all thy getting,
get understanding"
PROV. 4:7



SOLUTIONS

TEST 1


1. (a) -12 AMPS

(b) $i_1(t)$, $i_2(t)$, AND $i_4(t)$ ARE NOT ALLOWED SINCE THEY CHANGE INSTANTANEOUSLY

(c) CIRCUITS a AND d WILL "BLOW UP"

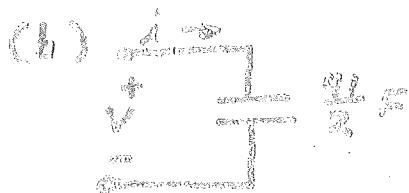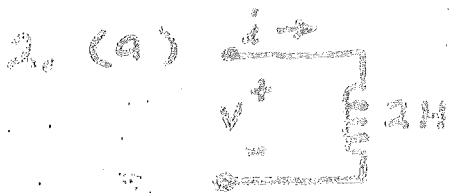

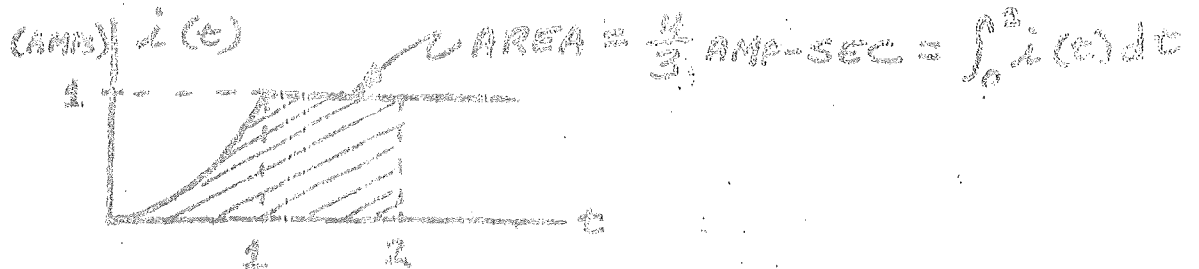3. (a) $v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt \Rightarrow \frac{1}{2} \int_0^2 i(t) dt + v(t=0) = v(2)$



$\therefore v(2) = \frac{1}{2} \left(\frac{4}{3} \right) = \frac{2}{3}$ VOLT


(b) $P(2) = v(2) i(2) = \left(\frac{2}{3} \text{ VOLT} \right) (1 \text{ AMP}) = \frac{2}{3}$ WATT

(c) $v(2) = \frac{1}{2} \int_0^2 i(t) dt + 1 \text{ VOLT} = \frac{5}{3}$ VOLT

4. (a) $i_3 = -2$ AMPS

(b)
$$\left. \begin{aligned} -2 + 3i_1 - i_2 &= 0 \\ 11i_2 - i_1 - 4i_3 &= 0 \\ 4i_3 - 4i_2 + v_c &= 0 \end{aligned} \right\}$$

5.

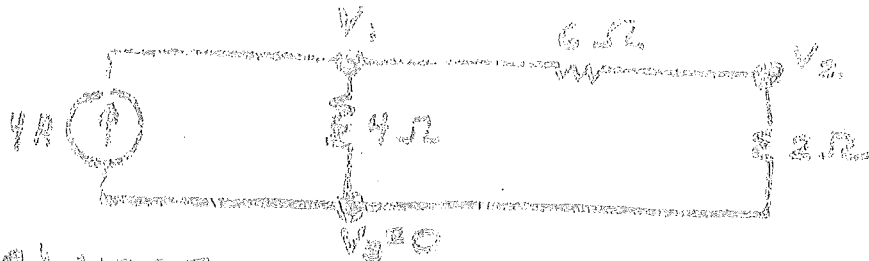

(a) NODES SPECIFIED BY "0" $V_2 = 0$

$$(b) \begin{cases} \frac{V_1 - V_1}{4} + \frac{V_1 - V_2}{6} + 4 = 0 \\ \frac{V_1 - V_2}{6} + \frac{V_2 - V_2}{2} = 0 \end{cases}$$

NOTE: $V_2 = 0$


6. FIND, FIRST, THE EFFECT OF THE V SOURCE



BY VOLTAGE DIVIDER:

$$V_v = \frac{4}{4+4} 3 = 1.5 \text{ VOLTS} \Rightarrow i_v = \frac{1.5}{4} = 0.375 \text{ AMP}$$

SECOND, FIND EFFECT OF CURRENT SOURCE

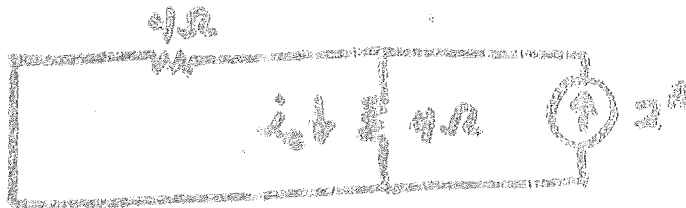


BY CURRENT DIVIDER:

$$i_c = \frac{2}{4+4} 2 = 0.5 \text{ AMP}$$

AND

$$i_v = i_v + i_c = 0.375 + 0.5 = 0.875 \text{ AMP}$$

7. (a)

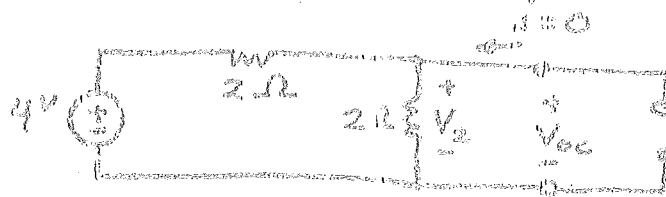


BY VOLTAGE DIVIDER

$$V_{oc} = V_2 = \frac{2}{2+2} 4 = 2 \text{ VOLTS}$$

(b)




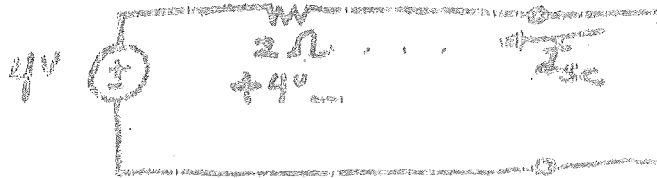WE HAVE "SHORTED" A 2Ω RESISTOR. AN EQUIVALENT CIRCUIT IS THUS




OBVIOUSLY, $I_{sc} = \frac{-4 \text{ VOLTS}}{2 \text{ OHMS}} = -2 \text{ AMPS}$

(c)

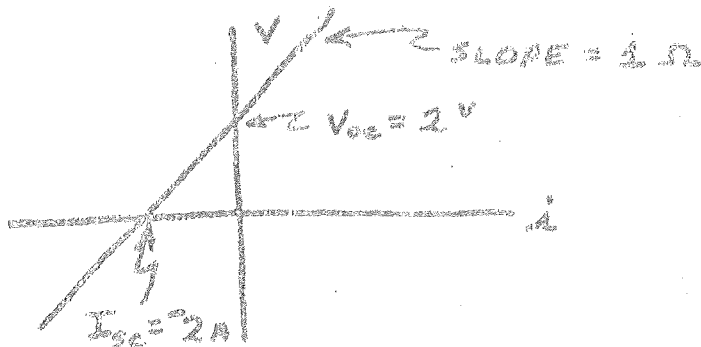


(d) $R_T = R_N = \frac{-V_{oc}}{I_{sc}} = 1 \Omega$

THEVININ:

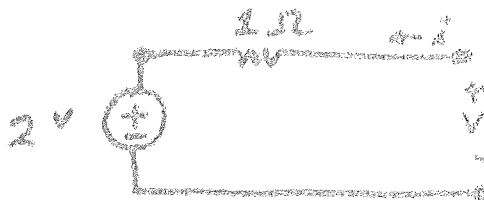

NORTON:

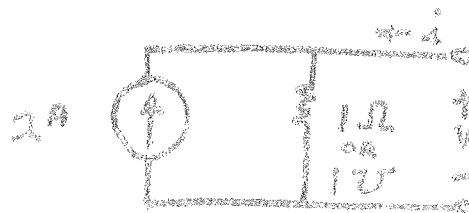

EE 233

TEST #2 NOV. 5, 1976

BOB MARSH


WORK ALL PROBLEMS. SPECIFY YOUR UNITS.

1. (15) (a) SHOW THAT $e^{j\pi} = j$
(b) GIVEN THE COMPLEX NUMBER

$$W = 1 + j$$

→ WRITE W IN POLAR FORM

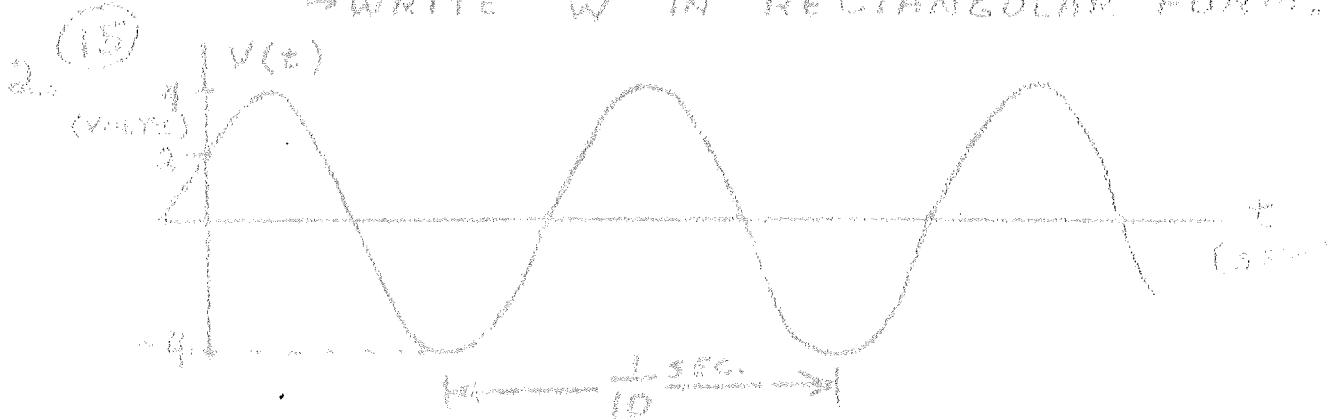→ WRITE $\frac{1}{W}$ IN RECTANGULAR FORM.



THE EQUATION FOR THE ABOVE WAVEFORM IS

$$V(t) = V_0 \cos(2\pi f t + \phi)$$

(a) WHAT ARE V_0 , f , AND ϕ ? (HINTS: $\phi < 0$


$$\text{AND } \cos \frac{\pi}{3} = \cos 60^\circ = \frac{1}{2})$$

(b) WHAT IS ω = ANGULAR FREQUENCY


AND T = PERIOD

(c) USING $\cos 2\pi f t$ AS A REFERENCE, SKETCH
THE PHASOR DIAGRAM CORRESPONDING TO

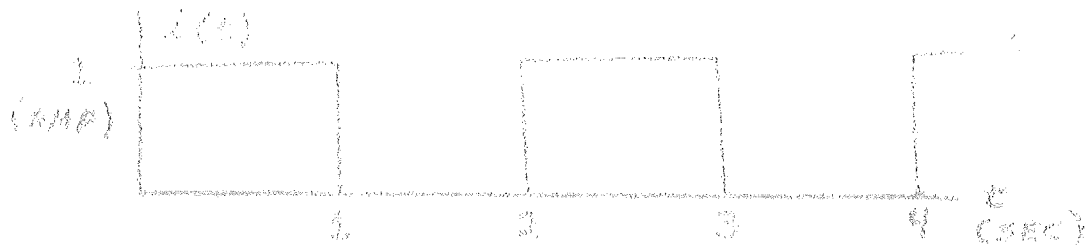3. (20) FIND I_{AVE} AND I_{RMS} ($= I_{EFF}$) FOR THE PERIODIC CURRENT WAVEFORM:




4. (20)

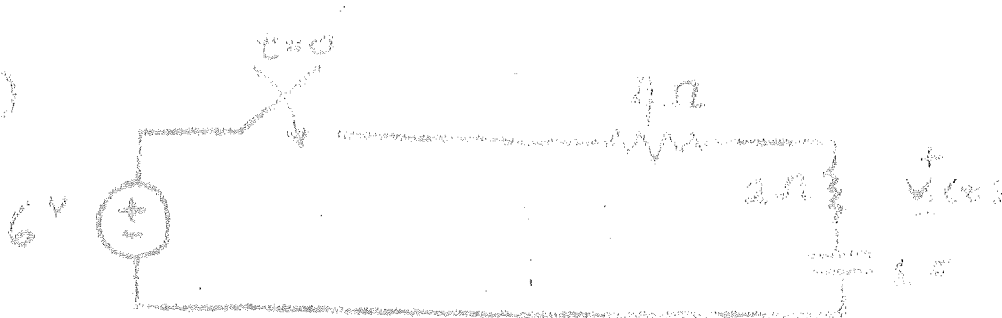


AND SKETCH
IN THE ABOVE CIRCUIT, FIND $v(t)$ = VOLTAGE ACROSS THE 2Ω RESISTOR. ASSUME THAT THE VOLTAGE ACROSS THE CAPACITOR, BEFORE THE SWITCH IS THROWN, IS ZERO. (HINT: USE THE "4 NUGGETS")

5.

(20)

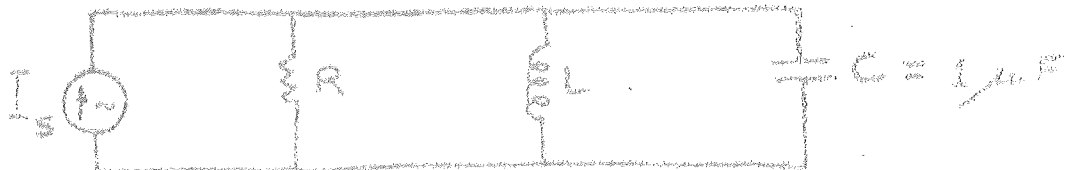

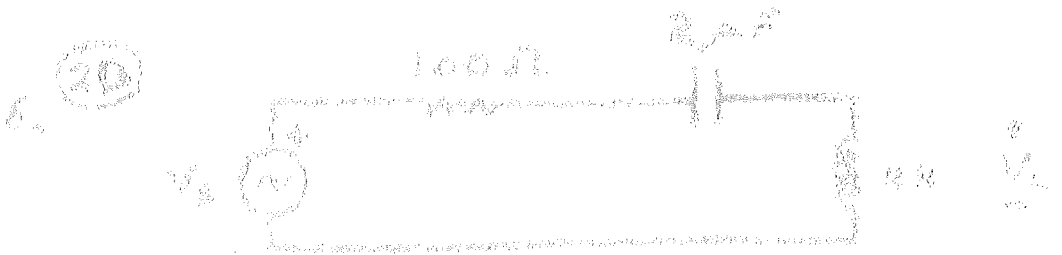
THE CURRENT SOURCE SHOWN IS SINUSOIDAL WITH AN ANGULAR FREQUENCY $\omega = 100 \frac{\text{RADIANS}}{\text{SEC}}$. GIVEN THAT $C = 1 \mu F$, FIND THE VALUE OF L SUCH THAT 50% OF THE CURRENT FROM THE CURRENT SOURCE WILL PASS THROUGH THE RESISTOR, R .



$Z_L = j\omega L$

9. ASSUMING $V_s = 10$ VOLTS RMS, FIND THE VOLTAGE (IN PHASOR FORM) OF ACROSS THE 4 HENRY INDUCTOR. SIMPLIFY YOUR ANSWER TO RECTANGULAR FORM (HINT: USE A VOLTAGE DIVIDER).

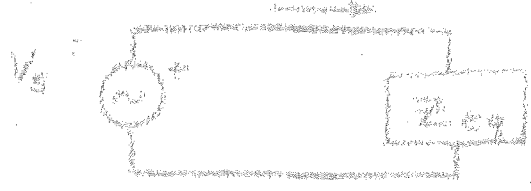10. REDUCE THE CIRCUIT TO AN EQUIVALENT IMPEDENCE. THAT IS, FIND $Z_{eq} + I$



STATE YOUR ANSWER IN POLAR FORM.

QUESTIONS SOLUTIONS

1. a. $e^{j\frac{\pi}{2}} = \cos\frac{\pi}{2} + j \sin\frac{\pi}{2}$
 $\cos\frac{\pi}{2} = 0, \sin\frac{\pi}{2} = 1 \Rightarrow e^{j\frac{\pi}{2}} = j$

b. $w = 1 + j$

$\theta = \tan^{-1} 1 = \pi/4$

$r = \sqrt{2} \Rightarrow w = \sqrt{2} e^{j\pi/4}$

$w^* = \frac{1}{\sqrt{2}} e^{-j\pi/4} = \frac{1}{\sqrt{2}} e^{-j\pi/4}$

$= \frac{1}{\sqrt{2}} \cos\frac{\pi}{4} - j \frac{1}{\sqrt{2}} \sin\frac{\pi}{4}$

$= \frac{1}{\sqrt{2}} \cdot \frac{1}{\sqrt{2}} - j \frac{1}{\sqrt{2}} \cdot \frac{1}{\sqrt{2}} = \frac{1}{2} - j\frac{1}{2}$

2. a. FROM THE SKETCH:

$V_0 = 4$ VOLTS $f = 1/10 = 10 \frac{\text{CYCLES}}{\text{SEC}}$


$V(0) = V_0 \cos \phi = 4 \cos \phi = 2$

$\Rightarrow \cos \phi = 1/2 \therefore \phi = -\pi/3$ radians

b. $T = 10$ SECOND

$\omega = 2\pi f = 20\pi \frac{\text{RADIAN}}{\text{SEC}}$

c.

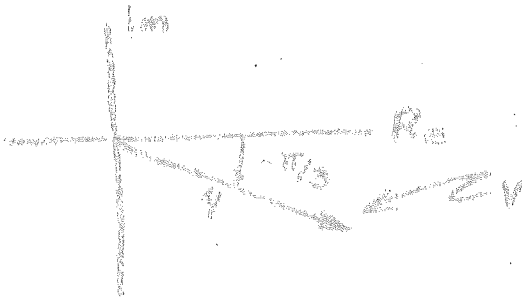

3. FROM SKETCH; $T = 2$ SECONDS

$$I_{\text{AVE}} = \frac{1}{T} \int_T i(t) dt$$
$$= \frac{1}{2} \left[\int_0^1 (1) dt + \int_1^2 (0) dt \right]$$
$$= \frac{1}{2} [1 + 0] = \frac{1}{2} \text{ AMP.}$$

$$I_{\text{RMS}} = \sqrt{\frac{1}{T} \int_T i^2(t) dt}$$

$$I_{\text{RMS}}^2 = \frac{1}{2} \left[\int_0^1 (1)^2 dt + \int_1^2 (0)^2 dt \right]$$
$$= \frac{1}{2} \Rightarrow I_{\text{RMS}} = \frac{1}{\sqrt{2}} \text{ AMP}$$

4. USE THE FOUR NUGGETS:

(1) $V_r(0^-) = 0$ (NO CURRENT IS FLOWING BEFORE THE SWITCH CLOSES)

(2) $V_r(0^+) = 2$ VOLTS (USE A VOLTAGE DIVIDER RECOGNIZING THAT, AT $t=0^+$, THE CAPACITOR ACTS AS A SHORT)

(3) $V_r(\infty) = 0$ (AT $t=\infty$, CAPACITOR ACTS LIKE AN OPEN CIRCUIT)

(4) $T = R_{\text{eq}} C = (2+4) \text{ } \mu\text{s} = 6 \text{ SEC}$




$$V_r(t) = \begin{cases} 0 & ; t < 0 \\ 2e^{-t/6} & ; t > 0 \end{cases}$$

5. ALL CURRENT WILL PASS THRU RESISTOR WHEN $L \neq C$ ARE IN RESONANCE AT WHICH POINT THEY LOOK LIKE AN OPEN CIRCUIT, THUS, OUR DESIRED INDUCTANCE IS FROM THE RELATION:

$$f = \frac{1}{2\pi\sqrt{LC}} \Rightarrow 2\pi f = \omega = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow LC = \frac{1}{\omega^2} \Rightarrow L = \frac{1}{C\omega^2}$$
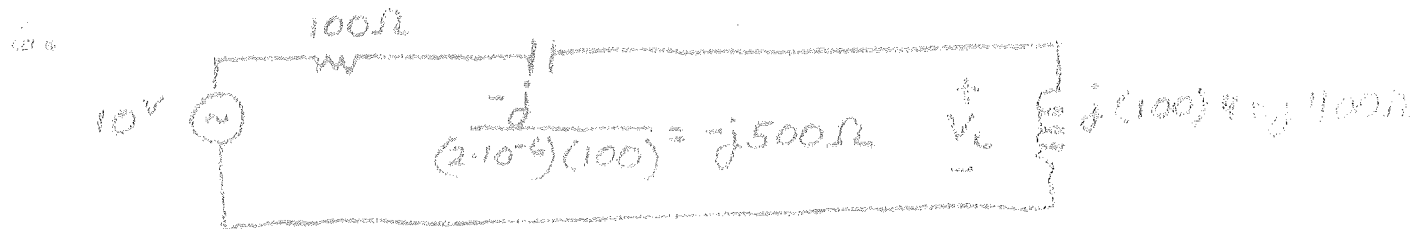
$$L = \frac{1}{(1 \times 10^{-4})(100)^2} = \frac{1}{10^{-2}} = 100 \text{ H}$$



a. BY VOLTAGE DIVIDER

$$V_L = \frac{j400}{100 - j500 + j400} \cdot 10 = \frac{j400}{100 - j100} \cdot 10$$


$$= \frac{j40}{1-j} \cdot \frac{1+j}{1+j} = \frac{-40 + j40}{2} = -20 + j20 \text{ volts}$$

b. $Z_{eq} = 100 - j500 + j400 = 100 - j100 \Omega$

$$\theta = -45^\circ = -\frac{\pi}{4}$$

$$r = \sqrt{2} \cdot 100$$
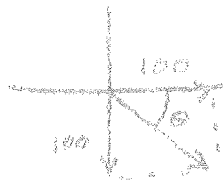
$$\Rightarrow Z_{eq} = \sqrt{2} \cdot 100 e^{-j\frac{\pi}{4}}$$



Complex Exponentials (Euler's)

Let $e^{j\theta} = \cos \theta + j \sin \theta$ and $e^{-j\theta} = \cos \theta - j \sin \theta$

$$\frac{d}{dt} e^{j\theta} = \frac{d}{dt} (\cos \theta + j \sin \theta)$$

$$\Rightarrow \frac{d}{dt} (\cos \theta) + j \frac{d}{dt} (\sin \theta) = -\sin \theta + j \cos \theta = j (\cos \theta + j \sin \theta) = j e^{j\theta}$$

Given Euler's Equation:

$$e^{j\theta} = \cos \theta + j \sin \theta$$

Show that:

$$(1) \cos \theta = \frac{1}{2} [e^{j\theta} + e^{-j\theta}]$$

$$(2) \sin \theta = \frac{1}{j} [e^{j\theta} - e^{-j\theta}]$$

Let

$$e^{j\theta} = \cos \theta + j \sin \theta$$

$$\Rightarrow e^{j(-\theta)} = e^{-j\theta} = \cos(-\theta) + j \sin(-\theta)$$

$$\text{or } e^{-j\theta} = \cos \theta - j \sin \theta$$

$$\Rightarrow e^{j\theta} = \cos \theta + j \sin \theta \quad (a)$$

$$e^{-j\theta} = \cos \theta - j \sin \theta \quad (b)$$

Adding (a) + (b) gives

$$e^{j\theta} + e^{-j\theta} = 2 \cos \theta$$

$$\Rightarrow \cos \theta = \frac{1}{2} [e^{j\theta} + e^{-j\theta}]$$

Subtracting (a) - (b) gives

$$e^{j\theta} - e^{-j\theta} = j 2 \sin \theta$$

$$\Rightarrow \sin \theta = \frac{1}{j 2} [e^{j\theta} - e^{-j\theta}]$$

If any of the above questions are not clear, please ask me in the comments or DM. I will be happy to help.

If you are interested in learning more about this topic, please check out my video on "Complex Numbers and Euler's Formula".

Thank you for watching!

Date: 10/10/2023

$$w = a + jb = r e^{j\theta}$$

SHOW

(a) $|w| = |w^*|$

METHOD 1: $|w| = |a + jb| = \sqrt{a^2 + b^2}$

$$|w^*| = |a - jb| = \sqrt{a^2 + (-b)^2}$$

METHOD 2: $|w| = |r e^{j\theta}| = r |e^{j\theta}| = r$

$$|w^*| = |r e^{-j\theta}| = r |e^{-j\theta}| = r$$

(b) $|w|^2 = w w^*$

METHOD 1: $|w|^2 = |a + jb|^2 = (a^2 + b^2) = a^2 + b^2$

$$w w^* = (a + jb)(a - jb) = a^2 + b^2$$

METHOD 2: $|w|^2 = |r e^{j\theta}|^2 = r^2 |e^{j\theta}|^2 = r^2$

$$w w^* = (r e^{j\theta})(r e^{-j\theta}) = r^2 e^{j(\theta - \theta)} = r^2$$

(c) $\arg w = -\arg w^*$

METHOD 1: $\arg w = \arg a + jb = \tan^{-1} \frac{b}{a}$

$$\arg w^* = \arg a - jb = \tan^{-1} \frac{-b}{a}$$

$$= -\tan^{-1} \frac{b}{a}$$

METHOD 2: $\arg w = \arg r e^{j\theta} = \theta$

$$\arg w^* = \arg r e^{-j\theta} = \arg r e^{j(-\theta)} = -\theta$$

EXTRA CREDIT FOR PROBLEM (LOSER TIME)

GIVEN THAT β AND γ ARE CONSTANTS, FIND THAT

$$f_2(x) = \frac{\beta e^x + \gamma - \beta^2 e^{2x} + (\beta^2 + \gamma^2) e^x - \beta^2}{e^x - 1}$$


FIND

$$f'(x) = \frac{\beta^2}{\pi} \left[\frac{1}{\beta^2 + \gamma^2} \left(\frac{d}{dx} \right) - \frac{1}{\beta^2 + \gamma^2} \left(\frac{d}{dx} \right) \right]$$

WHERE $f_1(x)$ AND $f_2(x)$ REFER TO $f_2(x)$ USING THE "+" AND THE "-" SIGNS RESPECTIVELY

HOMEWORK

(13)

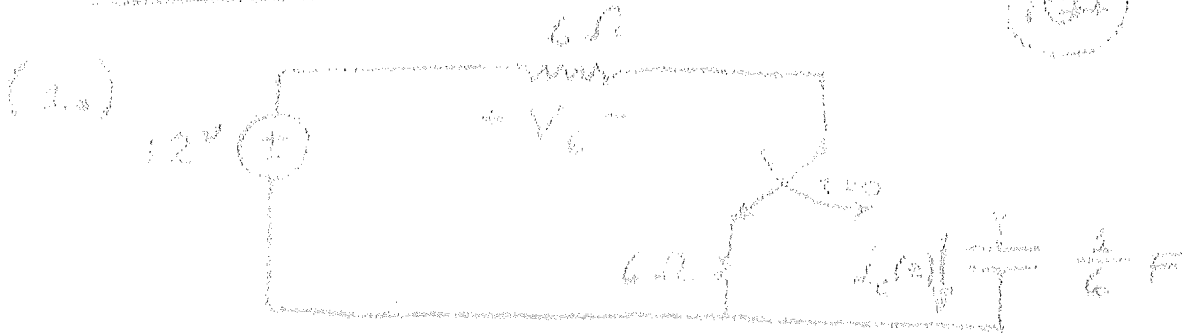


(a) USE THE "4 NUGGETS" TO FIND $V_c(t)$

(b) (i) USE THE "4 NUGGETS" TO FIND $i_c(t)$

(ii) USING KIRCHHOFF'S VOLTAGE LAW, SHOW THAT, FOR $t > 0$, $i_c(t)$ MUST SATISFY THE DIFFER. EQ.:

$$\frac{di_c(t)}{dt} = -i_c(t)$$

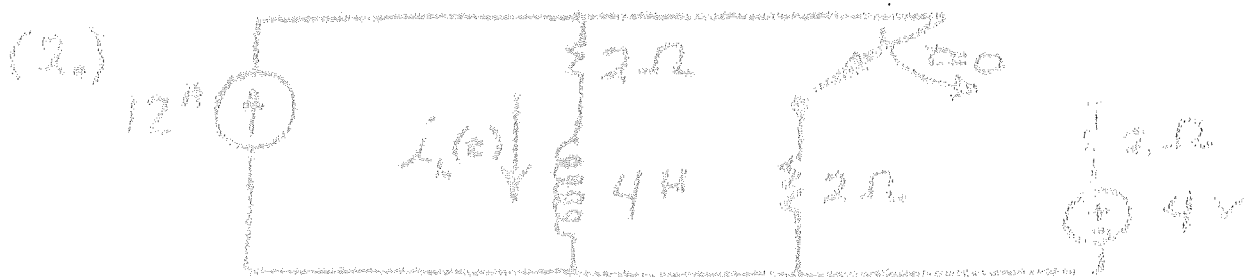(iii) VERIFY THAT YOUR ANSWER IN (b) SATISFIES THIS DIFFER. EQ.



USING THE "4 NUGGETS", FIND $i_L(t)$
 [HINTS: TO FIND $i_L(\infty)$, USE THE SUPERPOSITION THEOREM WITH VOLTAGE AND CURRENT DIVIDERS.]

HOMEWORK



(1.)



(a) USE THE "4 NUGGETS" TO FIND $V_0(t)$


(b) (1) USE THE "4 NUGGETS" TO FIND $i_C(t)$

(ii) USING KIRCHHOFF'S VOLTAGE LAW, SHOW THAT, FOR $t > 0$, $i_C(t)$ MUST SATISFY THE DIFFER. EQ:

$$\frac{di_C(t)}{dt} = -i_C(t)$$

(iii) VERIFY THAT YOUR ANSWER IN (b) SATISFIES THIS DIFFER. EQ.


(2.)

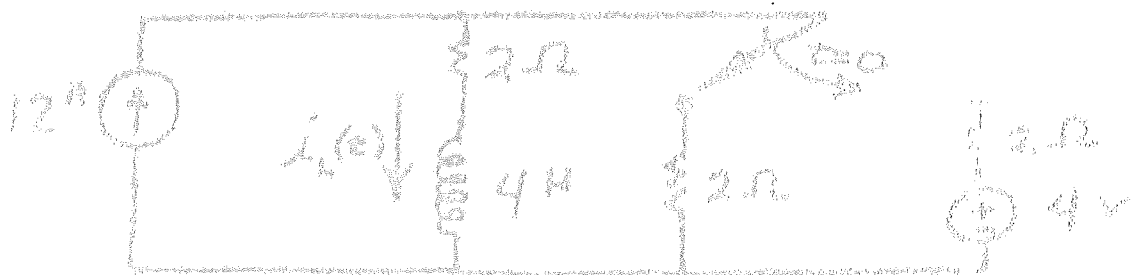

USING THE "4 NUGGETS", FIND $i_L(t)$
 [HINT: TO FIND $i_L(\infty)$, USE THE SUPERPOSITION THEOREM WITH VOLTAGE AND CURRENT DIVIDERS]

HOMEWORK SOLUTION

PROBLEM:

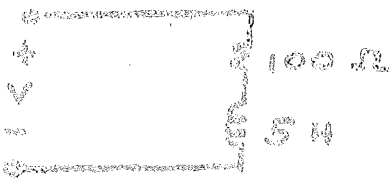

THE IMPEDANCE OF THIS CIRCUIT IS, AT $\omega = 100$, $Z = 100 + j50$. FIND THE ADMITTANCE (Y), CONDUCTANCE (G), AND THE SUSCEPTANCE (B).

SOLUTION:

$$Y \triangleq \frac{1}{Z} = \frac{1}{100 + j50} = \frac{1}{50} \cdot \frac{1}{(2 + j)}$$

USE "COMPLEX CONJUGATE" TRICK:

$$Y = \frac{1}{50} \cdot \frac{1}{(2 + j)} \cdot \frac{(2 - j)}{(2 - j)}$$
$$= \frac{1}{50} \frac{2 - j}{4 - j2 + j2 + 1} = \frac{2 - j}{50(5)} = \frac{2 - j}{250}$$

$$\Rightarrow Y = \left(\frac{1}{125} - \frac{j}{250} \right) U \quad (\text{MHOS})$$

NOW, IN GENERAL

$$Y = G + jB$$

THUS, FROM THE EXPRESSION FOR Y :

$$G = \frac{1}{125} U = 0.008$$

$$\text{AND } B = -\frac{1}{250} U = -0.004$$

HOMEWORK SOLUTION

1. PROB: FIND f_{RMS} AND f_{AVE} WHEN, FOR a AND ϕ CONSTANT, $f(t) = a \cos(2\pi ft + \phi)$

SOLUTION:

$$\begin{aligned} \dots (a) f_{AVE} &\triangleq \frac{1}{T} \int_T f(t) dt \\ &= \frac{a}{T} \int_0^T \cos(2\pi ft + \phi) dt \\ &= \frac{a}{T} \int_0^T \cos\left[\frac{2\pi t}{T} + \phi\right] dt \quad (T = \frac{1}{f}) \\ &= \frac{a}{T} \left(\frac{T}{2\pi}\right) \sin\left\{\frac{2\pi t}{T} + \phi\right\} \Big|_0^T \\ &= \frac{a}{2\pi} [\sin(2\pi + \phi) - \sin \phi] \end{aligned}$$

$$\text{BUT } \sin(2\pi + \phi) = \sin \phi$$

$$\Rightarrow f_{AVE} = 0$$

$$(b) f_{RMS} \triangleq \sqrt{\frac{1}{T} \int_T f^2(t) dt} = f_{EFF}$$

$$\begin{aligned} \therefore f_{RMS}^2 &= \frac{a^2}{T} \int_0^T \cos^2\left(\frac{2\pi t}{T} + \phi\right) dt \\ &= \frac{a^2}{2T} \int_0^T [1 + \cos\left\{\frac{4\pi t}{T} + 2\phi\right\}] dt \\ &= \frac{a^2}{2T} \left[t + \left(\frac{T}{4\pi}\right) \sin\left\{\frac{4\pi t}{T} + 2\phi\right\} \right]_0^T \\ &= \frac{a^2}{2T} [(T - 0) \\ &\quad + \left(\frac{T}{4\pi}\right) \{\sin(4\pi + 2\phi) - \sin 2\phi\}] \end{aligned}$$

$$\text{BUT } \sin(4\pi + 2\phi) = \sin 2\phi$$

$$\Rightarrow f_{RMS}^2 = \frac{a^2}{2}$$

OR

$$f_{RMS} = \frac{a}{\sqrt{2}}$$

NOTE THAT THE RMS VALUE OF ANY SINUSOID IS INDEPENDENT OF ITS FREQUENCY (f) AND PHASE (ϕ).

1. PROB: SHOW THAT $f(t) = a = \text{CONSTANT}$ IS
"PERIODIC." FIND f_{RMS} AND f_{AVE} .

SOLUTION:

(a) OBVIOUSLY, FOR ANY T , $f(t) = f(t+T) = a$.
THUS, BY DEFINITION, $f(t) = a$ IS
"PERIODIC."

$$(b) f_{\text{AVE}} = \frac{1}{T} \int_0^T f(t) dt \\ = \frac{1}{T} \int_0^T a dt = \frac{1}{T} (aT) = a$$


$$(c) f_{\text{RMS}}^2 = \frac{1}{T} \int_0^T a^2 dt \\ = \frac{1}{T} (a^2 T) = a^2$$

OR

$$f_{\text{RMS}} = a = f_{\text{AVE}}$$


TRANSIENT ANALYSIS

(3)

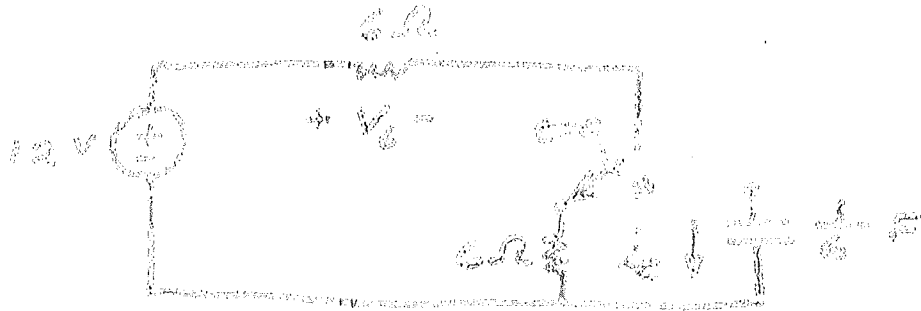

(a) FIND $V_L(t)$

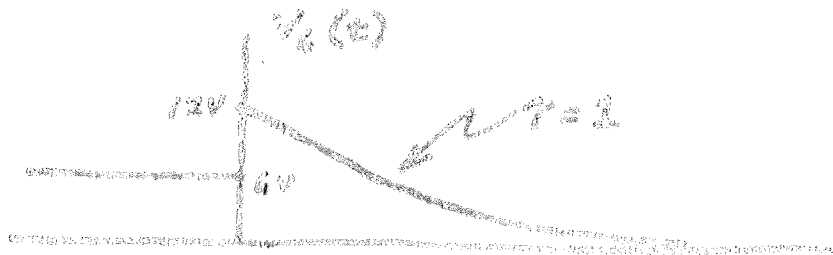1. $V_L(0^-) = 6 \text{ V}$ (FROM VOLTAGE DIVIDER)
2. $V_L(0^+) = 12 \text{ V}$ (SINCE VOLTAGE ACROSS CAPACITOR REMAINS 0 FOR $t = 0^+$)
3. $V_L(\infty) = 0$ (@ $t = \infty$, CAPACITOR ACTS AS AN OPEN CIRCUIT)
4. $\tau = RC = (6\Omega)(\frac{1}{6} \text{ F}) = 1 \text{ SEC}$



THIS:

$$V_L(t) = \begin{cases} 6 & ; t < 0 \\ 12e^{-t} & ; t > 0 \end{cases}$$

(3) FIND $i_c(t)$

(1) $i_c(0^-) = 0$ (SINCE CAPACITOR IS OUT OF CIRCUIT FOR $t < 0$)

(2) $i_c(0^+) = 2 \text{ AMP}$ (CAPACITOR VOLTAGE = 0 FOR $t = 0^+ \Rightarrow 12 \text{ V}$ ARE ACROSS 6Ω RESISTOR $\Rightarrow \frac{12 \text{ V}}{6 \Omega} = 2 \text{ AMPS}$ ARE THRU RESISTOR \neq CAPACITOR)

(3) $i_c(\infty) = 0$ (@ $t = \infty$, CAPACITOR ACTS AS AN OPEN CIRCUIT)

(4) $\tau = 1 \text{ SEC}$



THUS:

$$i_c(t) = \begin{cases} 0 & ; t < 0 \\ 2e^{-t} & ; t > 0 \end{cases}$$

(ii) SUMMING VOLTAGES AROUND LOOP

FOR $t > 0$:

$$-12 + 6 i_c(t) + \left[6 \int_{0^+}^t i_c(t) dt + V_c(t_0) \right] = 0$$

DIFFERENTIATE:

$$6 \frac{d i_c(t)}{dt} + 6 i_c(t) = 0$$

OR

$$\frac{d i_c}{dt} = -i_c(t)$$

(iii) OUR SOLUTION IN (i) WAS

$$i_L(t) = 2e^{-t} \quad ; t > 0$$

THUS

$$\frac{di_L}{dt} = -2e^{-t} = -i_L(t)$$

(2)




(1) $i_L(0^-) = 6$ AMPS (INDUCTOR ACTS LIKE A SHORT, AND WE ARE LEFT WITH A CURRENT DIVIDER.)

(2) $i_L(0^+) = 6$ AMPS (ENERGY CONTINUITY)

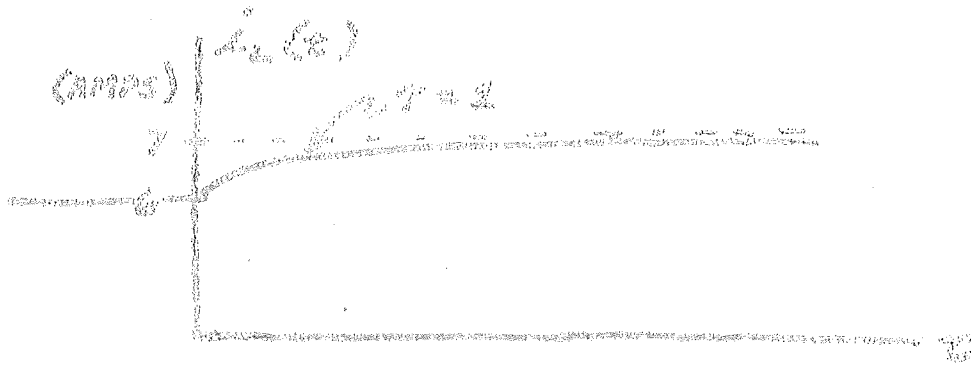(3) $i_L(\infty) = 7$ AMPS (@ ∞ , L ACTS AS SHORT. USE SUPERPOSITION ON REMAINING CIRCUIT. SHORTING 4V SUPPLY, AND LOOKING AT CURRENT SUPPLY, WE GET, USING A CURRENT DIVIDER, $i_L(\infty) = 6$ AMPS DUE TO CURRENT SUPPLY. NEXT, OPEN CURRENT SUPPLY AND LOOK AT EFFECT OF 4V SUPPLY. BY VOLTAGE DIVIDER, WE HAVE 2 VOLTS ACROSS OUR RESISTOR $\Rightarrow i_V(\infty) = \frac{2}{2} = 1$ AMP. USING SUPERPOSITION, $i_L(\infty) = i_L(\infty) + i_V(\infty) = 7$ AMPS

$$(4) \tau = \frac{L}{R_{eq}} = \frac{4H}{2R + 2R} = 1 \text{ sec}$$



$$i_1(t) = \begin{cases} 6 & ; t < 0 \\ 6 + 1(1 - e^{-t/\tau}) & ; t > 0 \end{cases}$$

$$= \begin{cases} 6 & ; t < 0 \\ 7 - e^{-t} & ; t > 0 \end{cases}$$

"WORK MAKES LIFE SWEET"

OLD GERMAN PROVERB.

"EH?"

OLD GERMAN




(a) GIVEN THAT $\omega = 100 \frac{\text{RAD}}{\text{SEC}}$, AND USING I AS A REFERENCE, SKETCH A PHASOR DIAGRAM OF I AND V_s .

(b) FROM THIS SKETCH, FIND THE POWER ANGLE, θ .

(c) WHAT IS THE ^{AVERAGE} ACTIVE POWER ASSOCIATED WITH THE $1k\Omega$ RESISTOR? WHAT PERCENT OF P_{VI} IS THUS UTILIZED AS ACTIVE (USEFUL) POWER?

(d) IS THE CIRCUIT INDUCTIVE OR CAPACITIVE?

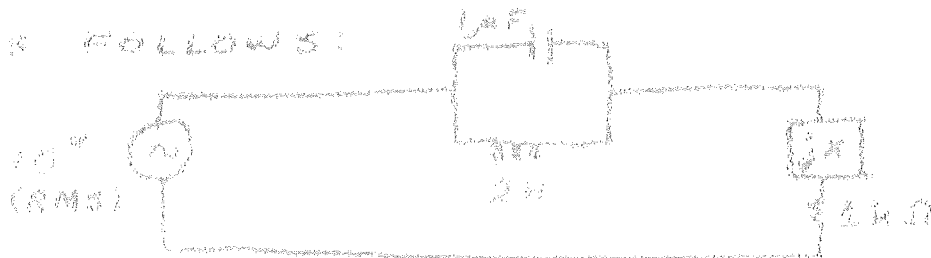2. WE WISH TO COMPENSATE THE ABOVE CIRCUIT AS FOLLOWS:




(a) FIND jX SUCH THAT THE RATIO OF ACTIVE POWER TO V_I IS MAXIMUM (HINT: SET ALL SERIES REACTANCE TO ZERO)

(b) IS X CAPACITIVE OR INDUCTIVE? THAT IS, DO WE NEED A CAPACITOR FOR COMPENSATION, OR DO WE NEED AN INDUCTOR?

(c) AT $\omega = 100$, WHAT IS THE REQUIRED VALUE OF THE CAPACITOR OR INDUCTOR?

(d) AFTER COMPENSATION, WHAT IS THE TOTAL ACTIVE POWER ASSOCIATED WITH THE $1k\Omega$ RESISTOR?


3.

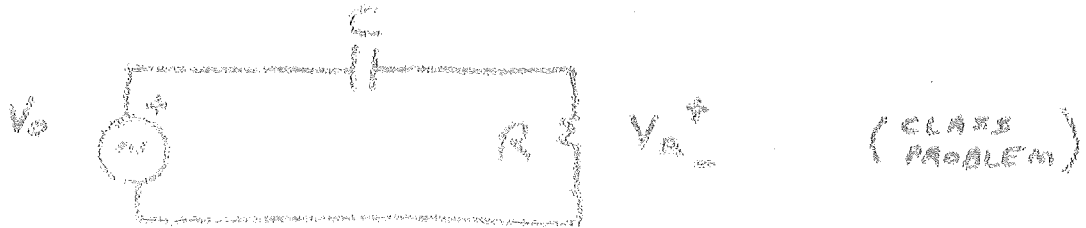

SHOW THAT

$$|V_R|/|V_0| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

4.

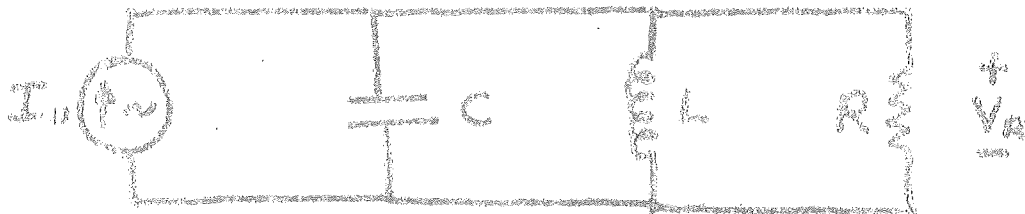

(a) FIND $|V_R|$ AS A FUNCTION OF I_0 , ω , C , R , AND L (USE CURRENT DIVIDER)

(b) WHAT IS $|V_R(\omega=0)|$?

WHAT IS $|V_R(\omega=\infty)|$?

FOR WHAT VALUE OF ω IS $|V_R(\omega)|$ MAXIMUM? WHAT IS

$|V_R(\omega)|$ AT THIS FREQUENCY?


(c) MAKE A GENERAL SKETCH OF

$\frac{|V_R|}{I_0 R}$ VS ω USING THE

RESULTS OF (b).

(d) IF WE WERE TO INCREASE THE VALUE OF L , WHAT WOULD HAPPEN TO THE PEAK OF THE CURVE IN PART C?

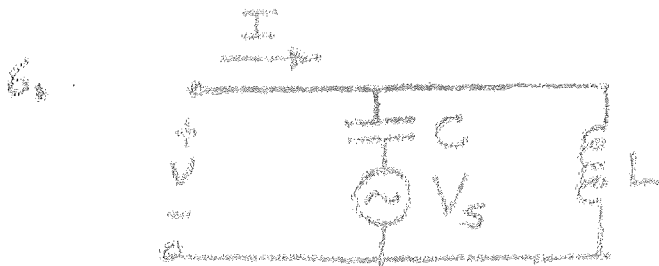5. THE FREQUENCY RESPONSE IN PROBLEM (3) WAS SHOWN IN CLASS TO BE A ~~LOW~~^H PASS FILTER. IF JOHNNY CASH (LOW VOICE) AND TINY TIM (HI VOICE) SANG A DUET INTO A MICROPHONE (CORRESPONDING TO V_o) AND YOU LISTENED THROUGH HEADPHONES (CORRESPONDING TO R AND V_R), WHICH OF THE TWO SINGERS WOULD YOU HEAR BEST? WHY?




(a) SHOW THAT: $I_{sc} = -j\omega C V_s$
 $V_{oc} = \frac{\omega L V_s}{\omega L - 1/j\omega C}$ AND $Z_{eq} = \frac{-j\omega L}{\omega^2 LC - 1}$

(b) SKETCH THE THEVININ AND NORTON EQUIVALENT CIRCUITS


(c) WHAT DO ^{ES} THE ^{→ NORTON →} CIRCUIT CORRESPOND TO WHEN L AND C ARE AT RESONANCE?

7.

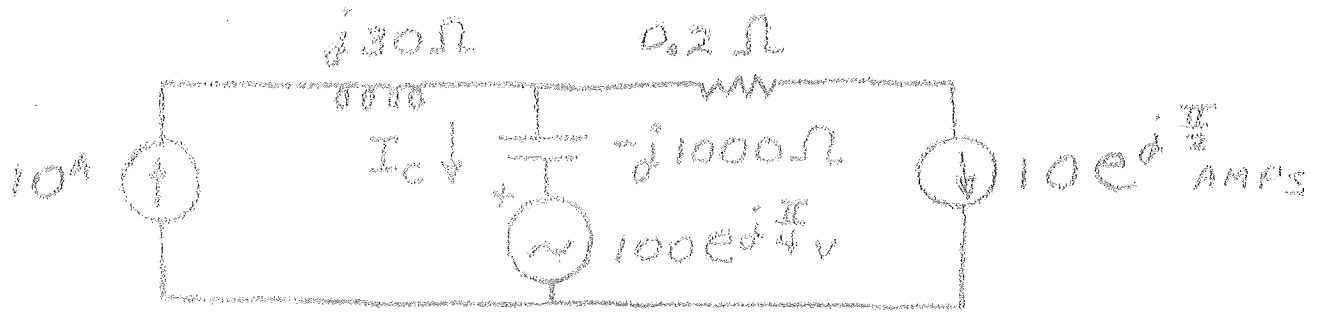

- (a) USING SUPERPOSITION, FIND I_c
 (b) WHICH LUMPED CIRCUIT ELEMENTS
 HERE DO NOT HAVE AN EFFECT
 ON THE VALUE OF I_c ?

8.

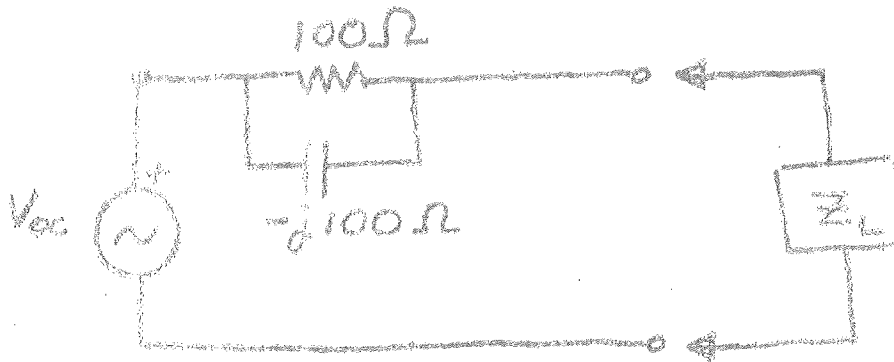


- (a) FIND Z_L SUCH THAT MAXIMUM
 POWER IS TRANSFERRED TO
 THE LOAD.
 (b) ASSUMING THAT $\omega = 25 \frac{\text{RAD}}{\text{SEC}}$,
 DETERMINE A TWO ELEMENT
 SERIES COMBINATION WHICH
 WILL GIVE THE DESIRED Z_L .
 SPECIFY EACH ELEMENT'S
 VALUE IN OHMS, FARADS, OR
 HENRIES AS APPROPRIATE.

9. Pg. 203, #5

HOMEWORK SOLUTIONS

1. $10 \angle 0^\circ$

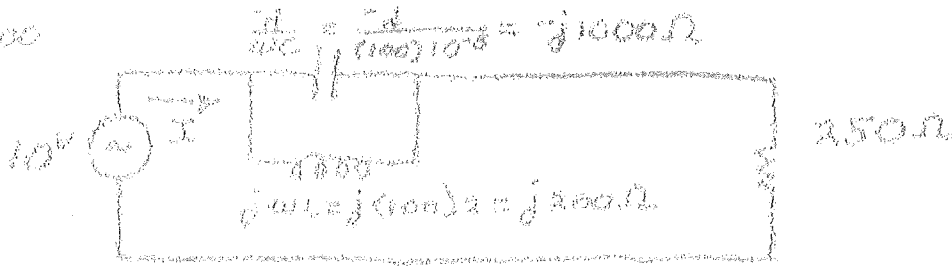


a. COMBINING L & C:

$$\frac{1}{Z_{eq}} = \frac{1}{j200} + \frac{1}{-j1000} = \frac{1}{j200} \left[1 - \frac{1}{5} \right]$$

$$= \frac{1}{j200} \left(\frac{4}{5} \right) = \frac{1}{j1250} \Rightarrow Z_{eq} = +j1250 \Omega$$

COMBINING THIS AND RESISTOR GIVES ETC

$$Z_{eq} = 250 + j250$$

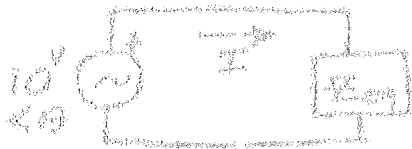

NOW $V = IZ$

$$10 \angle \theta = [1250] [250 + j250]$$

$$10 e^{j\theta} = 250 I (1 + j)$$

$$= \sqrt{2} 250 I e^{j45^\circ}$$


EQUATING THE MAGNITUDES:

$$10 = \sqrt{2} 250 I \Rightarrow I = \frac{1}{\sqrt{2} 25} \text{ AMPS}$$

EQUATING ARG (): :

$$\theta = +\pi/4$$
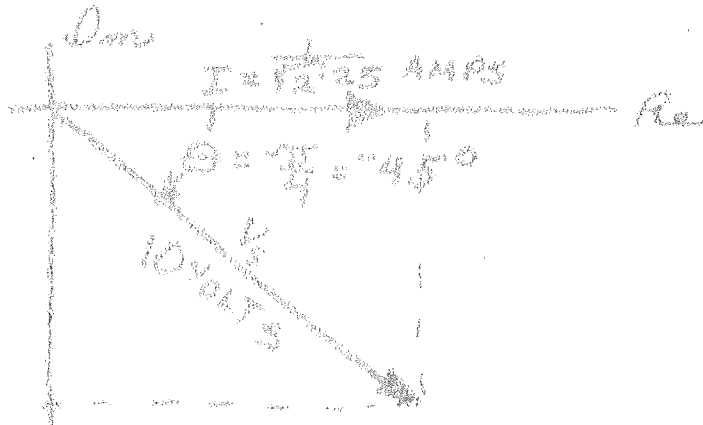
$$\Rightarrow V = 10 e^{+j\pi/4}, \quad I = \frac{1}{\sqrt{2} 25} = 0.0283$$



b. OBVIOUSLY, $\theta = +\frac{\pi}{4} = +45^\circ$

c. $I = \sqrt{2} \cdot 25$ AMPS (RMS)

$P_R =$ AVERAGE POWER IN RESISTOR

$$= I^2 R = \frac{\text{RMS}}{2} \cdot 250 \Omega = \frac{1}{2} \text{ WATT}$$

$$|VI| = P_R / \cos \theta = \sqrt{2} P_R = \sqrt{2} / 5 \text{ VOLT-AMPS}$$


$$\text{THUS } P_R / |VI| = \frac{1/2}{\sqrt{2}} = 70.7\%$$

d. THE CIRCUIT IS CAPACITIVE SINCE THE SUM TOTAL OF THE REACTANCE IS NEGATIVE.

2. IN PROB. 1, WE SHOWED THAT

$$Z_{eq} = 250 - j250 \Omega$$

THUS OUR CIRCUIT IS

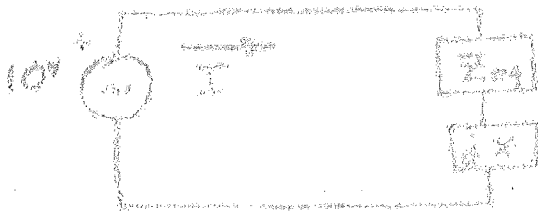

a. TO MAXIMIZE RATIO OF USEFUL POWER TO $|VI|$, WE SET ALL REACTANCE TO ZERO:

$$0 = j\omega L [Z_{eq}] + jX = -j250 + jX$$

$$\text{THUS } X = 250 \Omega$$

b. SINCE $X > 0$, IT IS INDUCTIVE

$$X = \omega L \Rightarrow 250 = (100) L \Rightarrow L = 2.5 \text{ HENRIES}$$


c. AFTER COMPENSATION, WE ARE @

RESONANCE AND $V_R = RI \Rightarrow$ THUS

$$P_{\text{ACTIVE}} = \frac{V_R^2}{R} = \frac{100^2}{250} = 0.4 \text{ WATTS}$$

(NOTE THIS IS LARGER THAN OUR POWER IN PROBLEM 1c).

3.

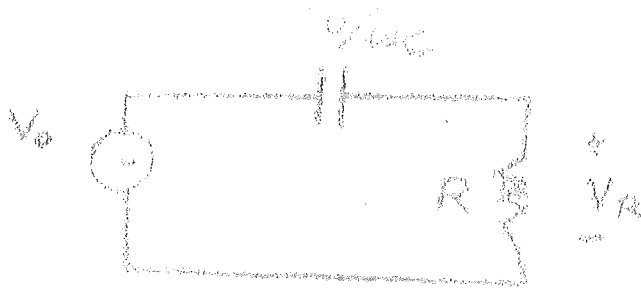

BY VOLTAGE DIVIDER:

$$V_R = \frac{R}{R - j/\omega C} V_0 = \frac{V_0}{1 - j/\omega RC}$$

$$\Rightarrow V_R/V_0 = \frac{1}{1 - j/\omega RC}$$

$$\Rightarrow |V_R/V_0| = \frac{1}{\sqrt{1 + (1/\omega RC)^2}}$$

4.



(a) BY CURRENT DIVIDER

$$I_R = \frac{1/R}{1/R - j/\omega C + j\omega L} I_0$$

$$= \frac{I_0}{1 + j(\omega RC - R/\omega L)}$$

$$V_R = I_R R = \frac{I_0 R}{1 + j(\omega RC - R/\omega L)}$$

THUS

$$|V_R| = \frac{|I_0| R}{\sqrt{1 + (\omega RC - \frac{R}{\omega L})^2}}$$


(b) $|V_R(\infty)| = |V_R(0)| = 0$

$|V_R(\omega)|$ WILL BE MAXIMUM WHEN L & C ARE AT RESONANCE:


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

AT $\omega = \omega_0$; $|V_R(\omega)| = |I_0| R$


(c) $\left| \frac{V_R}{I_0 R} \right| = \frac{1}{\sqrt{1 + (\omega RC - \frac{R}{\omega L})^2}}$

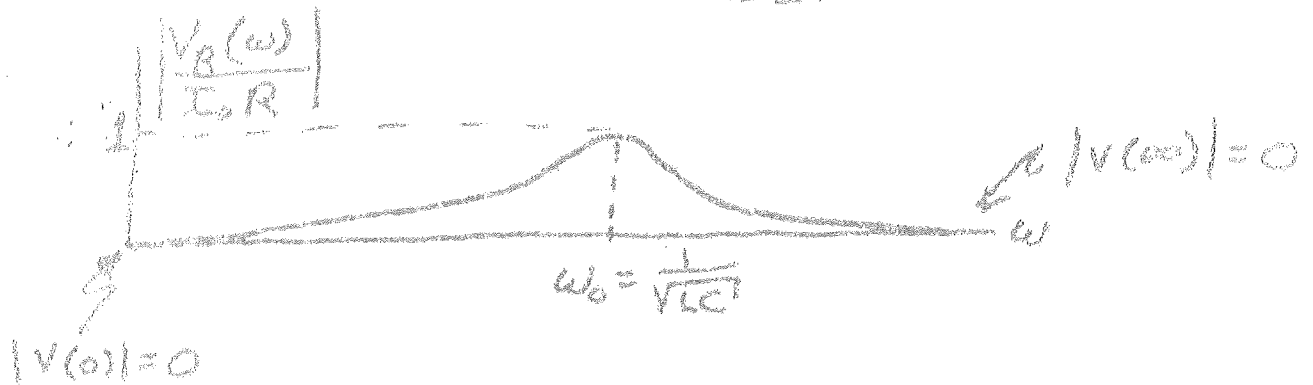

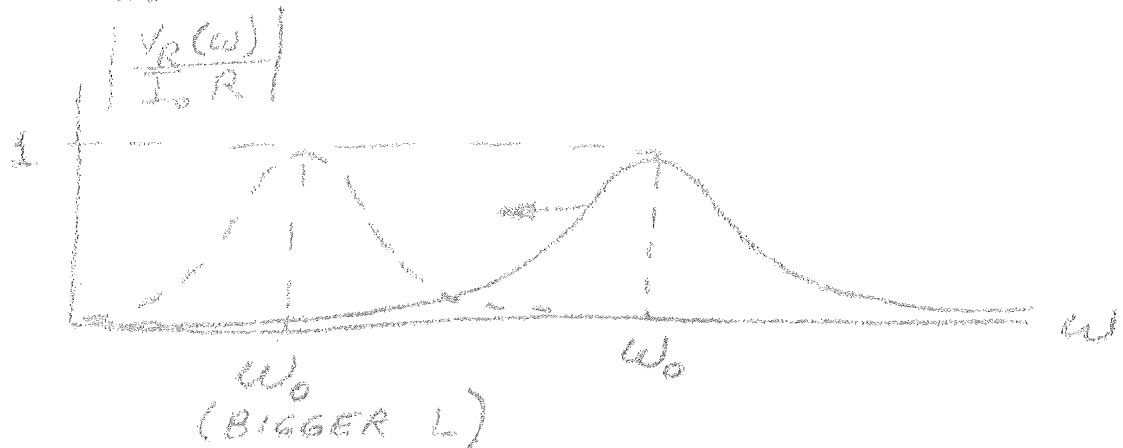(d) INCREASING L DECREASES $\omega_0 = \frac{1}{\sqrt{LC}}$
 THUS, THE PEAK OF THE CURVE
 WILL SHIFT TO THE LEFT




6. (a) FIND Z_{eq}

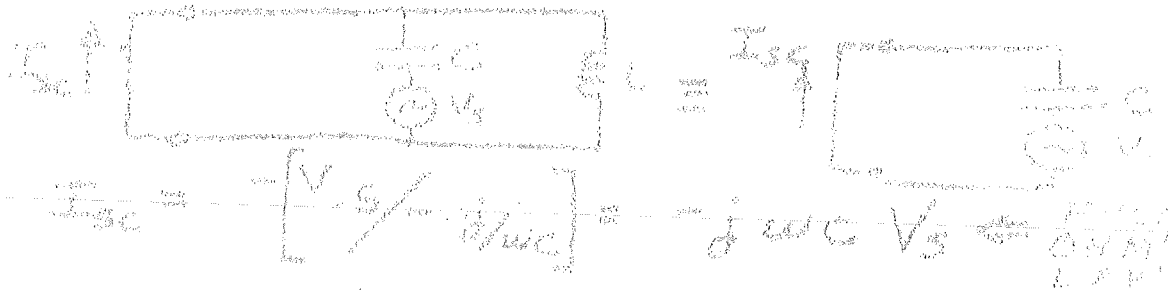

$$I_{sc} = \frac{V_s}{j\omega C} = j\omega C V_s \quad \leftarrow \text{OHMS LAW}$$

FIND V_{oc}

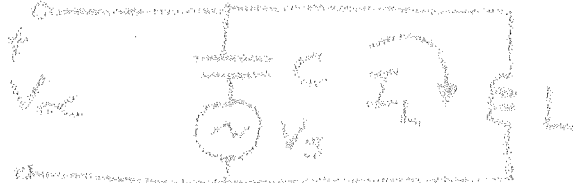

$$V_s = \left(\frac{1}{\omega C} + j\omega L \right) I_L \quad \leftarrow \text{KIRCHHOFF LOOP LAW}$$

$$\Rightarrow I_L = \frac{V_s}{\frac{1}{\omega C} + j\omega L} = \frac{V_s}{j(\omega L - \frac{1}{\omega C})}$$

SINCE L IS IN PAR. WITH V_{oc} :

$$V_{oc} = (j\omega L) I_L \quad \leftarrow \text{OHMS LAW}$$

$$= \frac{(j\omega L) V_s}{j(\omega L - \frac{1}{\omega C})} = \frac{\omega L V_s}{\omega L - \frac{1}{\omega C}}$$


NOW

$$Z_{eq} = \frac{V_{oc}}{-I_{sc}} = \frac{\frac{\omega L V_s}{\omega L - \frac{1}{\omega C}}}{-j\omega C V_s}$$


$$= \frac{-jL}{C(\omega L - \frac{1}{\omega C})}$$

$$= \frac{-jL}{\omega LC - \frac{1}{\omega}} = \frac{-j\omega L}{\omega^2 LC - 1}$$

(b) NORTON

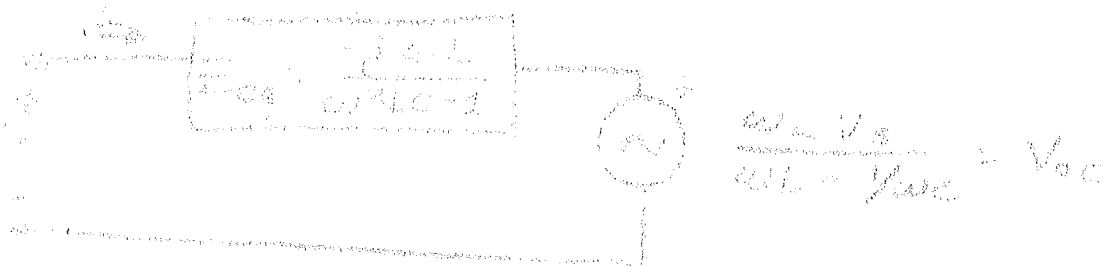


NORTON

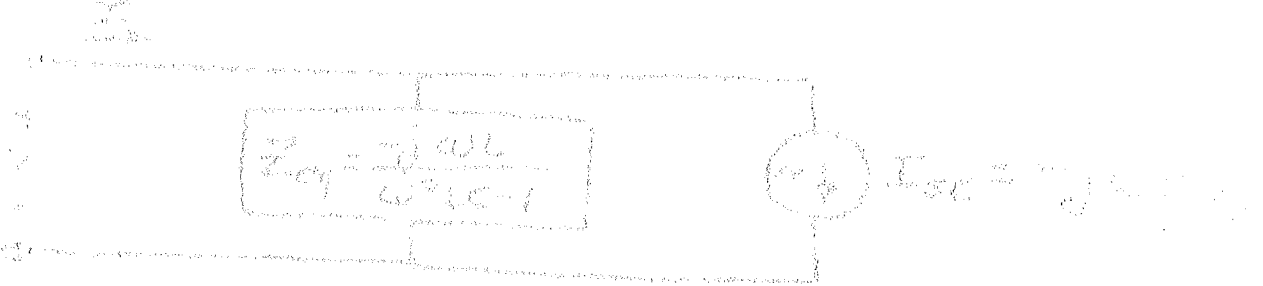


(c) AT RESONANCE, $\omega^2 = 1/LC = \omega_0^2$

AND $Z_{eq} = \infty = \text{OPEN CIRCUIT}$,


THE NORTON EQUIVALENT BECOMES

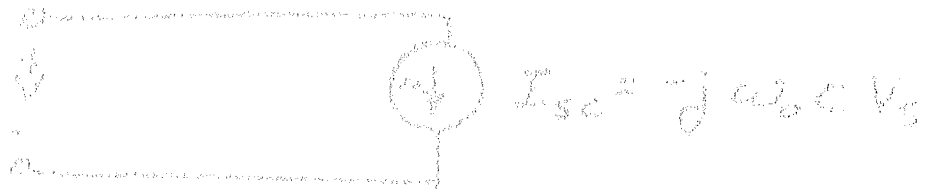

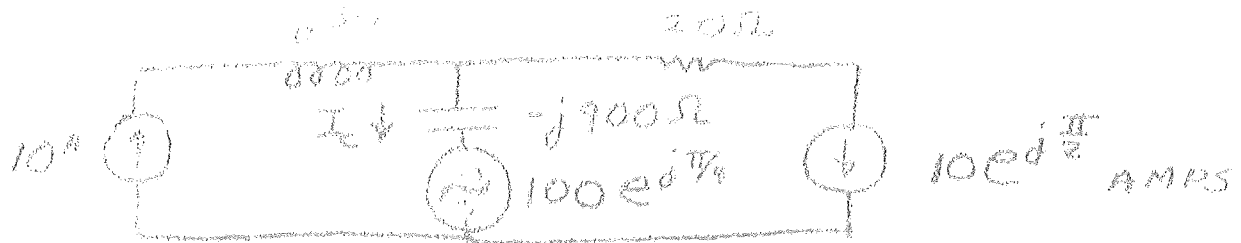THIS, OF COURSE, IS AN IDEAL CURRENT SOURCE.




(a) FIND I_c
FOR 10^4 SOURCE:

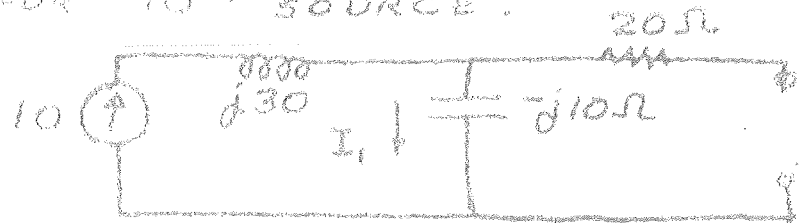


OBVIOUSLY, $I_1 = 10$ AMPS

FOR $100e^{j\pi/4}$ VOLT SUPPLY:

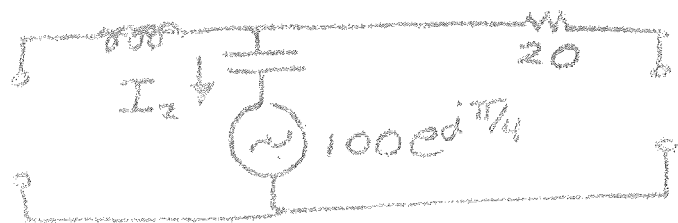


OBVIOUSLY, $I_2 = 0$

FOR $20e^{j\pi/2}$ CURRENT SUPPLY:

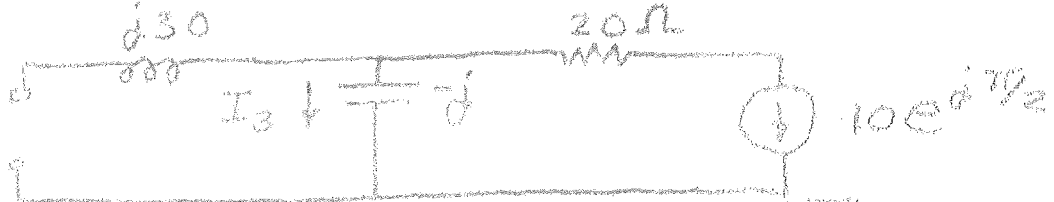


OBVIOUSLY, $I_3 = -10e^{j\pi/2}$
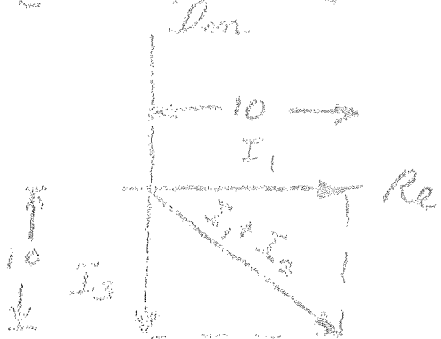
$$I_c = I_1 + I_2 + I_3 = \sqrt{2} 10 e^{-j\pi/4} \text{ AMPS.}$$



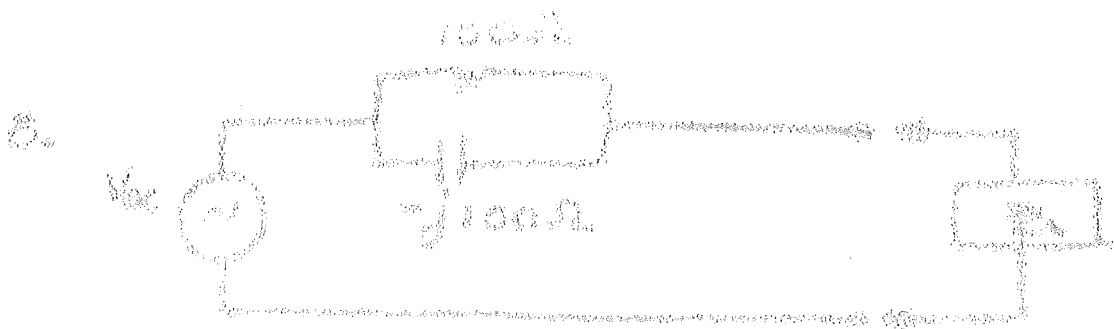b. ONLY THE
CURRENT SOURCES
HAVE AN EFFECT
ON I_c , $\Rightarrow I_c$ IS
INDEPENDENT OF
VOLTAGE SOURCE, R,
L, AND C.



(a) $\frac{1}{Z_{eq}} = \frac{1}{100} + \frac{1}{-j100} = \frac{1}{100} (1 + \frac{1}{j}) = \frac{j+1}{100}$
 $\Rightarrow Z_{eq} = \frac{100}{j+1} \frac{(j+1)}{(j+1)} = \frac{100(1-j)}{2} = 50 - j50 \Omega$


MAXIMUM POWER WILL BE XMITTED WHEN
 $Z_L = Z_{eq}^* = 50 + j50 \Omega$

(b) $Z_L = 50 + j50 \Omega$
 $R_L = 50 \Omega \quad X_L = 50 \Omega$

$X_L > 0 \Rightarrow$ WE MUST USE AN INDUCTOR:

$X_L = 50 = \omega L = 25 L \Rightarrow L = 2 \text{ mH}$

THUS, OUR RESULTING CIRCUIT IS:

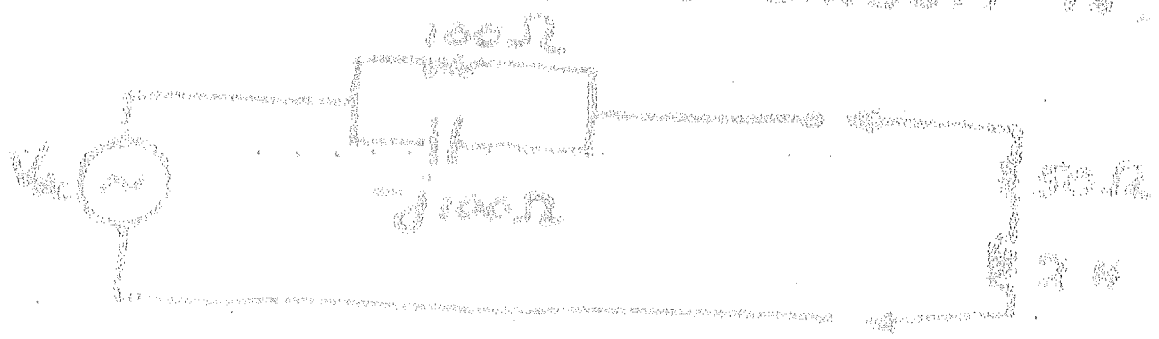


"COMMON SENSE IS PREJUDICE LEARNED BEFORE THE AGE 10"

ALBERT EINSTEIN

TEST # 3

DEC. 10, 1976


BOB MARKS

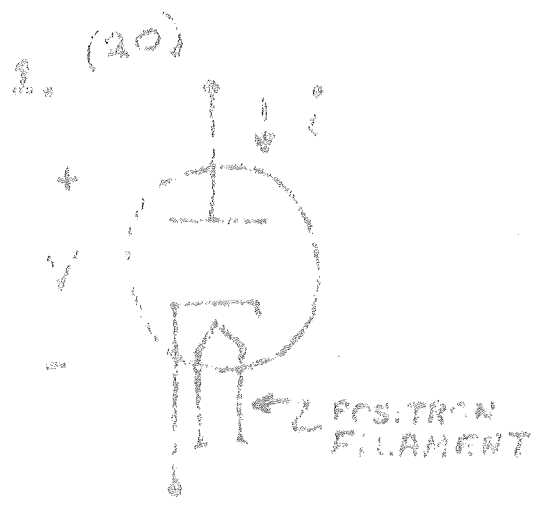


SUPPOSE AN ELECTRONICS FIRM HAS INVENTED A "POSITRON FILAMENT" THAT BOILS OFF POSITRONS INSTEAD OF ELECTRONS. (A POSITRON HAS AN EQUAL BUT OPPOSITE CHARGE OF AN ELECTRON).

EXPLAINING YOUR REASONING, SKETCH THE $V-I$ CURVE OF A TUBE-TYPE DIODE WHICH USES THIS POSITRON FILAMENT. USE I AS YOUR VERTICAL AXIS AND ASSUME THAT THE DIODE IS A SHORT CIRCUIT WHEN IT CONDUCTS.


2. (20)

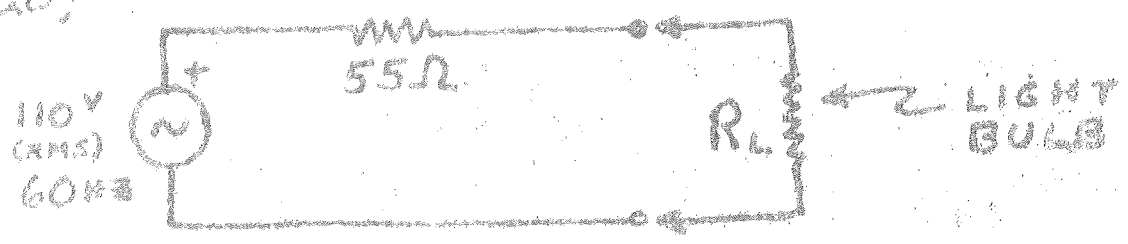

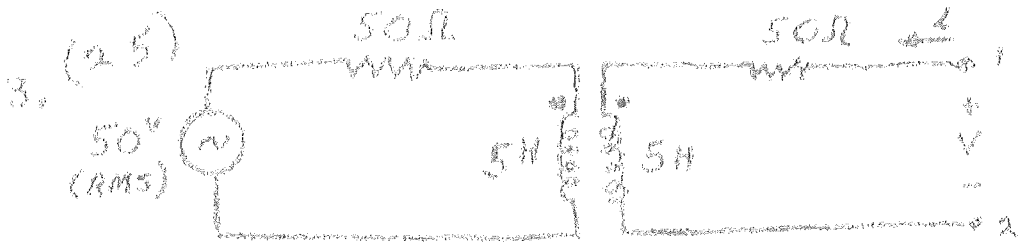A LIGHT BULB, DENOTED BY R_L , IS PLUGGED INTO A 110 VOLT (RMS) 60 HZ OUTLET. WHAT AVERAGE POWER IS DISSIPATED BY THE BULB WHEN THE MOST EFFICIENT USE IS MADE OF THE SOURCE? HOW WOULD THIS POWER BE EFFECTED IF WE RAISED THE FREQUENCY TO 120 HZ?



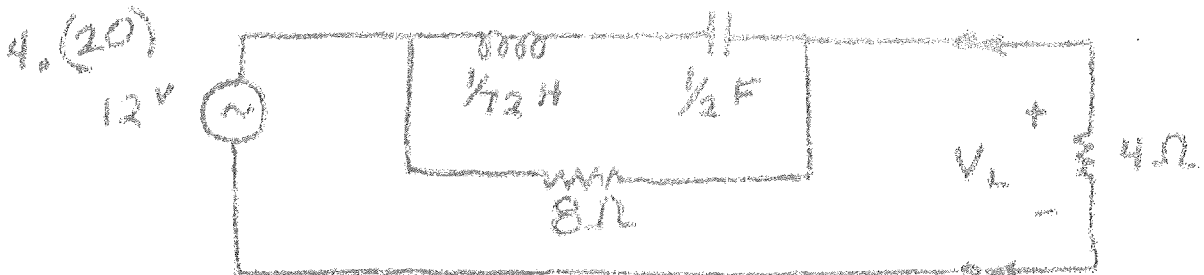
- AN IDEAL TRANSFORMER ($k=1$) IS USED IN THE ABOVE CIRCUIT WITH $\omega=10$
- (a) DETERMINE AND SKETCH THE THEVENIN AND NORTON EQUIVALENT CIRCUITS.
- (b) IF WE WISHED TO CONNECT AN IMPEDANCE Z_L BETWEEN TERMINALS 1 AND 2 SUCH THAT MAXIMUM POWER IS TRANSFORMED, WHAT VALUE OF Z_L WOULD WE USE? IS Z_L CAPACITIVE OR INDUCTIVE? WHY?




- (a). DETERMINE $V_L(\omega)$ FOR $\omega=0$ AND $\omega=\infty$
- (b). AT WHAT FREQUENCY IS $|V_L(\omega)|$ MAXIMUM? WHY? WHAT IS THE VALUE OF $V_L(\omega)$ AT THIS FREQUENCY?
- (c). USING THE RESULTS OF (a) AND (b), MAKE A ROUGH SKETCH OF $|V_L(\omega)|$.

(25)

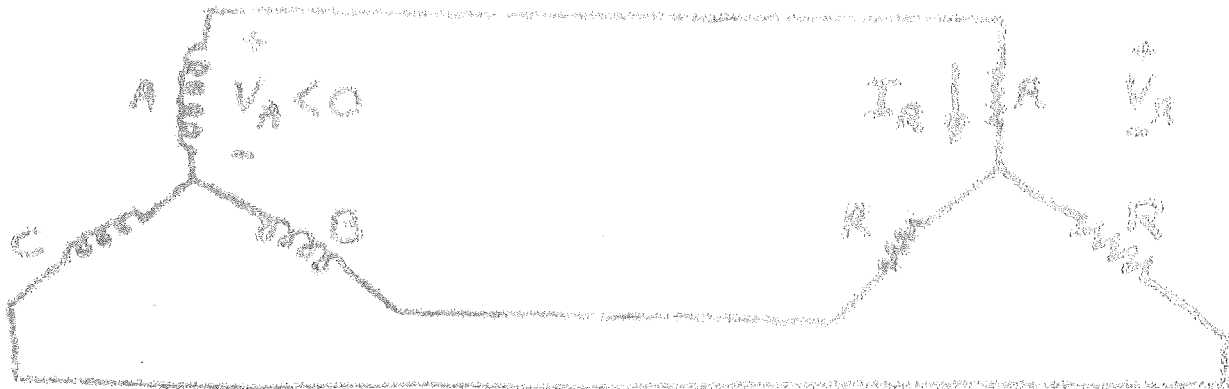5. FOR THE FOLLOWING 3-PHASE CIRCUIT, USE THE VOLTAGE ACROSS COIL A, V_A , AS A REFERENCE, AND FIND I_A AND V_R AS A FUNCTION OF THE VOLTAGE V_A AND THE RESISTANCE R .




TEST # 3 SOLUTIONS 4 MARKS

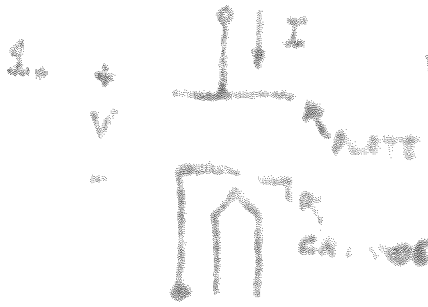

WHEN WE MAKE $V > 0$, THE PLATE WILL BE AT A HIGHER VOLTAGE THAN THE CATHODE. THE NEGATIVE CATHODE WILL ATTRACT THE POSITRONS AND THE POSITIVE PLATE WILL REPEL THEM. THUS, NO POSITRION FLOW AND WE HAVE AN OPEN CIRCUIT:

$$I = 0 \text{ FOR } V > 0$$

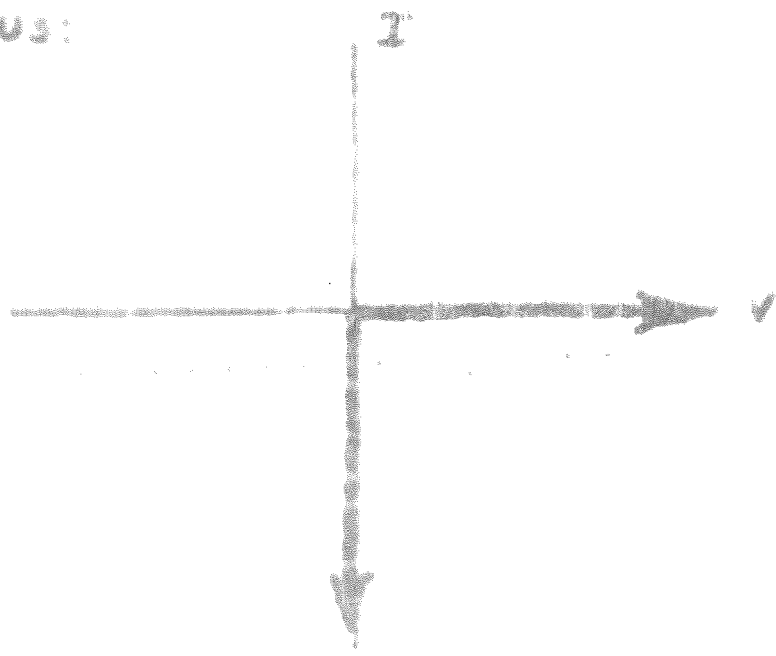AS SOON AS WE TRY TO MAKE $V < 0$, POSITRONS WILL START TO FLOW AND WE WILL HAVE A CURRENT FLOWING FROM THE CATHODE TO THE PLATE (ie, POSITIVE CHARGE FLOW). THUS, FOR $I < 0$, $V = 0$. THE V-I CURVE IS THUS:



2. MAXIMUM POWER IS TRANSFERED WHEN $Z_L = Z_{eq}^*$. THUS, WE HAVE $Z_L = (55\Omega)^*$
 $= R_L = 55\Omega$. WITH THIS LOAD, WE MAY

USE A VOLTAGE DIVIDER TO FIND THE VOLTAGE ACROSS R_L :

$$V_L = \frac{R_L}{R_L + 55} 110V = \frac{1}{2} 110V = 55V \text{ (RMS)}$$

THE AVERAGE POWER IS


$$P_{AVE} = \frac{V_L^2}{R_L} = \frac{(55V_{RMS})^2}{55\Omega} = 55 \text{ WATTS}$$

FREQUENCY HAS NO EFFECT ON THIS POWER.


3(a) FIRST, COMPUTE M:

$$M = k\sqrt{L_1 L_2} = 1\sqrt{5 \cdot 5} = 5H$$

NOW, USE THE T EQUIVALENT CIRCUIT:

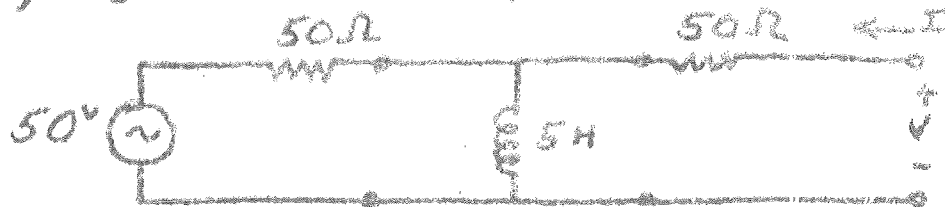

USE $\omega = 10$ AND WRITE IMPEDANCE:

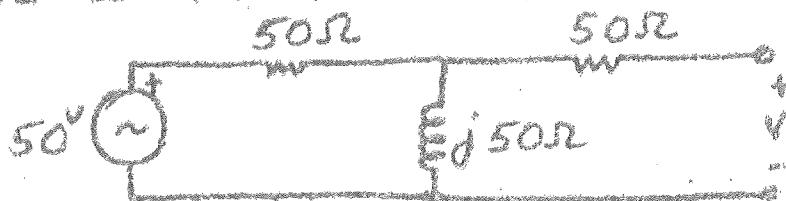


USE VOLTAGE DIVIDER TO FIND V_{oc} :

$$V_{oc} = \frac{j50}{50 + j50} * 50 = \frac{j50}{1 + j} \cdot \frac{1 - j}{1 - j} = 25(1 + j) \text{ VOLTS (RMS)}$$

(3b) MAXIMUM POWER IS TRANSFERRED WHEN $Z_L = Z_{eq}^* = (75 + j25)^* = 75 - j25 \Omega$. Z_L IS CAPACITIVE SINCE IT HAS A NEGATIVE REACTANCE.

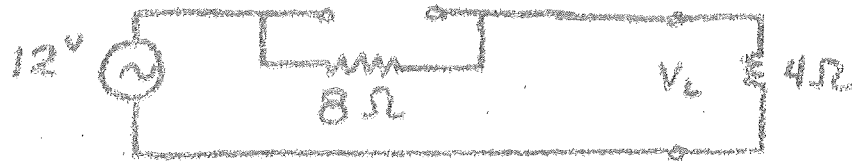4. (a) AT $\omega = 0$, THE CAPACITOR ACTS LIKE AN OPEN CIRCUIT:



USING A VOLTAGE DIVIDER:

$$V_L = \frac{4}{4+8} 12 = 4 \text{ VOLTS}$$


AT $\omega = \infty$, THE INDUCTOR ACTS LIKE AN OPEN CIRCUIT. THUS

$$V_L(\infty) = V_L(0) = 4 \text{ VOLTS}$$

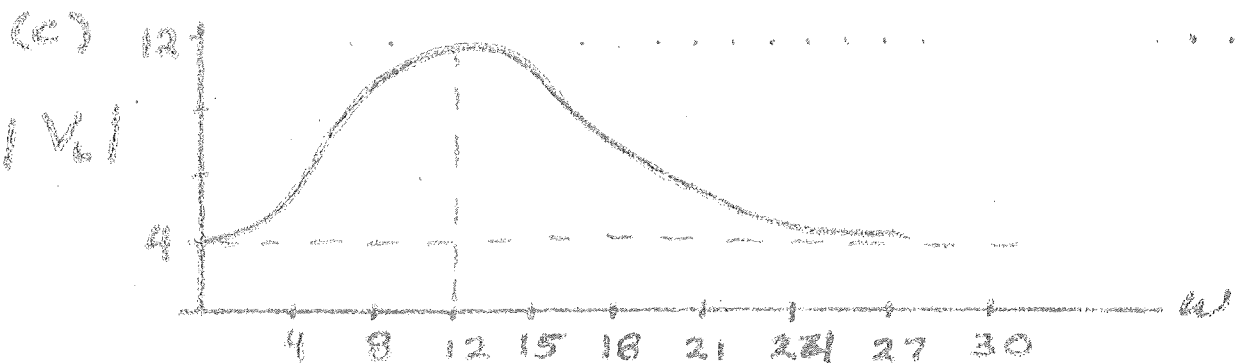(b) $V_L(\omega)$ WILL BE MAXIMUM WHEN L AND C ARE AT RESONANCE:

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\frac{1}{2} \cdot \frac{1}{2}}} = \sqrt{4} = 2 \text{ RAD/SEC}$$

AT THIS FREQUENCY, L AND C ACT LIKE A SHORT CIRCUIT:



(NAME)

EE 133

"ELECTRICAL SYSTEM'S ANALYSIS"

SECTION 002

BOB MARKS

FINAL EXAM

- TIME: 2 1/2 HOURS
- 270 POINTS TOTAL
- WORK PROBLEMS IN THIS BOOKLET. FOR ADDITIONAL PAPER, SEE INSTRUCTOR.



"...THE WISDOM OF THIS WORLD IS FOOLISHNESS WITH GOD."

1 COR. 3:19

"COMMIT THE WORKS UNTO THE LORD, AND THY THOUGHTS SHALL BE ESTABLISHED"

PROV. 16:3



1	
2	
3	
4	
5	
6	
7	
8	
9	
FINAL SCORE	
	%

#1. (60)

TRUE/FALSE

STATE YOUR ANSWER WITH A "T" FOR TRUE AND AN "F" FOR FALSE. ANSWERS RESEMBLING "F" WILL NOT BE GRADED. DO NOT ANSWER QUESTIONS YOU ARE COMPLETELY UNSURE OF.



TOTAL SCORE = TOTAL RIGHT - $\frac{1}{2}$ TOTAL WRONG


1. CURRENT MAY BE DEFINED AS THE RATE OF CHANGE OF VOLTAGE WITH RESPECT TO TIME.
2. POWER IS THE RATE AT WHICH ENERGY IS TRANSFERRED WITH RESPECT TO TIME.
3. FOR A UNIFORM CURRENT DENSITY, THE RESISTANCE OF A CYLINDRICAL CONDUCTOR IS PROPORTIONAL TO ITS CROSS SECTIONAL AREA.
4. CONDUCTANCE, ADMITTANCE, AND SUSCEPTANCE ARE ALL MEASURABLE IN UNITS OF "SIEMENS".
5. CAPACITORS, INDUCTORS, AND RESISTORS ARE ALL CAPABLE OF STORING ENERGY.
6. CAPACITORS STORE ENERGY IN AN ELECTRIC FIELD.
7. VOLTAGE CANNOT CHANGE INSTANTANEOUSLY ACROSS AN INDUCTOR.
8. OHM'S LAW MAY BE WRITTEN: $I = GV$.
9. THE V-I CHARACTERISTIC OF AN INDUCTOR IS: $i = L \frac{dv}{dt}$.

FOR OFFICIAL USE ONLY

YOUR LAB GRADE:
YOUR COURSE GRADE
FOR EE233 IS:

10. A CURRENT SOURCE WITH $I=0$ IS THE SAME THING AS AN OPEN CIRCUIT.
11. ALL MESHES ARE LOOPS AND VISA VERSA.
12. IF TWO OR MORE LUMPED CIRCUIT ELEMENTS HAVE IDENTICAL VOLTAGES ACROSS THEM, THEY ARE SAID TO BE CONNECTED IN PARALLEL.
13. IF C_1 AND C_2 ARE CONNECTED IN SERIES, THE EQUIVALENT CAPACITANCE IS $C_1 C_2 / (C_1 + C_2)$.
14. NEITHER THEVENIN'S NOR NORTON'S THEOREM MAY BE APPLIED TO A CIRCUIT CONTAINING DIODES.
15. TWO CURRENT SOURCES CONNECTED IN PARALLEL VIOLATE KIRCHHOFF'S VOLTAGE LAW.
16. THE SUSCEPTANCE OF A CAPACITOR IS PROPORTIONAL TO THE APPLIED FREQUENCY.
17. REACTIVE POWER CAN BE USED TO COOK TOASTED CHEESE SANDWICHES ON AN ELECTRIC STOVE.
18. A LARGE POWER FACTOR IS GOOD. A LARGE POWER ANGLE IS BAD.
19. AT $\omega=0$, A CAPACITOR ACTS LIKE A SHORT CIRCUIT.
20. INDUCTIVE REACTANCE IS NON-NEGATIVE.
21. IF W IS A COMPLEX NUMBER, THEN $\text{Re}\{W\}$ IS ALSO A COMPLEX NUMBER.
22. THE MUTUAL INDUCTANCE BETWEEN TWO INDUCTORS IS PROPORTIONAL TO THEIR COUPLING COEFFICIENT.

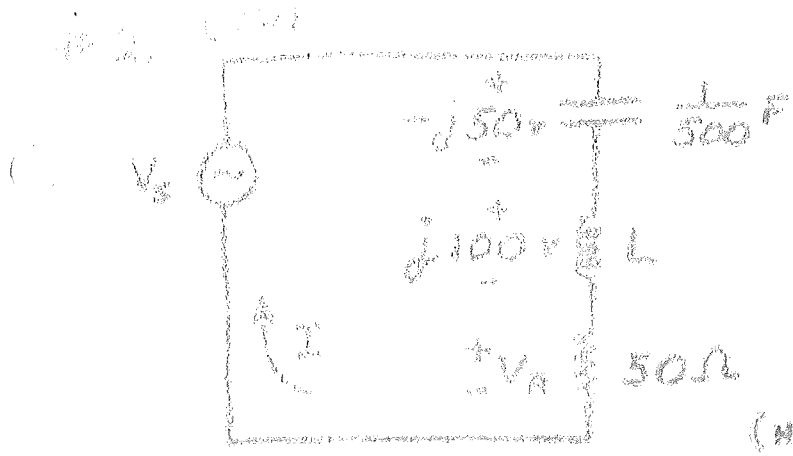23. IN A DEL CONNECTED THREE PHASE SYSTEM, $V_{\text{LINE}} = \sqrt{3} V_{\text{COIL}}$
24. THE DIFFUSION LENGTH IN A SEMI-CONDUCTOR DIODE DECREASES WHEN THE DIODE CONDUCTS
25. REVERSE BIASED SEMICONDUCTOR DIODES CONDUCT
26. COULOMB'S LAW SAYS (AMONG OTHER THINGS) THAT THE MAGNITUDE OF THE FORCE BETWEEN TWO POINT CHARGES IS PROPORTIONAL TO THE PRODUCT OF THE CHARGES
27. A DOPED SEMICONDUCTOR REFERS TO AN INTOXICATED ORCHESTRA LEADER WITH ONE ARM
28. A P DOPED SEMICONDUCTOR HAS A NUMBER OF FREE HOLES
29. AN IDEAL VOLTMETER WOULD DRAW NO CURRENT
30. SILICON SEMICONDUCTORS MAY BE DOPED WITH ARSENIC AND SHOULD TRUE NOT BE SWALLOWED.



GIVEN THAT $\omega = 10$


FIND

- ① V_s (IN POLAR FORM)
- ② L (IN HENRIES)

(HINT: FIRST DETERMINE I)

(30)

13.

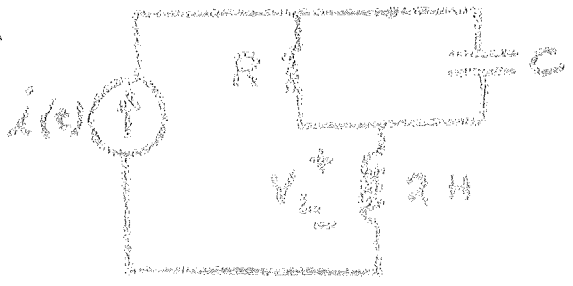



GIVEN THAT
 $i(t) = \begin{cases} -t(1-t) \text{ amps} & ; 0 < t < 1 \\ 0 & ; \text{ OTHERWISE} \end{cases}$

WHERE t IS IN SECONDS,
FIND AND SKETCH $V_L(t)$
FOR ALL t .



(30)


*4.

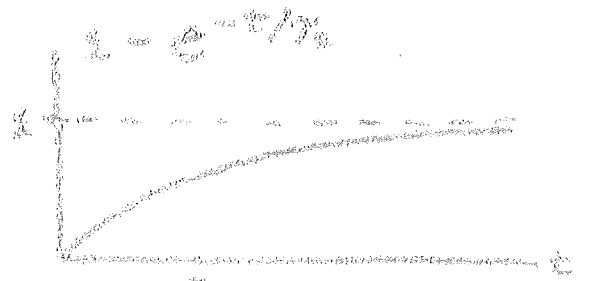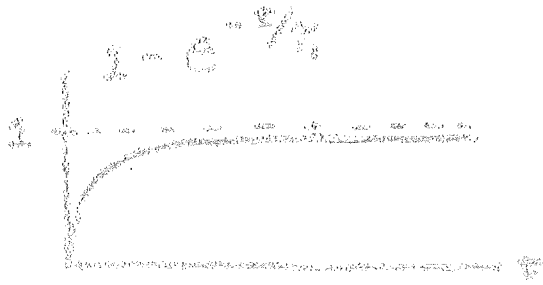

WHICH IS LARGER: τ_1 OR τ_2 ?
EXPLAIN YOUR REASONING.

(30)

5.

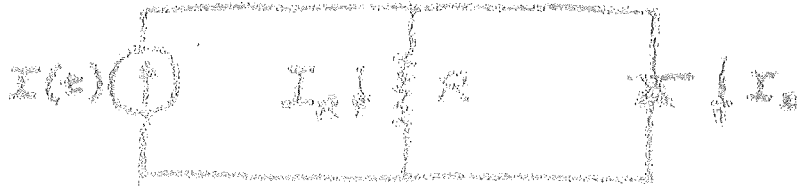


GIVEN THAT $I(t) = I_0 \sin \omega t$, SKETCH $I_R(t)$ AND $I_D(t)$. EXPLAIN YOUR REASONING.



(30)

*6

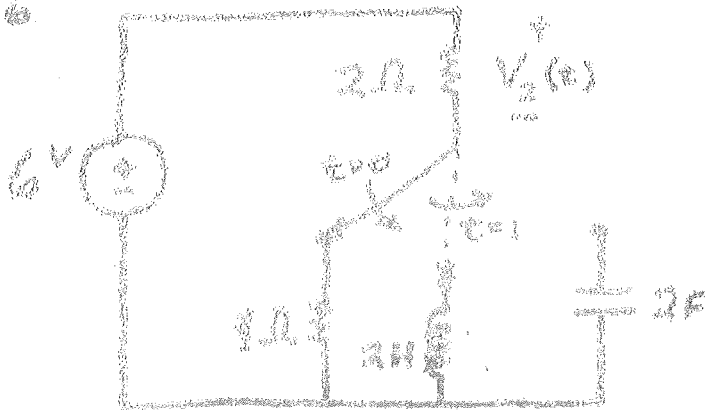


THE SWITCH IS THROWN FROM THE 4Ω RESISTOR TO THE 2H INDUCTOR AT $t=0$ AND THEN TO THE 2F CAPACITOR ONE SECOND LATER.

SKETCH $V_2(t)$ NOTING

ALL TRANSIENT AND LIMITING VALUES FOR ALL TIME t . SPECIFY ALL TIME CONSTANTS IN YOUR SKETCH.


(20)

#7.

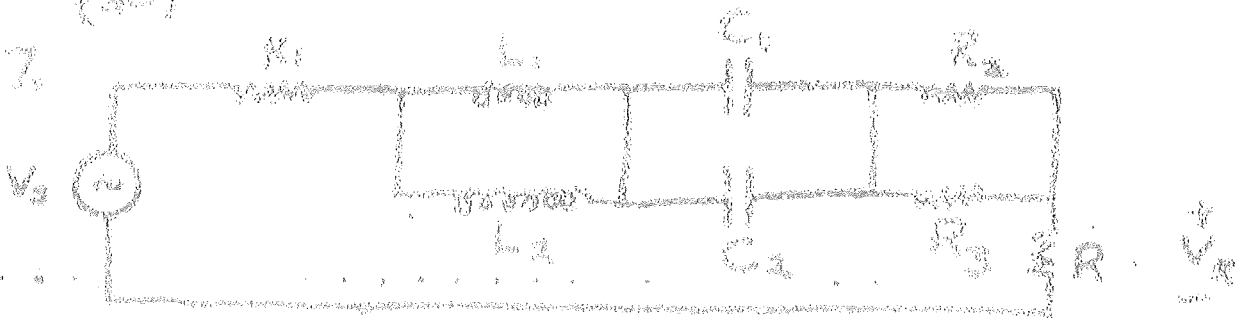

ASSUMING $R_1 = R_2 = R_3 = R$, $L_1 = L_2$, AND $C_1 = C_2$, SKETCH $|V_R(\omega)|$. SPECIFY $|V_R(\infty)|$, $|V_R(0)|$, AND THE FREQUENCY (OR FREQUENCIES) WHICH MAXIMIZE (OR MINIMIZE) $|V_R(\omega)|$

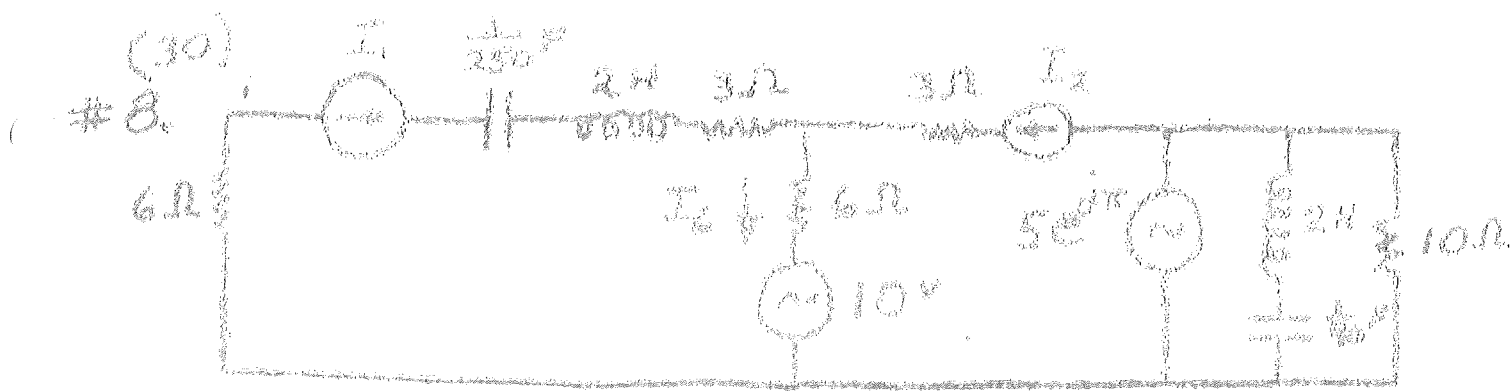ALSO ~~WHAT~~ WHAT TYPE OF FILTER IS THIS? ~~ANSWER~~



FIND THE RELATION BETWEEN I_1 AND I_2
 SUCH THAT $I_6 = \frac{1}{250}$ AMP, USE SUPERPOSITION
 AND SHOW WORK. $\omega = 10$.

EE 233
SEC 002
BOB
MARKS



FINAL
SOLUTIONS

TRUE/FALSE

STATE YOUR ANSWER WITH A "T" FOR TRUE AND AN "F" FOR FALSE. ANSWERS RESEMBLING "BT" WILL NOT BE GRADED. DO NOT ANSWER QUESTIONS YOU ARE COMPLETELY UNSURE OF.

TOTAL SCORE = TOTAL RIGHT - 1/2 TOTAL WRONG

1. CURRENT MAY BE DEFINED AS THE RATE OF CHANGE OF VOLTAGE WITH RESPECT TO TIME. F
2. POWER IS THE RATE AT WHICH ENERGY IS TRANSFERRED WITH RESPECT TO TIME. T
3. FOR A UNIFORM CURRENT DENSITY, THE RESISTANCE OF A CIRCULAR CONDUCTOR IS PROPORTIONAL TO ITS CROSS SECTIONAL AREA. F
4. CONDUCTANCE, ADMITTANCE, AND SUSCEPTANCE ARE ALL MEASURABLE IN UNITS OF "SIEMENS". T
5. CAPACITORS, INDUCTORS, AND RESISTORS ARE ALL CAPABLE OF STORING ENERGY. F
6. CAPACITORS STORE ENERGY IN AN ELECTRIC FIELD. T
7. VOLTAGE CANNOT CHANGE INSTANTANEOUSLY ACROSS AN INDUCTOR. F
8. OHM'S LAW MAY BE WRITTEN: $I = GV$. T
9. THE V-I CHARACTERISTIC OF AN INDUCTOR IS: $i = L \frac{dv}{dt}$. F

THE SIGNAL SET UP YOUR LAB GRADE: <input type="text"/> YOUR COURSE GRADE FOR EE233 102: <input type="text"/>

10. A CURRENT SOURCE WITH $I=0$ IS THE SAME THING AS AN OPEN CIRCUIT. T

11. ALL MESHES ARE LOOPS AND VISAVERSA F

12. IF TWO OR MORE LUMPED CIRCUIT ELEMENTS HAVE IDENTICAL VOLTAGES ACROSS THEM, THEY ARE SAID TO BE CONNECTED IN PARALLEL. T

13. IF C_1 AND C_2 ARE CONNECTED IN SERIES, THE EQUIVALENT CAPACITANCE IS $C_{eq} = C_1 + C_2$ F

14. NEITHER THEVININ'S NOR NORTON'S THEOREM MAY BE APPLIED TO A CIRCUIT CONTAINING DIODES T

15. TWO CURRENT SOURCES CONNECTED IN PARALLEL VIOLATE KIRCHHOFF'S VOLTAGE LAW F

16. THE SUSCEPTANCE OF A CAPACITOR IS PROPORTIONAL TO THE APPLIED FREQUENCY T

17. REACTIVE POWER CAN BE USED TO COOK TOASTED CHEESE SANDWICHES ON AN ELECTRIC STOVE F

18. A LARGE POWER FACTOR IS GOOD, A LARGE POWER ANGLE IS BAD. T

19. AT $\omega=0$, A CAPACITOR ACTS LIKE A SHORT CIRCUIT. F

20. INDUCTIVE REACTANCE IS NON-NEGATIVE T

21. IF W IS A COMPLEX NUMBER, THEN $\arg W$ IS ALSO A COMPLEX NUMBER F

22. THE MUTUAL INDUCTANCE BETWEEN TWO INDUCTORS IS PROPORTIONAL TO THEIR COUPLING COEFFICIENT T

23. IN A DELTA CONNECTED THREE PHASE SYSTEM, $V_{LINE} = \sqrt{3} V_{COIL}$ F

24. THE DIFFUSION LENGTH IN A SEMI-CONDUCTOR DIODE DECREASES WHEN THE DIODE CONDUCTS T

25. "REVERSE" BIASED SEMICONDUCTOR DIODES CONDUCT F


26. COULOMB'S LAW SAYS (AMONG OTHER THINGS) THAT THE MAGNITUDE OF THE FORCE BETWEEN TWO POINT CHARGES IS PROPORTIONAL TO THE PRODUCT OF THE CHARGES T

27. A "DOPED" SEMICONDUCTOR REFERS TO AN INTERMIXED ORCHESTRA LEADER WITH ONE ARM F

28. A P DOPED SEMICONDUCTOR HAS A NUMBER OF FREE HOLES T

29. AN IDEAL VOLTMETER WOULD DRAW NO CURRENT T

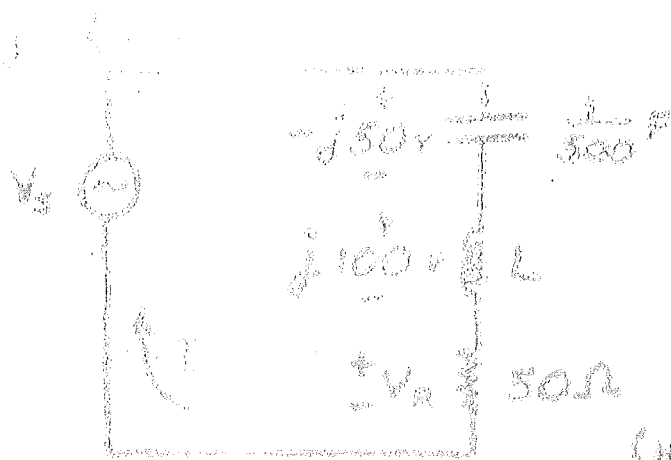30. SILICON SEMICONDUCTORS MAY BE DOPED WITH ARSENIC AND SHOULD THIS NOT BE SWALLOWED T



GIVEN THAT $\omega = 10$

FIND

- ① V_s (IN POLAR FORM)
- ② L (IN HENRIES)

(HINT: FIRST DETERMINE I)

NOW, THE CAPACITOR'S VOLTAGE IS

$$V_C = \frac{1}{j\omega C} I$$

$$\Rightarrow -j50 = (10) \left(\frac{1}{500} \right) I$$

THUS

$$I = (50)(10) \left(\frac{1}{500} \right) = 1 \text{ AMP}$$

$$\text{① } \Rightarrow V_R = (50 \Omega)(1 \text{ AMP}) = 50 \text{ VOLTS}$$

SUMMING THE VOLTAGES AROUND THE LOOP:

$$V_s = (-j50) + (j100) + (50)$$

$$= 50 + j50 = \sqrt{2} 50 e^{j\pi/4}$$

③ NOW THE VOLTAGE ACROSS INDUCTOR IS

$$V_L = (j\omega L)I$$

OR


$$100 = j(10)L(1)$$

WHICH GIVES

$$L = 10 \text{ H}$$

(30)

#3.

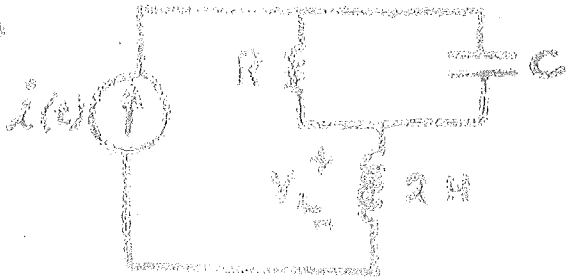

GIVEN THAT

$$i(t) = \begin{cases} -t(1-t) \text{ amps} & ; 0 < t < 1 \\ 0 & ; \text{ OTHERWISE} \end{cases}$$


WHERE t IS IN SECONDS,
 FIND AND SKETCH $V_L(t)$
 FOR ALL t .



FIRST, WE NOTE THAT THE R AND THE C HAVE NO EFFECT ON THE CURRENT THRU THE INDUCTOR. THAT IS, THE INDUCTOR AND CURRENT SOURCE ARE IN SERIES. FOR AN INDUCTOR:

$$V_L = L \frac{di}{dt}$$

THUS
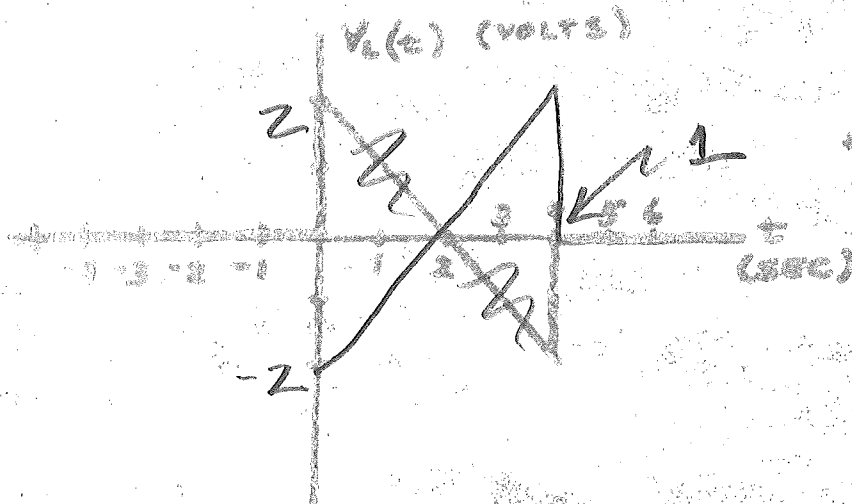
$$\begin{aligned} V_L(t) &= (2H) \frac{d}{dt} [-t(1-t)] \\ &= 2H \frac{d}{dt} [t^2 - t] \\ &= 2 [2t - 1] \\ &= 4t - 2 \text{ (VOLTS)}; \quad 0 < t < 1 \end{aligned}$$



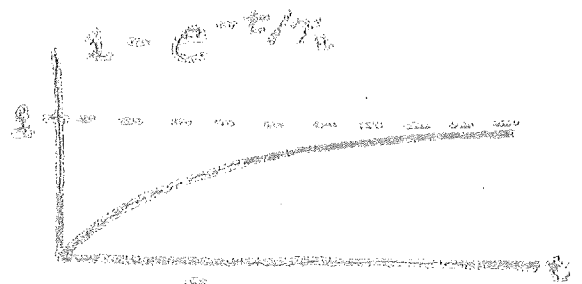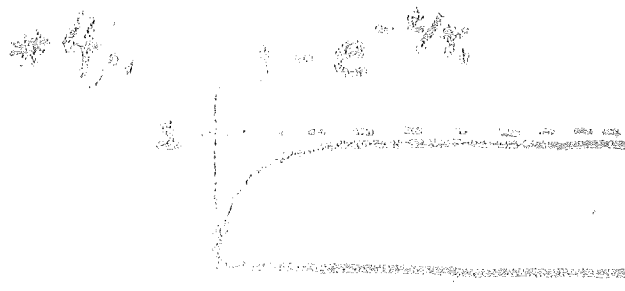

WHICH IS LARGER: τ_1 , OR τ_2 ?
EXPLAIN YOUR REASONING.




THERE ARE A NUMBER OF WAYS IN WHICH THIS PROBLEM CAN BE WORKED. I WOULD DO THE FOLLOWING. LET

$$V_1(t) = 1 - e^{-t/\tau_1}$$


$$V_2(t) = 1 - e^{-t/\tau_2}$$

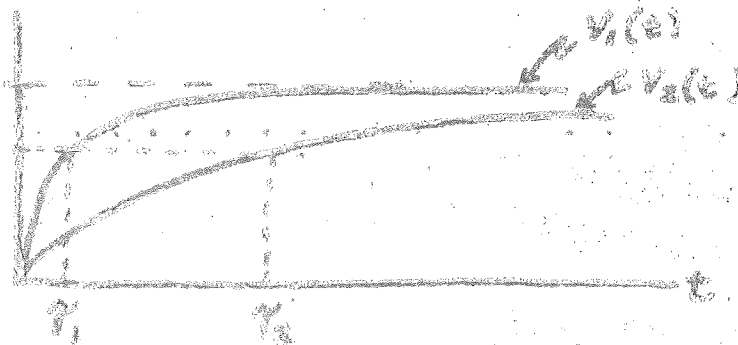NOTE THAT $V_1(\tau_1) = V_2(\tau_2) = 1 - e^{-1} \approx 0.63$
LOOKING AT THE GRAPHS:



OBVIOUSLY, $\tau_2 > \tau_1$.


#5.

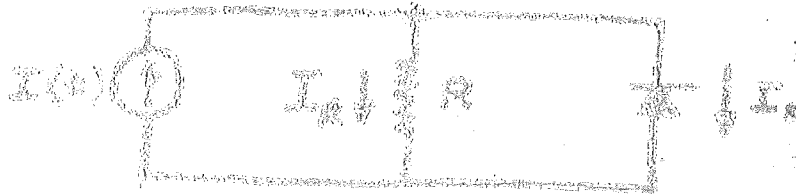


GIVEN THAT $I(t) = I_0 \sin 2\pi t$, SKETCH $I_R(t)$ AND $I_D(t)$. EXPLAIN YOUR REASONING.



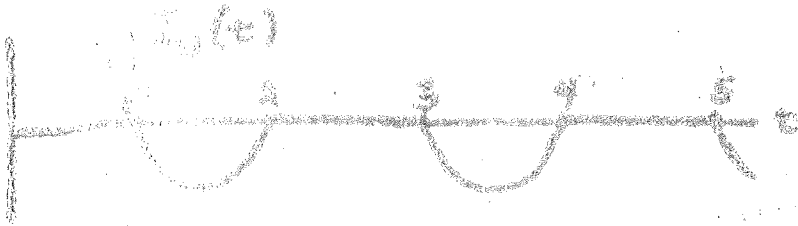FOR $I(t) < 0$, THE DIODE WILL CONDUCT, AND ALL OF THE CURRENT WILL GO THRU THE DIODE (WHICH IS A SHORT)



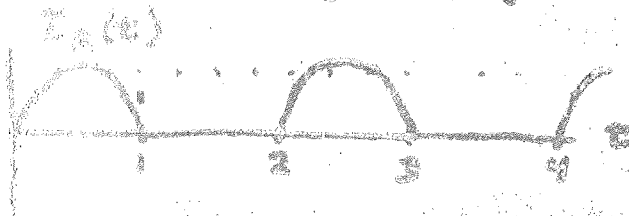
FOR $I(t) > 0$, THE DIODE IS AN OPEN CIRCUIT AND ALL OF $I(t)$ MUST GO THRU THE RESISTOR



NOTE THAT $I_R(t) + I_D(t) = I(t)$, CONFIRMING KIRK'S NODE LAW AT A

(30)

#6

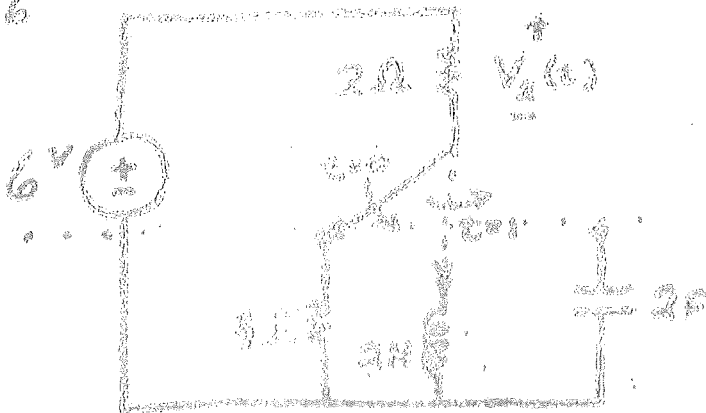


THE SWITCH IS THROWN FROM THE 4Ω RESISTOR TO THE 2H INDUCTOR AT $t=0$ AND THEN TO THE 2F CAPACITOR ONE SECOND LATER.

SKETCH $V_2(t)$ NOTING

ALL TRANSIENT AND LIMITING VALUES FOR ALL TIME t . SPECIFY ALL TIME CONSTANTS IN YOUR SKETCH.

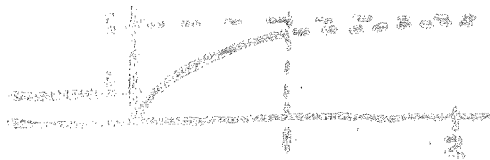
BEFORE SWITCH IS THROWN, WE USE A VOLTAGE DIVIDER $\Rightarrow V_2(t) = \frac{2}{2+4} 6 = 2$ VOLTS. ; $t < 0$
 AT THE INDUCTOR, WE CAN'T ALLOW CURRENT $\Rightarrow V_2(0^+) = 0$. IF WE WERE TO LEAVE THE SWITCH ON L, WE WOULD GET $V_2(\infty) = 6$. THAT IS, AT $t = \infty$, L WOULD ACT LIKE A SHORT. OBVIOUSLY, $\tau_1 = L/R = 1$ SECOND. OUR CURVE WOULD LOOK LIKE



THE EQUATION FOR $0 < t < 1$ IS

$$V_2(t) = 6(1 - e^{-t})$$


NOTE THAT $V_2(t) = 6(1 - e^{-t})$

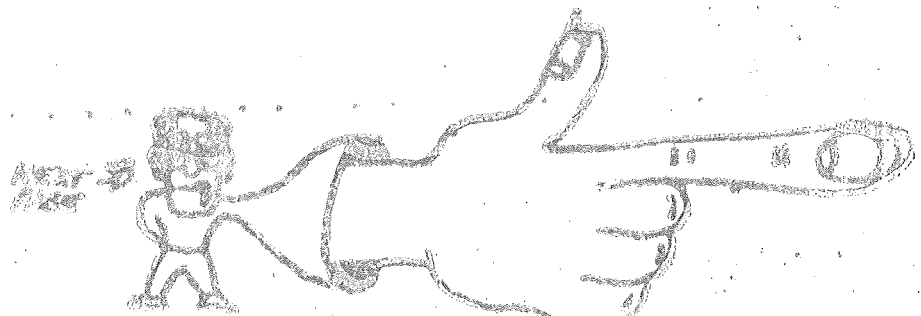

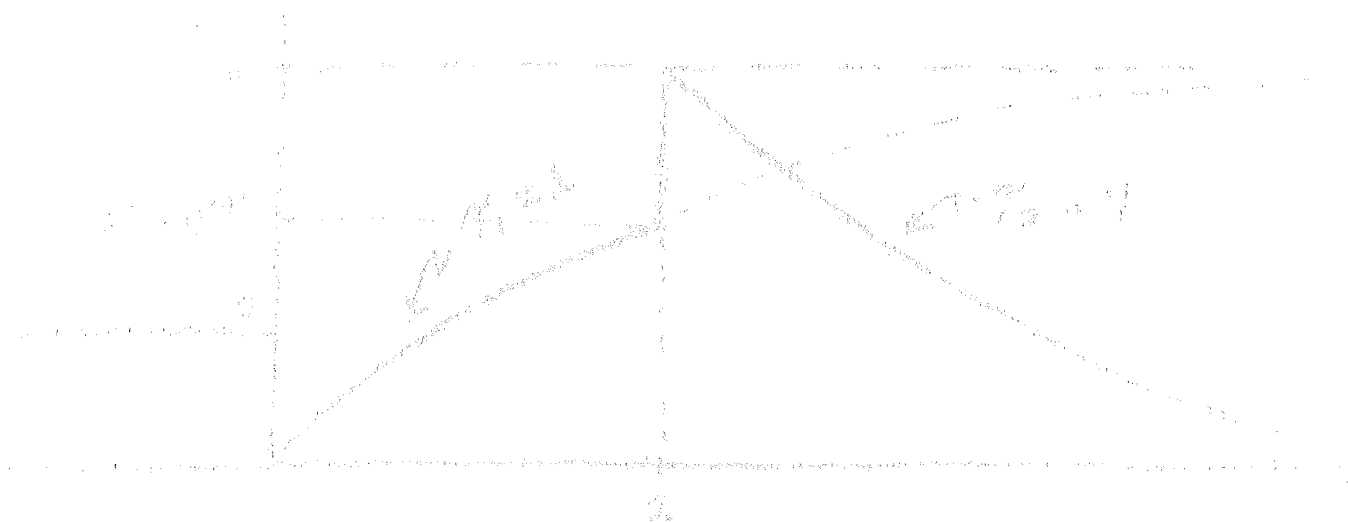(c) IMMEDIATELY AFTER THROWING THE SWITCH, THE
 CAPACITOR IS CHARGED TO 6 VOLTS AND
 THEREFORE BEGINS TO DISCHARGE THROUGH THE
 RESISTOR SINCE VOLTAGE CANNOT
 CHANGE INSTANTANEOUSLY ACROSS
 THE CAPACITOR, THUS


$$V_C(0^+) = 6 \text{ VOLTS}$$

IMMEDIATELY AFTER THE CAPACITOR LOOKS LIKE
 AN OPEN CIRCUIT, THUS, $V_R(0^+) = 0$
 AND $\tau = RC = (2\Omega)(2F) = 4 \text{ SEC}$
 ON A SIMILAR CURVE THEN LOCATE THE



POINTS ON THE GRAPH BE MARKING AND

LABELING AS DEPTH, LINE OF THE

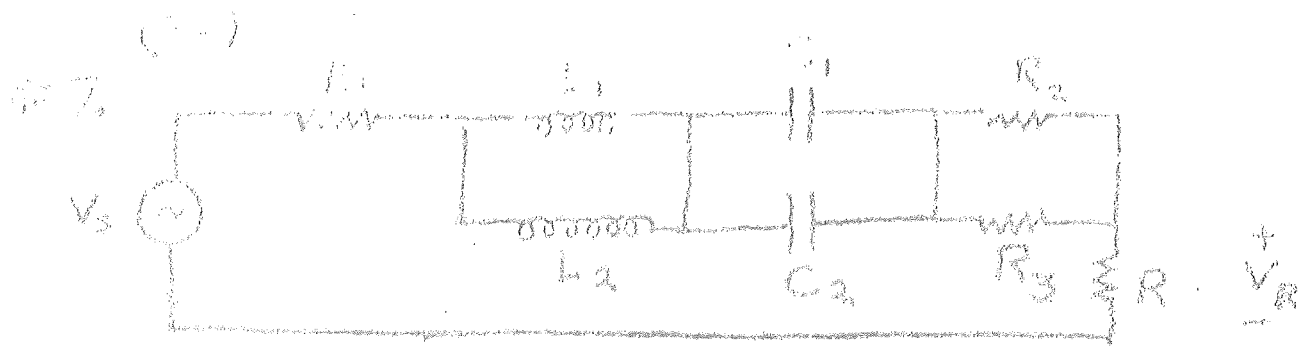


ASSUMING $R_1 = R_2 = R_3 = R$, $L_1 = L_2$, AND $C_1 = C_2$, SKETCH $|V_R(\omega)|$. SPECIFY $|V_R(\infty)|$, $|V_R(0)|$, AND THE FREQUENCY (OR FREQUENCIES) WHICH MAXIMIZE (OR MINIMIZE) $|V_R(\omega)|$

ALSO \Rightarrow WHAT TYPE OF FILTER IS THIS? \leftarrow

Answer

LET $L = L_1 = L_2$, $R = R_1 = R_2 = R_3$, $C = C_1 = C_2$.

FIRST OFF SIMPLIFY THE CIRCUIT

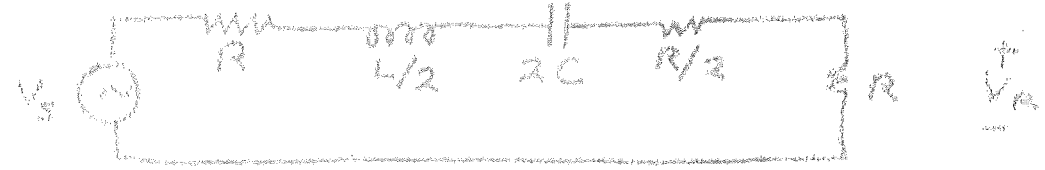



AT $\omega = \infty$, THE INDUCTOR LOOKS LIKE AN OPEN CIRCUIT $\Rightarrow |V(\infty)| = 0$

AT $\omega = 0$, THE CAPACITOR LOOKS OPEN $\Rightarrow |V(0)| = 0$

AT $\omega_0 = \sqrt{\frac{L}{C}} = \frac{1}{\sqrt{LC}}$, THE INDUCTOR AND CAPACITOR ARE AT RESONANCE (SHORT CIRCUIT). USING A VOLTAGE


DIVIDER: $|V_R(\omega_0)| = \frac{R}{\sqrt{2} R} V_s = \frac{2}{\sqrt{2}} V_s$. HERE, $|V_R(\omega)|$ IS MAXIMIZED

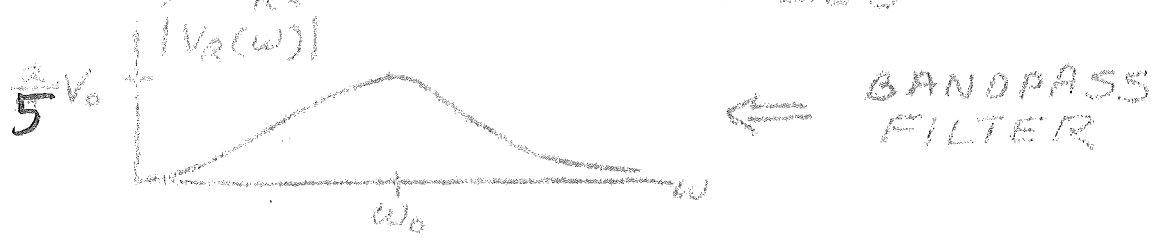

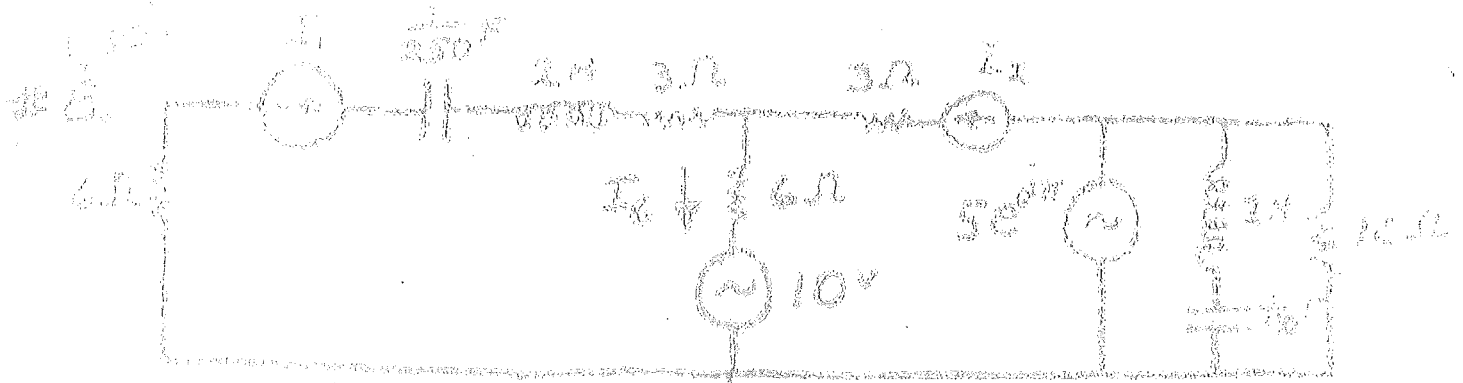


FIND THE RELATION BETWEEN I_1 AND I_2 ,
 SUCH THAT $I_3 = 250$ AMP. USE SUPERPOSITION
 AND SHOW WORK. $\omega = 10$.

(a) FOR I_1

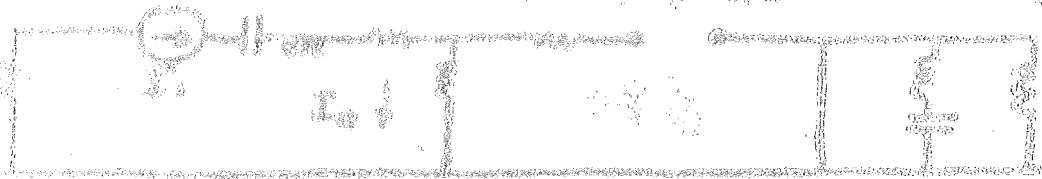

OBVIOUSLY, $I_1 = I_1$

(b) FOR I_2

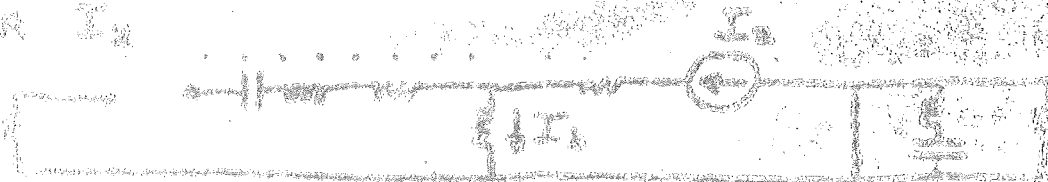

OBVIOUSLY, $I_2 = I_2$

(c) WHETHER VOLTAGE SUPPLY WILL HAVE AN
 EFFECT SINCE OPENING I_1 AND I_2
 LEAVES NO CURRENT PATH. THUS

$$I_3 = I_1 + I_2 = 250 \text{ AMP}$$



~40
 SWEAT

B

space here

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS WAS AN A now a B (as result of last test)

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS A if I make a A on the final

3. I TOOK THIS COURSE (a) FOR GRADES (b) CAUSE I WANTED TO (c) CAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SHODDY JOB (e) VERY RESTFUL

* well presented and clearer than in the book

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN (SOMETIMES)

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS SUPERPOSITION THEOREM

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS to understand electricity a lot more (really didn't care about it before)

asked to spell KIRCHHOFF

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING. CH. E.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS
CHECK MARK IF YOU USED BACK

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS A

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS A

3. I TOOK THIS COURSE (a) FOR GAINS (b) CAUSE I WANTED TO (c) CAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SHODDY JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS THREE PHASE

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS CRUISES BY TUBS

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS →
[] CHECK HERE IF YOU NEED ASK

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS A

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS A if I do well on the final.

3. I TOOK THIS COURSE (a) FOR GRADE (b) BECAUSE I WANTED TO (c) BECAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSES I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SHOW JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS Three Phase circuits

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (A) A-

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS There are Duals all over the place.

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON-EXISTANT (e) ALL OF THE ABOVE

PLEASE CHECK THE COMMENTS AND
✓ CHECK HERE IF NO USES BEEN

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS C

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS B

3. I TOOK THIS COURSE (a) FOR GRADES (b) BECAUSE I WANTED TO (c) BECAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSES I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SHODDY JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS Norton + Thevenin

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) B

9. THE MOST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS an understanding of // + series circuit design + what AC does.

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) APOOR (d) NONEXISTANT (e) ALL OF THE ABOVE

PLEASE USE BACK TWO COMMENTS AND CHECK THEM IF YOU HAD THEM

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS A-B

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS A if I study for the final

3. I TOOK THIS COURSE (a) FOR GRINS (b) CAUSE I WANTED TO (c) CAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SHODDY JOB (e) VERY RESTFUL

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS Thevenin's & Norton's Theorem + three phase

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS the general vague idea of how electricity is used

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL

(d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS
✓ CHECK HERE IF YOU USED BACK

B

space here

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS WAS AN A now a B (as result of last test)

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS A if I make a A on the final

3. I TOOK THIS COURSE (a) FOR GRINS (b) CAUSE I WANTED TO (c) CAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SHODDY JOB (e) VERY RESTFUL. & well presented and clearer than in the book

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN (SOMETIMES)

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS SUPERPOSITION THEOREM

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS to understand electricity a lot more (really didn't care about it before)

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING. CH. E.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NONEXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS
CHECK HERE IF YOU WERE ASKED

I feel that Bobby did a good job in teaching this class. The lectures were presented with the material made easy to understand. I would recommend Mr. Markis to my fellow constituents.

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS A

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS A

3. I TOOK THIS COURSE (a) FOR GRADES (b) CAUSE I WANTED TO (c) CAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SHODDY JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS THREE PHASE

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS College by rules

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS +
[] CHECK HERE IF YOU NEED ASK

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS A

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS A if I do well on the final.

3. I TAKE THIS COURSE (a) FOR GRADE (b) BECAUSE I WANTED TO (c) BECAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSES I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SHODDY JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS Three Phase circuits

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A-

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS There are Duals all over the place.

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) WILL BE OF NO HELP AT ALL

(c) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON-EXISTANT (e) ALL OF THE ABOVE

PLEASE SIGN FOR COMMENTS AND
✓ CHECK HERE IF YOU USED BUBBLES

I enjoyed the way the instructor presented the material.
It helps if he is interested and involved in what he's teaching.
I would have enjoyed this course a lot had I been
interested in EE to begin with. It was a good course and
worth the time even though it was required.

The tests were O.K., fair as a whole, and usually ~~not~~^{of}
~~too long~~ ~~reasonable~~ ~~too~~ reasonable length.

Merry Christmas!

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS C

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS B

3. I TOOK THIS COURSE (a) FOR GRADES (b) BECAUSE I WANTED TO (c) BECAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSES I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SHODDY JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS Norton & Thevenin

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) (b)

9. THE NEAREST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS an understanding of // + series circuit design + what AC does.

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) WILL BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY COURAGE IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

12. I'D LIKE TO SEE THE COMMENTS (b) CHECK THEM AS YOU WOULD LIKE.

The Lectures were very good and well organized.

The one complaint I have, is that the tests do not reflect the Lectures & what I learned somehow.

Homework problems that call for a proof, followed by a test with practical problems is a poor practice I think. I wish that I could have been able to use the book more, but, somehow it didn't follow the lectures as well as it should.

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS A-B

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS A if I study for the final

3. I TOOK THIS COURSE (a) FOR GRADES (b) BECAUSE I WANTED TO (c) CAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSES I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SHODDY JOB (e) VERY RESTFUL

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS Thevenin's or Norton's Theorem + three phase

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS the general vague idea of how electricity is used

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL

(d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS
✓ CHECK MARK IF YOU USED BACK

One thing I enjoy is hearing about common applications of some particular theories and how they are ~~so~~ put to use.

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS B

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS B

3. I TOOK THIS COURSE (a) FOR GRADING (b) BECAUSE I WANTED TO (c) BECAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSES I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SHODDY JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL

(b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS Skewered + Norton's Equ

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) B

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS Linear circuit analysis

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON-EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS →
[] CHECK HERE IF YOU USED BACK

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS B

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS B

3. I TOOK THIS COURSE (a) FOR GRINS (b) CAUSE I WANTED TO (c) CAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SNOW JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS THEVEN-NORTONS EQ CIRCUITS

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS POWER

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS
[] CHECK HERE IF YOU USED BACK

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS B

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS B

3. I TOOK THIS COURSE (a) FOR GRADES (b) BECAUSE I WANTED TO (c) BECAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSES I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SHODDY JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS _____

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) B

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS _____

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NONEXISTENT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS
 CHECK HERE IF YOU USED BACK

DEC 10

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS B
2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS I'm NOT SURE
3. I TOOK THIS COURSE (a) FOR GRINS (b) CAUSE I WANTED TO (c) CAUSE I HAD TO
4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE
5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SNOW JOB (e) VERY RESTFUL
6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN
7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS THREE PHASE
8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A ^{EXCELLENT}
9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS DIODES + CRT ^(TV)
10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING
11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS →
 CHECK HERE IF YOU USED BACK

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS A

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS A

3. I TOOK THIS COURSE (c) FOR GRADE (d) CAUSE I WANTED TO (c) CAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSES I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SNOW JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS _____

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A

9. THE NEAREST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS EE courses are not hard if you

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING. having a good instructor

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) MONEY WASTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS
[] CHECK HERE IF YOU USED BACK

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS A+

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS A-

3. I TOOK THIS COURSE (a) FOR GOING (b) COURSE I WANTED TO (c) CAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSES I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SNOW JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS Ther & Nort Equivalents.

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A good

9. THE WERTEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS 3 phase

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT OF ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

JD

USE BACK FOR COMMENTS
OR CHECK NAME IF YOU USED BACK



1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS C

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS C

3. I TOOK THIS COURSE (a) FOR GRINS (b) CAUSE I WANTED TO (c) CAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSES I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE

(c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT

(b) PRETTY GOOD (c) AVERAGE (d) A SHODDY JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL

(b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS polyphase systems

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS complex #'s

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL

(c) WILL BE OF NO HELP AT ALL

(d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS

(f) CHECK HERE IF YOU USED BACK

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS B.

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS B.

3. I TOOK THIS COURSE (a) FOR GRINS (b) CAUSE I WANTED TO (c) CAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SNOW JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS Power and I'm behind

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (N) A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS How a TV works

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS →
☐ CHECK HERE IF YOU USED BACK

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS A

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS A

3. I TOOK THIS COURSE (a) FOR GRINS (b) CAUSE I WANTED TO (c) BECAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEEE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SNOW JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS Three Phase Connection

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (N) A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS how circuit components work

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL

(d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS →
[] CHECK HERE IF YOU USED BACK

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS B

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS C

3. I TOOK THIS COURSE (a) FOR SOME (b) CAUSE I WANTED TO ~~(c)~~ CHASS I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEZE ~~(b)~~ ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT ~~(b)~~ PRETTY GOOD (c) AVERAGE (d) A SHODDY JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS ~~(a)~~ HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS _____

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) _____ A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS _____

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL ~~(b)~~ BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WITH _____ ~~(a)~~ GOOD (b) FAIR (c) POOR (d) NONE EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS
[] CHECK HERE IF YOU WERE ASKED



1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS B (MAYBE)

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS B

3. I TOOK THIS COURSE (a) FOR GRINS (b) BECAUSE I WANTED TO (c) BECAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SHODDY JOB (e) VERY RESTFUL

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS THERMODYNAMICS + FLUIDS

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS ...

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS
 CHECK HERE IF YOU USED BACK

EXAMS ARE A LITTLE LONG. (USUALLY ONE PROBLEM TOO LONG).

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS D.

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS A.

3. I TOOK THIS COURSE (a) FOR GRADES (b) BECAUSE I WANTED TO (c) BECAUSE I HAD TO

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SNOW JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS THEVININ & NORTON

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) B+

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS HOW LUCKY I AM TO BE

10. AS FAR AS MY CAREER GOES, IN THE INSTEAD OF EE. THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) WILL BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS
[] CHECK HERE IF YOU USED BACK



1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS C+ → B:

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS B

3. I TOOK THIS COURSE (a) FOR GRADES (b) CAUSE I WANTED TO (c) CAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SNOW JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL

(b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS THEMININ & NORTON EQUIVALENCE (MORE PROBLEMS)

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS CRT

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL

(c) WILL BE OF NO HELP AT ALL

(d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NONEXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS

✓ CHECK HERE IF YOU USED BACK



1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS B → A

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS A

3. I TOOK THIS COURSE (a) FOR GRINS (b) CAUSE I WANTED TO (c) CAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SNOW JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS How - Norton's

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS How A TV WORKS

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL

(d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS →

CHECK HERE IF YOU USED BACK

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS B

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS A

3. I TOOK THIS COURSE (a) FOR GRADE (b) BECAUSE I WANTED TO (c) BECAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSES I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SNOW JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS three phase

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (N) B

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS Ohm's LAW

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NONEY STANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS

CHECK HERE IF YOU USED BACK

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS _____

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS B

3. I TOOK THIS COURSE (a) FOR GRINS (b) CAUSE I WANTED TO (c) CAUSE I HAD TO. ✓

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE ✓ (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD ✓ (c) AVERAGE (d) A SNOW JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL ✓ (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS _____ ✓


8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (N) A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS an circuit synth

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL ✓ (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

 11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS
[] CHECK HERE IF YOU USED BACK



1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS C.

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS C.

3. I TOOK THIS COURSE (a) FOR GRINS (b) BECAUSE I WANTED TO (c) BECAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSES I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SHODDY JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS ALL OF IT

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS the lesson of two

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON-EXISTANT (e) ALL OF THE ABOVE

COME BACK FOR COMMENTS
ON GRADE HERE IF YOU WOULD PLEASE

The lectures were very well organized &
you know the main idea. Unfortunately I
didn't understand it.

The labs were about all the time
it was for the lab instructor (lost part)
- would have been completely lost.

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS C

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS B

3. I TOOK THIS COURSE (a) FOR GRADES (b) BECAUSE I WANTED TO (c) BECAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SHODDY JOB (e) VERY RESTFUL

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS Circuit analysis

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A (Excellent)

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS about a CRT

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) IS SOMEWHAT HELPFUL (c) WILL BE OF NO HELP BY ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS
OR CHECK HERE IF YOU WISH TO

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS A

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS A

3. I TOOK THIS COURSE (a) FOR GRADES (b) BECAUSE I WANTED TO (c) BECAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSES I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SNOW JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS open & short circuits

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS _____

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NONEXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS
✓ CHECK HERE IF YOU USED BACK

I think you did a very good job helping us understand this course. I appreciated the extra time you spent by giving us reviews, it's too bad more people didn't take advantage of them.

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS A

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS A ~~not A~~ ^{I never am, because I} ~~sure, always feel I could do better.~~

3. I TOOK THIS COURSE (a) FOR GRINS (b) CAUSE I WANTED TO (c) CAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSE'S I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SNOW JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL QUITE DON'T UNDERSTAND (IF ANY) IS _____

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A(N) A ^{no kidding}

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS Application ^{overall} T.V., Radio

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL (c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING. ^{I am working for S.W. Bell this summer and it had help}

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NONEXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS
[] CHECK HERE IF YOU USED BACK

While I didn't get anything out of lab, I learned
a great deal in here and enjoyed. My major
is engineering physics and am hoping to direct my graduate
work toward an area in which I could use this then.

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE IS B

2. THE GRADE I FEEL I SHOULD RECEIVE IN THIS COURSE IS B

3. I TOOK THIS COURSE (a) FOR GRINS (b) CAUSE I WANTED TO (c) CAUSE I HAD TO.

4. COMPARED WITH THE DIFFICULTY OF OTHER ENGINEERING COURSES I'VE HAD, THIS ONE WAS (a) A BREEZE (b) ABOUT AVERAGE (c) HARD (d) IMPOSSIBLE

5. THE LECTURES WERE (a) EXCELLENT (b) PRETTY GOOD (c) AVERAGE (d) A SNOW JOB (e) VERY RESTFUL.

6. AS FAR AS UNDERSTANDING THE MATERIAL, THE HOMEWORK WAS (a) HELPFUL (b) KIND OF HELPFUL (c) NOT HELPFUL (d) A PAIN

7. THE PRIMARY TOPIC COVERED IN THIS COURSE WHICH I STILL DON'T UNDERSTAND (IF ANY) IS Hevinia & Norton Theorem

8. IF YOU WERE TO GIVE THE INSTRUCTOR A GRADE, IT WOULD BE A (a) A+

9. THE NEATEST THING I LEARNED IN THIS COURSE (IF ANYTHING) IS Kirckhoffs Law

10. AS FAR AS MY CAREER GOES, I FEEL THAT THIS COURSE (a) WILL BE VERY HELPFUL (b) BE SOMEWHAT HELPFUL

(c) WILL BE OF NO HELP AT ALL (d) HAS DESTROYED MY CONCEPT IN ENGINEERING.

11. THE LECTURE AND LAB COORDINATION WAS (a) GOOD (b) FAIR (c) POOR (d) NON EXISTANT (e) ALL OF THE ABOVE

USE BACK FOR COMMENTS →

CHECK MARK IF YOU USE A BACK

Bob, your a damn good teacher!
if you teach next semester I would
like to take the course that follows
this one.

K L

12 To by W. Oyer ✓

1. Bob Ballard ✓

78. Steve Jones ✓

17 ELYAHOUZADEH, YOUSSEF.

109 DEE MAXEY ✓

13 Dean Pierce ✓

2. Joe Craig ✓

6 Lynn Howerton ✓

47. Mike E. Little ✓

2. Clifton M Bloodworth ✓

15 ~~14~~ Manny Sings ✓

14 Robert Ross ✓

16 Walter WHEELER ✓

11 10 Tim Mc Clasky ✓

98 Rail Madrid ✓

0 5. Kelly Davis ✓

0 4. Greg Boston ✓

1
7
Marks

S.E. 228 ABL. INSTRUCTIONS

THE ABL. SCHEDULE FOR S.E. 228 IS AS FOLLOWS:

EXPT. # 1 MARCH 7-11

EXPT. # 3 APRIL 13-15

EXPT. # 2 MARCH 20-April 1

EXPT. # 4 APRIL 25-29

LET'S MEET IN ROOM EE67 ON FRIDAY, MARCH 4, AT 2PM TO COLLECT
EQUIPMENT AND DO EXPT. # 1.

Tom Stenio


QUIZ # 1

1. A VOLTAGE $V(t) = \frac{2V_0}{3}t$ IS APPLIED ACROSS AN INDUCTOR WHICH AT TIME $t=0$, HAS ONE AMP FLOWING THROUGH IT. IF THE INDUCTOR HAS A VALUE OF 2 mH ($= 2 \times 10^{-3} \text{ H}$), FIND THE CURRENT THROUGH THE INDUCTOR AT TIME $t=2$ SECONDS. ASSUME $S = 2 \times 10^3 \text{ SEC}$ AND $V_0 = 4 \text{ VOLTS}$.
 [HINT: $i_L(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(t) dt$]

2. FOR THE SAME VOLTAGE WAVEFORM, FIND THE CURRENT THROUGH A 2 mF ($= 2 \times 10^{-3} \text{ F}$) CAPACITOR AT TIME $t=2 \text{ SEC}$.
 [$i_C(t) = C \frac{dv}{dt}$]

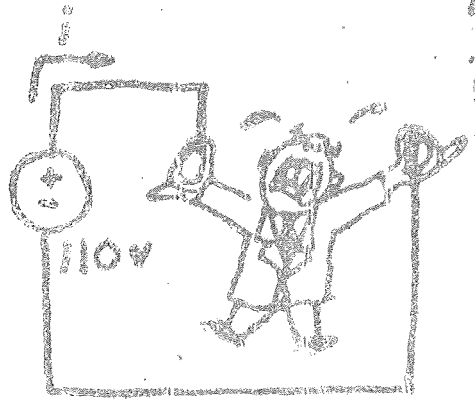3. 10 mA TO 100 mA ($1 \text{ mA} = 10^{-3} \text{ AMPS}$) THRU THE BODY COULD RESULT IN MUSCULAR PARALYSIS AND EXTREME BREATHING DIFFICULTIES. OVER 100 mA COULD RESULT IN DEATH.

SUPPOSE MR. SNURD ACCIDENTLY GRABS THE LEADS OF A 110 VOLT SOURCE (LIKE A WALL SOCKET). ASSUME



MR. SNURD IS WET, AND THAT THE RESISTANCE BETWEEN HIS RIGHT AND LEFT HANDS IS 1000Ω . IF 100 mA THRU MR. SNURD'S HEART WILL KILL HIM, WHAT WILL HIS CONDITION BE? SHOW YOUR WORK.

QUIZ 2 A - SOLUTIONS

$$1. i_L(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(t) dt$$

$$t_0 = 0, \quad i(0) = 1 \text{ AMP} \quad L = 2 \times 10^{-3} \text{ H},$$

$$v(t) = \frac{2V_0}{3} t; \quad S = 2 \times 10^3 \text{ SEC}, \quad V = 4 \text{ VOLTS}$$

$$\Rightarrow i_L(t) = 1 + \frac{1}{L} \int_0^t \frac{2V_0}{3} t dt$$

$$= 1 + \frac{V_0}{3L} \int_0^t 2t dt = 1 + \frac{V_0 t^2}{3L}$$

AT $t = 2 \text{ SEC}$

$$i_L(2) = 1 + \frac{(4V)(2\text{SEC})^2}{(2 \times 10^3 \text{ SEC})(2 \times 10^{-3} \text{ H})} = 1 + 4 = 5 \text{ AMPS}$$

$$2. i_C(t) = C \frac{dv}{dt}$$

$$= C \frac{d}{dt} \frac{2V_0}{3} t = \frac{2CV_0}{3}$$

$$= \frac{2(2 \times 10^{-3} \text{ F})(4 \text{ VOLT})}{2 \times 10^3 \text{ SEC}} = 8 \times 10^{-6} \text{ A} = 8 \mu\text{A}$$

THUS, @ $t = 2 \text{ SEC}$, $i_C(2) = 8 \times 10^{-6} \text{ A} = 8 \mu\text{A}$

3. OHM'S LAW: $V = IR$


$$V = 110 \text{ V}$$

$$I = 100 \text{ mA} = 0.1 \text{ A}$$

$$R = \frac{V}{I} = \frac{110 \text{ V}}{0.1 \text{ A}} = 1100 \Omega$$

$$= 1.1 \text{ k}\Omega$$

MINIMUM
ALLOWABLE
RESISTANCE

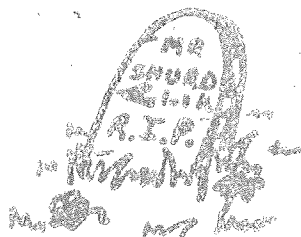

(1)(a) $8 + 9i_1 - i_2 = 0 \Rightarrow -8 = 9i_1 - i_2$

(b) $-15 = i_1 + 10i_2 = 0 \Rightarrow 15 = -i_1 + 10i_2$

MATRIX:
$$\begin{bmatrix} -8 \\ 15 \end{bmatrix} = \begin{bmatrix} 9 & -1 \\ -1 & 10 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

(b) $\Delta = \det \begin{bmatrix} 9 & -1 \\ -1 & 10 \end{bmatrix} = 90 - 1 = 89$

$\Delta_1 = \det \begin{bmatrix} -8 & -1 \\ 15 & 10 \end{bmatrix} = -80 - (-15) = -65$

$\Delta_2 = \det \begin{bmatrix} 9 & -8 \\ -1 & 15 \end{bmatrix} = 135 - 8 = 127$

$i_1 = \Delta_1 / \Delta = -65 / 89 = 0.73 \text{ AMPS}$, $i_2 = \Delta_2 / \Delta = 127 / 89 = 1.42 \text{ AMPS}$

(c) $V_1 = (i_1 - i_2) 1 \Omega = \frac{-65 - 127}{89} = \frac{-192}{89} = 2.16 \text{ volts}$

(2)(a) $2 + 4(-V_1) + (V_2 - V_1)8 = 0 \Rightarrow 2 = 12V_1 - 8V_2$

(b) $9(-V_2) + 2(4 - V_2) + 8(V_1 - V_2) = 0 \Rightarrow 8 = -8V_1 + 14V_2$

MATRIX:
$$\begin{bmatrix} 2 \\ 8 \end{bmatrix} = \begin{bmatrix} 12 & -8 \\ -8 & 14 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

(b) $\Delta = \det \begin{bmatrix} 12 & -8 \\ -8 & 14 \end{bmatrix} = 168 - 64 = 104$

$\Delta_1 = \det \begin{bmatrix} 2 & -8 \\ 8 & 14 \end{bmatrix} = 28 + 64 = 92$

$\Delta_2 = \det \begin{bmatrix} 12 & 2 \\ -8 & 8 \end{bmatrix} = 96 + 16 = 112$

$V_1 = \Delta_1 / \Delta = 92 / 104 = 0.885 \text{ volts}$, $V_2 = \frac{\Delta_2}{\Delta} = \frac{112}{104} = 1.08 \text{ volts}$

(c) $i = (V_2 - 4) 2 = \left(\frac{112}{104} - 4 \right) 2 = -5.85 \text{ AMPS}$

"A REPROOF ENTERETH MORE INTO A WISE MAN THAN A HUNDRED STRIPES INTO A FOOL"


Q.1) (a) (b) (c) (d) (e) (f) (g) (h) (i) (j) (k) (l) (m) (n) (o) (p) (q) (r) (s) (t) (u) (v) (w) (x) (y) (z)

(1) (a) (b) (c) (d) (e) (f) (g) (h) (i) (j) (k) (l) (m) (n) (o) (p) (q) (r) (s) (t) (u) (v) (w) (x) (y) (z)


(i) DETERMINE V_{oc} AND I_{sc} .

(ii) OBTAIN THE THEVENIN & NORTON EQUIVALENTS.

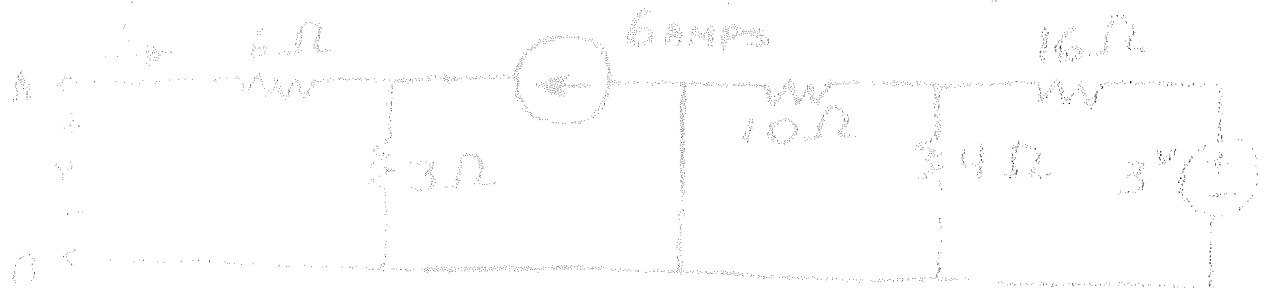(iii) IF WE CONNECTED A 9Ω RESISTOR BETWEEN TERMINALS A AND B, WHAT WOULD BE THE CORRESPONDING VOLTAGE AND CURRENT? (μ , V & I)



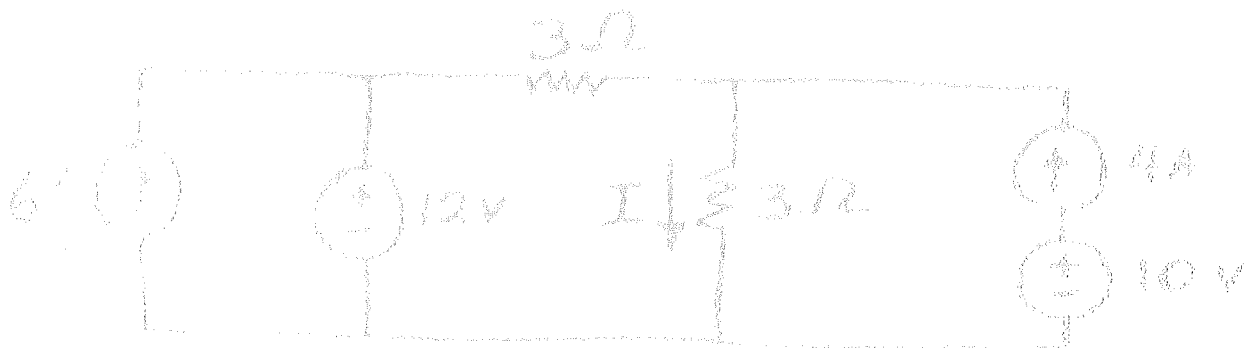(2) USING SUPERPOSITION, DETERMINE THE CURRENT I THRU THE 3Ω RESISTOR.



QUESTION 3, SOLUTIONS (MARKS) 2, 17



(1) UNDER SHORT CIRCUIT CONDITIONS, THE 2 AND 3 OHM RESISTORS FORM A CURRENT DIVIDER WITH THE 6 AMP SOURCE, THUS

$$I_{sc} = \frac{1}{\frac{1}{6} + \frac{1}{3}} \times 2 = 2 \text{ AMPS}$$

UNDER OPEN CIRCUIT CONDITIONS, ALL OF THE 6 AMPS MUST PASS THRU THE 3 OHM RESISTOR

$$\Rightarrow V_{oc} = (6 \text{ AMPS})(3 \text{ OHMS}) = 18 \text{ VOLTS}$$

$$(4) R = V_{oc} / I_{sc} = 9 \Omega$$

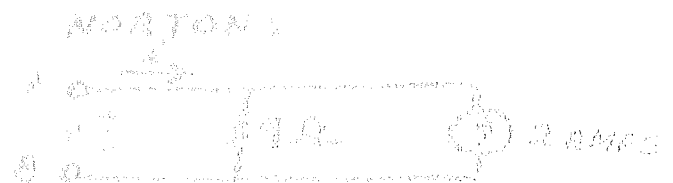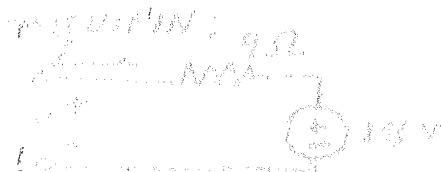

(c) THE THEVININ:



BY VOLTAGE DIVIDER

$$V = 9 \text{ VOLTS}$$

$$I = \frac{9}{4} = 2.25 \text{ AMP}$$

(2) (1) 6 AMP SOURCE \Rightarrow

ALL 6 AMPS GOES THRU THE BRANCH WITH 2 OHMS



(2) 10V SOURCE \Rightarrow

CURRENT, $I_1 = \frac{10}{5} = 2 \text{ AMPS}$



(3) 4 AMP SOURCE \Rightarrow

BE CURRENT DIVIDER

$I_2 = 2 \text{ AMPS}$



(4) 10 VOLT SOURCE \Rightarrow

PREVIOUSLY, $I_3 = 0$



$$I = I_1 + I_2 + I_3 + I_4 = 4 \text{ AMPS}$$

1. The following are the main types of ...
... ..




2. The following are the main types of ...
... ..



3. The following are the main types of ...
... ..

QUESTION SOLUTIONS (by Method)

1. FIND THE CURRENT THROUGH 2Ω RESISTOR

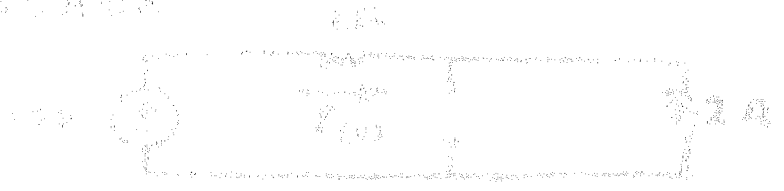

simply;

$$I_{2\Omega} = 12/3 = 4 \text{ amp}$$

now, apply KVL of loop source:




now current divider, $I_c = \frac{3}{3+4} \times 4 = 2.4 \text{ amp}$

$$\text{now, } I = I_{2\Omega} + I_c = 0$$

2. CHANGE INTO NORTON:



combine parallel elements:

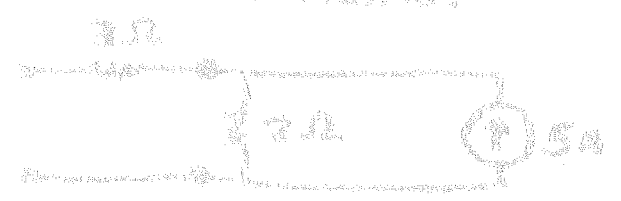

change back to a Thevenin:




$$I = 5A$$



(Ques 10) Ques 11 Ques 12

(a) 1. Show that $e^{j\omega t} = \cos \omega t + j \sin \omega t$

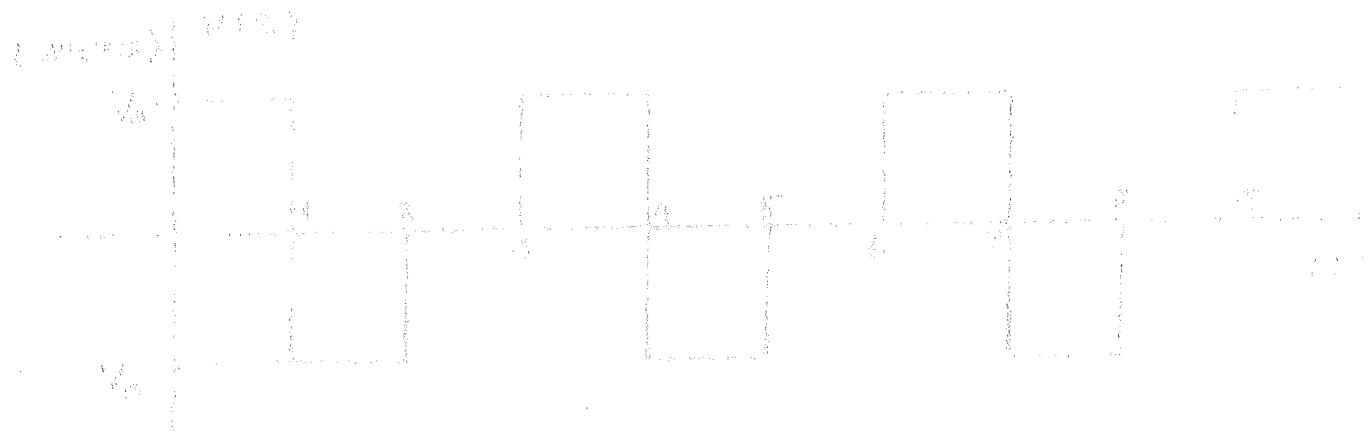(b) 2. Calculate V_{rms} and V_{avg} (a) for a sine wave and (b) for a periodic voltage waveform



(c) 3. Sketch the following complex number in the complex plane, noting magnitude and phase angle, (ϕ)

(a) $z = 3 + j$ (b) $z = 5 \angle 30^\circ$

4. Find the magnitude and phase angle of the following complex numbers

- (a) $z = 3 + j$
- (b) $z = 5 \angle 30^\circ$
- (c) $z = 3 + j$
- (d) $z = 5 \angle 30^\circ$

(Ques 13)

PROB. 1.1.1. (10) (10) (10) (10) (10) (10) (10) (10) (10) (10)

(1) (1) EULER. $e^{j\omega t} = \cos \omega t + j \sin \omega t$

2. SINCE, IN A PERIOD, THERE IS AN EQUAL AMOUNT OF POSITIVE & NEGATIVE AREA, $V_{ave} = 0$. (EASY)
 V_{rms} IS V_0^2 FROM 0 TO 2 AND 0 FROM 2 TO 3.
 THE $V_{rms}^2 = \frac{1}{3} [2V_0^2] \Rightarrow V_{rms} = \sqrt{\frac{2}{3}} V_0$ (EASY)
 ANOTHER WAY: $T=3$

$$V_{ave} = \frac{1}{T} \int_0^T v(t) dt = \frac{1}{3} \left[\int_0^1 V_0 dt + \int_1^2 (-V_0) dt + \int_2^3 0 dt \right]$$

$$= \frac{1}{3} (0) = 0$$

$$V_{rms}^2 = \frac{1}{T} \int_0^T v^2 dt = \frac{1}{3} \left[\int_0^1 V_0^2 dt + \int_1^2 0 dt \right]$$

$$= \frac{2}{3} V_0^2 \Rightarrow V_{rms} = \sqrt{\frac{2}{3}} V_0$$

3. (a)




$$r = \sqrt{1^2 + 1^2} = \sqrt{2}$$

$$\beta = \tan^{-1}(-1) = -45^\circ = -\pi/4$$

$$\Rightarrow w = \sqrt{2} e^{-j\pi/4}$$

(b) same as (a)

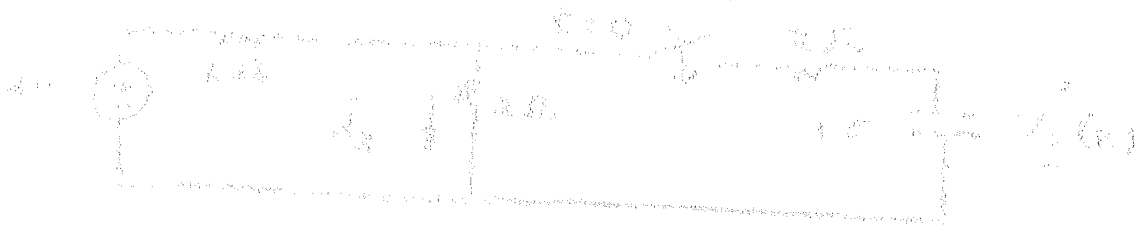Q.10) (10 marks) (10 marks) (10 marks) (10 marks)
 (a) SOLUTION!!!
 USE THE "FOUR NUGGETS" TO FIND $V_c(t)$ AND $i_2(t)$
 IN THE FOLLOWING CIRCUIT. SKETCH RESULTS.
 [EQUATIONS NOT NECESSARY]




(a) find $V_c(t)$:

$$V_c(0^-) = 0$$

$V_c(0) = 0$ \Rightarrow V can't change instantaneously across C

$V_c(\infty) = 1$ VOLT \Rightarrow @ ∞ , C ACTS AS OPEN CIRCUIT
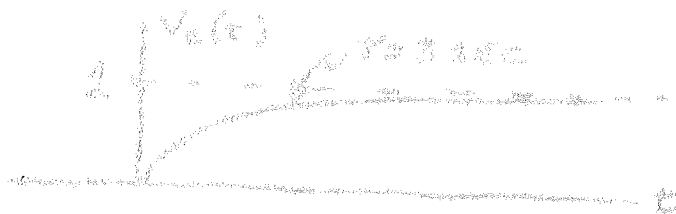
$$\tau = RC = 3 \Rightarrow (2\Omega \parallel 2\Omega) + 2\Omega = R_{eq} = 3\Omega$$



$$V_c(t) = (1 - e^{-t/3})$$

(b) find $i_2(t)$


$$i_2(\infty) = \frac{1}{2} \text{ AMP}$$

$$i_2(0^+) = \frac{1}{3} \text{ AMP}$$

$$i_2(\infty) = \frac{1}{2} \text{ AMP}$$

$$\tau = 3 \text{ sec}$$

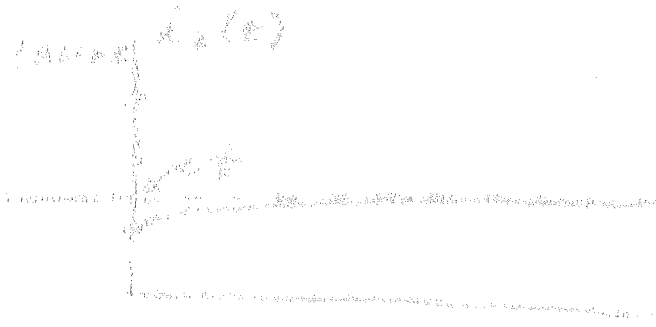* WHEN LIFE GOES TO
 YOU A LITTLE
 MORE LEARNINGS
 ONE CHANGE



$$i_2(t) = \frac{1}{2} + \left(\frac{1}{3} - \frac{1}{2}\right) e^{-t/3}$$

$$= \frac{1}{2} - \frac{1}{6} e^{-t/3} \quad ; t > 0$$

→ 1977

1. The first part of the report deals with the general situation of the country and the progress of the work.

2. The second part of the report deals with the results of the work done during the year.

3. The third part of the report deals with the conclusions drawn from the work.

4. The fourth part of the report deals with the recommendations.

5. The fifth part of the report deals with the summary of the work done during the year.

6. The sixth part of the report deals with the conclusions drawn from the work.

7. The seventh part of the report deals with the recommendations.

8. The eighth part of the report deals with the summary of the work done during the year.

9. The ninth part of the report deals with the conclusions drawn from the work.

10. The tenth part of the report deals with the recommendations.

11. The eleventh part of the report deals with the summary of the work done during the year.

12. The twelfth part of the report deals with the conclusions drawn from the work.

13. The thirteenth part of the report deals with the recommendations.

marks

EE 33 Lab. Instructions

- (1) Here are some extra problem sets you can use in the lab problem sessions. The chapter headings do not refer to our textbook, but to the text which I am reading. I would appreciate a copy of any accurate solution to any of these problems.

Tom Stroh

1. A point charge $Q_1 = +1.6 \times 10^{-18}$ coulombs, is separated from another point charge $Q_2 = -3.2 \times 10^{-17}$ coulombs, by a distance of 10^{-3} meters. The charges are in a vacuum.

a) Sketch a diagram of the physical layout.


b) Find the force on each charge and indicate the direction on the sketch.

2. A $+1.6 \times 10^{-19}$ coulombs charge (Q_3) is brought into the vicinity of the charges of problem 1. If $Q_1 + Q_2$ remains fixed in position, find at least one point where Q_3 could be located and the net force on it be zero. How many such points are there?

3. In the glass tube of fig. 2, the density of free electron is equal to the density of free ions, and is 1.6×10^{22} coulombs per cubic meter. If the electrons are travelling at 10^4 m/sec. and the ions at 10^6 m/sec., calculate the current from plate (a) to (b), assuming plate (a) is positively charged.

4. A copper wire, 0.01 meters in diameter, has a density of free electrons equal to 84×10^{23} electrons/m³. If a current in the wire is 2 amperes what is the average velocity of the electrons?

5.

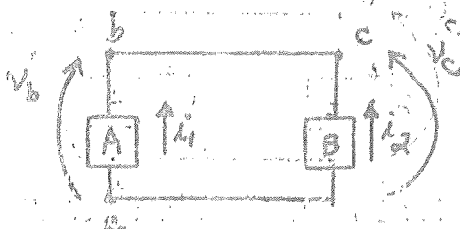

In the circuit shown,
 $i_1 = 1$ ampere $= -i_2$, $v_b = v_c$
 $= 5t$.

1) Sketch curves of i_1 , v_b and power supplied by box A vs. time, from zero to 10 seconds.

2) Calculate the power supplied by box A at time = 1, 2, and 5 seconds.

3) Calculate the power absorbed by box B at 1, 2 and 5 seconds.

4) Calculate the energy supplied by box A from 0 to 5 seconds.

6. In the circuit of problem 5, $v_b = 10 - 5t$, $i_1 = -i_2 = 10t$.

a) Sketch the curve of p_s of box A vs t , from 0 to 5 seconds.

b) Calculate p_s of box A at $t = 0, 1, 2, 3, 4$ seconds.

c) Calculate energy supplied by box A from 0 to 5 seconds.

7. Draw a plot of ϵ vs. r for $\epsilon = \frac{1}{4\pi\epsilon_0} \frac{Q}{r^2}$

8. For problem 7, find the power absorbed by box B as $t = 0, 1, 2$ seconds

9. *Omit*

A glass-ceramic rod, 0.1 meters long, 1 cm in diameter, has equal charges concentrated at each end. This is crude model of an ion-exchange capacitor between two conductors. Consider the charges as point charges. What is the maximum charge, Q_0 , before the rod will break in tension. The tensile strength of the glass-ceramic is 20,000 psi. Assume the forces will produce a uniform stress throughout the material.

*P.132 CRC Handbook of Tables for Applied Engineering Science.

10. A consumer of electrical energy requires 200 amperes of steady current over an 8 hour period, from a steady voltage source of 110 volts.

- What power is the customer using?
- How much energy in joules and watt-sec. is he using in the 8 hr. period?
- If he is paying 3¢ per kilowatt-hr. for the energy what is the cost for the 8 hrs?

11. How many electrons make up a coulomb? If a gas ion is doubly ionized (losing 2 orbital electrons), how many such ions are there in 1 coulomb of charge?

12.




Using the defined voltages shown in the figure, write KVL around the following loops:

- 1) A b c d a 2) d c e d 3) a b c d a
- 4) d e c d 5) a d c b a

7. Repeat problem 6; for $i = -10 + 10x = -i_2$.

8. For problem 7, find the power absorbed by box B at $t = 0, .5, 1$ and 2 seconds.

9. Omit

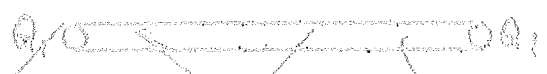

A glass-ceramic rod, 0.7 meters long, 1 cm in diameter, has equal charges concentrated on each end. This is crude model of an insulator supporting two conductors. Consider the charges as point charges. What is the maximum charge, Q_1 , before the rod will break in tension. The tensile strength of the glass-ceramic is 20,000 psi.* Assume the forces will produce a uniform stress throughout the material.


*P.132 CRC Handbook of Tables for Applied Engineering Science.

10. A consumer of electrical energy requires 100 amperes of steady current over an 8 hour period, from a steady voltage source of 110 volts.

- a) What power is the customer using?
- b) How much energy in joules and watt-sec. is he using in the 8 hr. period?
- c) If he is paying 3 ¢ per kilowatt-hr. for the energy, what is the cost for the 8 hrs?

11. How many electrons make up a coulomb? If a gas ion is doubly ionized (losing 2 orbital electrons), how many such ions are there in a coulomb of charge?

12.

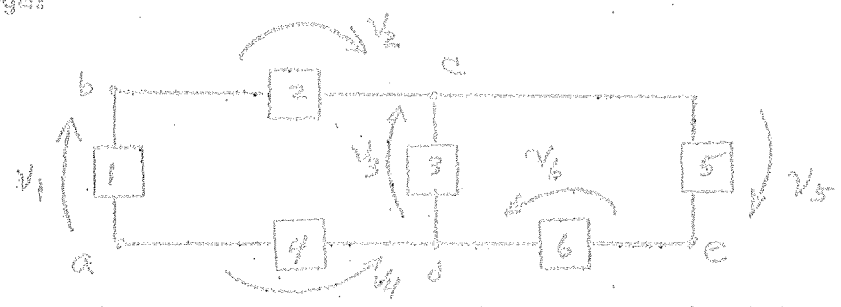

Using the defined voltages shown in the figure, write KVL around the following loops:

- 1) a b c d a 2) d c e d 3) a b c e d a
- 4) d e c d 5) a d c b a

A wire of length l and cross-sectional area A is connected to a battery of emf \mathcal{E} and internal resistance r . The wire is at a temperature T and has a resistance R . The current in the wire is I .

Derive:

Boice, Roy E., and Mary A. Hill. "Methods of Physics for Experimental Science." Ohio: The Chemical Rubber Company, 1954.

- What is the resistance of the wire at T in terms of l , A , and ρ ?
- What is the resistance of the wire at T in terms of l , A , and ρ ?
- What is the diameter of the wire in terms of l , A , and ρ ?
- What is the power absorbed by the wire at T in terms of \mathcal{E} , r , and R ?
- What is the voltage across the wire at T in terms of \mathcal{E} , r , and R ?

2. A wire of length l and cross-sectional area A is connected to a battery of emf \mathcal{E} and internal resistance r .

The wire is at a temperature T and has a resistance R . The current in the wire is I . The wire is at a temperature T and has a resistance R . The current in the wire is I . The wire is at a temperature T and has a resistance R . The current in the wire is I .

- What length of wire is required at T ?
- What is the voltage across the resistor in terms of \mathcal{E} , r , and R ?
- If the temperature rises to 60°C , what is the resistance?


3. A wire of length l and cross-sectional area A is connected to a battery of emf \mathcal{E} and internal resistance r . The wire is at a temperature T and has a resistance R . The current in the wire is I .

- What is the voltage across the load?
- What is the power absorbed by the load in terms of \mathcal{E} , r , and R ?

4. A wire of length l and cross-sectional area A is connected to a battery of emf \mathcal{E} and internal resistance r .


- What is the maximum power that can be dissipated in the load in terms of \mathcal{E} , r , and R ?
- What is the maximum power that can be dissipated in the load in terms of \mathcal{E} , r , and R ?

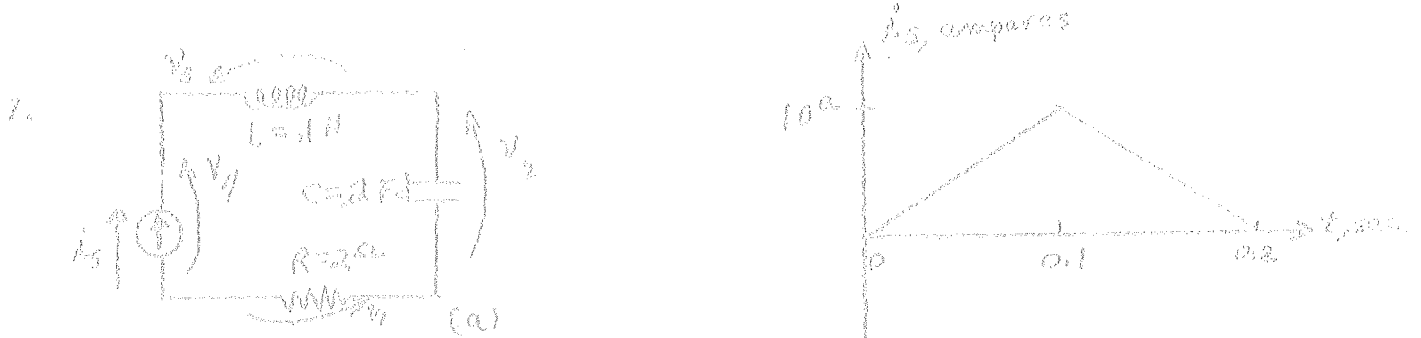6. a) A 10,000 ohm resistor in an electrical circuit will have 100 volts across it. What should be its power-rating?
- b) If two 5000 ohm resistors in series are substituted for the 10,000 ohm resistor, what should be the power-rating of each one?




The circuit shown in fig. (a) has a source supplying current as shown in figure (b). There is zero energy stored in L and C at $t = 0$.

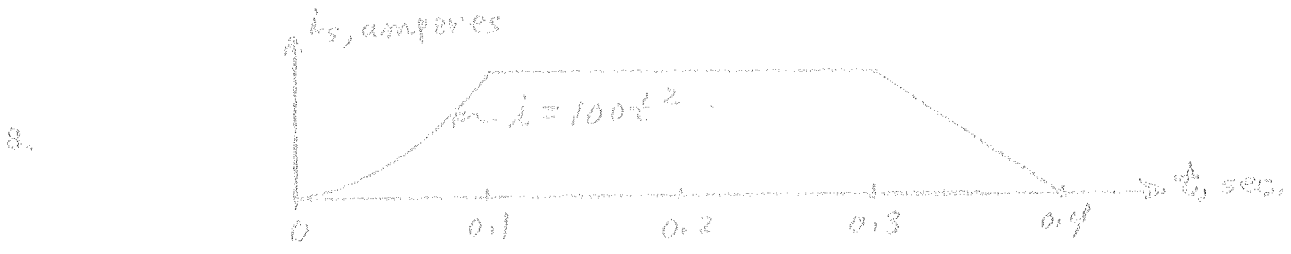- a) Sketch curves of v_1 , v_2 , and v_3 vs. t , showing values at $t = 0, .1$ and $.2$ seconds, $.3$ and $.4$ sec. for prob. 8.
- b) Sketch curves of energy stored in L and energy stored in C vs t , showing values at $t = 0, .1$ and $.2$ seconds, $.3$ and $.4$ seconds for prob. 8.
- c) What is the instantaneous power absorbed by R at $t = 0.05$ and 0.35 seconds?
- d) Repeat (c) for the inductor, and for the capacitor.



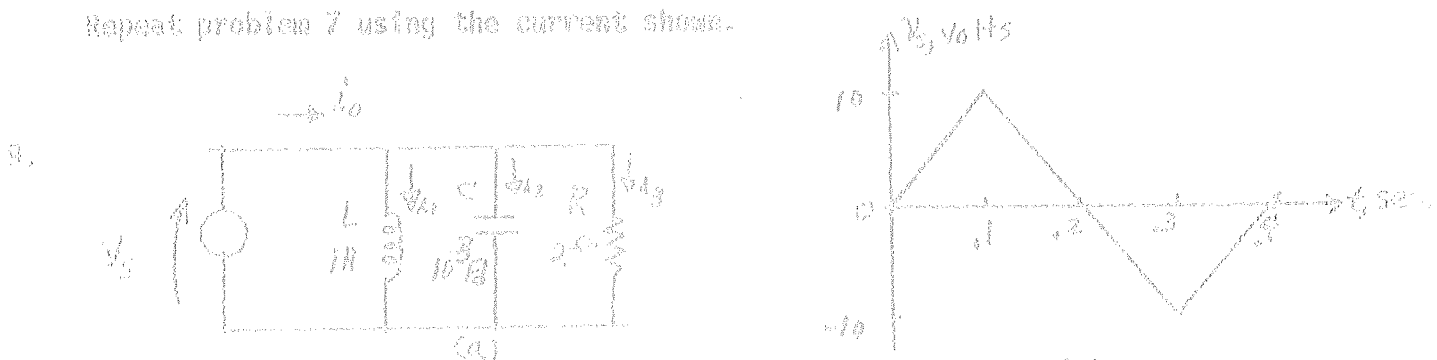Repeat problem 7 using the current shown.



The source voltage waveform for circuit (a) is given in fig. (b). No energy is stored in L or C at $t = 0$.

- a) Sketch i_1 , i_2 and i_3 vs t . Show values at $t = .1, .2, .3, .4$ and $.5$ seconds.
- b) Sketch a curve of i_0 vs t .
- c) What energy is stored in L and in C at $t = .3$ seconds?
- d) What instantaneous power is the source supplying at $t = 0.2$ seconds?

- c) How much energy has each of the elements absorbed by time $t = 0.5$ seconds?
 d) Find the energy supplied by the source, by time $t = 0.5$ seconds.

33.

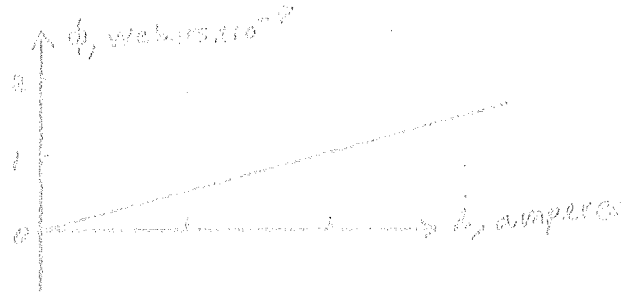
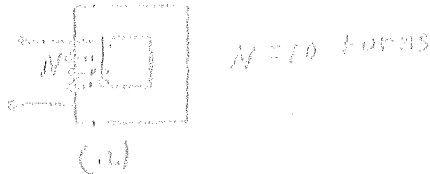



Figure (a) shows a coil with a closed iron core. The ϕ - I curve for this coil without the iron core is shown in fig. (b).

- a) What is the inductance of the coil without the iron core?
 b) If the iron core increases the slope of curve fig. (a) by 2000 times, what is the inductance of the coil with the iron core?
 c) If the number of turns for coil of part (b) is doubled, find the new value of inductance.

32. A parallel plate condenser with an air dielectric has a value of capacitance of 10^{-9} Fd.

- a) What is the new value of c if the distance between plates is doubled? How much is c increased by changing the dielectric to polystyrene?


33.

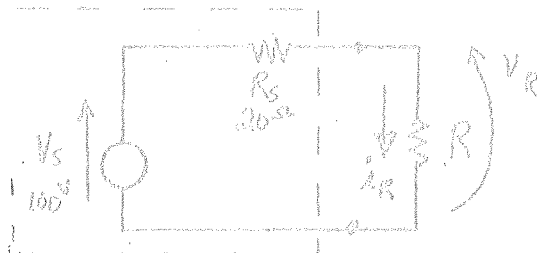

The model for a practical source connected to a load is shown in the figure.

- a) Find v_R and i_R for the following values of R (in ohms).
 $R = 1, 5, 10, 20, 100, 200$ and infinity.
 b) Plot a curve of v_R vs i_R .
 c) On the same set of axes, plot a curve of power absorbed by R and power absorbed by R_s vs R .
 d) What is the relative values of the two resistors (R, R_s) for the case of maximum power absorbed by R ?

14.

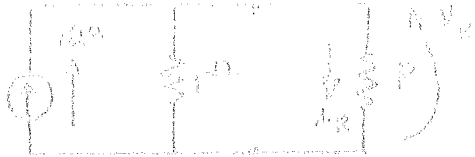

Plot curves of v_R and i_R vs R , using these values of R (ohms): 0, 50, 1, 2, 10, 100, infinity.


15.



$v_c(0) = -2$ volts

- a) Define loop currents.
- b) Write the voltage equations in terms of the defined currents and circuit elements.

16.

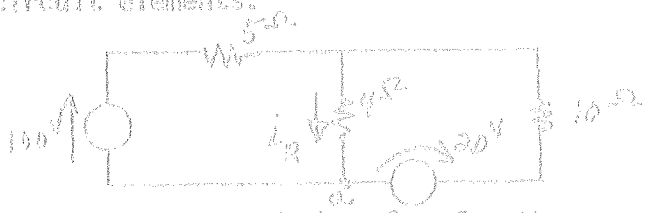

- a) Using the loop method, solve for the currents in each source.
- b) Find the power supplied by each source
- c) Find the power absorbed by each resistor.

17.

- a) For the circuit in problem 16, define branch currents and solve for the current in the 20 volt source.
- b) Find the power supplied by the 20 volt source.

18.

- a) For the circuit of problem 16, define the minimum number of unknown voltages, using node 'a' as a reference.
- b) Solve for the voltage(s) of part (a).
- c) Find i_R .

19.




- Solve for current i_1 using the loop method.
- Solve for voltage v_0 using the node method.

20. For the circuit of problem 19:

- Solve for current i_2 using the loop method.
- Solve for voltage v_0 using the node method.

21.

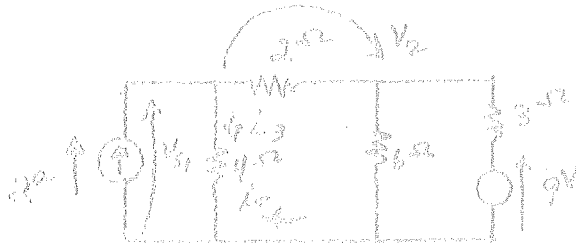

Find the current in the 4 ohm resistor.
Find V_2 , power supplied by the 9 volt source.

22. For the circuit of problem 21, find the voltage across the 6 ohm resistor.
Find i_3 , V_{9V} , power supplied by the 2ampere source.

23. For the circuit of problem 21, find the current in the 2 ohm resistor, and i_5 .

24.

When maximum detail is desirable, and a digital computer is available for a solution, circuit analysis can be done using the following procedure:

- Define branch voltages $v_1, v_2, v_3, v_4, v_5, v_6$.
- Define branch currents $i_1, i_2, i_3, i_4, i_5, i_6$.
- Write KVL in terms of voltages defined in step 1.


$$v_1 + v_2 - v_4 = 0$$

$$v_4 - v_5 - v_6 = 0$$

$$v_3 - v_5 - v_2 = 0$$
- Write ohms law relations for each branch voltage

$$v_1 = v_3 + i_1 R_1 \quad v_3 = i_3 R_3 \quad v_5 = i_5 R_5$$
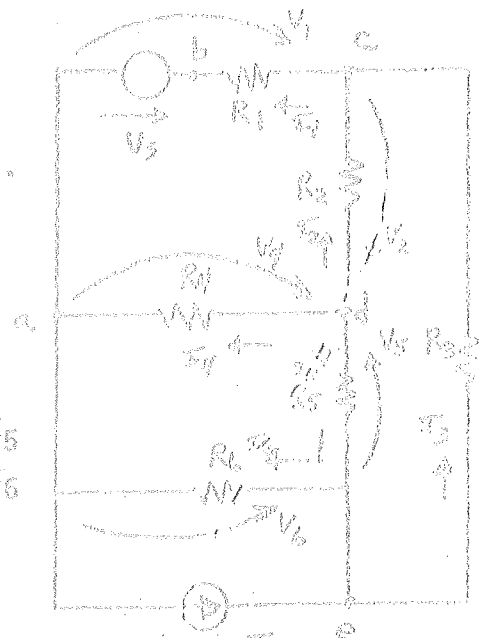
$$v_2 = i_2 R_2 \quad v_4 = i_4 R_4 \quad v_6 = i_6 R_6$$



5. Write KCL for each major node

$$\text{Node C: } -I_1 + I_2 + I_3 = 0$$

$$\text{Node D: } I_2 + I_4 + I_5 = 0$$

$$\text{Node E: } I_5 + I_6 - I_6 - I_3 = 0$$

6. Solve the above 12 equations for the particular unknowns of interest.


PROBLEM 24

a) Write the determinant for the voltage V_d .

b) Write the determinant for the current I_1 .

c) What computer language is best suited for the solution of equations of part (a) or (b)?

25.

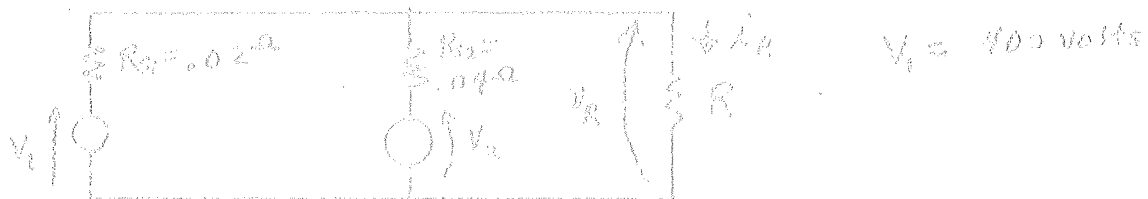

Two generators are supplying power to an industrial plant, represented by $R = 0.5 \text{ ohms}$. The voltage v_R is to be 392 volts.

a) Find the value of v_2 needed to provide the required v_R .

b) Find the power supplied by each source. (Subtract the loss in R_{s1} or R_{s2}).

c) Express the power loss in each generator as a percent of the power absorbed by the load.

d) Efficiency.

26. Generator 2 (v_2) in problem 24, is removed from the circuit, (open circuited).

a) Find V_1 needed to provide 392 volts to the load.

b) If the maximum voltage for V_1 is 410 volts, what will be the maximum value of v_R ?

27. In the circuit of problem 24, $V_2 = 400$ volts.

- What value will V_R have?
- What power will each generator be supplying?
(subtract power loss in R_{s1} or R_{s2} .)


28. A 12 battery is discharged when its terminal voltage is 10.5 volts. It has internal resistance of 0.01 ohms. A source is connected in series with the battery in order to charge it.

- Draw the circuit and indicate the polarity of the battery and charging source.
- What charging voltage is needed to provide 5 amperes of charging current?
- After one hour's time, the battery voltage has risen to 13.2 volts. What charging voltage is needed to maintain the 10 amperes charging current?

29.



(a)

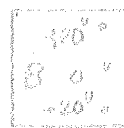

(b)

Several power supplies of each type available in a laboratory.

depicted in the figure are

- How should two supplies of the Fig. (a) type be connected to provide simultaneous voltages of 0, +10, and +20 volts? Indicate the reference node in the connection. Draw the connections.
- Show how to connect two supplies of Fig. (b) to provide simultaneous voltages of: 0, +20, +40, -20, -40 volts.
- Show the connections required to provide simultaneous voltages of -40, -20, 0, +10 volts.

Marks


I am sure that you will be
for the work of marks assigned to
expect on them, must be at
12:30 P.M. (if you can) to
reasonable equipment and perform
the experiments.

T. J. Stone

98
①

The instruments to be used in this experiment are the variable frequency audio oscillator (see HP 400 manual), a voltmeter (VTVM), and the oscilloscope (CRO). The VTVM is a high impedance voltmeter with reasonable accuracy over the audio frequency range. Learn to use the oscilloscope to measure voltage, frequency and to observe the actual waveforms. Current resonance in the series circuit and voltage resonance in the parallel circuit will be observed as the source frequency is varied.

Series Resonance

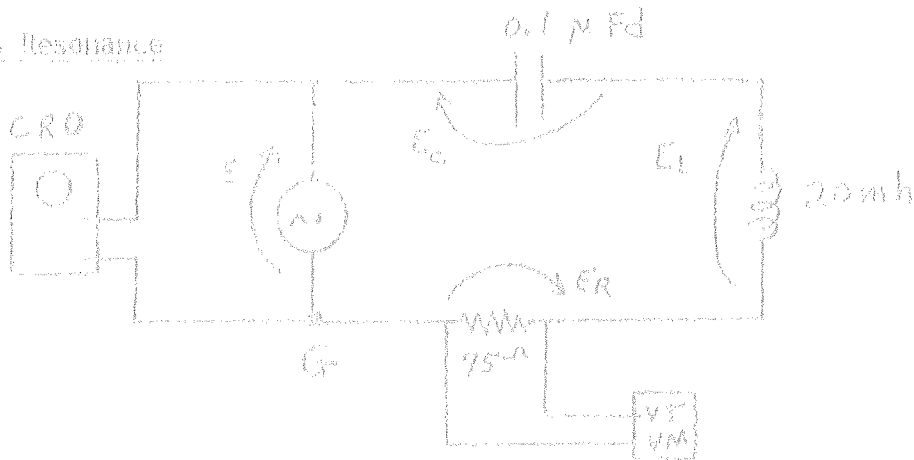

A) Connect the circuit shown. (Caution) Since the CRO and VTVM are each grounded through the a.c. line, be sure the ground terminal of each is connected to point G of the circuit. E is the audio oscillator with the amplitude dial set to give 8 volts peak-to-peak. Use the oscilloscope to measure E and the VTVM to measure I_R .

B) Vary the frequency until resonance (Max. $E_R = E_{R0}$) occurs. At resonance record the frequency, E_R , and E. Keep E constant for parts B, C, D, and E. Measure the frequency using the CRO.

C) Disconnect the CRO (both terminals), and measure E_C and E_L at resonance with VTVM.

D) Reconnect the system as in part (A), and with E set at each half power point ($.707E_{R0}$), record the readings of part (B).

Application of the sweep

In the practical experiment, a limited frequency range, Δf , is used, but the sweep is not linear over the whole range of frequencies. The sweep is linear over a limited range, Δf , which is a small fraction of the total frequency range Δf . The positive Δf sweep is used with the rate of sweep ω .



The time range of the modulation Δt is determined by the rate of sweep ω . For the VLF to measure f_0 the VLF has a frequency f_0 (in the range $10^4 - 10^5$).

Let us assume that f_0 varies according to the frequency $f_0(t) = f_0 + \Delta f_0 \sin(\omega t)$. The VLF is measured by measuring $f_0(t) = f_0 + \Delta f_0 \sin(\omega t)$ at various frequencies. The VLF is measured f_0 with the VLF and with the frequency $f_0(t) = f_0 + \Delta f_0 \sin(\omega t)$.

The VLF is measured with a constant rate $f_0(t) = f_0 + \Delta f_0 \sin(\omega t)$ for a fixed rate of sweep ω . The VLF is measured with a constant rate $f_0(t) = f_0 + \Delta f_0 \sin(\omega t)$.

$$\omega = \frac{df_0}{dt}$$

The VLF is measured with a constant rate $f_0(t) = f_0 + \Delta f_0 \sin(\omega t)$ for a fixed rate of sweep ω . The VLF is measured with a constant rate $f_0(t) = f_0 + \Delta f_0 \sin(\omega t)$.

The VLF is measured with a constant rate $f_0(t) = f_0 + \Delta f_0 \sin(\omega t)$ for a fixed rate of sweep ω . The VLF is measured with a constant rate $f_0(t) = f_0 + \Delta f_0 \sin(\omega t)$.

The VLF is measured with a constant rate $f_0(t) = f_0 + \Delta f_0 \sin(\omega t)$ for a fixed rate of sweep ω . The VLF is measured with a constant rate $f_0(t) = f_0 + \Delta f_0 \sin(\omega t)$.

Meters Used in A.C. Circuits

This experiment is to acquaint the student with ammeters and voltmeters as used in a.c. circuits. The measurements will verify phasor relationships existing among the voltages and currents. Power will be obtained using the circuit of Fig. 1. The auto-transformer is an inductor connected in parallel with the power line, and has a variable tap, so that the source voltage V_S can be set to any value up to about 150 volts RMS.


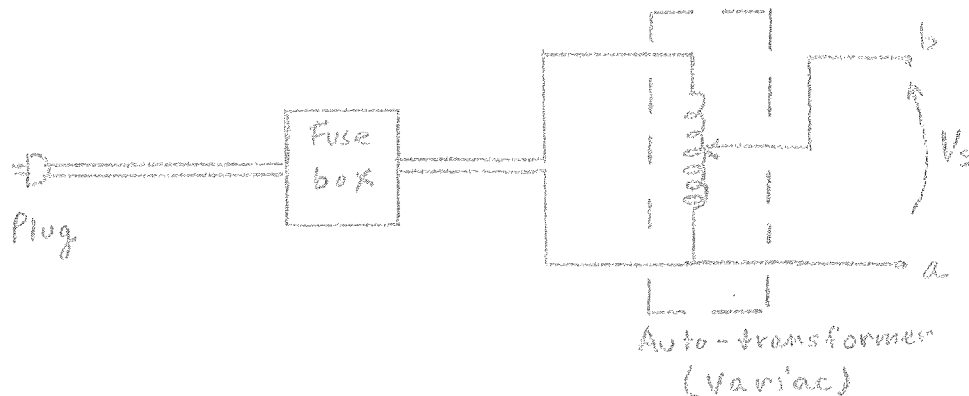


Fig. 1

Make all connections with the circuit unplugged and variac set to zero. After the lab instructor has checked the connections, the circuit can be plugged in and variac increased gradually to the proper value.

1. Series R-L Circuits

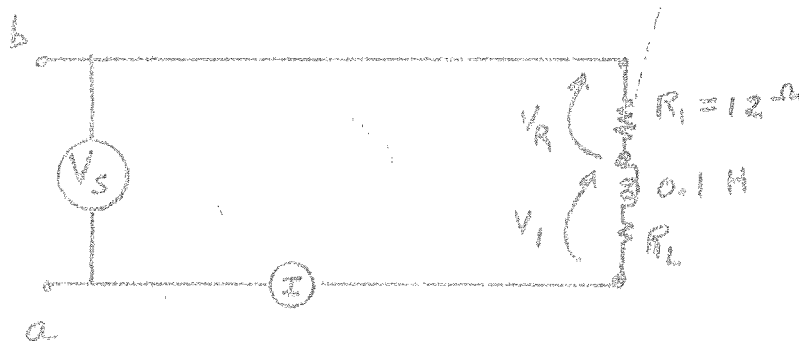


- a) Connect the circuit shown and have the instructor check connections. Then energize the circuit and increase V_S to 60 volts (RMS) and record meter readings for I , V_S , V_L and V_R .
- b) Measure the D.C. resistance of R_1 and of the coil (R_L).

Resonance in a Parallel RLC Circuit

As the frequency of the AC source is varied, the impedance of the parallel RLC circuit changes. At resonance, the impedance is purely resistive and is at its minimum value. This occurs when the inductive reactance and capacitive reactance are equal in magnitude but opposite in phase, canceling each other out. The circuit then behaves like a simple resistor. The current through the circuit is at its maximum value, and the voltage across the resistor is at its maximum value. The power dissipated in the resistor is also at its maximum value.

Figure 1: Resonance in a Parallel RLC Circuit

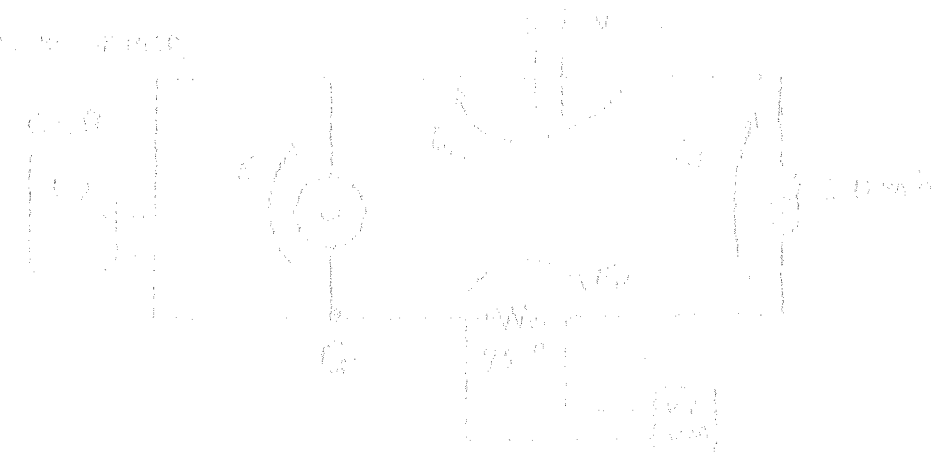

At resonance, the circuit behaves like a simple resistor. The current through the circuit is at its maximum value, and the voltage across the resistor is at its maximum value. The power dissipated in the resistor is also at its maximum value. The resonance frequency ω_0 is the frequency at which the circuit is at resonance.

The resonance frequency ω_0 is given by the equation $\omega_0 = \frac{1}{\sqrt{LC}}$. The resonance frequency ω_0 is the frequency at which the circuit is at resonance. The resonance frequency ω_0 is the frequency at which the circuit is at resonance.

The resonance frequency ω_0 is the frequency at which the circuit is at resonance. The resonance frequency ω_0 is the frequency at which the circuit is at resonance.

The resonance frequency ω_0 is the frequency at which the circuit is at resonance. The resonance frequency ω_0 is the frequency at which the circuit is at resonance.

1. Introduction

The purpose of this report is to provide a comprehensive overview of the current state of research in the field of quantum mechanics, focusing on the development of new theoretical models and their experimental verification. The report is organized into several sections, each addressing a specific aspect of the research.



The first section discusses the historical context of quantum mechanics, highlighting key experiments and theoretical breakthroughs. The second section focuses on the mathematical formalism, including the Schrödinger equation and the concept of wave functions.

The third section explores the application of quantum mechanics in modern technology, such as quantum computing and quantum cryptography. The fourth section discusses the philosophical implications of quantum mechanics, particularly the measurement problem and the role of the observer.

The fifth section provides a summary of the current state of the field and outlines future research directions. The report concludes with a list of references and a bibliography.

References

1. Dirac, P. A. M. (1930). *The Principles of Quantum Mechanics*. Cambridge University Press.

2. Heisenberg, W. (1927). Über den anschaulichen Inhalt der quantentheoretischen Kinematik und Mechanik. *Zeitschrift für Physik*, 41, 1-51.

3. Schrödinger, E. (1926). Quantenmechanik der Materie. *Annalen der Physik*, 79, 361-376.

marks

DATE: _____



Figure 1: A rectangular frame with a central point. The corners are labeled 1, 2, 3, and 4. The lines connecting the center to the corners are labeled A, B, C, and D.

The diagram illustrates the geometry of the frame. The central point is equidistant from all four corners. The lines A, B, C, and D represent the connections between the center and the corners. The corners are numbered 1, 2, 3, and 4 in clockwise order starting from the top-left corner.

The diagram shows the relationship between the central point and the corners of the frame. The lines A, B, C, and D are labeled accordingly.

The diagram illustrates the geometry of the frame. The central point is equidistant from all four corners. The lines connecting the center to the corners are labeled A, B, C, and D.

The diagram shows the relationship between the central point and the corners of the frame. The lines A, B, C, and D are labeled accordingly.

Figure 2

The diagram shows the relationship between the central point and the corners of the frame. The lines A, B, C, and D are labeled accordingly.

The diagram illustrates the geometry of the frame. The central point is equidistant from all four corners. The lines connecting the center to the corners are labeled A, B, C, and D.

The diagram shows the relationship between the central point and the corners of the frame. The lines A, B, C, and D are labeled accordingly.

The diagram illustrates the geometry of the frame. The central point is equidistant from all four corners. The lines connecting the center to the corners are labeled A, B, C, and D.

Text: Smith, Circuits, Devices and Systems, Wiley Vines, Automation of Petrochemical and Chemical Systems, Tech Printed, Tech Bookstore

Week	Chapter	Topics
1	Ch. 1 (Vines)	Overview of Automation Smith last Ch.
2	Ch. 2 (Vines)	Rise time, freq. resp, reliability
3	Ch. 3 (Vines)	Smith ch Transducers
4	Quiz	Transducers
5		Transducers and signal conditioning
6	Ch. 4 (Vines)	Telemetry, communications
7		Telemetry
8	Quiz	Vines Ch. 5 Computers ✓
9		Computers
10		Programming
11	Quiz	Vines Ch. 6 Motors and Controls
12		Motors.
13		Vines Ch. 7 Systems Overview
14	Quiz	Systems Overview

22 234 Tour an automated Petrochemical Plant in groups of 3 or 4 no earlier than March 13

Write report and present to class if required in last week.

23 234 Write a computer Program to test 4 wells, produce into 2 separators, dump oil/water

into tanks, don't overflow!

24 234 Five labs to be conducted with class, suggested times 7:30-9:30 as required.

25 234 Do library reports each week for articles related to topic of discussion. Do not

repeat these in annotated Bibliography

HOMWORK GRADING

26 234 Labs as scheduled

27 234 Tour may be optional

$m = \#$ PROBLEMS ASSIGNED
 $q = \#$ " NOT ATTEMPTED
 $n = \#$ " GRADED $\geq m/2$
 $p_i = \#$ POINTS GIVEN ON i th PROBLEM. $i = 1, \dots, n$
 $I(d) =$ NEXT HIGHEST INTEGER $\geq d$

$0 \leq p_i \leq 10$

SCORE = $I(d)$ WHERE

$$d = \left(\sum_{i=1}^n p_i \right) \left(\frac{m-q}{n} \right)$$

$$d_{MAX} = I_{MAX} = 10M$$

Text: Circuits, Devices and System's by Ralph Smith Third Edition (Second Edition)

<u>Topic</u>	<u>Ch</u>	<u>Pages</u>
1 Semiconductor diodes	11 (9)	290-303 (267-280)
2 Diode Models & Application	12 (10,12)	311-319 (311-315, 391-396)
3 Field Effect Transistor (FET)	13 (9)	335-340 (286-288)
4 Bipolar Junction Transistor (BJT)	13 (9)	340-349 (289-293, 297-300)
5 Integrated Circuits	13 (9)	348-354 (293-295)
6 Practical Amplifiers	16 (11)	409-413 (343-348)
7 Biasing BJT	16 (11)	419-423 (352-356)
8 Power Amplifiers	16 (11)	423-431 (357-364)
9 Other Amplifiers	16 (11)	431-433 (379-382)
10 Triodes & Pentodes	10 (9)	274-278 (282-287)
11 Two Port parameters	8, 17 (8, 10)	217-218, 445-446 (223-224, 316-317)
12 FET parameters & model	17 (notes)	446-450
13 BJT Parameters & Model	17 (10)	452-459 (327-335)
14 RC Coupled Amplifiers	18 (11)	465-481 (364-375)
15 Multistage Amplifiers	18 (11)	481-484 (375-379)
16 Modulation	17 (12)	440-443 (407-412)
17 A Communication System	17 (12)	443-458-9 (412-14)
18 Operational Amplifiers	19 (20)	506, 512 (641-44, notes)
19 Analog Computer	19 (20)	523-28 (645-50)
20 Instrumentation	27 (21)	709-735 (653-681)
21 A. C. Machines	25 (18)	659-679 (577-596)
22 D. C. Machines	24 (18)	631-648 (557-573)

- PRELIMINARY CLASS ROLLS -

PR001

DEPARTMENT 590 (E E) COURSE 234 SECTION 004

INSTRUCTOR ~~WISE~~ *Marka* ~~GARY~~ *Bob* L

STUDENT NUMBER	LAST NAME	FIRST NAME	MI	SCHOOL	CLASS	SEX
496 70 8304	ABU-SARRIS	FAHMI	H	04	4	1
462 84 0851	ANTHONY JR	WILLIAM	R	04	9	1
460 92 8241	BOU-CHEBL	SABA	S	04	4	1
456 80 1932	CAGLE	BILLY	R	04	2	2
460 04 6744	CAVINESS	WYNDELL	R	04	4	1
454 08 9465	DUNN ✓	TIMOTHY	M	04	4	1
366 72 3166	EL-SABAALY	BOUTROS	G	04	4	1
459 88 3465	HENDRIX	ROBERT	E	04	3	1
465 76 3151	HILL	WILLIAM	B	04	4	2
463 80 8812	HOLSOMBACK	THEODORE	W	04	4	2
465 11 7454	MOORE	KEITH	W	04	3	1
466 90 8616	MOORE	MICHAEL	L	04	4	2
465 06 8496	PRATHER	RICKY	K	04	3	1
452 02 7517	PUCKETT ✓	KENT	S	04	4	1
465 04 7489	RDACH	GARY	B	04	2	1
466 08 3306	SAUER	PAUL	W	04	4	1
454 15 4927	SAVAGE	KELLY	B	04	3	1
328 38 9752	SCIALO	ANTHONY	M	04	4	2
478 80 0190	TU	QUT	H	04	4	4
459 92 2258	WHITE	GARY	L	04	4	1

*TOTAL NUMBER OF STUDENTS 20

- PRELIMINARY CLASS ROLLS -

RR001

Mark

DEPARTMENT 590 (B E) COURSE 234 SECTION 004

INSTRUCTOR WISE GARY L

STUDENT NUMBER	LAST NAME	FIRST NAME	MI	SCHOOL	CLASS	SEX
496 70 8304	ABU-SARRIS	FAHMI	H	04	4	1
462 84 0851	ANTHONY JR	WILLIAM	R	04	9	1
460 92 8241	BOU-CHEBL	SABA	S	04	4	1
456 80 1932	CAGLE	BILLY	R	04	3	2
460 04 6744	CAVINESS	WYNDELL	R	04	4	1
454 08 9465	DEHKORDI DUNN	FAHSH. TIMOTHY	M	04	4	1
366 72 3166	EL-SABAALY	BOUTROS	G	04	4	1
459 88 3465	HENDRIX	ROBERT	E	04	3	1
365 76 3151	HILL	WILLIAM	B	04	4	2
463 80 8812	HOL SOMBACK LUNSFORD	THEODORE	W	04	4	2
465 11 7454	MOORE	KEITH	W	04	3	1
466 90 8616	MOORE	MICHAEL	L	04	4	2
466 06 8496	NAPIER PRATHER PAKRAVAN	BUDDY RICKY FARHAD	K	04	3	1
452 02 7517	PUCKETT PIERCE	KENT JOHN	S	04	4	1
465 04 7489	ROACH	GARY	B	04	2	1
466 08 3306	ROSS SAUER	GLYDEN PAUL	W	04	4	1
454 15 4927	SAVAGE	KELLY	B	04	3	1
328 38 9752	SCIALO THAXTON	ANTHONY SABER	M	04	4	2
478 80 0190	TU	QUI	H	04	4	4
* 459 92 2398	WHITE	GARY	L	04	4	1

*TOTAL NUMBER OF STUDENTS 20

SEMESTER		DEPARTMENT	NUMBER	SECTION	PAGE NO.
SPRING 1977 FEB 01, 1977		590 ()	234	004	1
INSTRUCTOR			DESCRIPTIVE TITLE		
CILING T (1)			ELECTRONIC INSTRUMENTATION		
SOC. SEC. NO.	STUDENT'S NAME		SCH.	CLASS	REMARKS
496 70 8304	ARIE-SAPORTIS	PAUL	H	04 4	
562 80 0831	ANTHONY JR	WILLIAM	R	03 5	
460 92 3241	DEBI-CHESL	SARA X	S	05 4	
456 80 1932	EAGLE	BILLY	P	0 - 3	
460 03 7744	SAINTON	RYAN L X		04 4	DROP
442 68 7757	DEKOPET	SHABROKH		04 4	
454 08 3405	GUNN	TIMOTHY	M	0 - 1	
366 72 3166	GL-SABAALY	BOUTECS	G	04 4	
459 88 3465	NEUBERT	ROBERT X	E	04 4	DROP
465 76 3151	HILL	WILLIAM	B	04 4	
463 80 3812	HILCOMBACK	THEODORE X	M	04 4	
450 11 1748	LUNSFORD	JAY	L	01 4	
465 11 7454	MIDDE	KEITH	M	04 4	
466 90 3616	MUIRE	MICHAEL	L	0 - 4	
463 13 7394	MARTIN	BARNIS X	G	04 4	
119 50 5642	PAKAVAN	FARHAD		04 4	
461 05 2588	PICCOL	JOHN	M	04 4	
466 06 3476	QUINN	TICKY X	K	04 4	DROP
452 07 7517	PUCKETT	KEITH	S	05	
438 03 2600	RAHCAMER	MUSHMANN		04 3	
465 04 7480	QUACH	GARY	B	01 2	
466 52 3440	ROSS JR	GLYNDON	G	04 3	
466 08 3106	SAUER	PAUL	B	04 4	
455 15 3927	SAVAGE	KELLY	B	04 3	
528 33 7752	SEALANT	ANTHONY	B	04 4	DROP
535 92 3425	BAXTON	SABER	K	01 3	
478 80 0100	UI	QUI	B	04 4	
459 92 2358	WILLY	GARY	L	01 4	
TOTAL	26, ACTIVE	28, CREDIT HOURS	84		

INSTRUCTOR'S SIGNATURE *Ciling - Tran Paul*
 DATE *Feb 14, 77* TELEPHONE EXT. *742-3528*

marks.

LE 2246, References

Topic	Vine's Book	Smith's Book	
		2nd Edition	3rd Edition
Relay	3-4	541	616
FET		277-78	336
Load Line		Similar to Ex 9, p.297	Similar to Ex 5, p281
BJT	3-4,5	292-3	345-6
Load Line		p. 299 Ex 10	p. 349 Ex. 5
Transducers	3-5 to 3-15	p. 667-679	p. 722-733
Fabricating Integrated Circuits		p. 293-4	p. 348-351
Motors and Controls	Ch. 6	Ch. 18	Ch. 24-25
Op. Amps.	3-18-20	Ch. 20	Ch. 19

75.

Marhs

Texas Tech University

Registrar P.O. Box 4570 Lubbock, Texas 79409 Phone (806) 742-2201

April 1, 1977

Department Chairman and Faculty Member:

Attached are your Revised Class Rolls for the Spring 1977 semester.

PLEASE CHECK THIS ROLL IN CLASS.

- A. If Students are attending this class and their name does not appear on this roll, advise them to see their Academic Dean immediately.
- B. If a student's name is on your roll who is not attending your class, notify the student's Academic Dean that he is not attending. (Refer to General Catalog, Pages 56 and 57.)
- C. Students may not change courses or sections except by the official "Change in Registration" form initiated and approved by their Academic Dean.

This is the final check point for correcting all class rolls before producing the Final Grade Roll. We request that you check these rolls carefully, since it will be most difficult and time consuming to make additions to the Final Grade Roll. A student whose registration has not been cleared for a particular course and section, will not appear on the Final Grade Roll, thus causing a serious inconvenience to you, the student and the Dean's Office.

The Department Chairman is furnished two (2) copies of this class roll, one of which is forwarded to the professor. We do not want a copy of this class roll returned to the Registrar's Office. Departments and faculty are requested to use it for the sole purpose of correcting all discrepancies so the Final Grade Roll will be correct.

Students who registered but did not pay their registration fees are not shown on this roll.

Sincerely,

Don Wickard

Don Wickard
Associate Registrar

DW/gw

SPRING 1977 REVISED CLASS ROLL 590 (E E) 234 004 1 1

PAN OFING T (1) ELECTRONIC INSTRUMENTATION

494	70	8304	ABU-SARRIS	FAHMI	H	04	4		1
462	84	0851	ANTHONY JR	WILLIAM	P	04	9		2
480	92	8261	BOU-CHEBL	SABA	S	04	5		3
456	80	1932	CAGLE	BILLY	R	04	3		4
3 460	04	6744	CAVINESS	WYNDELL	R	04	6	W OR WF	5
585	16	6289	DAVIS	JEDIE	L	04	4		6
442	66	6757	DEHKERDI	SHAFROKH		04	4		7
454	08	9465	DUNN	TIMOTHY	M	04	4		8
366	72	3166	EL-SABAALY	BGUTROS	G	04	4		9
459	88	3465	HENDRIX	ROBERT	E	04	3	W OR WF	10
465	76	3151	HILL	WILLIAM	B	04	4		11
463	80	8812	HOLSEMBACK	FEECCRE	W	04	4		12
450	11	1764	LUNSFORD	JAY	L	04	6		13
465	11	7454	MOORE	KEITH	W	04	3		14
466	50	9616	MOORE	MICHAEL	L	04	6		15
463	13	7394	NAPIER	HARRIS	G	04	4		16
119	50	5642	PAKPAVAN	FAPEAD		04	4		17
461	94	2855	PIERCE	JOHN	W	04	3		18

Approved Business Forms, Inc. 8

SPRING 1977 REVISED CLASS ROLL 590 (E F) 234 004 2 1

PAN CHING T (1) ELECTRONIC INSTRUMENTATION

3	466	06	8496	PRATHER	RICKY	K	04 3	W OP MF	1
	452	02	7517	BUCKETT	KENT	S	04 4		2
	438	08	2600	RAHMANIFAR	HOSHMAND		04 3		3
	465	04	7489	ROACH	GARY	B	04 2		4
	466	92	3440	ROSS JR	GLYNDCN	G	04 3		5
	466	08	3306	SAUER	PAUL	W	04 4		6
	454	15	4927	SAVAGE	KELLY	B	04 3		7
2	328	38	5752	SCIALO	ANTHCNY	M	04 4	WITHDREW	8
	585	92	5429	THAXTON	SABER	K	04 3		9
	478	80	0190	TU	GUI	H	04 4		10
	459	92	2358	WHITE	GARY	L	04 4		11

TOTAL STUDENTS 29, ACTIVE STUDENTS 25

Moore Business Forms, Inc. 5

GARY WHITE ✓	
Paul Sauer ✓	797 - 2006
SABA BOU-CHEBL ✓	742-4550
o Rick Prather ✓	744-1928
Rob Hendrix ✓	744-1928
JOHN PIERCE ✓	747 - 3901
KEITH MOORE ✓	744-5218
MIKE MOORE ✓	795-5659
BUD HILL ✓	793-0985
Wyndell Caviness ✓	797-0187
Bill Cagle ✓	797-5474
KELLY SAVAGE ✓	797-3142
BILL ANTHONY ✓	762-5756
Wendell	
Zed Zolombach ✓	799-7797
Yong Smith ✓	799-7687
o QUI TU ✓	762-1235
GARY ROACH ✓	765-5411
Fahmi Abu-Sarris ✓	747-7675
Farhad Pakravan ✓	765-5998
o EL-SABAALY, BOUTROS ✓	744-6780
TIM DJINN or	799-1519
DEHKORDI, SHAHROKH ✓	742-4066
QAMIR HOSSEIN ^{SHAHAD} Rahmanifar ✓	747-3530
Glyndon Ross ✓	762-1478
Saber Thaxton ✓	765-9128
Jodie Davis ✓	744-3032
o KENT S PUCKETT ✓	742-5067
Buddy Napier ✓	744-2981
LEA LUNSFORD ✓	747-5865

MEMORANDUM

Office of the Dean of Engineering
Texas Tech University
Lubbock, Texas 79409

TO: PROFESSOR (SEE BELOW) DATE: APRIL 18, 1977

SUBJECT: ABSENCE OF STUDENT

FROM: ROBERT L. NEWELL, ASSOCIATE DEAN OF ENGINEERING


John William Pierce, Social Security No. 461-94-2555, is enrolled in one of the classes taught by you, as noted below.

We have just learned from a telephone conversation with his father, that Mr. Pierce is in the hospital under doctor's care (effective April 11, 1977), and will remain there for an extended period of time and will not be able to return to school this semester.

Because Mr. Pierce is a good student, and because of this particular situation, we are requesting that a grade of Incomplete (I), be given the student. We understand that he will be contacting all his instructors after May 15th.

Thank you for your attention to this matter.

Mr. Tom Sawyer	for	BA 3391-002
Mr. Sam Boyd	for	BA 3391-PPP
Mr. Bob Marks	for	EE 234-004
Dr. Charles Burford	for	IE 3334-001
Mr. Robert E. Martin	for	ME 3342-002-B

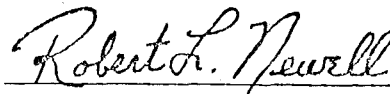

Robert L. Newell

RLN:ad

CC: Mr. William C. Pierce
9714 Lanward Drive
Dallas, Texas 75238


II. SEMICONDUCTOR DIODES

A. CONDUCTION IN SOLIDS

1. COVALENT SEMICONDUCTORS: GERMANIUM & SILICON

VALLENCE OF FOUR

BONDING: COVALENT BONDS

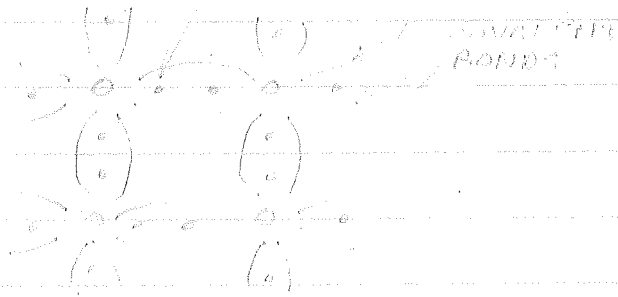

CONDUCTION IN A SEMICONDUCTOR IS DONE

BY ELECTRON AND HOLE CURRENT.

HOLES ARE VACANCY LEFT BY AN ELECTRON.

WE TREAT A HOLE LIKE AN ELECTRON.

WITH A POSITIVE CHARGE.

IN A PURE SEMICONDUCTOR

$$n = p$$

n = ELECTRON CONCENTRATION

p = HOLE CONCENTRATION

$n = p = n_i$

n_i = INTRINSIC CONCENTRATION

$$n_i = 1.5 \times 10^{16} / m^3$$

$$n_i = 2.4 \times 10^{17} / m^3$$




2. DOPED SEMICONDUCTOR

ADDITIONAL "IMPURITY" ATOMS ARE ADDED TO THE SEMICONDUCTOR TO PRODUCE EXTRA FREE HOLES OR ELECTRONS.

N-DOPED SEMICONDUCTORS

IMPURITY IS A PENTAVALENT ATOM (DONOR) $\begin{matrix} \cdot & \cdot \\ \cdot & \cdot \end{matrix}$
 $\begin{matrix} Sb & P & As \\ \text{ANTIMONY, PHOSPHORUS, ARSENIC} \end{matrix}$


BONDING:

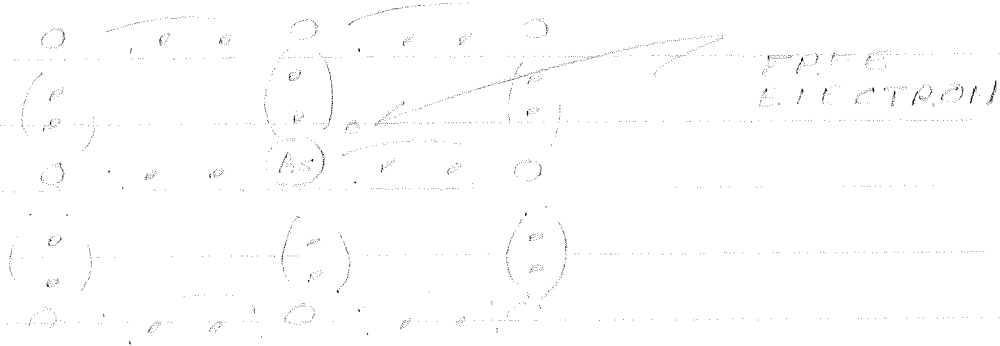

P-DOPED SEMICONDUCTORS

IMPURITY IS A TRIVALENT ATOM (ACCEPTOR) $\begin{matrix} \cdot \\ \cdot \\ \cdot \end{matrix}$
 $\begin{matrix} Al & B & Ga & In \\ \text{(ALUMINUM, BORON, GALLIUM, INDIUM)} \end{matrix}$

BONDING

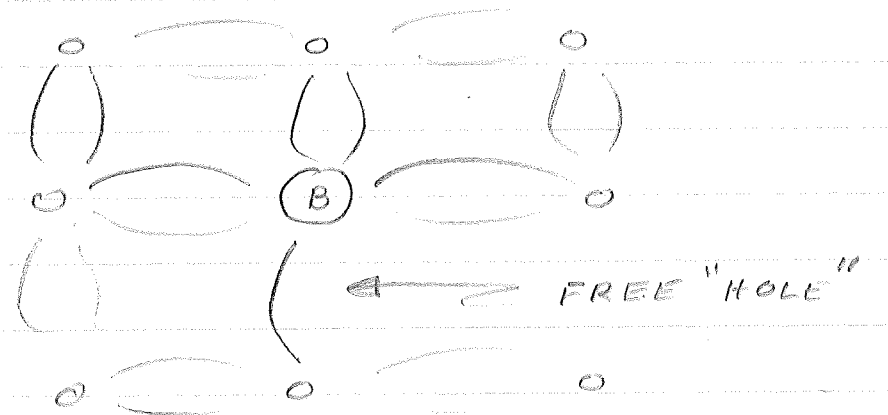

B. CONDUCTION

IMPURITIES INCREASE A SEMICONDUCTOR'S CONDUCTANCE.

a. MASS-ACTION LAW

$$R = r n p$$

R = RECOMBINATION RATE $\left(\frac{e-h \text{ PAIRS}}{s-m^3} \right)$

n = ELECTRON CONCENTRATION $\left(\frac{\#}{m^3} \right)$

p = HOLE " $\left(\frac{\#}{m^3} \right)$

r = PROPORTIONALITY CONSTANT

R MEASURES THE RATE AT WHICH ELECTRON-HOLE PAIRS ARE RECOMBINING. - IT SAYS: RATE OF REC. IN PRO. TO # OF REACTING ELEMENTS.

REGENERATION, g , MEASURES THE RATE AT WHICH ELECTRON HOLE PAIRS ARE BEING FORMED.


IN A PURE SEMICONDUCTOR, $n_i = p_i$

$$\Rightarrow R = g = r n_i^2$$

THIS IS ALSO ROUGHLY TRUE IN A DOPED SEMICONDUCTOR SINCE

IMPURITY ATOMS \ll # SEMICONDUCTOR ATOMS

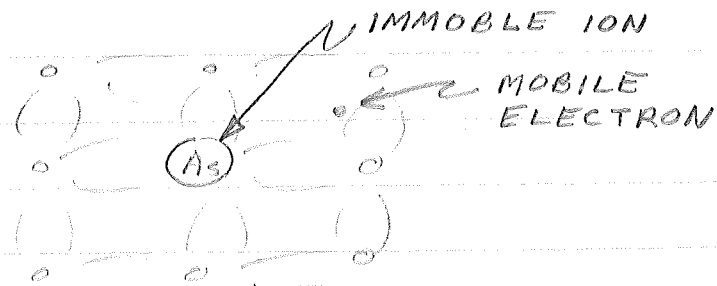b. A DOPED SEMICONDUCTOR IS, OVERALL,
ELECTRICALLY NEUTRAL



DEFINE

$N_d = \#$ OF DONOR IONS (+)

$N_a = \#$ OF ACCEPTOR ION (-)

IN GENERAL $\Rightarrow p + N_d = n + N_a$

FOR n DOPED SEMICOND., $N_a = 0$ AND

$$n_n = N_d + p_n$$

IN PRACTICAL CASES, $N_d \gg p_n$ AND

$$n_n \approx N_d \quad (1)$$

THE HOLE DENSITY IS GIVEN BY

$$n_n p_n = n_i^2$$

$$p_n = \frac{n_i^2}{n_n} \approx \frac{n_i^2}{N_d} \quad (2)$$


HOMEWORK #1 DERIVE THE APPROPRIATE

EQUATIONS FOR p_p AND n_p

IN A p DOPED SEMICONDUCTOR.

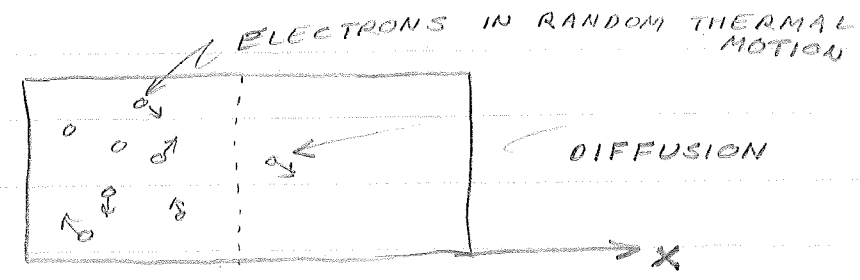4. DIFFUSION (LIKE PERFUME, SMOKE IN A ROOM)

- A STATISTICAL REDISTRIBUTION
- OCCURS IN SEMI CONDUCTORS WHEN THERE IS AN ABRUPT CHANGE IN DOPING FROM ONE AREA TO ANOTHER



J_n = CURRENT DENSITY FOR ELECTRONS

$$= e D_n \frac{dn}{dx}$$


D_n = ELECTRON DIFFUSION CONSTANT

ALSO, FOR HOLES

$$J_p = -e D_p \frac{dp}{dx}$$

B. JUNCTION DIODES

1. PN JUNCTION BEHAVIOR

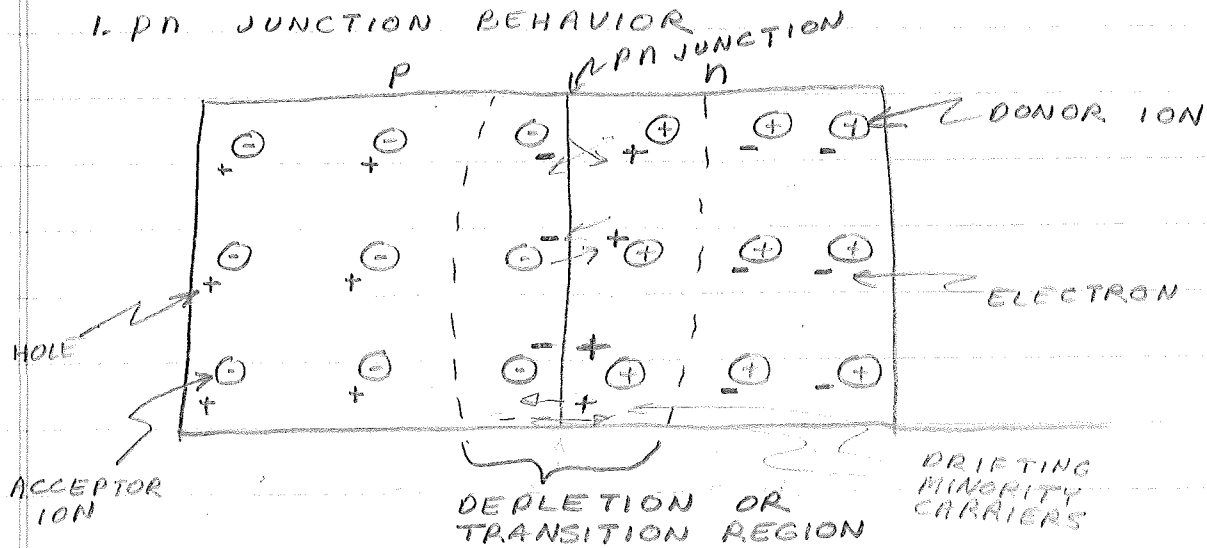

MAJORITY CARRIERS - ELECTRONS (HOLES)

IN THE n (p) REGION.

MINORITY CARRIERS - ELECTRONS (HOLES)

IN THE p (n) REGION (DUE TO THERMAL AGITATION)


OUR CONDUCTION MECHANISMS ARE

1. DIFFUSION

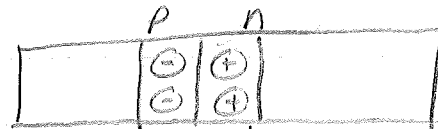2. DRIFT - UNDER E FIELD, MINORITY CARRIERS

TEND TO DRIFT ACROSS JUNCTION

WITH NO APPLIED VOLTAGE, THERE IS STILL A POTENTIAL DIFFERENCE ACROSS DIODE



$\rho =$ CHARGE DENSITY




$$E = \text{ELECTRIC FIELD} = \frac{1}{\epsilon} \int \rho dx$$

THE "POTENTIAL HILL" TENDS TO OPPOSE
 MAJORITY CARRIER DIFFUSION AND
 ENCOURAGE MINORITY CARRIER
 DRIFT.

2. BIASED DIODES

0. FORWARD BIAS (CONDUCTION)

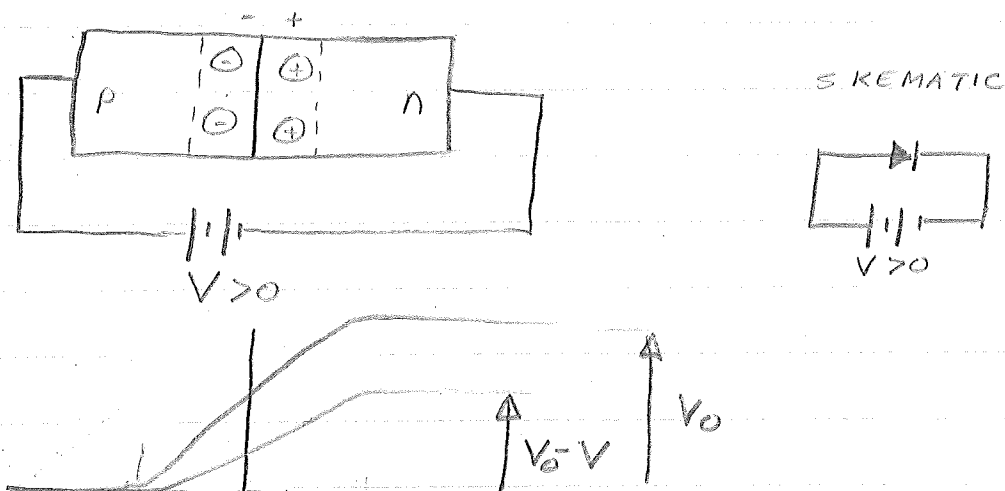

- THE HILL IS REDUCED.

- MAJORITY CARRIERS ARE NOW ENCOURAGED


TO FLOW WHERE THEY ARE MINORITY

CARRIERS. HENCE, CONDUCTION: DIODE
 ACTS ESSENTIALLY AS SHORT CIRCUIT.


- CURRENT (POSITIVE CHARGE) FLOWS

FROM P TO N.

b. REVERSE BIASED DIODES

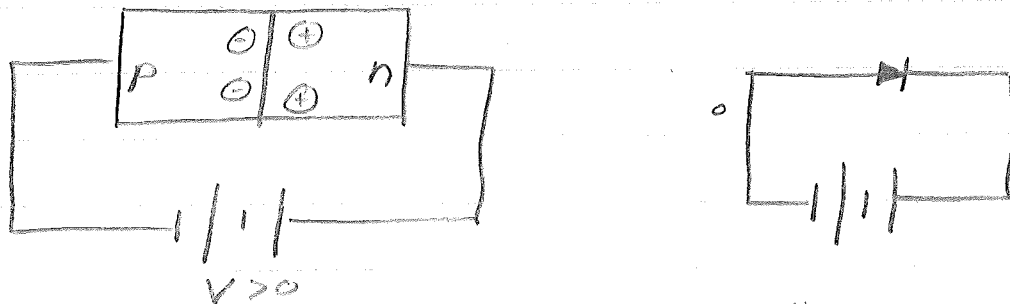

HERE, THE HILL IS MADE "STEEPER"

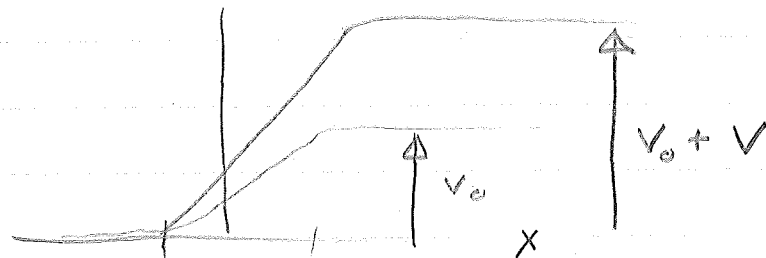


-THE NET DIFFUSION OF MAJORITY CARRIERS
IS REDUCED TO PRACTICALLY ZERO.
⇒ NO CONDUCTION AND DIODE ACTS AS
AN OPEN CIRCUIT.


SATURATION CURRENT: A REVERSE (N TO P REGION)
CURRENT DUE
TO MINORITY CARRIERS, WHICH IS
INSENSITIVE TO APPLIED BIAS AND
WHICH IDEALLY IS ZERO.

C. DIODE MODELS

V-I CURVES OF DIODE

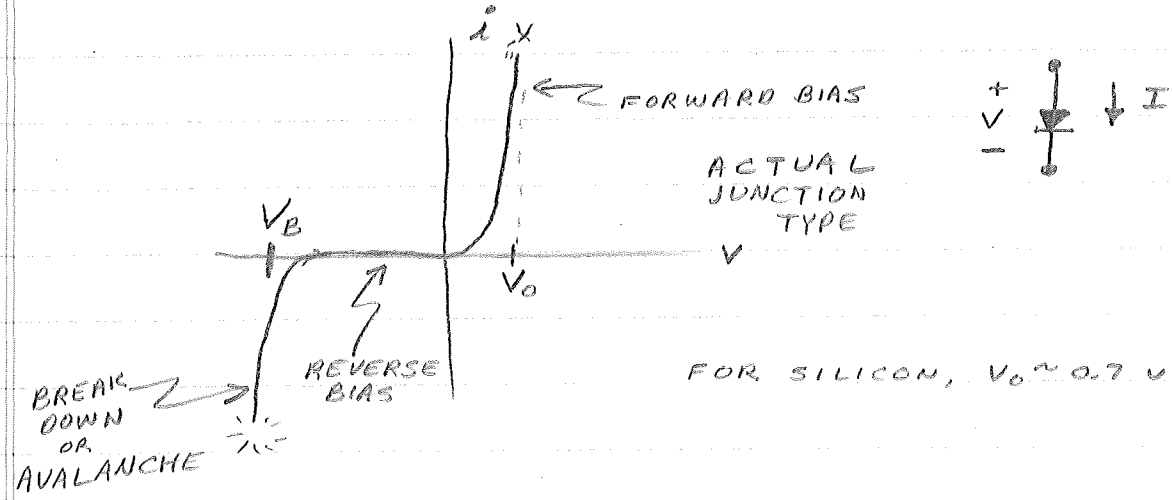


a. IDEAL JUNCTION DIODE

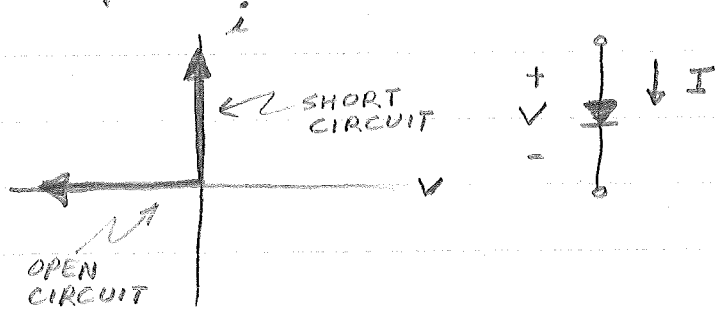

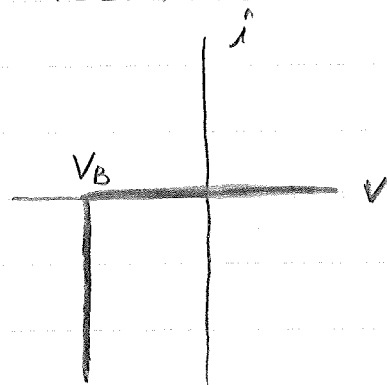b. BREAKDOWN OR ZENER DIODE

BREAKDOWN OCCURS WHEN JUNCTION POTENTIAL IS HIGH ENOUGH TO BREAK e's FROM COVALENT BONDS.



c. TUNNEL DIODES - DISPLAY TUNNELING

EFFECT PREDICTED BY QUANTUM MECHANICS.

CAN ACHIEVE NEGATIVE RESISTANCE

OSCILLATION

d. SCHOTTKY DIODE: USES METAL

SEMICONDUCTOR INTERFACE. VERY

FAST SWITCHING.

e. LIGHT-EMITTING DIODES

ON $e-h$ RECOMBINATION, PHOTON IS

EMITTED IN CERTAIN SEMICONDUCTORS.

EE 234 SEC 4 SPRING, 1977

"ELECTRONICS, INSTRUMENTATION

TEXT: AUTOMATION OF PETROLEUM AND CHEMICAL

SYSTEMS by VINES, GUSTAFSON, & PASSMORE

GRADING:

QUIZES: 40%

HOMEWORK: 10%

LAB: 20%

FINAL: 30%

(STRICT CURVE)

INSTRUCTOR: BOB MARKS

ROOM EE 216

OFFICE HRS: 2:30-3:30 MWF


CLASS POLICIES

1. ALL GRADES FINAL

2. NO MAKE UP TESTS


THE IDEAL DIODE

SKEMATIC:

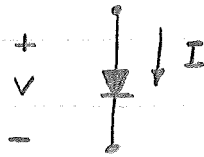

IDEAL
THE DIODE IS A NONLINEAR LUMPED CIRCUIT
ELEMENT THAT EITHER ACTS AS A
SHORT CIRCUIT OR AN OPEN CIRCUIT.

V-I CURVE

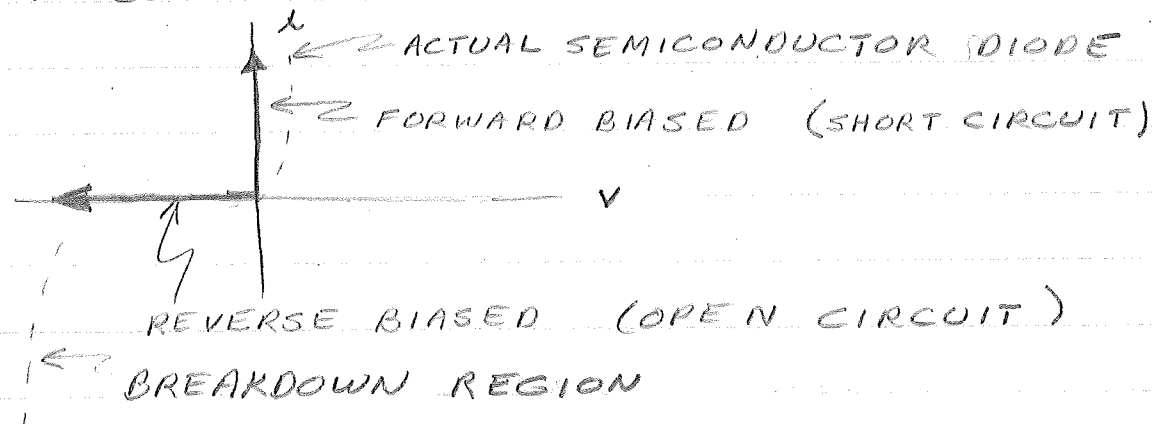



NOTE ON THEORY APPLICATION:

- (a) LINEAR THEORY: SUPERPOSITION, THEVININ'S
‡ NORTON'S THEOREM, ‡ IMPEDANCE TO NOT
APPLY (IN THE GENERAL SENSE) TO NONLINEAR
CIRCUITS
- (b) GENERAL THEORY: KIRCHOFF'S LOOP AND NODE
LAWS


RECTIFIER - A CIRCUIT USED TO OBTAIN UNIDIRECTIONAL CURRENT (OR VOLTAGE)

(p. 315 SMITH)

1. HALF WAVE RECTIFIER

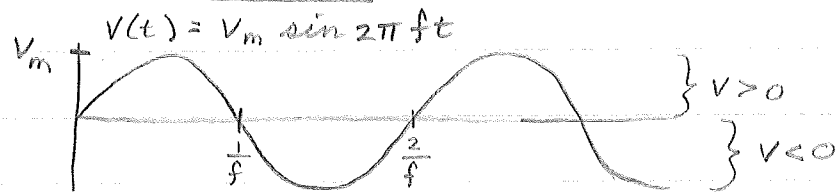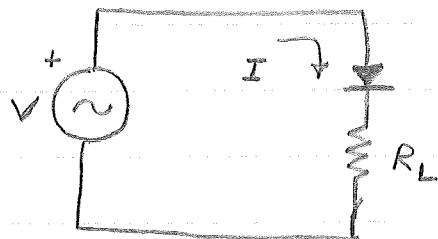


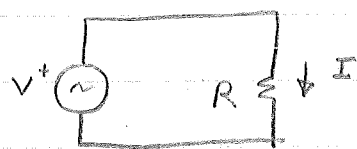WHEN $V > 0$, THE DIODE IS FORWARD BIASED AND ACTS LIKE A SHORT CIRCUIT:




THUS, $I = \frac{V}{R}$ FOR $V > 0$

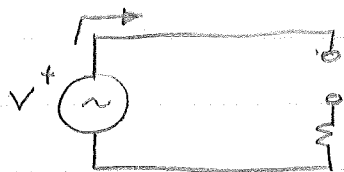
WHEN $V < 0$, THE DIODE IS REVERSE BIASED AND ACTS LIKE AN OPEN CIRCUIT:




THUS, $I = 0$ FOR $V < 0$

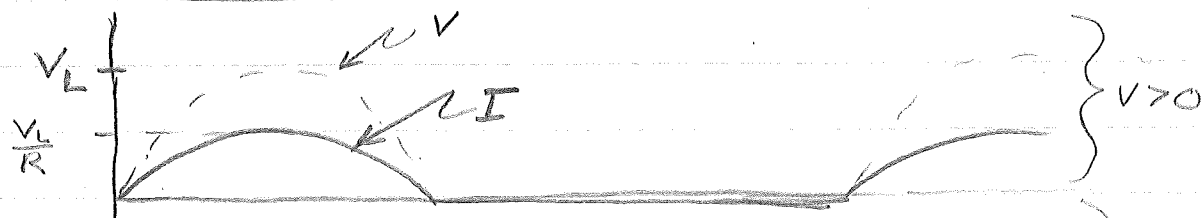


(b) PHASE INVERTER FULL WAVE RECTIFIER

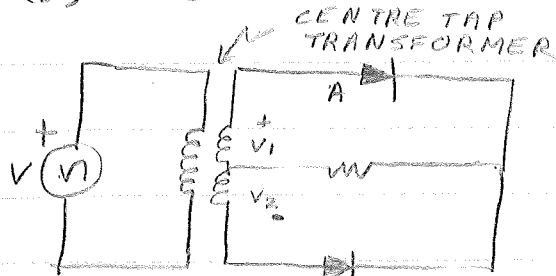

ASSUME $V_1 = -V_2 = \frac{V}{2}$

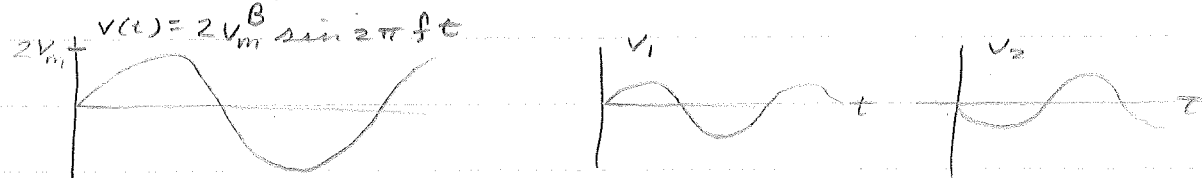


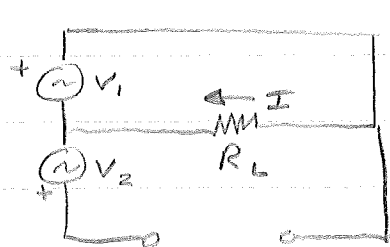WHEN $V_1 > 0$ ($\Rightarrow V_2 < 0$), DIODE A IS FORWARD BIASED AND B IS REVERSE BIASED:




$I = \frac{V_1}{R_L} ; V_1 > 0$
OR $= \frac{V}{2R_L} ; V > 0$

FOR $V_1 < 0$ ($\Rightarrow V_2 > 0$)

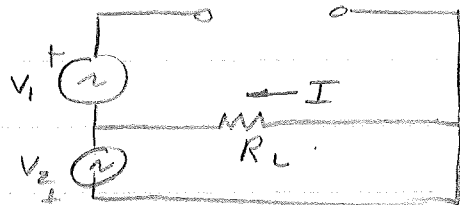

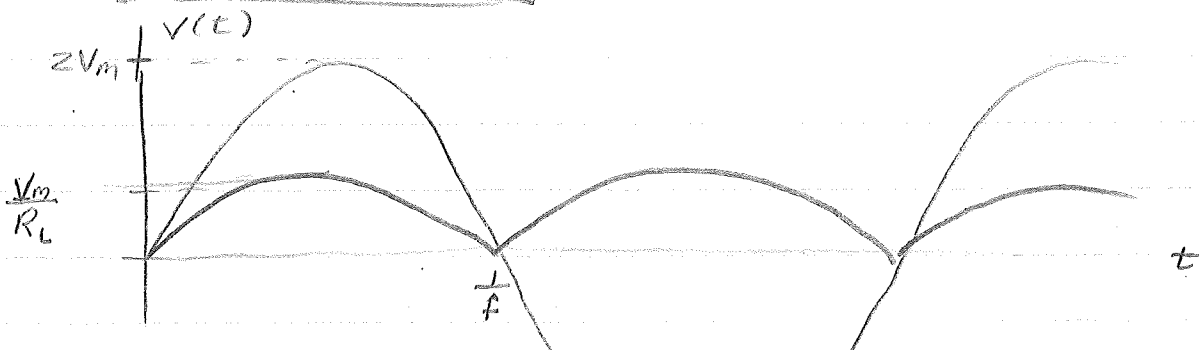$I = \frac{V_2}{R_L} ; V_2 > 0$
OR $= \frac{-V_1}{R_L} ; V_1 < 0$



RIPPLE FACTOR: MEASURE OF THE "BUMPINESS"
OF A RECTIFIED WAVEFORM

$$r = \frac{I_{ac}}{I_{dc}} = \frac{V_{ac}}{V_{dc}} = \frac{\text{RMS VALUE OF A.C. COMPONENT}}{\text{D.C. COMPONENT}}$$

LET $V(t)$ BE RECTIFIED SIGNAL, THEN

$$V_{ac}^2 = V_{RMS}^2 - V_{DC}^2$$

WHERE

$$(a) V_{RMS} = V_{EFF} = \left[\frac{1}{T} \int_T V^2(t) dt \right]^{\frac{1}{2}}$$


$$(b) V_{DC} = V_{AVE} = \frac{1}{T} \int_T V(t) dt$$

SINCE $V_{ac} = \sqrt{V_{RMS}^2 - V_{DC}^2}$


THEN

$$r = \frac{\sqrt{V_{RMS}^2 - V_{DC}^2}}{V_{DC}} = \left[\left(\frac{I_{RMS}}{I_{DC}} \right)^2 - 1 \right]^{\frac{1}{2}}$$

A LOW RIPPLE FACTOR IS GOOD

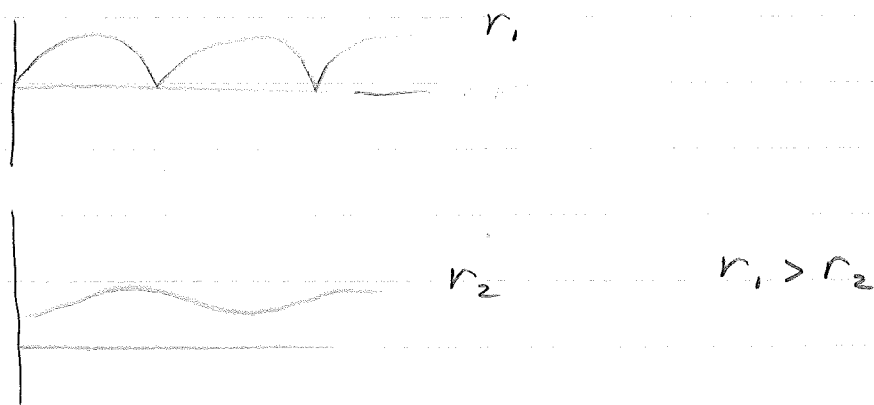

CAPACITIVE FILTER (DECREASES r)

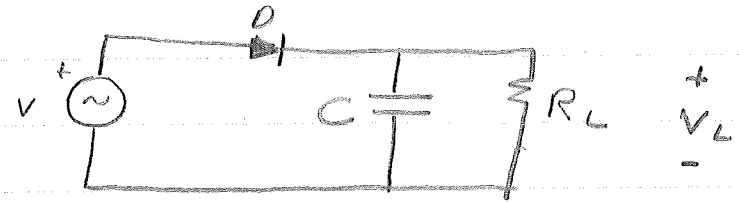


$$V = V_m \sin 2\pi f t$$


[WITHOUT CAPACITOR \Rightarrow $\frac{1}{2}$ WAVE RECTIFIER.]



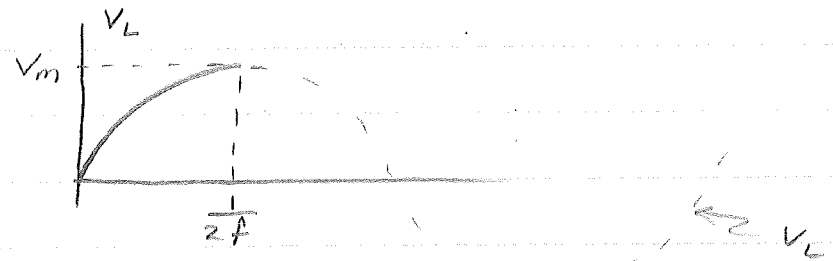
D WILL CONDUCT ^{ONLY} WHEN $V \geq V_L$. UNTIL, V REACHES ITS FIRST PEAK, $V_L = V$ (TRANSIENT)



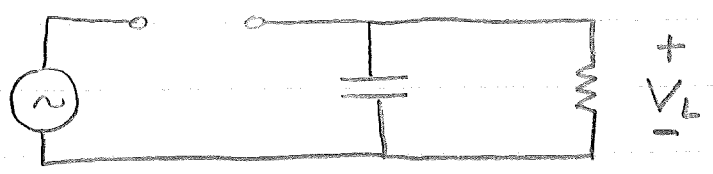WHEN V_L STARTS TO GO DOWN AGAIN, D WILL OPEN



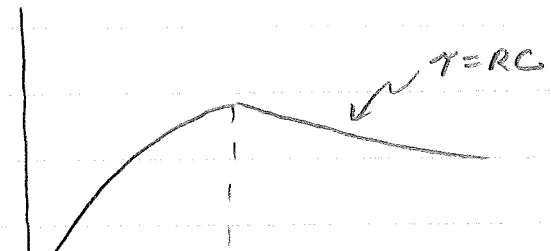THE VOLTAGE, V_m IN C WILL EXPONENTIALLY DRAIN THRU R_L WITH $\tau = RC$



HOMEWORK # 1 (DUE 2/1/76)

1. (a) FOR THE FOLLOWING CIRCUIT, FIND $V_d^{(c)}$ GIVEN


THAT $V_s(t) = V_m \sin \omega t$. SKETCH YOUR

RESULT AND EXPLAIN YOUR REASONING. ^{ASSUME R_s} _{IN} ~~NEGLECT~~

(b) WHAT IS THE RIPPLE FACTOR OF $V_d(t)$

(c) EXPLAIN WHY THE CIRCUIT IS CALLED A



"DIODE CLAMPER"

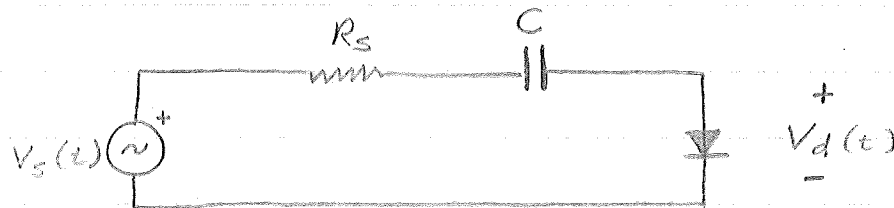


2. FOR THE HALF WAVE RECTIFIER WITH CAPACITIVE FILTER, SKETCH THE SOURCE VOLTAGE, DIODE VOLTAGE AND DIODE CURRENT ON THE SAME GRAPH. DOCUMENT YOUR RESULTS

III. FIELD EFFECT TRANSISTORS.



A. JFET (JUNCTION GATE FET'S)

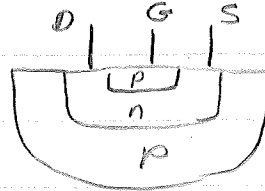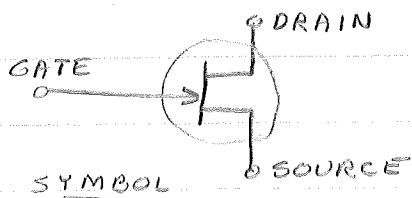


V-i CURVE

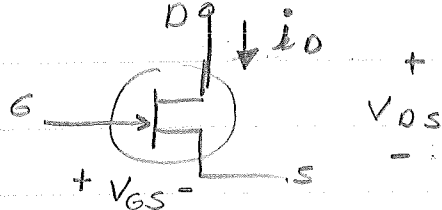

RECALL DIODE

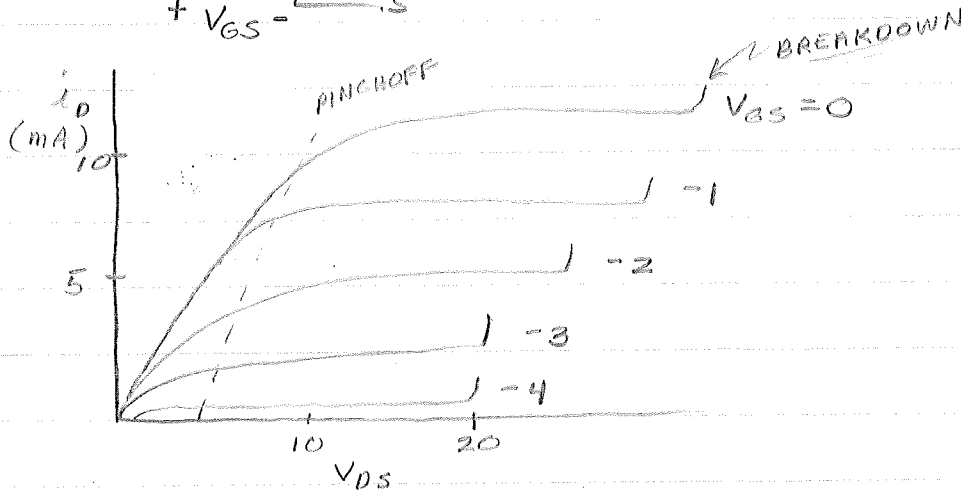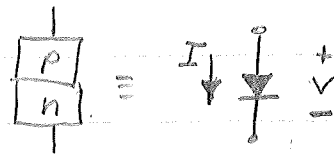

WHAT HAPPENS:

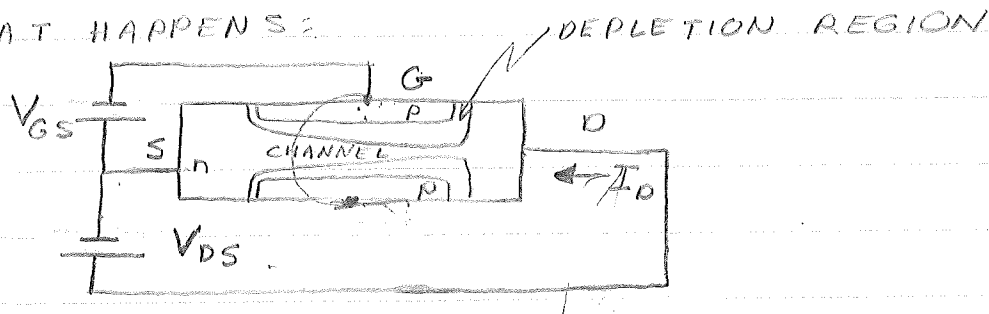

I_D (FROM S TO D) FOR A GIVEN V_{DS} , DEPENDS ON THE CHANNEL DIMENSION. IF BOTH p-n JUNCTIONS ARE REVERSED BIASED, THE CHANNEL GETS SMALLER. PINCHOFF OCCURS @ ABOUT $5V = V_{GS}$

PART I

ANSWER EACH OF THE FOLLOWING QUESTIONS WITH A "T" OR AN "F". AMBIGUOUS MARKS, LIKE "F" WILL NOT BE GRADED. DO NOT GUESS. THERE WILL BE A PENALTY FOR WRONG ANSWERS. IF YOU DO NOT KNOW AN ANSWER, IT IS BEST TO LEAVE THE SPACE BLANK. (NO ANSWER IS "2, WRONG ANSWER IS "3, CORRECT ANSWER IS "4).

1. A DIODE IS A NONLINEAR DEVICE.
2. THEVININ'S THEOREM CANNOT BE APPLIED TO DIODE TYPE CIRCUIT ELEMENTS.
3. KIRCHHOFF'S VOLTAGE AND CURRENT LAWS CANNOT BE APPLIED TO A DIODE-TYPE CIRCUIT.
4. A REVERSE BIASED DIODE CONDUCTS.
5. A RECTIFIER CAN TAKE A PERIODIC WAVEFORM OF ZERO AVERAGE VALUE & RECTIFY IT TO GIVE ANOTHER PERIODIC WAVEFORM WITH NON-ZERO AVERAGE POWER.
6. RECTIFIER TYPES INCLUDE FULL AND HALF WAVE RECTIFIERS.
7. A LOW RIPPLE FACTOR DENOTES A MORE "BUMPY" WAVEFORM.
8. CAPACITIVE FILTERS ARE USED TO INCREASE THE RIPPLE FACTOR OF A RECTIFIED WAVEFORM.
9. THE FET IS MODULATED BY CONTROLLING THE SIZE OF THE CONDUCTING CHANNEL.
10. DE MOSFET MEANS "DEPLETION EFFECT METAL OXIDE SEMICONDUCTOR FIELD EFFECT TRANSISTOR".
11. IN NORMAL BJT USE, THE EMITTER JUNCTION IS REVERSE BIASED.
12. THE LAPLACE TRANSFORM IS A LINEAR OPERATION.
13. ALL LINEAR NON-CAUSAL SYSTEMS ARE LINEAR.
14. ALL KNOWN SYSTEMS ARE CAUSAL IN THE PHYSICAL WORLD.
15. A LINEAR TIME-INVARIANT SYSTEM'S TRANSFER FUNCTION IS DEPENDENT ON THE SYSTEM INPUT.
16. A BANDLIMITED SIGNAL HAS INFINITE BANDWIDTH.
17. A SIGNAL OF BANDWIDTH 200HZ MUST BE SAMPLED AT LEAST AT A RATE OF 400 SAMPLES PER SECOND IF WE WISH TO LOSE NO INFORMATION.
18. A FOURIER SERIES DECOMPOSES A PERIODIC WAVEFORM INTO ITS COMPONENT HARMONICS.
19. "MTBF" DENOTES "MEDIAN TIME BETWEEN FAILURES".
20. THE TOTAL MTBF OF A SYSTEM COMPOSED OF A NUMBER OF ELEMENTS CONNECTED IN SERIES IS SIMPLY THE SUM OF THE ELEMENTS' MTBF'S.
21. THE RECIPROCAL OF MTBF IS FAILURE RATE.
22. THE BATHUB CURVE IS A PLOT OF FAILURE RATE VS. TIME.

- 1. MAINTAINABILITY IS NOT A PROBABALISTIC MEASURE
- 25. AVAILABILITY IS THE RATIO BETWEEN MTBF & MTTR
- 26. MTTR IS A MEASURE OF MAINTAINABILITY
- 27. QUIESCENCE DENOTES THE NO SIGNAL OPERATING POINT OF A TRANSISTOR CIRCUIT
- 28. KIRCHHOFF'S LAWS CANNOT BE USED WHEN ANALYZING NONLINEAR TRANSISTOR CIRCUITS
- 29. THE PARAMETERS OF A BJT ARE RELATIVELY INSENSITIVE TO AMBIENT TEMPERATURE
- 30. BJT'S CAN EITHER BE npn OR pnp
- 31. A CRUDE BJT CAN BE MADE FROM TWO DIODES
- 32. WHEATSTONE BRIDGES ARE USED FOR MEASURING RESISTANCES TO HI PERCISION
- 33. A MAXWELL BRIDGE IS CAPABLE OF MEASURING TWO UNKNOWN COMPONENTS IN A SINGLE BALANCE OF THE BRIDGE
- 34. AN IDEAL OP AMP HAS AN INPUT IMPEDANCE OF ∞
- 35. ANALOG COMPUTERS IN GENERAL ARE MORE EXACT THAN DIGITAL COMPUTERS
- 6. OP AMPS CAN BE USED TO SUM VOLTAGES AND PERFORM VOLTAGE WAVEFORM INTEGRATION
- 7. OP AMPS ARE GENERALLY SEMICONDUCTOR DEVICES
- 8. AN UNMODULATED AM CARRIER IS SIMPLY A UNIFORM SQUARE WAVE
- 1. THE AMPLITUDE ENVELOPE OF A MODULATED FM CARRIER VARIES WITH THE APPLIED SIGNAL
- 2. WHEN WE SELECT AN AM OR FM STATION ON OUR RADIOS, WE ARE SIMPLY SELECTING THE CARRIER FREQUENCY OF THAT STATION
- 1. PAM IS THE DIGITAL EQUIVALENT OF AM
- 1. PAM DENOTES "PHASE AMPLITUDE MODULATION"
- 2. PDM DENOTES "PHASE DURATION MODULATION"
- 1. MULTIPLEXING MEANS THE ACT OF SENDING TWO OR MORE SIGNALS OVER THE SAME CHANNEL
- 1. PPM DENOTES "PULSE POSITION MODULATION"
- 1. ONLY ANALOG SIGNALS CAN BE MULTIPLEXED
- 1. AN "APRIORI" PROBABILITY MEANS A "BEFOREHAND" PROBABILITY
- 1. THE PHRASE "I WILL BE HERE OR THERE" CONTAINS AN EXCLUSIVE OR
- 1. EVENTS "A" AND "A" PLACED AS INPUTS TO AN (INCLUSIVE) OR GATE WILL ALWAYS GIVE A LOGIC ZERO AS OUTPUT

50. WITH A SINUSOID INPUT, THE OUTPUT OF A DIODE CLAMPER CIRCUIT HAS A ZERO O-C VALUE.
51. THE EXISTENCE OF A FEEDBACK CIRCUIT ASSURES THAT THE OUTPUT WILL NOT OSCILLATE.
52. LAPLACE TRANSFORMS CAN BE USED TO REDUCE THE CONVOLUTION OPERATION TO MULTIPLICATION.
53. THE FREQUENCY RESPONSE OF A LINEAR TIME INVARIANT SYSTEM CAN BE OBTAINED FROM THE SYSTEM'S TRANSFER FUNCTION.
54. THE BALANCING POINT OF ALL IMPEDANCE BRIDGES IS INDEPENDENT OF THE SOURCE FREQUENCY.
55. IN ORDER TO DOUBLE THE O-B GAIN OF AN AMP, WE MUST MULTIPLY THE ACTUAL AMP GAIN BY 20.
56. A BALANCED MAXWELL BRIDGE IS INDEPENDENT OF BOTH THE SOURCE FREQUENCY AND AMPLITUDE.
57. ALL IMPEDANCE BRIDGES CAN BE BALANCED.
58. A POSITIVE REACTANCE IS AN INDUCTIVE REACTANCE.
59. A GAIN OF 1 IS THE SAME THING AS A 0-B GAIN OF ZERO.
60. AN EIGHT-WAY LIGHT SWITCH CANNOT BE IMPLEMENTED USING ANY KNOWN TECHNIQUE.
61. AN EVEN ONES PARITY CODE IS AN ERROR DETECTION CODE AND NOT A CORRECTION CODE.
62. A HAMMING CODE IS AN ERROR CORRECTION CODE.
63. A HALF ADDER PERFORMS BINARY ADDITION AND DIVIDES THE RESULT BY TWO (IN BINARY).
64. TWO SWITCHES IN PARALLEL CAN BE USED AS AN AND GATE.
65. IF MASS IS TAKEN AS THE MECHANICAL DUAL OF CAPACITANCE, THEN COMPLIANCE IS THE MECHANICAL DUAL OF INDUCTANCE.
66. IF THE VELOCITY OF A CHARGE MOVING IN A UNIFORM MAGNETIC (B) FIELD IS PARALLEL TO THAT FIELD, THERE IS NO RESULTING FORCE ON THE CHARGE.
67. THERE IS FORCE ON A CURRENT CARRYING WIRE IN A B FIELD.
68. HAMMING, THE ORIGINATOR OF THE HAMMING CODE, ALSO ORIGINATED HAMMING EGGS.
69. A BIASED TRANSISTOR IS A BIGOTED TRANSISTOR.
70. AN ELECTROMAGNET PRODUCES A B FIELD.
71. THE FORCE RESULTING FROM MOTION OF A CHARGE IN A B FIELD IS PERPENDICULAR TO THE PLANE DEFINED BY THE VELOCITY DIRECTION AND THE UNIFORM B FIELD DIRECTION.
72. ONE CAN MAKE A MOTOR BY APPROPRIATELY USING THE PROPERTIES OF A MAGNETIC FIELD. SUCH IS NOT THE CASE FOR AN ELECTRIC FIELD.
73. IN A'ALSONVAL MOVEMENT, THE RESULTING TORQUE ON THE NEEDLE IS PROPORTIONAL TO THE APPLIED INDUCTANCE.

IF WE PASS A SQUARE WAVE OF FREQUENCY SOME THRU
A LOW PASS FILTER THAT ONLY PASSES FREQUENCIES
UP TO 75KHZ, OUR OUTPUT WILL BE A SINUSOID
RIDING ON A D-C BIAS TERM.
FOR THE ABOVE, IF THE CUT OFF IS AT 25KHZ, WE WILL
HAVE ONLY THE D-C TERM IN THE OUTPUT.
THE FOURIER SERIES OF THE SIGNAL $V(t) = 4 \text{ VOLTS MAX}$
ONLY WAY TO COMBAT CHANNEL NOISE IS TO CHANGE ALL
ONE'S TO ZERO'S IN OUR CODE.
IF A SIGNAL IS UNDERSAMPLED, THEN, ACCORDING TO THE
SAMPLING THEOREM, HIGH FREQUENCIES ARE DISTORTED.
ONE WAY TO INCREASE RELIABILITY IS REDUNDANCY.
CHANNEL NOISE IS A PRODUCT OF NATURE THE EFFECTS
OF WHICH CANNOT BE REDUCED BY MAN'S CLEVERNESS.
ALL TRANSISTORS ARE FET'S.
ALL FET'S ARE TRANSISTORS.
AN INDUCTOR IS A DIFFICULT COMPONENT TO INCLUDE
ON AN INTEGRATED CIRCUIT CHIP.
WHEN WE MODEL A MECHANICAL CIRCUIT, LAPLACE TRANS-
FORMS CANNOT BE USED IN THE SOLUTION.
A DIODE IS A TIME-VARIANT ELECTRONIC COMPONENT.
A SMOKE DETECTOR IS A TIME-VARIANT SYSTEM.
A HANNING CODE CAN DETECT AN ERROR IN A PARITY BIT.
LOGIC CIRCUITS CAN BE DESIGNED DIRECTLY FROM
TRUTH TABLE.
TWO TYPES OF "OR" GATES ARE IRON AND COPPER.
WE MAY FABRICATE A "NOT" GATE BY CONNECTING THE
TWO INPUT TERMINALS OF AN "AND" GATE.
NEEDING 100% MODULATION IN AM CAUSES DISTORTION.
IN IDEAL DIODE IS EITHER A SHORT OR AN OPEN CIRCUIT.
ALTHOUGH NECESSARY FOR OPERATION, BRUSHES ON A
D-C MACHINE DO NOT CONDUCT ANY CURRENT.
ONE WAY TO INCREASE THE FREQUENCY ON AN INDUCTION
MACHINE IS TO INCREASE THE NUMBER OF POLES.
D/A CONVERTER CONVERTS A DIGITAL INPUT INTO
AN AM MODULATED SIGNAL.
SLIP RINGS ROTATE.
SPLIT SLIP RINGS CAN RECTIFY.
SLIPPING SPLIT SLIP RINGS SLURP SLOP ON SPLITTING SLIPS.
MOTOR FLOATS ON OIL.
THIS IS THE LAST TRUE-FALSE QUESTION ON THIS TEST.
CREDIT:
THE ANSWER TO THIS QUESTION IS FALSE.

PART II

A SINGLE PROTOTYPE MACHINE IS PUT ON TEST FOR 100 HRS. IN THAT TIME, THERE WERE 2 FAILURES. THE TIMES TO REPAIR THE MACHINE FROM THESE TWO FAILURES WERE 60 HRS AND 40 HRS. WE ASSUME THAT, WHILE OPERATING, THE MACHINE EXPERIENCES A CONSTAN Y FAILURE RATE.

- a) WHAT IS THE MACHINE'S MTBF?
- b) " " " " FAILURE RATE?
- c) " " " " MTTR?
- d) WHAT IS THE PROBABILITY THE MACHINE WILL HAVE NO FAILURES IN 200 HRS. OF USE?
- e) IN 500 HRS OF USE?
- f) WHAT LENGTH OF TIME COULD WE USE THE MACHINE AND HAVE A 50-50 (i.e. 50%) CHANCE OF IT'S NOT FAILING?

50
3

2.

AT A RECEIVER, YOU RECEIVE THE FOLLOWING 15 BIT STRING OF BITS WHICH YOU KNOW IS AN 11 BIT HAMMING CODE WITH FOUR PARITY BITS. (ASSUME EVEN ONES PARITY).

- (a) HAS THERE BEEN AN ERROR IN TRANSMITTING THE CODE? HOW DO YOU KNOW?
- (b) ASSUMING ONLY ONE BIT ERROR WAS MADE, CORRECT THIS CODE.

RECEIVED CODE:

1 0 1 0 1 0 1 1 1 0 1 0 1 0 1
 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1


(c):

ASSUME WE RECEIVED THIS CODE OVER A BINARY SYMMETRIC CHANNEL. BEARING IN MIND YOUR ANSWER IN (a), WHAT IS THE PROBABILITY OUR CORRECTED CODE IS THE CODE SENT? THAT IS, COMPUTE:

$$P_r[1 \text{ BIT ERROR} / \text{AN ERROR HAS OCCURED}]$$

ASSUME $P_1 = P_0 = 1/2$ AND $p = q = 0.99$.


3.

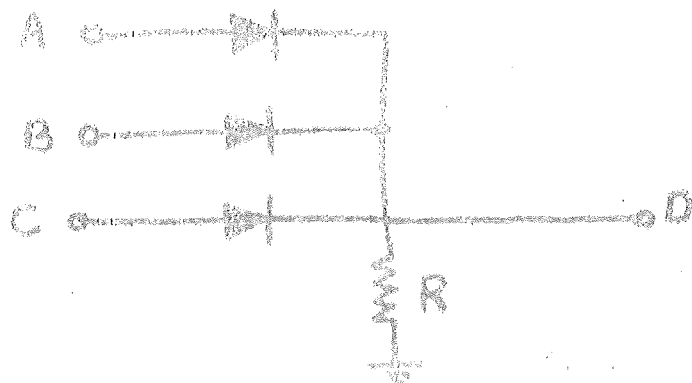

IN THE ABOVE LOGIC CIRCUIT, A, B, AND C ARE AT A LOGIC ZERO WHEN THERE IS NO APPLIED VOLTAGE AND AT A LOGIC ONE WHEN 5 VOLTS IS APPLIED. THE SAME IS TRUE FOR THE GATE OUTPUT, D.

- (a) IN THE SPACE PROVIDED BELOW, DETERMINE THE TRUTH TABLE FOR THIS GATE.
 (b) WHAT TYPE OF LOGIC GATE IS THIS?

A	B	C	D
0	0	0	_____
0	0	1	_____
0	1	0	_____
0	1	1	_____
1	0	0	_____
1	0	1	_____
1	1	0	_____
1	1	1	_____

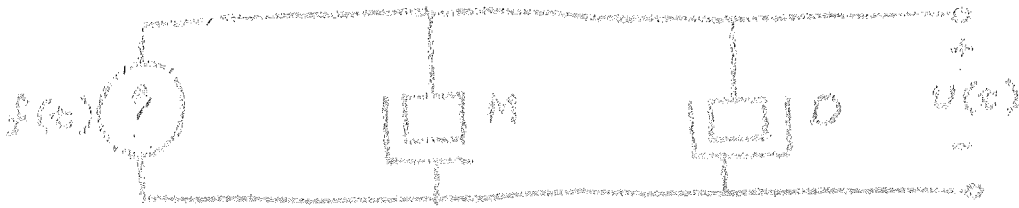

CONSIDER THE ABOVE MECHANICAL CIRCUIT, A MASS M IS SUBJECTED TO AN APPLIED FORCE, $f(t)$. D DENOTES MECHANICAL RESISTANCE. ASSUME $f(t) = f_0 u(t)$ WHERE $u(t)$ IS THE UNIT STEP FUNCTION AND f_0 IS CONSTANT, FURTHER, ASSUME ZERO INITIAL CONDITIONS (I.E., THE INITIAL VELOCITY IS ZERO).

(a) FIND THE RELATIONSHIP FOR THE VELOCITY, $u(t)$, (IN TERMS OF M , D , AND f_0) AS A FUNCTION OF TIME.

(b) GIVEN $M = 5 \text{ kg}$, $D = 1 \frac{\text{NT-SEC}}{\text{M}}$, AND $f_0 = 30 \text{ NT}$, HOW LONG WILL IT TAKE THE MASS TO ACHIEVE A VELOCITY OF 10 METERS/SEC?

(c) IN TERMS OF f_0 AND D AND M , WHAT IS THE SPEED, $u(t)$, IN STEADY STATE (AFTER A "LONG TIME")

WHAT IS THE STEADY STATE VALUE OF $u(t)$ FOR THE PARAMETERS GIVEN IN (b)?

d) DETERMINE THE REQUIRED FORCE, f_0 , THAT IS REQUIRED TO ACHIEVE A VELOCITY OF 100 METER/SEC IN 10 SECONDS. USE

$$D = 1 \frac{\text{NT-SEC}}{\text{M}} \text{ AND } M = 5 \text{ kg.}$$

EE 234 FINAL SOLUTIONS by MARKS! (May 1995)

1. T	26. T	51. F	76. F
2. T	27. T	52. T	77. F
3. F	28. F	53. T	78. T
4. F	29. F	54. F	79. T
5. T	30. T	55. F	80. F
6. T	31. T	56. T	81. F
7. F	32. T	57. F	82. T
8. F	33. T	58. T	83. T
9. T	34. F	59. T	84. F
10. T	35. F	60. F	85. F
11. F	36. T	61. T	86. T
12. F	37. T	62. T	87. T
13. T	38. F	63. F	88. T
14. T	39. F	64. F	89. F (nc)
15. T	40. T	65. T	90. F
16. F	41. T	66. T	91. T
17. F	42. F	67. T	92. T
18. T	43. F	68. F (nc)	93. F
19. T	44. T	69. F (nc)	94. F
20. F	45. T	70. T	95. F
21. F	46. F	71. T	96. T
22. T	47. T	72. F	97. T
23. T	48. T	73. F	98. F (nc)
24. F	49. T	74. T	99. F
25. F	50. F	75. T	100. F (nc)

(nc) = NOT GRADED = AUTOMATIC CREDIT.

1. MACHINE ON TIME = 1000 HRS
 MACHINE REPAIR TIME = 100 HRS
 # FAILURES = 2

(a) $MTBF = \frac{1000 \text{ HRS}}{2 \text{ FAILURES}} = 500 \text{ HRS}$

(b) $\lambda = \frac{1}{MTBF} = 0.002 \text{ FAILURES / HR}$

(c) $MTTR = \frac{100}{2} = 50 \text{ HRS}$

(d) $R = e^{-t/MTBF} \Rightarrow R(200) = e^{-\frac{200}{500}} = 0.67 \Rightarrow 67\%$
 $R(500) = e^{-500/500} = \frac{1}{e} \Rightarrow 37\%$

$0.5 = e^{-t/500}$

$\frac{t}{500} = \ln 2$

$t = 500 \ln 2$
 $= 347 \text{ HRS}$

2. 1 0 1 0 1 0 1 1 1 0 1 0 1 0 1

15 14 13 12 11 10 9 8 7 6 5 4 3 2 1

P_3

P_2

P_1, P_0

(b) OUR RECEIVED PARITY BITS ARE

$P_3 P_2 P_1 P_0 = 1001$

ASSUMING CORRECT CODE, OUR P_0 PARITY BIT SHOULD BE

1 3 5 7 9 11 13 15
 P_0 1 1 1 1 1 1 1
 7 ONES $\Rightarrow P_0 = 1$

FOR P_1 :

2 3 6 7 10 11 14 15
 P_1 1 0 1 0 1 0 1
 4 ONES $\Rightarrow P_1 = 0$

FOR P_2 :

4 5 6 7 12 13 14 15
 P_2 1 0 1 0 1 0 1
 4 ONES $\Rightarrow P_2 = 0$

FOR P_3 :

8 9 10 11 12 13 14 15
 P_3 1 0 1 0 1 0 1
 4 ONES $\Rightarrow P_3 = 0$

RECEIVED: $P_3 P_2 P_1 P_0 = 1001$

SHOULD BE 0001

DIFFERENCE: 1000 \Rightarrow ERROR IN BIN 8.

(a) THE CODE HAD TO BE WRONG SOMEWHERE BECAUSE THE PARITY BITS DIDN'T CHECK.

$$(c) P_p [1 \text{ UNIT ERROR / AN ERROR HAS OCCURRED}] = \frac{P_p [1 \text{ UNIT ERROR AND AN ERROR HAS OCCURRED}]}{P_p [AN ERROR HAS OCCURRED]}$$

$$P_p [1 \text{ UNIT ERROR AND AN ERROR}] = P_p [1 \text{ UNIT ERROR}] = 15 p^{14} (1-p) = 0.1303$$

$$P_p [AN ERROR HAS OCCURRED] = 1 - P_p [NO ERROR HAS OCCURRED] = 1 - p^{15} = 0.1399$$


$$\Rightarrow P_p [1 \text{ UNIT ER / AN ERROR}] = \frac{0.1303}{0.1399} = 0.9312$$

3. THIS IS AN "OR" GATE SINCE ANY TIME A, B OR C ARE FORWARD BIASED BY THE APPLIED $E_{APPLIED}$ ALL OF THE VOLTAGE APPEARS ACROSS THE RESISTOR R. (SEE P. 366 OF SMITH, FIG. 11.4) OUR TRUTH TABLE IS:

A	B	C	D
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

YOUR LAB GRADE	TOTAL % FINAL	RANK IN CLASS	YOUR FINAL GRADE IN THEORY

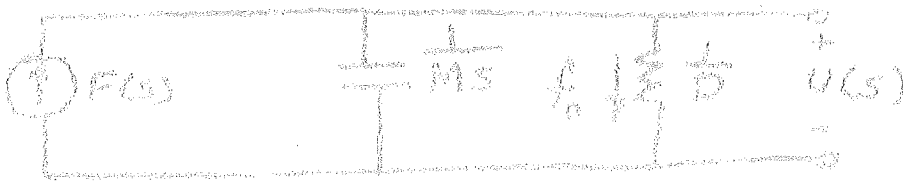4. FIRST, TRANSLATE CIRCUIT INTO LAPLACE DOMAIN



(a) BY CURRENT DIVIDER:

$$f_D = \frac{1/M}{1/D + 1/M} F(s) = \frac{DF(s)}{D+MS}$$

AND $U(s) = \frac{1}{D} f_D = \frac{F(s)}{D+MS}$

NOW $f(t) = f_0 u(t) \Rightarrow F(s) = \frac{f_0}{s} \Rightarrow U(s) = \frac{f_0}{s(D+MS)}$

$$U(s) = \frac{f_0/M}{s(M+s)} = \frac{f_0}{M} \left(\frac{1/s}{1} - \frac{1/(s+D/M)}{1} \right) \quad \left(\leftarrow \begin{array}{l} \text{FROM} \\ \text{HINT} \\ \text{(PARTIAL} \\ \text{FRACTION)} \end{array} \right)$$

$$= \frac{f_0}{D} \frac{1}{s} - \frac{f_0}{D} \frac{1}{s+D/M}$$

INVERSE LAPLACING:

$$U(t) = \frac{f_0}{D} u(t) - \frac{f_0}{D} e^{-t/M} u(t)$$

$$= \frac{f_0}{D} (1 - e^{-t/M}) u(t)$$

(b) $10 = \frac{30}{1} (1 - e^{-t/30})$

$$e^{-t/30} = 2/3 \Rightarrow t = 30 \ln \frac{3}{2} = 12.06$$

(c) $U(t) = \frac{f_0}{D} (1 - e^{-t/M}) u(t)$

$$\Rightarrow U(\infty) = f_0/D = \frac{30}{1} = 30 \text{ m/sec}$$

(d) $U = \frac{f_0}{D} (1 - e^{-tD/M})$



$$\Rightarrow \frac{f_0}{D} = \frac{UD}{1 - e^{-tD/M}} = \frac{(100)(2)}{1 - e^{-10/30}}$$

$$= 352.8 \text{ NEWTONS}$$



marks

Frequency Response Time constant and Fourier series.

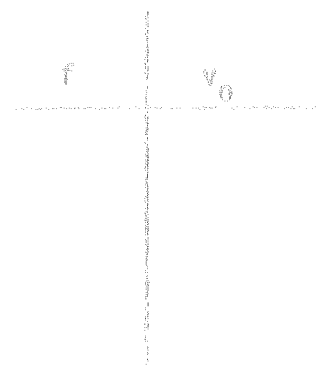
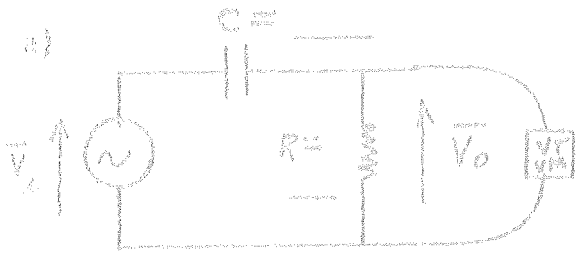
1. Frequency response. For the circuits shown, measure V_o using a sinusoidal input signal set at 2 volts, and vary the frequency from 20 Hz to 5 kHz. Be sure to include the half power point (cut-off frequency) as one of the measurements.



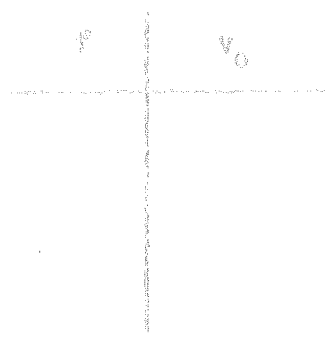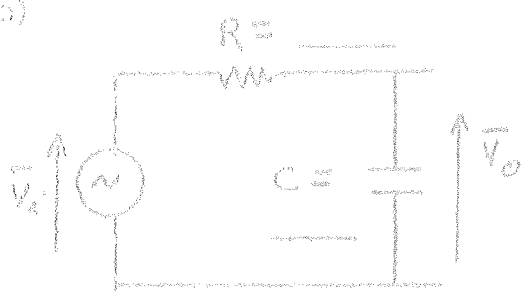cut-off frequency (ω_{co}) = _____ rad/s.





cut-off frequency (ω_{co}) = _____ rad/sec.

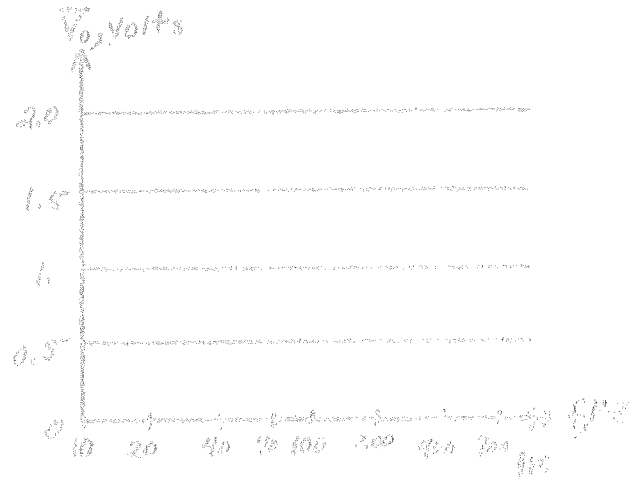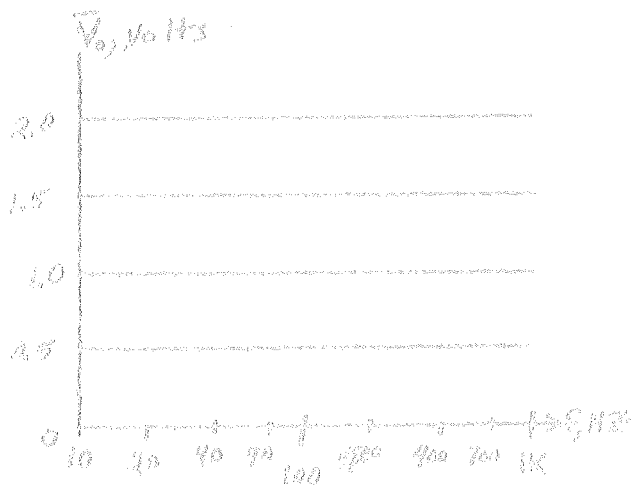

Experiment 10

Date: _____

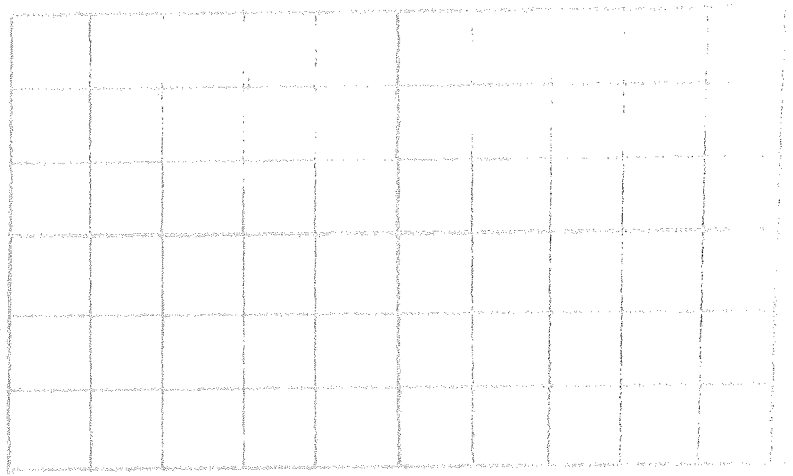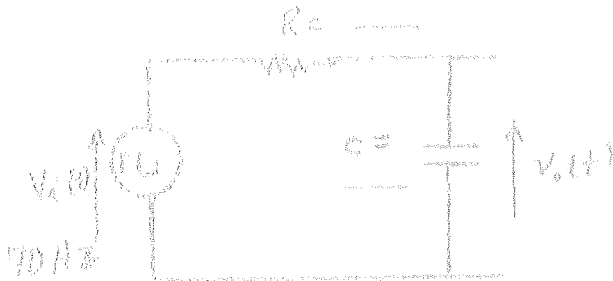The square wave generator is set with the amplitude dial set to the maximum of 10 V and a frequency input of 10 Hz. Use the circuit of part 1(a) and observe $v_o(t)$ with a CRO. Set the horizontal sweep to only one cycle appear on the screen. Then switch the horizontal display knob from "Normal" to "Zero". Record the waveform below and calculate the time constant.




Time constant (τ_c) = _____

DC = _____

$\frac{1}{RC}$ (from part 1(a)) = _____

4) Fourier Series

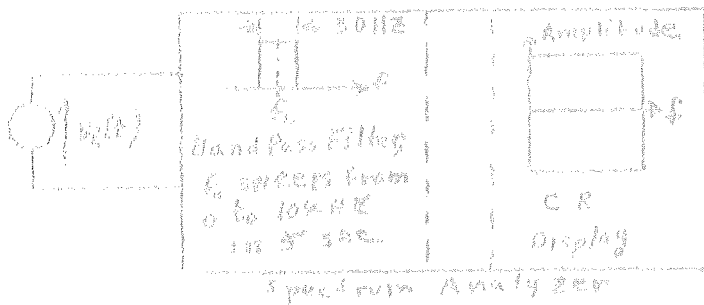

A 1 kHz square wave signal is applied to the input of an HP 3570A Spectrum Analyzer, which displays the harmonics of the signal vs. frequency.

Record the amplitude and frequency of each harmonic. Repeat for the triangular and sinusoidal waves.

Wave	amplitude						
	square	frequency					
triangular	amplitude						
	frequency						
sinusoidal	amplitude						
	frequency						

Marks _____

Ques 13 (17 marks)
 For part (a) (5M) and part (b) (12M).


The objective of this experiment is to measure the current and voltage gains of a BJT amplifier, and the voltage gain of a JFET amplifier. The list of parts and their values are shown below:

Material: 2N4338 JFET and
 2N2222 BJT

OSWICK-TO-SWEE
 p-channel



Part (a) amplifier

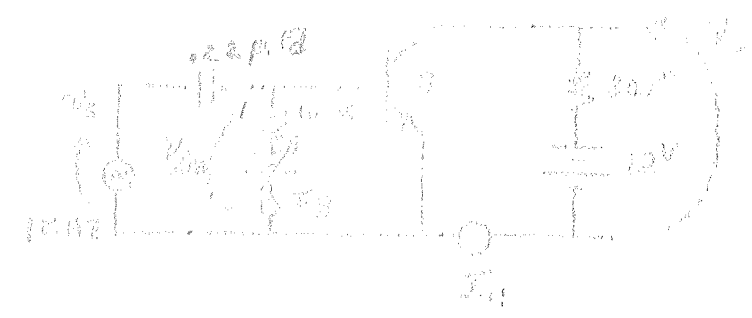


(a)

(b)

- Construct the circuit of Fig. (a), and in part (i) find each of the following values of I_B (mA): 2, 3, 4, 5, 6 and $I_{B(max)}$ (mA).
- Construct the circuit of Fig. (b) and adjust I_G to 1 mA, measure I_D . Connect a load of 10kΩ to the output and measure I_D and V_D again. Repeat the above steps for the input slightly until the output becomes undistorted. Measure V_D and I_D (at 10kΩ load) with the aid of a multimeter.

Part (b) amplifier

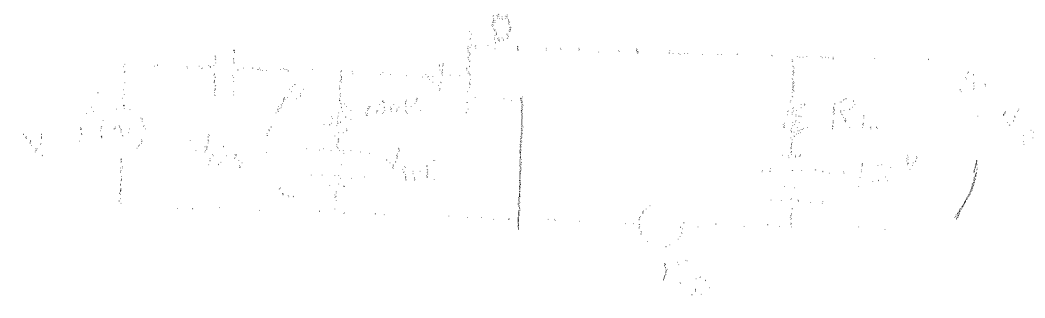

1. Connect the above circuit with the following values: $V_s = 0$, $R_L = 0$. Measure I_B for each of the following values of V_{GG} (volts): 3, 2, 1, 0.5, .1, 0.
2. Set V_{GG} to 2 volts and R_L to 3 k ohms. Connect a CRO to the output and gradually increase V_s until V_o appears distorted. Reduce the input until distortion is eliminated. Measure V_o and V_{in} (peak to peak) with the CRO.

Report

- Part A (1). a) Calculate the d.c. beta (current gain) for $I_B = 0.2$ ma.
 b) Calculate the a.c. current gain (a.c. beta) as follows:

$$B = \frac{\Delta I_C}{\Delta I_B} \quad (V_{CE} \text{ constant}).$$

use the .2 to .3 change for ΔI_B .

- A (2). Calculate the voltage gain.

- B (1). The amount of control that the gate voltage has over the drain current is measured by the change in I_D per volt change in V_{GG} . This is called g_m (mhos) and is expressed as

$$g_m = \frac{\Delta I_D}{\Delta V_{GG}} \quad (\text{constant } V_{DS}).$$

Calculate g_m using data for V_{GG} change from 0.5 to 1 volt.

- B (2). Calculate the voltage gain.

marks

Recording Instruments

The purpose of the laboratory is to demonstrate:

1. The basic ideas of operation of the most commonly used recording instruments,
2. Ways to calibrate recording instruments,
3. Frequency limitations of instruments,
4. Sensitivity of the instruments and noise effects at high sensitivity positions of the instruments.

Equipment:

- | | |
|--------------------------|----------------------|
| 1. Strip chart recording | 2. X-Y plotter |
| 3. Function generator | 4. D.C. Power Supply |

Lab Procedure

A. X-Y plotter

Connect the function generation (sine wave) to the X-Y plotter. Set the function generator frequency to 0.1 HZ, and the plotter sensitivity to 1 volt/division. Increase the generator output until the recorder output produces 5 inches of deflection (peak to peak).

1. Keep the generator voltage constant (use a CRO or a digital voltmeter to measure it). Plot a curve of deflection vs. frequency (frequency response curve), using frequencies of 0.1, 1, 3, 3, 4, and 5 HZ, or until the half power point is found.
2. Replace the generator with d.c. source. Increase the d.c. voltage to get 1 inch of deflection. Calibrate the recorder. (Note that this is a d.c. amplifier). Use this reading for calculating sensitivity.
3. Remove the source from the input to the plotter. Set the sensitivity to maximum. Touch the input terminals with the fingers. Note the results.
4. Set the function generator to produce a ramp at .1 HZ. Use the plotter to get a graph of this voltage vs. time. Use a 1 V/division sensitivity setting.
5. Repeat for triangle and square wave.

Strip Chart Recorder

1. Set the input of the recorder to the 5 volt range. Connect the function generator to the recorder and set the generator amplitude to produce a peak-to-peak deflection of 3 inches. Set the chart speed to 8 inches/minute. Note the type of marking pen used. How does it differ from the X-Y plotter pen?
2. Repeat steps 1 through 5 of part A, for the strip chart recorder.

Reports:

1. Describe a galvanometer type recorder.
2. For the X-Y plotter, describe the mechanism and associated circuits used to move the pen in the X direction. What is the maximum speed that the pen will move?
3. Plot a curve of maximum deflection vs. frequency for the X-Y plotter and strip-chart recorder.
4. Describe a capillary ink writing system and a heated stylus system.
5. Define sensitivity and calculate it for the strip-chart recorder and X-Y plotter.

References:


Principles of Modern Instrumentation - Spitzer, Howarth
Guide to Electronic Measurements and Laboratory - Stanley Wolf
Electrical Measurements and Instrumentation - Oliver and Page

Marks


IC OP-AMP

This experiment will provide an introduction to integrated circuit operational amplifiers (IC op-amps). Today op-amps are used in a wide range of analog signal processing including signal amplification, wave shaping, servo and process control. Op-amps are also used in many non-linear applications such as comparators, analog to digital and digital to analog convertors and non-linear function operators. We will be concerned with the use of an op-amp as an amplifier, a summer, and an integrator.

In this experiment you will be using type 741 op-amps. They have a gain of about 200,000 open circuit and a bandwidth of about 1 MHz for unity gain. The 741 is an integrated circuit, meaning that the op-amp is implemented by transistors and resistors grown or deposited on a single chip of semiconductor material (in this instance it is silicon).

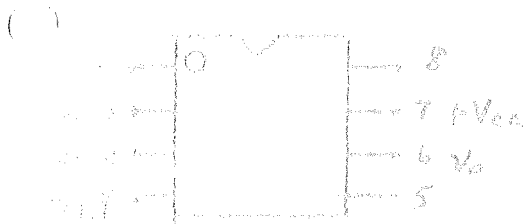

(Fig. 1.1) (741-8 pin)

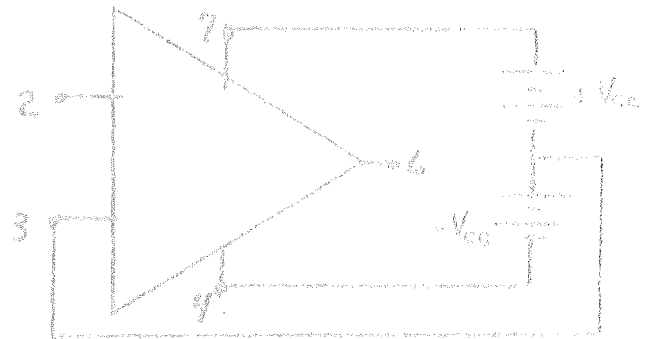

- (a) Pin 1 - non-inverting input
- (b) Pin 2 - inverting input

Power Supplies

In order to achieve the ability to produce both positive and negative voltages the op-amp requires both $+V_{cc}$ and $-V_{cc}$ supplies. The 741 will operate on supply voltages of from $\pm 9V$ to $\pm 22V$. We will use $\pm 12V$ for our work. The two power supplies are connected as shown above and need not be disconnected (though they should be turned off while changing circuits) during the experiment. This connection will not be shown on subsequent diagrams.

Scope Triggering


To observe the inversion of the input signal by the op-amp it will be necessary (on a one channel scope) to synchronize the scope trigger from some reference - usually the output of the signal generator. This is done by connecting the scope trigger input to the ungrounded side of the signal generator and putting the scope trigger source control on ext + or - and the trigger coupling control on AC or DC - and then adjusting the trigger level control. The lab instructor will review this with the class before beginning the experiment.

If a two channel scope is available, connect the amplifier input to one channel, and the output to the other, and observe the inversion.

Amplifiers

A. Inverting Amplifier

Connect the op-amp as shown below:

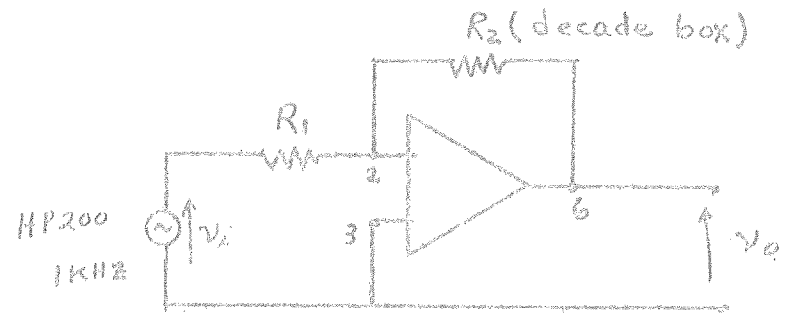


- a) Use 5K ohms for R_1 , and set R_2 to give theoretical gains of 10, 20, 40 and 80. Set the input signal to give about 12 volts peak-to-peak for v_o . Adjust the input to eliminate distortion. Measure the gain in each case, using the CRO as a voltmeter.
- Q1. How does the measured gain compare with the theoretical gain?
- b) With the x80 theoretical gain setting, increase the signal input until you observe clipping on both the upper and lower portions of the output. Measure the voltage difference between the upper and lower clipping points on the output. The clipping is caused by the op-amp reaching its maximum and minimum output voltages (the saturation voltages), which are determined by the power supply voltages. A gain of x100 does not mean that the output will be 100 times the input

(1) v_{out} since the amplifier gain is much the greater (100).
 If $v_{in1} = 100$ and $v_{in2} = 1$ our op-amp would not give 100 but rather
 $v_{out} = -$ because it inverts.

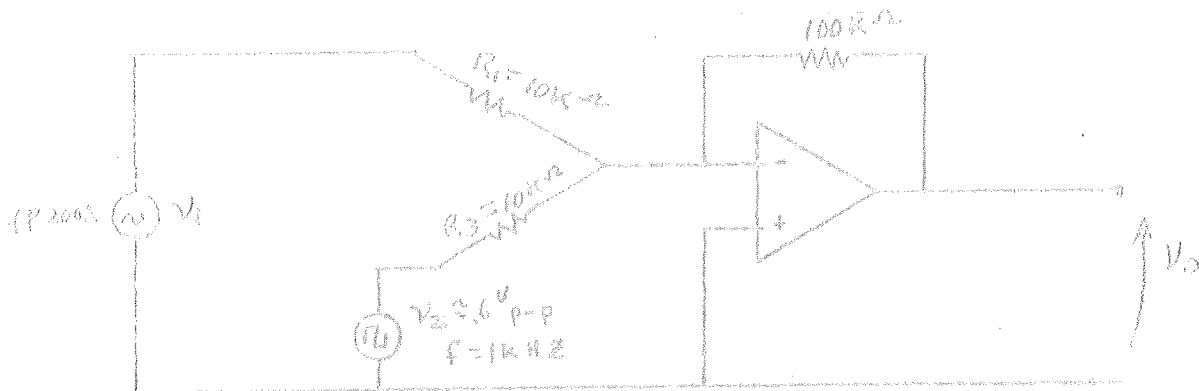2. Summer

With the op-amp connected as a x10 amplifier ($R_1 = 10K$, $R_2 = 100K$)
 connect R_3 to the - input terminal (also known as the "summing point")
 and connect the output of the square wave generator to it as shown.




Adjust the square wave generator so v_2 is 0.6 v p to p. Observe
 v_1 with the scope synched to the square wave and sketch the wave-
 form. Now connect the H-P oscillator, set its freq. to 45Hz and
 slowly increase its amplitude to about 1/2 the amplitude of v_2 ,
 and sketch v_1 . Slowly change the frequency of v_1 until a steady
 pattern results in v_0 .

Q? Sketch the output with both generators connected. Is it the
 sum of the two inputs?

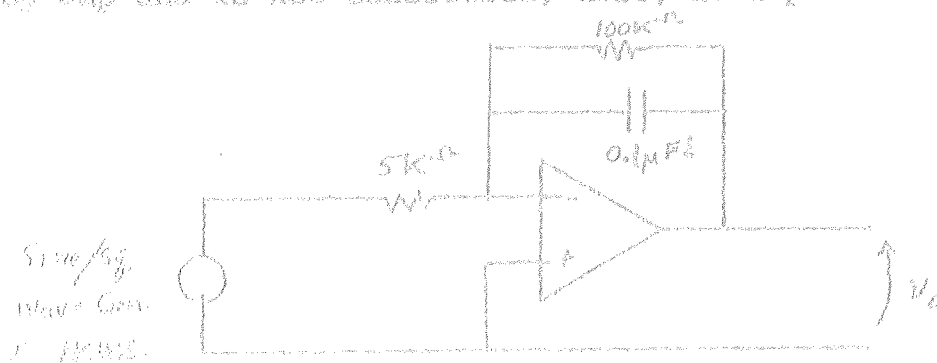3. Integrator

For integration a capacitor is added in the feedback loop, as
 shown below. The 100K resistor is present for d.c. stabilization of
 the op-amp and is not considered, here, as a part of the feedback loop.



()

- Q1) Connect the circuit as shown. Set the generator for a square wave output, $f = 1\text{kHz}$, $V_{in} = 5\text{V}$, p to p. Observe the output.
- Q2) Sketch output waveform - what sort of wave is this? Is it the integral of the input? Explain?
- Q3) Switch the generator to sine wave output, increase its output maximum. Observe the output v_o . Use ext. trigger for the osc.
- Q4) What output does an integrator produce if the input is a sine wave? Did this circuit really integrate? Explain.

()

()


Voltage Divider

The voltage divider circuit is used to divide the input voltage into a smaller output voltage. It consists of two resistors connected in series. The output voltage is taken across one of the resistors. The voltage divider rule states that the voltage across a resistor in a series circuit is proportional to its resistance. The formula for the output voltage V_o is given by:

$$V_o = V_i \frac{R_2}{R_1 + R_2}$$

where V_i is the input voltage, R_1 and R_2 are the resistances of the two resistors, and V_o is the output voltage across R_2 .

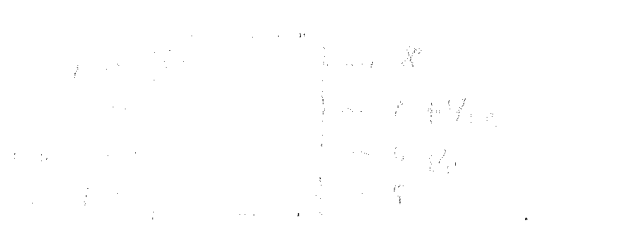The voltage divider circuit is widely used in electronics for various applications. It is used to provide a reference voltage, to bias transistors, and to measure the voltage across a component in a circuit. The circuit is simple and easy to implement, and it provides a reliable and accurate way to divide the input voltage.



The voltage divider circuit is a fundamental building block in electronics. It is used in a wide variety of applications, from simple voltage measurement to complex signal processing. Understanding the voltage divider rule is essential for designing and analyzing electronic circuits.


The voltage divider circuit is a simple and effective way to divide the input voltage. It is used in a wide variety of applications, from simple voltage measurement to complex signal processing. The voltage divider rule is a fundamental principle in electronics, and it is essential for understanding the behavior of resistors in a series circuit. The voltage divider circuit is a simple and effective way to divide the input voltage, and it is widely used in electronics for various applications.

To observe the effect of the input impedance of the scope on the source impedance, connect the input impedance of the scope to the output of the circuit. The input impedance is set by connecting the scope to the circuit. This can be done by connecting the scope to the output of the circuit. The input impedance of the scope can be adjusted by changing the gain control of the scope or by using a probe. The input impedance of the scope is typically 1 MΩ or higher. The output impedance of the circuit is typically 100 Ω or lower. The frequency coupling of the scope can be set to AC or DC. The trigger level control of the scope can be used to adjust the trigger level of the scope. The scope should be used to observe the effect of the input impedance of the scope on the source impedance of the circuit.

If a dual channel scope is available, connect the scope to use both channels, and observe the effect of the input impedance on the output.

3. Inverting amplifier

Connect the system, as shown below:

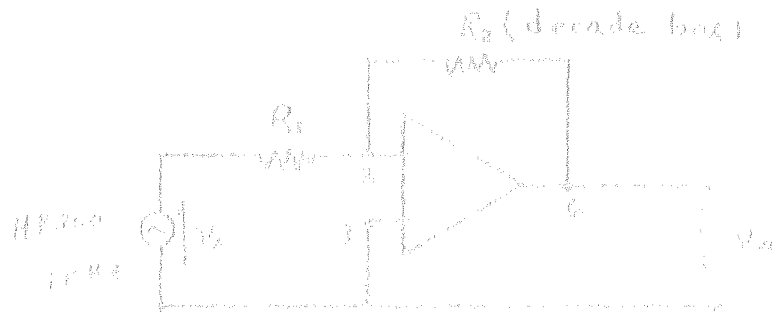


Set the gain of the amplifier to 10, and set V_s to give theoretical output of 10, 20, 40 and 80. Set the input signal to give about 1V peak-to-peak for V_s . Adjust the input to produce a theoretical output. Measure the gain in each case, using the 100 mV/div setting.

Compare the measured gain with the theoretical gain. As the gain increases, increase the input signal until you observe clipping on both the upper and lower portions of the output. Measure the voltage difference between the upper and lower clipping points on the output. The clipping is caused by the op-amp reaching its maximum and minimum output voltages (the saturation voltages) which are determined by the power supply voltages. The gain of the circuit will be less than the theoretical gain.

... the output of the square wave generator is v_1 and the output of the sine wave generator is v_2 .

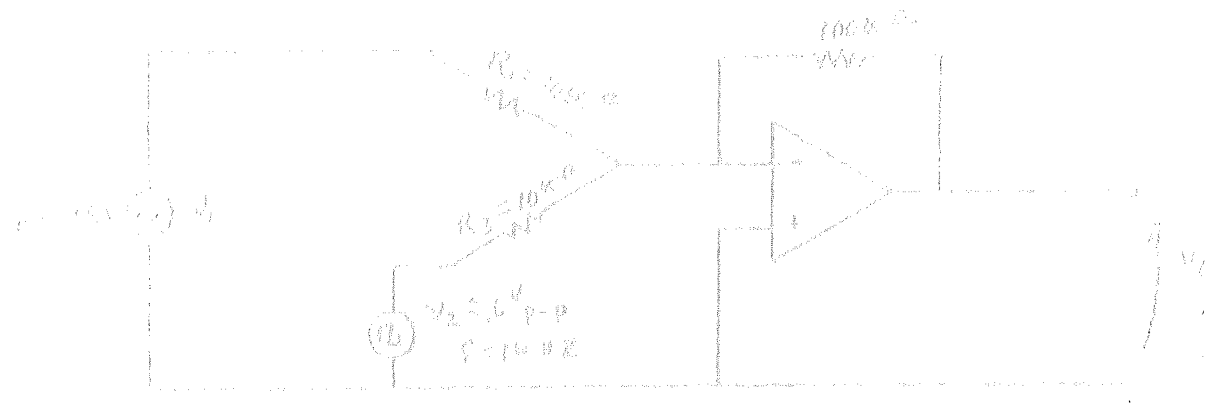... the circuit is connected to a uA761 multi-level op-amp. The circuit is shown below. The input terminals are labeled v_1 and v_2 . The output is labeled v_o .




... adjust the square wave generator so v_1 is 0.6 V p-p. Observe v_1 with the scope and sketch v_1 with the scope and sketch v_2 with the scope. Now connect the uA761 oscillator, set its frequency to 100 Hz and slowly increase its amplitude to about 1/2 the amplitude of v_1 and sketch v_2 . Slowly change the frequency of v_2 until a steady waveform results in v_o .

... sketch the output with both generators connected. Is v_o the sum of the two inputs?

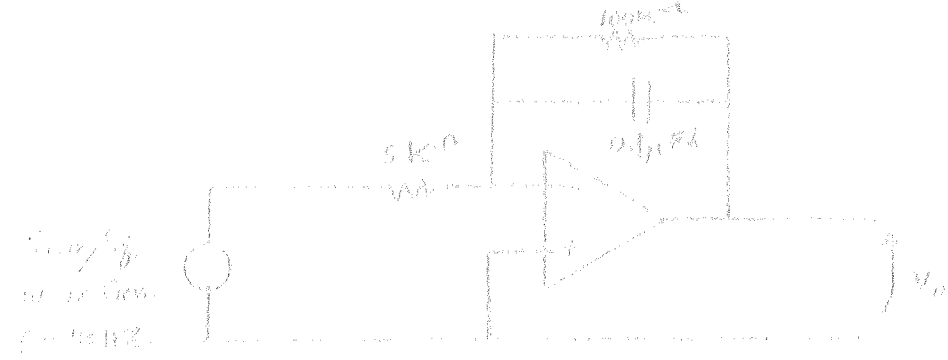4. Integrator

For integration a capacitor is added in the feedback loop, as shown below. The 100kΩ resistor is present for d.c. stabilization of the op-amp and is not considered, here, as a part of the feedback loop.



()

- a) Compute the Fourier transform $\hat{v}_1(\omega)$ of the signal $v_1(t)$ and compare it with the Fourier transform $\hat{v}_2(\omega)$ of the signal $v_2(t)$ obtained in part (a).
- b) Compute output envelope $v_{out}(t)$ and compare with the envelope $v_{in}(t)$ of the input. Why?
- c) Switch the generator to sine wave output, amplitude 10, and phase zero. Observe the output $v_{out}(t)$ and compare with the input $v_{in}(t)$.
- d) Switch output down to frequency produced by the input sine wave. Did this circuit really "labelize" signals?

()

OILFIELD AUTOMATION SIMULATION

May 9, 1975

By Mark Carpenter

OILFIELD AUTOMATION SIMULATION

This program is a dynamic simulation of an oilfield to be utilized as a teaching aid in the understanding of digital control systems. The complete systems dynamics are incorporated in the program so that the user may write a control program for the field.

Designation of Program Variables

The following is a list of matrix variables, their dimensions, and usage in the program.

Q(4) Well
Q(K)=J

P(4) Well Status P(K)=1 then Well K is on
P(K)=0 then Well K is off

X(4) X-axis position of well in a fractional number

Y(4) Y-axis position of a well in a fractional number

W(4) Manifold Status W(K)=1 means Well K feeds Separator 1
W(K)=2 means Well K feeds Separator 2

Z(4) Complement of W(K)-1

B(6) Total tank capacities for the two separators, two oil holding tanks, and two water holding tanks

L(14) Various valves in the oilfield

C(14) Pump capacities of the pumps
 E(2) Water outlet levels in the two separators
 F(2) Oil outlet levels in the two separators
 T(6) Total fluid volume in the six tanks
 O(2) Oil volume in the two separators
 I(2) Water volume in the two separators

The letter T designates the sample time in hours, and T9 is a counter to keep up with the total time period accumulated. Also used in the program are O1, O2, O3, O4, I1, I2, I3, I4, S5, S6, S7, S8, W1, W2, K, and K6. Care should be taken in the writing of the control program to prevent an overlapping of variables.

The Oilfield

The oilfield (Figure 1) has four wells, two separators, two oil holding tanks, and two water holding tanks. The valves are designated by X and are numbered. The pump locations are marked with a V and have the same subscript number as the valves at that location. For instance, C(6), or pump number 6, is located at valve L(6), where at valve number 9, L(9), there is no pump.

T(1) and T(2) are Separator 1 and Separator 2, T(3) and T(4) are the water holding tanks, and T(5) and T(6) are the oil holding tanks.

The entire control scheme centers around the two separators. Figure 2 shows a separator and various outlet locations.

Since the tanks are cylindrical, the volume is directly proportional to the height of the fluid. The main program sets $F(K)$ at 30% and $E(K)$ at 33.3% of the total tank height or volume. $I(K)$ is the water level of the tank and $T(K)$ is the total fluid level in the tank.

The control program will contain $R(K)$, $F(K)$, $T(K)$, $I(K)$, and $O(K)$ as fractional portions of the total tank capacity, $B(K)$.

The Control Program

The control program will be interfaced with the main program so that the main program will record accumulations in the tank and the control program will control the flows into and out of these tanks. Figure 3 shows a flow chart of the relationship between the main and control programs.

When the program is initially started, it goes through the dynamics first and then to the control program. The control program should monitor the tanks and make appropriate valve status changes. After the control operations are completed, the main program will transfer to the system dynamics, and the tank accumulations will again be calculated with the new valve statuses.

Inputs by the Operator

The following questions will be asked to the operator when the program is initially started:

1. Is Well 1-4 ON or OFF
2. Does Well 1-4 feed Separator 1 or Separator 2
3. What are the tank capacities in barrels
4. What are the Pump Capacities in GPM (the program will convert it to barrels/hour)
5. What is the valve status of L(9) and L(10) (water holding tank manifold)
6. What is your sample time in minutes (the program will convert it to hours)

These values will be asked only once during the program. The sample time will determine how often the control loop will monitor the various tank and interface levels.

The System Dynamics

The system dynamics are simple rate and accumulation equations whose dimensions are barrels and hours. The change in accumulation is calculated by multiplying the difference of the input and output by the sample time. A number of IF statements are used to prevent the mathematical equations from exceeding the systems physical limitations. For instance, the total fluid volume cannot exceed a tank volume. The program will terminate anytime a tank overflows, water gets in the oil tank, or oil gets in the water tank.

Print Out

The main program will print once each sample time. The total accumulated time, the volumes of fluid in all the tanks,

on the control level. From two separate calls he received any data information needed by the operator should be provided from the control program.

Safe Needs for writing the Control Program


1. The variables $H(K)$ and $L(K)$ are the only variables that the control program should alter. All other variables can be compared with a control variable, but they should not be changed.
2. The control program will see the sample time in hours, not minutes.
3. The fluid volumes $V(K)$, interface levels $I(K)$, oil volume $O(K)$, will be given as a fractional part of the total tank capacities $B(K)$.
4. The water outlet level and oil outlet level $B(K)$ and $F(K)$ respectively, are also in a fractional form of the total tank size.
5. The control program should be written from statements 2500 to 8999. Statements 1-10 can be used to initialize counters.
6. The last statement in a control program should be a Remark Statement. Any time the program needs to be transferred to the main program, send it to your last statement. The main program will pick it up at this point.

Conclusion

This program is set up to aid in the teaching of digital control systems. The program has the potential of demonstrating to a user about the operation of digital control systems. However, the amount of understanding derived from the program is proportional to the amount of time and effort put in by the operator.

A group of Chemical Engineering students wrote the first control programs for the system. Two students in particular, Gerald Grossman and James Simpson, did exceptional work, and their control programs aided in the final polishing of the main program.

TESTON TOLLUPTIO - SIKIDOLU

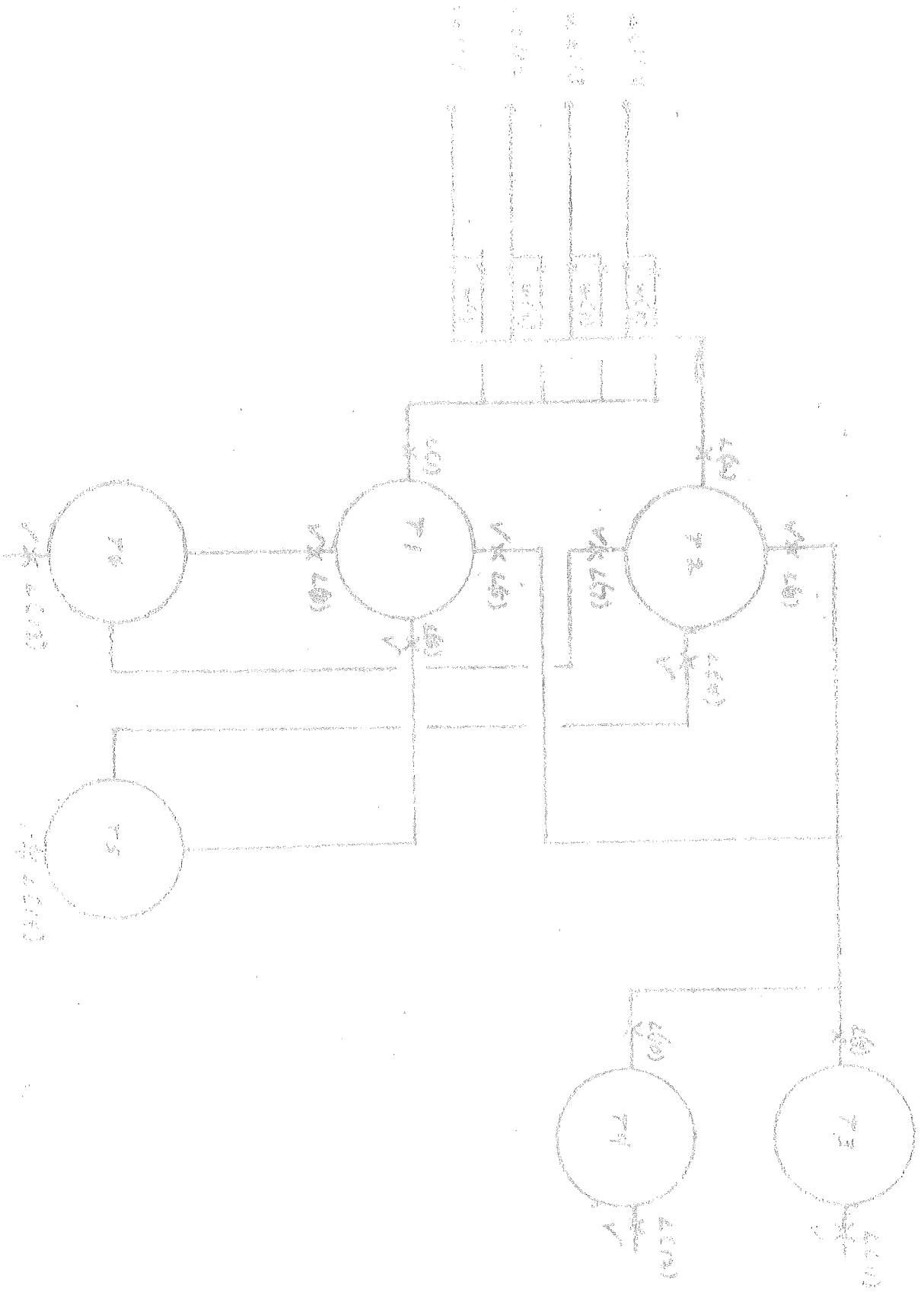

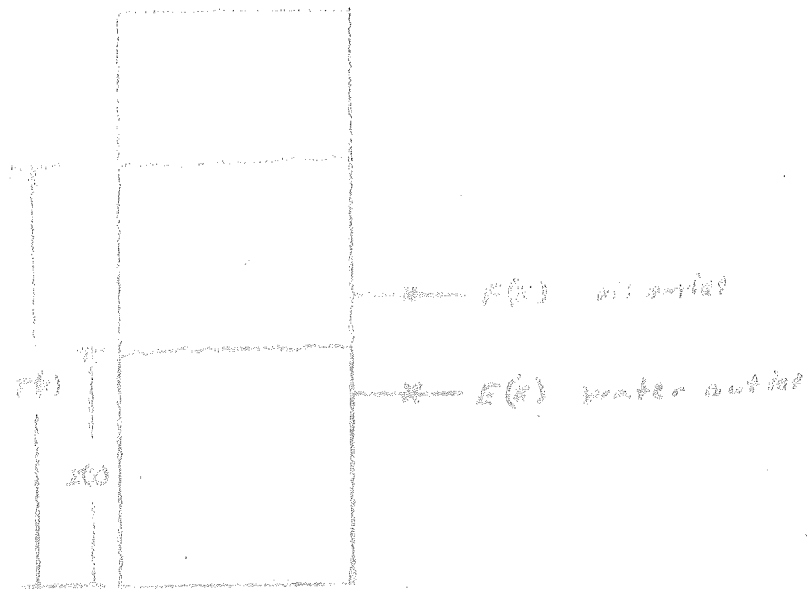


FIGURE 2
A SEPARATOR


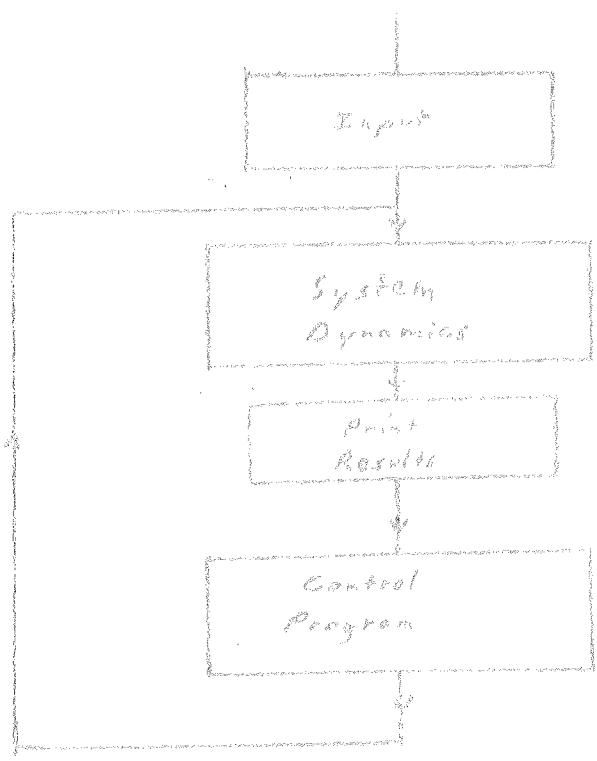


FIGURE 3
PROGRAM FLOW CHART

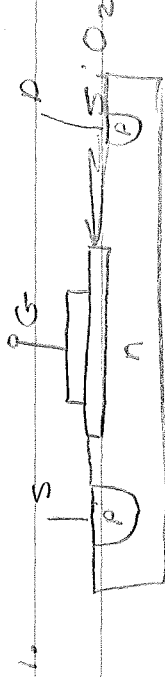
B. MOSFET

(METAL-OXIDE-SEMICONDUCTOR FET)

THIN LAYER OF SiO_2 SEPARATES GATE FROM CHANNEL



P-CHANNEL ENHANCEMENT-MODE MOSFET

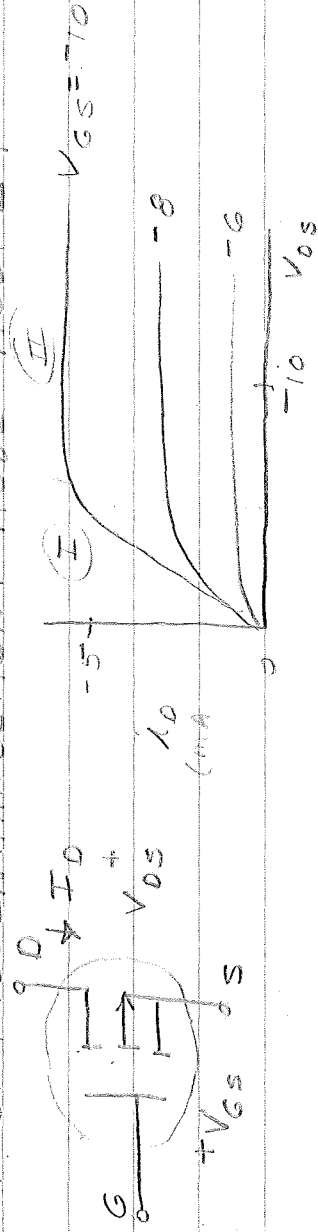

I


WITH SMALL GATE VOLTAGE (V_{GS}), ELECTRONS IN ADJACENT N MATERIAL ARE REPELLED AND A DEPLETION LAYER FORMS.

II


BY MAKING V_{GS} EVEN SMALLER, AN "INVERSION LAYER" OF ^{MOBILE} HOLES IS FORMED IN THE N MATERIAL, WHICH BECOMES A P MATERIAL. CONDUCTION IS "ENHANCED"

2. DEPLETION-MODE OR ENHANCEMENT

MODE MOSFET

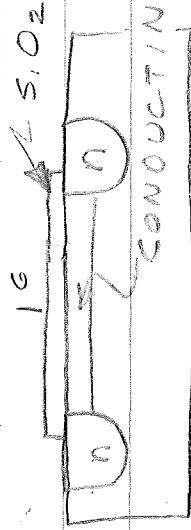


ALLOWS BOTH POS & NEG. V_{GS}

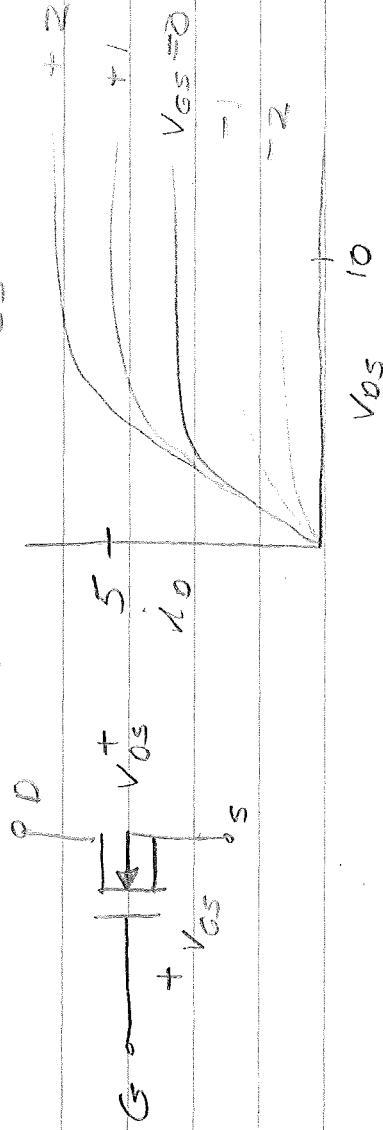

3. TRANSFER CHARACTERISTICS

PINCHOFF

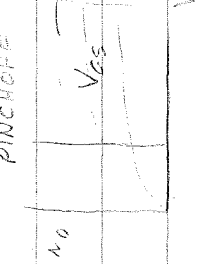


BREAKDOWN

BETWEEN PINCHOFF & BREAKDOWN

I_D IS ROUGHLY INDEPENDENT OF

V_{DS}.

V_{GS}

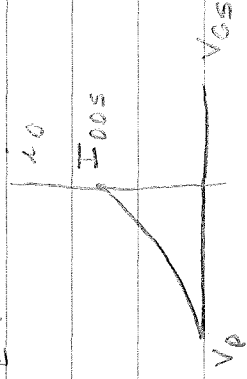


$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P}\right)^2$$

$$V_P \approx 5V$$

I_{DSS} → DRAIN SHORTED TO SOURCE

DEPLETION-ENHANCEMENT MOSFET

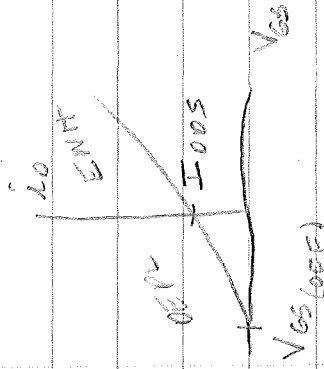


ENHANCEMENT ONLY

$$I_D = K(V_{GS} - V_T)^2$$


V_{GS}

IV. JUNCTION TRANSISTORS

A. FABRICATION

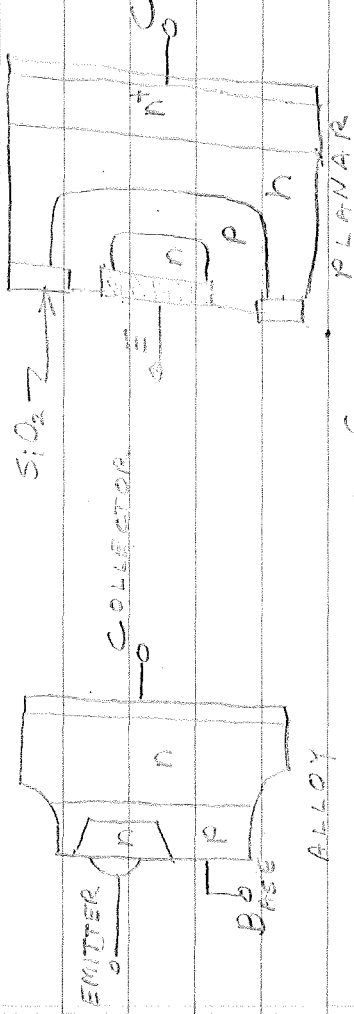


SYMBOL:

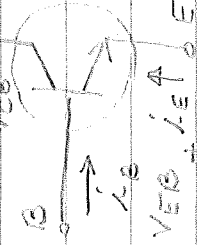

ARROW POINTS IN MATERIAL.

\Rightarrow THIS IS AN NPN RESISTOR

B. OPERATION

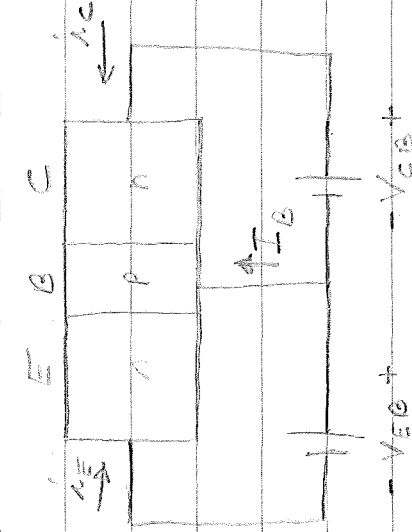

EMITTER JUNCTION FORWARD BIASED
 POTENTIAL BARRIER AT
 EMITTER IS REDUCED. THIS
 FACILITATES INJECTION OF
 e^- INTO BASE WHERE
 THEY ARE MINORITY CARRIERS

COLLECTOR JUNCTION IS REVERSE BIASED.

(POTENTIAL BARRIER @ COLLECTOR IS INCREASED.)

ALMOST ALL e^- 'S FROM EMITTER DIFFUSE ACROSS

THE BASE AND ARE SWEEP UP POTENTIAL HILL

WHERE THEY RECOMBINE WITH BATTERY HOLES

RESULT: XFER FROM E TO C A CURRENT


INDEPENDENT OF V_{CE} (MODULATION OF

E PRODUCES CORRESPONDING CURRENT

CHANGES IN I_{EC} CURRENTS OR $(I_{EC})_{MOD}$ OF BASE

CONTROLS I_C FOR CURRENT AMPLIFICATION

C. D.C. BEHAVIOR

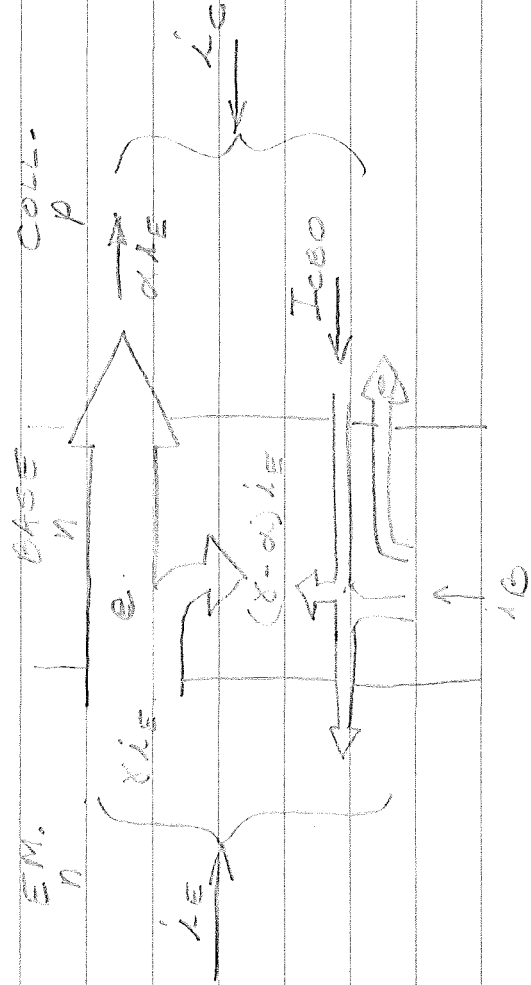

{ E IS FORWARD BIASED

{ C IS REV. BIASED


$\gamma =$ EMITTER EFFICIENCY ≈ 1

$$I_C = -\alpha I_E + I_{C_{EO}}$$


$\alpha =$ FORWARD CURRENT XFER RATIO

(INCREASES WITH V_{CB})


D. COMMON BASE CHARACTERISTICS

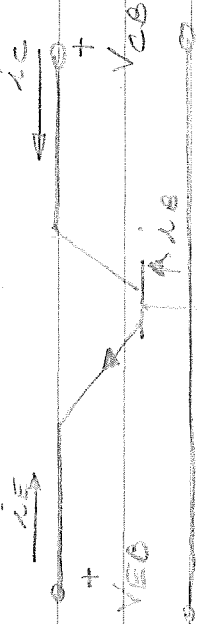

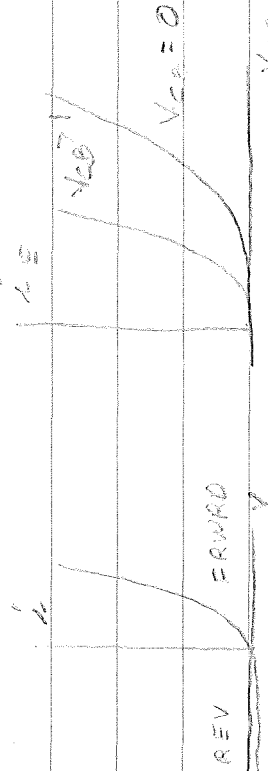
EMITTER-BASE SECTION IS A FORWARD-BIASED DIODE



DIODE Emitter Characteristics

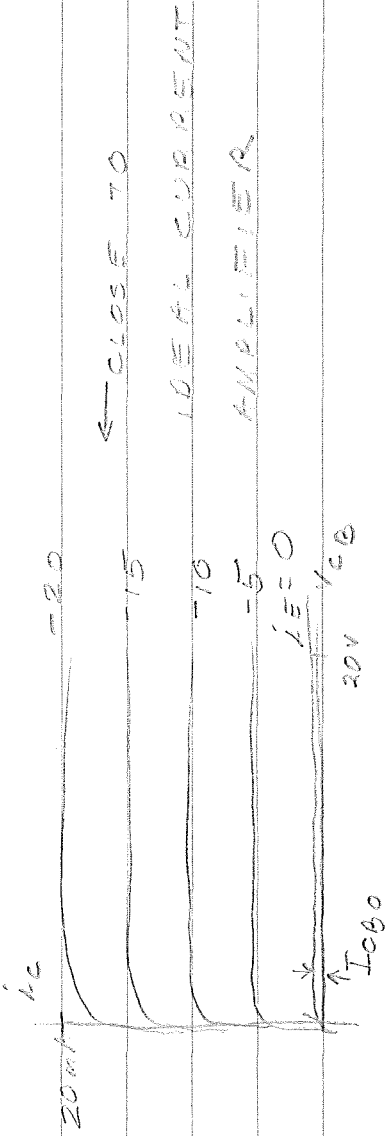

E. COMMON-EMITTER CHARACTERISTICS

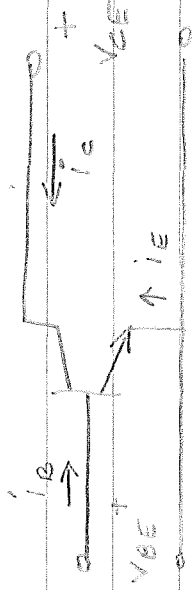

NON

$$I_C = \alpha I_E + I_{CEO} = \alpha (I_C + I_E) + I_{CEO}$$

$$\Rightarrow I_C = \frac{\alpha}{1-\alpha} I_E + \frac{I_{CEO}}{1-\alpha}$$

$$\beta = \frac{\alpha}{1-\alpha} ; \frac{1-\alpha}{1-\alpha} I_{CEO} = (1+\beta) I_{CEO} = I_{CEO} \rightarrow$$

$$\therefore I_C = \beta I_E + I_{CEO} \quad (\text{CONT}) \rightarrow$$

EXAMPLE:

$$\alpha = 0.99, I_{CEO} = 10^{-9} \text{ A}$$

$E = 10 \text{ V}, I_C, I_E, V_{CE}$



$$I_B = 20 \mu\text{A}$$

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.99}{0.01} = 99$$

$$I_{CEO} = (1+\beta) I_{CEO} = 10^{-9} \text{ A}$$


$$I_C = \beta I_E + I_{CEO}$$

$$= 99 (20 \times 10^{-6}) + 10^{-9} = 1.98 \text{ mA}$$

$$I_E = -(I_C + I_B) = -2 \text{ mA}$$

$$V_{CE} = 10 - I_C (2k) = 10 - (1.98)(2) = 6 \text{ V}$$


(CONT) \rightarrow

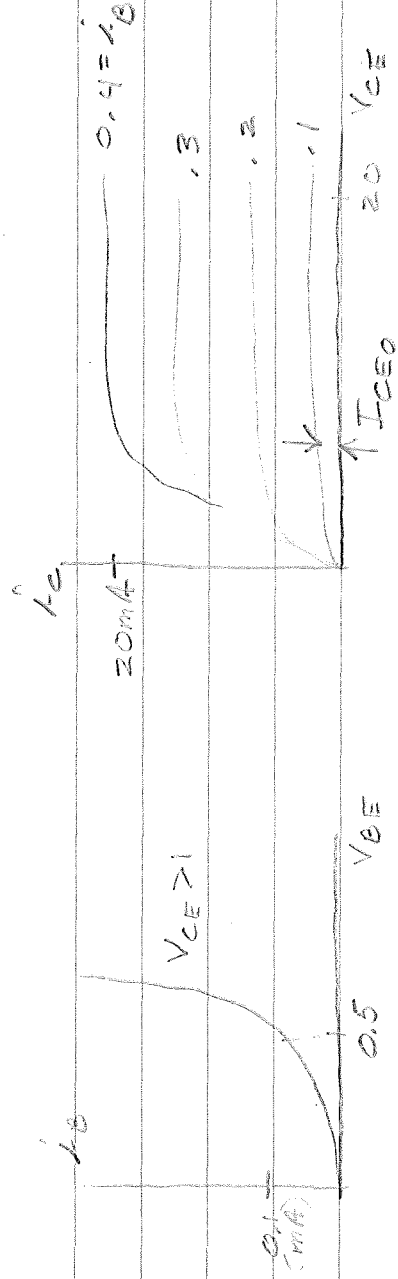

EXAMPLE

$\beta = 15$

$i_C \downarrow \approx 1 k\Omega$

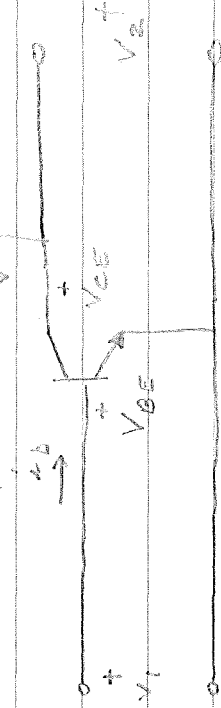

$\beta = 50, I_{CE0} \approx 10^{-9} A$

(a) $V_1 = 0.2 V$

FROM GRAPH, $V_1 = V_{BE} = 0.2 V \Rightarrow i_B \approx 0$

$$i_C = \beta i_B + I_{CE0} \approx I_{CE0} \approx 10^{-9} A \approx 1 nA$$

$$\Rightarrow V_2 = V_{CE} = 15 = i_C (4 k\Omega) \approx 15 V$$

(b) $V_1 = 0.8 V$

FROM GRAPH, $V_1 = V_{BE} = 0.8 V \Rightarrow i_B = 0.4 mA$

$$i_C = \beta i_B + I_{CE0} = (50)(0.4) = 20 mA$$



BUT THIS IS IMPOSSIBLE SINCE THERE IS ONLY 15V @ A 1 k RESISTOR.

FROM TOP RT. FIGURE, THE CONCEPT IS

NOT VALID FOR SMALL V_{CE} . WE HAVE

INSTEAD, $V_{CE} = 1 V$ FOR $V_1 = 0.8 V$

F. CURRENT AMPLIFICATION

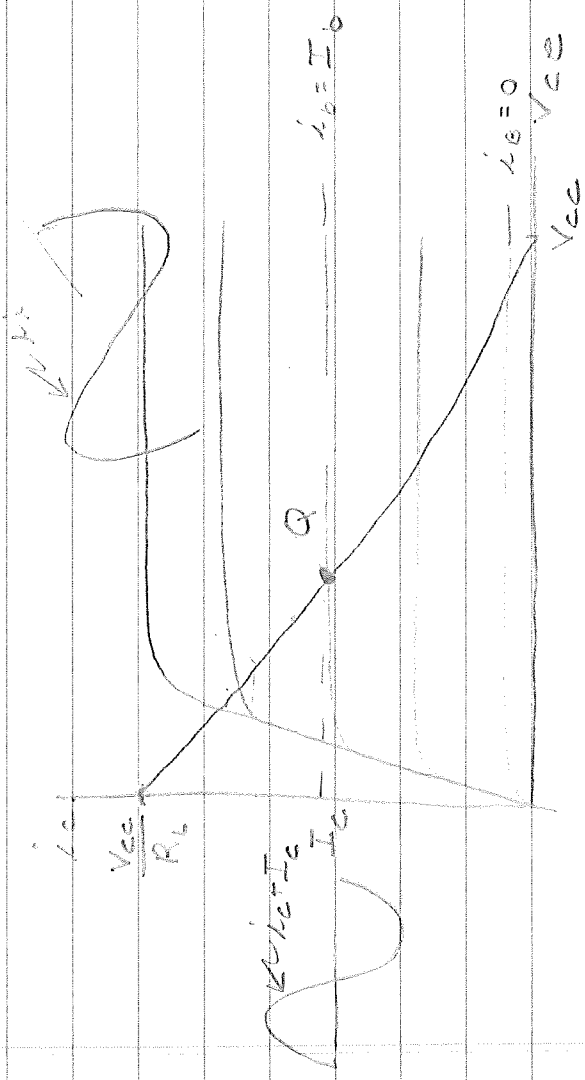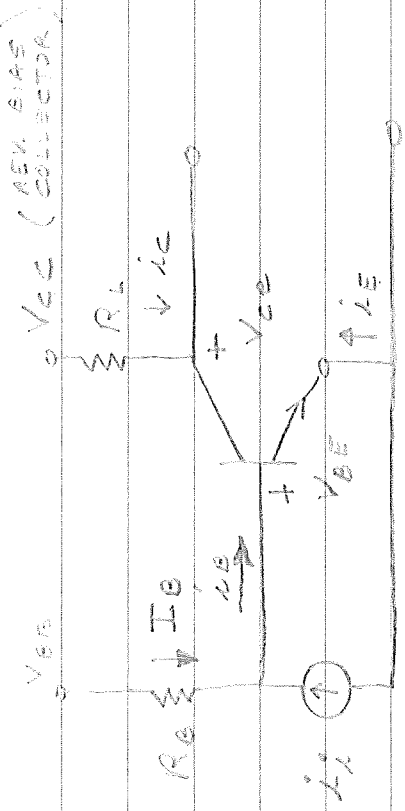

Q = QUIESCENT POINT ($i_i = 0$)

$$\Rightarrow i_b = I_B \Rightarrow i_c = I_C$$

HERE, $V_{CE} = I_C R_L - V_{BE} = 0$
 $V_{BE} \sim 0.7V \Rightarrow I_B = \frac{V_{CC} - 0.7}{R_B}$

APPLYING SIGNAL CURRENT: $i_b = I_B + i_i$

$$V_{CE} = V_{CC} - i_c R_L \leftarrow \text{LOAD LINE} \Rightarrow i_c = \frac{V_{CC} - V_{CE}}{R_L}$$

V. INTEGRATED CIRCUITS

A. FABRICATION

$$R = \frac{\rho}{t} \frac{L}{W} \approx R_s \frac{L}{W} \leftarrow \text{RESISTORS}$$



\leftarrow TYPICAL

$$C = \epsilon \frac{A}{t} \leftarrow \text{CAPACITANCE}$$


VI. PRACTICAL AMPLIFIERS

A. AMPLIFIER CLASSIFICATION

B. AMPLIFICATION AND DISTORTION

$$A_v = \frac{V_{out}}{V_{in}} = A e^{j\theta}$$

$A = A(f) \Rightarrow$ FREQUENCY DISTOR

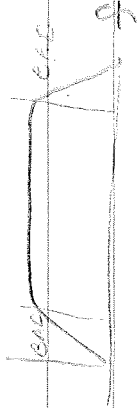

$\theta = \theta(f) \Rightarrow$ PHASE DISTORTION

AMPLITUDE DISTORTION (NON-LINEAR)

LINEAR SYSTEM THEORY



• LINEAR IF: $S[X_1(t) + X_2(t)] = S[X_1(t)] + S[X_2(t)]$

AND $S[aX(t)] = aS[X(t)]$

• TIME INVARIANT: IF $S[X(t)] = Y(t)$

$$S[X(t-\tau)] = Y(t-\tau)$$

• CAUSAL: THE OUTPUT DOES NOT DEPEND ON
NOT
SOMETHING THAT'S HAPPENED YET IN
THE INPUT.

FOR A LINEAR TIME INVARIANT SYSTEM:

$$Y(s) = T(s)X(s)$$

$$Y(s) = \mathcal{L}[Y(t)]$$

$$X(s) = \mathcal{L}[X(t)]$$

$T(s)$ = SYSTEM TRANSFER FUNCTION
= FREQUENCY RESPONSE

LAPLACE TRANSFORM REVIEW:

$$X(s) = \mathcal{L}[X(t)] = \int_0^{\infty} X(t) e^{-st} dt$$

$$X(t) = \mathcal{L}^{-1}[X(s)] = \int_0^{\infty} X(s) e^{st} dt$$

TABLE

$X(t)$ $X(s)$

$$aX_1(t) + bX_2(t) \quad aX_1(s) + bX_2(s)$$

$$\frac{d^n}{dt^n} X(t) = X^{(n)}(t) \quad s^n X(s) - s^{n-1} X(0^+) - \dots - X^{(n-1)}(0^+)$$

1/t

$$\frac{1}{s+a}$$

$$\frac{1}{s^2+a^2}$$

$$\frac{s}{s^2+a^2}$$

1/s


$$e^{-as}$$

$$\frac{1}{a} \sin at$$

$$\cos at$$

PHYSICALLY, WE INTERPRET $s = j\omega$

IMPEDANCES:

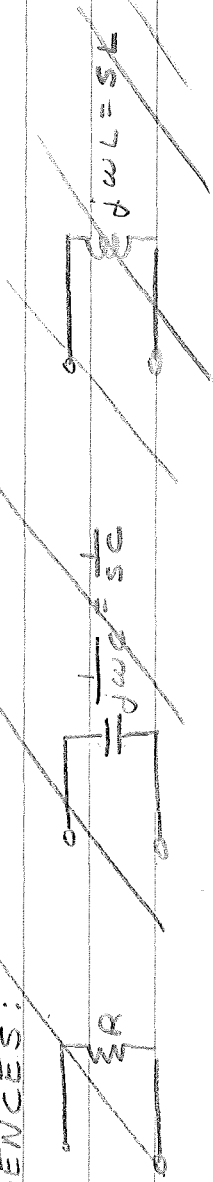

EXAMPLE: MOTOR

INPUT: LOAD OUTPUT: SPEED (COMPARED TO A FIXED SPEED)

$$T(s) = \frac{-1}{s+a}$$

SUPPOSE LOAD IS ABRUPTLY CHANGED

$$X(t) = b\mu(t) \Rightarrow X(s) = \frac{b}{s}$$



$$Y(s) = T(s)X(s)$$

$$= \frac{-b}{s(s+a)} = \frac{-b}{as} + \frac{b}{a(s+a)}$$

$$Y(t) = \frac{-b}{a} \mathcal{L}^{-1}\left[\frac{1}{s}\right] + \frac{b}{a} \mathcal{L}^{-1}\left[\frac{1}{s+a}\right]$$

$$= \frac{-b}{a} \left[\mu(t) - e^{-at} \right]$$

LOAD

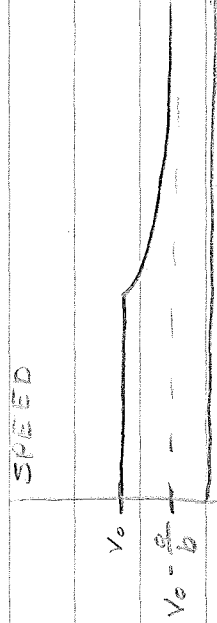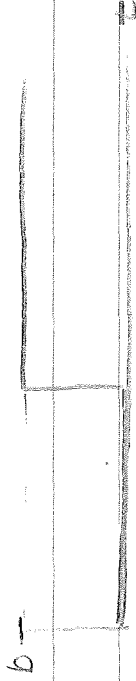


(FIG. 2.11 ON PG. 2-2 SHOULD LOOK LIKE THIS)

HERE, $a = \frac{1}{T}$, $T = \text{TIME CONSTANT}$

WE PHYSICALLY INTERPRET $s = j\omega$



EXAMPLE:

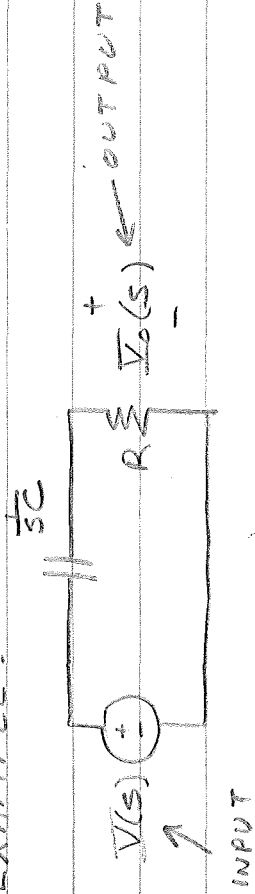

BY VOLTAGE DIVIDER


$$V_o(s) = \frac{R}{R + \frac{1}{sC}} V(s)$$

TRANSFER FUNCTION

$$= \frac{sR}{s + \frac{1}{RC}} V(s)$$

LET $V(t) = V_o(t) \Rightarrow V(s) = \frac{V_o}{s}$
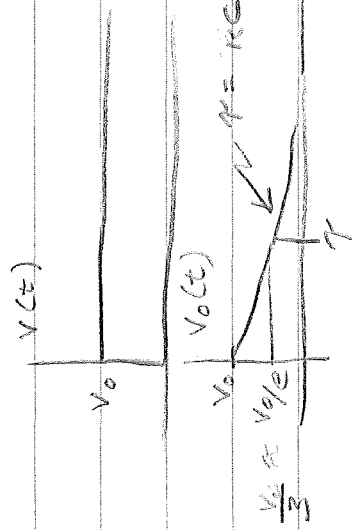
$$V_o(s) = \frac{V_o}{s + \frac{1}{RC}} \Rightarrow V_o(t) = V_o e^{-t/RC}$$



THE TRANSFER FUNCTION IS ALSO THE FREQUENCY RESPONSE.

IN PR. EXAMPLE:

$$T(s) = \frac{s}{s + RC}$$

$$T(j\omega) = \frac{j\omega}{j\omega + RC} =$$


$$|T(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + (RC)^2}}$$

$$|T(0)| = 0$$

$$|T(\infty)| = 1$$

$$|T(\omega = \frac{1}{RC})| = \frac{\frac{1}{RC}}{\sqrt{\frac{1}{(RC)^2} + (RC)^2}} = \frac{1}{\sqrt{2}} \leftarrow \text{HALF POWER POINT}$$

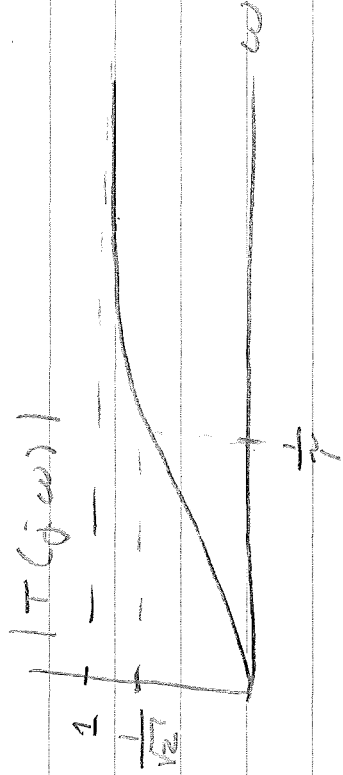HERE, HALF POWER POINT IS AT $\omega = \frac{1}{RC}$




SAMPLING RATES (MOTIVATE)

THE FOURIER TRANSFORM:

$$X(\omega) = \int_{-\infty}^{\infty} x(t) e^{-j\omega t} dt ; x(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} X(\omega) e^{j\omega t} d\omega$$

SOMETIMES SAME AS LAPLACE TRANSFORM WITH $S = j\omega$


EXAMPLES:

(1) $x(t) = \cos \omega_0 t \Rightarrow$ 



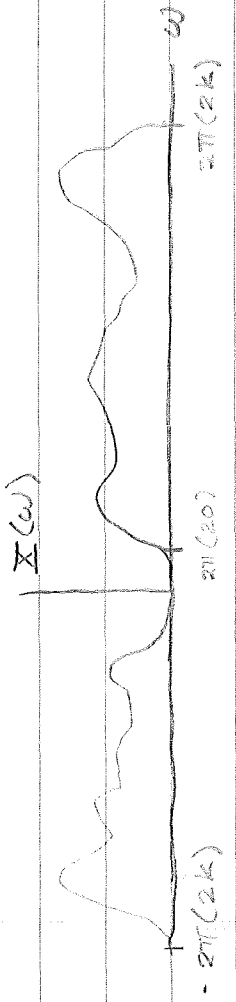(2) $x(t) = \cos^2 t = \frac{1}{2} + \frac{1}{2} \cos 2t$ ~~$x(t) = \cos^2 t$~~

AUDIO FREQUENCIES RANGE FROM ABOUT 20 HZ TO 20 KHZ




DEFN: A SIGNAL (FUNCTION) IS BANDLIMITED

IF IT'S FOURIER TRANSFORM HAS FINITE SUPPORT. THE INTERVAL OVER WHICH

THE FOURIER XFORM IS NON-ZERO


IS THE BANDWIDTH

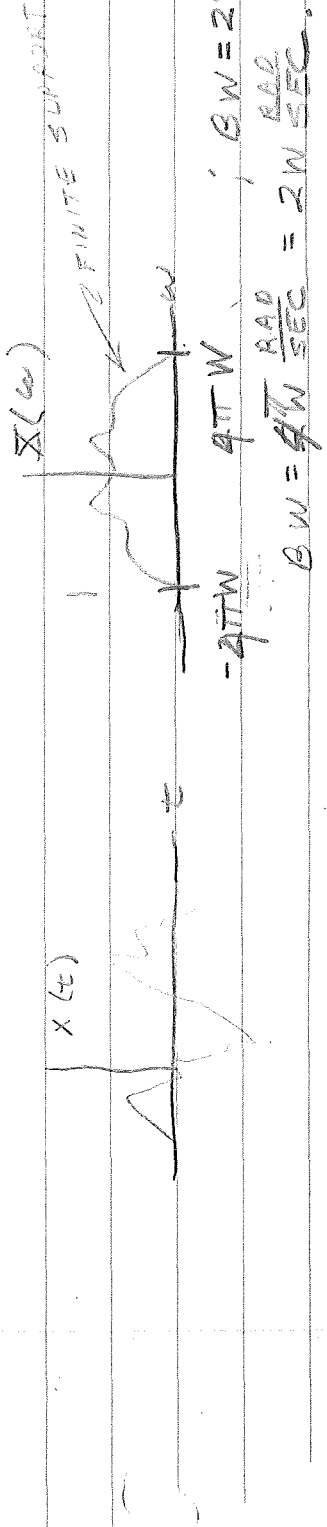


WHITTAKER-SHANNON SAMPLING THEOREM:

A BANDLIMITED FUNCTION, $x(t)$, CAN BE DETERMINED EXACTLY BY SAMPLING IT.

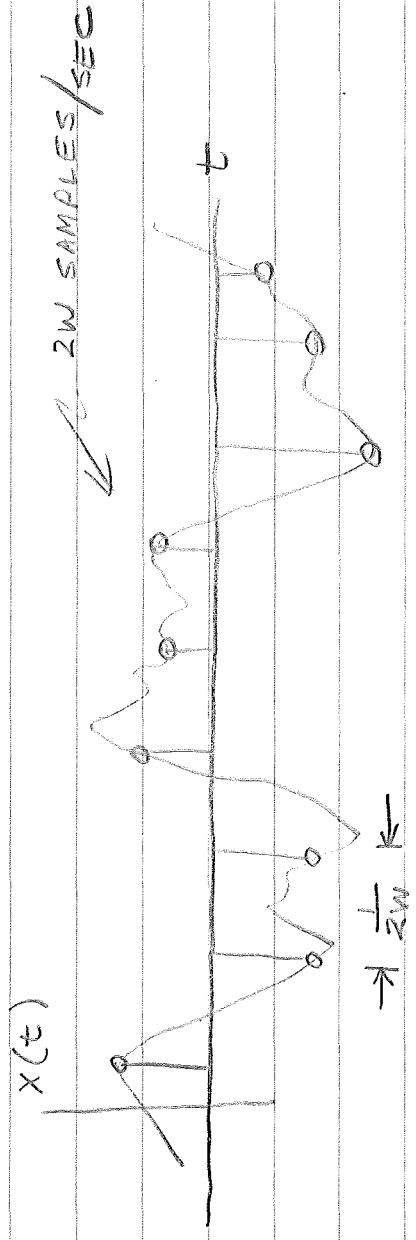AT A RATE EQUAL TO THE BANDWIDTH, (TWICE ITS HIGHEST FREQUENCY)




$x_s(t)$

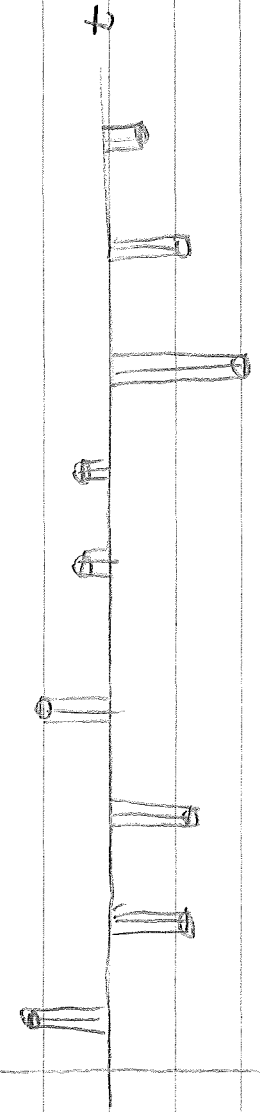


$x(t)$ IS RECOVERED BY PASSING $x_s(t)$ THRU

A LOW PASS FILTER OF BANDWIDTH RW

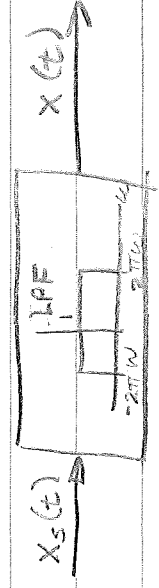


WHAT'S HAPPENING:

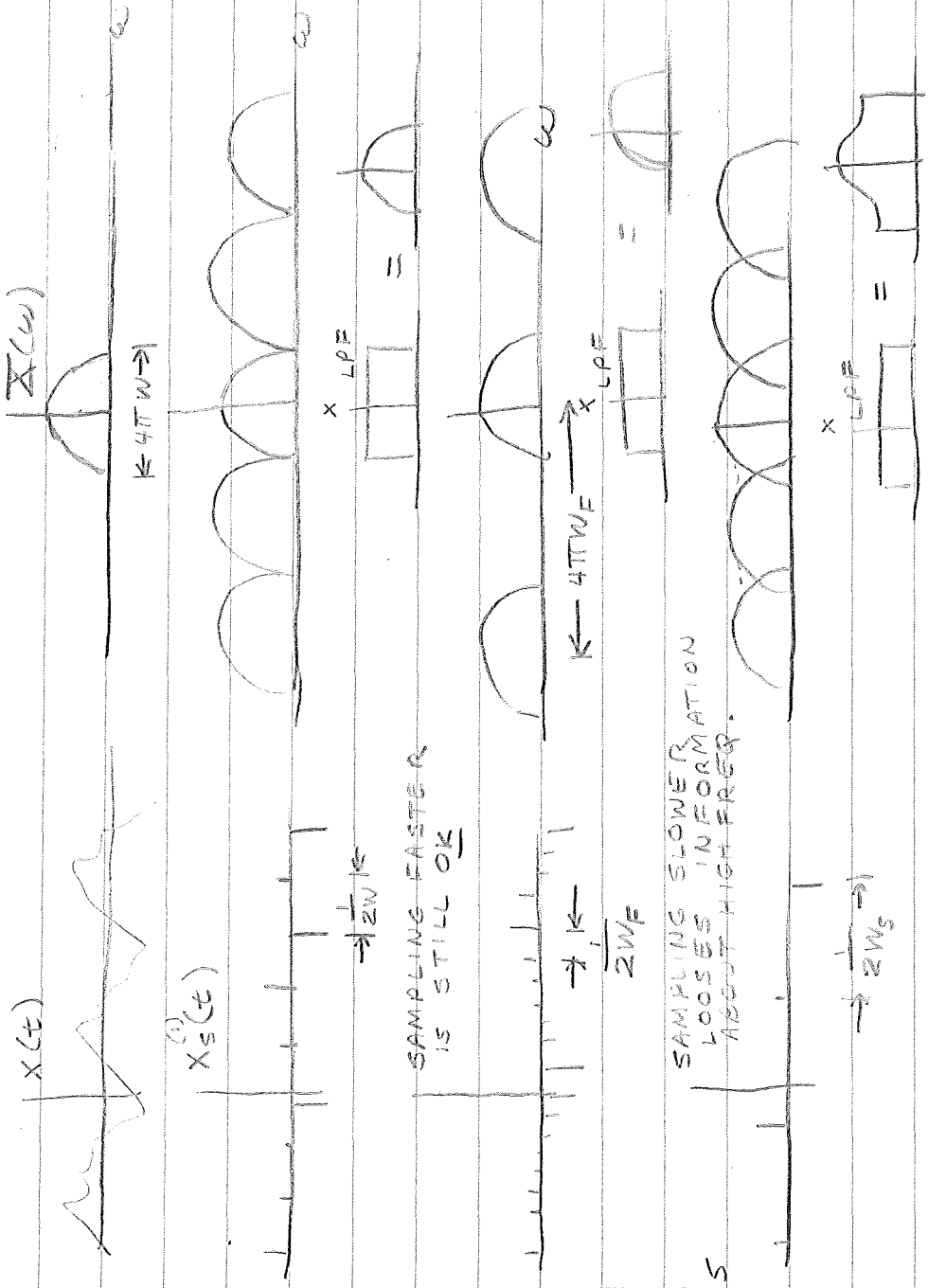

SAMPLES MAY BE INTERLACED

OIL WELLS

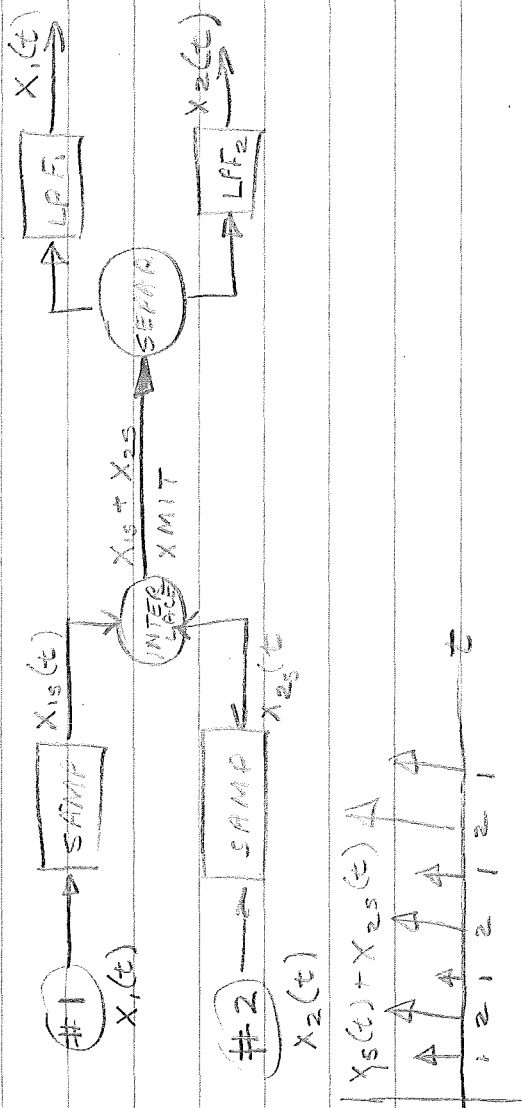

FOURIER SERIES

DEF: A SIGNAL $x(t)$ IS PERIODIC IF THERE EXISTS A $2T$ SUCH THAT $x(t) = x(t+2T)$ FOR ALL t , $2T = \text{PERIOD}$.

FOURIER SERIES: LET $x(t)$ BE PERIODIC WITH PERIOD T . THEN

$$x(t) = \sum_{n=-\infty}^{\infty} a_n e^{j2\pi n t/T}$$

WHERE

$$a_n = \frac{1}{T} \int_{2T} x(t) e^{-j2\pi n t/T} dt$$


ALTERNATE FORM:

$$x(t) = \frac{a_0}{2} + \sum_{n=1}^{\infty} a_n \cos \frac{n\pi t}{T} + b_n \sin \frac{n\pi t}{T}$$

$$\begin{cases} a_n = \frac{1}{T} \int_{2T} x(t) \cos \frac{n\pi t}{T} dt \\ b_n = \frac{1}{T} \int_{2T} x(t) \sin \frac{n\pi t}{T} dt \end{cases}$$

$$a_n = \begin{cases} \frac{1}{2} (a_n - j b_n) & ; n > 0 \\ \frac{1}{2} (a_{-n} + j b_{-n}) & ; n < 0 \\ \frac{1}{2} a_0 & ; n = 0 \end{cases}$$

EXAMPLE: HALF WAVE RECTIFIER OUTPUT:

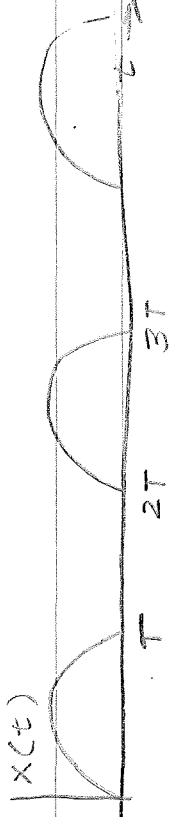

$$x(t) = \begin{cases} \sin \frac{2\pi t}{T} & ; 0 < t < T \\ 0 & ; T < t < 2T \end{cases}$$

$$x(t) = x(t - 2T)$$

$$\alpha_n = \frac{1}{T} \left[\int_0^T \sin \frac{\pi t}{T} e^{-j2\pi n t/T} dt + \int_T^{2T} (0) e^{-j2\pi n t/T} dt \right]$$

$$= \frac{1}{T} \int_0^T \sin \frac{\pi t}{T} e^{-j2\pi n t/T} dt$$

$$= \frac{1}{T} \int_0^T \frac{1}{j2} \left[e^{j\frac{\pi t}{T}} - e^{-j\frac{\pi t}{T}} \right] e^{-j2\pi n t/T} dt$$

$$= \frac{1}{j2T} \left[\int_0^T e^{j\frac{\pi t}{T} [1-2n]} dt - \int_0^T e^{-j\frac{\pi t}{T} [1+2n]} dt \right]$$

$$= \frac{1}{j2T} \left[\frac{T}{j\pi(1-2n)} e^{j\frac{\pi t}{T} (1-2n)} \Big|_0^T - \frac{T}{j\pi(1+2n)} e^{-j\frac{\pi t}{T} (1+2n)} \Big|_0^T \right]$$

$$= \frac{1}{j2T} \left[\frac{T}{j\pi(1-2n)} (e^{-j\pi(1-2n)} - 1) - \frac{T}{j\pi(1+2n)} (e^{j\pi(1+2n)} - 1) \right]$$

$$= \frac{1}{j2T} \left[\frac{T}{j\pi(1-2n)} (e^{-j\pi(1-2n)} - 1) - \frac{T}{j\pi(1+2n)} (e^{j\pi(1+2n)} - 1) \right]$$


BUT $e^{j\pi(1+2n)} = (-1)^{1+2n} = (-1)^{2n+1} = -1$

$$\Rightarrow \alpha_n = \frac{1}{j2T} \left[\frac{T}{j\pi(1-2n)} + \frac{T}{j\pi(1+2n)} \right]$$

$$= \frac{1}{\pi} \left[\frac{1}{1-2n} + \frac{1}{1+2n} \right] = \frac{2}{\pi(1-2n)(1+2n)}$$


$$\Rightarrow X(t) = \sum_{n=-\infty}^{\infty} \frac{2}{\pi(1-2n)(1+2n)} e^{j2\pi n t/T}$$

HARMONIC SPECTRA:

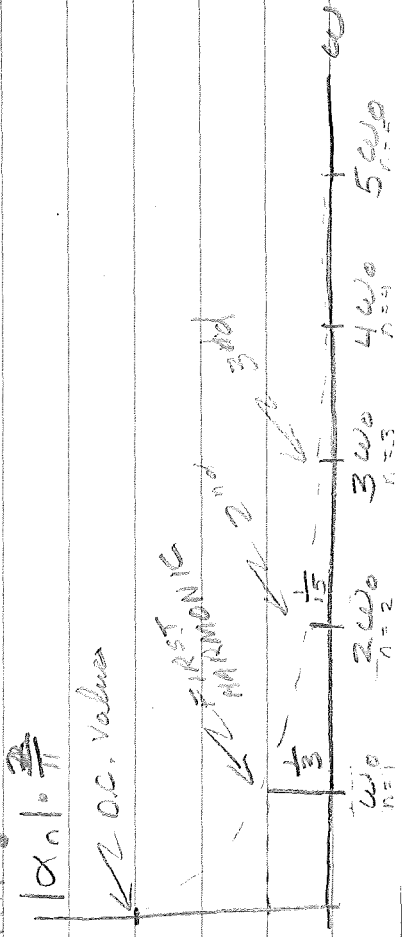

RELIABILITY

BATH TUB CURVE

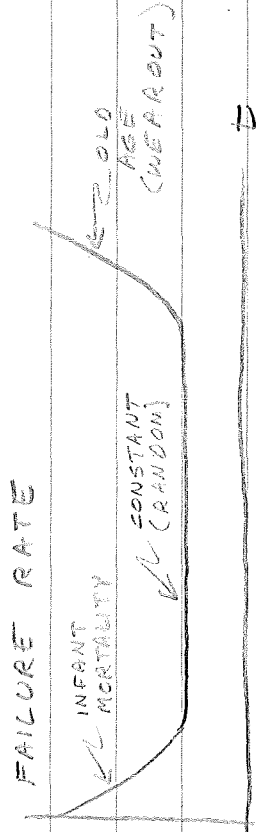

RELIABILITY: THE PROBABILITY THAT A GIVEN


UNIT WILL BE OPERABLE AT A GIVEN

TIME t

MTBF = MEAN TIME BETWEEN FAILURES

(A RELIABILITY MEASURE) = $\frac{\text{TEST TIME}}{\# \text{ OF FAILURES}}$

EXAMPLE:

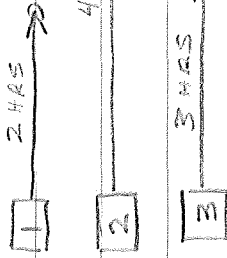

$$\text{MTBF} = \frac{2 + 4 + 3}{3} = 3 \text{ HRS}$$

ON THE CONSTANT PART OF BATH TUB CURVE

$$R(t) = e^{-\frac{t}{\text{MTBF}}}; t > 0$$

EX. A UNIT HAS A MTBF = 2 YEARS. WHAT


IS THE PROB IT WILL BE FUNCTIONAL

AFTER 16 YEARS OF USE?

$$R(16 \text{ YEARS}) = e^{-\frac{16}{2}} = e^{-8} = 0.00033$$

OR 1 CHANCE IN $e^8 = 2981$

2. PARALLEL CONNECTION

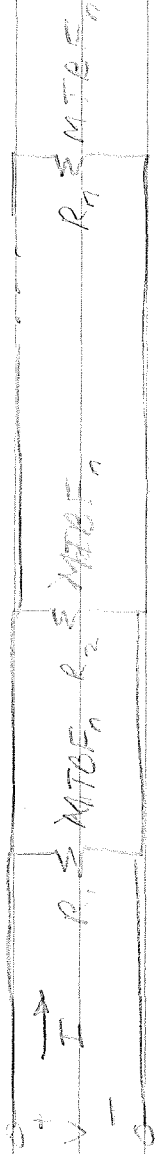

HERE, LET OPERABLE MEAN THAT A CURRENT HAS A PATH TO FLOW
(IN FAILURE \Rightarrow ALL RESISTORS OPEN)

$$MTBF_{sys} = \sum_{k=1}^n MTBF_k$$

$$\frac{1}{\lambda_{sys}} = \sum_{k=1}^n \frac{1}{\lambda_k}$$

PARALLEL (OR REDUNDANT) CONNECTIONS
INCREASE RELIABILITY

EXAMPLE: THE MTBF OF UNIT IS 2 YEARS.

HOW MANY UNITS SHOULD YOU BUY IF YOU WANT AT LEAST A 50% CHANCE AT LEAST ONE UNIT WILL BE RUNNING 10 YEARS

FROM NOW? (ASSUME NO MAINTENANCE) $MTBF = n \cdot MTBF_0 = 20$

$$R_3(t) = e^{-t/MTBF_3} = 0.5$$

$$R_3(10) = e^{-10/2n} = e^{-5/n} = 0.5$$

$$-5/n = \ln 0.5$$

$$\Rightarrow n = -5 / \ln 0.5 = \frac{-5}{-0.693} = 7.2$$

\therefore AT LEAST 8 UNITS

NOTE: IN REDUNDANT CONFIGURATION, YOU CAN PERFORM "PREV. MAINTENANCE" ON FAILED UNITS WHILE SYSTEM IS STILL "OPERABLE", THUS, GREATLY INCREASING MTBF


EX A MOTOR IS RUN OFF TWO HAMSTERS.

(MTBF = 20 YRS) AND A MAN CRANKING

A HANDLE, (MTBF = 30 YRS), IF EITHER THE HAMSTERS

OR THE MAN CAN RUN THE MOTOR,

HOW DOES THE SYSTEM MTBF?

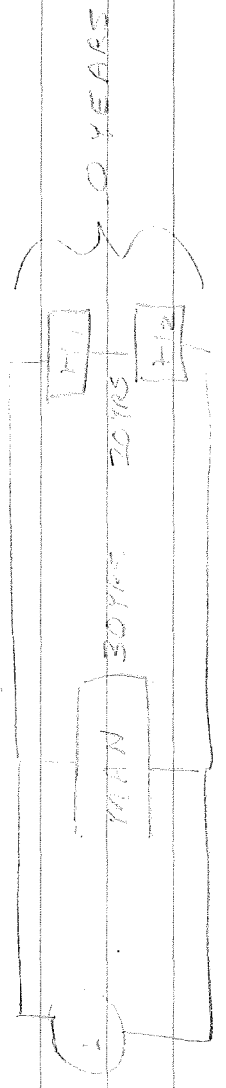


MTBF = 40 YEARS

SYSTEM VS UNIT RELIABILITY

[FOR A SYSTEM, WE MUST DEFINE WHAT WE MEAN BY "OPERABLE" TO COMPUTE MTBF]

1. SERIES CONNECTION:

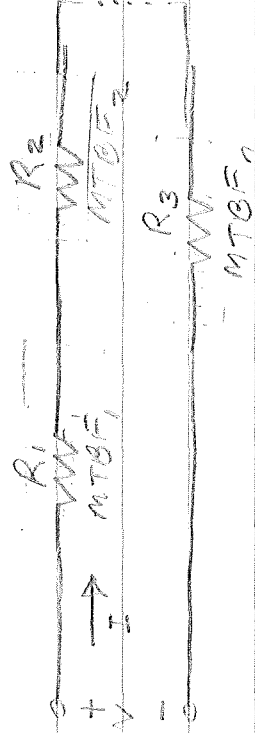


HERE, LET OPERABLE MEAN THAT A CURRENT IS FLOWING (THUS A FAILURE MEANS A RESISTOR HAS BLOWN) (OPEN CIRCUIT) [SHORT CIRCUIT FAILURE NOT CONSIDERED]

$$\frac{1}{MTBF_{SYSTEM}} = \sum_{k=1}^n \frac{1}{MTBF_k}$$

$$\lambda = \frac{1}{MTBF} = \text{FAILURE RATE}; \quad \lambda_{SYS} = \sum_{k=1}^n \lambda_k$$

EXAMPLE

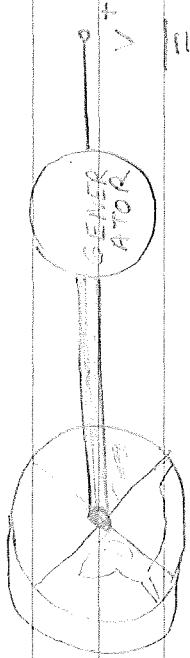

$$MTBF_{MOTOR} = 2 \text{ YEARS}$$

$$MTBF_{GEAR} = 50 \text{ YEARS}$$

$$MTBF_{GEN} = 1000 \text{ YEARS}$$

$$MTBF_{GEN} = 3 \text{ YEARS}$$

$$\lambda_{SYS} = \frac{1}{MTBF_{SYS}} = \frac{1}{2} + \frac{1}{50} + \frac{1}{1000} + \frac{1}{3} = 0.854 / \text{YR} = \lambda_k$$

$$\Rightarrow MTBF_{SYS} = 1.17 \text{ YEARS}$$

$$P[\text{LAST TWO YEARS}] = e^{-2/1.17} = 18.9\%$$

NOTE: SERIES TYPE CONNECTIONS REDUCE RELIABILITY

MAINTAINABILITY - GIVEN THAT A UNIT IS DOWN

② $t=0$, THE UNIT'S MAINTAINABILITY IS THE PROBABILITY THAT IT WILL BE FIXED AT TIME $= t$.

MTTR = MEAN TIME TO REPAIR
 $= \frac{\text{TOTAL DOWN TIME}}{\text{\# FAILURES}}$

EX



$$MTBF = \frac{6 \text{ YEARS}}{3 \text{ FAILURES}} = 2 \text{ YEARS}$$

$$MTTR = \frac{3 \text{ DAYS}}{3 \text{ FAILURES}} = 1 \text{ DAY}$$

AVAILABILITY - A MEASURE OF THE PERCENT OF TIME A UNIT IS OPERABLE

$$A = \frac{MTBF}{MTBF + MTTR}$$

FOR ABOVE EXAMPLE

$$A = \frac{2 \text{ YEARS}}{2 \text{ YEARS} + 1 \text{ DAY}} = \frac{730 \text{ DAYS}}{731 \text{ DAYS}} = 99.8639\%$$

TEST # 1 ON THURS.

[OPEN BOOK & NOTES, 1 HR.]
[5 PROBLEMS, 100 PTS]

(15)

1. RECTIFIERS, DIODE AND/OR FET (PERFORMANCE, WAVEFORM)

2. LINEAR SYSTEM REDUCTION

PROBLEM (15)

3. LAPLACE XFORM NETWORK SOLUTION AND/OR

FREQUENCY RESPONSE (25)

4. SYSTEM EFFECTIVENESS (RELIABILITY,

MAINTAINABILITY, ETC.) (25)

(20)

5. SAMPLING THEOREM AND/OR FOURIER SERIES

CORRECT SOLUTION

$$\frac{\sum_{n=0}^{\infty} a^n}{1-a} = \begin{cases} 1 & ; a=0 \\ 0 & ; \text{OTHERWISE} \end{cases}$$

ALSO, MTR IS REDUCED, NOT THE SAME

III. TRANSISTOR BIASING CIRCUITS


PURPOSE: ESTABLISH AND MAINTAIN PROPER

OPERATING POINTS

A. FET BIASING

LINEAR

- AN IDEALY AMPLIFIER (p. 274 SMITH)

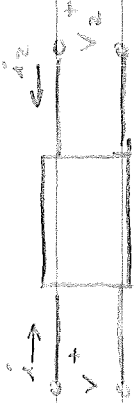


i_2 $V_3 = 3$

$V_1 = 2$

$V_1 = 1$


V_2

i_2 DEPENDS ONLY ON INPUT VOLTAGE

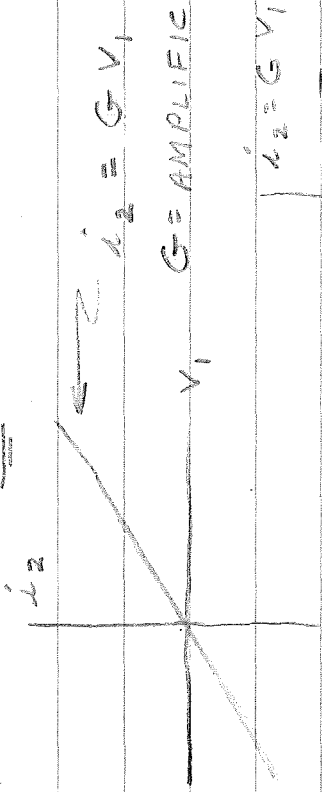

$G =$ AMPLIFICATION (IN MHOS)

$i_2 = G V_1$

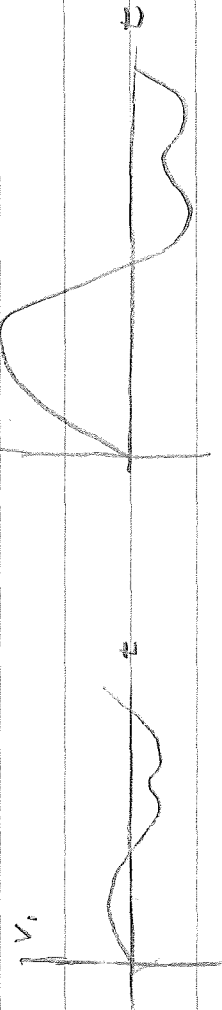


THIS TRANSODDER TAKES AN INPUT VOLTAGE AND OUTPUTS A AMPLIFIED CURRENT.

1. DE MOSFET BIASING

(DEPLETION OR ENHANCEMENT MODE


METAL-OXIDE-SEMICONDUCTOR FET (SMITH P. 337)

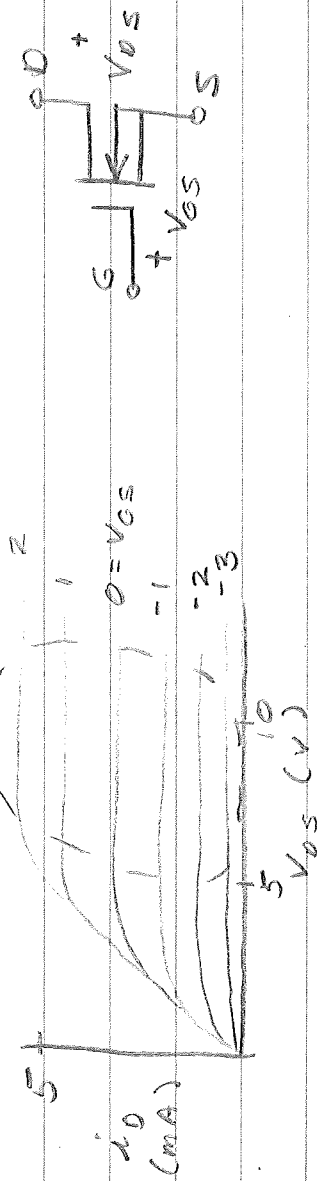V-I CURVE ← IDEAL AMP REGION (P. 414 SMITH)



WE MUST ESTABLISH "QUIESCENT" OR "NO SIGNAL" CONDITION IN IDEAL AMP REGION.


A BIASING CIRCUIT:

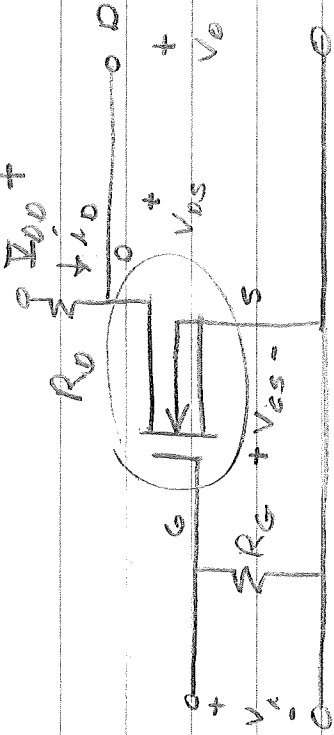


FOR DE MOSFET WE MAY ALLOW $V_{GS} = 0$ FROM CURVE, $I_{DQ} = 2\text{mA}$ FOR $V_{GS} = 0$ AND $V_{DS} > 4\text{VOLTS}$ AS QUIESCENT POINT. CHOICE OF R_D GIVES

QUIESCENT V_{DS} AS $V_{DS} = V_{DD} - R_D I_{DQ}$.


IN GENERAL

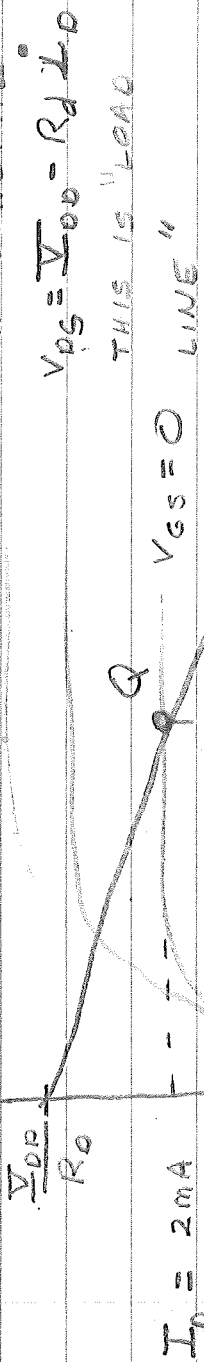

$I_{DQ} = 2\text{mA}$

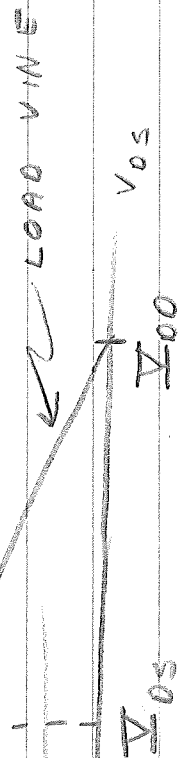


2. JFET BIASING (p. 415)

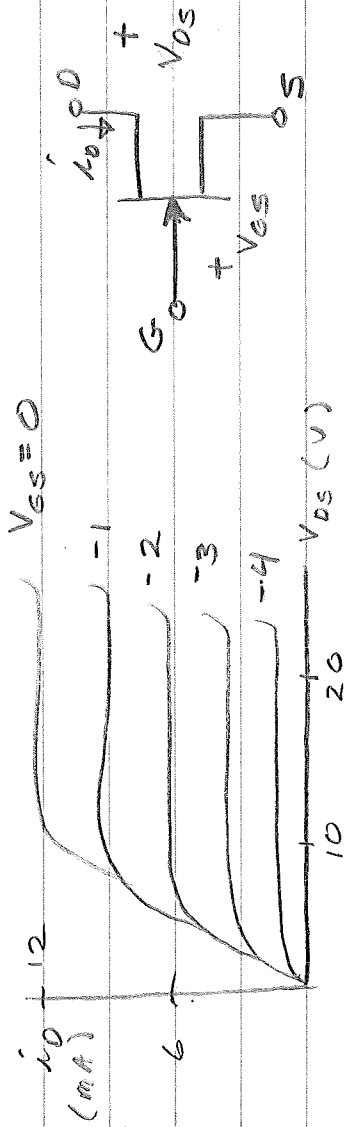


MORE COMPLICATED, SINCE $V_{GS} < 0$, MUST PUT

V_{GS} ON A "BIAS"

INPUT + BIAS = V_{GS}

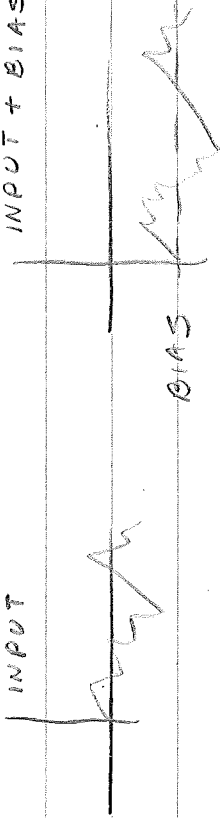

A BIASING CIRCUIT:

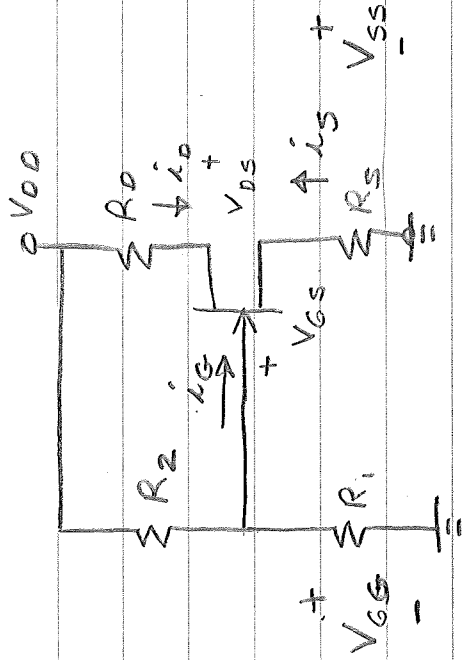

ANALYSIS

1. GATE CURRENT, (i_g) IS SMALL

(a) THUS, SINCE $i_g + i_s + i_d = 0 \Rightarrow i_s \approx -i_d$

AND $V_{SS} \approx R_s i_d$

(b) R_1 & R_2 FORM A VOLTAGE DIVIDER:

$$V_{GG} = \frac{R_2}{R_1 + R_2} V_{DD}$$


2. SUMMING VOLTAGES AROUND LOOP

$$V_{GG} - V_{SS} - V_{GS} = 0 \Rightarrow V_{GG} - V_{SS} - V_{GS} = 0$$

$$\Rightarrow V_{GS} = \frac{R_1}{R_1 + R_2} V_{DD} - R_s i_d$$

WE MAY ESTABLISH QUIESCENCE WITH THIS RELATIONSHIP. USUALLY, $V_{GG} \gg$

EX

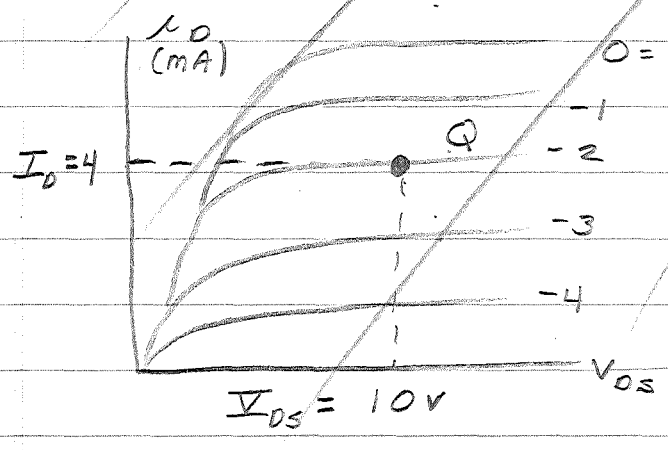

WE WISH TO ESTABLISH Q AT $V_{GS} = 2$ V $\Rightarrow I_D = 4$ mA

$$\text{OR } I_D = \frac{V_{GG} - V_{GS}}{R_S}$$

3. TO ESTABLISH QUIESCENCE,

CHOOSE (I_D, V_{GS}) ON CURVE. ALSO,

SPECIFY A BIAS, V_{GG} . WE WISH

TO KEEP THE INPUT RESISTANCE

HIGH, SO CHOOSE $R_G = R_1 // R_2 = \frac{R_1 R_2}{R_1 + R_2}$
TO BE "HI"


OUR EQUATIONS ARE THEN (H.W)

$$R_S = \frac{V_{GG} - V_{GS}}{I_D}$$

$$R_2 = R_G \frac{V_{GS}}{V_{GG}}$$

$$R_1 = R_G R_2 / (R_2 - R_G)$$

BJT

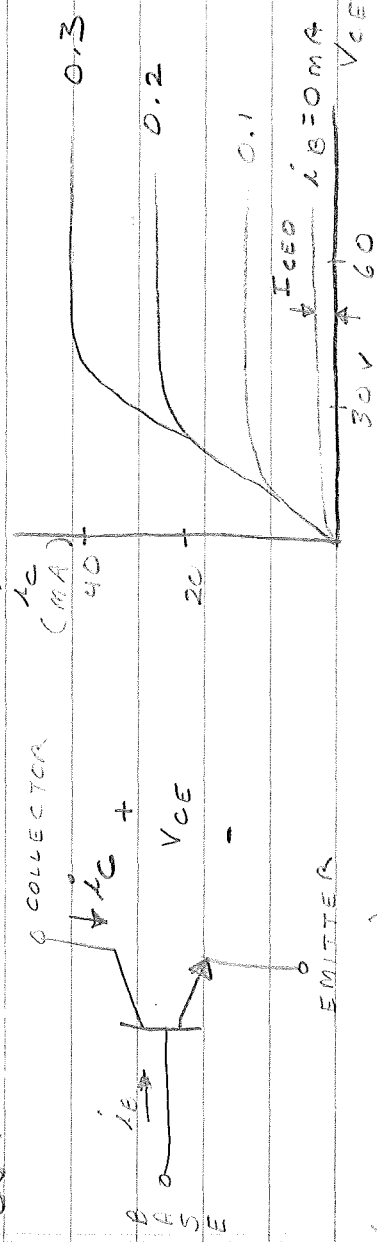

(PARTS OF SMITH)

$I_{CE0} = I_C$ WHEN COLLECTOR EMITTER JUNCTION IS OPEN

$I_{CB0} = I_E$ " " " " " " " " " " " "

$I_{CE0} = (1 + \beta) I_{CB0}$


$\beta =$ "CURRENT TRANSFER RATIO"

$\alpha =$ "FORWARD CURRENT XFER RATIO"

$\beta = \frac{\alpha}{1 - \alpha}$ $0 < \alpha < 1$

IN LINEAR PART OF XISTOR CURVE: $I_C = \beta I_B + I_{CE0}$

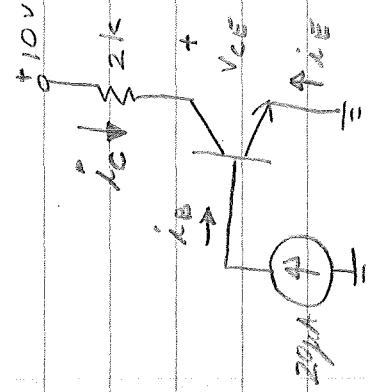EX $\beta = 99$, $I_{CB0} = 10^{-10}$ AMPS (10 V PUTS US ON LIN PART)



$I_{CE0} = (1 + \beta) I_{CB0} = 10^{-9} A$

$I_C = \beta I_B + I_{CE0}$

$= (99)(20 \times 10^{-6}) + 10^{-9} = 1.98 mA$

FIND I_E :

FROM K'NODE LAW

$I_E = (I_B + I_C)$

$= - (20 \times 10^{-6} + 1.98 \times 10^{-3}) = -2 mA$

FIND V_{CE}

FROM K'S V LAW:

$V_{CE} = 10 - I_C R_C = 10 - (2 mA) \times 2 k \Omega = 6 V$


NECESSARY THAT

* COLLECTOR - BASE JUNCTION REVERSED BIASED

EMITTER " " "

FORWARD BIASED

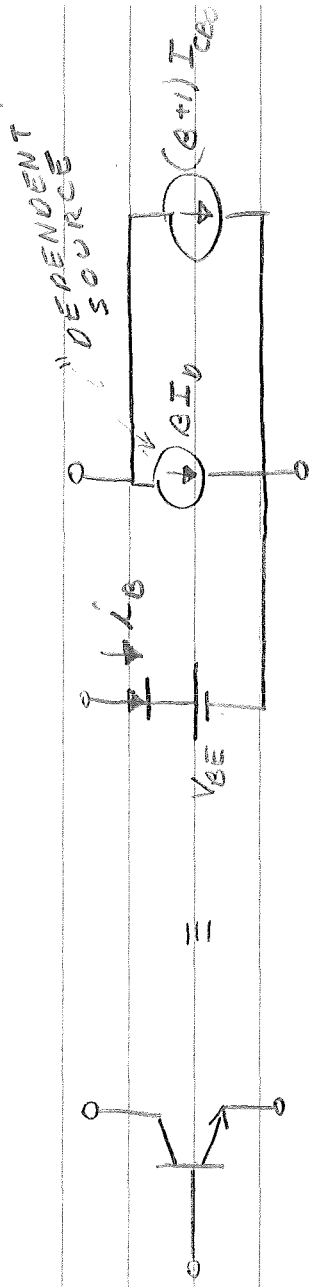IN LINEAR REGION, WE MAY REPLACE
TRANSISTOR WITH "DC MODEL"




$V_{BE} = \text{"DROOP" ACROSS FORWARD BIASED P-N JUNCTION}$

$\approx 0.7 \text{ V FOR Si}$

BJT BIASING (p. 412)

- FIXED CURRENT BIAS

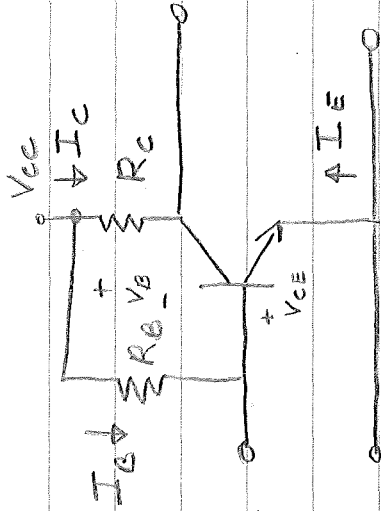
EMITTER JUNCTION FORWARD BIASED $\Rightarrow V_{CE} \approx 0$ (ACTUALLY, $V_{CE} \approx 0.7V$ FOR SILICON)

$$\Rightarrow V_B \approx V_{CC} \text{ AND } I_B = \frac{V_{CC}}{R_B}$$

$$I_C = \beta I_B + I_{CEO}$$

PARAMETERS VARY WIDELY WITH TEMP / β CHANGES FROM UNIT TO UNIT
THERMAL RUNAWAY: I_C INCREASES TEMP INCREASES I_C ... pow.

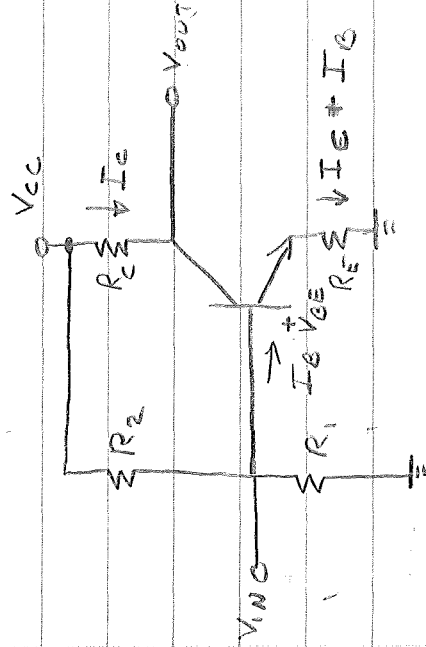- SELF BIAS (REDUCES EFFECTS OF β AND TEMP ON QUIESCENT OPER. POINT)




OPERATION (CHARACTERISTIC)

I_C TRIES TO INCREASE $\Rightarrow I_C + I_B$ INCREASES

\Rightarrow VOLTAGE ACROSS R_E INCREASES $\Rightarrow V_{BE}$ DECREASES


$\Rightarrow I_B$ REDUCED $\Rightarrow I_C = \beta I_B + I_{CEO}$ REDUCED

QUANTITATIVE:

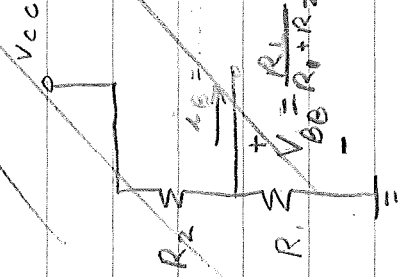

$$V_{BE} = \frac{R_1}{R_1 + R_2} V_{CC} = \frac{R_1}{R_1 + R_2} V_{CC} = \frac{R_1}{R_1 + R_2} V_{CC}$$

QUANTITATIVE:

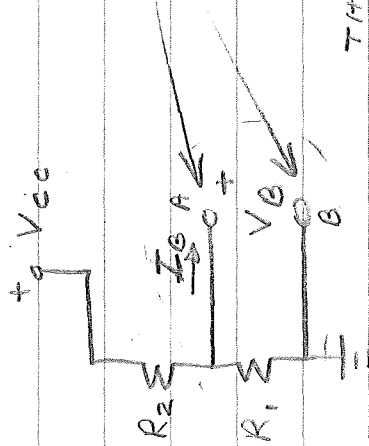


FIND THEVENIN EQUIVALENT FOR THIS PORT

THEVENIN:


$V_{OC} = \frac{R_1}{R_1 + R_2} V_{CC}$ (OPEN CIRCUIT VOLTAGE)

$I_{SC} = \frac{V_{CC}}{R_2} \Rightarrow R_{\theta} = \frac{V_{OC}}{I_{SC}} = \frac{R_1 R_2}{R_1 + R_2} = R_1 || R_2$

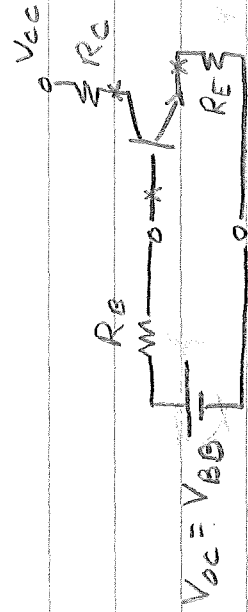
$\Rightarrow V_{\theta} = V_{OC} + R_{\theta} I_b$



REPLACE TRANSISTOR BY A "D.C. MODEL"

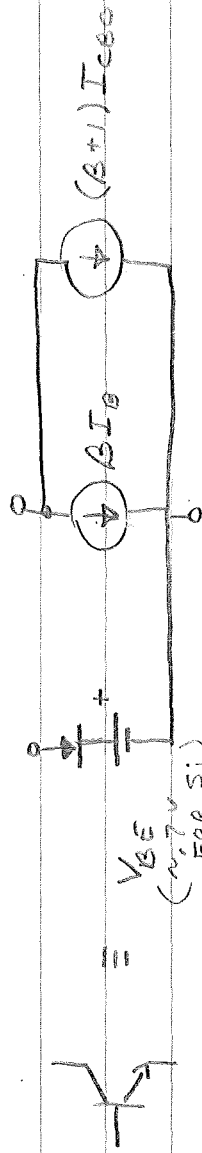

OUR CIRCUIT IS

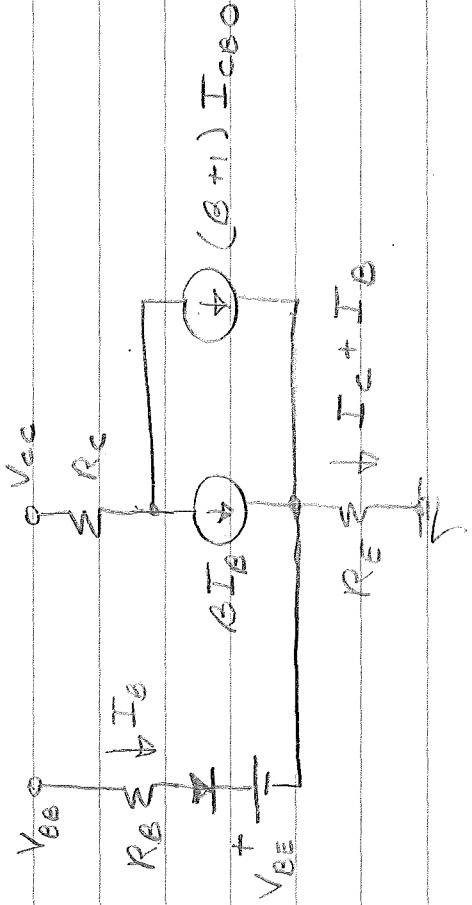

KIRCHOFF'S V LAW FROM V_{CE} DOWN IS:

$$V_{CE} - I_B R_B - V_{CE} - (I_C + I_B) R_E = 0 \quad (1)$$

SUMMING I @ NODE AT R_E :

$$I_B + \beta I_B + (1 + \beta) I_{CBO} = I_C + I_E$$

$$\Rightarrow I_B = \frac{I_C}{\beta} - \frac{\beta + 1}{\beta} I_{CBO} \quad (2)$$

SUBSTITUTING INTO (1) AND CRANKING:

$$I_C = \frac{V_{CE} - V_{CE} + \left(\frac{\beta + 1}{\beta}\right) I_{CBO} (R_B + R_E)}{R_E + \frac{R_B + R_E}{\beta}}$$

NOTE: V_{BE} , β , AND I_{CBO} ARE DEVICE PARAMETERS

$\frac{\beta + 1}{\beta} \approx 1$ FOR LARGE β

$$\text{NUM} \quad V_{CE} - V_{CE} \gg \left(\frac{\beta + 1}{\beta}\right) I_{CBO} (R_B + R_E) \leftarrow \text{NUM}$$

$$\approx I_{CBO} (R_B + R_E)$$

DEN


$$\text{MAKE} \quad \frac{R_B + R_E}{\beta} \ll R_E$$

$$R_B + R_E \ll \beta R_E$$


$$R_B \ll (\beta - 1) R_E \approx \beta R_E$$

$$R_B / R_E \ll \beta$$


POWER AMPLIFIERS

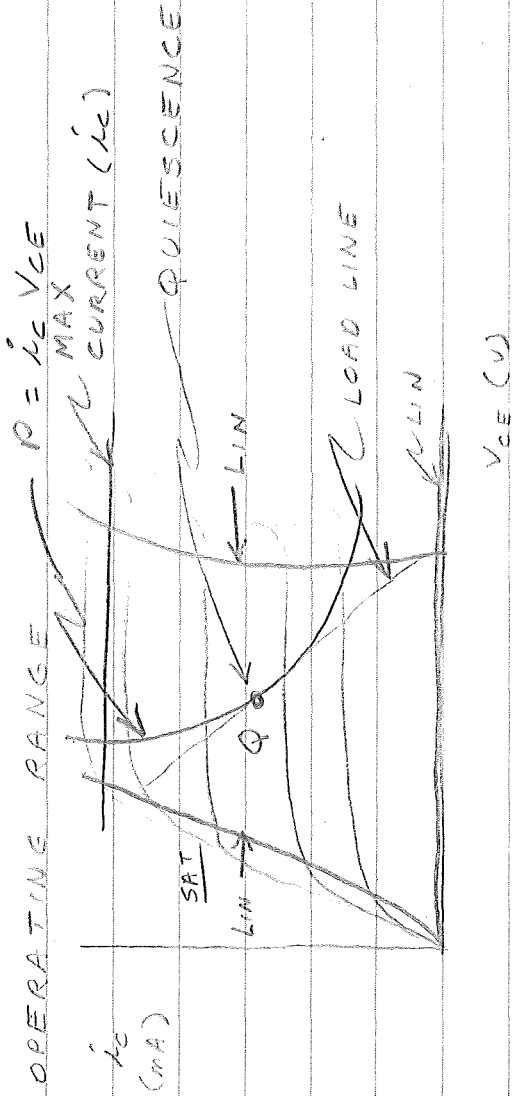

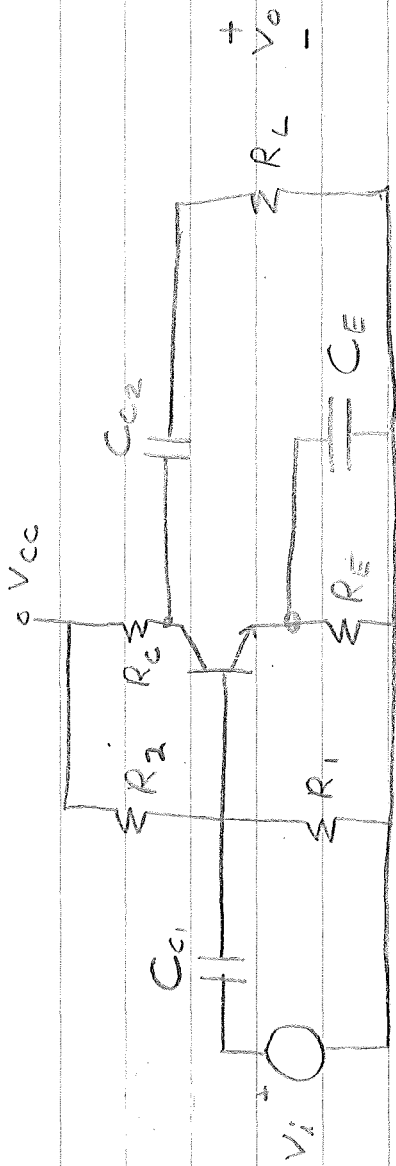
IS BEST TO PLACE Q ON PWR HYPERBOLA
AND HAVE LOAD LINE TANGENT
A LARGE SCALE AMP



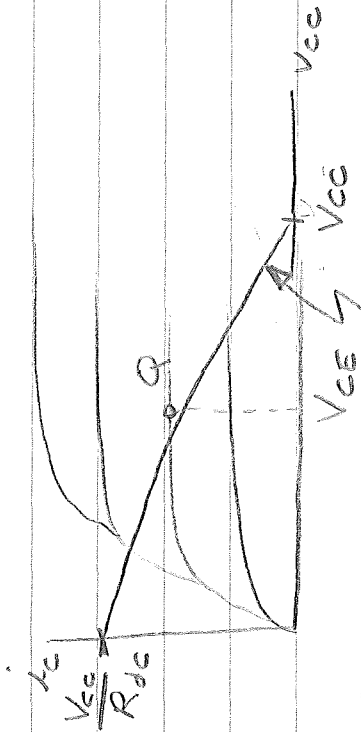PURPOSE OF C'S IS TO ALLOW SIGNAL & BIAS
VOLTAGES TO OPERATE INDEPENDENTLY
RULE OF THUMB: ASSUME C'S "LARGE"
DC \Rightarrow C'S ARE "OPEN CIRCUITS"
AC (SIGNAL) \Rightarrow C'S ARE SHORT



D.C. LOAD LINE:

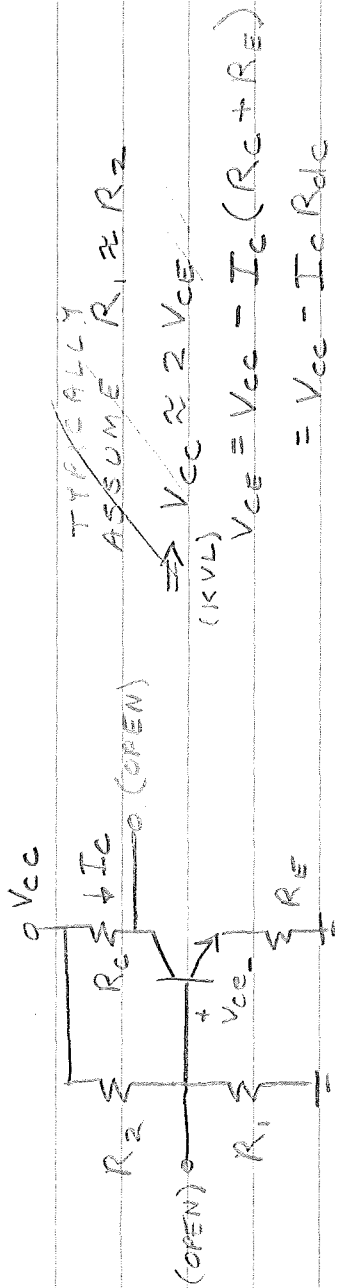


TYPICALLY
ASSUME $R_1 \approx R_2$

(KVL) $\Rightarrow V_{CC} \approx 2 V_{CE}$
 $V_{CE} = V_{CC} - I_C (R_C + R_E)$
 $= V_{CC} - I_C R_{DC}$


(D.C. CIRCUIT)

A.C. LOAD LINE

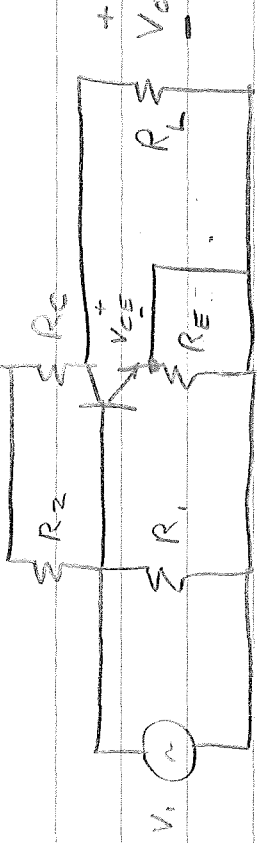

ANY A.C. SIGNAL ON R_C MUST ALSO APPEAR

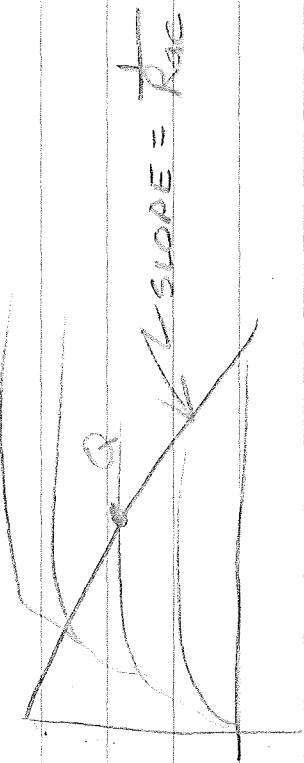ACROSS R_L (OR, IN A.C. UPPER END OF R_C IS GROUND) $\Rightarrow R_{AC} = R_C \parallel R_L = \frac{R_C R_L}{R_C + R_L}$




TRANSDUCER: TRANSFORMS ONE TYPE OF INFORMATION OR SIGNAL INTO ANOTHER TYPE

INSTRUMENTATION TRANSDUCERS (p. 722 SMITH) (3.5, 3.15 VIMOT)

{ ANALOG VS DIGITAL }
{ ACTIVE VS PASSIVE }


EXAMPLES: (1) FIRE/HEAT DETECTORS (DIGITAL)

FIRE, STAGES:

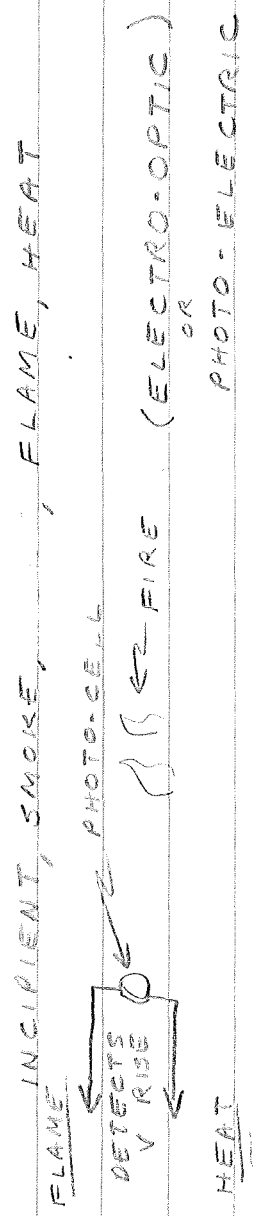


OTHER TRANSDUCER MEDIUMS

PIEZOELECTRIC

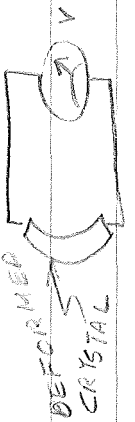


ELECTROMAGNETIC

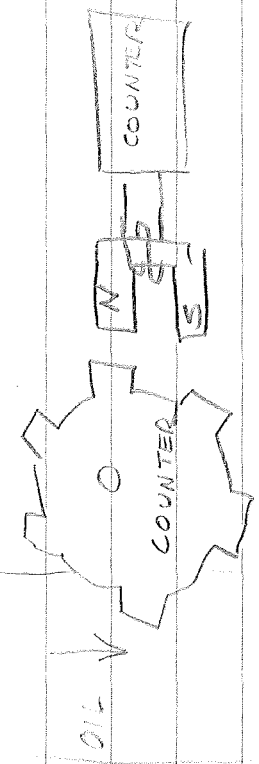

RESISTANCE DETECTION (STRAIN GAGES)

WHEATSTONE BRIDGE (MEASURES VERY ACCURATE R)

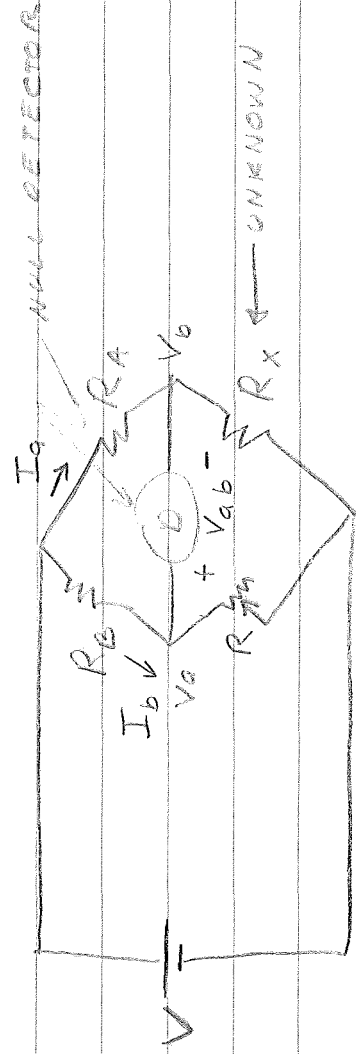FOR BALANCE, $V_a = V_b = 0$

$$\Rightarrow V_a = V_b$$

$$\text{THUS } R_B I_B = I_A R_A$$

$$R I_B = I_A R_X$$

$$\text{DIVIDING } \Rightarrow R_X = R \frac{R_A}{R_B} \quad (\text{NOTES (V IND)})$$

EXAMPLE

$$\left. \begin{array}{l} R_A = 500 \Omega \\ R_B = 5000 \Omega \end{array} \right\} 0.0176 \text{ RESISTORS}$$

R TUNED TO $270.4 \Omega \pm 0.02\%$

$$R_X = R \frac{R_A}{R_B} = 270.4 (1 \pm 0.0002) \frac{500 (1 \pm 0.0001)}{5000 (1 \pm 0.0001)}$$

FOR SMALL $X \neq Y$

$$\frac{1}{1 \pm X} \approx 1 \mp X$$

$$(1 + X)(1 + Y) = 1 + X + Y + XY \approx 1 + X + Y$$



 \Rightarrow WORST CASE ERROR

$$(1 \pm 0.0002)(1 \pm 0.0001)(1 \pm 0.0001)$$

$$\approx 1 + 0.0004$$

$$\Rightarrow R_X = 270.4 (1 \pm 0.0004) \Omega$$

STRAIN GAUGE TRANSDUCER

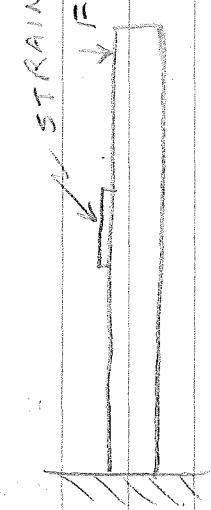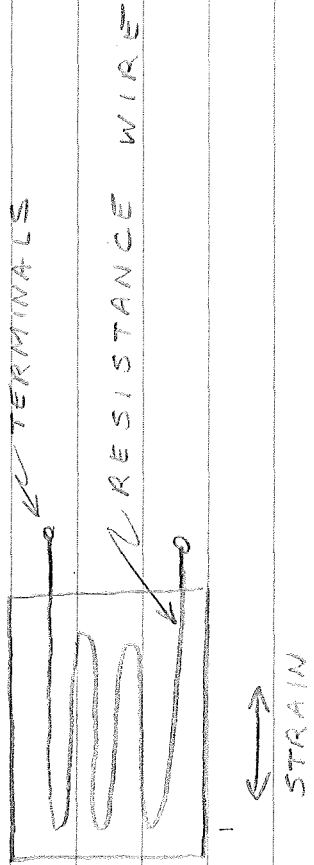

$$\frac{\Delta R}{R} = K_G \epsilon = K_G \frac{\Delta L}{L}$$

$K_G \approx 2-4$ (METALLIC)
(SEVERAL HUNDREDS (SEMICONDUCTOR))

K_G = GAUGE FACTOR


ϵ = STRAIN

$\frac{\Delta L}{L}$ = STRAIN

R, L = INITIAL RESISTANCE & LENGTH OF GAUGE

$R + \Delta R, L + \Delta L \Rightarrow R \approx L$ AFTER STRAIN

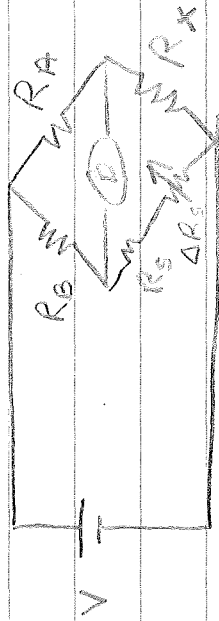ΔR IS SMALL, MEASURE IT WITH WHEATSTONE BRIDGE.




PROBLEM: R_x CHANGES WITH TEMP

SOLN: USE AN IDENTICAL STRAIN GAUGE

UNATTACHED TO BEAM AT SAME


TEMP FOR A REFERENCE

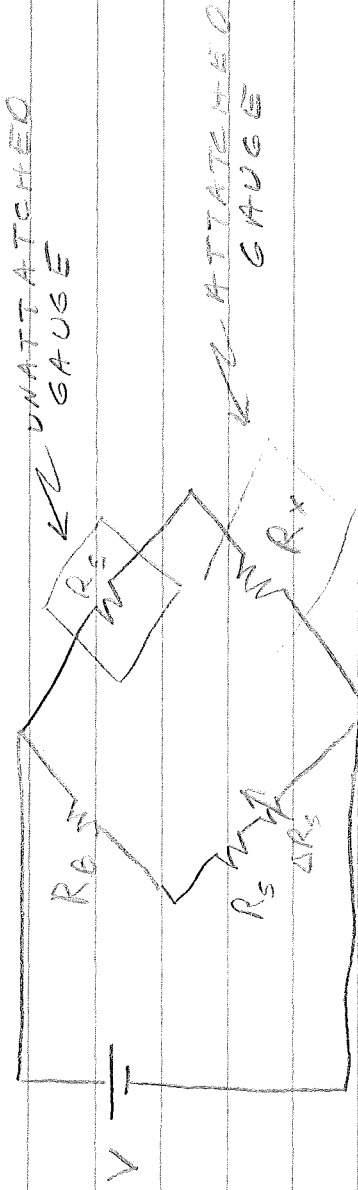

$$\Rightarrow R_x = (R_0 + \Delta R_1) \frac{R_2}{R_0}$$

SINCE R_x IS PROP TO R_2 , CHANGES IN R_x WILL BE COUNTERACTED BY CHANGES IN R_2 .

IMPEDANCE BRIDGE

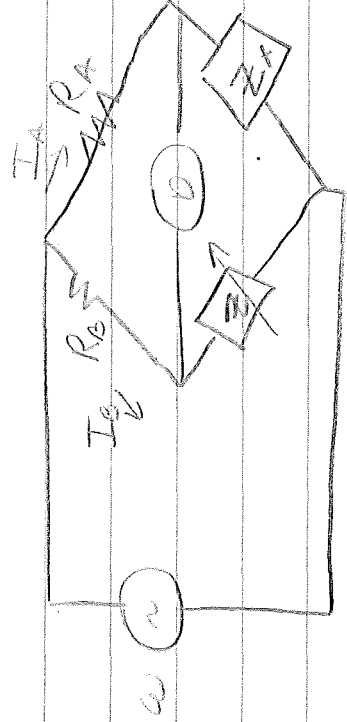


AT BALANCE: $R_B I_0 = I_A R_A$
 $Z I_0 = I_A Z_X$

THUS

$$Z_X = Z_{R_A/R_B}$$

EX:

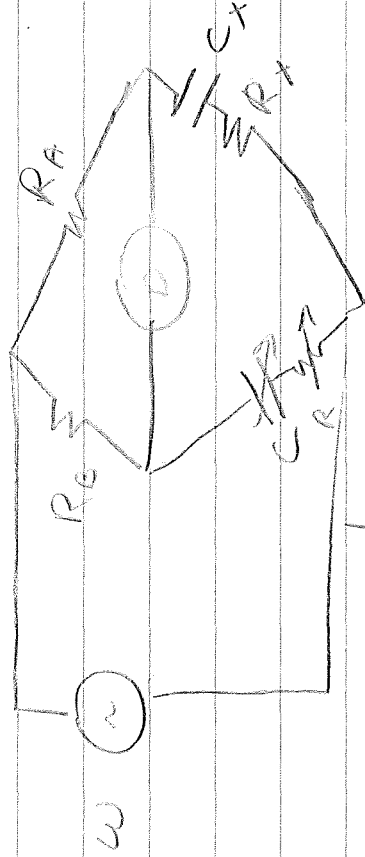

$$Z_X = R_X + \frac{j}{\omega C_X}$$

$$Z = R + \frac{j}{\omega C}$$

$$\Rightarrow R_X - \frac{j}{\omega C_X} = \left(R - \frac{j}{\omega C} \right) \frac{R_A/R_B}{R_B} = \frac{R R_A}{R_B} - j \frac{R_A/R_B}{\omega C}$$


EQUATING REAL & IMAG. PARTS

$$R_X = R \cdot R_A / R_B$$

$$C_X = C \cdot R_B / R_A$$

OPERATIONAL (OP) AMPS

IDEAL:

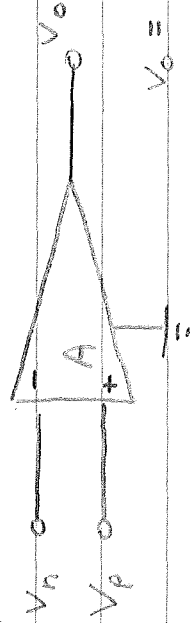

$$V_o = A (V_p - V_n)$$

$A = \infty$ (i_i , VERY LARGE)


$V_n = V_p \Rightarrow V_o = 0$

BANDWIDTH $\rightarrow \infty$ (i_o , DOES NOT DEPEND ON ω)

INPUT $Z = \infty$

OUTPUT $Z = 0$

BASIC INVERTING CIRCUIT:

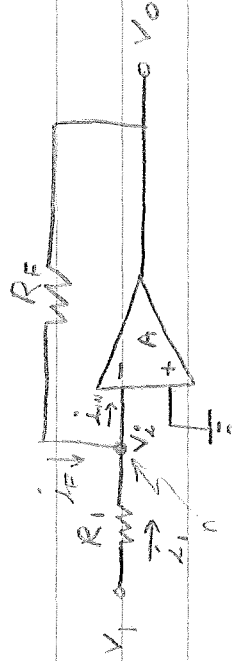

SINCE $Z_{in} = \infty$, $i_{in} = 0$

$$i_F = \frac{V_o - V_i}{R_F} = \frac{V_o - V_o/A}{R_F} = \frac{V_o}{R_F} \left(1 - \frac{1}{A}\right)$$

$$i_1 = \frac{V_1 - V_i}{R_1} = \frac{1}{R_F} \left(V_1 - \frac{V_o}{A}\right)$$

K'S NODE LAW

$$i_F + i_1 = 0 = \frac{V_i - V_o}{R_1} + \frac{V_o - V_i}{R_F} \quad (1)$$

$$V_i = V_o/A \quad (2)$$

SUBSTITUTE (2) INTO (1) AND SOLVE FOR V_o :

$$V_o = \frac{-V_1 (R_F/R_1)}{1 - (1/A) (1 + R_F/R_1)}$$

FOR $A = \infty$


$$V_o = -\frac{R_F}{R_1} V_1$$

THIS IS AMPLIFIER WITH VOLTAGE GAIN $-\frac{R_F}{R_1}$,


• $i_1 \approx \frac{V_1}{R_1}$ (IND. OF OUTPUT) (SINCE $V_1 \approx 0$)

• AMPLIFICATION, $A_F = -R_F/R_1$ IS IND. OF OP. AMP. GAIN, A. (OPERATION NOT AFFECTED BY TEMP. CHANGE)

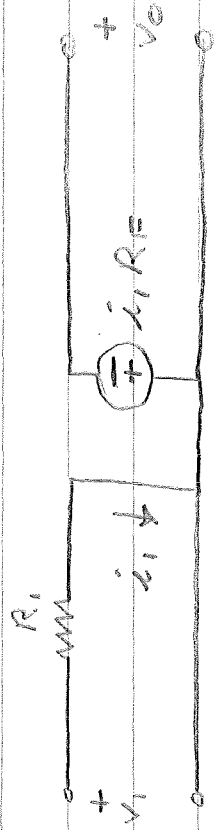BASIC INVERTING CIRCUIT EQUIVALENT CIRCUIT



SUMMING CIRCUIT

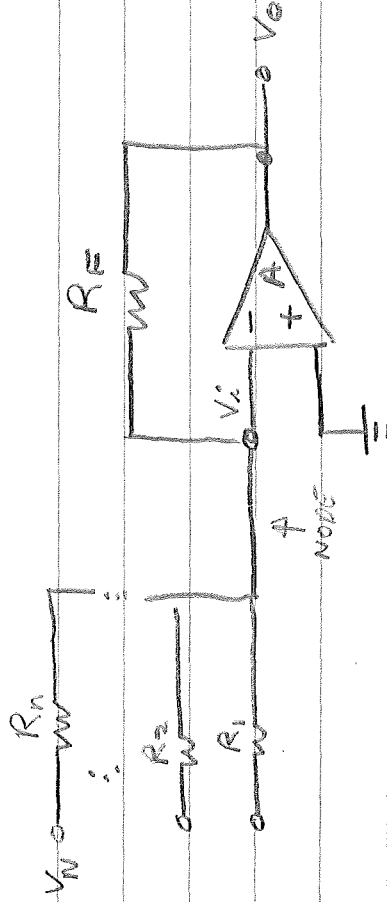

SUMMING CURRENTS AT NODE:


$$\frac{V_1 - V_i}{R_1} + \frac{V_2 - V_i}{R_2} + \dots + \frac{V_n - V_i}{R_n} = \frac{V_i - V_o}{R_F}$$

$$V_i = V_o/A \Rightarrow V_i \ll 1$$


$$\Rightarrow \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + V_n/R_n = -V_o/R_F$$

OUTPUT IS "WEIGHTED" SUM OF INPUT VOLTAGES.

BASIC NON-INVERTING CIRCUIT

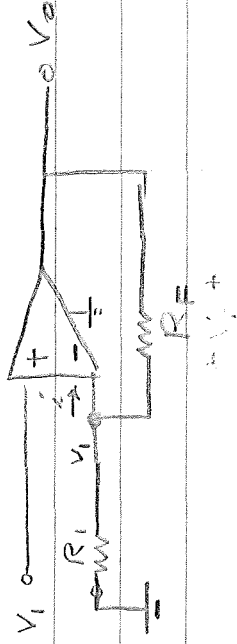

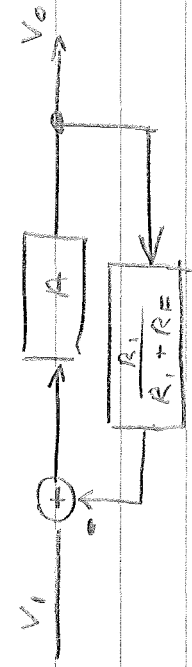SINCE β IS SMALL,
 $R_F \approx R_1$ FORM V DIVIDER WITH V_o
 $\Rightarrow V_1 = \frac{R_1}{R_1 + R_F} V_o$




(FEEDBACK) GAIN IS $\frac{A}{1 + A \frac{R_1}{R_1 + R_F}}$
 $A_F = \frac{G}{1 + GH} = \frac{A}{1 + A \frac{R_1}{R_1 + R_F}}$
 $= \frac{1}{\frac{1}{A} + \frac{R_1}{R_1 + R_F}}$

FOR LARGE A

$A_F = \frac{R_1 + R_F}{R_1}$

INTEGRATOR

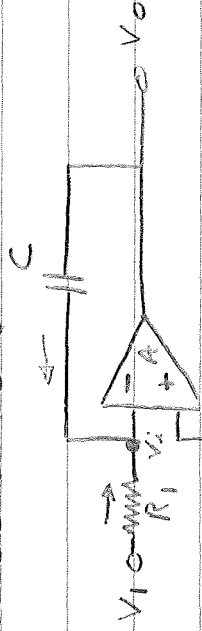

SINCE $V_o = A V_i$, $|V_i| \ll |V_o| \Rightarrow V_i \approx 0$


A CURRENTS AT V_i :

$$\frac{(V_i - V_i)}{R_1} + C \frac{d(V_o - V_i)}{dt}$$

$$\approx \frac{V_i}{R_1} + C \frac{dV_o}{dt} = 0$$

$$\Rightarrow V_o = -\frac{1}{R_1 C} \int V_i(t) dt$$

DIFFERENTIATOR

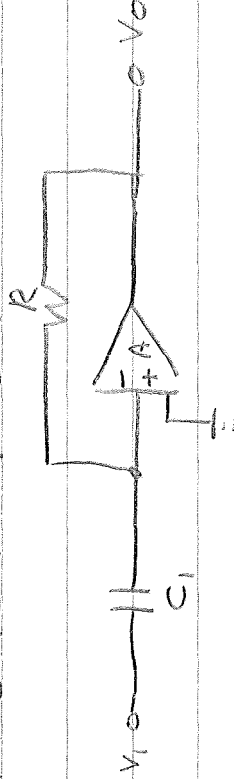

AGAIN, $V_i \approx 0$

$$C_1 \frac{dV_i}{dt} + \frac{V_o}{R} = 0 \Rightarrow V_i = -R_1 C_1 \frac{dV_i}{dt}$$


SOLUTION OF DIFFERENT EQUATIONS

CONVERTER

$$\frac{dV}{dt} = bV(t) = V_1 + V_0 \sin \omega t$$



ANALOG COMPUTING SOLUTION

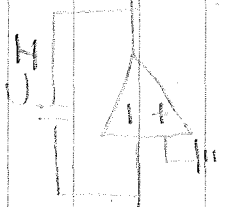TAP HERE FOR $V(t)$ - RICI IN EQUATION TO EQ



$$\frac{dV}{dt} = -R_1 C I / R_2$$

INTEGRATOR

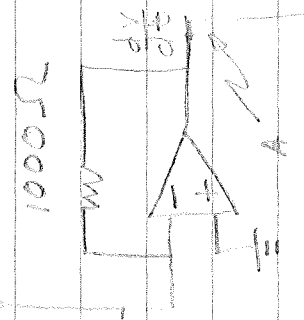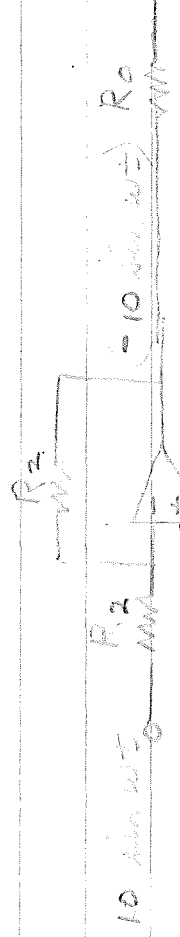

SUMMER

AT "A"

$$\frac{dV}{dt} = \frac{+R_1 C I}{R_2} = \frac{+R_1 C I}{R_2} V(t) = \frac{10}{R_1} + \frac{10}{R_2} \sin \omega t$$

THUS, CHOOSE $b = (R_1 C I / R_2) 1000$

$$V_1 = \left(\frac{10}{R_1}\right) (1000)$$


$$V_0 = (10/R_2) 1000$$

NOTES WE MUST

ASSUME b, V_1, V_0 ARE POSITIVE

MODELING

20

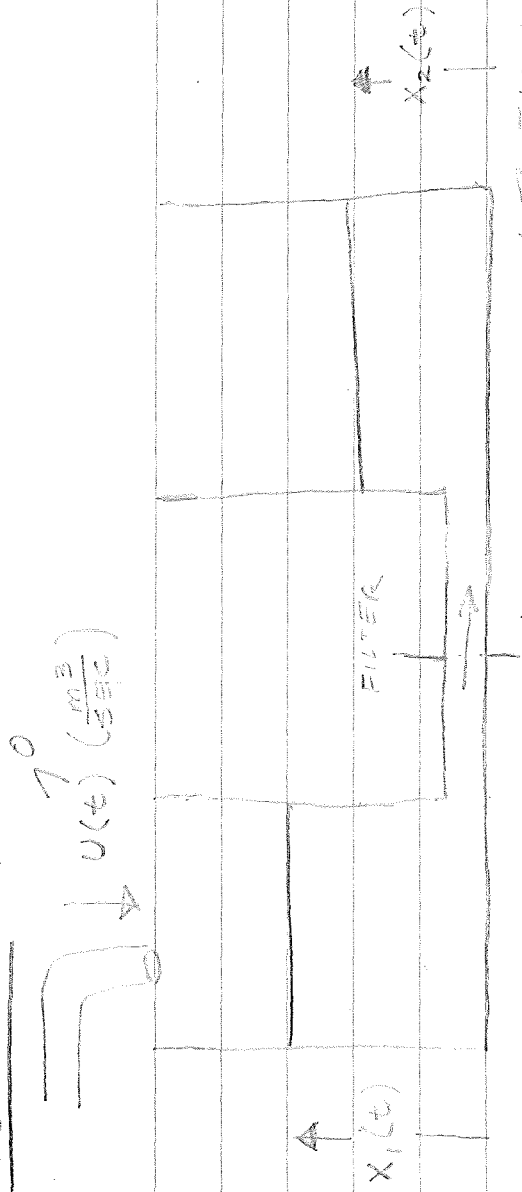

SECTIONAL FLOW RATE
TO HEAD DIFFERENCE
SECTIONAL FLOW RATE
TO HEAD DIFFERENCE

SECTIONAL FLOW RATE
TO HEAD DIFFERENCE

SECTIONAL FLOW RATE
TO HEAD DIFFERENCE

$$\alpha \dot{x}_1 = -q(t) + u(t)$$

$$\dot{x}_1 = -\frac{d}{dt} [x_1 - x_2] + u$$

OR

$$\dot{x}_1 = -\frac{d}{dt} x_1 + \frac{d}{dt} x_2 + \frac{d}{dt} u$$

ALSO

$$\alpha \dot{x}_2 = q = dx_1 - dx_2$$

OR


$$\dot{x}_2 = \frac{d}{dt} x_1 - \frac{d}{dt} x_2$$

"STATE" EQUATIONS:


$$\dot{x}_1 = -\frac{d}{dt} x_1 + \frac{d}{dt} x_2 + \frac{d}{dt} u$$

$$\dot{x}_2 = \frac{d}{dt} x_1 - \frac{d}{dt} x_2$$

ANALOG COMPUTER SOLUTION


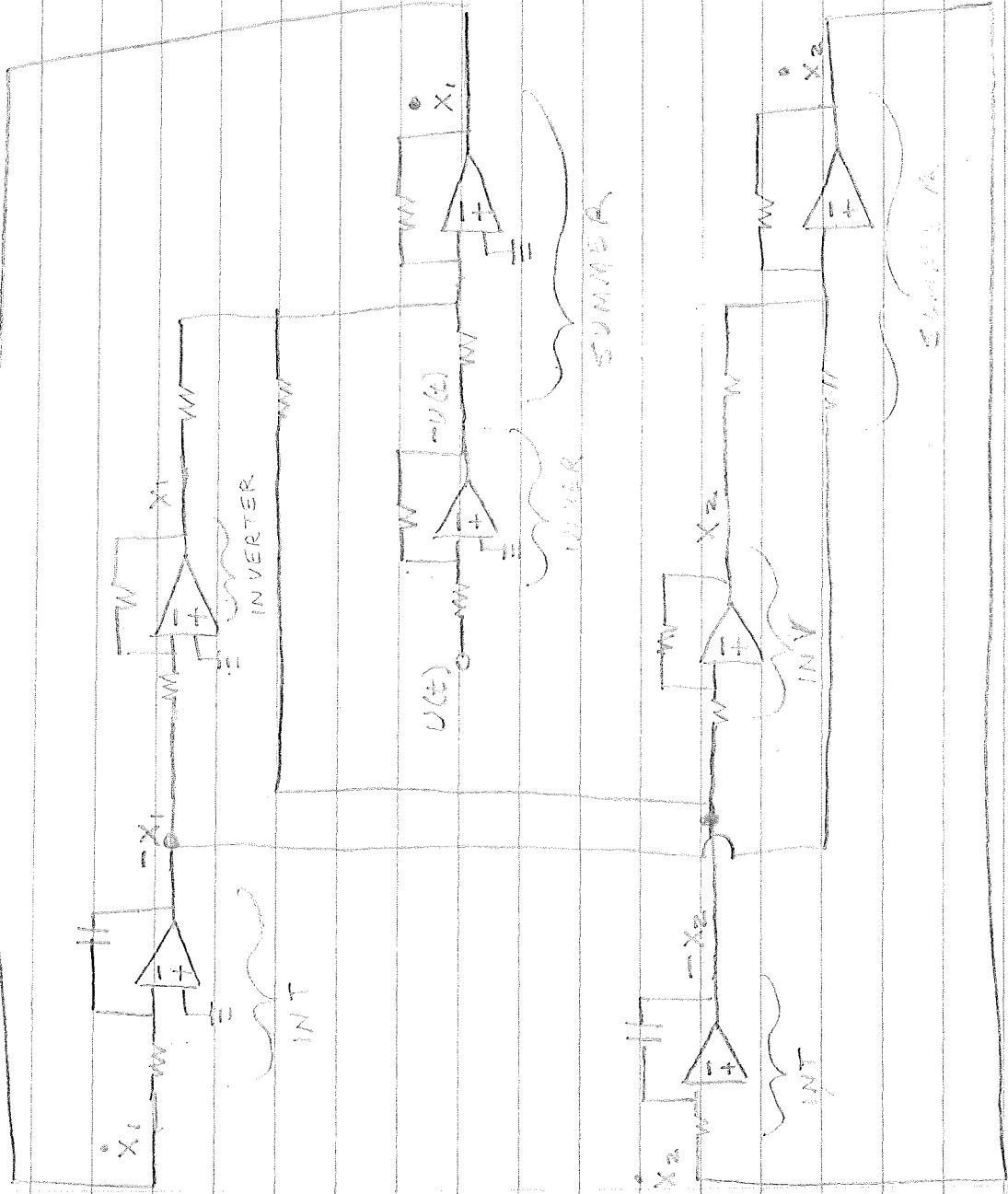


BASIC COMMUNICATION SYSTEM

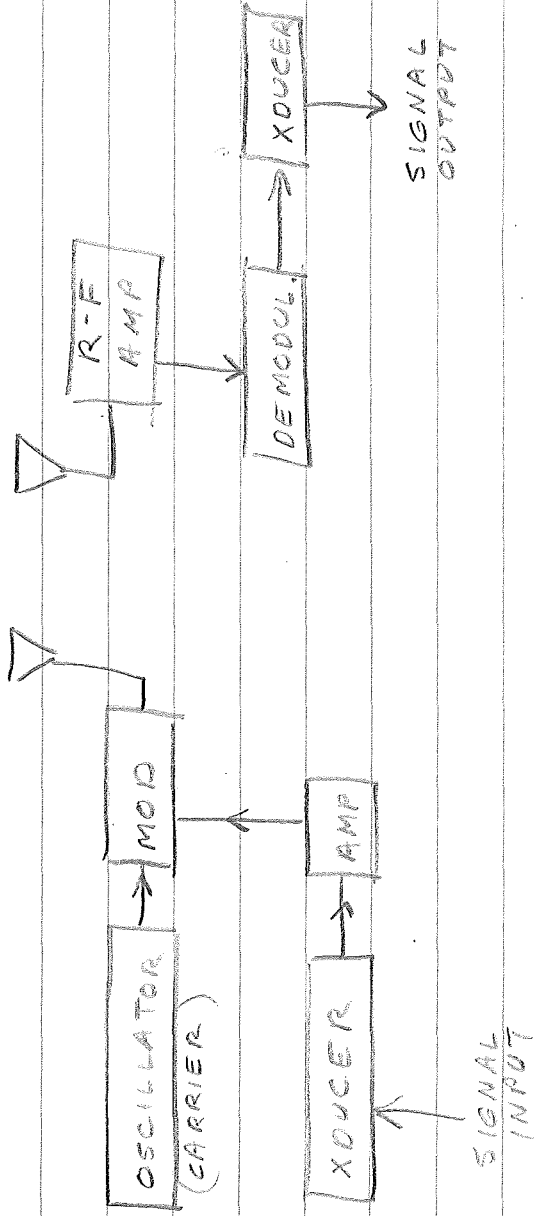



MODULATION

- AMPLITUDE MODULATION (p. 441)

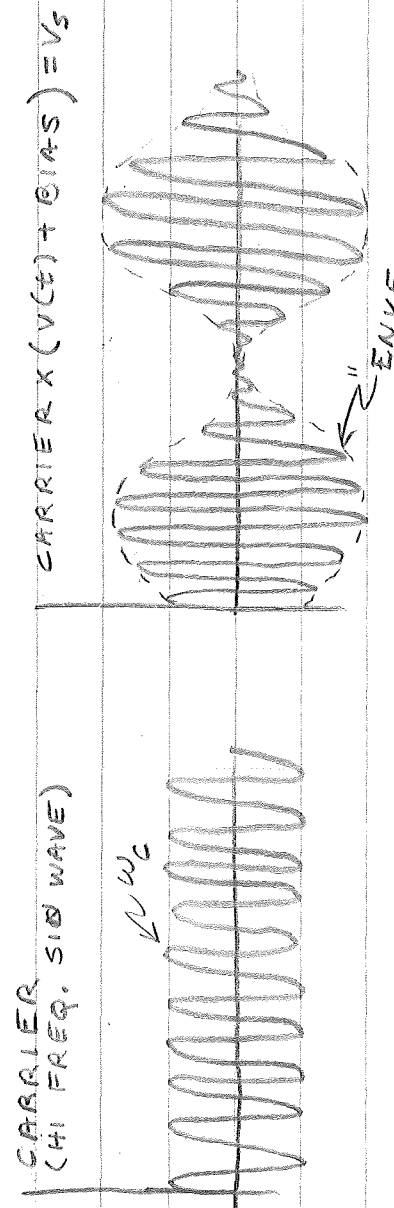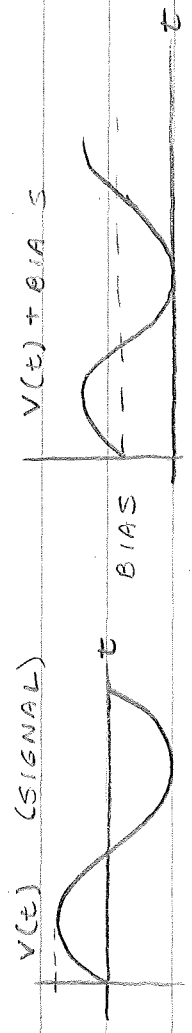

$V_s(t) = (1 + m \sin \omega_m t) (V_c \sin \omega_c t)$; $\omega_c \gg \omega_m$
 CARRIER


m = DEGREE OF MODULATION ; $0 < m < 1$

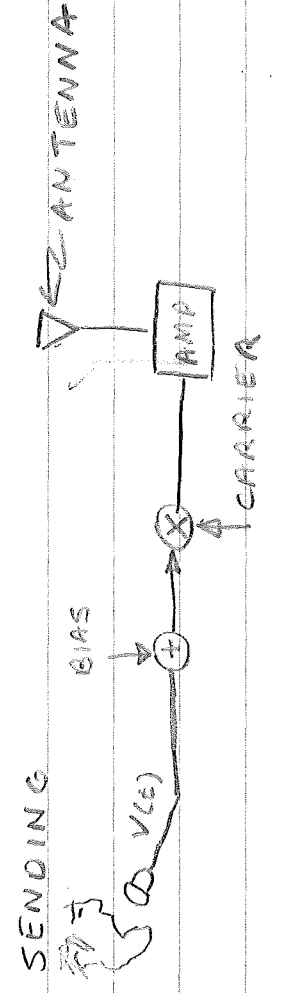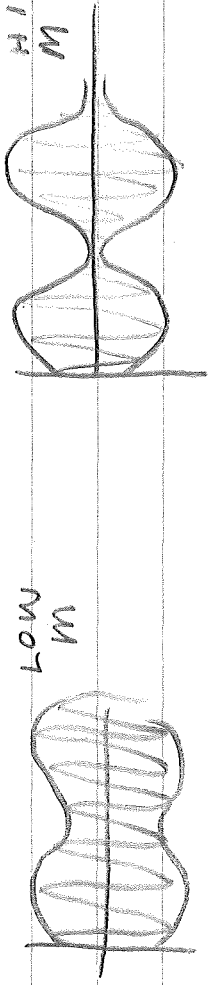


$$\begin{aligned}
 V_s(t) &= V_c \sin \omega_c t + m V_c \sin \omega_m t \sin \omega_c t \\
 &= V_c \sin \omega_c t + \frac{m V_c}{2} \cos(\omega_m - \omega_c) t \\
 &\quad - \frac{m V_c}{2} \cos(\omega_m + \omega_c) t
 \end{aligned}$$

FREQ. IN SIGNAL:

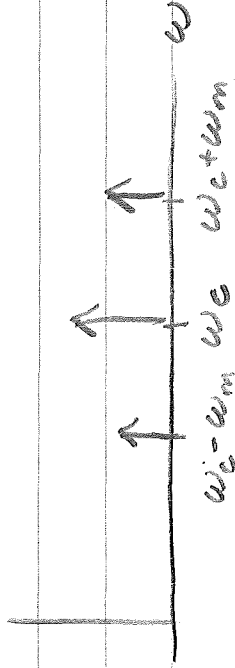ω_c , $\omega_c - \omega_m$, $\omega_c + \omega_m$



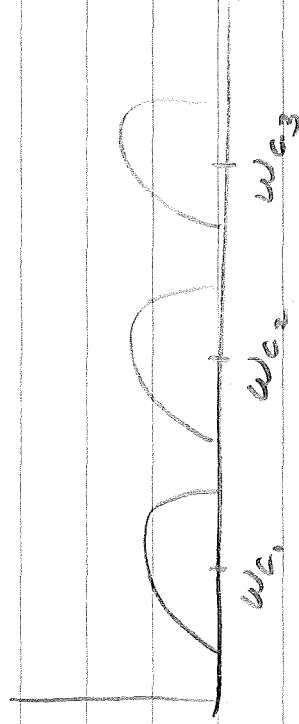
BY PLACING DIFFERENT SIGNALS ON DIFFERENT CARRIERS, WE CAN HAVE A NUMBER OF STATIONS:




SPECTRUM CONTROLLED BY FCC.

FREQUENCY MODULATION:


SIGNAL

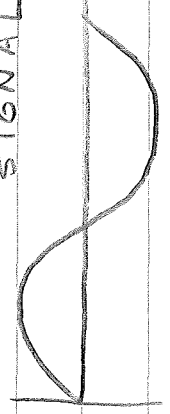

CARRIER

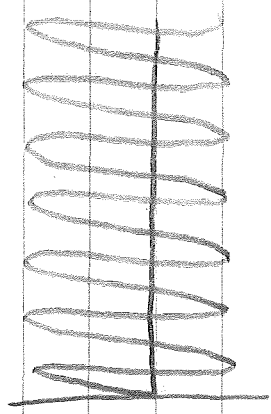

FM SIGNAL

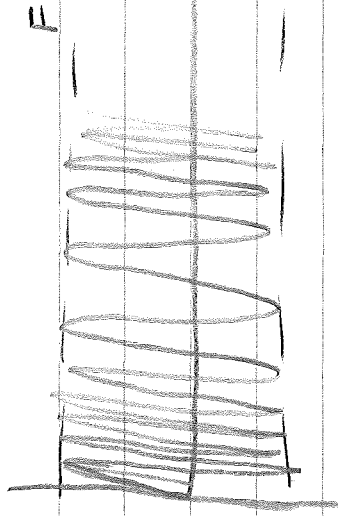


FM. ANALYTICALLY:

$$s(t) = A \cos \left[\omega_c t + \Delta\omega \int m(t) dt \right]$$


↑
↑
↑
↑
↑
↑
↑

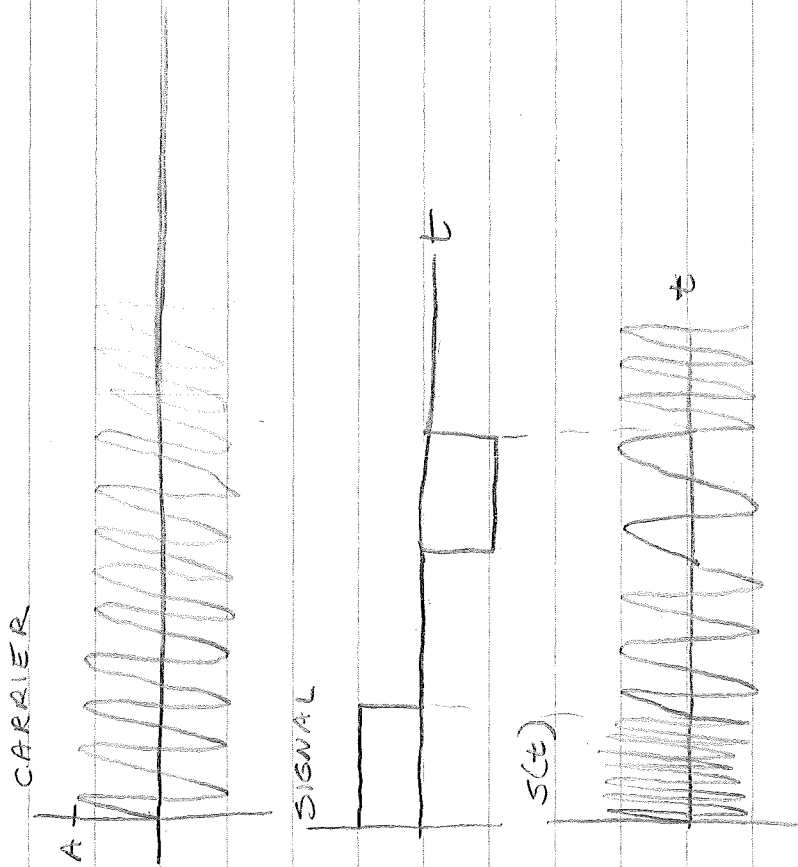CARRIER MAX SIGNAL
 ANGLE ANGLE ANGLE
 DEVIATION DEVIATION DEVIATION






PHASE MODULATION:
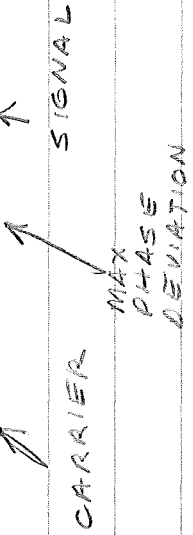
$$s(t) = A \cos(\omega_c t + \phi_m m(t))$$




FOR $m(t)$ BINARY, WE GET 180° SHIFT

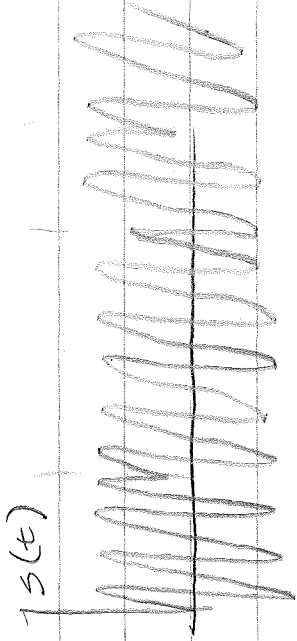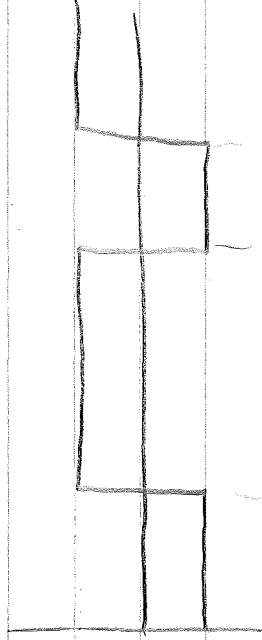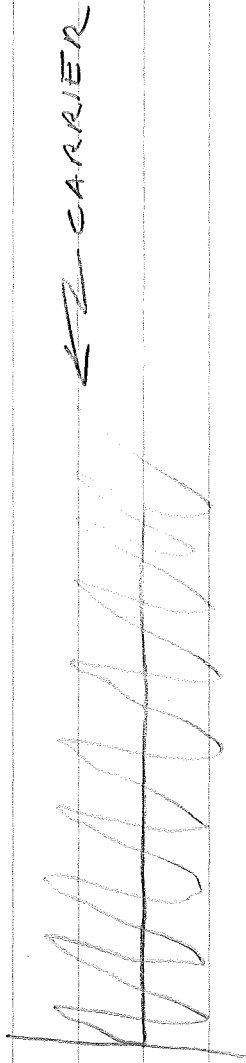


PULSE MOD


PULSE AMPLITUDE MODULATION: (PAM)

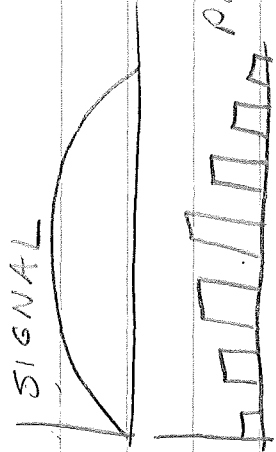

PULSE DURATION MODULATION: (PDM)

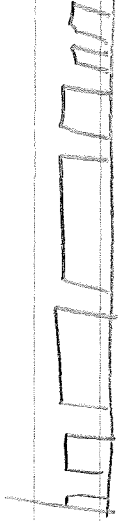

PULSE POSITION MOD (PPM)
REF. PULSES

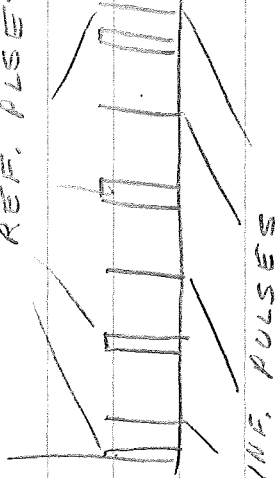

SEP BETWEEN REF PULSES \propto INF

PULSES \propto AMPLITUDE

PULSE CODE MODULATION (PCM)
(NEED BINARY #'S, LATER)

MULTIPLEXING: PLACING TWO OR MORE SIGNALS OVER THE SAME CHANNEL (PULSE)


1. TIME DIVISION (TDM)

SAMPLING THM \Rightarrow SAMPLING RATE = $2 \times \text{HI FREQ}$



VOICE \rightarrow 3000 Hz

\Rightarrow 6000 SAMPLING/SEC

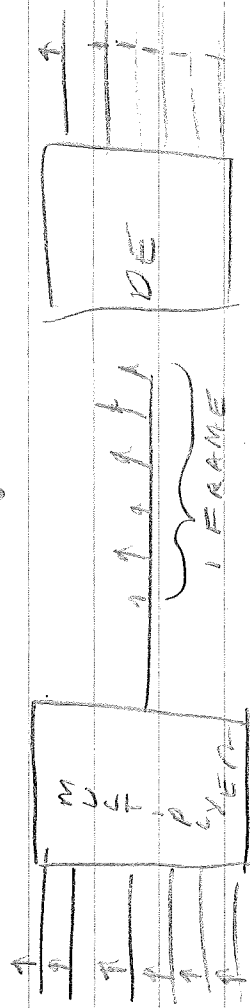CHANNEL CAP = 36,000 Hz ($6 \times / \text{SEC}$)



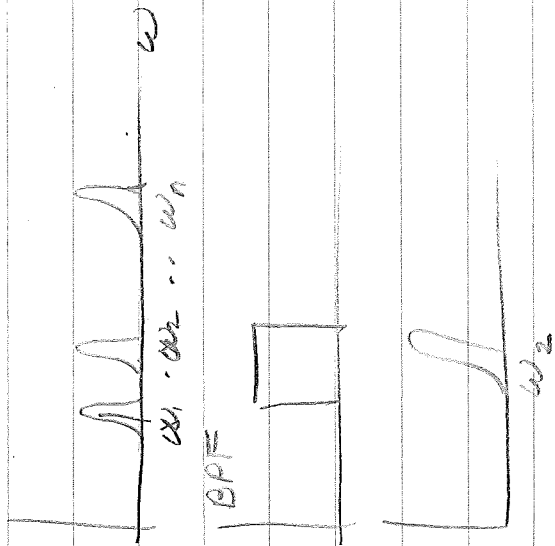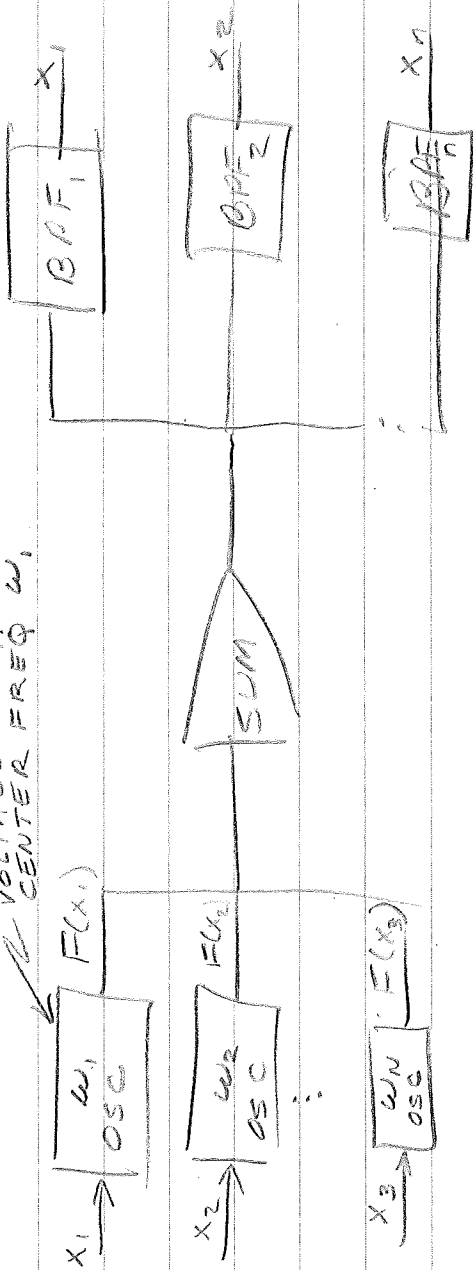2. FREQ DIV. M (FDM) \leftarrow VOLTAGE CONT. OSC. CENTER FREQ ω_1



TEST # 2

5 PROBLEMS, 20 PTS EACH

OPEN BOOK & OPEN NOTE

1. (20) 10 T-F QUESTIONS

(PENALTY FOR GUESSING)

-2 OR -3 OR +2

2. (20) MODULATION & MULTIPLEXING (SAMPLING THEM)

3. (20) TRANSISTOR CIRCUITRY & BIASING

4. (20) BRIDGES: WHEATSTONE, MAXWELL, BALANCING,
TOLERANCES, STRAIN GAUGES, ETC.

5. (20) OP AMP


BINARY NUMBERS (VINES-CHAPT. 5)

2^5 2^4 2^3 2^2 2^1 2^0
 \uparrow \uparrow \uparrow \uparrow \uparrow \uparrow
 1 0 1 1 0 1


$$(110)_2 = (1 \times 2^2 + 1 \times 2^1 + 0 \times 2^0) = 6$$

$$(1001)_2 = (1 \times 2^3 + 0 \times 2^2 + 0 \times 2^1 + 1 \times 2^0) = 9$$

BINARY D/A CONVERTER

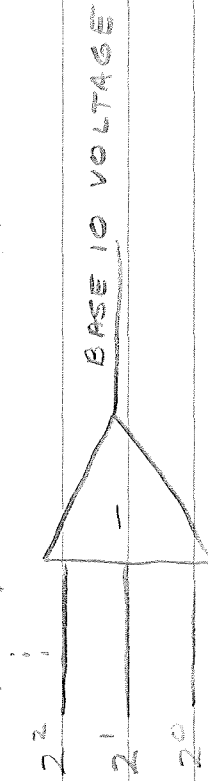


EXAMPLE:

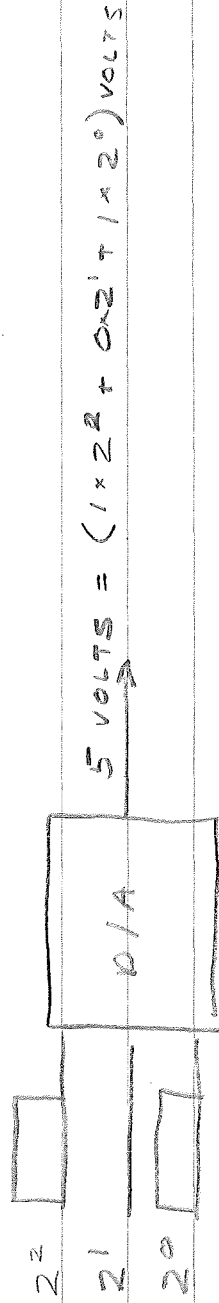


A/D CONVERTOR GOES OPPOSITE.

PULSE CODE EXAMPLE: 3 BITS LONG

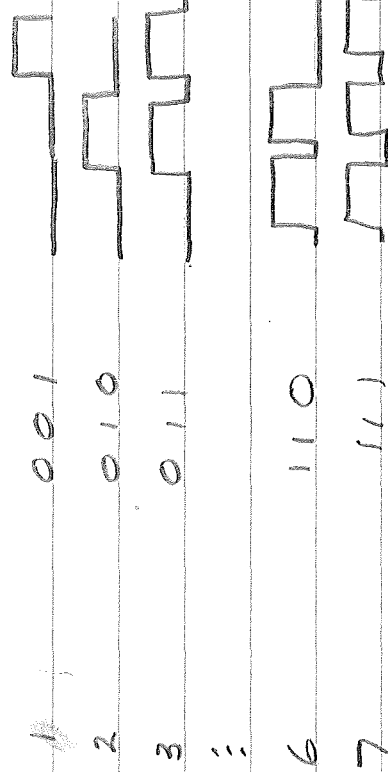


CODING

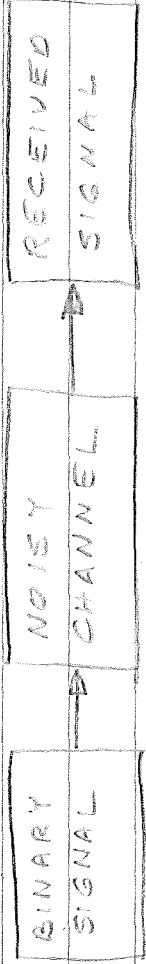

CODING CAN BE USED TO MINIMIZE
EFFECTS OF ACCEPTING
ERRONEOUS SIGNALS.

EX

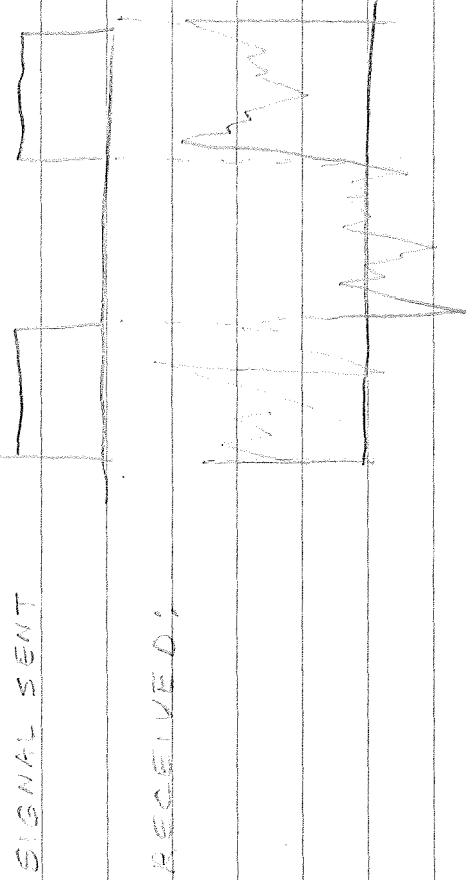

G

EXAMPLE

3 LETTERS IN A 3 BIT STRING. (a, b, c)

WHICH CODE IS BETTER?

#1: a = 001

b = 010

c = 011

#2: a = 001

b = 010

c = 100

CODE #2 IS BETTER FOR NOISE IMMUNITY.

DISTANCE BETWEEN CODES

#1 a = 001

b = 010

c = 011

$$\sqrt{0+1+1} = 2$$

$$d(a, b) = \sqrt{2} = d(b, a)$$

b = 010

c = 011

$$\sqrt{0+0+1} = 1$$

$$d(b, c) = 1$$

a 001

c 011

$$\sqrt{0+1+0} \Rightarrow d(a, c) = 1$$

#2 $d(a, b) = d(a, c) = d(b, c) = \sqrt{2}$

IN GENERAL, THE GREATER THE DISTANCE,
THE BETTER THE NOISE IMMUNITY.

~~SAN WE IMPROVE ON CODE?~~

~~YES: a = 1, 1, 1~~

~~b = 0, 0, 1~~

ERROR CORRECTING CODES

1. ZERO ERROR CORRECTING: a, b, c

a = 01

b = 10

c = 11

WE RECEIVE, VIA NOISY CHANNEL, 11

(1) 11 = c SENT

(2) 01 = a SENT WITH SINGLE BIT ERROR

(3) 10 = b " " " " " "

2. SINGLE BIT ~~ERROR~~ ^{AND SINGLE BIT} ERROR DETECTION CODES a, b, c

a = 0101

b = 1010

c = 1111

CHANGING 1 BIT IN a, b, OR c DOES NOT RESULT IN ANOTHER LETTER.

EX, RECEIVE 0111 ~~IS~~ MISTAKE!

MISTAKE ON a \Rightarrow 0101 \Rightarrow 0111

OR c \Rightarrow 1111 \Rightarrow 0111

~~all b 2-bit error~~ (FEES APPLICABLE)
RECEIVE 0110 \Rightarrow 2 BIT ERROR ON EITHER a, b, OR c.

3. ERROR DETECTION & CORRECTION CODE

a = 000000

b = 000110

c = 111111

RECEIVE 111101 \Rightarrow c PROBABLY SENT

" 000100 \Rightarrow b PROBABLY SENT

THIS IS "SINGLE BIT" ERROR CORRECTING CODE. FOR EXAMPLE

RECEIVE 010111 = DOUBLE BIT ERROR

IN BOTH b AND c. FOR DOUBLE BIT

... ..

TO INCREASE GOODNESS OF TRANSMISSION

1. SLOWER MORE ACCURATE TRANSMISSION
(ERROR DET. & CORR. CODES ARE
LONGER IN DURATION)

2. HIGHER CHANNEL CAPACITY

(i.e., LARGER CHANNEL BANDWIDTH)

⇒ MORE PULSES PER SECOND

3. CLEVER (OPTIMAL) CODING SCHEMES

TO MAKE THE MOST FROM WHAT
WE HAVE.

A "CLEVER" CODING SCHEME (SINGLE BIT ERROR DETECTION)

FOUR BIT WORDS

USE A FIFTH BIT FOR "PARITY CHECK"

EVEN PARITY CHECK:

0 \Rightarrow # OF 1's IN WORD IS EVEN

1 \Rightarrow # OF 0's IN WORD IS ODD

= WORD PARITY

0 0000 0

1 0001 1

2 0010 1

3 0011 0

4 0100 1

5 0101 0

6 0110 0

7 0111 1

8 1000 1

...

EX: RECEIVE

01111 \leftarrow THIS IS PROB. RIGHT.

01011 \leftarrow THIS IS WRONG!

EX: RECEIVE;

00000 1

MOST PROBABLE SENT: (DISTANCE = 1)

00000 0


00001 1

00100 1

01000 1

10001

A SIMPLE BINARY CHANNEL

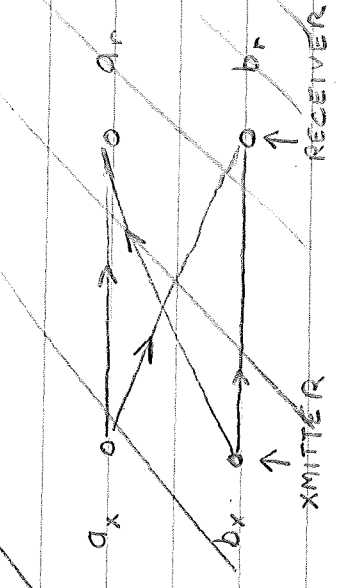

A LITTLE PROBABILITY OF THE OCCURANCE OF AN EVENT

$P[E] = \text{PROBABILITY OF THE OCCURANCE OF AN EVENT } E$
 JOINT PROB: $P_c[E, F] = P_c[\text{EVENTS } E \text{ AND } F \text{ OCCUR}]$

CONDITIONAL PROB

$P_r[E/F] = P_c[E \text{ OCCURS GIVEN } F \text{ HAS OCCURED}]$
 RELATION:

$P_c[E, F] = P_r[E/F] P_c[F]$

EX: ROLL OF TWO DICE: EVENT IS OUTCOME


$P_r[E=2] = 1/6$

$P_r[E \text{ EVEN}] = 1/2$

$P_r[E \text{ EVEN AND } E=3] = 0$

$P_r[E \text{ EVEN AND } E=2] = 1/6$

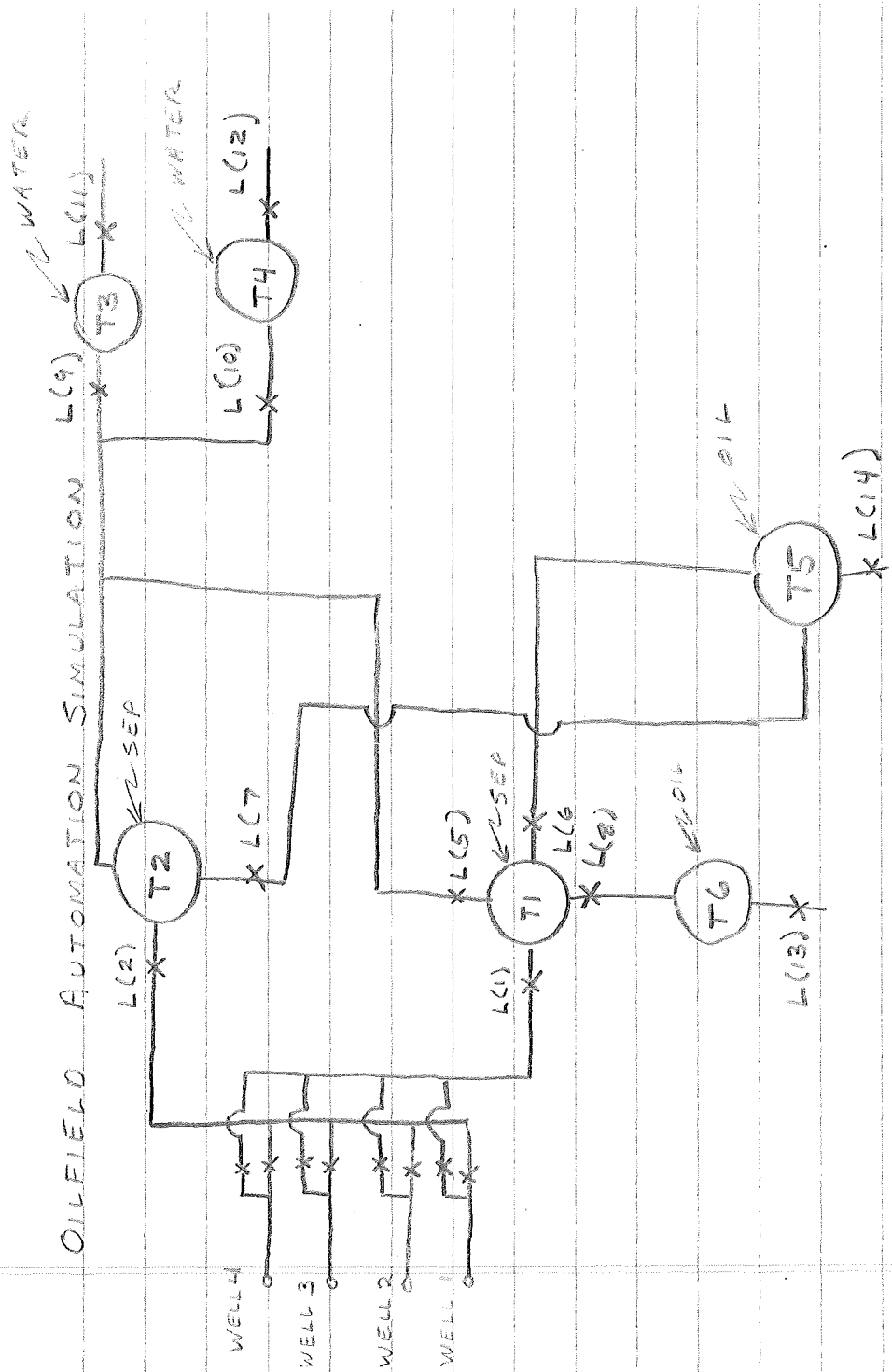$P_r[E=2 \text{ GIVEN } E \text{ EVEN}] = \frac{1/6}{1/2} = 1/2$



FOUR WELLS

TWO SEPARATORS: T(1) & T(2)


TWO OIL HOLDING TANKS: T(5) & T(6)

TWO WATER HOLDING TANKS: T(3) & T(4)

CONTROL SYSTEM CENTERS ARE ALL SEPARATORS (CYLINDRICAL TANKS)

⇒ VOLUME × HEIGHT

B(K) = TOTAL TANK VOLUME

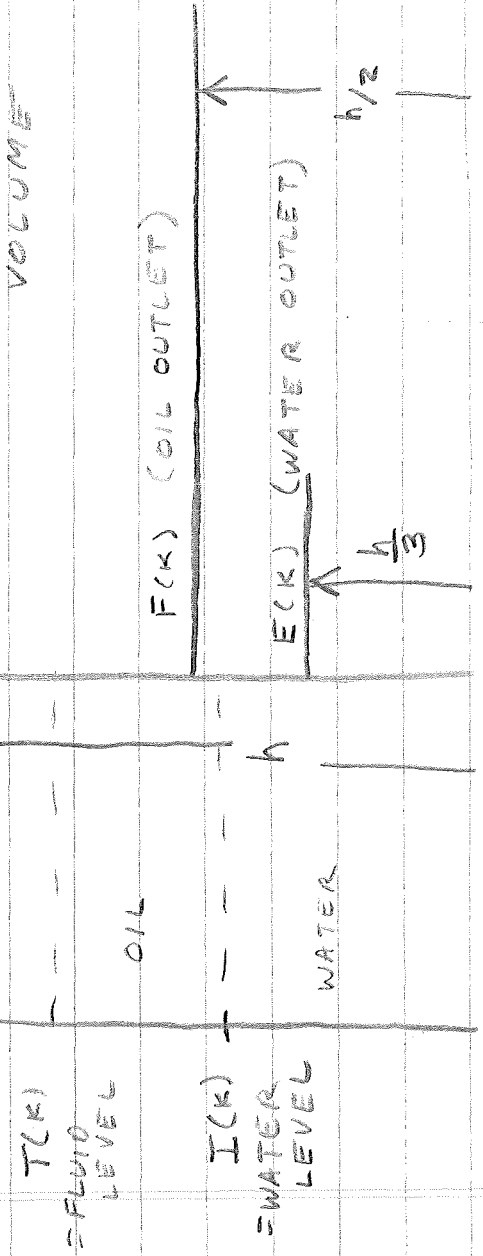

AUTOMATIC CONTROL

MAIN PROGRAM: WILL RECORD ACCUMULATIONS

INTO THE TANKS ACCORDING TO WELLS


AND VALVE SETTINGS

CONTROL PROGRAM PURPOSE: TO CONTROL

THE FLOWS INTO AND OUT OF THE

TANKS VIA THE VALVES.

FLOW:

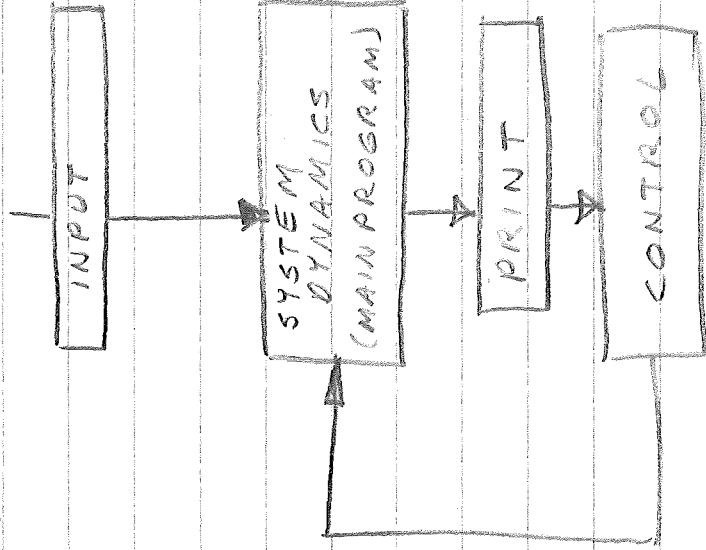

INPUT (INITIALIZATION)

1. ARE WELLS (1-4) ON OR OFF?

2. WHICH WELL FEEDS WHICH
SEPARATOR (T1 OR T2)

3. WHAT ARE PUMP CAPACITIES (GPM),

4. STATUS OF LG) $\frac{3}{4}$ L(C10) (ON OR OFF)

5. SAMPLE TIME (MINUTES)

(OR, HOW LONG DO YOU WANT THEM TO
RUN BEFORE CHECKING)

PROGRAM TERMINATIONS: (BAO)

1. OVERFLOW

2. WATER GETS INTO OIL

3. OIL GETS INTO WATER

REVIEW

$$P_r[E]$$

$$P_r[E, F] = P_r[E \text{ AND } F] = P_r[E, F]$$

$$P_r[E|E] = P_r[E \text{ GIVEN } E]$$

$$\text{RELATION: } P_r[E, F] = P_r[E/F] P_r[F]$$

$$\text{ALSO } P_r[E \text{ OR } F] = P_r[E] + P_r[F]$$

IF E & F CAN'T
OCCUR BOTH AT
SAME TIME

EX DRAW FROM A DECK OF CARDS

E = FIRST DRAW

F = SECOND DRAW

$$P_r[E = \text{JACK}] = \frac{4}{52} \quad \left(\frac{4 \text{ JACKS}}{52 \text{ CARDS}} \right)$$

$$P_r[F = \text{JACK} / E = \text{JACK}] = \frac{3}{51} \quad \left(\frac{3 \text{ JACKS}}{51 \text{ CARDS}} \right)$$


$$\text{SINCE } P_r[F, E] = P_r[F/E] P_r[E]$$

$$P_r[F = \text{JACK AND } E = \text{JACK}]$$

$$= P_r[F = \text{JACK} / E = \text{JACK}] P_r[E = \text{JACK}]$$

$$= \frac{3}{51} \times \frac{4}{52} = \frac{1}{17} \times \frac{1}{13} = \frac{1}{221}$$

BINARY CHANNEL

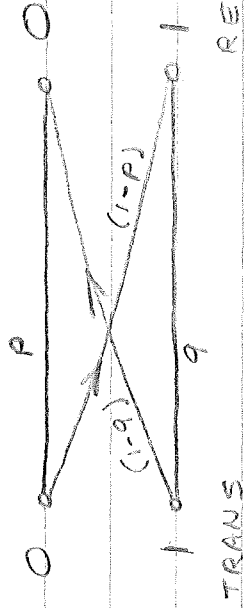

$$P = P_r[0 \text{ RECEIVED} / 0 \text{ TRANSMITTED}] = P_r[O_R / O_T]$$

$$1 - P = P_r[1_R / O_T]$$

NOTE: $P_r[O_R / O_T] + P_r[1_R / O_T] = 1$ SINCE,

GIVEN 0 IS TRANSMITTED, SOMETHING

MUST BE RECEIVED. (HARD DECISION)

$$q = P_r[1_R / 1_T]$$

$$1 - q = P_r[O_R / 1_T]$$

EX: GIVEN 1001 WAS XMITTED, WHAT IS PROB. 1001 IS RECEIVED?

$$P_r[1001] \text{ RECEIVED} = qppq = q^2 p^2$$

- WHAT IS $P_r[1110]$ IS RECEIVED?

$$q(1-p)(1-p)p = pq(1-p)^2$$

FOR $p = 0.9$ & $q = 0.8$:

$$P_r[(1001)_R / (1001)_T] = (0.9)^2 (0.8)^2 = 51.84\%$$

$$P_r[(1110)_R / (1001)_T] = (0.8)(0.9)(0.1)^2 = 0.72\%$$

"PRIORI" OR BEFOREHAND KNOWLEDGE

$$p_0 = P_r[O_t]$$

$$= P_r[A \text{ ZERO IS TRANSMITTED}]$$

$$p_1 = P_r[1_t]$$

$$= P_r[A \text{ 1 IS TRANSMITTED}]$$

EX: WHAT IS $P_r[O_R]$?

$$P_r[O_R] = P_r[(1_t \text{ AND } O_R) \text{ OR } (0_t \text{ AND } O_R)]$$

$$= P_r[1_t, O_R] + P_r[0_t, O_R]$$

$$= P_r[O_R/1_t] P_r[1_t] + P_r[O_R/0_t] P_r[0_t]$$

$$= (1-q) p_1 + p_0$$

$$\text{FOR } p_1 = P_r[1_t] = p_0 = P_r[0_t] = \frac{1}{2}$$

$$p = 0.9 \quad q = 0.8$$

$$P_r[O_R] = [(0.2) + (0.9)] \frac{1}{2} = 55\%$$

EX: WHAT IS $P_r[\text{ERROR}]$?

$$P_r[E] = P_r[(O_t, 1_R) \text{ OR } (1_t, O_R)]$$

$$= P_r(O_t, 1_R) + P_r(1_t, O_R)$$

$$= P_r[1_R/0_t] P_r[0_t] + P_r[0_R/1_t] P_r[1_t]$$

$$= (1-p) p_0 + (1-q) p_1$$

$$\text{FOR } p_0 = p_1 = \frac{1}{2}$$

$$p = 0.9 \quad q = 0.8$$

$$P_r[E] = \frac{1}{2} (0.2 + 0.1) = 15\%$$

$$P_r[\text{NO ERROR}] + P_r[E] = 1$$

$$\Rightarrow P_r[\text{NO ERROR}] = 1 - [(1-p) p_0 + (1-q) p_1]$$

CONSIDER "BINARY SYMMETRIC CHANNEL"

$$p = q$$

$$\text{ASSUME } p_0 = q_0 = \frac{1}{2}$$

WHAT

FOR A SINGLE BIT, WHAT IS $P[\text{ERROR}]$

$$\begin{aligned} P[\text{ERROR}] &= P_r[0 \rightarrow 1] + P_r[1 \rightarrow 0] \\ &= P_r[1_n / 0_n] P(0_n) + P_r[0_n / 1_n] P(1_n) \\ &= \frac{1}{2}[(1-p) + \frac{1}{2}(1-q)] \\ &= \frac{1}{2}(1-p) \end{aligned}$$

WHAT IS $P_r[\text{NO ERROR}]$

$$P[\text{NO ERROR}] = 1 - P[\text{ERROR}] = A$$

CONSIDER N BIT WORD

$$P_r[\text{NO ERROR}] = P^n$$

WHAT IS $P_r[1 \text{ BIT ERROR}]$?

$$= (1-p)p \dots p$$

$$+ P(1-p) \dots p$$

$$\uparrow \text{OR} \quad + \dots + p \cdot p \dots (1-p)$$

$$= n(1-p)p^{n-1}$$

IN GENERAL, $P_r(k \text{ ERRORS})$ ($0 \leq k \leq n$)

$$= \binom{n}{k} (1-p)^k p^{n-k}$$

$$\binom{n}{k} = \frac{n!}{k!(n-k)!}$$

NOTE:

$$\sum_{k=0}^n P_r[k \text{ ERRORS}] = \sum_{k=0}^n \binom{n}{k} (1-p)^k p^{n-k}$$

$$= [(1-p) + p]^n = 1$$

BOOLEAN OPERATIONS (READ CHART. 4 IN VINES)

"AND" FUNCTION 0 - "FALSE"
1 - "TRUE"


$A \cdot B = C$

0	0	0
0	1	0
1	0	0
1	1	1

TRUTH
TABLE

BOTH A & B MUST BE TRUE FOR
C TO BE TRUE.

AND GATE:

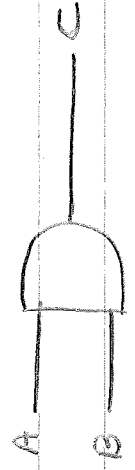


"OR" FUNCTION (INCLUSIVE)

$A + B = C$

0	0	0
0	1	1
1	0	1
1	1	1

EITHER A OR B MUST BE TRUE
FOR C TO BE TRUE

OR GATE

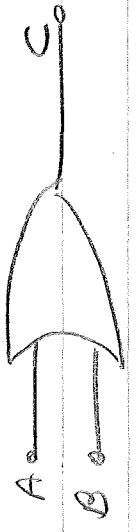

"NOT" FUNCTION

A	\bar{A}
0	1
1	0



EXCLUSIVE OR

INCLUSIVE: BAD HEALTH MAY RESULT

FROM INFECTION OR POOR DIET

(ONE OR THE OTHER IS POSSIBLE)

EXCLUSIVE: I WILL GRADUATE EITHER
IN MAY OR IN DEC.


(ONLY ONE IS POSSIBLE)

$$A \oplus B = C$$

0	0	0
0	1	1
1	0	1
1	1	0



"NAND" GATE

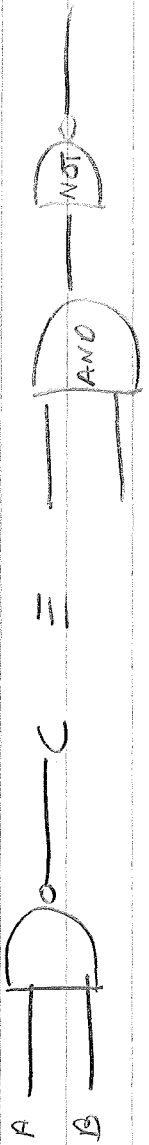

"NOR" GATE



DE MORGAN'S THEM:

$$\overline{AB} = \overline{A} + \overline{B}$$

$$\overline{A+B} = \overline{A} \overline{B}$$

EX: HALF ADDER

$$A \oplus B = A \oplus B \quad \text{SUM}$$

$$0 \quad 0 \quad 0 \quad 1 \quad 1 \quad 0 \quad 0 \quad 0$$


$$0 \quad 1 \quad 1 \quad 0 \quad 0 \quad 1 \quad 1 \quad 0$$

$$1 \quad 0 \quad 0 \quad 1 \quad 1 \quad 0 \quad 0 \quad 0$$


$$1 \quad 1 \quad 1 \quad 0 \quad 0 \quad 1 \quad 1 \quad 1$$

$A \oplus B$ IS EXCLUSIVE OR ~~AND~~ GATE


CARRY IS "AND" GATE

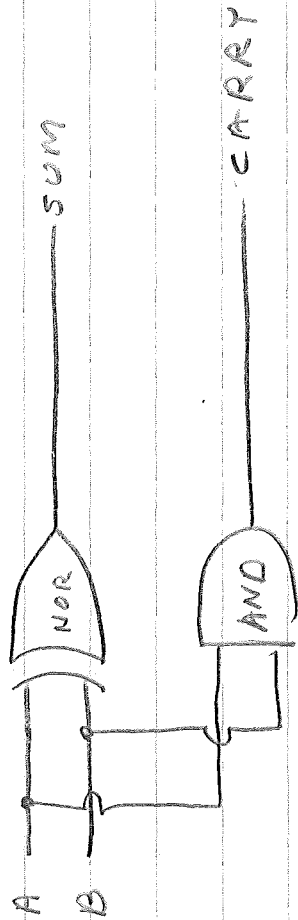

OR

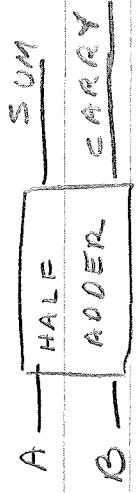


CAN COMBINE HALF ADDERS TO

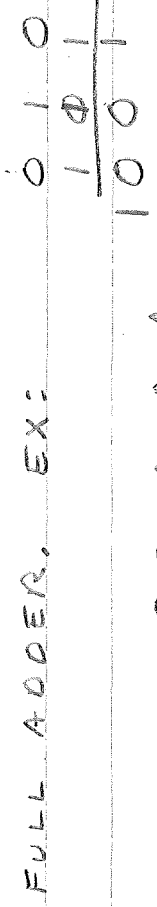


$010 = A_2 A_1 A_0$

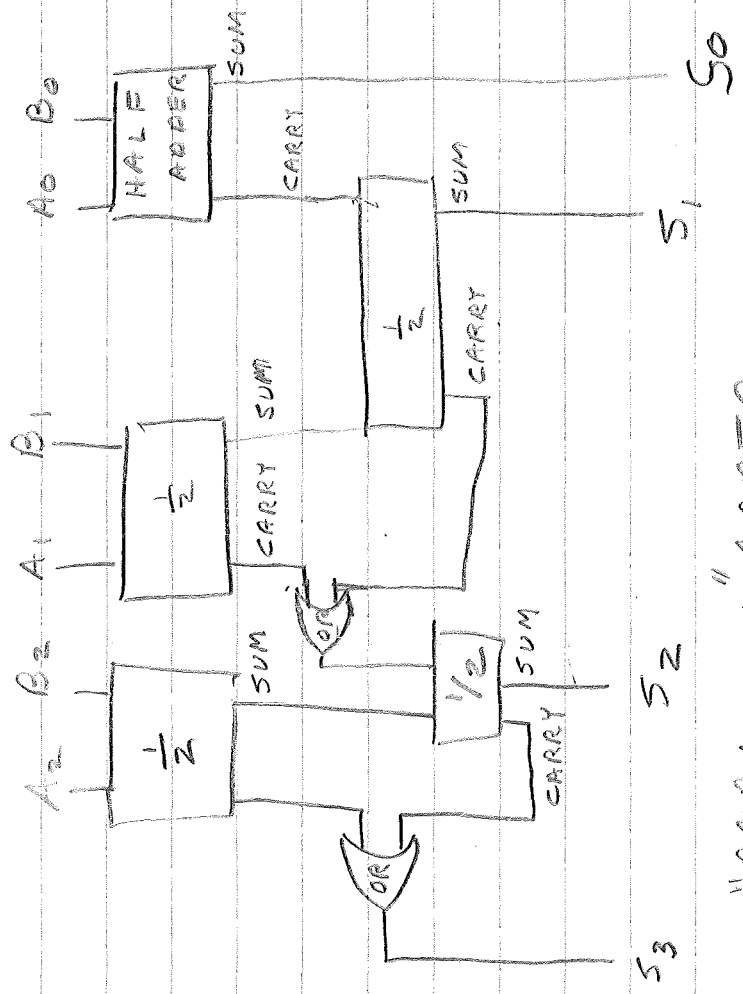$111 = B_2 B_1 B_0 \quad 1001 = S_3 S_2 S_1 S_0$



"PARALLEL" ADDER


EX: TWO WAY LIGHT SWITCH

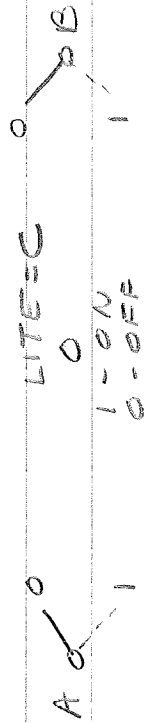


ASSUME $A = B = 0 \Rightarrow$ LITE OFF

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

THIS IS "EXCLUSIVE" OR

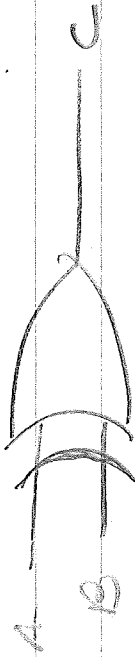


WITH SWITCHES:

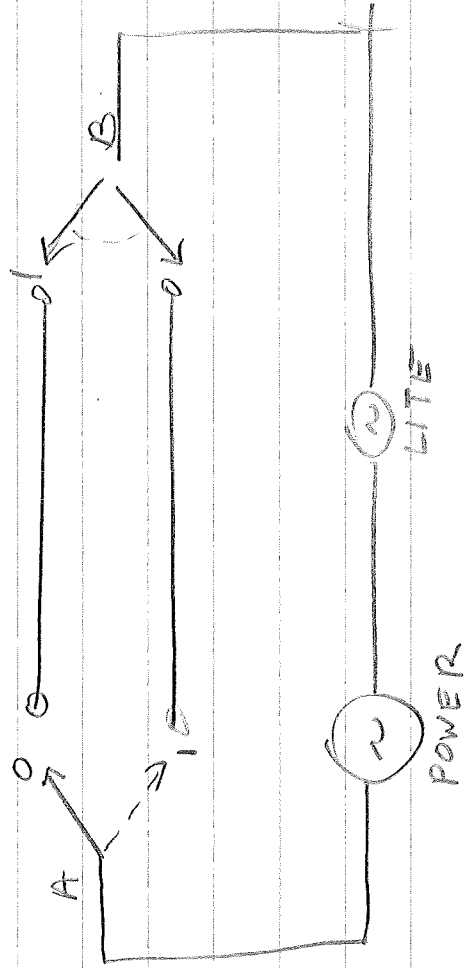


SWITCHES:

"AND"

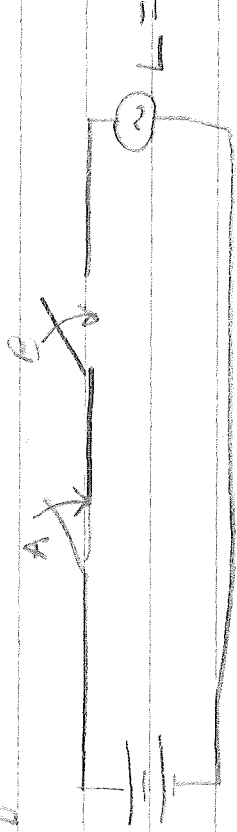

$L = AB$

"OR"

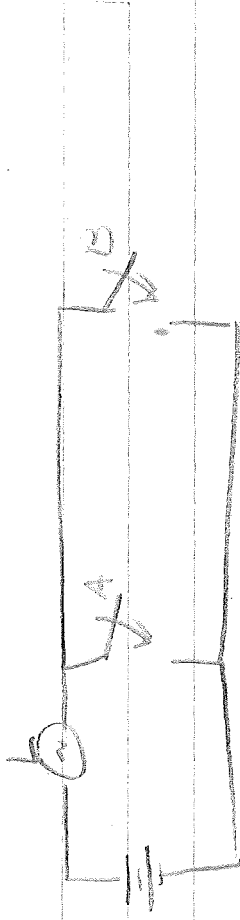

$L = A + B$

EX: THREE WAY LITE

A	B	C	L
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

STARTING POINT
←

ONE BIT

ONE BIT

TWO BIT

ONE BIT


TWO

TWO

THREE BIT



$$L = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

↑
OR

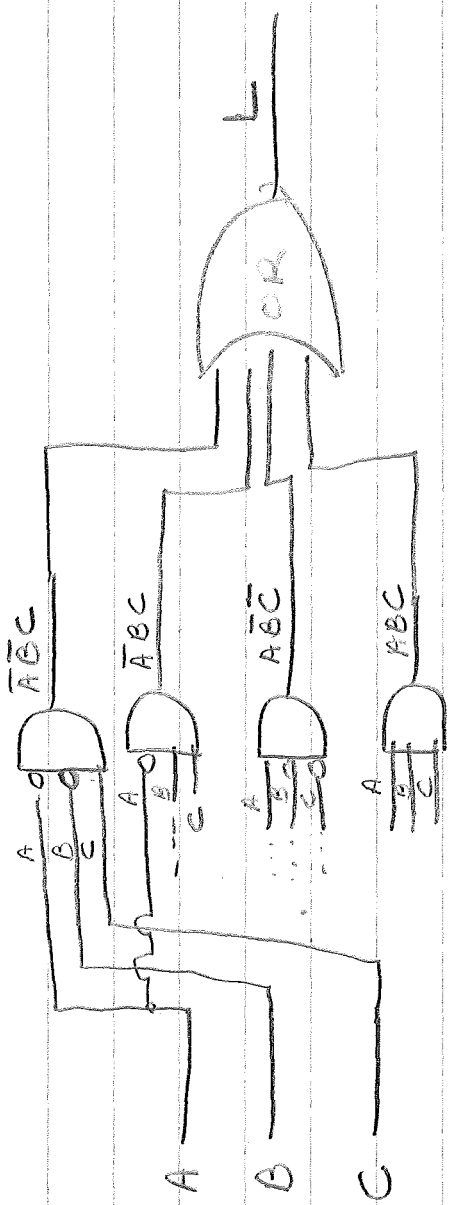


USING SWITCHES
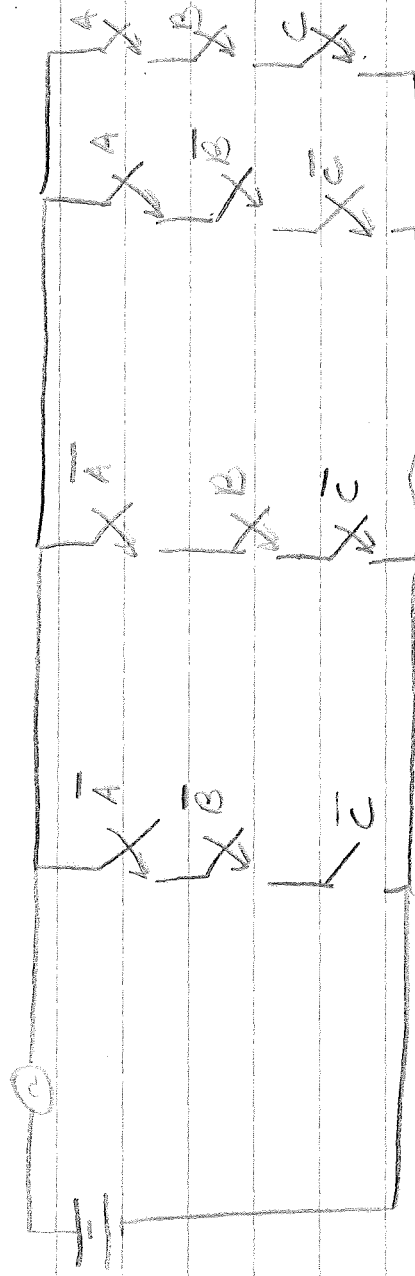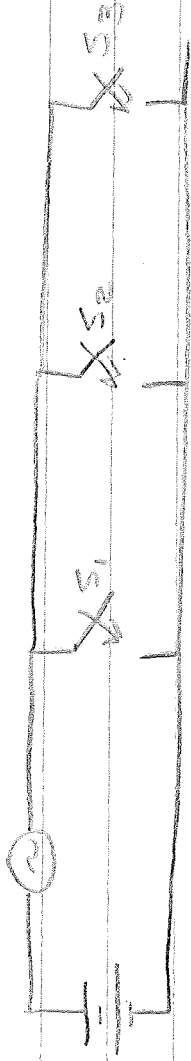
$$L = \underbrace{\bar{A}\bar{B}C}_{S_1} + \underbrace{\bar{A}B\bar{C}}_{S_2} + \underbrace{A\bar{B}\bar{C}}_{S_3} + \underbrace{ABC}_{S_4}$$



USE DOUBLE POLE - DOUBLE THROW SWITCHES




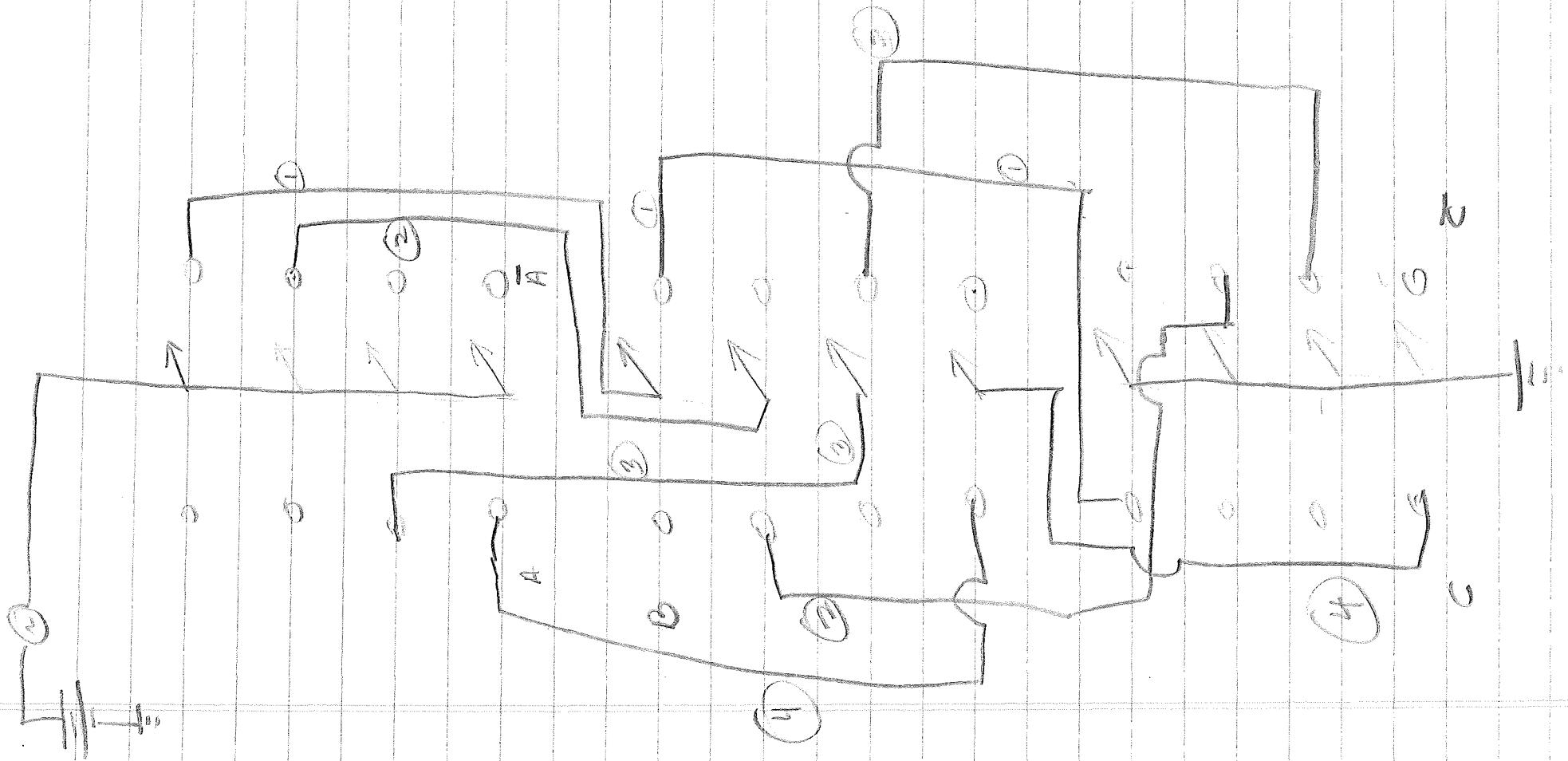

SIMPLIFYING (SWITCHING THEORY)

$$L = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$
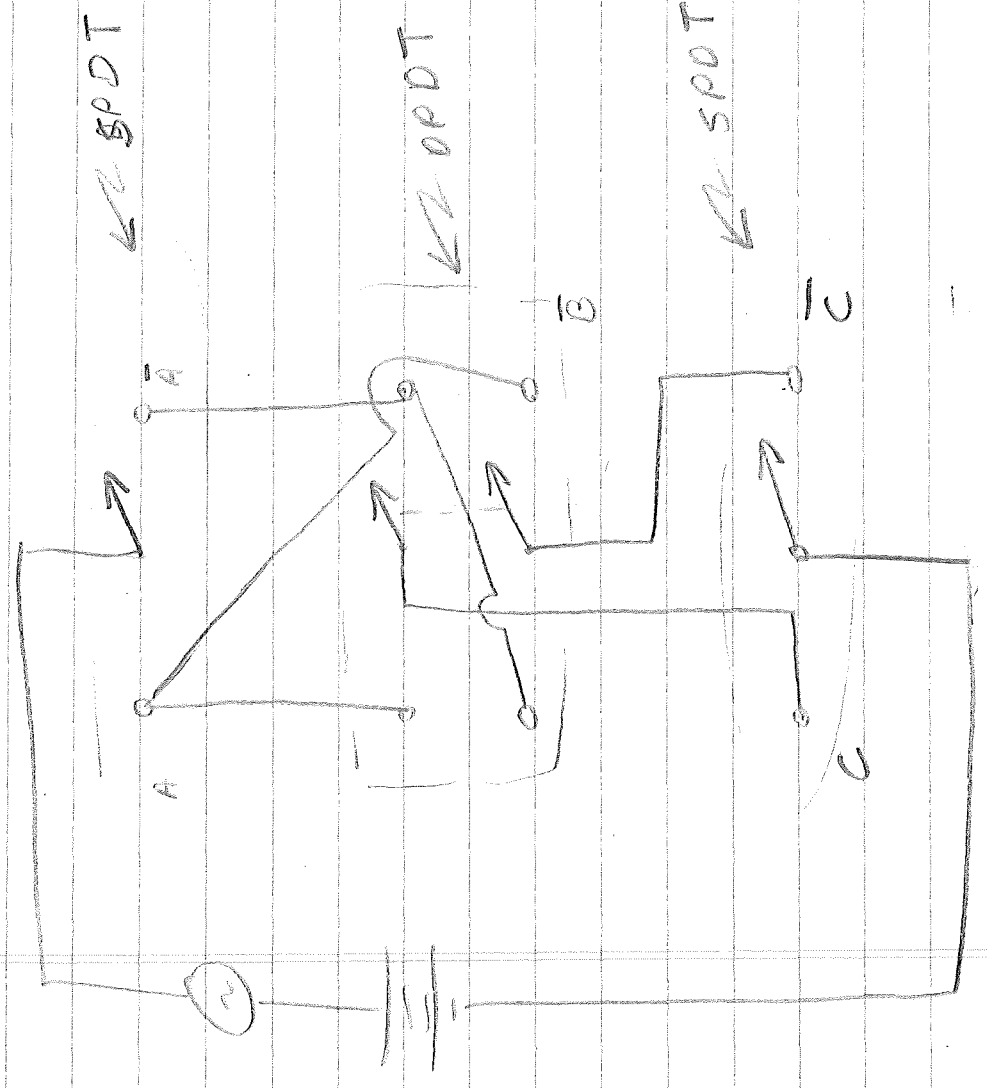
$$= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + BC)$$



TEST #3

5 PROBLEMS, 20 PTS PER PROBLEM

1. TRUTH TABLE FABRICATION, LOGIC CIRCUIT DESIGN

2. PARITY BIT ERROR CODING,

BINARY SYMMETRIC CHANNEL

3. SWITCHING, BOOLEAN FUNCTIONS FROM

TRUTH TABLES.

4. LOGIC GATES




5. BINARY SYMMETRIC CHANNEL, HAMMING CODE,

IMPORTANT:

BRING COPY ON VINE'S BOOK
AND CALCULATOR THAT CAN
COMPUTE Y^X .

EX: D'ARSONVAL MECHANISM

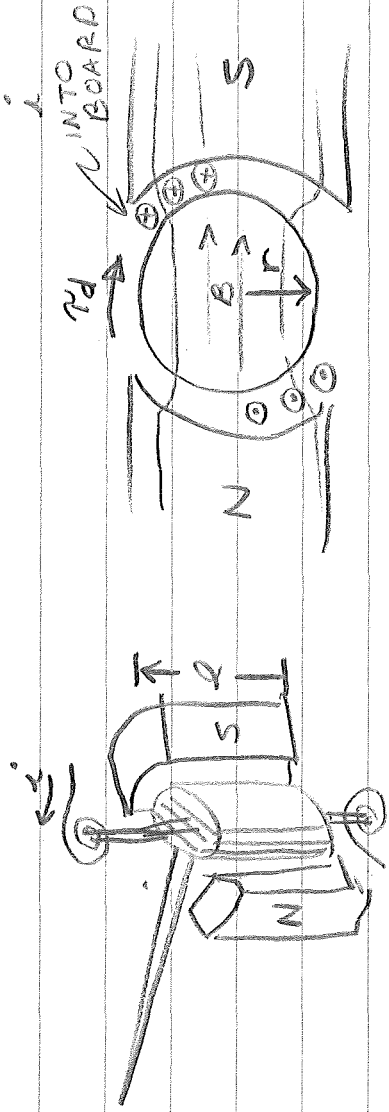

$$\tau_d = f_d \cdot r$$

$$f_d = B \hat{l} i$$

N WINDINGS EACH WITH TWO SIDES

$$\hat{l} = 2NB$$

$$\Rightarrow f_d = B 2NB \hat{l} i \Rightarrow \tau_d = 2NB \hat{l} r i$$

$$= k_M i$$

FROM THE SPRINGS:

$$\tau_s = \ominus / K_R$$

K_R = ROTATIONAL COMPLIANCE

$$\tau_s = \tau_d \Rightarrow \ominus = (2NB \hat{l} r K_R) i = k_{\ominus} i$$



\therefore ROTATION IS PROP. TO CURRENT

CIRCUIT:

$J = \text{ROTATIONAL INERTIA}$

$\omega = \frac{d\theta}{dt} = \text{ANGULAR VELOCITY}$

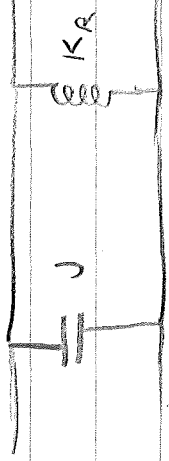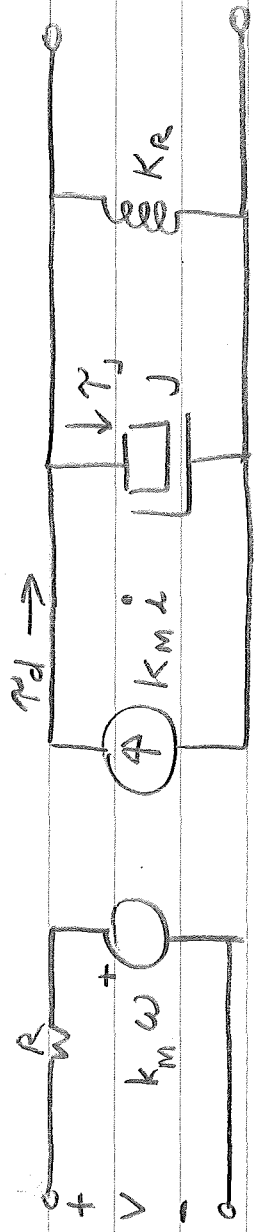$K_r = \text{COMBINED SPRING COMPLIANCE}$



$$\tau = \left(\frac{L}{R} \right) = \frac{K_R}{J}$$

FINAL: OPEN BOOK & NOTE

100 T-F \Rightarrow 200 PTS

4 PROBLEMS \Rightarrow 50 PTS/PROB \Rightarrow 200 PTS

MAJOR TOPICS COVERED:

✓ 1. DIODES AND RECTIFIERS

✓ 2. FET AND BJT CIRCUITS

- BIASING
- EQUIV. CIRCUITS

✓ 3. LINEAR SYSTEM THEORY

- LAPLACE

- XFER FUNCTIONS & FREQ RESPONSE

- FEEDBACK

✓ 4. SAMPLING THEOREM & FOURIER SERIES

✓ 5. RELIABILITY (SYSTEM EFFECTIVENESS)

✓ 6. IMPEDANCE BRIDGES

✓ 7. OP AMPS

✓ 8. MODULATION & MULTIPLEXING

✓ 9. CODING & BINARY CHANNELS

✓ 10. BOOLEAN LOGIC AND GATES

✓ 11. ELECTRO-MECHANICS

- MECHANICAL CIRCUITS

- MOTORS & GENERATORS

FINAL GRADE

$G = (0.1) (\text{HW } 9\%) + (0.4) (T 9\%)$

\uparrow 300PTS \uparrow 300PTS


$+ (0.2) (L 9\%) + (0.3) (F 9\%)$

\uparrow 400PTS


$0 < G < 100\%$

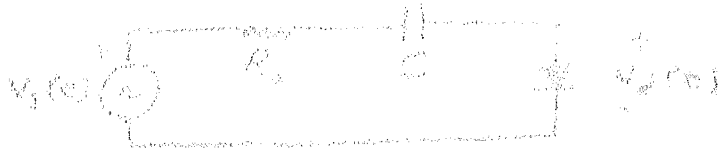1. Diode Clamping and Voltage Doubling

Consider the following circuit. First, $V_1(t)$ shows that $V_1(t) = V_m \sin \omega t$. After the circuit has reached steady state, the voltage across the diode is $V_2(t)$ which is the peak value of $V_1(t)$ clamped with the circuit. The circuit is shown below.



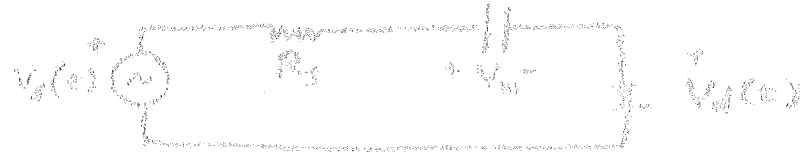(a) As $V_1(t)$ first starts to rise, the diode is forward biased and the capacitor charges to (approximately) the peak value of $V_1(t)$ which is V_m . It furthermore retains this charge in the steady state. As such, we have the circuit:




Assuming negligible voltage drop across R_1 , we find, from Kirchhoff's voltage law, that

$$V_2(t) = V_1(t) - V_m$$


$$= V_m [\sin \omega t - 1]$$

Our source voltage looks like

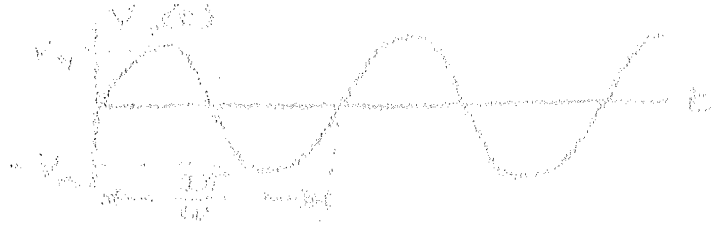

Thus our diode voltage is

$$V_2(t) = V_1(t) - V_m$$

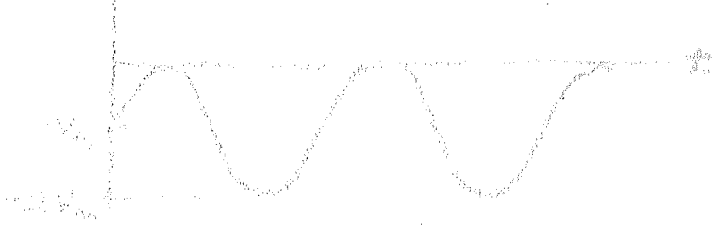

(b) We call this circuit a "diode clamper" since it "clamps" the sinusoidal input to the V_m axis.

$$V_{rms} = \frac{V_m}{\sqrt{2}} = 1$$

$$V_{oc} = \frac{1}{T} \int_0^T v_o(t) dt = \frac{1}{2\pi} \int_0^{2\pi} (1 - \sin \omega t) dt$$

$$= \frac{1}{2\pi} \left[\frac{t}{\omega} - \frac{\cos \omega t}{\omega} \right]_0^{2\pi} = V_m$$

$$V_{rms}^2 = \frac{1}{T} \int_0^T v_o^2(t) dt$$

$$= \frac{1}{2\pi} \int_0^{2\pi} (1 - \sin \omega t)^2 dt$$

$$= \frac{1}{2\pi} \omega V_m^2 \left[\int_0^{2\pi/\omega} dt - 2 \int_0^{2\pi/\omega} \sin \omega t dt + \int_0^{2\pi/\omega} \sin^2 \omega t dt \right]$$

$$= \frac{1}{2\pi} \omega V_m^2 \left[\frac{t}{\omega} - 2(0) + \frac{1}{2} \int_0^{2\pi/\omega} [1 - \cos 2\omega t] dt \right]$$

$$= \frac{1}{2\pi} \omega V_m^2 \left[\frac{2\pi}{\omega} + 0 + \frac{1}{2} \left(\frac{2\pi}{\omega} - 0 \right) \right]$$


$$= \frac{1}{2\pi} \omega V_m^2 \left(\frac{3\pi}{\omega} \right)$$

$$= \frac{3}{4} V_m^2$$


$$\Rightarrow r = \frac{3/4 V_m^2}{V_m^2} = 1 \cdot \frac{3}{4} = \frac{3}{4} \Rightarrow r = \frac{1}{\sqrt{2}}$$

20.707

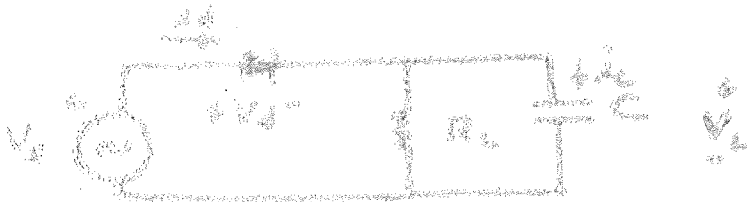
2. FOR THE HALF-WAVE RECTIFIER WITH CAPACITIVE FILTER, SKETCH THE SOURCE VOLTAGE, DIODE VOLTAGE, AND DIODE CURRENT ON THE SAME GRAPH. DOCUMENT YOUR RESULTS.



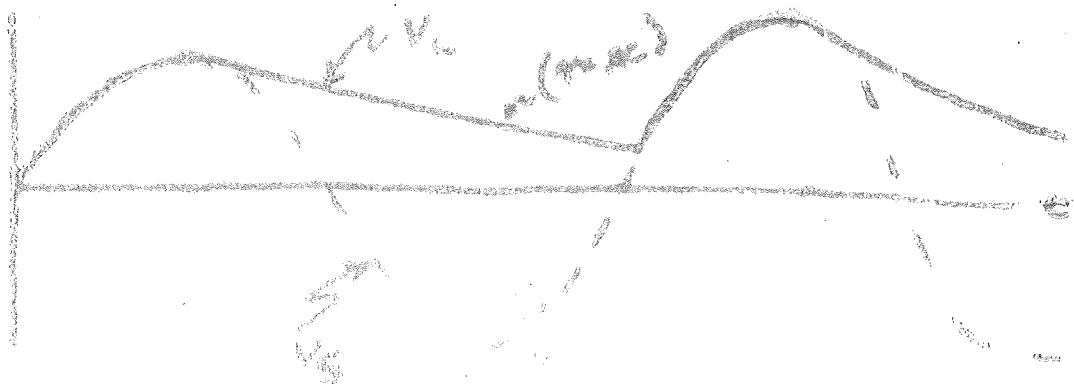
THE GRAPH OF SOURCE VOLTAGE VS. V_L WAS GIVEN IN CLASS:



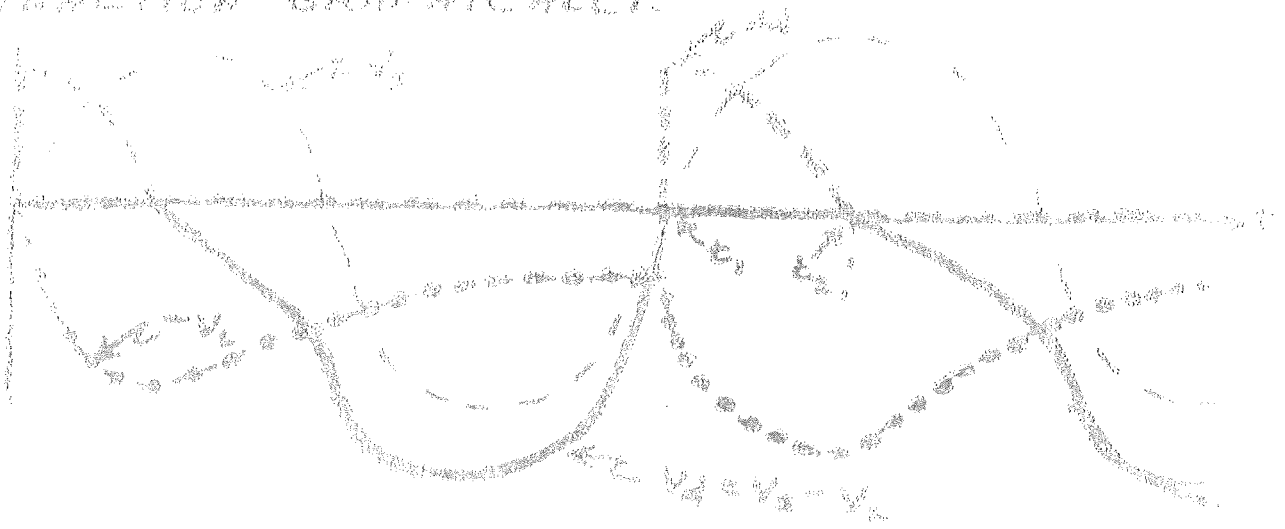FROM KIRCHHOFF'S VOLTAGE LAW: $V_d = V_s - V_L$
 FROM THE PREVIOUS SKETCH, WE MAKE THIS
 SUBSTITUTION GRAPHICALLY:



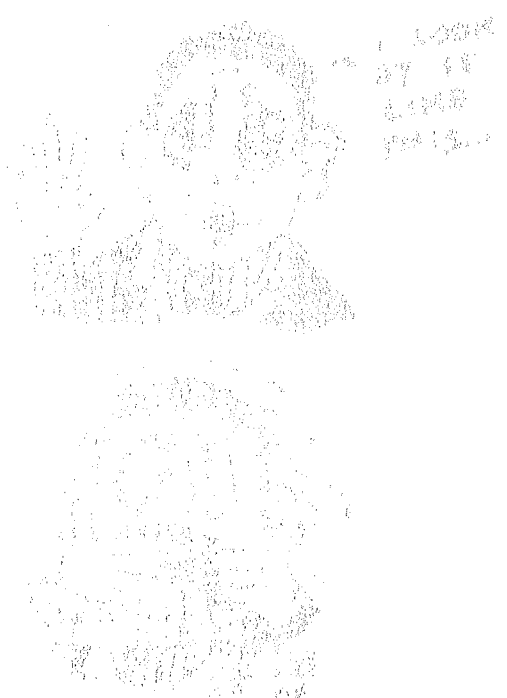THE DIODE WILL BE CONDUCTING IN THAT REGION DURING
 THE TIME WHEN $V_d > 0$. AT t_1 , THE SUPPLY VOLTAGE
 V_s , SLIGHTLY EXCEEDS V_L AND THE DIODE CONDUCTS.
 THE DIODE CURRENT RISES ACCORDING TO EQUATION
 1. RELATION $i_d = C dv/dt$ AND THEN
 GOES BACK DOWN TO ZERO.



"WHATEVER THE MIND OF
 MAN CAN CONCEIVE AND
 BELIEVE, IT CAN ACHIEVE"

NAPOLEON HILL.


1. (a) SHOW THAT, IF $X(s) = \int_0^\infty [x(t)] e^{-st} dt$ AND $x(t) = 0$ FOR $t < 0$, THEN $\int_0^\infty [x(t-\tau)] e^{-st} dt = X(s) e^{-s\tau}$

(b) THE INPUT-OUTPUT RELATION OF A LINEAR TIME-INVARIANT SYSTEM CAN BE EXPRESSED BY THE "CONVOLUTION INTEGRAL"

$$y(t) = \int_0^\infty x(\tau) \phi(t-\tau) d\tau$$

WHERE $\phi(t) = \mathcal{L}^{-1}[T(s)]$. USING THE RESULTS OF (a), SHOW THAT IT FOLLOWS THAT $Y(s) = X(s) T(s)$.

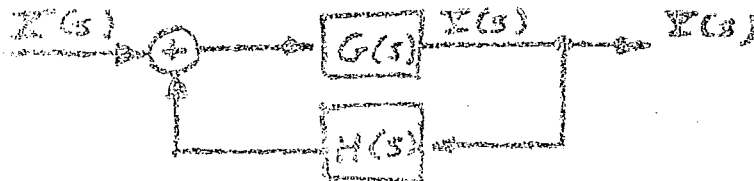2. CONSIDER TWO SYSTEMS CONNECTED IN A "FEEDBACK" CONFIGURATION:



DERIVE THE TRANSFER FUNCTION $T(s) = \frac{Y(s)}{X(s)}$ (HINT: SEE P. 233 OF SMITH)

3. CLASSIFY THE FOLLOWING SYSTEMS ACCORDING TO LINEARITY, TIME INVARIANCE, AND CAUSALITY.

(a) $y(t) = \frac{d^2}{dt^2} x(t)$

(d) $y(t) = [x(t) - 1]^2$

(b) $y(t) = a x(t) + b$

(e) $y(t) = t x(t)$

(c) $y(t) = \int_0^t x(\tau) d\tau$

(f) $y(t) = x(t-4)$

WHICH SYSTEMS CAN WE USE LAPLACE TRANSFORMS ON?


4. FOR THE FOLLOWING CIRCUIT

(a) FIND THE TRANSFER FUNCTION $T(s) = \frac{V_o(s)}{V_i(s)}$

(b) FIND THE OUTPUT FOR $V_i(t) = V_o \cos(\omega t)$

(c) DISCUSS YOUR RESULT IN (b)

(d) COMPUTE AND SKETCH THE FREQUENCY RESPONSE $|T(j\omega)|$.

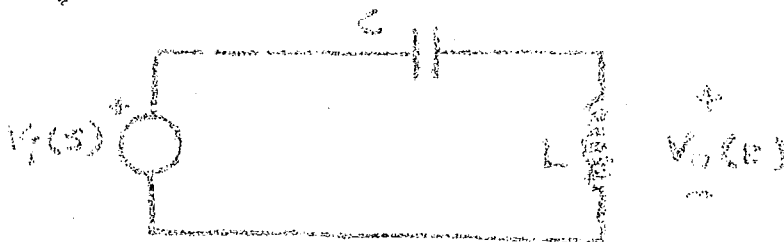

HOMEWORK # 2: SOLUTIONS

1. (a) $Y(s) = \mathcal{L}\{x(t-\tau)\} = \int_0^{\infty} x(t-\tau) e^{-st} dt$

Let $t' = t - \tau \Rightarrow dt' = dt$

$\Rightarrow Y(s) = \int_{-\tau}^{\infty} x(t') e^{-s(t'+\tau)} dt'$, BUT $x(t) = 0$ FOR $t < 0$

$\Rightarrow Y(s) = \int_0^{\infty} x(t') e^{-s(t'+\tau)} dt' = \int_0^{\infty} x(t') e^{-st'} dt' e^{-s\tau}$
 $= \int_0^{\infty} x(t') e^{-st'} dt' e^{-s\tau} = X(s) e^{-s\tau}$


(b) $y(t) = \int_0^{\infty} x(\tau) \gamma(t-\tau) d\tau$

$\mathcal{L}\{y(t)\} = \int_0^{\infty} x(\tau) \mathcal{L}\{\gamma(t-\tau)\} d\tau = \int_0^{\infty} x(\tau) \mathcal{L}\{\tau(t) e^{-s\tau}\} d\tau$

$= \int_0^{\infty} x(\tau) e^{-s\tau} d\tau \mathcal{L}\{\tau(t)\} = \mathcal{L}\{x(t)\} \mathcal{L}\{\tau(t)\}$

THUS $Y(s) = X(s) T(s)$

2.

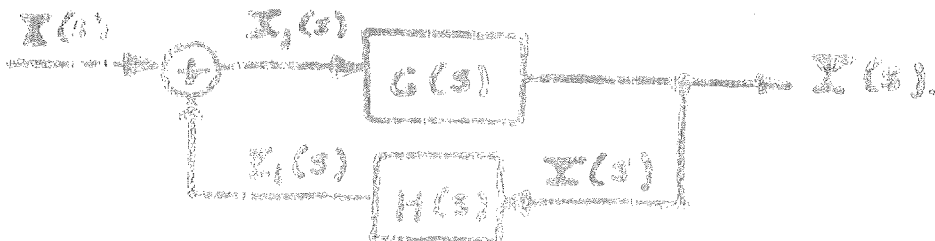

$X_1(s) = X(s) + X_2(s) = X(s) + Y(s)H(s)$ (1)

ALSO $Y(s) = X_1(s)G(s) \Rightarrow X_1(s) = Y(s)/G(s)$ (2)

EQUATING (1) AND (2):

$X(s) + Y(s)H(s) = Y(s)/G(s)$

SOLVING FOR $Y(s)$ GIVES $\Rightarrow Y(s) = \frac{G(s) X(s)}{1 + G(s)H(s)}$

THUS $T(s) = \frac{Y(s)}{X(s)} = \frac{G(s)}{1 + G(s)H(s)}$

3. (a) $y(t) = \int_{-\infty}^t x(\tau) d\tau$

$= \int_{-\infty}^t [a x_1(\tau) + b x_2(\tau)] d\tau = a \int_{-\infty}^t x_1(\tau) d\tau + b \int_{-\infty}^t x_2(\tau) d\tau$ ← LINEAR

$y(t-\tau) = \int_{-\infty}^{t-\tau} x(\tau) d\tau$ ← TIME INVARIANT

$y(t)$ DEPENDS ONLY ON $x(t)$ TO t ← CAUSAL

(b) $y(t) = c x(t) + b$

$= [c x_1(t) + b] + [a x_2(t) + b] \neq a [x_1(t) + x_2(t)] + b$ ← NOT LINEAR

$y(t-\tau) = c x(t-\tau) + b$ ← TIME INVARIANT

$=$ CAUSAL

(c) $y(t) = \int_0^t x(\tau) d\tau$

$= c \int_0^t x_1(\tau) d\tau + b \int_0^t x_2(\tau) d\tau = \int_0^t [c x_1(\tau) + b x_2(\tau)] d\tau$ ← LINEAR



$y(t-\tau) = \int_0^{t-\tau} x(\tau) d\tau$ ← TIME INVARIANT

$=$ CAUSAL

- (a) $y(t) = [x(t) - d]^2$
- $[x_1(t) + x_2(t) - d]^2 \neq [x_1(t) - d]^2 + [x_2(t) - d]^2$ (not linear)
 - $y(t) = x(t - m) - d$ is TIME-INVARIANT
 - CAUSAL

- (b) $y(t) = 0$ for $t < 0$
- $y(t) = x(t) + x_2(t) = x(t) + 0$ for $t < 0$ (causal)
 - $y(t) = x(t) + x_2(t)$ is TIME-VARIANT (input time change)
 - CAUSAL

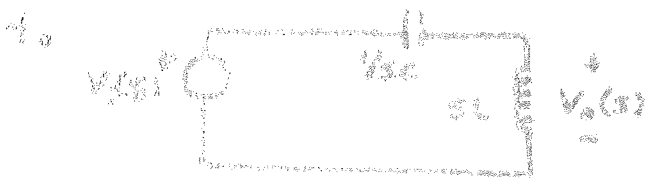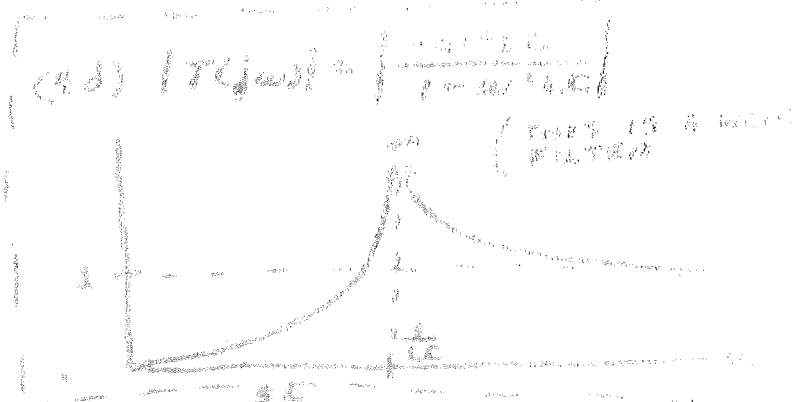- (c) $y(t) = x(t)$
- LINEAR
 - TIME INVARIANT
 - ~~CAUSAL~~ CAUSAL



(e) BY VOLTAGE DIVIDER: $V_2(s) = \frac{SL}{SL + \frac{1}{j\omega C}} V_1(s)$

$\Rightarrow T(s) = \frac{V_2(s)}{V_1(s)} = \frac{SL}{SL + \frac{1}{j\omega C}} = \frac{SLC}{1 + j\omega LC}$

(f) $V_1(s) = \frac{1}{s} \Rightarrow V_1(s) = \frac{1}{s}$

$V_2(s) = T(s) V_1(s) = \frac{SLC}{1 + j\omega LC} = \frac{V_0}{\left(\frac{\omega}{\omega_c}\right)^2 + 1}$


FROM LAPLACE TRANSFORM TABLE:

$V_2(s) = V_0 \cos \frac{1}{LC} t$

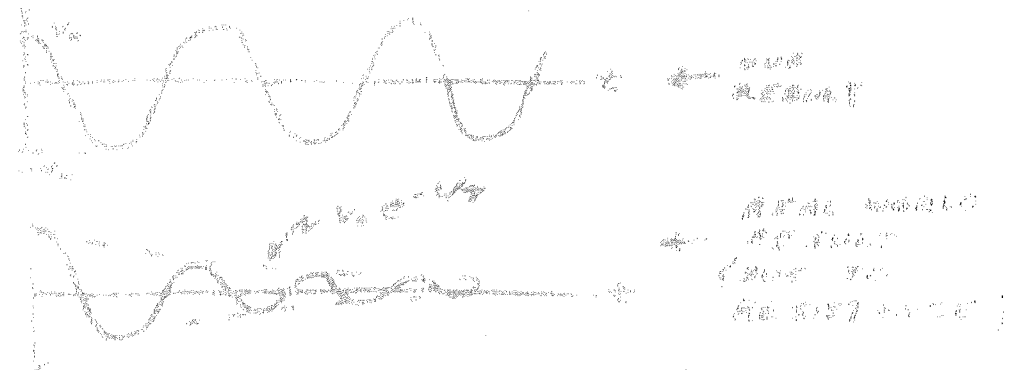(g) THIS CIRCUIT IS AN OSCILLATOR. IN PRACTICE, THE COSINE WILL BE "DAMPED" SINCE SOME RESISTANCE IN THE CIRCUIT WILL ABSORB POWER IN ACTUAL PHYSICAL WORLD


$V_2(t) = V_0 \cos \omega t e^{-\gamma t}$

WHERE γ IS DETERMINED BY CIRCUIT PARAMETERS



1/2 (1000 Hz) = 500 Hz (1000/2) Hz

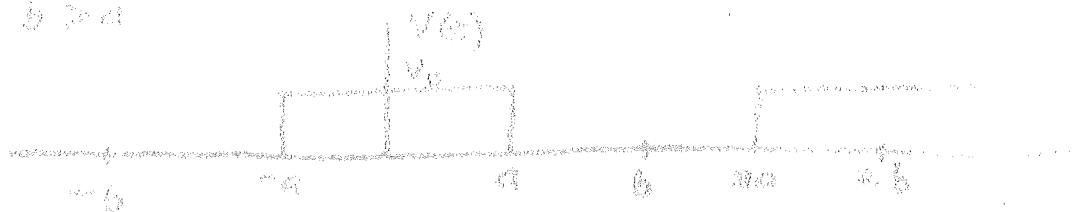FOR THE FOLLOWING PERIODIC WAVEFORM $x(t)$ FIND THE FOURIER SERIES COEFFICIENTS, α_n , AND THAT $b > a$



[HINT: $\frac{1}{j} [e^{j\theta} - e^{-j\theta}] = \sin\theta$]

(A) ASSUME THAT $b = 2a$, WHAT IS α_n FOR

$n = 0$ [HINT: $\lim_{n \rightarrow \infty} \frac{\sin n\pi}{n\pi} = 1$]

n EVEN

$n = 1, 5, 9, 13, 17, \dots$

$n = 3, 7, 11, 15, 19, \dots$

(C) PLOT $\pi |\alpha_n| / V_0$ FOR n UP TO 7.

(2) FOR $x(t) = \sum_{n=-\infty}^{\infty} \alpha_n e^{jn\pi t/T}$

(A) SHOW THAT $\int_{-a}^b x(t) dt = \sum_{n=-\infty}^{\infty} \alpha_n \int_{-a}^b e^{jn\pi t/T} dt$

[HINT: $\int_{-a}^b e^{jn\pi t/T} dt = \frac{1}{j n \pi} [e^{jn\pi b/T} - e^{-jn\pi a/T}]$]

(B) PROVE "PARSEVAL'S THEOREM"

$$\int_{-a}^b |x(t)|^2 dt = \sum_{n=-\infty}^{\infty} \frac{|\alpha_n|^2}{2T}$$

[HINTS: $|\sum_n B_n|^2 = \sum_n \sum_m B_n B_m^*$


$$\int_{-T}^T e^{jn\pi t} e^{-jm\pi t} dt = \frac{1}{T} \delta_{nm}$$

$$\delta_{nm} = \begin{cases} 1 & ; n=m \\ 0 & ; n \neq m \end{cases} \text{ = KRONECKER D.}$$

(3) JOHNNY CASH AND TINY TIM (LO & HI VOICES) REC. A 3 MINUTE 55 SECOND RECORDING. IF NEITHER VOICE EXCEEDED 20 kHz (= 20,000 CYCLES/SEC) WE WISHED TO STORE THE RECORD IN SAMPLE FORM, HOW MANY SAMPLES WOULD WE NEED TO STORE? IF WE LOST EVERY OTHER SAMPLE, WOULD VOICE BE DISTORTED? WHY?

NO

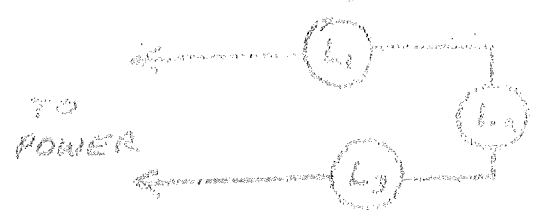(4) CONSIDER A SYSTEM CONSISTING OF THREE LIGHTBULBS HOOKED IN SERIES.



WE CONSIDER THE SYSTEM OPERATIONAL IF TWO OR MORE OF THE LIGHTS ARE ON.

(a) ASSUMING THAT THE MTBF OF EACH BULB IS TWO MONTHS, AND THAT THEY ARE ON THE RANDOM FAILURE PORTION OF THE BATHTUB CURVE, COMPUTE THE SYSTEM MTBF AND THE PROBABILITY THAT THE SYSTEM WILL BE DOWN FOR TWO MONTHS OF USE.

(b) IF IT TAKES 30 MINUTES (ON AVERAGE) TO REPLACE A BULB, COMPUTE THE SYSTEM AVAILABILITY. (ASSUME 1 MONTH OF USE.)


(c) CONSIDERING OUR DEFINITION OF RELIABILITY, SUGGEST A BETTER WAY OF CONNECTING THE LIGHTS SO THAT THE OPERATIONAL RELIABILITY IS INCREASED. FOR THIS EFFECT THE SYSTEM CAN BE MAINTAINED. [CAN YOU COMPUTE THE MTBF OF THE NEW SYSTEM?]

(d) IN THE IMPROVED SYSTEM OF (c) EXPLAIN HOW THE AVAILABILITY AND RELIABILITY OF THE SYSTEM CAN BE IMPROVED BY INTRODUCING THE CONCEPT OF "PREVENTATIVE MAINTENANCE". WILL THIS EFFECT THE MTBF?

* i.e., REPLACING A BURNT OUT BULB BEFORE THE SYSTEM IS "UNOPERABLE"

"HE THAT REPOSETH INSTRUCTION ON HIS OWN SOUL."


PROBLEM 10.10 (continued) (b) $b > a$

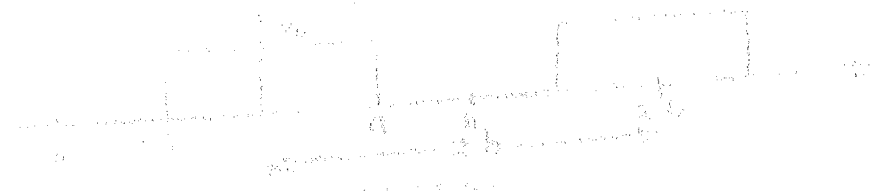

$b > a$

$$\begin{aligned}
 (a) \quad a_n &= \frac{1}{a} \int_{-a/2}^{a/2} e^{j n \pi t / b} dt \\
 &= \frac{1}{a} \left[\frac{e^{j n \pi t / b}}{j n \pi / b} \right]_{-a/2}^{a/2} \\
 &= \frac{1}{a} \frac{b}{j n \pi} \left[e^{j n \pi a / 2b} - e^{-j n \pi a / 2b} \right] \\
 &= \frac{b}{a} \frac{2 \sin(n \pi a / 2b)}{j n \pi} \\
 &= \frac{2b}{a n \pi} \sin(n \pi a / 2b)
 \end{aligned}$$
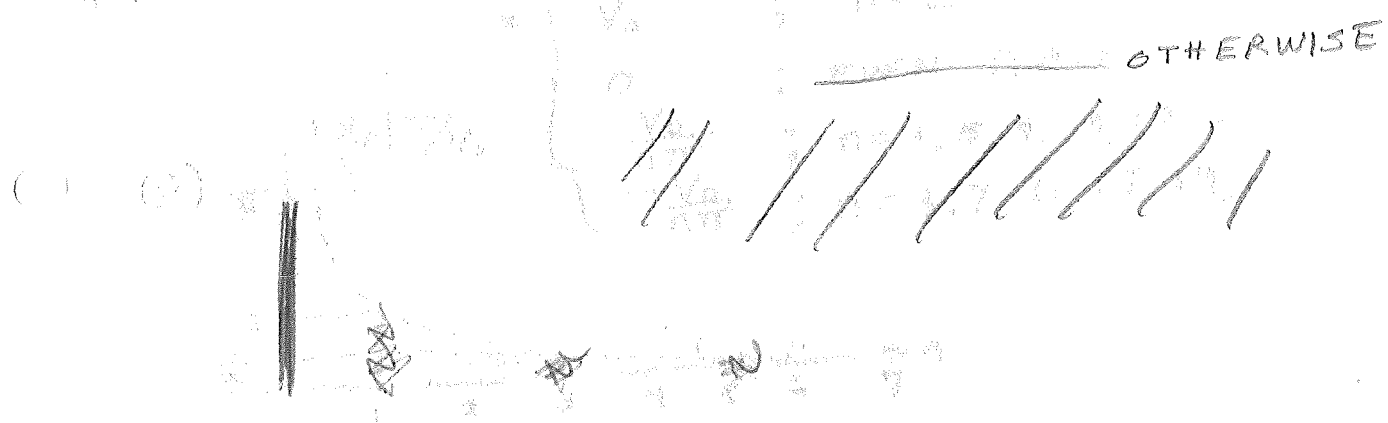
$$(b) \quad b = 20 \Rightarrow a_n = \frac{20}{a n \pi} \sin(n \pi a / 40)$$



$$\begin{aligned}
 (c) \quad x(t) &= \sum_{n=-\infty}^{\infty} a_n e^{j n \pi t / b} \\
 \int_{-a/2}^{a/2} x(t) dt &= \sum_{n=-\infty}^{\infty} a_n \int_{-a/2}^{a/2} e^{j n \pi t / b} dt = \sum_{n=-\infty}^{\infty} a_n \frac{2 \sin(n \pi a / 2b)}{j n \pi} \\
 \int_{-a/2}^{a/2} x(t) dt &= \sum_{n=-\infty}^{\infty} \sum_{m=-\infty}^{\infty} a_n a_m^* e^{j n \pi t / b} \\
 \int_{-a/2}^{a/2} x(t) dt &= \sum_{n=-\infty}^{\infty} \sum_{m=-\infty}^{\infty} a_n a_m^* \frac{2 \sin(n \pi a / 2b)}{j n \pi} \\
 &= \sum_{n=-\infty}^{\infty} |a_n|^2 \frac{2 \sin(n \pi a / 2b)}{j n \pi} \\
 &= \sum_{n=-\infty}^{\infty} |a_n|^2
 \end{aligned}$$

(3) $S = \text{TOTAL SAMPLES}$

$$= (3 \text{ MIN } 55 \text{ SEC}) (2 \times 20 \text{ MHz})$$

$$= (235 \text{ SEC}) (40,000 / \text{SEC}) = 9.4 \text{ MILLION SAMPLES}$$

UNDER-SAMPLING DISTORTS THE ORIGINAL FREQUENCIES. THUS, TINY TINY, HIGH FREQUENCY HIGHER VOICE, WOULD BE DISTORTED.

NO (4) SINCE ONE LIGHT BULB FAILING CAUSES IN SYSTEM FAILURE, THE SYSTEM MTBF IS

$$MTBF_s = \frac{MTBF_L}{3} = \frac{2}{3} \text{ MONTH}$$

$$R_s(t) = e^{-t/MTBF_s} = R_s(2 \text{ MONTH}) = e^{-3}$$

$$= e^{-3} \approx 0.05 \Rightarrow \text{THERE IS ABOUT A}$$


5% CHANCE THE SYSTEM WILL OPERATE FOR TWO STRAIGHT MONTHS.

(b) $MTTR = 30 \text{ MIN}$

$$A = \frac{MTBF}{MTBF + MTTR} = \frac{\frac{2}{3} \times 30 \times 24 \times 60}{\frac{2}{3} \times 30 \times 24 \times 60 + 30}$$

$$= \frac{28800}{28830} = 99.896\%$$

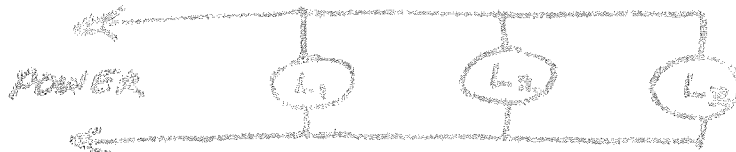(c) IT WOULD BE BETTER TO CONNECT LIGHTS IN PARALLEL




HERE, IF ONLY ONE LIGHT FAILS, THE SYSTEM IS STILL "OPERABLE"

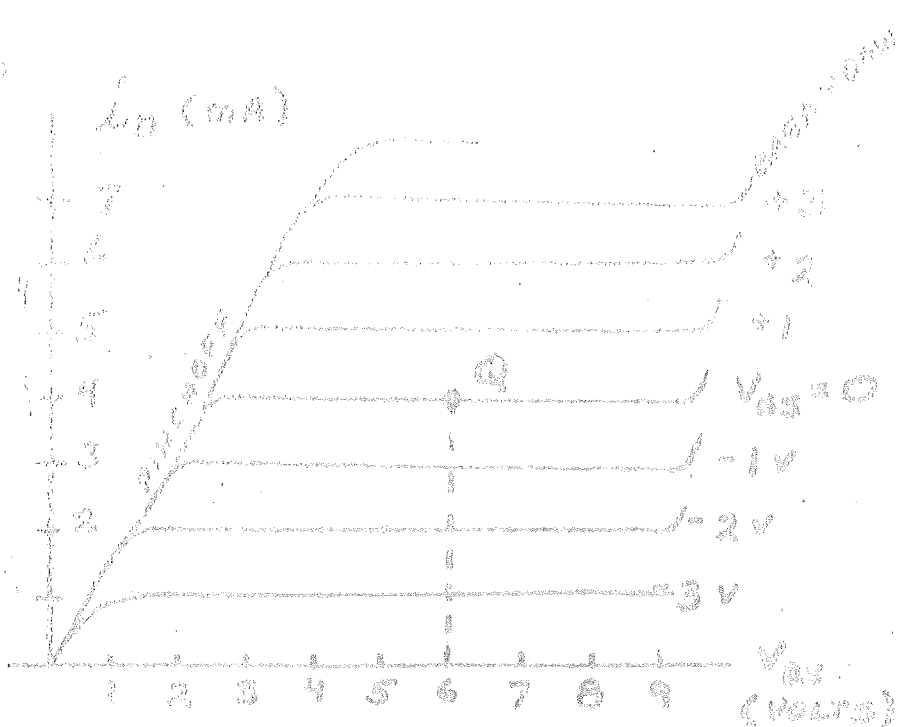(d) BY REPLACING A LIGHT WHICH HAS BURNT OUT WHILE THE SYSTEM IS "OPERABLE" WE ARE PERFORMING "PREVENTIVE MAINTENANCE"



THE MTTR IS ^{REDUCED} STILL THE SAME, BUT THE MTBF (AND THUS THE AVAILABILITY) IS INCREASED.

"HE THAT HANDETH A MATTER WISELY SHALL FIND GOOD AT THE END." TRUSTETH IN THE LORD, HAPPY IS HE"



DUE MARCH 1

OF MOSFET

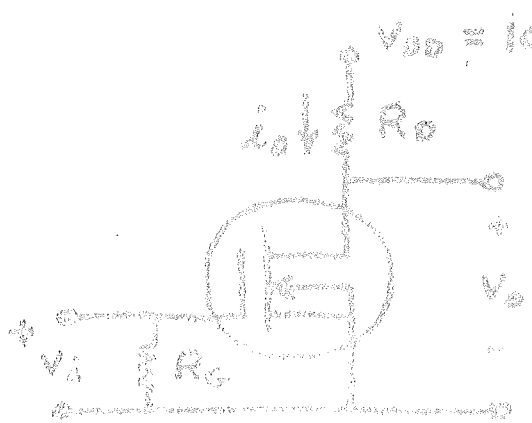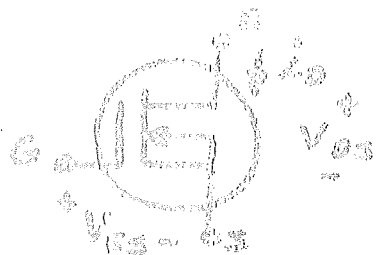

(a) DETERMINE R_D TO ESTABLISH QUIESCENCE AT THE POINT INDICATED. $V_{DD} = 10V$


(b) DETERMINE THE EQUATION FOR THE LOAD LINE AND SKETCH IT ON THE ABOVE

OF MOSFET $V-I$ CURVE.

(c) FROM (b), MAKE A PLOT OF SOME POINTS FOR THE CURVE I_D vs. V_{GS} . ASSUMING V_{GS} IS THE INPUT AND I_D THE OUTPUT, WHAT IS THE "GAIN" OF THIS TRANSDUCER IN MMDS?

(d) GIVE AN ESTIMATE OF THE INTERVAL V_{GS} MUST BE LIMITED TO TO AVOID "GROSS OUTPUT 'DISTORTION'"

(2) OUR TRANSISTOR D.C. MODEL WAS

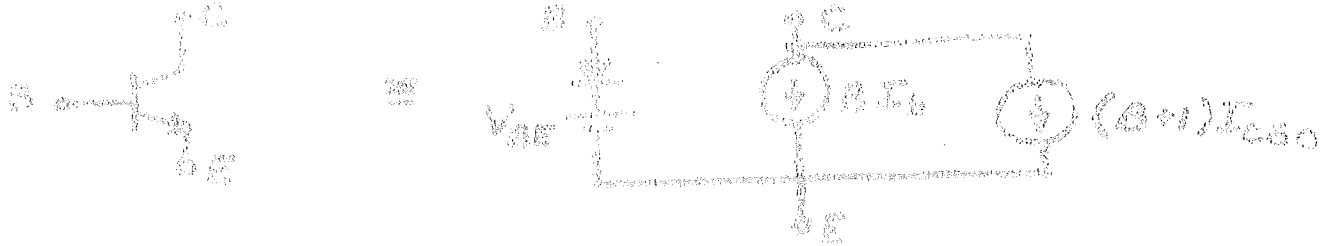

(a) FOR $I_{CBO} = 5 \text{ nA}$, SKETCH I_C (VERTICAL AXIS) VS. V_{CE} ON THE SAME GRAPH FOR

$I_B = 0.1, 0.2, 0.3, 0.4 \text{ mA}$. ASSUME $\beta = 100$

(b) REPEAT (a) FOR $\beta = 200$. HOW HAS THE CURVE CHANGED?

(c) COMPARE YOUR SKETCH IN (a) TO THE CORRESPONDING TRANSISTOR CURVE.

(d) EXPLAIN WHY WE WOULD REQUIRE $I_B > 0$ (IN THE MODEL AND PHYSICALLY)

(3) IN A CERTAIN TRANSISTOR, THE PARAMETERS CHANGE WITH TEMPERATURE BUT ARE KNOWN TO FALL WITHIN THE BOUNDS:

$$30 < \beta < 180$$

$$0.5 < V_{BE} < 0.9 \text{ VOLTS}$$

$$1 < I_{CBO} < 10 \text{ nA}$$


BY ASSUMING WORST CASE CONDITIONS, FIND THE BOUNDS ON THE VARIATION OF I_C IN A SELF-BIASING CIRCUIT. THAT IS, FIND $I_{C \text{ minimum}}$ AND $I_{C \text{ maximum}}$ SUCH THAT

$$I_{C \text{ minimum}} \leq I_C \leq I_{C \text{ maximum}}$$

NOTE THAT THE CIRCUIT VALUES ARE

$$R_1 = 10 \text{ k}\Omega, R_2 = 100 \text{ k}\Omega, R_E = 1 \text{ k}\Omega$$
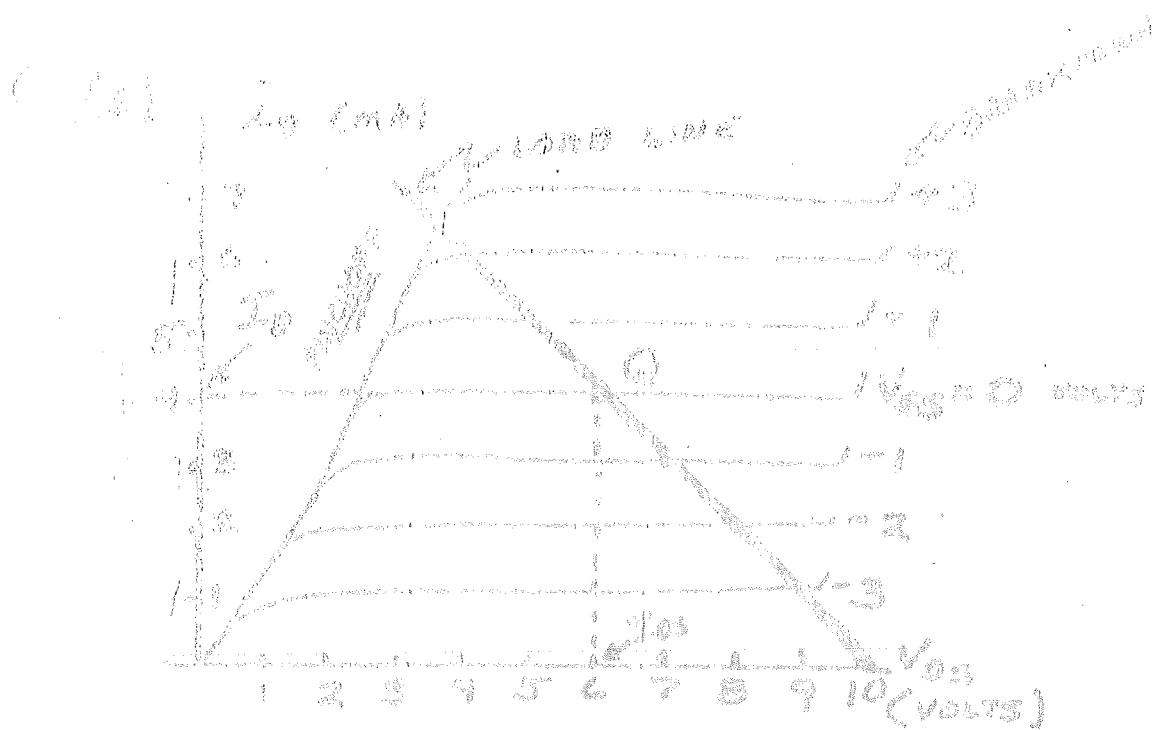
$$R_C = 5 \text{ k}\Omega \text{ AND } V_{CC} = 22 \text{ VOLTS}$$




(a) $V_{OS} = V_{OO} - R_D I_O$
 $\Rightarrow R_D = (V_{OO} - V_{OS}) / I_O = (10 \text{ volts} - 6 \text{ volts}) / 4 \text{ mA} = 1 \text{ k}\Omega$


(b) LOAD LINE: $V_{OS} = V_{OO} - R_D I_O$
 $\Rightarrow V_{OS} = 10 - 10^3 I_O$
 $\Rightarrow I_O = 10^{-3} (10 - V_{OS})$

(c) FROM LOAD LINE


V_{OS}	I_O (mA)
2	6
4	5
6	4
8	3
10	2
12	1

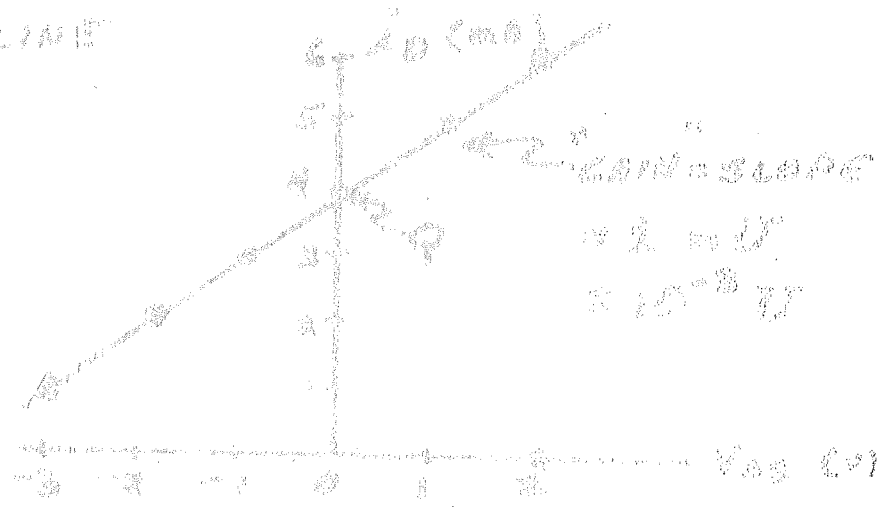



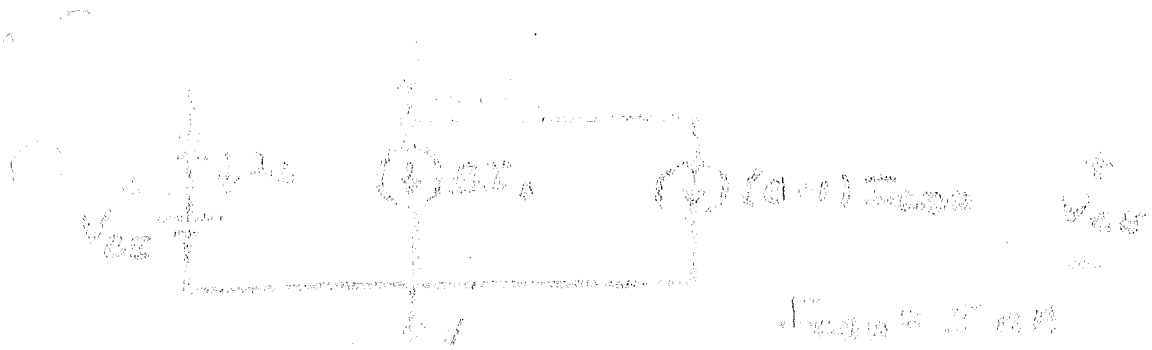
(d) For $V_{OS} > 2V$, we are in the "saturation" region.
 $V_{OS} < 2V$, we are in the "linear" region.
 REGION LIMIT IS $0 < V_{OS} < 2V$



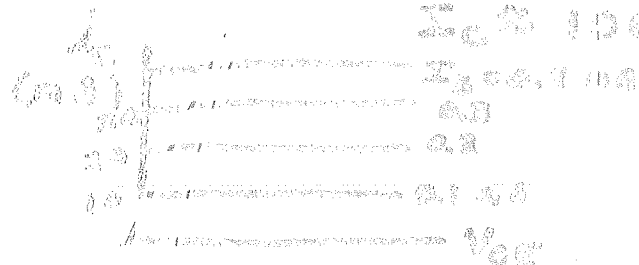(a) SUMMING CURRENT AT COLLECTOR: $I_C = \beta I_B + (1 + \beta) I_{EEO}$
 $\beta = 100$ $I_C = 100 I_B + 101 I_{EEO}$
 FOR $I_B = 0.1, 0.2, 0.3, 0.4$ mA
 $I_C \approx 100 I_B = 10, 20, 30, 40$ mA



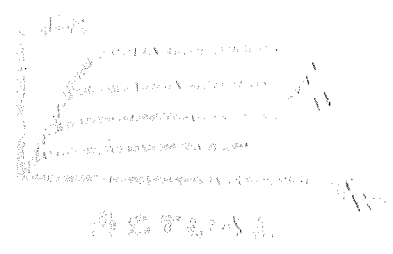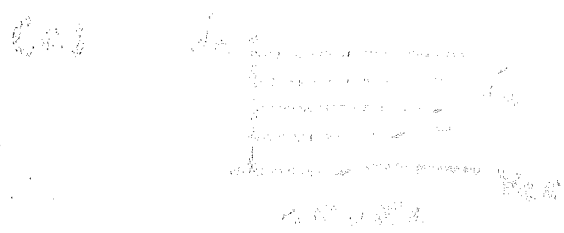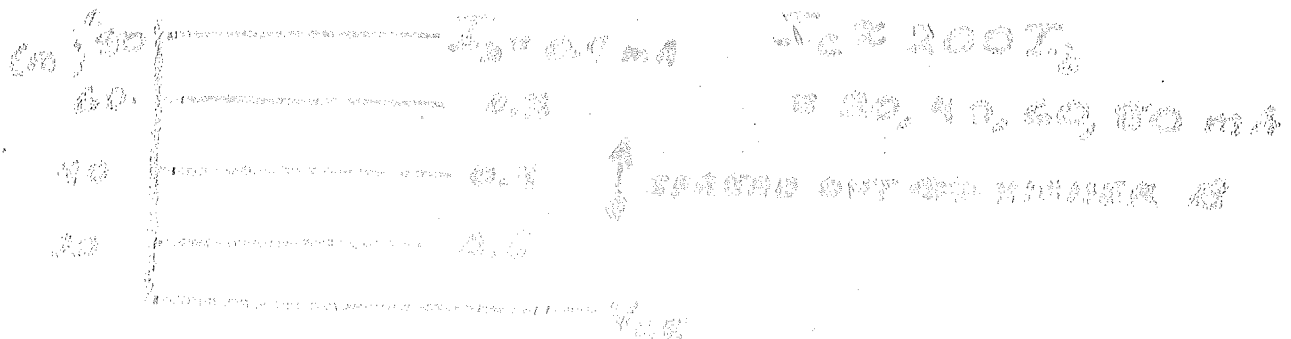
(b) FOR $\beta = 200$, CURVE IS SIMPLY "SPREADS OUT"



(c) I DO SIMPLY DO THAT "CAN BE" THROUGH THE BIAS IN OUR MODEL. (FOR THE BIAS CURRENT βI_B CURRENT IN OUR ACTUAL TRANSISTOR).

(d) THIS PROBLEM IS WORKED IN EXAMPLE 2, PAGE 42) OF SAITH, 3RD ED.

AC bridge circuit (10 marks) (30 marks)

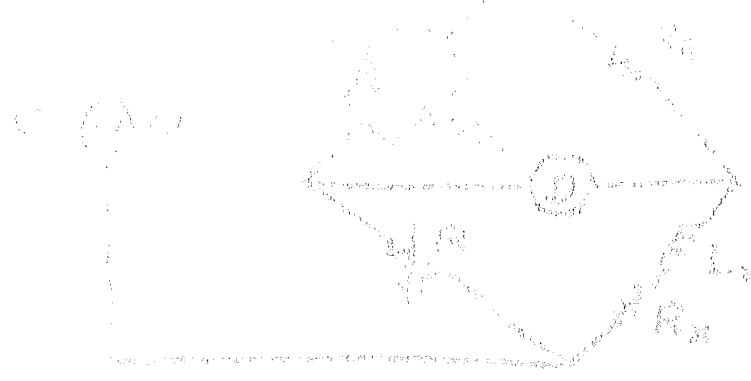

AC bridge, V and the unknowns, L_x and R_x are adjusted R_1 and R_2 until the

null detector, D , detects no voltage. Show that, when this bridge is balanced, that $R_x = RR_1/R_2$ and $L_x = C_0 RR_1$. (1) If the variable resistors have accuracy $\pm 1\%$, R_1 is $\pm 1\%$, and C_0 is $\pm 5\%$, find the accuracy of our measurements of L_x and R_x . (2) What dependence does our measurement have on the amplitude and frequency of our source. If none, why don't we set the amplitude and/or frequency to zero?



In this bridge, Z_1 and Z_2 are fixed, Z_3 is adjustable, and Z_4 is unknown. If this bridge is adjusted find Z_4 in terms of Z_1, Z_2 , and Z_3 . What happens if the source terminals of the bridge are shorted?




Now, Z_1 is fixed and Z_2, Z_3 and Z_4 are variable. Can the bridge be balanced? If so, find Z_4 in terms of Z_1, Z_2 , and Z_3 .

(NOT USE RESULTS FROM Q3)

EXTRA CREDIT: DISCUSS THE CREATION OF A...

HOMEWORK #5 SOLUTIONS (by Marcus J.)

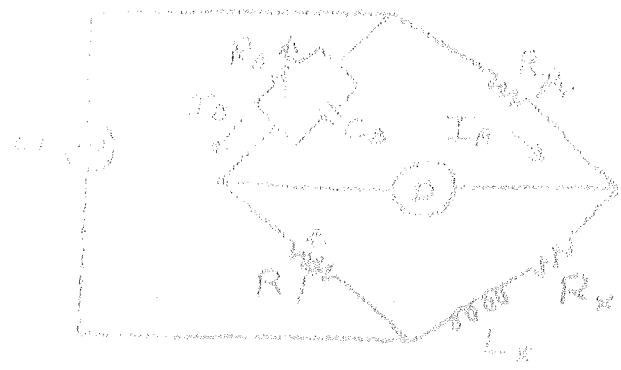

(a) UNDER BALANCED CONDITIONS

$$1^{\circ} I_B Z_B = I_A R_A$$

WHERE $Z_B = \frac{R_0 / j\omega C_0}{R_0 + \frac{1}{j\omega C_0}} = \frac{R_0}{1 + j\omega C_0 R_0}$

$$2^{\circ} I_B R = I_A Z_x$$

WHERE $Z_x = R_x + j\omega L_x$

DIVIDING 1^o BY 2^o AND SOLVING FOR Z_x GIVES:

$$Z_x = R_A R / Z_B = R_A R (j\omega C_0 R_0 + 1) / R_0$$

$$\Rightarrow R_x + j\omega L_x = \frac{R_A R}{R_0} + j\omega [C_0 R_A R]$$

EQUATING REAL & IMAGINARY COMPONENTS:

$$R_x = R_A R / R_0 \quad L_x = C_0 R_A R$$

$$(b) \epsilon[R_0] = [1 \pm 0.0001][1 \pm 0.0002][1 \pm 0.0005]$$

$$= 1 \pm 0.0008 \Rightarrow \pm 0.08\%$$

$$\epsilon[L_x] = [1 \pm 0.0005][1 \pm 0.0002][1 \pm 0.0001]$$

$$= 1 \pm 0.0008 \Rightarrow \pm 0.08\%$$

(c) THERE IS NO DEPENDENCE ON ω OR $v(t)$.
 IF WE SET EITHER TO ZERO, THEN ALL OUR EQUATIONS BECAME DEGENERATE, IN THE SENSE OF GOING TO ZERO, INFINITY, OR BEING UNDEFINED.



(1) WHEN THE VOLTAGE BETWEEN a & b IS ZERO, WE HAVE

$$\left. \begin{aligned} I_1 Z_1 &= I_3 Z_3 \\ I_2 Z_2 &= I_4 Z_4 \end{aligned} \right\} \Rightarrow \frac{I_1}{I_2} = \frac{I_3}{I_4} \Rightarrow Z_x = \frac{Z_1 Z_2}{Z_3}$$

(2) NOTICING, THE POTENTIAL AT a & b IS THE SAME

(3)



USING RESULTS OF (2): IF BRIDGE IS BALANCED

$$Z_x = \frac{Z_1 Z_2}{Z_3}$$

$$j\omega L_x = \frac{R_a}{R_b} \frac{1}{j\omega C}$$

$$-\omega L_x = \frac{R_a}{R_b} \frac{1}{\omega C} \Rightarrow L_x = -\frac{R_a}{R_b} \frac{1}{\omega^2 C}$$

BT, ALL INDUCTANCE MUST BE POSITIVE
 THUS, WE CONCLUDE THAT THE BRIDGE
 CANNOT BE BALANCED.

4000 2012 (SEE 130) MARKS

(1) A LARGE GAIN IS MANY TIMES EXPRESSED IN "DECIBELS" OR "db". THE DC GAIN, A_{00} , IS RELATED TO THE GAIN A_f (VOUT/VIN) BY THE RELATION

$$A_{00} = 20 \log_{10} A_f$$

(a) DESIGN AN OP AMP BASIC INVERTING CIRCUIT WITH A GAIN OF $A_{00} = 20$ db AND AN INPUT IMPEDANCE (RESISTANCE) OF 200Ω


(b) SAME AS (a), BUT $A_{00} = 40$ db

(c) IN GENERAL, IF WE DOUBLE THE db GAIN, A_{00} , WHAT MUST WE DO TO THE GAIN, A_f ?

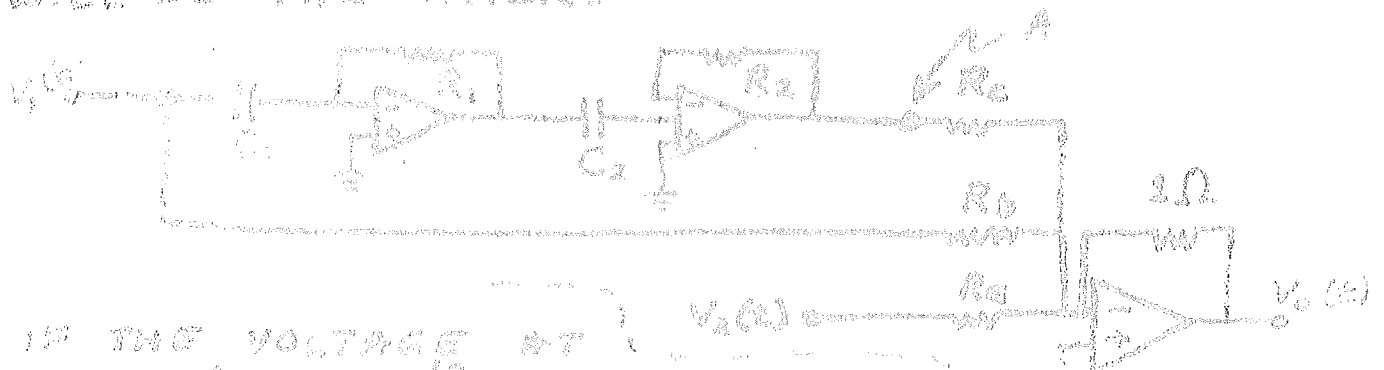(2) WE WISH TO COMBINE TWO VOLTAGES, $V_1(t)$ AND $V_2(t)$ INTO $V_0(t)$ WHERE

$$V_0(t) = a V_2(t) + b V_1(t) + c \frac{d^2 V_1(t)}{dt^2}$$

WHERE a , b , AND c ARE KNOWN NEGATIVE CONSTANTS. THE FOLLOWING ANALOG COMPUTER WILL DO THE TRICK:



IF THE VOLTAGE AT POINT A IS $\frac{d^2}{dt^2} V_1(t)$, FIND THE REQUIRED RELATIONSHIP BETWEEN THE PARAMETERS $R_1, C_1, R_2, C_2, R_3, R_4$; AND R_5 WITH THE NEGATIVE CONSTANTS, a, b , AND c . [NOTE: IF $V_2(t) = \frac{d^2 V_1(t)}{dt^2}$, THEN $R_1, C_1, R_2, C_2 = \text{CONSTANT}$. FINDING THIS CONSTANT WILL BE THE SOLUTION TO HALF THIS PROBLEM. CONSTANT IS INDEPENDENT OF a, b , AND c]

(3) OP AMPS AND ANALOG COMPUTERS CAN BE USED TO SOLVE DIFFERENTIAL EQUATIONS. CONSIDER:

$$\frac{d^2 v_1(t)}{dt^2} = -a_2 \frac{dv_1(t)}{dt} + a_1 v_1(t) - b u(t)$$

WE WISH TO FIND $v_1(t)$ FOR A GIVEN INPUT (OR "FORCING FUNCTION") $u(t)$. LET


$$v_2(t) = dv_1(t)/dt \quad \text{(a) SHOW THAT}$$

WE CAN COMBINE THESE ABOVE TWO RELATIONS INTO "STATE EQUATIONS":

$$\dot{v}_1 = a_1 v_1 - a_2 v_2 - b u$$

$$\dot{v}_2 = v_2 \quad \left[\dot{v} = dv/dt \right]$$

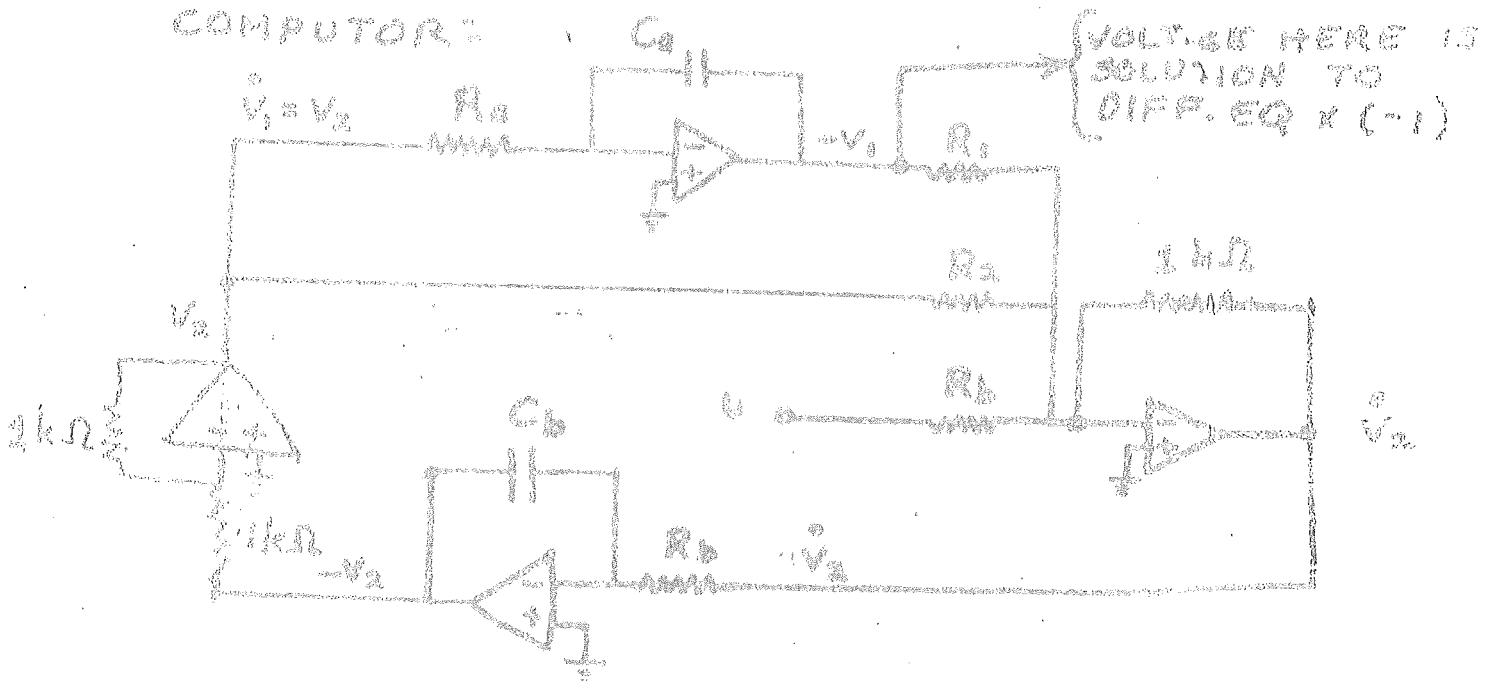(b) ASSUMING ZERO INITIAL CONDITIONS, AND THE RELATIONSHIPS BETWEEN THE CONSTANTS $a_1, a_2,$ AND b AND THE R'S AND C'S IN THE FOLLOWING COMPUTER:



ASSUME THAT CONSTANTS $a_1, b,$ AND a_2 ARE POSITIVE (HINT: AS AN EXAMPLE, $R_0 C_0 = 1$ AND $R_1 = (1/a_1) k\Omega$ USE VOLTAGES SHOWN ON CIRCUIT).

INTEGRATING CIRCUIT




$V_0 = -R_1 C \frac{dV_1}{dt}$

where impedance of C is $\frac{1}{sC}$

(1) $A_{dB} = 20 \log |A_v| = 20$, since $20 \log_{10} 10 = 20$
 $A_v = R_1 / R_2 = 10 \Rightarrow R_2 = 10^3 \Omega = 1 \text{ k}\Omega$

(2) $A_{dB} = 40 \text{ dB} \Rightarrow |A_v| = 100$ since $20 \log_{10} 10^2 = 40$
 $|A_v| = R_1 / R_2 = 100 \Rightarrow R_2 = 10^4 = 10 \text{ k}\Omega$

(3) LET $|A_v|$ CORRESPOND TO $A_{dB} = 20 \log_{10} |A_v|$
 THUS $|A_v| = 10^{A_{dB}/20}$. LET $\hat{A}_{dB} = 2 A_{dB}$. THEN
 $\hat{A}_v = 10^{\hat{A}_{dB}/20} = 10^{2 A_{dB}/20} = (10^{A_{dB}/20})^2 = A_v^2$
 THUS, IF WE DOUBLE A_{dB} , WE SQUARE A_v .

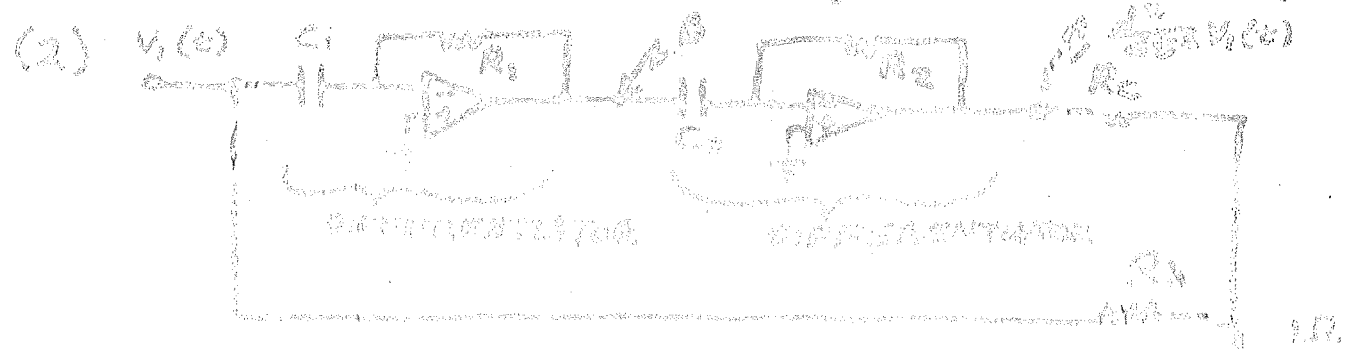

AT R_1 , WE HAVE

$V_1 = -R_f C_1 \frac{dV_1}{dt}$

AT R_2

$V_2 = (R_f C_2) \frac{dV_2}{dt} \Rightarrow V_2 = R_f C_2 \frac{dV_2}{dt}$


SINCE WE REQUIRE $V_0 = \frac{d^2 V_1}{dt^2} + \frac{d^2 V_2}{dt^2}$ SUMMER
 SUMMER OUTPUT IS

$\frac{d^2 V_0}{dt^2} = \frac{d^2 V_1}{dt^2} + \frac{d^2 V_2}{dt^2} + \frac{d^2 V_3}{dt^2}$

OR $V_0 = \frac{1}{R_3} \frac{d^2 V_1}{dt^2} + \frac{1}{R_2} V_2 + \frac{1}{R_1} V_3$

THUS, $c = -1/R_3$, $b = -1/R_2$, $a = -1/R_1$

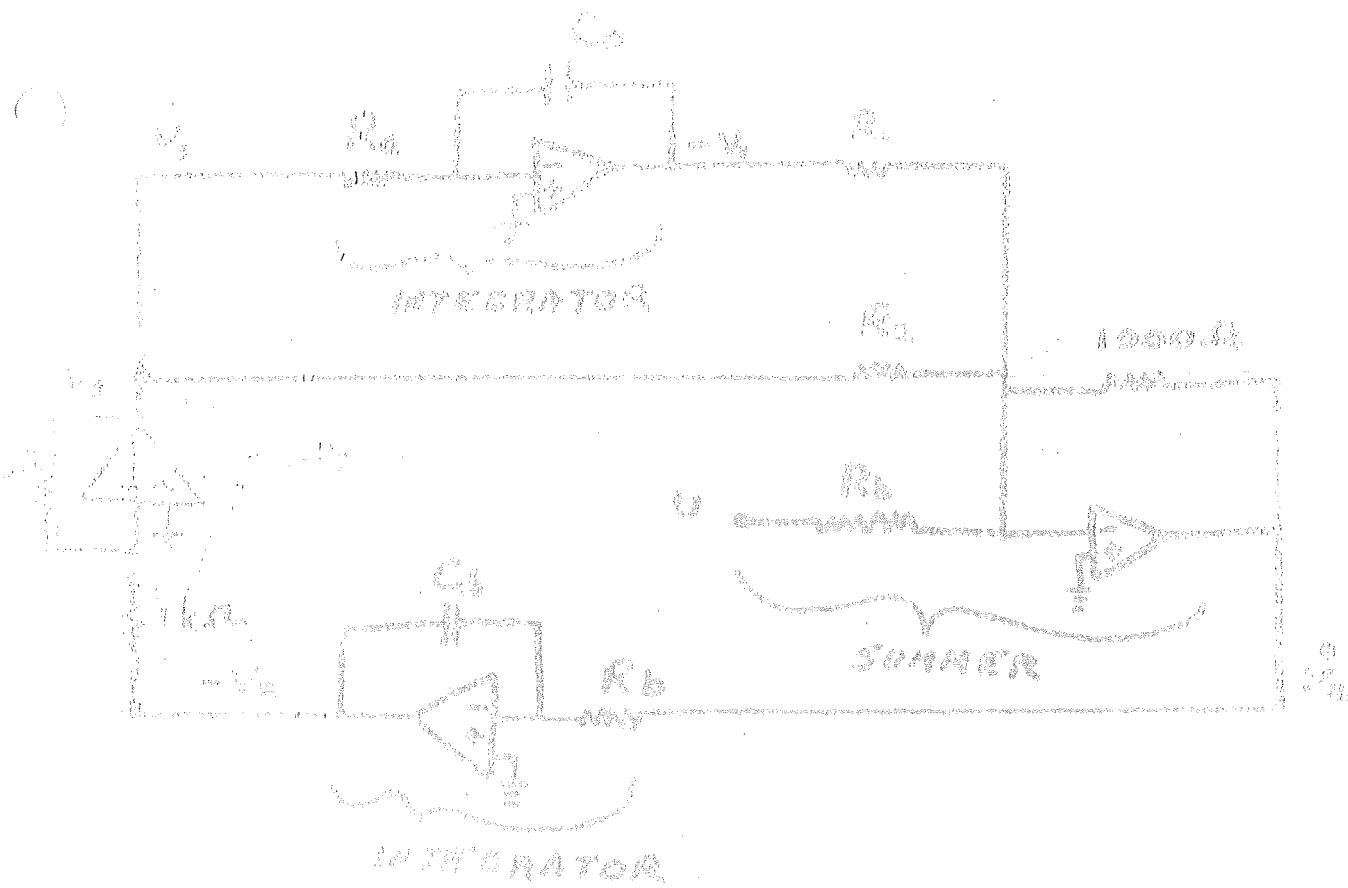OR $R_3 = -1/c$, $R_2 = -1/b$, $R_1 = -1/a$



IN THE 1ST INTEGRATOR, IN ORDER TO MAKE $-V_1$ AS THE OUTPUT WITH V_1 THE INPUT, WE NEED $R_1 C_1 = 1$. SIMILARLY, FOR THE BOTTOM INTEGRATOR, $R_4 C_2 = 1$. IN THE SUMMER, WE OBVIOUSLY WANT:

$$R_1 = (1/C_1)k\Omega, R_2 = (1/C_2)k\Omega; R_3 = (1/C_1)k\Omega$$

THROUGH ALL THINGS; HOLD FAST THAT WHICH IS GOOD

-THAT IS: 5:11-

BEING GREAT WAS EVER RECEIVED WITHOUT
"CONGRATULATION"


-EMOTION-

PLEASE PROVIDE:

"HOMEWORK IS GOOD FOR YOU"

-OLD 56-

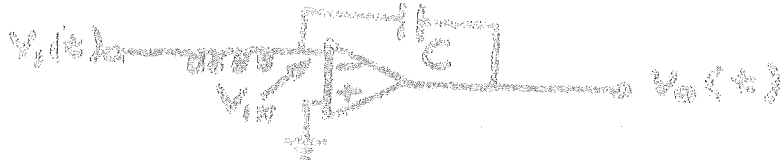(a) DETERMINE THE RELATIONSHIP BETWEEN $V_1(t)$ AND $V_2(t)$ IN THE FOLLOWING OP AMP CIRCUIT (ASSUME $V_{in} \approx \int \int V_1 dt dt \approx 0$). WHY MIGHT WE CALL THIS CIRCUIT A "DOUBLE INTEGRATOR"?




[HINT: YOU WILL NEED TO ASSUME THAT THE OP AMP INPUT CURRENT IS ≈ 0 .]

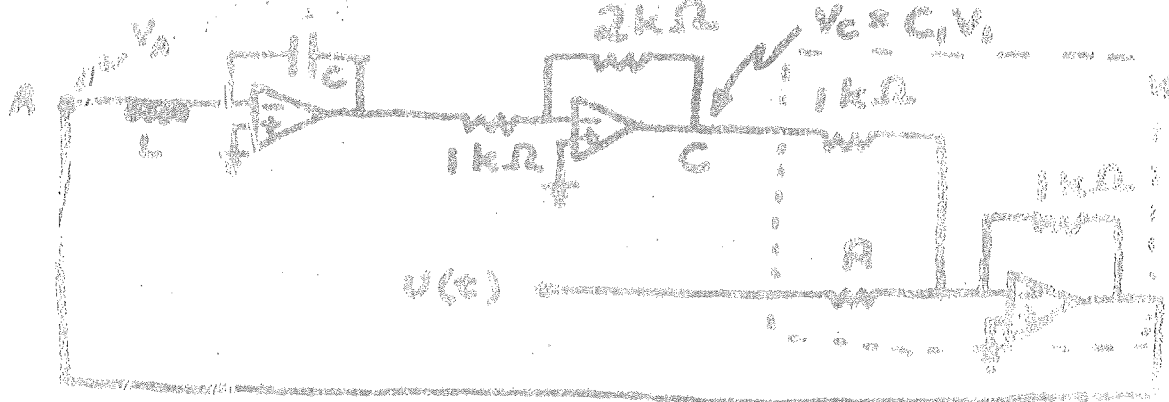(b) WE MAY USE THIS CIRCUIT TO SOLVE THE "DRIVEN WAVE EQUATION"

$$\frac{d^2 V}{dt^2} = -a V(t) - b U(t)$$

WHERE a & b ARE POSITIVE KNOWN CONSTANTS AND $U(t)$ IS THE "INPUT" OR "DRIVING TERM"




• GIVEN THAT THE VOLTAGE AT TERMINAL A $V_A = LC \frac{d^2 V}{dt^2}$, FIND THE NECESSARY INTERRELATIONS BETWEEN R, L, C IN TERMS OF a AND b


• THE VOLTAGE AT C IS PROPORTIONAL TO OUR SOLUTION. THAT IS, $V_C = C_1 V_1$. WHAT IS THE PROPORTIONALITY CONSTANT, C_1

2. WE SAY THAT AN IMPEDANCE, $Z = R + jX$, IS "INDUCTIVE" WHEN $X > 0$. FOR $X < 0$, Z IS "CAPACITIVE".

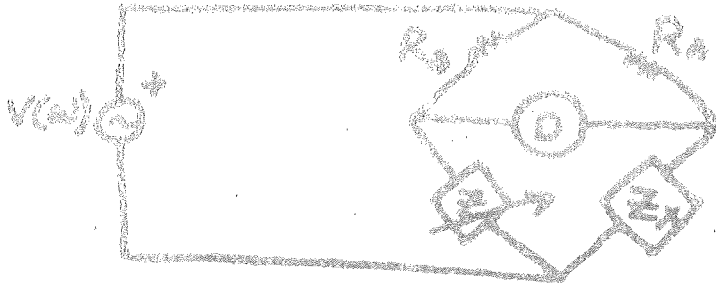(a) FOR THE FOLLOWING IMPEDANCE BRIDGE, SHOW THAT, IN ORDER TO ACHIEVE BALANCE, Z AND Z_x MUST BOTH EITHER BE INDUCTIVE OR BOTH CAPACITIVE



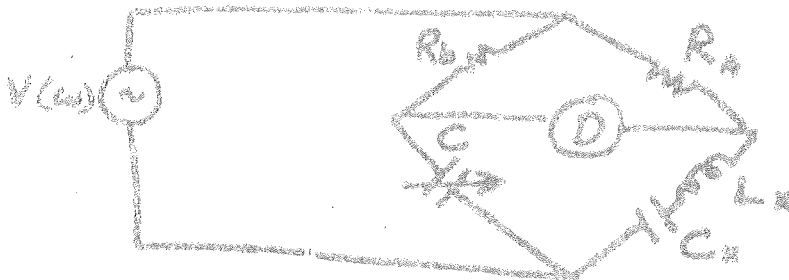(b) FOR WHAT FREQUENCY RANGE WILL THE FOLLOWING BRIDGE BALANCE? [RECALL THAT THE RESONANT FREQUENCY OF L_x AND C_x IS $\omega = \sqrt{1/L_x C_x}$] USE THE RESULTS OF (a)



(c) SHOW THAT, WHEN THE BRIDGE IS BALANCED, THAT L_x AND C_x ARE RELATED TO C BY

$$C = \frac{C_x R_b}{1 - \omega^2 L_x C_x R_a}$$

WHERE ω LIES IN THE RANGE DERIVED IN (b).

(d) EXPLAIN WHY THIS BRIDGE (PARTS b & c) IS A POOR SCHEME FOR MEASURING UNKNOWN L_x AND C_x . (AT LEAST TWO REASONS).

3. (a) FOR A SIGNAL, $\sin \omega_m t$, THE MODULATED SIGNAL:

$$V_3(t) = [1 + m \sin \omega_m t] \{V_c \sin \omega_c t\}$$

WHERE $V_c \sin \omega_c t$ IS OUR CARRIER AND m , OUR DEGREE OF MODULATION. IF $m > 1$, THE SIGNAL IS SAID TO BE OVER-MODULATED. SHOW, GRAPHICALLY, THAT OVERMODULATION "DISTORTS" OUR SIGNAL. [NOTE: ON THE MODULATED WAVEFORM, OUR SIGNAL IS THE ENVELOPE]

(b) A GOOD QUALITY ACOUSTIC REPRODUCTION SHOULD CONTAIN FREQUENCIES UP TO 20,000 HZ. HOW MANY SUCH SEPARATE REPRODUCTIONS CAN BE SENT OVER A CHANNEL WHOSE FREQUENCY CAPACITY RANGES FROM 0 TO 8 MEGA-HZ?

HOMEWORK #7 SOLUTIONS (BY MARK)



SUMMING CURRENTS AT V_{IN} :

$$\frac{1}{L} \int^t (V_1 - V_{IN}) dt + C \left[\frac{dV_0}{dt} - \frac{dV_{IN}}{dt} \right] = 0$$

(THE INPUT CURRENT TO OP AMP ≈ 0)

THUS:
$$\frac{d(V_0 - V_{IN})}{dt} = -\frac{1}{LC} \int^t (V_1 - V_{IN}) dt$$


$$\Rightarrow V_0 - V_{IN} = -\frac{1}{LC} \int^t \int^t (V_1 - V_{IN}) dt dt$$

OR, SINCE $V_{IN} \approx \int^t \int^t V_{IN} dt dt \approx 0$:

$$V_0(t) = -\frac{1}{LC} \int^t \int^t V_1(t) dt dt$$

WE PERFORM A DOUBLE INTEGRATION

ON THE INPUT, THUS "DOUBLE INTEGRATOR"

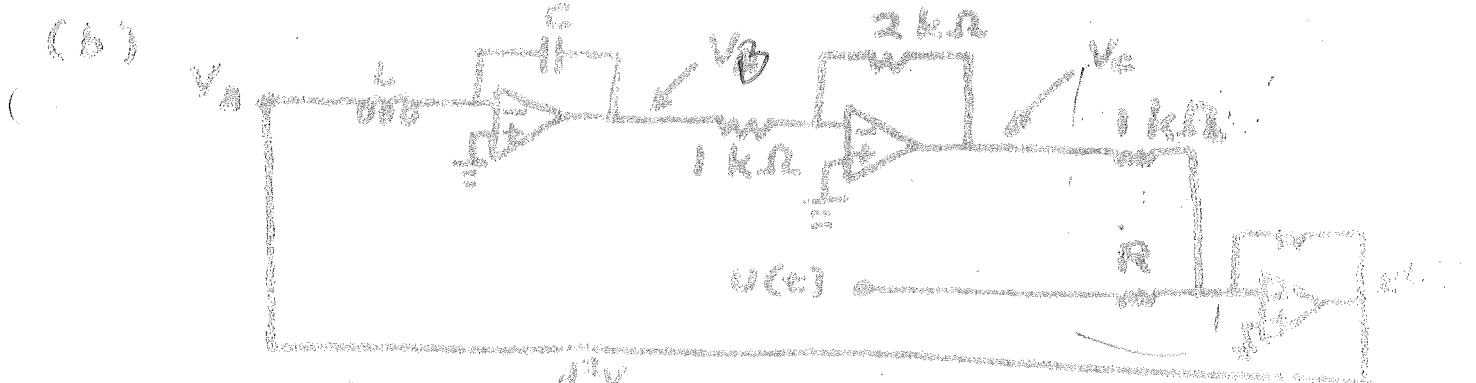

GIVEN $V_0 = LC \frac{d^2V}{dt^2}$, WE HAVE FROM (b) THAT $V_0 = -V_1$. THE AMP FOLLOWING HAS A GAIN OF -2 . THUS, $V_c = 2V_1$ (AND $C_1 = 2$). THE OUTPUT OF THE SUMMER IS:

$$\frac{V_0}{k\Omega} = \frac{-V_c}{1k\Omega} - \frac{U(t)}{R} \Rightarrow V_0 = -V_c - \frac{1k\Omega}{R} U(t)$$

BUT $V_0 = V_1 = LC \frac{d^2V}{dt^2} = -V_c - \frac{1k\Omega}{R} U(t)$

OR
$$\frac{d^2V}{dt^2} = -\frac{1}{LC} V_c - \frac{1k\Omega}{RLC} U(t)$$

IN ORDER FOR THIS TO BE OUR DIFF. EQ:

$$a = \frac{1}{LC}, \quad b = \frac{1k\Omega}{RLC} = \frac{2(1k\Omega)}{R}$$

2. (a) WHEN THE BRIDGE IS BALANCED:

$$Z_x = Z \frac{R_1/R_2}$$

LET $Z_x = R_x + jX_x$ AND $Z = R + jX$. EQUATING IMAGINARY PARTS:

$$X_x = \frac{R_1}{R_2} X$$

THUS, IF $X > 0$, THEN $X_x > 0$ (i.e., BOTH Z AND Z_x ARE INDUCTIVE). IF $X < 0$, THEN $X_x < 0$ (i.e., BOTH Z AND Z_x ARE CAPACITIVE).

(b) FOR THIS CIRCUIT:

$$X_x = \frac{-1}{\omega C} \quad X_x = (\omega L_x - \frac{1}{\omega C_x})$$

SINCE, FROM (a), X_x MUST BE NEGATIVE:

$$\omega L_x - \frac{1}{\omega C_x} < 0$$

$$\omega L < \frac{1}{\omega C_x} \Rightarrow \omega^2 < \frac{1}{LC_x}$$

$$\therefore \omega < \frac{1}{\sqrt{LC_x}} = \text{RESONANCE OF } L_x \text{ \& } C_x$$

(c) AT BALANCE:

$$Z_x = Z \frac{R_1/R_2}$$

$$j(\omega L_x - \frac{1}{\omega C_x}) = -j \frac{R_1}{R_2} \frac{1}{\omega C}$$

$$\frac{1}{\omega C_x} - \omega L_x = \frac{R_1}{R_2} \frac{1}{\omega C}$$


SOLVING FOR C:

$$C = \frac{C_x}{1 - \omega^2 L_x} \frac{R_1}{R_2}$$


(d)

THE VALUES OF L_x \& C_x ARE NOT UNIQUELY DETERMINED AND THE RESULT IS FREQUENCY DEPENDENT.

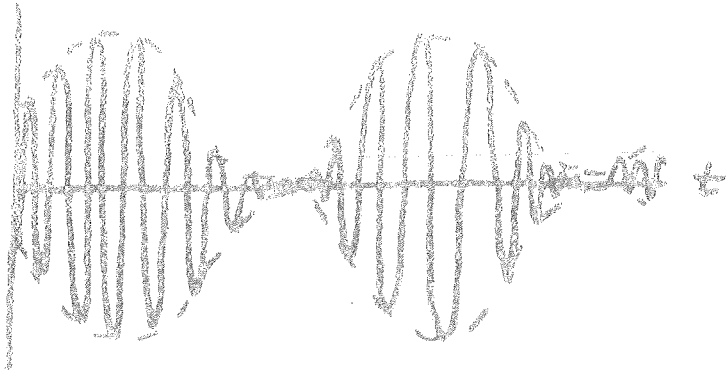3. (a) FOR $m \leq 1$, THE MODULATED SIGNAL LOOKS LIKE



FOR $m > 1$:

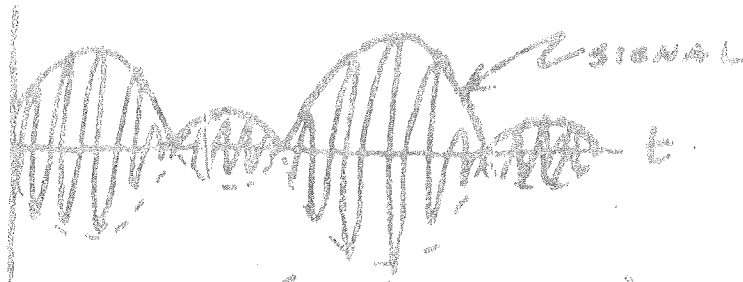

THE ENVELOPE (OUR SIGNAL) IS DISTORTED

$$(b) N = \frac{3 \times 10^6}{2(2 \times 10^4)} = 2 \times 10^2 = 200 \text{ REPRODUCTIONS}$$

1. CONSIDER THE FOLLOWING GROUPING OF NUMBERS.

0	1, 3, 5, 7, 9, 11, 13, 15
1	2, 3, 6, 7, 10, 11, 14, 15
2	4, 5, 6, 7, 12, 13, 14, 15
3	8, 9, 10, 11, 12, 13, 14, 15

IF ONE PICKS A NUMBER BETWEEN 1 AND 15, AND SPECIFIES WHICH OF THE ABOVE ROWS IT IS CONTAINED IN, THE UNKNOWN NUMBER CAN BE COMPUTED BY ADDING THE FIRST NUMBERS IN EACH ROW. FOR EXAMPLE, THE NUMBER 13 IS IN ROWS 0, 2 AND 3. THE FIRST NUMBERS OF THESE ROWS ARE 1, 4, AND 8 AND $1+4+8=13$.

- (a) EXPLAIN WHY THIS WORKS [HINT: USE BINARY NUMBERS IN YOUR REASONING]
- (b) MAKE A SIMILAR TABLE UP TO AND INCLUDING THE NUMBER 31 [HINT: IT WILL HAVE FIVE ROWS WITH 16 NUMBERS IN EACH ROW. HINT HINT: NOTICE THE PATTERN OF THE ROWS (LEFT TO RIGHT)]

2. A CODE WHICH CAN DETECT AND CORRECT A SINGLE BIT ERROR, CALLED THE "HAMMING" CODE, USES THE ABOVE IDEA. SUPPOSE WE WANTED TO SEND AN ELEVEN BIT CODE: 1110011110. WE BREAK IT UP INTO THE FOLLOWING:

	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1
BITS →	1	1	1	0	0	1	1	1	1	1	1	0	1	1	1

NOTE THAT, FOR THE 2⁰TH PLACE, WE HAVE PUT P₀ (EX: AT 2²=4, WE PUT P₂). THESE P'S ARE "PARITY" BITS. NOW WE GO TO COLUMN 0 IN PROBLEM 1. WE WANT THE BITS IN THIS ROW TO CONTAIN AN EVEN NUMBER OF 1'S. WE SEE THAT THERE ARE, IN FACT, AN ODD NUMBER (5) ONES IN BITS 15, 13, 11, 9, 7, 5 AND 3. TRUE, WE MUST CHOOSE P₀=1 SO THAT THE TOTAL NUMBER OF ONES IS EVEN. FOR ROW 1 IN PROBLEM 1, BITS 15, 14, 11, 10, 7, 6, AND 3 CONTAIN AN ODD NUMBER (5) OF 1'S SO WE MUST ALSO MAKE P₁=1.

- (a) SHOW THAT P₂=0 AND P₃=1 SO THAT OUR TOTAL CODE IS 111001111001110011.
- (b) PERFORM A HAMMING CODING ON THE ELEVEN BIT WORD 10101010101.

3. AT THE RECEIVING END OF A HAMMING CODE, WE CAN DETECT AND CORRECT A SINGLE BIT ERROR. SUPPOSE WE SENT THE WORD IN PROBLEM 2 AND RECEIVED

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1
1	1	1	0	0	1	1	1	1	0	1	0	0	1	1

(a) GOING THROUGH THE PROCEDURE IN PROBLEM 2, SHOW THAT THIS WORD SHOULD HAVE PARITY BITS $P_0=1, P_1=0, P_2=1, P_3=1$. NOW COMPARE THESE PARITY BITS WITH THOSE RECEIVED \rightarrow RECEIVED $\rightarrow P_3 P_2 P_1 P_0 = 1 0 1 1$ SHOULD BE $\rightarrow P_3 P_2 P_1 P_0 = 1 1 0 1$

BY "BITS DIFFERING" WE MEAN 0 WHEN P_n MATCHES AND 1 WHEN THEY'RE DIFFERENT. NOTE $(0110)_2 = 6$. THUS, OUR ERROR IS IN BIN 6. COMPARING THE ABOVE RECEIVED CODE TO OUR TRANSMITTED CODE IN PROBLEM 2, WE SEE THAT THIS IS TRUE. (NEAT, HUN?)

(b) IN YOUR HAMMING CODE DERIVED IN 2(b), MAKE AN ERROR IN BIN 13. BE A RECEIVER AND CORRECT YOUR MISTAKE AS WAS DONE IN PART a OF THIS PROBLEM.

4. (EXTRA CREDIT) NIM IS AN OLD CHINESE GAME WHERE THREE ROWS OF MATCHSTICKS ARE LAID OUT. ANY NUMBER OF MATCHSTICKS CAN BE IN ANY ROW, TWO PLAYERS ALTERNATELY TAKENS. DURING A TURN, A PLAYER CAN TAKE AS MANY MATCHSTICKS FROM ANY ONE ROW AS HE DESIRES. HE MUST TAKE AT LEAST ONE MATCHSTICK. THE PLAYER WHO PICKS UP THE LAST MATCHSTICK OR GROUP OF MATCHSTICKS WINS. BY USING BINARY NUMBERS, BELIEVE IT OR NOT, YOU CAN ALWAYS WIN. CONSIDER THE FOLLOWING "GAME BOARD" OF THREE ROWS OF MATCHSTICKS:

	\rightarrow	7 = (111) ₂
	\rightarrow	3 = (011) ₂
	\rightarrow	5 = (101) ₂
		<u>2 2 3</u> \leftarrow SUM (GAME'S)

NOTE THAT FOR EACH ROW, WE HAVE CONVERTED THE NUMBER OF MATCHSTICKS TO BASE 2 AND HAVE ADDED THEM (IN BASE 10) TO ARRIVE AT WHAT WE SHALL CALL THE GAME # (NUMBER). IF THE GAME NUMBER CONTAINS ONLY 0'S AND 2'S, IT IS "SAFE" OTHERWISE (IF IT CONTAINS ONE OR MORE 1'S OR 3'S), IT IS "UNSAFE" HERE IS THE BASIS FOR ALWAYS WINNING NIM: BY THE GAME RULES, IT IS ALWAYS POSSIBLE TO CHANGE AN UNSAFE NUMBER TO A SAFE NUMBER BUT IS IMPOSSIBLE TO CHANGE A SAFE NUMBER INTO ANOTHER SAFE NUMBER. (THIS IS A VERY NAIRY PROOF WHICH WE WILL NOT GO INTO). THUS, IN PLAYING, THE GAME NUMBER ALTERNATES BETWEEN SAFE AND UNSAFE UNTIL THE WINNING SAFE NUMBER OF 0 IS REACHED.

IN THE GAME BOARD AT THE BOTTOM OF THE PREVIOUS PAGE, THE GAME NUMBER CAN BE MADE SAFE BY TAKING ONE MATCHSTICK FROM THE THIRD ROW. THE NEW GAME NUMBER WILL BE 222.

(a) OBVIOUSLY, IF YOU PLAY NIM WITH ANOTHER PERSON WHO KNOWS HOW TO PLAY, YOU WON'T ALWAYS WIN. IN THIS CASE, HOW DOES THE INITIAL GAME BOARD AND WHO GOES FIRST DETERMINE WHO WINS?

(b) FOR THE FOLLOWING GAME BOARDS, DETERMINE IF THE GAME # IS SAFE OR UNSAFE. IF UNSAFE, TAKE A TURN & MAKE IT SAFE



(c) PLAY AND BEAT SOMEONE WHO DOESN'T KNOW HOW TO PLAY AT LEAST FIVE TIMES.

YOU CAN HOWEVER, MAKE AN UNSAFE # FROM ANOTHER UNSAFE #

(1)(a) CONSIDER THE NUMBER $13 = (0011)_2$. IT HAS 1'S IN THE $2^0, 2^1$, AND 2^3 PLACES, AND THUS IS IN THE $\textcircled{2}, \textcircled{1}$, AND $\textcircled{3}$ ROWS. IN SHORT, ROW $\textcircled{2}$ CONTAINS ALL THOSE BINARY NUMBERS THAT HAVE A 1 IN THE 2^0 PLACE.

- (b)
- $\textcircled{2}$ 1, 3, 5, 7, 9, 11, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31
 - $\textcircled{1}$ 2, 3, 6, 7, 10, 11, 14, 15, 18, 19, 22, 23, 26, 27, 30, 31
 - $\textcircled{3}$ 4, 5, 6, 7, 12, 13, 14, 15, 20, 21, 22, 23, 28, 29, 30, 31
 - $\textcircled{4}$ 8, 9, 10, 11, 12, 13, 14, 15, 24, 25, 26, 27, 28, 29, 30, 31
 - $\textcircled{5}$ 16, 17, 18, 19, 20, 21, 22, 23, 24, 25, 26, 27, 28, 29, 30, 31


(1)(a) ROW $\textcircled{2}$ IN PROBLEM (1a) HAS NUMBERS 1, 3, 5, 7, 9, 11, 13, 15. THE BITS IN THE RESPECTIVE BINS ARE $P_2, 1, 1, 1, 0, 1, 1, 1 = (6 \text{ ONE'S AND } P_2)$ THE NUMBER OF ONE'S IS EVEN, SO LET $P_2 = 0$. FOR $\textcircled{3}$, WE HAVE BINS 8 THRU 15 WHICH HAVE 5 ONE'S AND P_3 . TO MAKE THE NUMBER OF ONE'S EVEN, $P_3 = 1$.



- FOR $\textcircled{2}$: $P_2, 1, 0, 0, 1, 1, 1, 1 \Rightarrow P_2 = 1$ (6 ONE'S)
- $\textcircled{1}$: $P_1, 1, 1, 0, 0, 1, 0, 1 \Rightarrow P_1 = 0$ (4 ONE'S)
- $\textcircled{3}$: $P_3, 0, 1, 0, 0, 1, 0, 1 \Rightarrow P_3 = 1$ (4 ONE'S)
- $\textcircled{4}$: $P_4, 1, 0, 1, 0, 1, 0, 1 \Rightarrow P_4 = 0$ (4 ONE'S)

OUR CODE IS THEN
 1 0 1 0 1 0 1 0 1 1 0 1

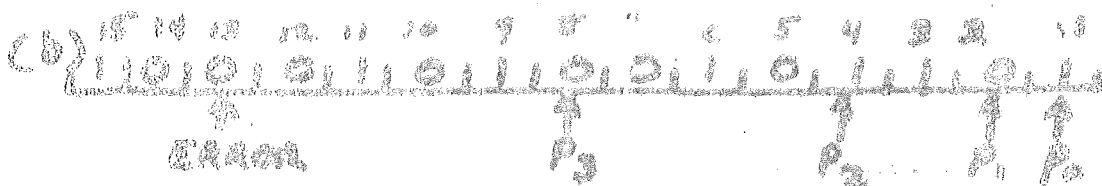- (3)(a) FOR
- $\textcircled{2}$: $P_2, 0, 1, 1, 1, 0, 1, 1 \Rightarrow P_2 = 1$
 - $\textcircled{1}$: $P_1, 0, 0, 1, 1, 0, 1, 1 \Rightarrow P_1 = 0$
 - $\textcircled{3}$: $P_3, 1, 0, 1, 0, 1, 1, 1 \Rightarrow P_3 = 1$
 - $\textcircled{4}$: $P_4, 1, 1, 0, 0, 1, 1, 1 \Rightarrow P_4 = 1$



PARITY BITS SHOULD BE

- ①: $P_0, 1, 0, 0, 1, 1, 0, 1 \Rightarrow P_0 = 0$
- ①: $P_1, 1, 1, 0, 0, 1, 0, 1 \Rightarrow P_1 = 0$
- ②: $P_2, 0, 1, 0, 0, 0, 0, 1 \Rightarrow P_2 = 0$
- ③: $P_3, 1, 0, 1, 0, 0, 0, 1 \Rightarrow P_3 = 1 \Rightarrow P_3 P_2 P_1 P_0 = 1000$

RECEIVED PARITY BITS ARE: $P_3 P_2 P_1 P_0 = 0101$
 BITS DIFFERING $\Rightarrow 1101$

THUS, WE HAVE AN ERROR IN BIN $(1101)_2 = 13$.

4.(a) A "WHO WINS TABLE" ^{INITIAL STATE} \rightarrow

YOU	OTHER
OTHER	YOU
YOU	OTHER

(b) (1) $5 \rightarrow 101$
 $5 \rightarrow 101$
 $2 \rightarrow 10$
 $\hline 212$

UNSAFE. MAY MAKE IS SAFE BY TAKING ALL THE MATCHSTICKS FROM THIRD COLUMN. NOTE: THERE IS USUALLY MORE THAN ONE WAY TO MAKE AN UNSAFE NUMBER SAFE.

(2) $3 \rightarrow 011$
 $6 \rightarrow 110$
 $1 \rightarrow 001$
 $\hline 172$

UNSAFE. MAY TAKE FOUR FROM SECOND ROW TO GIVE:
 $3 \rightarrow 011$
 $2 \rightarrow 010$
 $1 \rightarrow 001$
 $\hline 022 \leftarrow \text{SAFE}$

(3) $2 \rightarrow 010$
 $6 \rightarrow 110$
 $4 \rightarrow 100$
 $\hline 220 \leftarrow \text{SAFE}$

Pain of the Twenty-first Year

In my instruction;

I shall not pass.

He maketh vs to eat his wine ignorance before the whole class.

He telleth vs more than I can write,

He lowerth my grade.

Yes, tho I walk thru the corridors of knowledge,

I do not learn.

He tries to teach me;

He writeth equations before me in hopes that I will understand them.

He lay downeth my head with integritum.

My rule rule freezeth vs.

Only enthalpies and entropies shall follow me all the days of my life.

And I shall dwell in the College of Engineering Heaven.

-Anonymous

(COMP) HOMEWORK #9 (EE 234) BOB MARTS 9-26-97

- (1) CONSIDER A BINARY SYMMETRIC CHANNEL, OVER WHICH WE SEND AN ELEVEN BIT BINARY SIGNAL. ASSUME $p=q=0.9$ WHERE $p=P_0[0_r/0_r]$ AND $q=P_0[1_r/1_r]$. ASSUME $p_0=P_r[0_r]=1/2$ AND $p_1=P_r[1_r]=1/2$.
- (a) WHAT IS THE PROBABILITY NO ERROR IS MADE IN TRANSMITTING THIS SIGNAL OF ELEVEN BITS?
- (b) SUPPOSE WE CODED THE ELEVEN BIT SIGNAL WITH A HAMMING CODE. THIS REQUIRES AN ADDITIONAL FOUR (PARITY) BITS FOR A TOTAL OF FIFTEEN BITS. FIND THE PROBABILITY THAT WE WILL BE ABLE TO EXACTLY RECONSTRUCT THE SIGNAL SENT. SINCE THE HAMMING CODE CAN DETECT AND CORRECT A ONE BIT ERROR, THIS PROBABILITY WILL BE
 $P_r[\text{NO BIT ERRORS}] + P_r[2 \text{ BIT ERROR}]$
- (c) IN (a), WE TRANSMIT DIRECTLY. IN (b), WE USE A HAMMING CODE WHICH REQUIRES THE TRANSMISSION OF MORE BITS. IN TERMS OF CORRECTLY DETECTING WHAT WAS SENT, WHICH IS BETTER?

(2) USING TRUTH TABLES, VERIFY DEMORGAN'S THEM:


(a) $\overline{AB} = \overline{A} + \overline{B}$ HINT:

A	B	AB	\overline{AB}	\overline{A}	\overline{B}	$\overline{A} + \overline{B}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

(b) $\overline{A+B} = \overline{A} \overline{B}$

A	B	A+B	$\overline{A+B}$	\overline{A}	\overline{B}	$\overline{A} \overline{B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

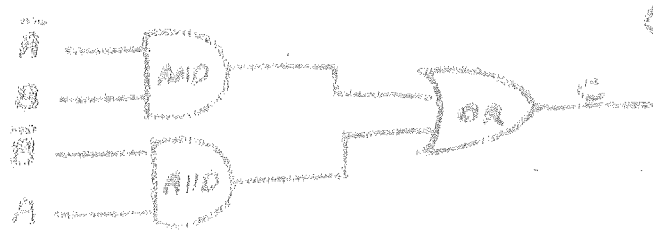(3) SHOW THAT THE FOLLOWING IS THE SAME AS AN EXCLUSIVE OR GATE. THAT IS, $C = A \oplus B$



(HINT: USE TRUTH TABLE)

(4) USING ONLY "AND" AND "OR" GATES (INCLUSIVE), DESIGN A CIRCUIT THAT FOLLOWS THE TRUTH TABLE =>

(CAN USE "NOT" GATES TOO)

A	B	C
0	0	0
0	1	1
1	0	0
1	1	0

[YOU MAY USE MULTI-TERMINAL GATES, LIKE

(5) SAME AS (4), BUT TRUTH TABLE IS

A	B	C	D
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	1	1

IF YOU WANT (THESE PROBLEMS ARE EASY)

EXTRA CREDIT: SPECIFY THE PERFORMANCE OF A "BUT" GATE, THAT IS, $C = A \text{ BUT } B$.

HOMEWORK 4

(1) (a) FOR $p=0.9$, THE PROBABILITY ALL BITS WILL BE CORRECTLY RECEIVED IS

$$(p)^n = (0.9)^{15} = 0.5133 \text{ OR } \sim 51.7\%$$

[THIS COMPUTATION REQUIRES $p_0 = p_1 = 1/2$]

(b) P_0 [NO ERRORS] = $(0.9)^{15} = 0.5170$
 P_0 [1 BIT ERROR] = P_0 [ONLY FIRST BIT IS WRONG] + P_0 [ONLY SECOND BIT IS WRONG] + ... + P_0 [ONLY 15TH BIT IS WRONG]

$$= (1-p) p \cdot p \dots p + p(1-p) p \dots p + \dots + p \cdot p \cdot p \dots (1-p)$$

$$= 15 \cdot [(1-p) p^{14}]$$

$$= 15 (0.1) (0.9)^{14} = 1.5 \cdot (0.9)^{14}$$

$$\Rightarrow P_0$$
 [CORRECT DETECTION] = $(0.9)^{15} + 1.5 \cdot (0.9)^{14}$

$$= [0.9 + 1.5] \cdot (0.9)^{14} = 0.5490 \sim 55\%$$

(c) HAMMING CODE IS BETTER. INCREASES OUR PROBABILITY OF CORRECT DETECTION BY OVER 20%.

(2) (a) $\overline{AB} = \overline{A} + \overline{B}$

A	B	AB	\overline{AB}	\overline{A}	\overline{B}	$\overline{A} + \overline{B}$	A	B
0	0	0	1	1	1	1	0	0
0	1	0	1	1	0	1	0	1
1	0	0	1	0	1	1	1	0
1	1	1	0	0	0	0	1	1


OBVIOUSLY, $\overline{AB} = \overline{A} + \overline{B}$

(b) $\overline{A+B} = \overline{A} \overline{B}$

A	B	A+B	$\overline{A+B}$	\overline{A}	\overline{B}	$\overline{A} \overline{B}$	A	B
0	0	0	1	1	1	1	0	0
0	1	1	0	1	0	0	0	1
1	0	1	0	0	1	0	1	0
1	1	1	0	0	0	0	1	1

$\therefore \overline{A+B} = \overline{A} \overline{B}$

(3) USING THE GATES SHOWN:

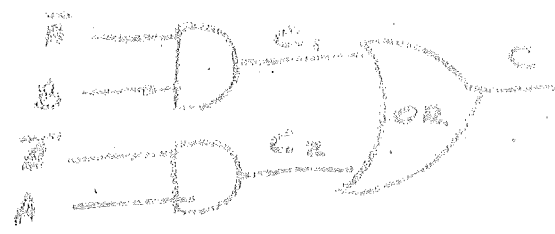

$$C = C_1 + C_2$$

$$= \overline{A} B + A \overline{B}$$

A	B	$\overline{A} B$	$A \overline{B}$	$C = \overline{A} B + A \overline{B}$
0	0	0	0	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	0

THE VALUES OF C ARE THE SAME AS FOR AN EXCLUSIVE OR GATE.


(4)

A	B	C
0	0	0
0	1	1
1	0	0
1	1	0


$$\Rightarrow C = \bar{A}B$$



OR

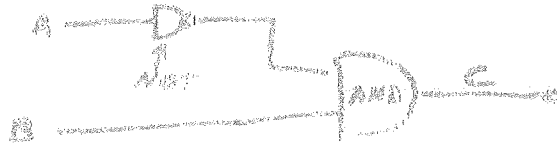

(5) $D = ABC + \bar{A}\bar{B}C$

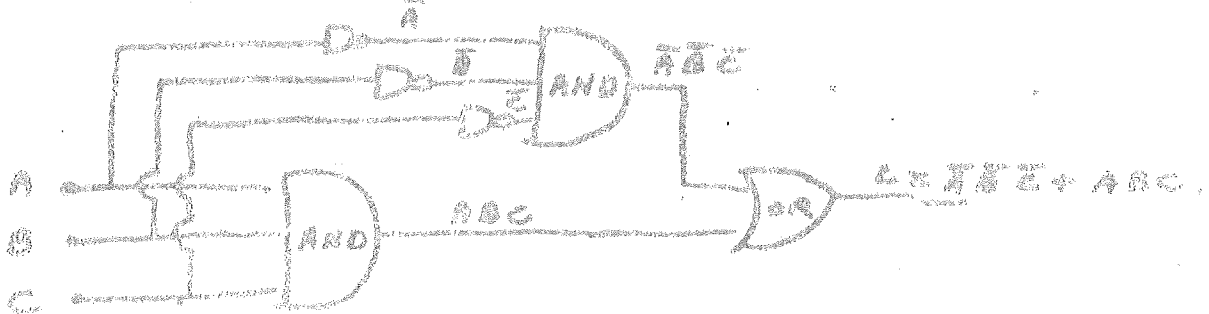

END OF 234 HOMEWORK!!

A FINAL NOTE OR TWO

• "TAKE WARNING! ALTERNATING CURRENTS ARE DANGEROUS! THEY ARE FIT ONLY FOR POWERING THE ELECTRIC CHAIR. THE ONLY SIMILARITY BETWEEN AN A-C AND A D-C LIGHTING SYSTEM IS THAT BOTH START FROM THE SAME COAL PILE"

THOMAS ALVA EDISON (1887 PAMPHLET)

• DID YOU KNOW A 100 WATT BULB GIVES OFF 50% MORE LIGHT THAN FOUR 25 WATT BULBS?

"BEAR YE ONE ANOTHER'S BURDEN'S, AND SO FULFILL THE LAW OF CHRIST"

GAL 6:2.

NAME

TEST 1

EE 234
BOB MARKS
2/17/77

INSTRUCTIONS:




- WORK ALL FIVE PROBLEMS. DO YOUR WORK ON THE BLANK PAGES PROVIDED IN THIS BOOKLET. BUDGET YOUR TIME CAREFULLY.
- THE POINT VALUE OF EACH PROBLEM IS GIVEN AT THE TOP RIGHT CORNER OF EACH PROBLEM STATEMENT. THERE ARE 100 POINTS TOTAL.
- THIS TEST IS OPEN BOOK, OPEN NOTES, CLOSED NEIGHBOR.

BEST OF LUCK



PROBLEM	SCORE	OUT OF
1		15
2		15
3		25
4		25
5		20
TOTAL		100

"THE THREE FOUNDATIONS OF LEARNING: SEEING MUCH, SUFFERING MUCH, AND STUDYING MUCH"
CATHEDRAL

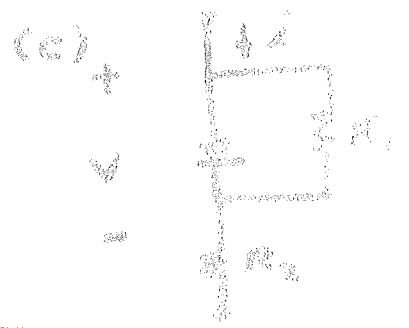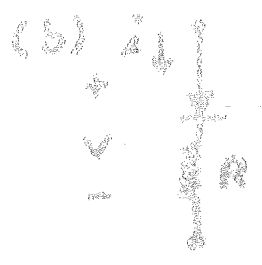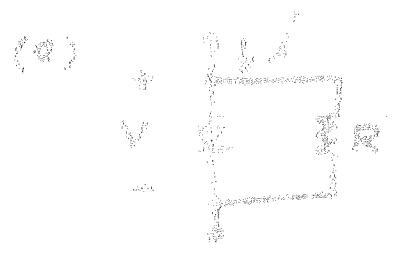
SKETCH THE $v-i$ CURVES FOR THE FOLLOWING RESISTOR-DIODE COMBINATIONS. ASSUME AN IDEAL DIODE. USE i AS VERTICAL AXIS.



HINTS:

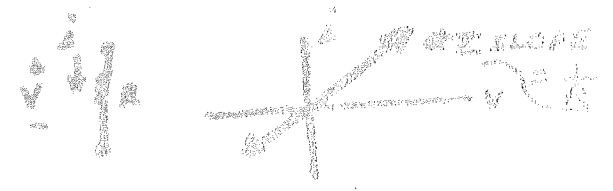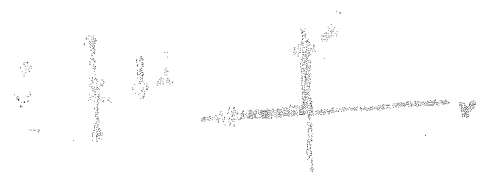

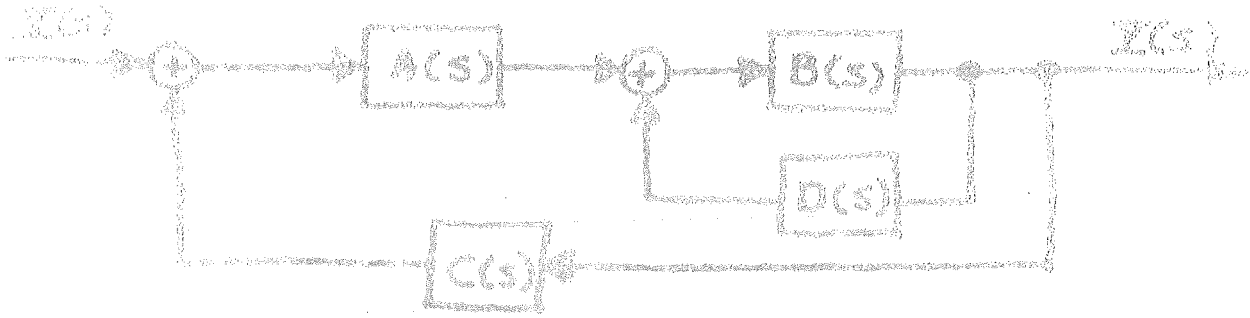
FOR THE FOLLOWING FEEDBACK SYSTEM,
FIND THE TRANSFER FUNCTION $T(s) = Y(s)/X(s)$



HINT: USE THE RESULT OF THE FEEDBACK PROBLEM
GIVEN AS HOMEWORK

FOR THE FOLLOWING CIRCUIT

(25 pts)

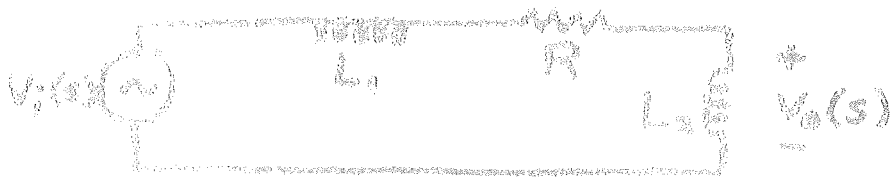


$\frac{V_o(s)}{V_i(s)}$

- (a) COMPUTE THE TRANSFER FUNCTION $T(s) = \frac{V_o(s)}{V_i(s)}$
- (b) COMPUTE $V_o(t)$ GIVEN THAT $V_i(t) = V_m \mu(t)$
 $[\mu(t) = \text{UNIT STEP FUNCTION}]$
- (c) SKETCH THE FREQUENCY RESPONSE $|T(j\omega)|$
 NOTING ITS VALUES AT $\omega = 0$ AND $\omega = \infty$
- (d) WHAT TYPE OF FILTER IS THIS?
 LO PASS, BANDPASS, OR HI PASS?

USE LAPLACE TRANSFORMS


$x(t)$	$X(s)$
1	$1/s$
e^{-at}	$1/(s+a)$
$\cos at$	$s/(s^2+a^2)$

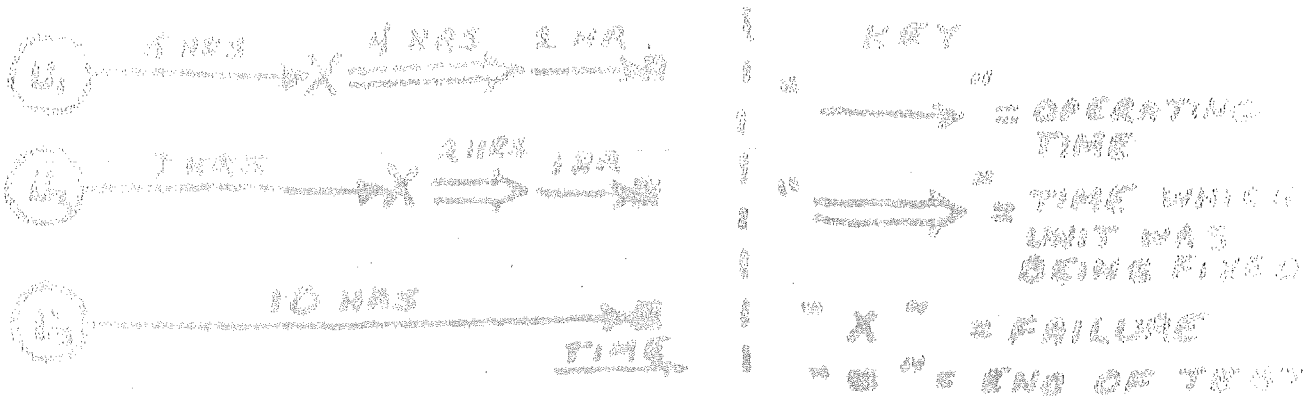(a) THREE IDENTICAL UNITS ARE PLACED ON TEST FOR 10 HOURS EACH. THE RESULTS ARE SHOWN BELOW.



COMPUTE THE UNITS' MTBF, MTTR, AND AVAILABILITY AS ESTIMATED BY THIS TEST.

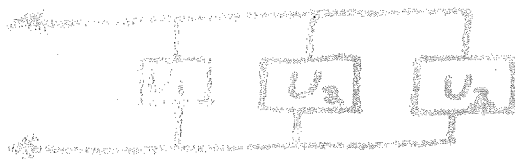(b) SUPPOSE THE UNITS TESTED IN (a) WERE CONNECTED IN THE SYSTEM SHOWN.



IF THE SYSTEM IS CONSIDERED "OPERABLE" WHEN AT LEAST TWO UNITS ARE WORKING, COMPUTE THE

ESTIMATES OF THE SYSTEM'S MTBF, MTTR, AND AVAILABILITY USING THE TEST DATA GIVEN IN PART (a).

(1) CONSIDER THE SIGNAL

$$y(t) = \int \sin 2\pi t + 2 \cos^2 \pi t$$

(a) what is the period, $2T$, of this periodic waveform? [hint: $\cos^2 \theta = \frac{1}{2} + \frac{1}{2} \cos 2\theta$]

(b) find the Fourier series:


$$y(t) = \sum_{n=-\infty}^{\infty} \alpha_n e^{jn\omega_0 t/T}$$

determining α_n . (if you are clever, no integration is required.)


$$\cos \theta = \frac{e^{j\theta} + e^{-j\theta}}{2}, \quad \sin \theta = \frac{1}{2j} [e^{j\theta} - e^{-j\theta}]$$

Equivalent circuit of a diode

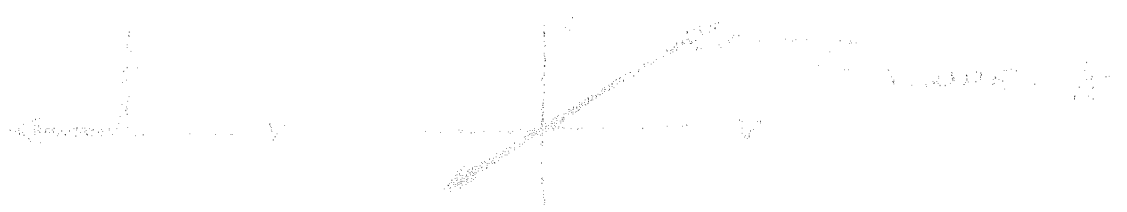
(1) When a diode is connected in series with a resistor, the combination acts like a resistor.



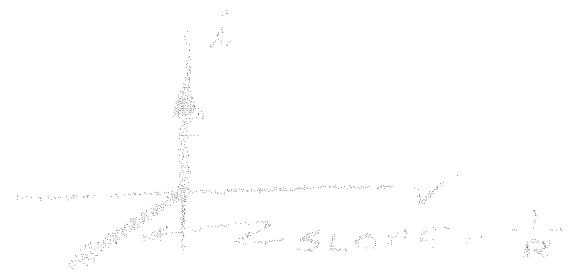
(2) When we try to make V positive, the diode is forward biased and thus a short. When the diode is reverse biased (an open circuit), the combination acts like a resistor.




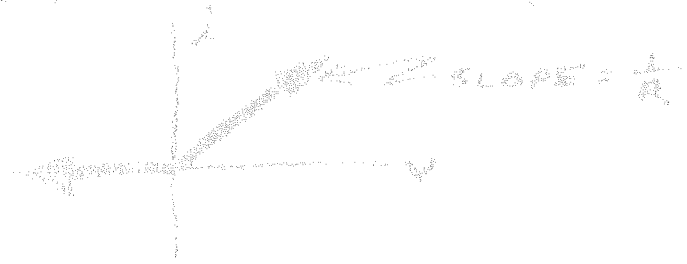
(3) When a diode is forward biased the combination acts like a resistor, a reverse bias gives an open circuit.



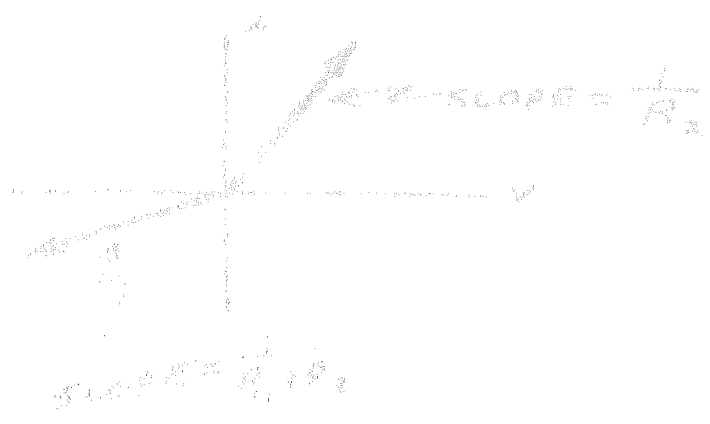
(4) When forward biased, this combination acts like R_1 , when reverse biased, like $R_1 + R_2$.



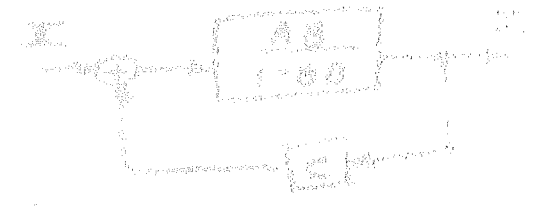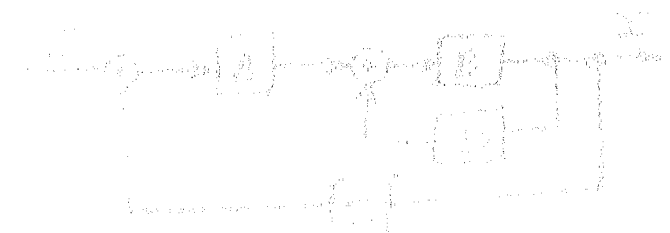REDUCTION OF THE NUMBER OF SUMMATION POINTS IN THE BLOCK DIAGRAM. SEE ABOVE.



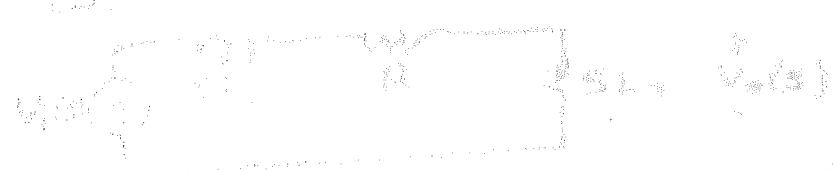(a)
$$T(s) = \frac{\frac{As}{1-s}}{1 - \frac{AsB}{1-s}} = \frac{As}{1-s-AsB}$$



(a) If voltage divider,
$$T(s) = \frac{V_o}{V_i} = \frac{sL_2}{s(L_1+L_2) + R}$$


(b)
$$V_i(s) = V_o(s) \Rightarrow V_i(s) = \frac{V_o}{s}$$

$$V_o(s) = T(s) V_i(s) = \left(\frac{sL_2}{s(L_1+L_2) + R} \right) \frac{V_o}{s}$$

$$V_o(s) = R^{-1} [V_o(s)] = \frac{V_o L_2}{L_1+L_2} e^{-(R/L_1+L_2)t}$$

(c)
$$|T(j\omega)| = \frac{L_2}{L_1+L_2} \frac{\omega}{\sqrt{\omega^2 + \left(\frac{R}{L_1+L_2}\right)^2}}$$
 , $T(0) = 0$

$$|T(\infty)| = \frac{L_2}{L_1+L_2}$$

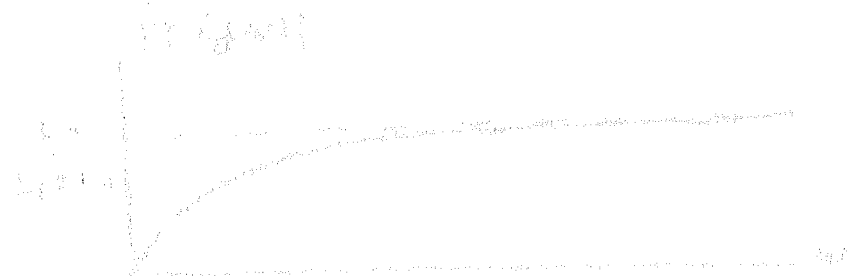

(d) THIS IS A LOW-PASS FILTER.

Time = 1 hour

Time = 1 hour

$$\frac{1}{10} = 0.10$$

According to our definition of "operating system" was operating only for 7 hrs. It took 2 additional hrs for repair and ran for 0.25 hr. Hour to the test's completion. There was only one system failure.

$$MTBF = \frac{8 \text{ hrs}}{1 \text{ failure}} = 8 \text{ hrs}$$

$$MTTR = \frac{2 \text{ hrs}}{1 \text{ failure}} = 2 \text{ hrs}$$

$$MTBF + MTTR = \frac{8}{10} = 0.80$$

$$A = 1 \text{ unit} + 2 \text{ unit} + 1 \text{ unit}$$

$$B = 1 \text{ unit} + 1 \text{ unit} + 1 \text{ unit}$$

$$C = \frac{1}{2} (e^{10000} + e^{10000}) + \frac{1}{2} e^{10000} + e^{10000}$$

$$D = e^{10000}$$


$$E = \sum_{i=1}^{\infty} a_i e^{i \lambda \text{ unit}/(\lambda \tau)}$$

$$\text{MTBF} = \frac{1}{\lambda}$$

$$a_1 = \frac{1}{2}, \quad \lambda = 0$$

$$a_2 = \frac{1}{2}, \quad \lambda = 1$$
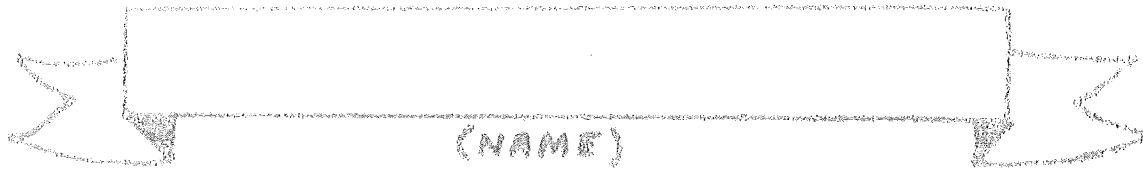
$$a_3 = 0, \quad \lambda = \text{for all other } a_i$$



(NAME)

TEST 2

EE 234
BOB MARKS
3/31/77

INSTRUCTIONS:

- WORK ALL 5 PROBLEMS. DO YOUR WORK ON THE BLANK PAGES PROVIDED IN THIS BOOKLET. BUDGET YOUR TIME CAREFULLY.
- EACH OF THE 5 PROBLEMS IS WORTH 20PTS FOR A TOTAL OF 100PTS.
- THIS TEST IS OPEN BOOK, OPEN NOTES, AND CLOSED NEIGHBOR.

- BEST OF LUCK -

PROBLEM	SCORE	OUT OF
1		20
2		20
3		20
4		20
5		20
TOTAL		100

"WHEN LIFE HANDS
YOU A LEMON...
MAKE LEMONADE"
DALE CARNEGIE


(1)

TRUE-FALSE: MARK T OR F AFTER EACH OF THE FOLLOWING STATEMENTS. MARKS SUCH AS "F" WILL NOT BE GRADED. DO NOT GUESS. THERE WILL BE A PENALTY FOR WRONG ANSWERS

- 1. THE OUTPUT IMPEDANCE OF AN IDEAL OP AMP IS THE SAME AS THAT OF A SHORT CIRCUIT WHICH HAS AN IMPEDANCE OF ZERO.....
- 2. THE EQUIVALENT CIRCUIT FOR A BJT WHICH CONTAINS IDEAL CURRENT SOURCES, IS A GOOD MODEL FOR THE ENTIRE OPERATING RANGE OF THE TRANSISTOR.....
- 3. THE THREE TERMINALS OF A MOSFET ARE THE COLLECTOR, BASE, AND EMITTER.....
- 4. ANALOG COMPUTERS ARE LESS EXACT IN GENERAL THAN DIGITAL COMPUTERS.....
- 5. AN AMPLITUDE MODULATED SINUSOID CONTAINS ONLY TWO FREQUENCIES.....
- 6. WE MAY SEND, AT MOST, 10 VOICES OF MAXIMUM FREQUENCY 3000 Hz OVER A 60,000 Hz CAPACITY CHANNEL.....
- 7. SELF BIASING CIRCUITRY REDUCES THE EFFECTS OF TEMPERATURE CHANGE ON BJT TRANSISTOR'S PARAMETERS.....
- 8. THE UNKNOWN RESISTANCE ON A BALANCED WHEATSTONE BRIDGE IS A FUNCTION OF THE APPLIED VOLTAGE.....
- 9. SHORTCIRCUITING THE VOLTAGE SUPPLY TO A BALANCED WHEATSTONE BRIDGE WILL HAVE NO EFFECT ON THE VOLTAGES AND CURRENTS WITHIN THE CIRCUIT.....
- 10. IF WE EXCEED 100% MODULATION IN AM, WE DISTORT OUR SIGNAL.....
- 11. EE IS GOOD FOR YOU.....





Q) 20%

WE WISH TO MODULATE THE SIGNAL:

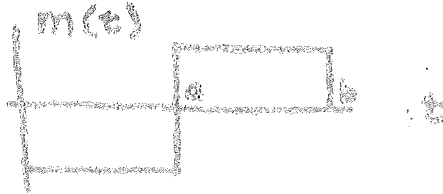


IN EACH OF THE FOLLOWING, STATE WHAT TYPE OF MODULATION IS USED

[CHOICES: AM, FM, PM, PAM, PDM, PPM]

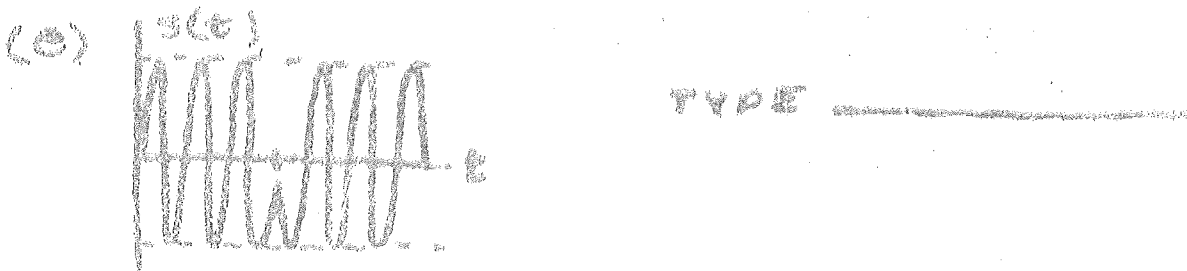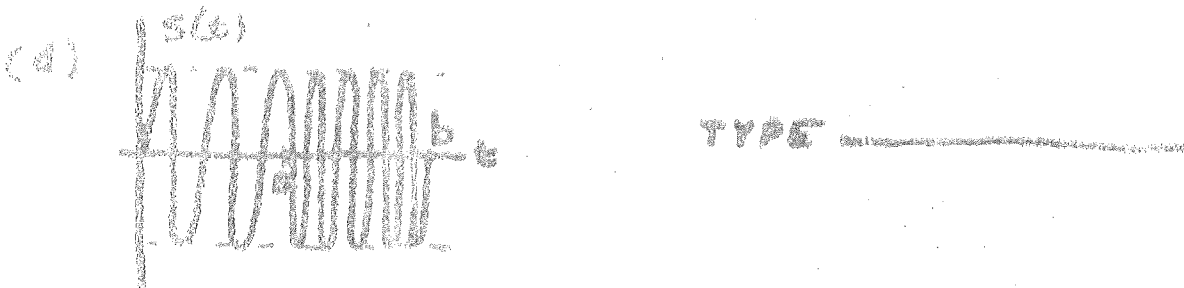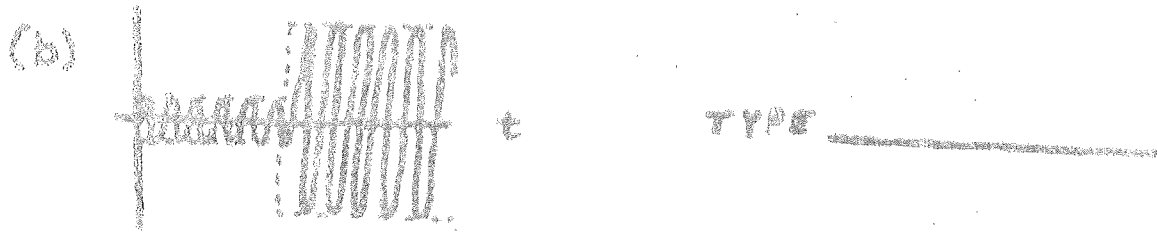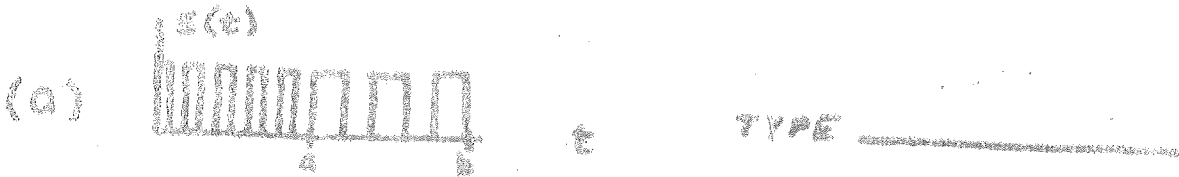


(3) 20%

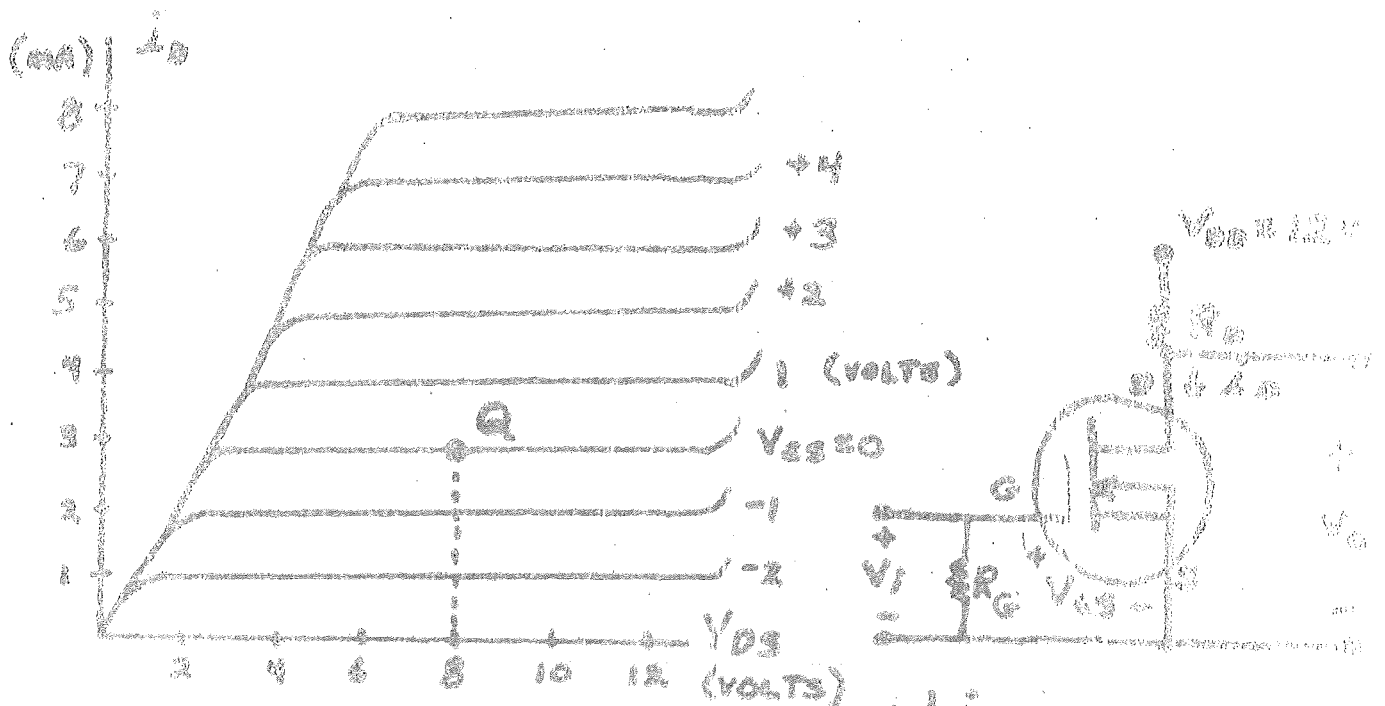

- (a) DETERMINE THE GAIN $G = \frac{d i_D}{d V_{GS}}$, IN AMPS, OF THIS DE MOSFET CIRCUIT. [USE ONLY TWO POINTS TO DETERMINE THE LINE ON THE i_D VS. V_{GS} CURVE, CONFINE ANALYSIS TO THE LINEAR PORTION OF THE TRANSISTOR CHARACTERISTICS.]
- (b) SKETCH THE LOAD LINE ON THE ABOVE i_D VS V_{DS} CURVE USING THE QUIESCENT POINT SHOWN.

(4) 20%

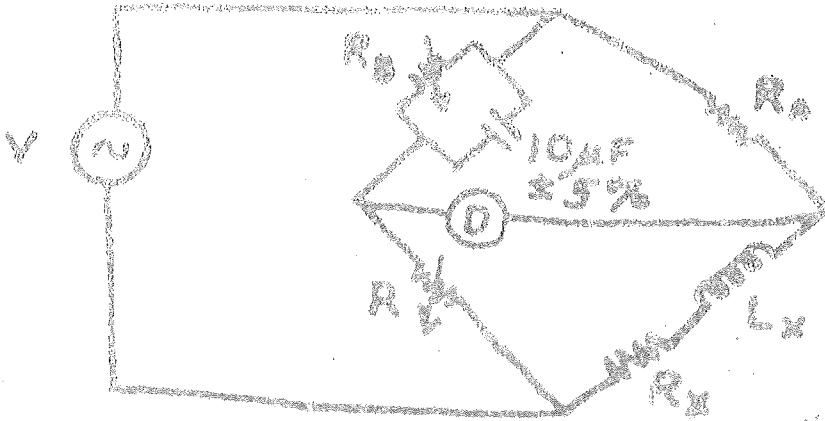


THIS "MAXWELL"
BRIDGE BALANCES
WHEN $R_B = 100 \Omega$
 $\pm 2\%$ AND
 $R = 10000 \Omega \pm 2\%$

IF WE KNOW THAT
 R_A LIES SOMEWHERE
BETWEEN 99Ω AND
 101Ω , FIND L_X

AND R_X AND THEIR
CORRESPONDING TOLERANCES IN $\pm (\quad)\%$
USE THE USUAL APPROXIMATIONS.

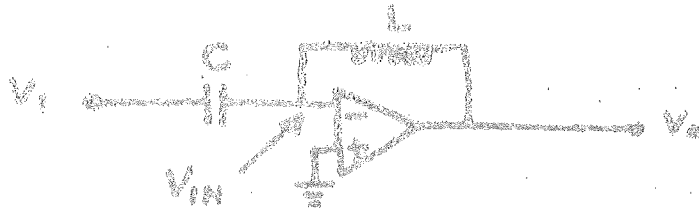(5) 20/2

DETERMINE $V_o(t)$ AS A FUNCTION OF $V_i(t)$ IN THE FOLLOWING OP-AMP CIRCUIT:




ASSUME THE OP AMP HAS INFINITE INPUT IMPEDANCE (i.e., ZERO INPUT CURRENT) AND THAT

$$\frac{d^2 V_{IN}}{dt^2} \approx V_{IN} \approx 0$$

(1) 1F, 2F, 3F, 4T, 5F, 6T, 7T, 8F, 9F, 10T, 11T


(a) (a) PAM, (b) AM, (c) PAM, (d) PM, (e) PM

(3)

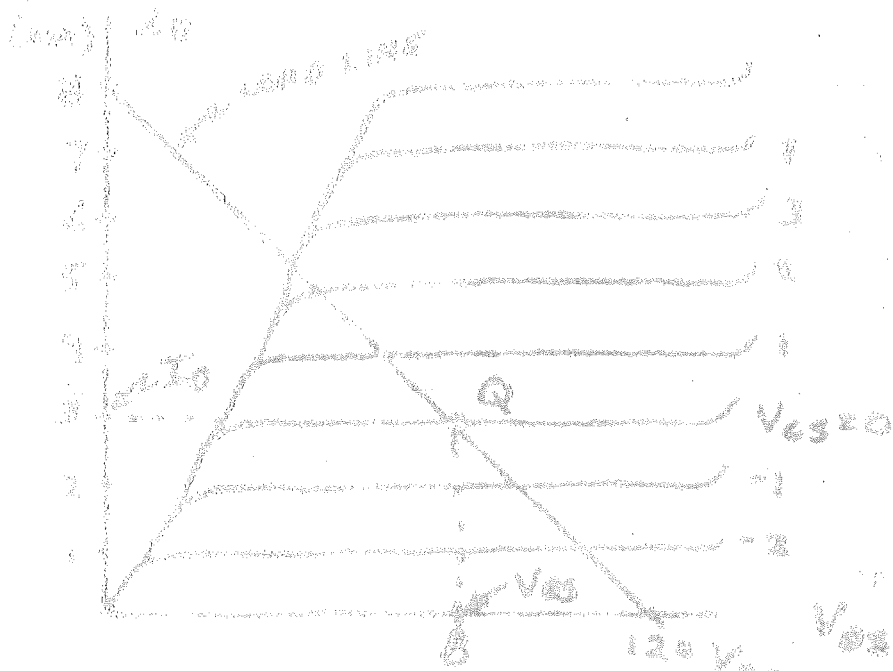

(a) $V_{DS} = 12V$ AND Q DETERMINE LOAD LINE.

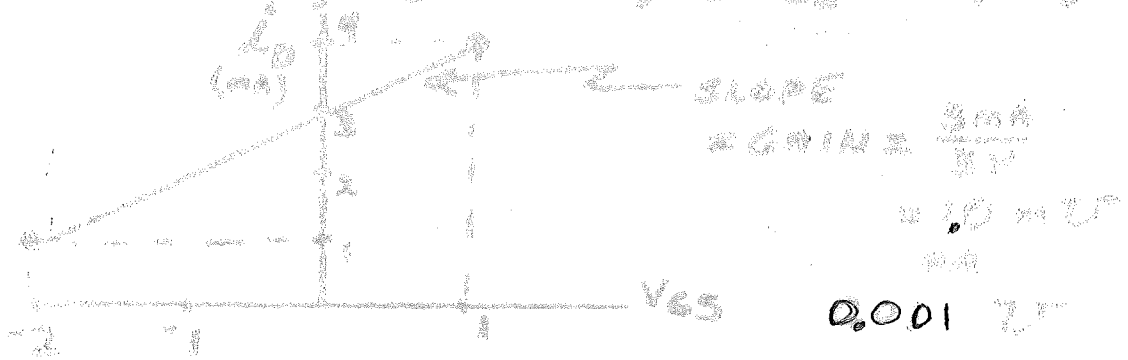(b) @ $V_{GS} = 1$, $I_D = 4mA$; @ $V_{GS} = 2$, $I_D = 8mA$



(1) $R_A = 29 \Omega \ll R_D = 10^4 \Omega \Rightarrow R_A = 100 \Omega \ll R_D = 10^4 \Omega$

WE SHOWED IN HOMEWORK #5, PROBLEM 3, THAT

$$R_2 = R_D R_A / R_D \quad \text{AND} \quad L_2 = C_D R_D R_A$$

THUS

$$R_2 = \frac{(10^3)(10^3)}{(10^2)} = \frac{(1 \pm 0.02)(0.5 \pm 0.02)}{(1 \pm 0.01)}$$


$$= 1000 \Omega \quad [(1 \pm 0.02)(1 \pm 0.02)(1 \pm 0.01)]$$

$$= 1000 \Omega \quad (1 \pm 0.05) = 1000 \Omega \pm 5\%$$

$$L_2 = (10^{-3})(10^3)(10^2) [(1 \pm 0.05)(1 \pm 0.02)(1 \pm 0.01)]$$

$$= 1 \text{ H} \pm 8\%$$

(2)

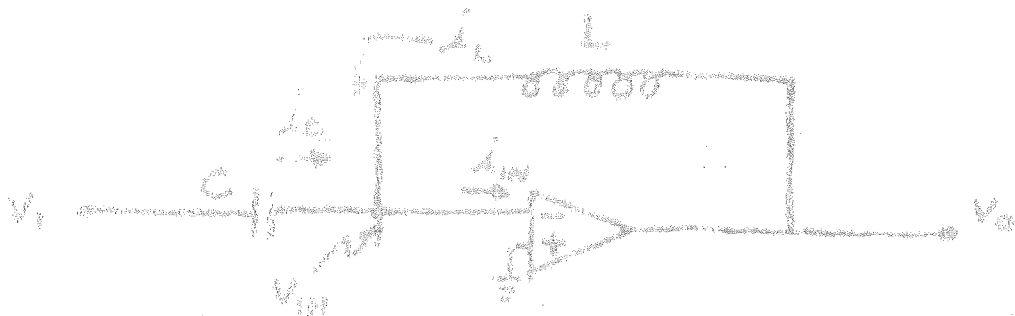

SUMMING CURRENTS AT v_{IN} WITH $i_{IN} = 0$:

$$i_C - i_L = 0 = C \frac{d(v_I - v_{IN})}{dt} + \frac{1}{L} \int (v_O - v_{IN}) dt$$

OR


$$\int (v_O - v_{IN}) dt = -LC \frac{d(v_I - v_{IN})}{dt}$$

DIFFERENTIATING:

$$v_O - v_{IN} = -LC \left[\frac{d^2 v_I}{dt^2} - \frac{d^2 v_{IN}}{dt^2} \right]$$

ASSUMING $v_{IN} \approx d^2 v_{IN}/dt^2 \approx 0$ GIVES
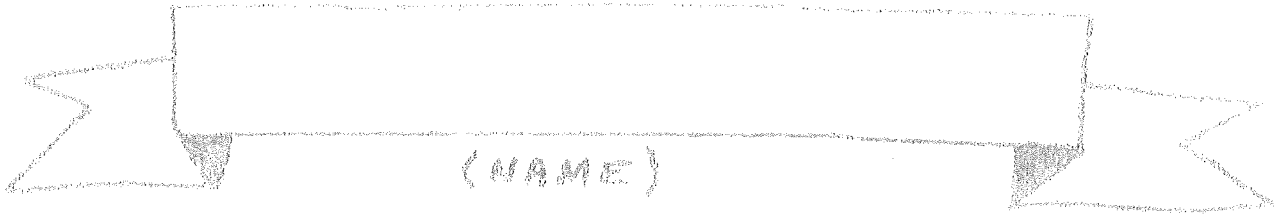
$$v_O = -LC \frac{d^2 v_I}{dt^2} \leftarrow \text{"DOUBLE DIFFERENTIATION"}$$



(NAME)

TEST 3

EE 234
Bob Mar...
4/26/77

INSTRUCTIONS

- WORK ALL 5 PROBLEMS. DO YOUR WORK ON THE PAGES IN THIS BOOKLET. BUDGET YOUR TIME CAREFULLY.
- EACH PROBLEM IS WORTH 20 PTS. (TOTAL = 100 POINTS)
- TEST IS OPEN BOOK, OPEN NOTE.

-BEST OF LUCK

PROB	TOTAL	OUT OF
1		20
2		20
3		20
4		20
5		20
		100
TOTAL		

"WISDOM IS THE
PRINCIPAL THING
THEREFORE, GET
WISDOM, AND WITH
ALL THY GETTING
GET UNDERSTANDING"

PROV. 4-7

(1) YOU RUN A FIELD WITH OIL WELLS A, B, AND C. EACH WELL IS FITTED WITH A SMOKE DETECTOR WHICH PUTS OUT A LOGIC "1" IF THE WELL IS ON FIRE. OTHERWISE, IT'S LOGIC ZERO.

(a) SUPPOSE YOU WANTED A SINGLE RED "IDIOT LIGHT" TO GO ON WHEN TWO OR MORE OF YOUR WELLS IS ON FIRE. ASSIGNING A "1" TO THIS LIGHT BEING ON, COMPUTE THE CORRESPONDING TRUTH TABLE.

(b) FROM YOUR TRUTH TABLE, DESIGN A LOGIC CIRCUIT TO LITE YOUR LITE USING THE SMOKE DETECTOR SIGNAL LEVELS AS INPUTS.

A	B	C	L
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

(2) (a) USING THE "AMERICAN STANDARD CODE FOR INFORMATION EXCHANGE" ON PAGES 5-8 TO 5-11 OF VINE'S BOOK, WRITE THE CODE FOR THE MESSAGE:


I LIKE LEE

AFTER EACH LETTER (OR SPACE), PUT AN EVEN ONES PARITY BIT FOR THAT CODED LETTER (OR SPACE). USE THE SPACES BELOW FOR YOUR CODE:

Four horizontal lines with vertical tick marks, intended for writing the parity-coded message.

- (b) LET P_c BE THE PROBABILITY OF RECEIVING THE CODE EXACTLY AS IT WAS SENT AND P BE THE PROBABILITY A BIT IS SENT OVER THE CHANNEL WITH NO ERROR. WHAT IS P_c FOR $P=0.9$? FOR $P=0.99$? FOR $P=0.999$?
- (c) WHAT MUST P BE IF $P_c=0.95$? (CARRY P TO AT LEAST FIVE PLACES).

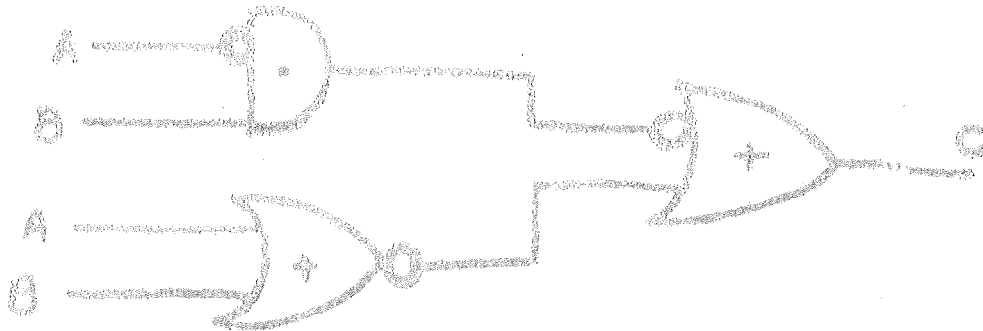(4) CONSIDER THE FOLLOWING LOGIC CIRCUIT:



(a) COMPUTE THE TRUTH TABLE FOR THE OUTPUT, C, GIVEN THE INPUT A, B

(b) WRITE THE BOOLEAN FUNCTION FOR C IN TERMS OF A AND B.


A	B	C
0	0	—
0	1	—
1	0	—
1	1	—

(5) WE WISH TO SEND AN ARBITRARY ELEVEN BIT WORD OVER A BINARY SYMMETRIC CHANNEL (BSC) WITH $p_0 = p_1 = \frac{1}{2}$. WE WISH TO HAVE A PROBABILITY OF CORRECT DETECTION OF 90%. COMPUTE THE REQUIRED VALUE OF CORRECTLY SENDING AN INDIVIDUAL BIT, p , FOR THE FOLLOWING TWO CASES.

(a) WE SEND THE ELEVEN BIT MESSAGE DIRECTLY WITH NO CODING.

(b) WE SEND THE ELEVEN BIT MESSAGE IN A SINGLE BIT ERROR CORRECTION HAMMING-CODE. (FOUR PARITY BITS FOR A TOTAL OF FIFTEEN BITS). YOU MAY FIND THE FOLLOWING GRAPH HELPFUL. SHOW YOUR WORK.

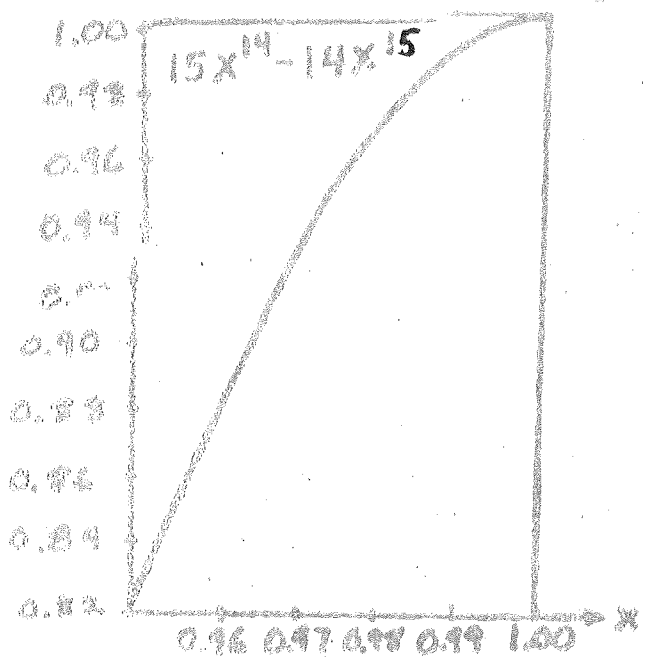(c) WHICH OF THE TWO SCHEMES REQUIRES THE LESS NOISY CHANNEL?



TEST # 3

(SOLUTIONS)

by MARKS

(1)(a) ANY TIME THERE ARE TWO OR MORE "1"'S, IN A, B, & C, WE WANT OUR LIGHT TO GO ON:


A	B	C	L
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

← TRUTH TABLE


(b) FROM OUR TRUTH TABLE:

$$L = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$$

THUS, A SCHEME WOULD BE:

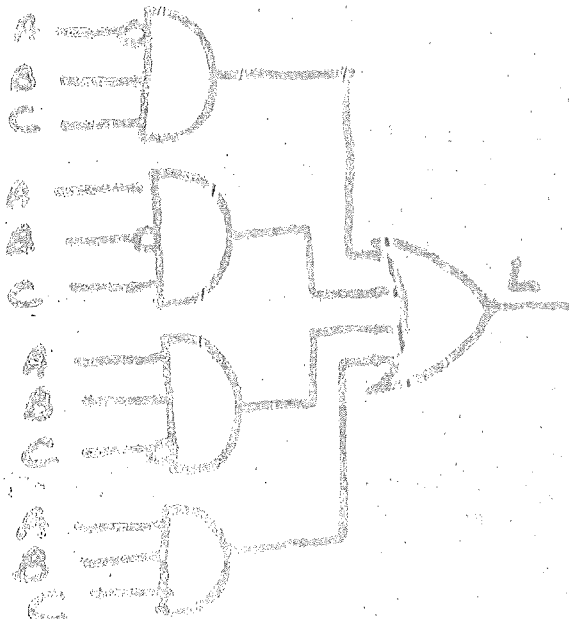

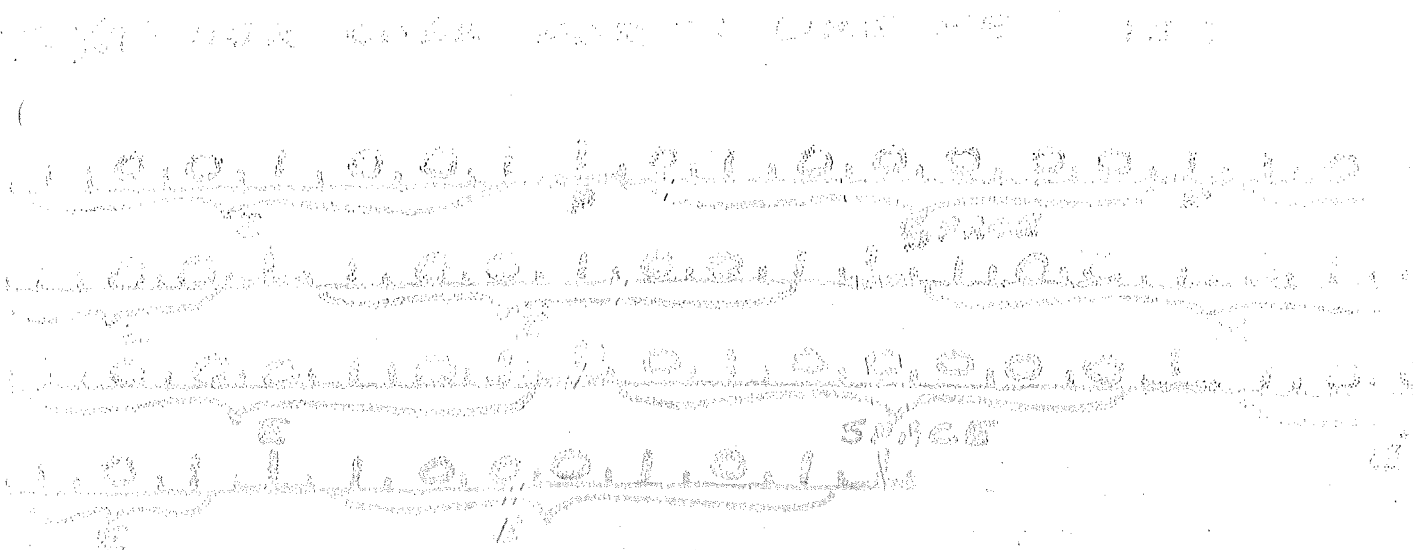NOTE: IN NO WAY IS THIS THE OPTIMAL IMPLEMENTATION SCHEME. CAN YOU REDUCE THE NUMBER OF REQUIRED GATES?



(1) THERE ARE 72 SLICES IN THE ABOVE CASE
 THUS $P_c = P^{72}$

$$P = 0.9 \Rightarrow P_c = (0.9)^{72} = 0.00024 = 2.4 \times 10^{-4}$$

$$P = 0.99 \Rightarrow P_c = (0.99)^{72} = 0.48$$

$$P = 0.999 \Rightarrow P_c = (0.999)^{72} = 0.93$$

$$(a) P_c = P^{72} \Rightarrow P = P_c^{1/72} = (0.95)^{1/72} = 0.99989$$


(3)(a)

A	B	C	D	L	A	B	C	D
0	0	0	0	0	1	0	0	0
0	0	0	1	1	1	0	0	1
0	0	1	0	1	1	0	1	0
0	0	1	1	0	1	0	1	1
0	1	0	0	1	1	1	0	0
0	1	0	1	0	1	1	0	1
0	1	1	0	0	1	1	1	0
0	1	1	1	1	1	1	1	1

(b) FROM TRUTH TABLE:

$$L = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D + \bar{A}B\bar{C}D$$

(4)

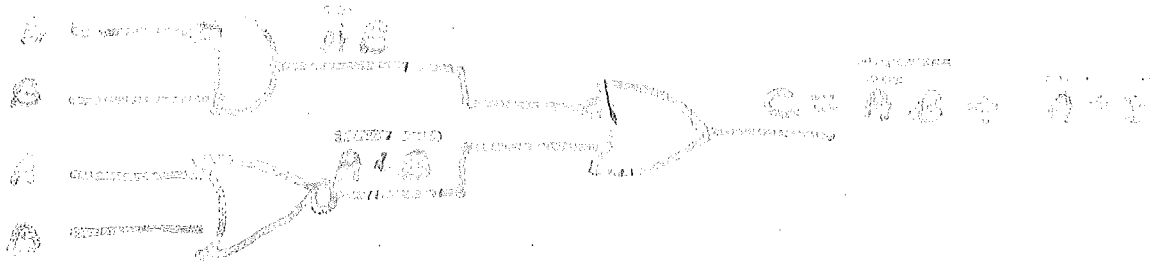

(a) $A=0, B=0 \Rightarrow \bar{A}B = 1 \cdot 0 = 0$

$A+B = 0+0 = 0$

$C = 1+0 = 1$

$A=0, B=1 \Rightarrow \bar{A}B = 1 \cdot 1 = 1$

$A+B = 0+1 = 1 = 0$

$C = 0+0 = 0$

$A=1, B=0 \Rightarrow \bar{A}B = 0 \cdot 0 = 0$

$A+B = 1+0 = 1 = 0$

$C = 1+0 = 1$

$A=1, B=1 \Rightarrow \bar{A}B = 0 \cdot 1 = 0$

$A+B = 1+1 = 1 = 0$

$C = 1+0 = 1$

TRUTH TABLE IS

A	B	C
0	0	1
0	1	0
1	0	1
1	1	1

(b) FROM FIGURE, $C = \bar{A}B + A\bar{B}$

OR, FROM TRUTH TABLE

$C = \bar{A}B \Rightarrow C = \bar{A}B = A+B$

OR $C = \bar{A}\bar{B} + A\bar{B} + AB$

(ALL OF THESE ARE CORRECT ANSWERS)

(1) $E = p^2 + (1-p)^2 = 2p^2 - 2p + 1$


(2) $p = 0.9$ and $1-p = 0.1$

$E = 2p^2 - 2p + 1 = 2(0.9)^2 - 2(0.9) + 1$

$= 2(0.81) - 1.8 + 1$


$= 1.62 - 1.8 + 1 = 1.42$

GRAPHING THE GRAPH:

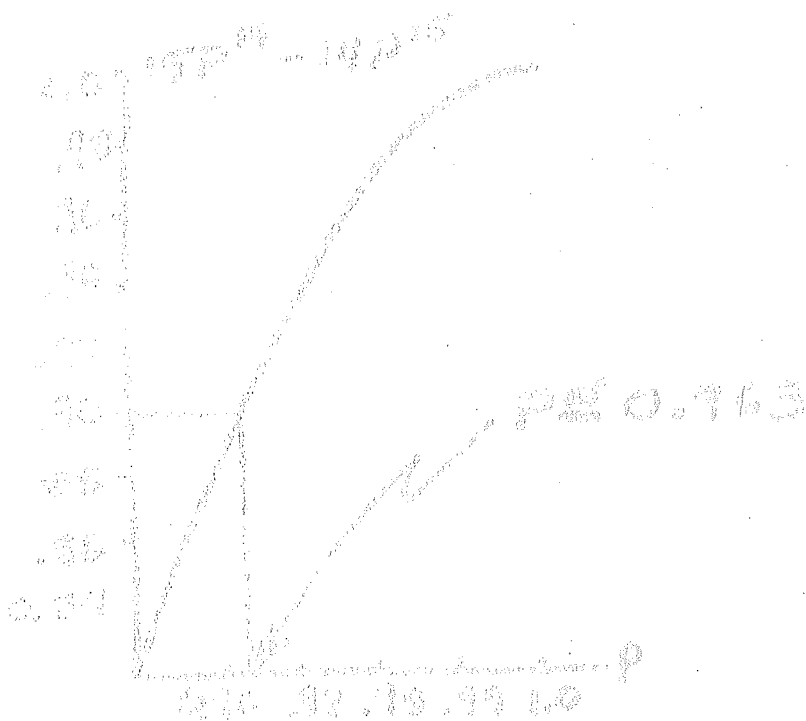

(3) THE ABOVE SCHEME DOES NOT

$0.963 < 0.970$

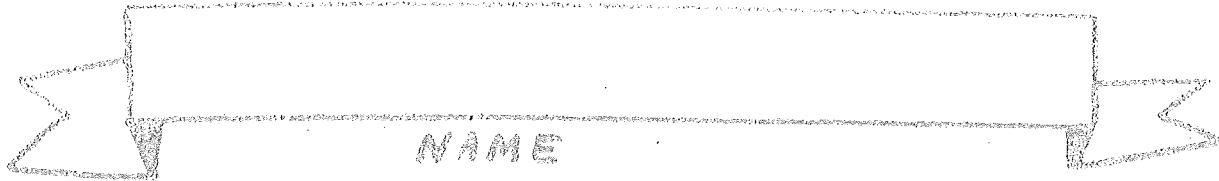

FINAL

EE 234
BOB MARKS
MAY 6, 1977

INSTRUCTIONS:

- THIS TEST IS DIVIDED INTO TWO SECTIONS:
- I. 100 TRUE-FALSE QUESTIONS (200 POINTS)
 - II. FOUR PROBLEMS (200 POINTS EACH)
- THE TOTAL # OF POINTS IS 400.

"ALL WISDOM OF THIS WORLD IS FOOLISHNESS WITH GOD"

1 COR 3:19

SOME RELATIONS:

$$e^{j\theta} = \cos \theta + j \sin \theta \leftarrow \text{EULER}$$

$$R(t) = e^{-\lambda t} \leftarrow \text{CONSTANT FAILURE RATE RELIABILITY}$$

$$\frac{1}{(s+a)(s+b)} = \frac{1}{(s+a)(b-a)} + \frac{1}{(s+b)(a-b)} \leftarrow \text{PARTIAL FRACTIONS}$$

$$\mathcal{L}[u(t)] = \frac{1}{s}$$

$$\mathcal{L}[e^{-at}] = \frac{1}{s+a}$$

$P_r[k \text{ ERRORS IN } n \text{ TRIALS EACH WITH PROBABILITY } p] = \binom{n}{k} (1-p)^k p^{n-k}$

TRUE		200
FALSE		
1		50
2		50
3		50
4		50

Experiment 1: Thevenin's Theorem

Objective: To determine the Thevenin voltage $V_{th}(t)$ and Thevenin resistance R_{th} of a network containing a dependent current source $I_s(t)$ and a resistor R_1 . The circuit is shown in Figure 1.



(a) As $V_d(t)$ first starts to rise, the diode is forward biased and the current through it is $I_s(t)$. The voltage across R_2 is $V_d(t) = I_s(t) R_2$. As $V_d(t)$ increases, the diode becomes reverse biased and the current through it is zero. At this point, the voltage across R_2 is $V_d(t) = I_s(t) R_2$.




As the diode becomes reverse biased, the current through it is zero. The voltage across R_2 is $V_d(t) = I_s(t) R_2$.

$$V_d(t) = V_s(t) - V_m$$


$$= V_m \sin(\omega t - \phi)$$

Our source voltage looks like

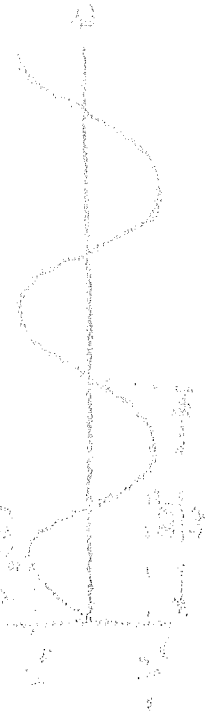

The diode voltage $V_d(t) = V_s(t) - V_m$

$$V_d(t) = V_s(t) - V_m$$

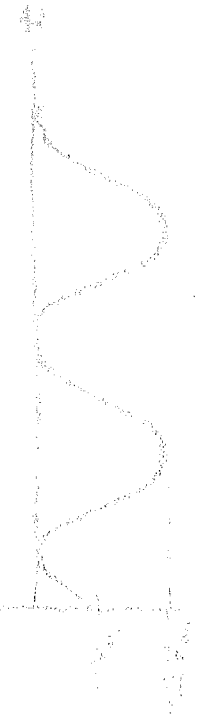

(b) We can calculate the current $I_d(t)$ through the diode. The current $I_d(t)$ is zero when the diode is reverse biased.

$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt = \frac{1}{2\pi} \int_0^{2\pi} v_m \sin \omega t dt$$

$$= \frac{v_m}{2\pi} \left[-\cos \omega t \right]_0^{2\pi} = \frac{v_m}{2\pi} (-\cos 2\pi + \cos 0) = \frac{v_m}{2\pi} (-1 + 1) = 0$$

$$V_{avg} = \frac{1}{T} \int_0^T v(t) dt$$

$$= \frac{1}{2\pi} \int_0^{2\pi} v_m \sin \omega t dt$$

$$= \frac{1}{2\pi} \omega v_m \left[-\cos \omega t \right]_0^{2\pi} = \frac{1}{2\pi} \omega v_m (-\cos 2\pi + \cos 0)$$

$$= \frac{1}{2\pi} \omega v_m (-1 + 1) = 0$$

$$= \frac{1}{2\pi} \omega v_m \left[\frac{2\pi}{\omega} + 0 - \frac{2\pi}{\omega} - 0 \right]$$


$$= \frac{1}{2\pi} \omega v_m \left(\frac{2\pi}{\omega} \right)$$

$$= \frac{1}{2} v_m$$

$$\text{avg } v = \frac{v_m}{2} = \frac{10}{2} = 5 \text{ V} \Rightarrow r = \sqrt{2}$$

200.707

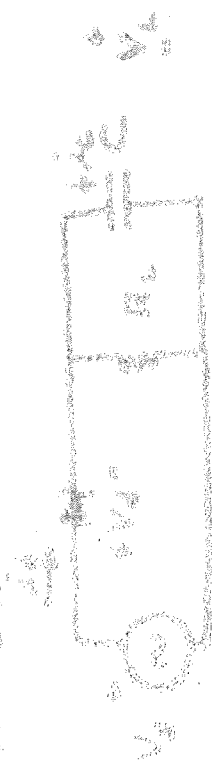2. FOR THE HALF-WAVE RECTIFIER WITH CAPACITIVE FILTER, SKETCH THE SOURCE VOLTAGE, DIODE VOLTAGE, AND DIODE CURRENT ON THE SAME GRAPH. DOCUMENT YOUR RESULTS.




THE GRAPH OF SOURCE VOLTAGE VS. V_L WAS GIVEN IN CLASS:



MORE AND MORE VOLTAGE IS APPLIED
 FROM THE POSITIVE JUNCTION, MORE AND MORE THIS
 SYSTEM BECOMES PLAIN CARBON.



THE DIODE WILL BE CONDUCTING IN THAT REGION UNTIL
 THE TIME WHEN $V_d = 0$. AT t_1 , THE DIODE WILL BE
 V_d , WITH THAT RESPECT V_d AND THE DIODE WILL BE
 THE DIODE WILL BE CONDUCTING IN THAT REGION UNTIL
 THE TIME WHEN $V_d = 0$. AT t_1 , THE DIODE WILL BE
 V_d , WITH THAT RESPECT V_d AND THE DIODE WILL BE
 THE DIODE WILL BE CONDUCTING IN THAT REGION UNTIL
 THE TIME WHEN $V_d = 0$. AT t_1 , THE DIODE WILL BE
 V_d , WITH THAT RESPECT V_d AND THE DIODE WILL BE

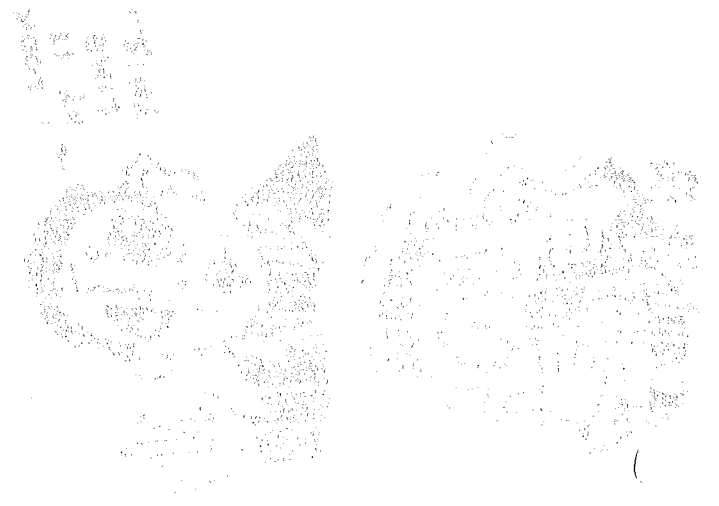

"WHEN THE DIODE IS THE DIODE OF
 THE DIODE CONDUCTIVE AND
 BECAUSE, IT IS THE DIODE OF
 THE DIODE OF THE DIODE"

DUE 2/10/77
11.22.26

HOMEWORK #2


1. (a) SHOW THAT, IF $X(s) = \mathcal{L}\{x(t)\}$ AND $x(t) > 0$ FOR ALL t , THEN $\int \mathcal{L}\{x(t-\tau)\} = X(s)e^{-s\tau}$

(b) THE INPUT-OUTPUT RELATION OF A LINEAR TIME-INVARIANT SYSTEM CAN BE EXPRESSED BY THE "CONVOLUTION INTEGRAL"

$$y(t) = \int_0^{\infty} x(\tau) h(t-\tau) d\tau$$

WHERE $h(t) = \mathcal{L}^{-1}\{T(s)\}$, USING THE RESULTS OF (a), SHOW THAT IT FOLLOWS THAT $Y(s) = X(s)T(s)$.

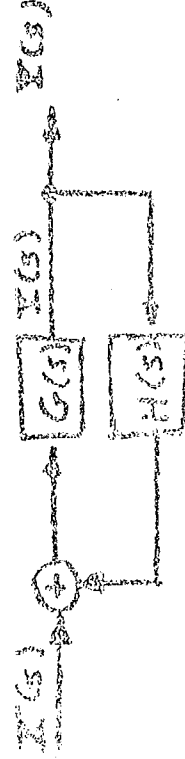2. CONSIDER TWO SYSTEMS CONNECTED IN A SERIES CONFIGURATION:



DERIVE THE TRANSFER FUNCTION $T(s) = Y(s)/X(s)$ (HINT: SEE P. 233 OF SMITH)

3. CLASSIFY THE FOLLOWING SYSTEMS ACCORDING TO LINEARITY, TIME INVARIANCE, AND CAUSALITY.

- (a) $y(t) = \int_0^t x(\tau) d\tau$
- (b) $y(t) = ax(t) + b$
- (c) $y(t) = \int_0^{\infty} x(\tau) d\tau$
- (d) $y(t) = \mathcal{L}\{x(t) - 1\}$
- (e) $y(t) = x_x(t)$
- (f) $y(t) = x(t-1)$

WHICH SYSTEMS CAN WE USE LAPLACE TRANSFORMS ON?


4. FOR THE FOLLOWING CIRCUIT

(a) FIND THE TRANSFER FUNCTION $Y(s) = V_o(s)/V_i(s)$

(b) FIND THE OUTPUT FOR $V_i(t) = V_o e^{-t}$

(c) DISCUSS YOUR RESULT IN (b)

(d) COMPUTE AND SKETCH THE FREQUENCY RESPONSE $|T(j\omega)|$.

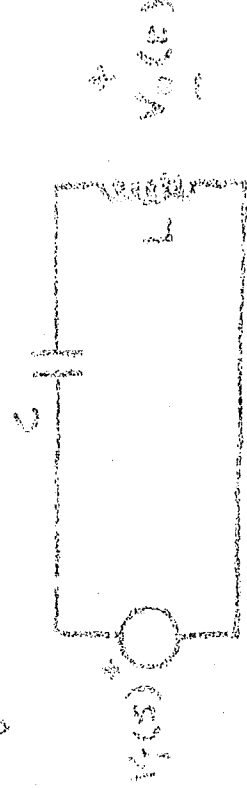

DATE 2/10/77
 W. S. S. S.

HOME WORK #2


1. (a) SHOW THAT, IF $X(S) = \int_0^\infty x(t)e^{-st} dt$ AND $Y(S) = \int_0^\infty y(t)e^{-st} dt$, THEN $\int_0^\infty x(t-\tau)e^{-st} dt = X(S)e^{-s\tau}$

(b) THE INPUT-OUTPUT RELATION OF A LINEAR TIME-INVARIANT SYSTEM CAN BE EXPRESSED BY THE "CONVOLUTION INTEGRAL"

$$Y(t) = \int_0^\infty x(\tau) h(t-\tau) d\tau$$

WHERE $h(t) = \mathcal{L}^{-1}\{T(S)\}$, USING THE RESULTS OF (a), SHOW THAT IT FOLLOWS THAT $Y(S) = X(S)T(S)$.

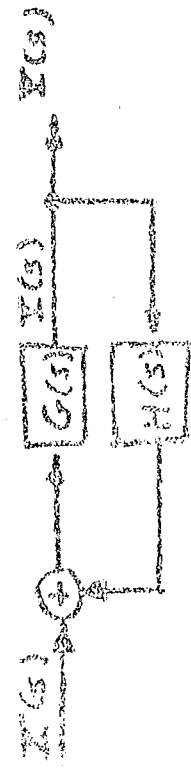2. CONSIDER TWO SYSTEMS CONNECTED IN A SERIES CONFIGURATION:



DERIVE THE TRANSFER FUNCTION $T(S) = Y(S)/X(S)$ (HINT: SEE P. 233 OF SMITH)

3. CLASSIFY THE FOLLOWING SYSTEMS ACCORDS TO LINEARITY, TIME INVARIANCE, AND CAUSALITY.

- (a) $y(t) = \frac{d}{dt} x(t)$
- (b) $y(t) = a x(t) + b$
- (c) $y(t) = \int_0^t x(\tau) d\tau$
- (d) $y(t) = [x(t) - 1]^*$
- (e) $y(t) = x(t)$
- (f) $y(t) = x(t-1)$

WHICH SYSTEMS CAN WE USE LAPLACE TRANSFORMS ON?


FOR THE FOLLOWING CIRCUIT

(a) FIND THE TRANSFER FUNCTION $T(S) = V_o(S)/V_i(S)$

(b) FIND THE OUTPUT FOR $V_i(t) = V_o \cos t$

(c) DISCUSS YOUR RESULT IN (b)

(d) COMPUTE AND SKETCH THE FREQUENCY RESPONSE $|T(j\omega)|$.

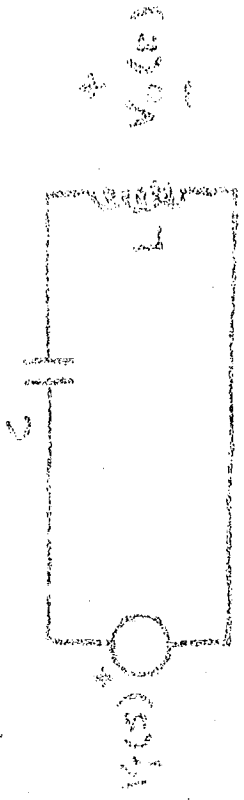

Now we can write the following:

$$1. (a) Y(s) = \int_{-\infty}^{\infty} [x(t-p)] e^{-st} dt = \int_{-\infty}^{\infty} x(t) e^{-s(t+p)} dt = e^{-sp} \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{-sp} X(s)$$

Let $t = t+p$ so $dt = dt$

$$\Rightarrow X(s) = \int_{-\infty}^{\infty} x(t) e^{-s(t+p)} dt = e^{-sp} \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{-sp} X(s)$$


$$\Rightarrow X(s) = \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{-sp} X(s)$$

$$\Rightarrow X(s) = \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{-sp} X(s)$$

$$(b) Y(s) = \int_{-\infty}^{\infty} x(t) e^{-st} dt = \int_{-\infty}^{\infty} x(t) e^{-s(t-p)} dt = e^{sp} \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{sp} X(s)$$

$$Y(s) = \int_{-\infty}^{\infty} x(t) e^{-s(t-p)} dt = e^{sp} \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{sp} X(s)$$

$$Y(s) = X(s) e^{sp}$$

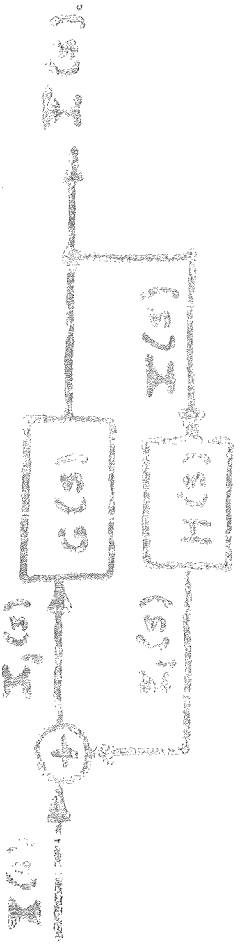

$$Y(s) = X(s) + H(s)Y(s) \Rightarrow Y(s) - H(s)Y(s) = X(s) \Rightarrow Y(s)(1 - H(s)) = X(s) \Rightarrow Y(s) = \frac{X(s)}{1 - H(s)}$$

Alternative 1 and 2:

$$Y(s) = X(s) + H(s)Y(s) \Rightarrow Y(s) - H(s)Y(s) = X(s) \Rightarrow Y(s)(1 - H(s)) = X(s) \Rightarrow Y(s) = \frac{X(s)}{1 - H(s)}$$

$$Y(s) = \frac{X(s)}{1 - H(s)}$$

$$3. (a) Y(s) = \int_{-\infty}^{\infty} x(t) e^{-st} dt = \int_{-\infty}^{\infty} x(t) e^{-s(t-p)} dt = e^{sp} \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{sp} X(s)$$

$$= \int_{-\infty}^{\infty} x(t) e^{-s(t-p)} dt = e^{sp} \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{sp} X(s)$$

$$= \int_{-\infty}^{\infty} x(t) e^{-s(t-p)} dt = e^{sp} \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{sp} X(s)$$

$$= \int_{-\infty}^{\infty} x(t) e^{-s(t-p)} dt = e^{sp} \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{sp} X(s)$$

$$(b) Y(s) = \int_{-\infty}^{\infty} x(t) e^{-st} dt = \int_{-\infty}^{\infty} x(t) e^{-s(t-p)} dt = e^{sp} \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{sp} X(s)$$

$$= \int_{-\infty}^{\infty} x(t) e^{-s(t-p)} dt = e^{sp} \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{sp} X(s)$$

$$= \int_{-\infty}^{\infty} x(t) e^{-s(t-p)} dt = e^{sp} \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{sp} X(s)$$

$$= \int_{-\infty}^{\infty} x(t) e^{-s(t-p)} dt = e^{sp} \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{sp} X(s)$$

$$(c) Y(s) = \int_{-\infty}^{\infty} x(t) e^{-st} dt = \int_{-\infty}^{\infty} x(t) e^{-s(t-p)} dt = e^{sp} \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{sp} X(s)$$

$$= \int_{-\infty}^{\infty} x(t) e^{-s(t-p)} dt = e^{sp} \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{sp} X(s)$$

$$= \int_{-\infty}^{\infty} x(t) e^{-s(t-p)} dt = e^{sp} \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{sp} X(s)$$

$$= \int_{-\infty}^{\infty} x(t) e^{-s(t-p)} dt = e^{sp} \int_{-\infty}^{\infty} x(t) e^{-st} dt = e^{sp} X(s)$$

$$(a) \quad Y(s) = \frac{1}{s^2 + 2s + 1}$$

$$= \frac{1}{(s+1)^2} = \frac{A}{s+1} + \frac{B}{(s+1)^2}$$

$$\Rightarrow Y(s) = \frac{1}{(s+1)^2} = \frac{A}{s+1} + \frac{B}{(s+1)^2}$$

where

$$(s+1) \cdot Y(s) = 1 = A(s+1) + B$$

$$\Rightarrow 1 = A(s+1) + B = As + A + B$$


$$\Rightarrow Y(s) = \frac{1}{(s+1)^2} = \frac{0}{s+1} + \frac{1}{(s+1)^2}$$

$$(b) \quad Y(s) = \frac{1}{s^2 + 1}$$

where

$$\Rightarrow Y(s) = \frac{1}{s^2 + 1} = \frac{A}{s-j} + \frac{B}{s+j}$$

where

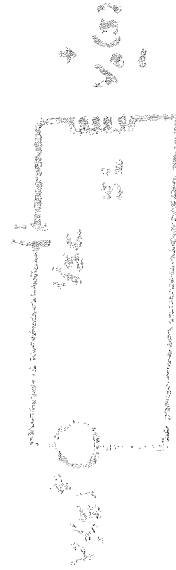

$$(c) \quad \text{VOLTAGE DIVIDER: } V_o(s) = \frac{s}{s+1} V_i(s)$$

$$\Rightarrow Y(s) = \frac{V_o(s)}{V_i(s)} = \frac{s}{s+1} = \frac{A}{s+1} + B$$

$$(d) \quad Y(s) = \frac{1}{s^2 + 1} = \frac{A}{s-j} + \frac{B}{s+j}$$

$$V_i(s) = \frac{1}{s^2 + 1} = \frac{A}{s-j} + \frac{B}{s+j}$$

where

where

$$V_i(s) = \frac{1}{s^2 + 1}$$

(c) THE CIRCUIT IS AN OSCILLATOR, IN PRACTICE,


THE OSCILLATOR WILL BE "DAMPED" SINCE THERE

ARE RESISTORS IN THE CIRCUIT WITH A POSITIVE

RESISTANCE. IN AN IDEAL OSCILLATOR, THERE

WOULD BE NO DAMPING.

WHEREAS IN AN IDEAL OSCILLATOR, THERE

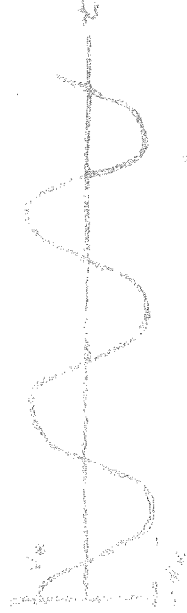


$$V_o(t) = e^{-\alpha t} \sin(\omega t)$$



$$V_o(t) = \sin(\omega t)$$

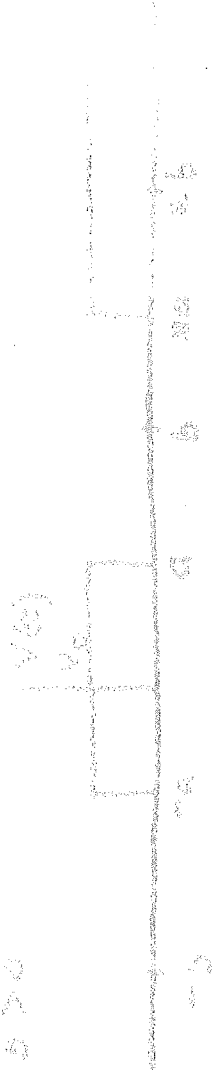FOR THE FOLLOWING PERIOD WAVEFORM $x(t)$ WITH THE FOURIER SERIES COEFFICIENTS B_n , ALSO THAT $b > 0$



[Hint: $\int_0^{2\pi} (e^{j\theta} - e^{-j\theta}) d\theta = 4j$]

(A) ASSUME THAT $b = 2a$. WHAT IS B_n FOR

$n = 0$ [Hint: $\lim_{x \rightarrow 0} \frac{\sin x}{x} = 1$]
 n EVEN

$n = 1, 5, 9, 13, 17, \dots$

$n = 3, 7, 11, 15, 19, \dots$

(B) PLOT $|x(t)|/V_0$ FOR n UP TO

(C) FOR $x(t) = \sum_{n=-\infty}^{\infty} B_n e^{jn\omega t}$

(a) SHOW THAT $\int_{-\infty}^{\infty} x(t) dt = \sum_{n=-\infty}^{\infty} B_n \int_{-\infty}^{\infty} e^{jn\omega t} dt$

[Hint: $\int_{-\infty}^{\infty} e^{j\omega t} dt = 2\pi \delta(\omega)$]

(b) PROVE PARSEVAL'S THEOREM

$\int_{-\infty}^{\infty} |x(t)|^2 dt = \sum_{n=-\infty}^{\infty} \frac{|B_n|^2}{2T}$

[Hint: $|\sum_{n=1}^M B_n|^2 = \sum_{n=1}^M \sum_{m=1}^M B_n B_m^*$


$\int_{-\infty}^{\infty} e^{j\omega t} e^{-j\omega' t} dt = 2\pi \delta(\omega - \omega')$

$B_m = \begin{cases} 1 & ; n = 0, 1, 2, \dots \\ 0 & ; n = 3, 4, 5, \dots \end{cases}$ ~~SEE KARNESEKIA D~~

(B) JOHNNY CASH AND TINY TIM (LO & MI VOICES ARE A 3 MINUTE 55 SECOND READING. IF NEITHER VOICE EXCEEDED 20 HZ ($= 20,000$ CYCLES PER SEC) WE WISHED TO STORE THE RECORD IN SAMPLES PER SEC, HOW MANY SAMPLES WOULD WE NEED TO STORE? IF WE LOST EVERY OTHER SAMPLE, WOULD VOICE WOULD BE DISTORTED? WHY?

NO

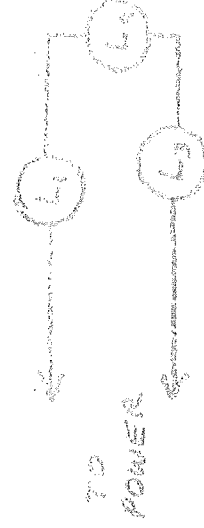(A) CONSIDER A SYSTEM CONSISTING OF THREE LIGHTBULBS WROGEO IN SERIES



WE CONSIDER THE SYSTEM 'OPERATIONAL' IF TWO OR MORE OF THE LIGHTS ARE ON

(a) ASSUMING THAT THE MTFD OF EACH BULB IS TWO MONTHS, AND THAT THERE ARE ON THE AVERAGE TWO PORTION OF THE BATHROOM EACH DAY, THE SYSTEM MTEF AND THE MTTBF THAT THE SYSTEM WILL BE OPERATIONAL TWO MONTHS OF USE.


(b) IF IT TAKES 30 MINUTES TO REPLACE A BULB, COMPUTE THE SYSTEM AVAILABILITY. (ASSUME 1 MONTH OF USE)

(c) CONSIDERING OUR DEFINITION OF RELIABILITY, SUGGEST A BETTER WAY OF DEFINING THE RELIABILITY OF THE SYSTEM. (CAN YOU COMPUTE THE MTTB FOR A NEW SYSTEM?)

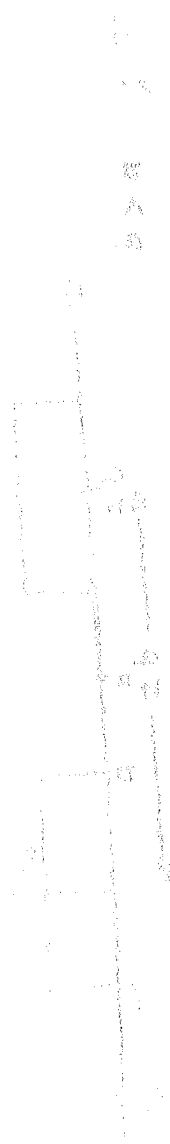(d) IN THE IMPROVED SYSTEM OF PART (c) EXPLAIN HOW THE AVAILABILITY OF THE SYSTEM IS IMPROVED BY INTRODUCING A MAINTENANCE POLICY OF PREVENTATIVE MAINTENANCE. WILL THIS EFFECT THE MTTB?

* i.e. REPLACING A BURNT OUT BULB BEFORE THE SYSTEM IS 'UNOPERABLE'

"HE THAT REFUSETH INSTRUCTION DETHENETH HIS OWN SOUL"



Find the area of the region bounded by the lines $x=0$, $x=1$, $y=0$, and $y=1$.

$$\begin{aligned}
 (a) \text{ Area} &= \int_0^1 \int_0^1 dx dy \\
 &= \int_0^1 [x]_0^1 dy \\
 &= \int_0^1 (1-0) dy \\
 &= \int_0^1 1 dy \\
 &= [y]_0^1 \\
 &= 1-0 \\
 &= 1
 \end{aligned}$$

(b) $x=0 \Rightarrow dx = 0$ OTHERWISE



$$\begin{aligned}
 (c) \text{ Area} &= \int_0^1 \int_0^1 dx dy \\
 &= \int_0^1 [x]_0^1 dy \\
 &= \int_0^1 (1-0) dy \\
 &= \int_0^1 1 dy \\
 &= [y]_0^1 \\
 &= 1-0 \\
 &= 1
 \end{aligned}$$

$$\begin{aligned}
 (d) \text{ Area} &= \int_0^1 \int_0^1 dx dy \\
 &= \int_0^1 [x]_0^1 dy \\
 &= \int_0^1 (1-0) dy \\
 &= \int_0^1 1 dy \\
 &= [y]_0^1 \\
 &= 1-0 \\
 &= 1
 \end{aligned}$$

$$\frac{1}{2} \times 1 \times 1 = \frac{1}{2}$$

(b) 5 = TOTAL SAMPLES

$$= (3 \text{ MIN } 55 \text{ SEC}) (2 \times 20 \text{ KHz})$$

$$= (235 \text{ SEC}) (40,000 / \text{SEC}) = 9.4 \text{ MILLION SAMPLES}$$

UNDEA-SAMPLING DISTORTS THE HIGHER FREQUENCY COMPONENTS. THUS, THE HIGHER FREQUENCY VOICE, WOULD BE DISTORTED.

(c) SINCE ONE LIGHT BULB FAILS EVERY 30 MIN IN SYSTEM FAILURE, THE SYSTEM MTBF IS

$$\text{MTBF}_S = \frac{\text{MTBF}_1}{3} = \frac{2}{3} \text{ MONTH}$$

$$P(t) = e^{-t/\text{MTBF}_S} \Rightarrow R_S(2 \text{ MONTH}) = e^{-3}$$

$$= e^{-3} \approx 0.05 \Rightarrow \text{THERE IS A 5% CHANCE THAT THE SYSTEM WILL OPERATE FOR TWO STRAIGHT MONTHS.$$


IF CHANCE THE SYSTEM WILL OPERATE FOR TWO STRAIGHT MONTHS.

(d) MTTR = 30 MIN

$$A = \frac{\text{MTBF}}{\text{MTBF} + \text{MTTR}} = \frac{\frac{2}{3} \times 30 \times 24 \times 60}{\frac{2}{3} \times 30 \times 24 \times 60 + 30}$$

$$= \frac{28800}{28830} = 99.9967\%$$

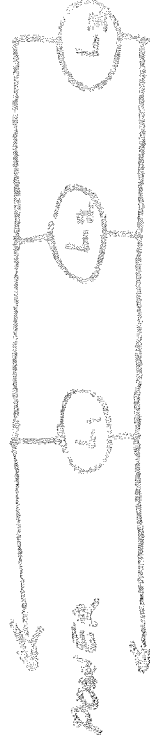(e) IT WOULD BE BETTER TO CONNECT THE BULBS IN PARALLEL




HERE, IF ONLY ONE LIGHT FAILS, THE SYSTEM IS STILL "OPERABLE"

(f) BY REPLACING A LIGHT WHICH HAS BURNT OUT WHILE THE SYSTEM IS "OPERABLE", WE ARE PERFORMING "PREVENTIVE MAINTENANCE". THE MTTR IS ^{REDUCED} STILL THE SAME, BUT THE MTBF (AND THUS THE AVAILABILITY) IS INCREASED.

WE THAT HANDLE A MATTER WISELY SHALL FIND GOD AT WHOSE TRUSTETH IN THE LORD, HAPPY IS HE."


QUESTION (20 MARKS) PART (A)

THE MOSFET

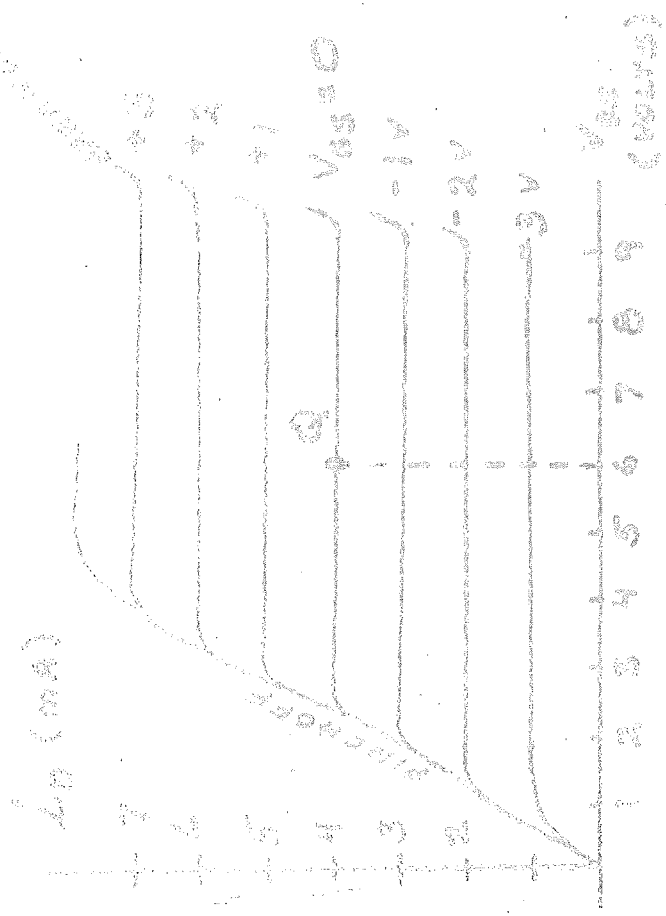

$V_{DD} = 10V$ (a) DETERMINE R_D TO ESTABLISH QUIESCENCE AT THE POINT INDICATED. $V_{DD} = 10V$

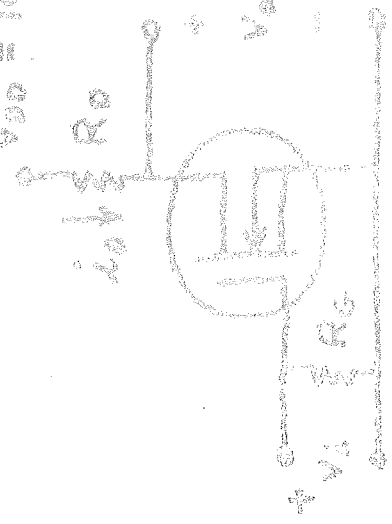
(b) DETERMINE THE EQUATION FOR THE LOAD LINE AND SKETCH IT ON THE ABOVE



(c) FROM (b), MAKE A PLOT OF SOME POINTS FOR THE CURVE i_D vs. V_{DS} . ASSUMING V_{GS} IS THE INPUT AND TO THE OUTPUT, WHAT IS THE 'GAIN' OF THIS TRANSDUCE IN AMO'S?

(d) GIVE AN ESTIMATE OF THE INTERVAL V_{GS} MUST BE LIMITED TO TO AVOID CROSS CURRENT 'DISTORTION'

(2) OUR TRANSISTOR P.D. MODEL HAS

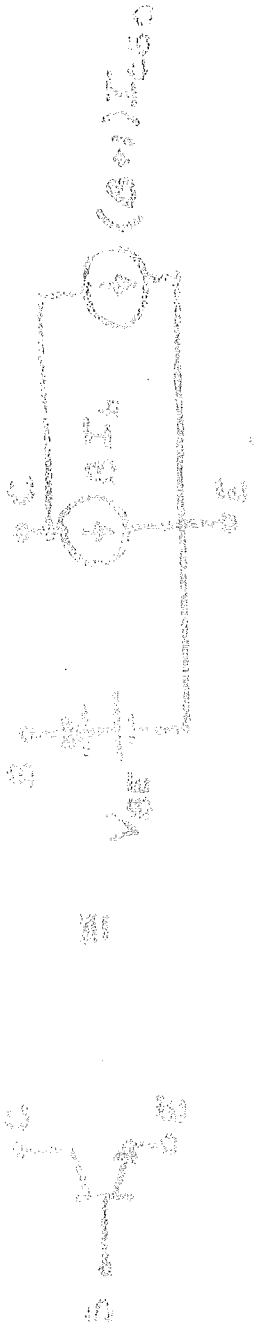

(a) FOR $I_{C0} = 5 \mu A$, SKETCH I_C (VERTICAL AXIS) VS. V_{CE} ON THE SAME GRAPH FOR $I_B = 0.1, 0.2, 0.3, 0.4 \text{ mA}$. ASSUME $\beta = 100$

(b) REPEAT (a) FOR $\beta = 200$. HOW HAS THE CURVE CHANGED?

(c) COMPARE YOUR SKETCH IN (a) TO THE CORRESPONDING TRANSISTION CURVE.

(d) EXPLAIN WHY WE WOULD REQUIRE $I_C > 0$ (IN THE MODEL AND PHYSICALLY)

(3) IN A CERTAIN TRANSISTOR, THE PARAMETER CHANGE WITH TEMPERATURE BUT ARE KNOWN TO FALL WITHIN THE BOUNDS:

$$30 < \beta < 180$$

$$0.8 < V_{BE} < 0.9 \text{ VOLTS}$$

$$I_C \leq I_{C0} = 10 \text{ nA}$$


BY USING WORST CASE CONDITIONS, FIND THE BOUNDS ON THE VARIATION OF I_C IN A SELF-BIASING CIRCUIT. WHAT IS THE MINIMUM AND MAXIMUM VALUE THAT

$$I_{C0} = I_{C0} \text{ IN THE CIRCUIT}$$

ASSUME THAT THE CIRCUIT VALUES ARE


$$R_A = 10 \text{ k}\Omega, R_B = 100 \text{ k}\Omega, R_E = 1 \text{ k}\Omega$$
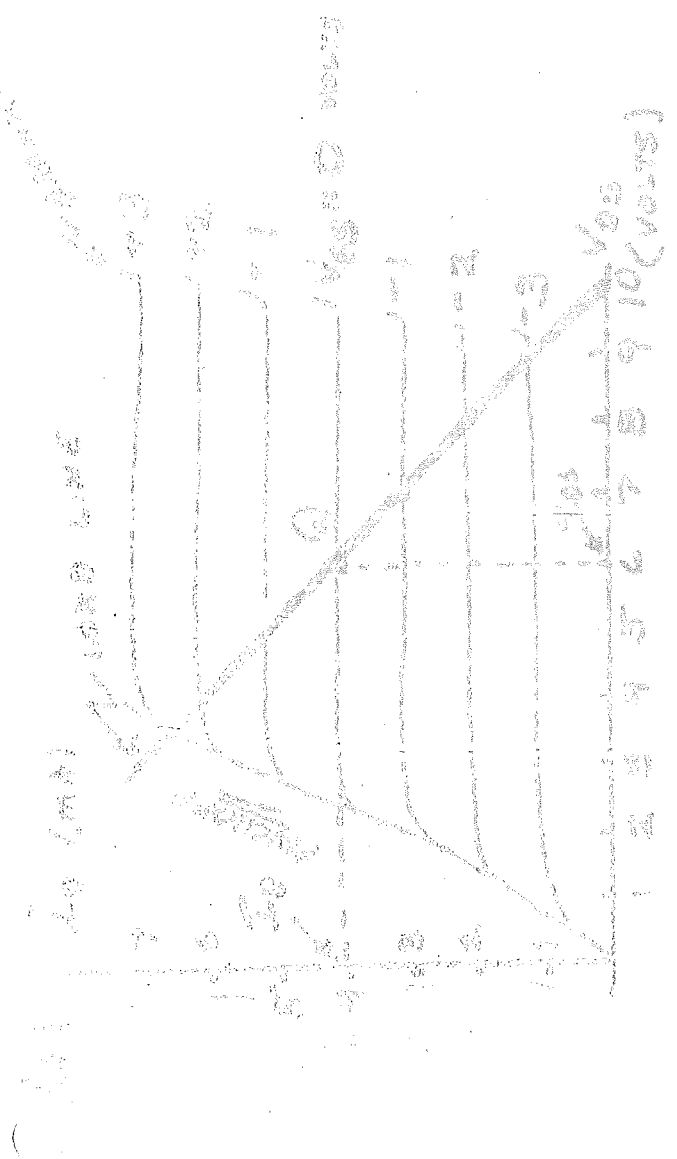
$$I_{C0} = 5 \text{ nA AND } V_{CE} = 22 \text{ VOLTS}$$




(a) $V_{GS} = V_{DS} = R_o I_D = 10^4 I_D$
 $\Rightarrow R_o = (V_{GS} - V_{GS0}) / I_D = 10^4 \text{ volts / amp} = 1 \text{ k}\Omega$

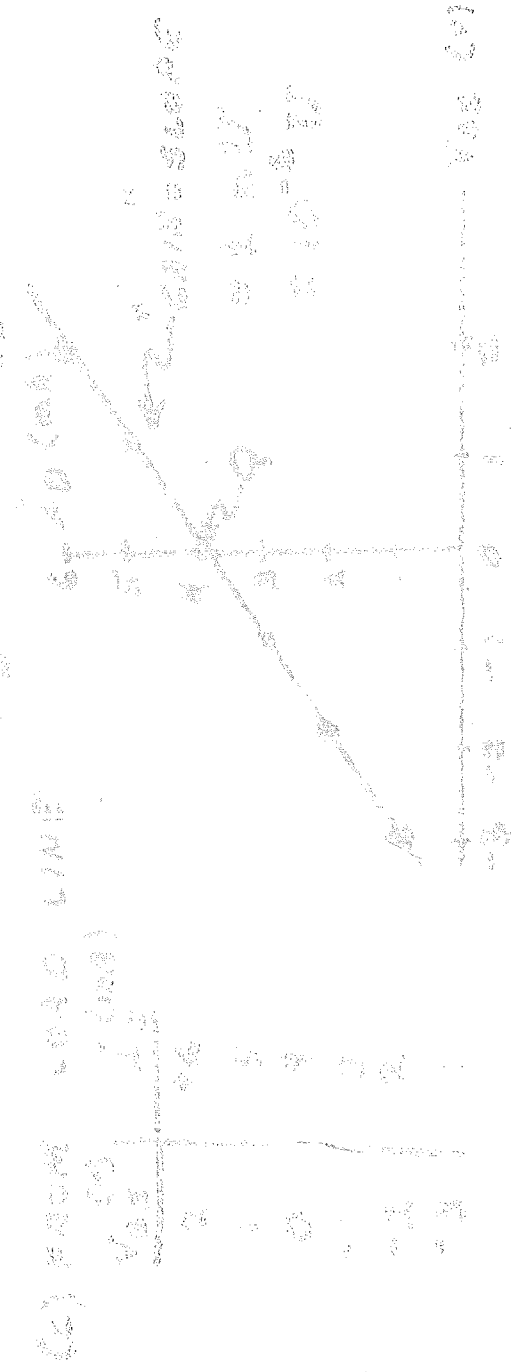(b) LOAD LINE: $V_{GS} = V_{DS} = R_o I_D$
 $\Rightarrow V_{GS} = 10^4 I_D = 10^4 I_D$
 $\Rightarrow I_D = 10^{-4} (V_{GS} / 10)$



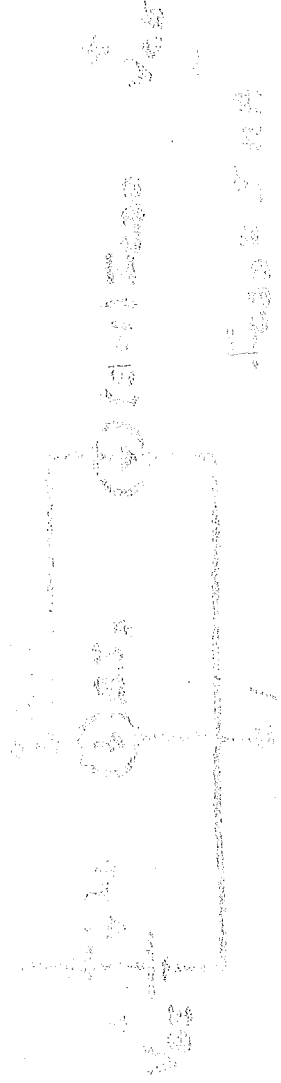(d) For $V_{GS} = 0$, $I_D = 0$, $V_{DS} = 10$ V. For $V_{GS} = 10$, $I_D = 10^{-4} (10 / 10) = 10^{-5}$ A. For $V_{GS} = 5$, $I_D = 10^{-4} (5 / 10) = 5 \times 10^{-5}$ A. For $V_{GS} = 10$, $I_D = 10^{-4} (10 / 10) = 10^{-4}$ A.



(a) SUMMING CURRENT AT CATHODE: $I_{D1} + I_{R1} + (20\mu)I_{D1}$
 EQUATION: $I_{D1} = 100 I_{D1} + 10 I_{R1}$
 FOR $I_{D1} = 0.1, 0.2, 0.3, 0.4 \text{ mA}$




(b) FOR 5 mA, CURVE IS SIMPLY 'SPRINGS UP'
 EQUATION: $I_{D1} = 100 I_{D1} + 10 I_{R1}$ $I_{D1} = 0.2, 0.4, 0.6, 0.8 \text{ mA}$
 FOR $I_{D1} = 0.1, 0.2, 0.3, 0.4 \text{ mA}$ $I_{D1} = 0.2, 0.4, 0.6, 0.8 \text{ mA}$



- (c) I DO SIMPLY SO THAT I CAN SHOW
 THAT THE VOLTAGE IS NOT IN OUR MEASUREMENTS
 (OUR VOLTAGE MEASUREMENTS ARE INVERTED)
 IN OUR ACTUAL TRANSMISSIONS.
- (d) THIS PROBLEM IS WORKED IN PART (b) & (c)
 (e) A PAGE 421 OF 5 WITH 3 NO. 20.

CHAPTER 5 SOLUTIONS (by Martin)

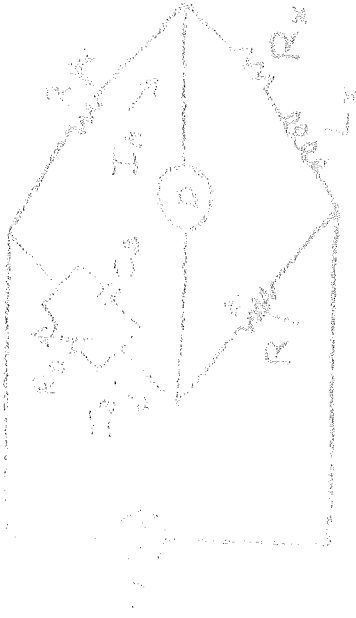

(a) UNDER BALANCED CONDITIONS

$$\Rightarrow I_0 Z_0 = I_A R_A$$

$$\text{WHERE } Z_0 = R_0 + j\omega C_0 = \frac{R_0}{1 + j\omega C_0 R_0}$$

$$\text{AND } I_0 R = I_A Z_x$$

$$\text{WHERE } Z_x = R_x + j\omega L_x$$

DIVIDING 1st BY 2nd AND SOLVING FOR Z_x GIVES:

$$Z_x = R_A R / Z_0 = R_A R (j\omega C_0 R_0 + 1) / R_0$$

$$\Rightarrow R_x + j\omega L_x = \frac{R_A R}{R_0} + j\omega [C_0 R_A R]$$

EQUATING REAL & IMAGINARY COMPONENTS:

$$R_x = R_A R / R_0 \quad L_x = C_0 R_A R$$

(b) $\epsilon[R_0] = [1 \pm 0.0001] [1 \pm 0.0002] [1 \pm 0.00001]$

$$\approx 1.00005 \Rightarrow \pm 0.5\%$$

$$\epsilon[L_x] = [1 \pm 0.0005] [1 \pm 0.0002] [1 \pm 0.0001]$$

$$= 1.00008 \Rightarrow \pm 0.8\%$$

(c) THERE IS NO DEPENDENCE ON ω OR V_0 .


IF WE SET EITHER TO ZERO, THE

OTHER EQUATIONS BECOME

DEFINITE, IN THE SENSE OF

GOING TO ZERO, INFINITY, OR

BEING UNDEFINED.

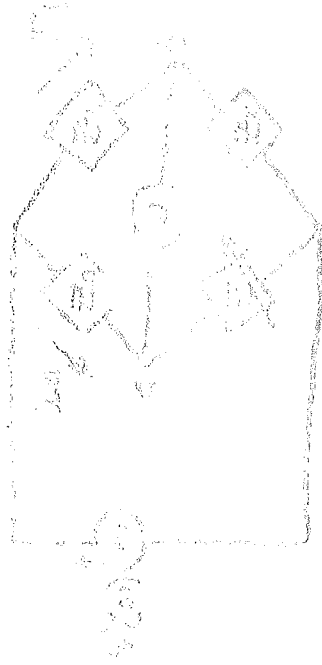


(A) WHEN THE VOLTAGE BETWEEN a & b IS ZERO, WE HAVE

$$I_1 Z_1 = I_2 Z_2 \quad \Rightarrow \quad \frac{I_1}{I_2} = \frac{Z_2}{Z_1}$$

$$I_3 Z_3 = I_4 Z_4 \quad \Rightarrow \quad \frac{I_3}{I_4} = \frac{Z_4}{Z_3}$$

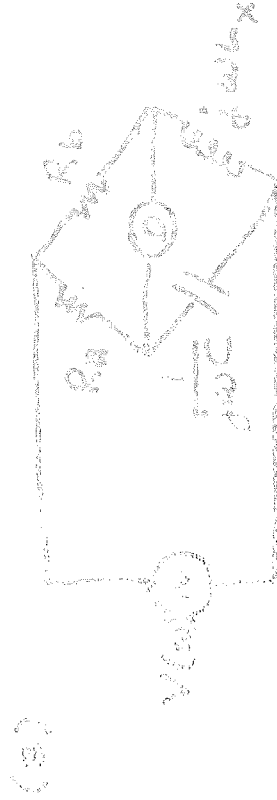(B) NOW, IF THE POTENTIAL AT a & b IS THE SAME



USING RESULTS OF (A) IN BRIDGE IS BALANCED

$$Z_1 = \frac{Z_2}{Z_3} Z_4$$

$$j\omega L_x = \frac{R_1}{R_2} j\omega C$$

$$\omega L_x \frac{R_2}{R_1} = \frac{1}{\omega C} \Rightarrow L_x = \frac{R_1}{R_2} \frac{1}{\omega^2 C}$$

LET, ALL INDUCTANCE MUST BE POSITIVE
THERE, WE CONCLUDE THAT THE BRIDGE
CANNOT BE BALANCED.

PROBLEM 10.10 (PROB 10.10) MARK

(1) DESIGN AN OP AMP CIRCUIT THAT EXAMINES A SIGNAL ABOUT 10 dB. THE DC GAIN, A_{0dB} , IS RELATED TO THE GAIN A_{ω} BY THE RELATION

$$A_{0dB} = 20 \log_{10} A_{\omega}$$

(a) DESIGN A 2ND AMP BASIC INVERTING CIRCUIT WITH A GAIN OF $A_{0dB} = 20$ dB AND AN INPUT IMPEDANCE (RESISTANCE) OF 100Ω


(b) SAME AS (a), BUT $A_{0dB} = 40$ dB

(c) IN GENERAL, IF WE DOUBLE THE dB GAIN, A_{0dB} , WHAT MUST WE DO TO THE GAIN, A_{ω} ?

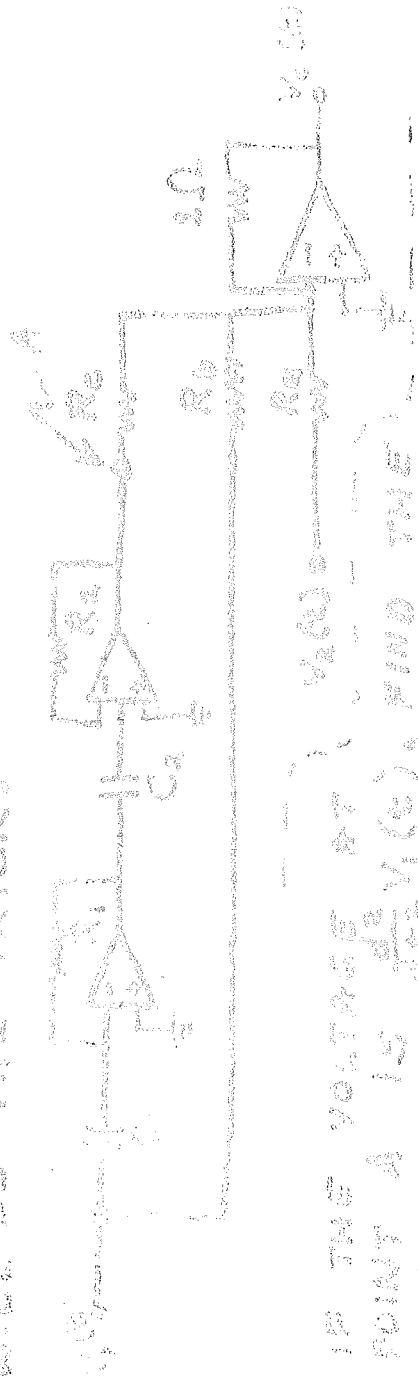(2) WE WISH TO COMBINE TWO VOLTAGES, $V_1(s)$ AND $V_2(s)$, INTO $V_3(s)$ WHERE

$$V_3(s) = aV_1(s) + bV_2(s) + c \frac{d^2V_2(s)}{dt^2}$$

WHERE a , b , AND c ARE KNOWN NEGATIVE CONSTANTS. THE FOLLOWING ANALOG COMPUTER WILL DO THE TRICK:



IF THE VOLTAGE AT $V_2(s)$ IS $V_2(s)$, FIND THE RELATIONSHIP BETWEEN THE REQUIRED PARAMETERS $R_1, C_1, R_2, C_2, R_3, R_4, R_5,$ AND R_6 WITH THE NEGATIVE CONSTANTS, $a, b,$ AND c . [HINT: IF $V_3(s) = d^2V_2(s)/dt^2$, THEN $R_1, C_1, R_2, C_2 =$ CONSTANT. FINDING THIS CONSTANT WILL BE THE SOLUTION TO HALF THIS PROBLEM. CONSTANT IS INDEPENDENT OF $a, b,$ AND c]

(a) OP AMPS AND ANALOG COMPUTERS CAN BE USED TO SOLVE DIFFERENTIAL EQUATIONS.

CONSIDER:

$$\frac{d^2 v_1(t)}{dt^2} = -a_2 \frac{dv_1(t)}{dt} + a_1 v_1(t) - b u(t)$$

WE WISH TO FIND $v_1(t)$ FOR A GIVEN INPUT, (OR "FORCING FUNCTION") $u(t)$. LET


$$v_2(t) = \frac{dv_1(t)}{dt} \quad \text{(a) SHOW THAT WE CAN COMBINE THESE ABOVE TWO RELATIONS INTO "STATE EQUATIONS":}$$

$$\dot{v}_1 = a_1 v_1 - a_2 v_2 - b u$$

$$\dot{v}_2 = v_2 \quad \left[v_2 = \frac{dv_1}{dt} \right]$$

(b) ASSUMING ZERO INITIAL CONDITIONS, FIND THE RELATIONS BETWEEN THE CONSTANTS $a_1, a_2,$ AND b AND THE R'S AND C'S IN THE FOLLOWING COMPUTER:

(SOLVE HERE IS SOLUTION TO DIFF. EQ (1))

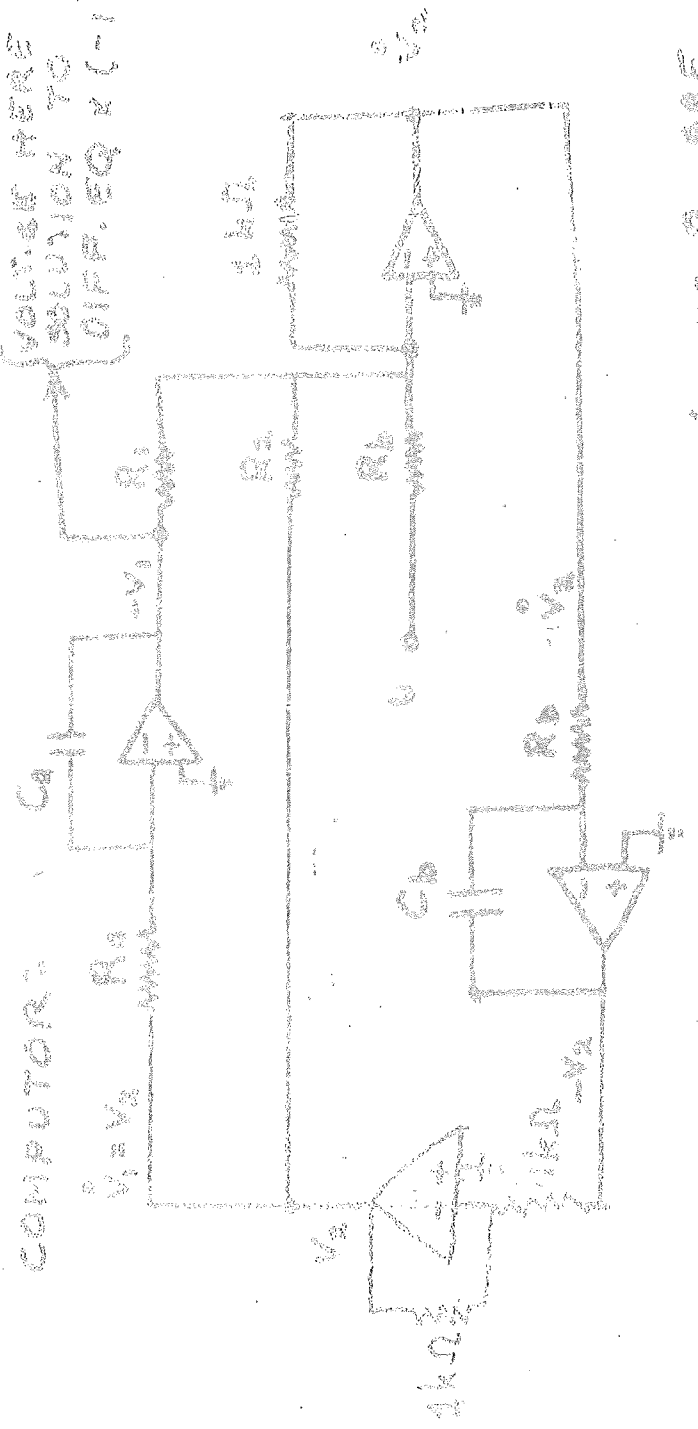

ASSUME THAT CONSTANTS $a_1, b,$ AND a_2 ARE POSITIVE (HINT: AS AN EXAMPLE, $R_2 C_a C_b = 1$ AND $R_1 = (1/a_1) k\Omega$ USE VOLTAGES SHOWN ON CIRCUIT)

1. The circuit is a common emitter amplifier with a load resistor R_L .

(a) The input signal is $v_i(t) = 10 \sin(10^4 t)$ mV. The output signal is $v_o(t) = 100 \sin(10^4 t)$ mV.



(b) The input signal is $v_i(t) = 10 \sin(10^4 t)$ mV. The output signal is $v_o(t) = 100 \sin(10^4 t)$ mV.

(c) The input signal is $v_i(t) = 10 \sin(10^4 t)$ mV. The output signal is $v_o(t) = 100 \sin(10^4 t)$ mV.

(d) The input signal is $v_i(t) = 10 \sin(10^4 t)$ mV. The output signal is $v_o(t) = 100 \sin(10^4 t)$ mV.

(e) The input signal is $v_i(t) = 10 \sin(10^4 t)$ mV. The output signal is $v_o(t) = 100 \sin(10^4 t)$ mV.

(f) The input signal is $v_i(t) = 10 \sin(10^4 t)$ mV. The output signal is $v_o(t) = 100 \sin(10^4 t)$ mV.

(g) The input signal is $v_i(t) = 10 \sin(10^4 t)$ mV. The output signal is $v_o(t) = 100 \sin(10^4 t)$ mV.

(h) The input signal is $v_i(t) = 10 \sin(10^4 t)$ mV. The output signal is $v_o(t) = 100 \sin(10^4 t)$ mV.

(i) The input signal is $v_i(t) = 10 \sin(10^4 t)$ mV. The output signal is $v_o(t) = 100 \sin(10^4 t)$ mV.



At 0, we have

$$v_o = -R_L C_1 \frac{dv_i}{dt}$$

$$v_o = (R_L C_1) \frac{dv_i}{dt} = R_L C_1 C_2 \frac{d^2 v_i}{dt^2}$$


Since we require $v_o = 100 \sin(10^4 t)$ mV, we have

$$\frac{d^2 v_o}{dt^2} = \frac{v_o}{R_L C_1} + \frac{v_o}{R_L C_2}$$

$$\text{or } v_o = \frac{v_o}{R_L C_1} + \frac{v_o}{R_L C_2} \Rightarrow v_o = \frac{v_o}{R_L C_1} + \frac{v_o}{R_L C_2}$$

Thus, $C_1 = -1/R_L C_2$, $C_2 = -1/R_L C_1$, $C_1 = -1/R_L C_2$

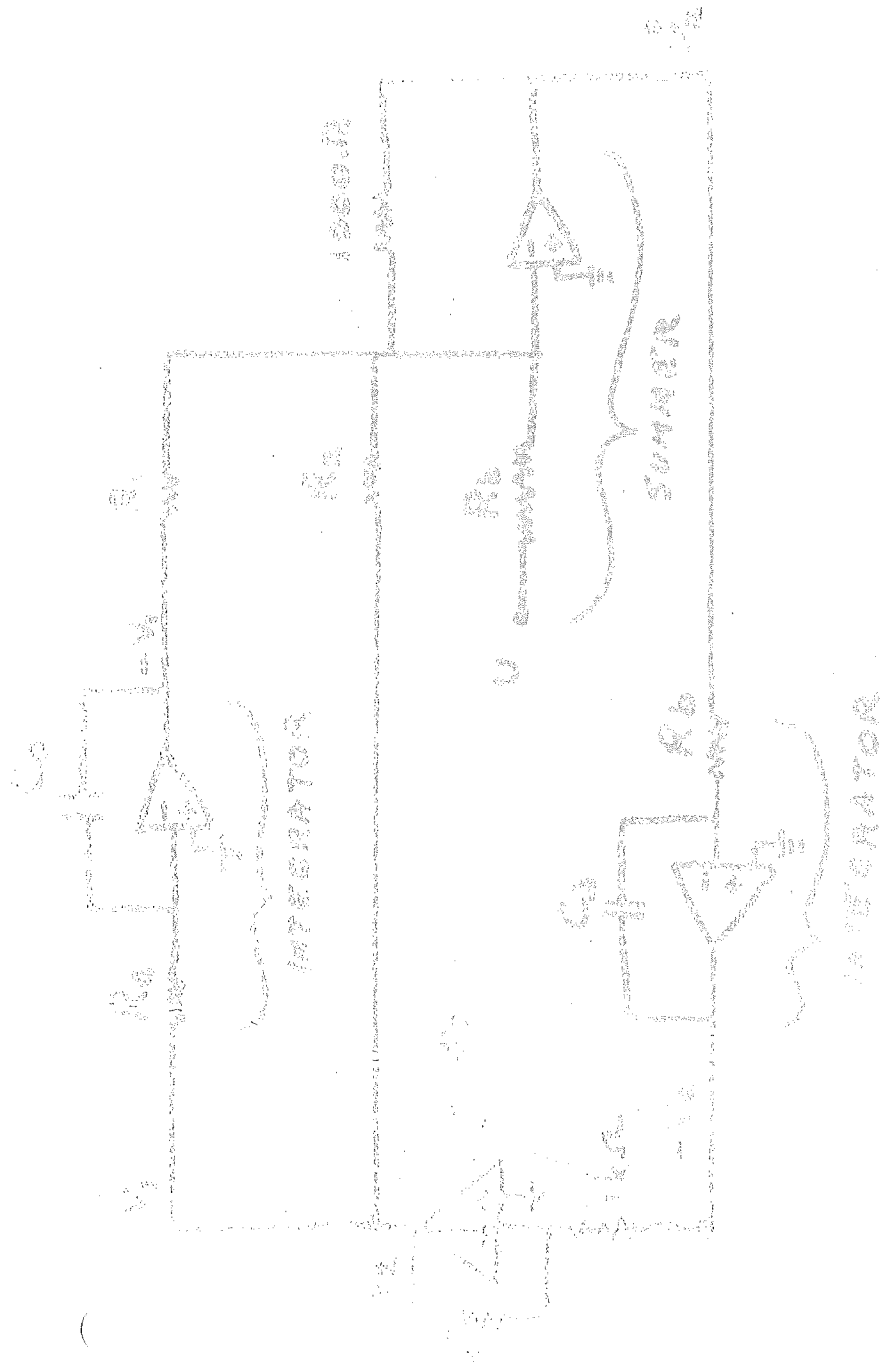or $R_L C_1 = -1/C_2$, $R_L C_2 = -1/C_1$, $R_L C_1 C_2 = -1$



THEY DO NOT INTERFERE, IN ORDER FOR THE
 SYSTEMS TO BE STABLE, THE PHASE MARGIN
 MUST BE POSITIVE, SIMILARLY, FOR THE SYSTEMS,
 THE PHASE MARGIN, $R_b C_b = 1$, IN THE SUMMER,
 WE SHOULD HAVE:

$$R_1 = (1/a)k_1, R_2 = (1/a_2)k_2, R_3 = (1/b)k_3$$

FROM ALL THESE, HOLD FAST THAT WHICH IS GOOD
 AND THE OTHERS ARE NEVER RECEIVED WITHIN
 THE SYSTEM - REVISION

THE PROVERB:
 'SOMEONE IS GOOD FOR YOU'
 -OLD FEE-

(EE 2334) MARKS

(a) DETERMINE THE RELATIONSHIP BETWEEN $V_0(t)$ AND $V_1(t)$ IN THE FOLLOWING OP AMP CIRCUIT (ASSUME $V_{in} \approx \int_0^t V_1 dt \approx 0$). WHY MIGHT WE CALL THIS CIRCUIT A "DOUBLE INTEGRATOR"?




[HINT: YOU WILL NEED TO ASSUME THAT THE OP AMP INPUT CURRENT IS 0.]

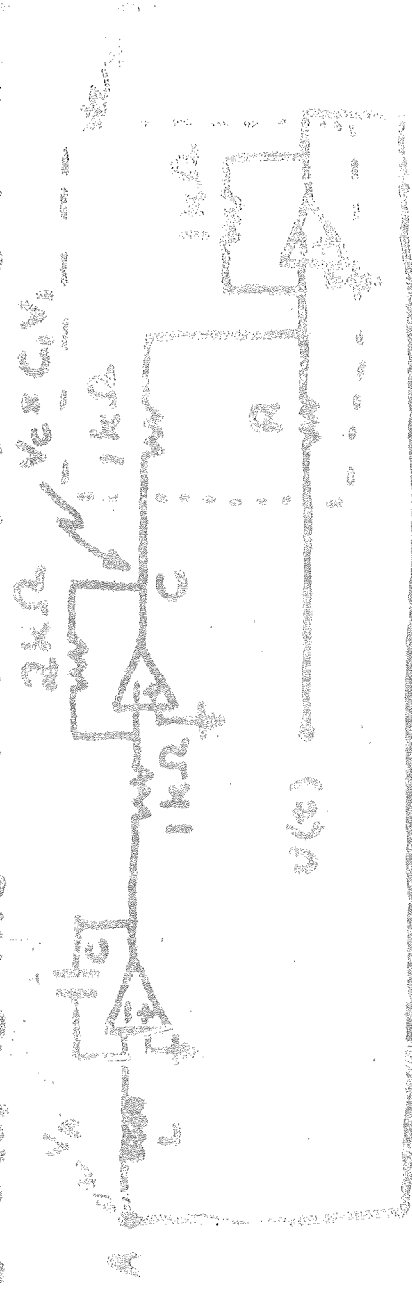(b) WE MAY USE THIS CIRCUIT TO SOLVE THE "DRIVEN WAVE EQUATION"

$$\frac{d^2y}{dt^2} + ay(t) = by(t)$$

WHERE a & b ARE POSITIVE KNOWN CONSTANT AND $u(t)$ IS THE "INPUT" OR "DRIVING TERM"




IF GIVEN THAT THE VOLTAGE AT TERMINAL A IS $V_1 = LC \frac{d^2V_1}{dt^2}$, FIND THE NECESSARY INTEGRATIONS BETWEEN R, L/C IN TERMS OF a AND b


THE VOLTAGE AT C IS PROPORTIONAL TO OUR SOLUTION. THAT IS, $V_C = C_1 V_1$. WHAT IS THE PROPORTIONALITY CONSTANT, C_1

2. WE SAY THAT AN IMPEDANCE $Z = R + jX$, IS "INDUCTIVE" WHEN $X > 0$. FOR $X < 0$, Z IS "CAPACITIVE".

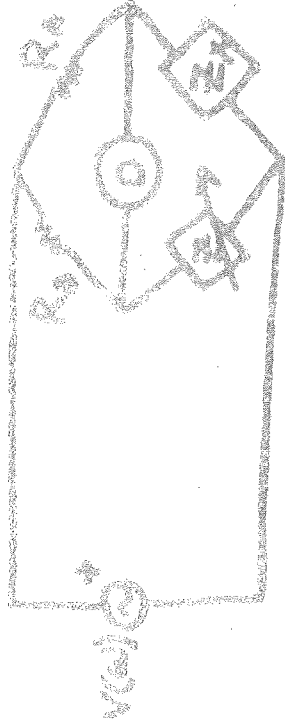(a) FOR THE FOLLOWING IMPEDANCE BRIDGE, SHOW THAT, IN ORDER TO ACHIEVE BALANCE, Z_1 AND Z_2 MUST BOTH EITHER BE INDUCTIVE OR BOTH CAPACITIVE



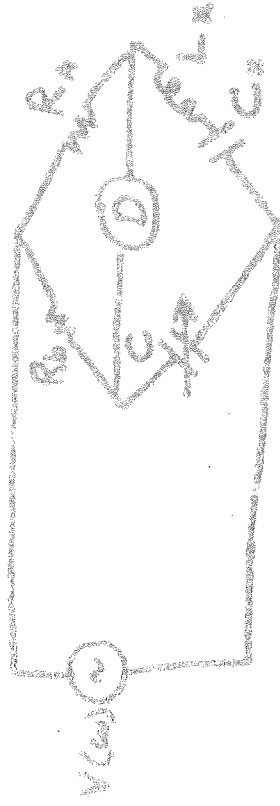(b) FOR WHAT FREQUENCY RANGE WILL THE FOLLOWING BRIDGE BALANCE? [RECALL THE RESONANT FREQUENCY OF L AND C IS $\omega = 1/\sqrt{LC}$]. USE THE RESULTS OF (a)



(c) SHOW THAT, WHEN THE BRIDGE IS BALANCED, THAT L AND C ARE RELATED BY (a)

$$C = \frac{C_x}{1 - \omega^2 L_x C_x} \frac{R_B}{R_A}$$

WHERE ω LIES IN THE RANGE DERIVED IN (b).

(d) EXPLAIN WHY THIS BRIDGE (PARTS b & c) IS A POOR SCHEME FOR MEASURING UNKNOWN L AND C . (AT LEAST TWO REASONS).

3. (a) For a signal, $x(t) = \cos(2\pi f_m t)$, our modulated signal is

$$y(t) = [1 + m \cos(2\pi f_m t)] \cos(2\pi f_c t)$$

where $y(t)$ is our signal, $x(t)$ is our carrier, and m , our carrier modulation, is our modulation. If $m = 1$, the signal is said to be over-modulated. Show, graphically, that over-modulation "distorts" our signal. [NOTE: ON THE ABOVE WAVEFORM, OUR SIGNAL IS THE ENVELOPE.]

(b) A good quality acoustic reproduction should contain frequencies up to 20,000 Hz. How many such separate reproductions can be sent over a channel whose frequency capacity ranges from 0 to 8 MHz?

HOMEWORK #2 SOLUTIONS (by Ahmad)



SUMMING CURRENTS AT V_{in} :

$$1 \int^t (V_1 - V_{in}) dt + C \left[\frac{dV_0}{dt} - \frac{dV_{in}}{dt} \right] = 0$$

(THE INPUT CURRENT TO OP AMP ≈ 0)

THUS: $\frac{d(V_0 - V_{in})}{dt} = -\frac{1}{RC} \int^t (V_1 - V_{in}) dt$


$$\Rightarrow V_0 - V_{in} = -\frac{1}{RC} \int^t \int^t (V_1 - V_{in}) dt dt$$

OR, SINCE $V_{in} \approx \int^t \int^t V_{in} dt dt \approx 0$:

$$V_0(t) = -\frac{1}{RC} \int^t \int^t V_1(t) dt dt$$

WE PERFORM A DOUBLE INTEGRATION

ON THE INPUT, THUS "DOUBLE INTEGRATOR"

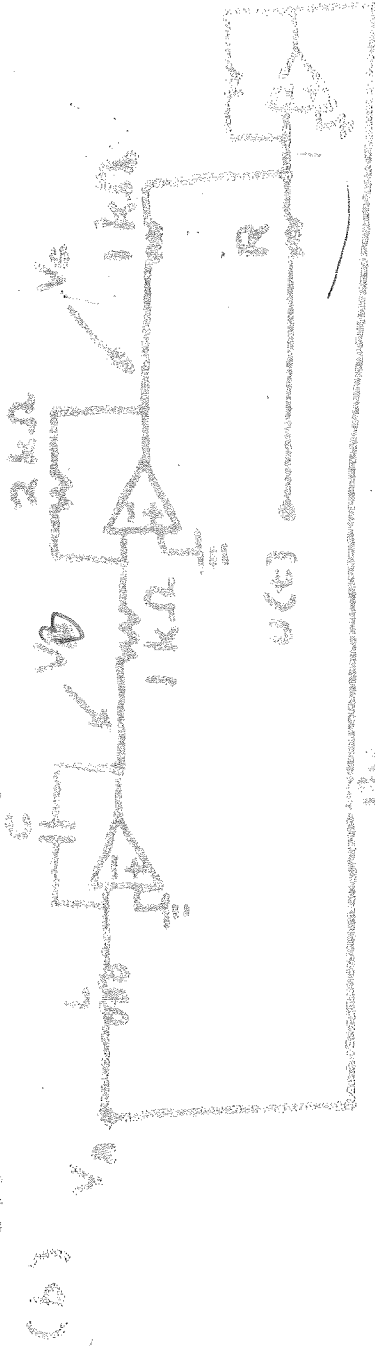

GIVEN $V_A = LC \frac{d^2V}{dt^2}$ WE HAVE FROM (a) THAT

$V_B = -V_1$. THE AMP FOLLOWING HAS A GAIN OF -2 . THUS, $V_C = 2V_1$ (AND C, B). THE OUTPUT OF THE SUMMER IS:

$$\frac{V_B}{k\Omega} = \frac{-V_C}{1k\Omega} - \frac{V_C(t)}{R} \Rightarrow V_0 = -V_C - \frac{1k\Omega}{R} V_C(t)$$

BUT $V_0, V_A = LC \frac{d^2V}{dt^2} = -V_C - \frac{1k\Omega}{R} V_C(t)$

OR $\frac{d^2V}{dt^2} = -\frac{1}{LC} V_C - \frac{1k\Omega}{RLC} V_C(t)$

IN ORDER FOR THIS TO BE OUR DIFF. EQ:

$$c = \frac{1}{LC}, \quad b = \frac{1k\Omega}{RLC} = \frac{a(1k\Omega)}{R}$$

2. (a) WHEN THE CIRCUIT IS BALANCED:

$$Z_x = Z_{R_A/R_B}$$

LET $Z_x = R_x + jX_x$ AND $Z = R + jX$. EQUATING THE
IMAGINARY PARTS:

$$X_x = \frac{R_A}{R_B} X$$

THUS, IF $X > 0$, THEN $X_x > 0$ (i.e., BOTH Z AND
 Z_x ARE INDUCTIVE). IF $X < 0$, THEN $X_x < 0$
(i.e., BOTH Z AND Z_x ARE CAPACITIVE).

(b) FOR THIS CIRCUIT:

$$X_x = \frac{-1}{\omega C} \quad X_x = (\omega L_x - \frac{1}{\omega C_x})$$

SINCE, FROM (a), X_x MUST BE NEGATIVE:

$$\omega L_x - \frac{1}{\omega C_x} < 0$$

$$\omega L < \frac{1}{\omega C_x} \Rightarrow \omega^2 < \frac{1}{L C_x}$$

$\therefore \omega < \frac{1}{\sqrt{L C_x}} = \text{RESONANCE OF } L \& C_x$

(c) AT BALANCE:

$$Z_x = Z_{R_A/R_B}$$

$$j(\omega L_x - \frac{1}{\omega C_x}) = -j \frac{R_A}{R_B} \frac{1}{\omega C}$$


$$\frac{1}{\omega C_x} - \omega L_x = \frac{R_A}{R_B} \frac{1}{\omega C}$$

SOLVING FOR C:

$$C = \frac{C_x}{1 - \omega^2 L_x \frac{R_A}{R_B}}$$

(d) THE VALUES OF L_x & C_x ARE NOT
UNIQUELY DETERMINED AND THE
RESULT IS FREQUENCY DEPENDENT.

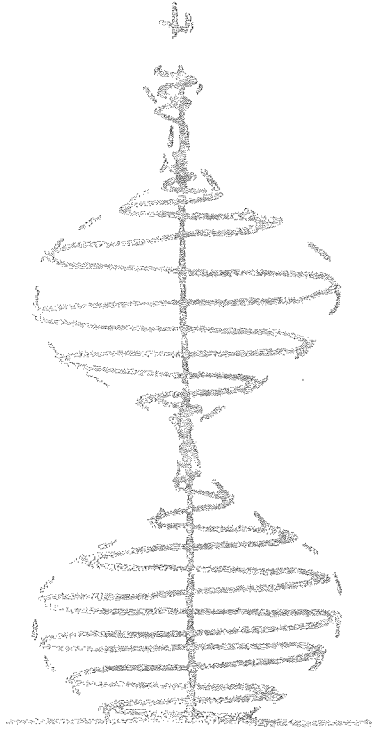3. (a) For $m < 1$, THE MODULATED SIGNAL LOOKS LIKE



FOR $m > 1$:



THE ENVELOPE (OUR SIGNAL) IS DISTORTED

$$(b) N = \frac{8 \times 10^6}{2(2 \times 10^4)} = 2 \times 10^2 = 200 \text{ REPLICATIONS}$$

1. CONSIDER THE FOLLOWING GROUPING OF NUMBERS

- (1) 1, 5, 7, 9, 11, 13, 15
- (2) 3, 6, 7, 10, 11, 14, 15
- (3) 4, 6, 7, 12, 13, 14, 15
- (4) 9, 10, 11, 12, 13, 14, 15

IF ONE PICKS A NUMBER BETWEEN 1 AND 15 AND SPECIFIES WHICH OF THE ABOVE ROWS IT IS CONTAINED IN, THE UNKNOWN NUMBER CAN BE COMPUTED BY ADDING THE FIRST NUMBERS IN EACH ROW. FOR EXAMPLE, THE NUMBER 13 IS IN ROWS (1), (2) AND (3). THE FIRST NUMBERS OF THESE ROWS ARE 1, 4, AND 8 AND $1+4+8=13$.

- (a) EXPLAIN WHY THIS WORKS [HINT: USE BINARY NUMBERS IN YOUR REASONING]
- (b) MAKE A SIMILAR TABLE UP TO AND INCLUDING THE NUMBER 31 [HINT: IT WILL HAVE FIVE ROWS WITH 16 NUMBERS IN EACH ROW. HINT HINT: NOTICE THE PATTERN OF THE ROWS (LEFT TO RIGHT).]

2. A CODE WHICH CAN DETECT AND CORRECT A SINGLE BIT ERROR, CALLED THE "HAMMING" CODE, USES THE ABOVE IDEA. SUPPOSE WE WANTED TO SEND AN ELEVEN BIT CODE: 1110011110. WE BREAK IT UP INTO THE FOLLOWING:

15 14 13 12 11 10 9 8 7 6 5 4 3 2 1
 111101011110111101010101

NOTE THAT, FOR THE 2⁰TH PLACE, WE HAVE PUT P_0 (EX: AT $2^2=4$, WE PUT P_2). THESE P'S ARE PARITY BITS. NOW WE GO TO COLUMN (3) IN PROBLEM 1. WE WANT THE BINS IN THIS ROW TO CONTAIN AN EVEN NUMBER OF 1'S. WE SEE THAT THESE ARE, IN FACT, AN ODD NUMBER (5) ONES IN BINS 15, 13, 11, 9, 7, 5 AND 3. THUS, WE MUST CHOOSE $P_0=1$ SO THAT THE TOTAL NUMBER OF ONES IS EVEN. FOR ROW 1 IN PROBLEM 1, BINS 17, 14, 11, 10, 7, 6, AND 3 CONTAIN AN ODD NUMBER (5) OF 1'S SO WE MUST ALSO MAKE $P_1=1$.

- (a) SHOW THAT $P_2=0$ AND $P_3=1$ SO THAT OUR TOTAL CODE IS 11100111101011.
- (b) PERFORM A HAMMING CODING ON THE ELEVEN BIT WORD 10101010101.

3. AT THE RECEIVING END OF A HAMMING CODE, WE CAN DETECT AND CORRECT A SINGLE BIT ERROR. SUPPOSE WE SENT THE WORD IN PROBLEM 2 AND RECEIVED

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1
1	1	1	0	0	1	1	1	0	1	0	0	1	0	1
													P_2	P_1

(a) GOING THROUGH THE PROCEDURE IN PROBLEM 2, SHOW THAT THIS WORD SHOULD HAVE PARITY BITS $P_0=1, P_1=0, P_2=1, P_3=1$. NOW COMPARE THESE PARITY BITS WITH THOSE RECEIVED $\rightarrow P_0 P_1 P_2 P_3 = 1 0 1 1$ RECEIVED $\rightarrow P_0 P_1 P_2 P_3 = 1 1 0 1$

BY "BITS' DIFFERING WE MEAN 0 WHEN P_0 MATCHES AND 1 WHEN THEY'RE DIFFERENT. NOTE $(0110)_2 = 6$. THUS, OUR ERROR IS IN BIN 6. COMPARING THE ABOVE RECEIVED CODE TO OUR TRANSMITTED CODE (NEXT, NUMB 2, WE SEE THAT THIS IS TRUE. (NEXT, NUMB 2, IN YOUR HAMMING CODE DERIVED IN EX), MAKE AN ERROR IN BIN 13. BE A RECEIVER AND CORRECT YOUR MISTAKE AS WAS DONE

IN PART a OF THIS PROBLEM.
 4. (EXTRA CREDIT) NIM IS AN OLD CHINESE GAME WHERE THREE ROWS OF MATCHSTICKS ARE LAID OUT. ANY NUMBER OF MATCHSTICKS BE IN ANY ROW. TWO PLAYERS ALTERNATE TAKING DURING A TURN, A PLAYER CAN TAKE AS MANY MATCHES HE MUST TAKE AT LEAST ONE MATCHSTICK. THE PLAYER WHO TAKES UP THE LAST MATCHSTICK OR BINARY NUMBERS, WICKLE WINS. BY USING BINARY NUMBERS, WE LEAVE IT OR NOT, YOU CAN ALWAYS WIN. CONSIDER THE FOLLOWING GAME BOARD:

OF THREE ROWS OF MATCHSTICKS:				
	1 1 1 1 1 1	\rightarrow	7 = (111) ₂	
	1 1 1 1	\rightarrow	3 = (011) ₂	
	1 1 1 1	\rightarrow	5 = (101) ₂	
			<hr/>	
			223	← sum (GAME#)

NOTE THAT FOR EACH ROW, WE HAVE CONVERTED THE NUMBER OF MATCHSTICKS TO BASE 2 AND HAVE ADDED THEM (IN BASE 10) TO ARRIVE AT WHAT WE SHALL CALL THE GAME # (NUMBER). IF THE GAME NUMBER CONTAINS ONLY 0'S AND 1'S, IT IS "SAFE" OTHERWISE (IF IT CONTAINS ONE OR MORE 2'S OR 3'S), IT IS UNSAFE. HERE IS THE BASIS FOR ALWAYS WINNING NIM: BY THE GAME RULES, IT IS ALWAYS POSSIBLE TO CHANGE AN UNSAFE NUMBER TO A SAFE NUMBER BUT IS IMPOSSIBLE TO CHANGE A SAFE NUMBER INTO ANOTHER SAFE NUMBER. (THIS IS A VERY NAIRY PROOF WHICH WE WILL NOT GO INTO). THUS, IN PLAYING, THE GAME NUMBER ALTERNATES BETWEEN SAFE AND UNSAFE UNTIL THE WINNING SAFE NUMBER OF 0 IS REACHED.

IN THE GAME BOARD AT THE BOTTOM OF THE PREVIOUS PAGE, THE GAME NUMBER CAN BE MADE SAFE BY TAKING ONE MATCHSTICK FROM THE THIRD ROW. THE NEW GAME NUMBER WILL BE 322.

(a) OBVIOUSLY, IF YOU PLAY NIM WITH ANOTHER PERSON WHO KNOWS HOW TO PLAY, YOU WON'T ALWAYS WIN. IN THIS CASE, NOW, DOES THE INITIAL GAME BOARD AND WHO GOES FIRST DETERMINE WHO WINS?

(b) FOR THE FOLLOWING GAME BOARD, DETERMINE IF THE GAME IS SAFE OR UNSAFE. IF UNSAFE, TAKE A TURN & MAKE IT SAFE

```

(1)  | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
    | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
    | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
    | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
    | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
    (2)  | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
        | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
        | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
        | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
        | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
    
```

(c) PLAY AND WHAT SOMEONE WHO DOESN'T KNOW HOW TO PLAY AT FIRST FIVE TIMES.

[* YOU CAN HOWEVER, MAKE AN UNSAFE # FROM ANOTHER UNSAFE #]

(a) Consider the number $13 \times (1011)_2$. It has 1's in the 2nd, 3rd, and 2nd places, and thus is in the ①, ①, and ③ rows. In short, row ① contains all those binary numbers that have a 1 in the 2nd place.

- (b) ③ 1, 3, 5, 7, 9, 11, 13, 15, 17, 19, 21, 23, 25, 27, 29, 31
① 2, 3, 6, 7, 10, 11, 13, 15, 18, 19, 22, 23, 26, 27, 30, 31
② 4, 5, 6, 7, 12, 13, 14, 15, 20, 21, 22, 23, 28, 29, 30, 31
④ 8, 9, 10, 11, 12, 13, 14, 15, 24, 25, 26, 27, 28, 29, 30, 31
⑤ 16, 17, 18, 19, 20, 21, 22, 23, 24, 25, 26, 27, 28, 29, 30, 31

(c) row ③ in problem (a) has numbers 1, 5, 6, 7, 12, 13, 14, 15. The bits in the respective bits are P2, 1, 1, 0, 1, 1, 1 = (6 ones and P2). The number is even, so let P2 = 0. For ①, we have bits 8 thru 15 which have 5 ones and P2. To make the number of ones even, P2 = 1.

(d) 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1
110101101101101101101101101101101101101101
For ⑤: P2, 1, 0, 0, 1, 1, 1, 1 => P2 = 1 (4 ones)
①: P2, 1, 1, 0, 0, 1, 0, 1 => P2 = 0 (4 ones)
③: P2, 0, 1, 0, 0, 1, 0, 1 => P2 = 1 (4 ones)
④: P2, 1, 0, 1, 0, 1, 0, 1 => P2 = 0 (4 ones)

Our code is true 1010101010101010101

- (e) (a) For ②: P2, 0, 1, 1, 1, 0, 1, 1 => P2 = 1
①: P2, 0, 0, 1, 1, 0, 1, 1 => P2 = 0
③: P2, 1, 0, 1, 0, 1, 1, 1 => P2 = 1
④: P2, 1, 1, 0, 0, 1, 1, 1 => P2 = 1


(b) 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1
110101101101101101101101101101101101101101
From P2 P3 P4 P5 P6 P7

PARTY BITS SHOULD BE

- ①: $P_1, 1, 0, 0, 1, 1, 0, 1 \Rightarrow P_0 = 0$
- ②: $P_1, 1, 1, 0, 0, 1, 0, 1 \Rightarrow P_0 = 0$
- ③: $P_2, 0, 1, 0, 0, 0, 0, 1 \Rightarrow P_2 = 0$
- ④: $P_3, 1, 0, 1, 0, 0, 0, 1 \Rightarrow P_3 = 1$

RECEIVED PARTY BITS ARE: $P_3 P_2 P_1 P_0 = 0101$
 BITS DIFFERING $\Rightarrow 1101$

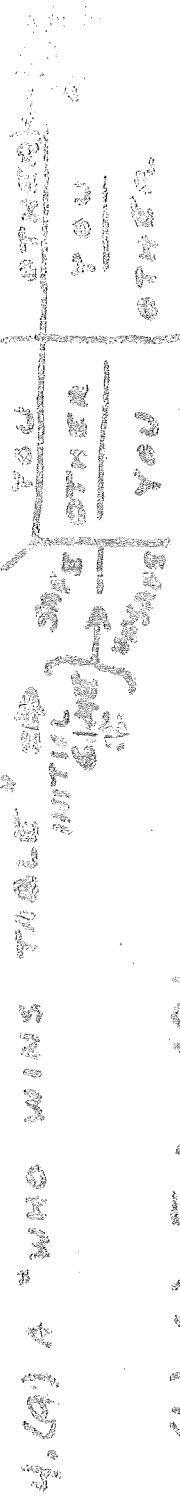THUS, WE HAVE AN ERROR IN BIN $(1101)_2 = 13$.



(b) (1) $\begin{array}{r} 101 \\ 101 \\ \hline 212 \end{array}$

UNSAFE.
 MAY MAKE IS SAFE BY TAKING ALL THE MATCHING BINARY TRIPLE COLUMN BITS ARE: THE FIRST IS USUALLY MORE THAN ONE MAY TO MAKE AN UNSAFE NUMBER SAFE.

(2) $\begin{array}{r} 3 \rightarrow 011 \\ 6 \rightarrow 110 \\ 1 \rightarrow 001 \\ \hline 122 \end{array}$

UNSAFE. MAY TAKE FOUR FROM SECOND ROW TO GIVE:

$\begin{array}{r} 3 \rightarrow 011 \\ 3 \rightarrow 010 \\ 1 \rightarrow 001 \\ \hline 012 \end{array}$

(3) $\begin{array}{r} 2 \rightarrow 010 \\ 6 \rightarrow 110 \\ 4 \rightarrow 100 \\ \hline 230 \end{array}$

UNSAFE

Paint it the Party-Plan year

I shall visit you.
 He will visit you to exhibit mine ignorance before the whole club.
 He tells me more than I can write.
 He lowers my prizes.
 Yes, the I will thru the contents of knowledge.
 I do not let it.
 He tries to / each me.
 He will visit you before me to let you that I will understand that.
 He by / each me / and with / each me.
 My job rate / each me.
 My only enthalpy and enthalpy will follow me all the days of my life.
 And I shall dwell in the College of Engineering forever.
 -J. J. J.

(LAST) MONTELOUKARARY (SEE 204) BOB MARKS (2007)

(1) CONSIDER A BINARY SYMMETRIC CHANNEL OVER WHICH WE SEND AN ELEVEN BIT BINARY SIGNAL. ASSUME $p = q = 0.9$ WHERE $p = P_0[0_0/0_0]$ AND $q = P_0[1_0/1_0]$. ASSUME $p_0 = P_0[0_0] = 1/2$ AND $p_1 = P_1[1_0] = 1/2$.

(a) WHAT IS THE PROBABILITY NO ERROR IS MADE IN TRANSMITTING THIS SIGNAL OF ELEVEN BITS? (b) SUPPOSE WE CODED THE ELEVEN BIT SIGNAL WITH A HAMMING CODE. THIS REQUIRES AN ADDITIONAL FOUR (PARITY) BITS FOR A TOTAL OF FIFTEEN BITS. FIND THE PROBABILITY THAT WE WILL BE ABLE TO EXACTLY RECONSTRUCT THE SIGNAL SENT. SINCE THE HAMMING CODE CAN DETECT AND CORRECT A ONE BIT ERROR, THIS PROBABILITY WILL BE $P_0[\text{NO BIT ERRORS}] + P_1[2 \text{ BIT ERRORS}]$

(c) IN (a), WE TRANSMIT DIRECTLY. IN (b), WE USE A HAMMING CODE WHICH RESULTS IN THE TRANSMISSION OF MORE BITS. IN TERMS OF CORRECTLY DETECTING WHAT WAS SENT, WHICH IS BETTER?


(2) USING TRUTH TABLES, VERIFY DE MOIRG'S THEM.

(a) $AB = \bar{A} + \bar{B}$ (b) $A+B = \bar{A}\bar{B}$

TRUTH TABLES:

A	B	\bar{A}	\bar{B}	$\bar{A} + \bar{B}$	$\bar{A}\bar{B}$
0	0	1	1	1	1
0	1	1	0	1	0
1	0	0	1	1	0
1	1	0	0	0	1

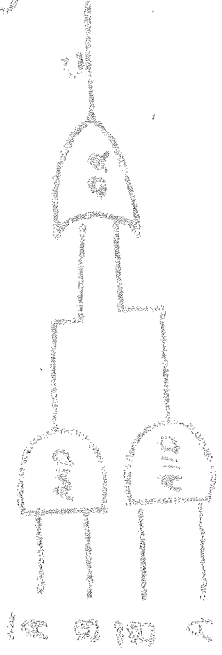(3) SHOW THAT THE FOLLOWING IS THE SAME AS AN EXCLUSIVE OR GATE. THAT IS, $C = A \oplus B$ (HINT: USE TRUTH TABLE)



(4) USING ONLY 'AND' AND 'OR' GATES (INCLUSIVE) DESIGN A CIRCUIT THAT FOLLOWS THE TRUTH TABLE (CAN USE 'NOT' GATES TOO)


TRUTH TABLE:

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

NOTE: YOU MAY USE MULTIPLE AND GATES, OR GATES, AND NOT GATES.

(5) SAME AS (4), BUT TRUTH TABLE IS

A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1

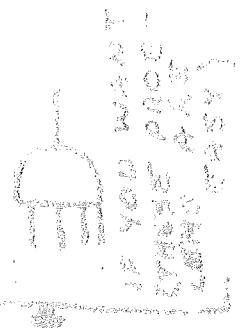

EXTRA CREDIT: SPECIFY THE PERFORMANCE OF A "BUT" GATE. THAT IS, $C = A \text{ BUT } B$.

COMPARISON

(1) (a) For $p=0.9$, the probability all bits will be correctly received is

$$(p)^n = (0.9)^{15} = 0.207133 \text{ OR } \approx 21\%$$

[THE COMPARISON REQUIRES $p_0 = p_1 = 1/2$]

(b) $P[\text{no errors}] = (0.9)^{15} = 20.84\%$

$P[\text{1 bit error}] = P[\text{only first bit is wrong}] + P[\text{only second bit is wrong}] + \dots$

$$= (1-p)p \dots p + p(1-p)p \dots p + p \dots p(1-p)$$

$$= 15 \times (1-p)p^{14}$$

$$= 15(0.1)(0.9)^{14} = 1.5 \times (0.9)^{14}$$

$\approx P[\text{correct detection}] = (0.9)^{15} + 1.5 \times (0.9)^{14}$

(c) HAMMING CODE IS BETTER IN INCREASING SUM PROBABILITY OF CORRECT DETECTION BY OVER 30%

(2) (a) $\overline{AB} = \overline{A} + \overline{B}$

A	B	AB	\overline{AB}	A	B	$\overline{A} + \overline{B}$
0	0	0	1	0	0	1
0	1	0	1	0	1	1
1	0	0	1	1	0	1
1	1	1	0	1	1	0


obviously, $\overline{AB} = \overline{A} + \overline{B}$

(b) $A+B = \overline{A}\overline{B}$

A	B	A+B	$\overline{A}\overline{B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

$$\therefore A+B = \overline{A}\overline{B}$$

(3) using the gates shown:

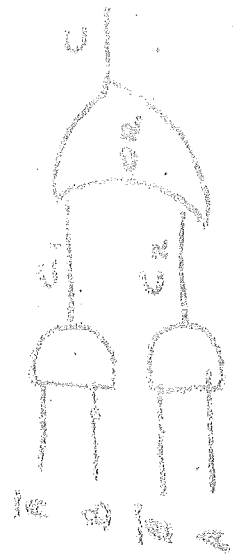

$$C = \overline{A}\overline{B} + AB$$

A	B	$\overline{A}\overline{B}$	AB	$C = \overline{A}\overline{B} + AB$
0	0	1	0	1
0	1	0	0	0
1	0	0	0	0
1	1	0	1	1

THE VALUES OF C ARE THE SAME AS FOR AN EXCLUSIVE OR GATE


(4)

A	B	C
0	0	0
0	1	1
1	0	0
1	1	0

$\Rightarrow C = \bar{A}B$



(5) $D = ABC + \bar{A}\bar{B}C$

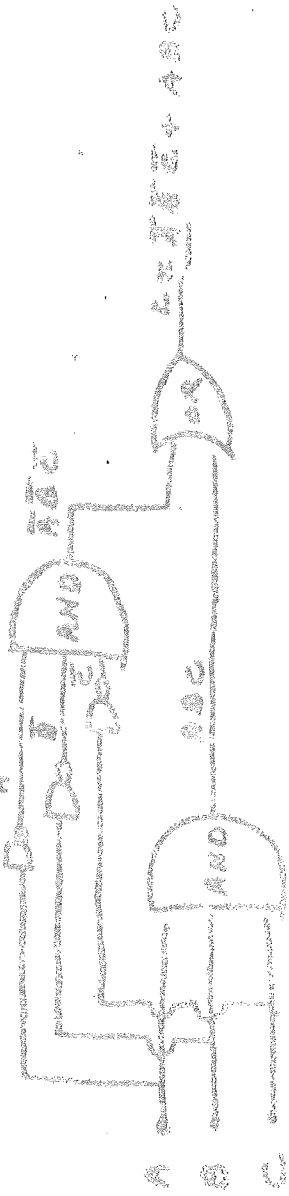

END OF 234 HOMEWORK!

A FINAL WARNING! TWO

DANGER! ALTERNATING CURRENTS ARE DANGEROUS! THEY ARE FIT ONLY FOR POWERING THE ELECTRIC CHAIN. THE ONLY SIMILARITY BETWEEN AN A-C AND D-C LIGHTING SYSTEM IS THAT BOTH START FROM THE SAME COAL PILE.

THOMAS ALVA EDISON (1877 PAMPHLET)

DID YOU KNOW A 100 WATT BULB BURNS OFF 50% MORE LIGHT THAN FOUR 25 WATT BULBS?

BEAR YE ONE ANOTHER'S BURDENS, AND DO FULL THE LAW OF CHRIST.

ALL E.S.

NAME

BEST 1

EE 234

BOB MARKS

2/17/77

INSTRUCTIONS:

- WORK ALL FIVE PROBLEMS. DO YOUR WORK ON THE BLANK PAGES PROVIDED IN THIS BOOKLET. BUDGET YOUR TIME CAREFULLY.
- THE POINT VALUE OF EACH PROBLEM IS GIVEN AT THE TOP RIGHT CORNER OF EACH PROBLEM STATEMENT. THERE ARE 100 POINTS TOTAL
- THIS TEST IS OPEN BOOK, OPEN NOTES, CLOSED NEIGHBOR.



BEST OF LUCK

PROBLEM	SCORE	OUT OF
1		15
2		15
3		25
4		25
5		20
TOTAL		100


"THE THREE FOUNDATIONS OF LEARNING: SEEING MUCH, SUFFERING MUCH, AND STUDYING MUCH"

CATHARINE

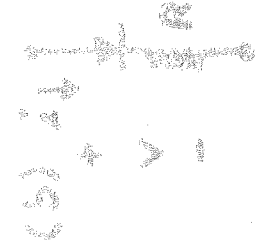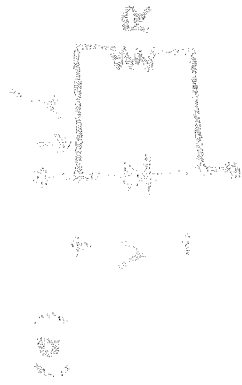(c) Sketch the $v-i$ curves for the following
 resistor-diode combinations. Assume an
 ideal diode. Use i as vertical axis.




ANSWERS:

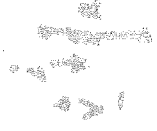

Q.1) FIND THE FOLLOWING FEEDBACK SYSTEM,

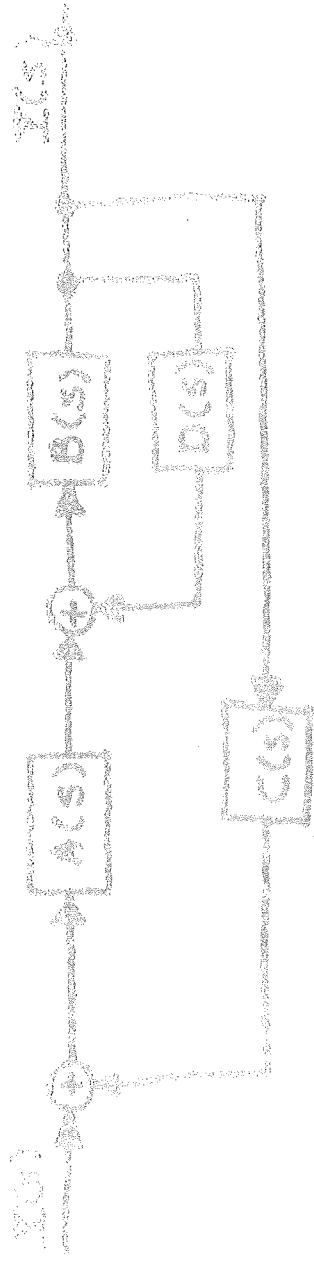(i) THE TRANSFER FUNCTION $T(s) = Y(s)/X(s)$.



HINT: USE THE RESULT OF THE FEEDBACK PROBLEM GIVEN AS HOMEWORK

FOR THE FOLLOWING CIRCUIT

(25 MARKS)



(a) COMPUTE THE TRANSFER FUNCTION $F(s) = \frac{V_o(s)}{V_i(s)}$

(b) COMPUTE $V_o(t)$ GIVEN THAT $V_i(t) = V_m \cos(\omega t)$

[$V_o(t) =$ UNIT STEP FUNCTION]



(c) SKETCH THE FREQUENCY RESPONSE $|T(j\omega)|$

NOTING ITS VALUES AT $\omega = 0$ AND $\omega = \infty$

(d) WHAT TYPE OF FILTER IS THIS?
LO PASS, BANDPASS, OR HIGHPASS?

TIME	LAPLACE	TRANSFORMS
$x(t)$	$X(s)$	$[1/x(t)]$
$x'(t)$	$sX(s)$	$1/s$
e^{-at}	$1/(s+a)$	
$\cos at$	$s/(s^2+a^2)$	

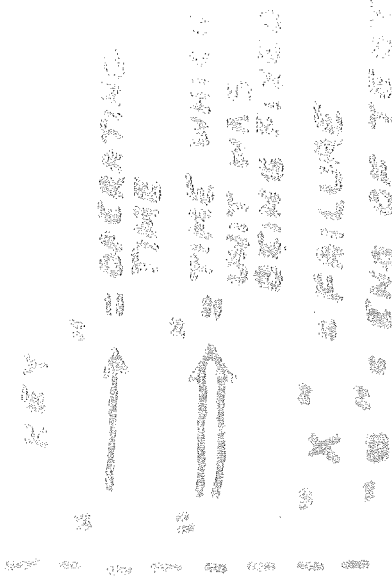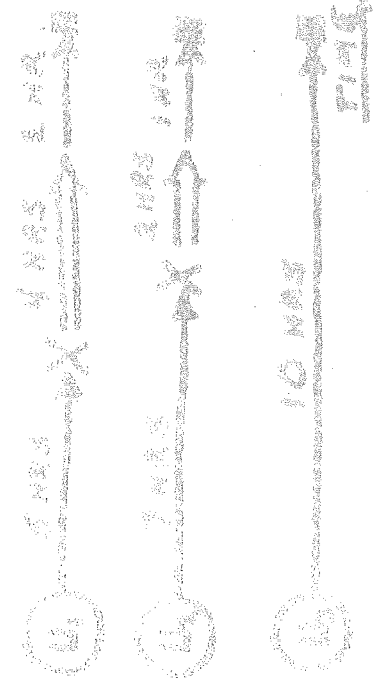(4) TAKE IDENTICAL UNITS AND PLACE ON TEST FOR 10 HOURS EACH. THE RESULTS ARE SHOWN BELOW



COMPUTE THE UNITS' MTBF, MTTR, AND AVAILABILITY AS ESTIMATED BY THIS TEST.

(b) SUPPOSE THE UNITS TESTED IN (a) WERE CONNECTED IN THE SYSTEM SHOWN.



IF THE SYSTEM IS CONSIDERED "OPERABLE" WHEN AT LEAST TWO UNITS

ARE WORKING, COMPUTE THE ESTIMATES OF THE SYSTEM'S MTBF, MTTR, AND AVAILABILITY USING THE TEST DATA GIVEN IN PART (a).

(1) CONTINUED TIME SIGNAL

$$y(t) = \int_{-\infty}^{\infty} x(\tau) e^{-\tau} + 2 \cos^2 \tau d\tau$$

(2) WITHIN THE PERIOD, 2τ , OF THIS PERIODIC WAVEFORM $y(t)$ (UNIT: $\cos^2 \tau = \frac{1}{2} + \frac{1}{2} \cos 2\tau$)

WAVEFORMS WITH PERIODIC SERIES:

$$y(t) = \sum_{n=-\infty}^{\infty} a_n e^{j n \omega_0 t}$$

DETERMINE a_n . (IF YOU ARE CLUELESS, AND


DEFINITION IS ACQUIRED.)

THE SOLUTION IS $\frac{1}{2} [e^{j n \omega_0 t} + e^{-j n \omega_0 t}]$, AND $\frac{1}{2} [e^{j n \omega_0 t} + e^{-j n \omega_0 t}]$

(1) When we try to make a closed circuit, the



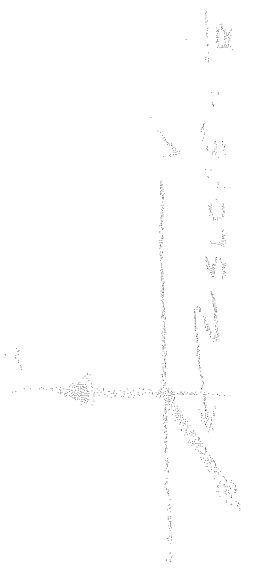
(1) WHEN WE TRY TO MAKE A POSITIVE V , THE DIRECTION IS FORWARD BIASED AND THIS IS SHORT. WHEN THE DIODE IS REVERSE BIASED (AN OPEN CIRCUIT), THE CONDUCTANCE IS LIKE A RESISTOR.




(2) WHEN DIODE IS FORWARD BIASED, THE CONDUCTANCE IS LIKE A RESISTOR. A REVERSE BIASED DIODE IS AN OPEN CIRCUIT.




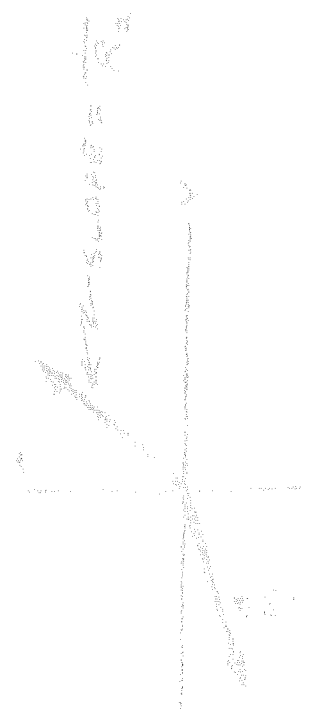
(3) WHEN FORWARD BIASED, THE CONDUCTANCE IS LIKE A RESISTOR. WHEN REVERSE BIASED, THE CONDUCTANCE IS LIKE A RESISTOR.



SLOPE = R

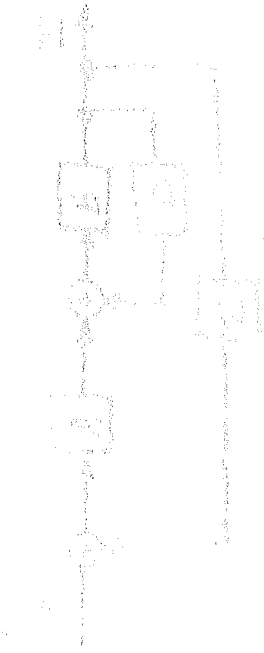

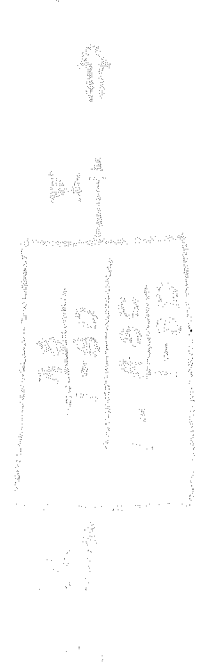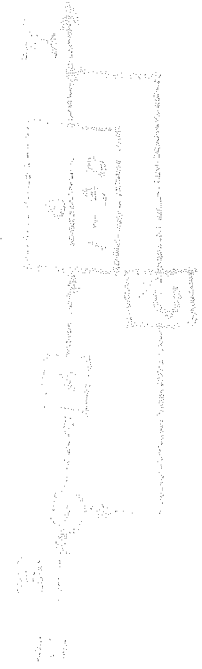Find output voltage $V_2(s)$ using thevenin theorem.



(a)
$$V_2(s) = \frac{V_1(s) \cdot \frac{sL \cdot R}{sL + R}}{R + \frac{sL \cdot R}{sL + R}}$$

(b) or voltage divider
$$V_2(s) = \frac{sL}{sL + R} \cdot \frac{V_1(s) \cdot R}{R + sL + R} = \frac{sL \cdot R \cdot V_1(s)}{s^2 L^2 + 2sLR + R^2}$$

(c)
$$V_2(s) = \frac{V_1(s) \cdot \frac{sL \cdot R}{sL + R}}{R + \frac{sL \cdot R}{sL + R}}$$

(d)
$$V_2(s) = \frac{V_1(s) \cdot \frac{sL \cdot R}{sL + R}}{R + \frac{sL \cdot R}{sL + R}}$$



(e)
$$V_2(s) = \frac{V_1(s) \cdot \frac{sL \cdot R}{sL + R}}{R + \frac{sL \cdot R}{sL + R}}$$

10/10/50

10/10/50 0.1ms 1.2ms 1.2ms

10/10/50 1.2ms 1.2ms

10/10/50

10/10/50 1.2ms 1.2ms

10/10/50 TO GUN DEFINITION OF 1000000
10/10/50 SYSTEM WAS DEFINITIVE ONE FOR
10/10/50 7 MS. I TOOK 2 920000
10/10/50 AGAIN AND RAN FOR 10
10/10/50 TO THE TESTS AND
10/10/50 ONLY ONE 920000

$$10/10/50 = \frac{1.2ms}{1.2ms} = 1$$

$$10/10/50 = \frac{1.2ms}{1.2ms} = 1$$

$$10/10/50 = \frac{1.2ms}{1.2ms} = 1$$

$$10/10/50 = 1.2ms$$

$$10/10/50 = 1.2ms$$

$$10/10/50 = 1.2ms$$

$$10/10/50 = 1.2ms$$


$$10/10/50 = 1.2ms$$

$$10/10/50 = 1$$

$$10/10/50 = 1$$

$$10/10/50 = 1$$

$$10/10/50 = 1$$

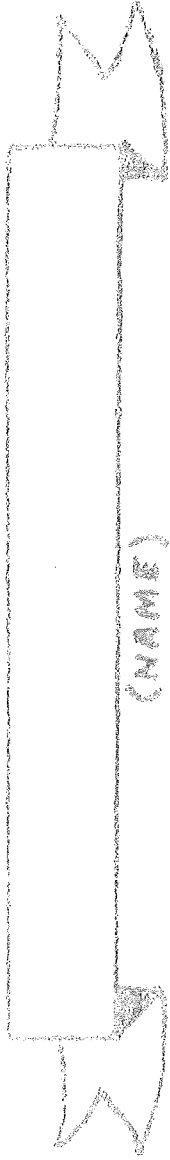

(NAME)

TEST 2

EF 234
808 MARKS
3/31/77

INSTRUCTIONS:

- WORK ALL 5 PROBLEMS. DO YOUR WORK ON THE BLANK PAGES PROVIDED IN THIS BOOKLET. BUDGET YOUR TIME CAREFULLY.
- EACH OF THE 5 PROBLEMS IS WORTH 20PTS FOR A TOTAL OF 100PTS.
- THIS TEST IS OPEN BOOK, OPEN NOTES, AND CLOSED NEIGHBOR.

- BEST OF LUCK -

PROBLEM	SCORE	OUT OF
1		20
2		20
3		20
4		20
5		20
TOTAL		100

"WHEN LIFE HANDS YOU A LEMON...
MAKE LEMONADE"


DALE CARMEINE

20
(1)
TRUE - FALSE: MARK T ON F AFTER EACH OF THE FOLLOWING STATEMENTS. MARKS SUCH AS "T" WILL NOT BE GRADED. DO NOT GUESS. THERE WILL BE A PENALTY FOR WRONG ANSWERS

1. THE OUTPUT IMPEDANCE OF AN IDEAL OP AMP IS THE SAME AS THAT OF A SHORT CIRCUIT WHICH HAS AN IMPEDANCE OF ZERO.....
2. THE EQUIVALENT CIRCUIT FOR A BJT WHICH CONTAINS IDEAL CURRENT SOURCES, IS A GOOD MODEL FOR THE ENTIRE OPERATING RANGE OF THE TRANSISTOR.....
3. THE THREE TERMINALS OF A MOSFET ARE THE COLLECTOR, BASE, AND EMITTER.....
4. ANALOG COMPUTERS ARE LESS EXACT IN GENERAL THAN DIGITAL COMPUTERS.....
5. AN AMPLITUDE MODULATED SINUSOID CONTAINS ONLY TWO FREQUENCIES.....
6. WE MAY SEND, AT MOST, 10 VOICES OR MAXIMUM FREQUENCY 3000 HZ OVER A 60,000 HZ CAPACITY CHANNEL.....
7. SELF BIASING CIRCUITRY REDUCES THE EFFECTS OF TEMPERATURE CHANGE ON BJT TRANSISTOR'S PARAMETERS.....
8. THE UNKNOWN RESISTANCE ON A BALANCED WHEATSTONE BRIDGE IS A FUNCTION OF THE APPLIED VOLTAGE.....
9. SHORTCIRCUITING THE VOLTAGE SUPPLY TO A BALANCED WHEATSTONE BRIDGES WILL HAVE NO EFFECT ON THE VOLTAGES AND CURRENTS WITHIN THE CIRCUIT.....
10. IF WE EXCEED 100% MODULATION IN AM, WE DISTORT OUR SIGNAL.....
11. EE IS GOOD FOR YOU.....




29/

(1) WE WISH TO MODULATE THE SIGNAL:

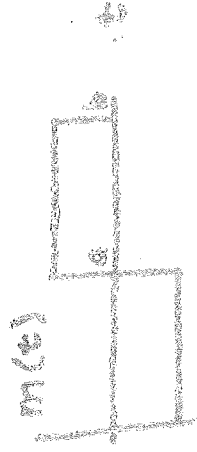


IN EACH OF THE FOLLOWING, STATE WHAT TYPE OF MODULATION IS USED

[CHOICES: AM, FM, PM, PAM, POM, PPM]

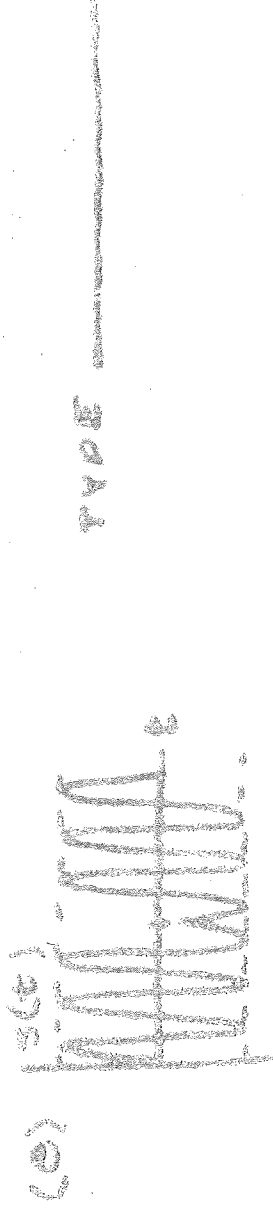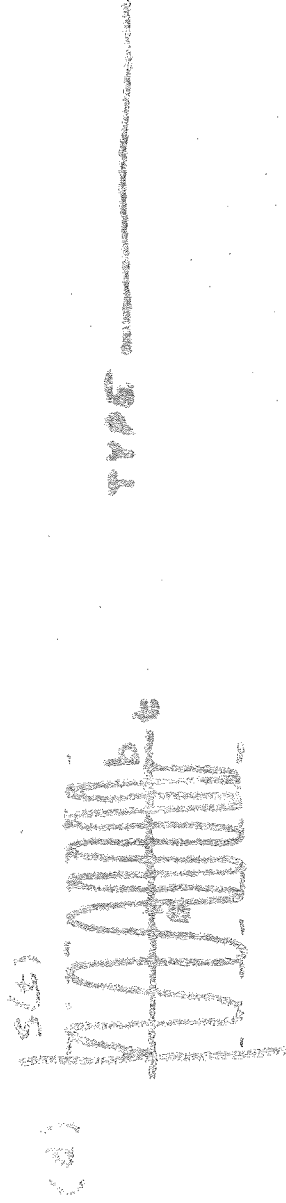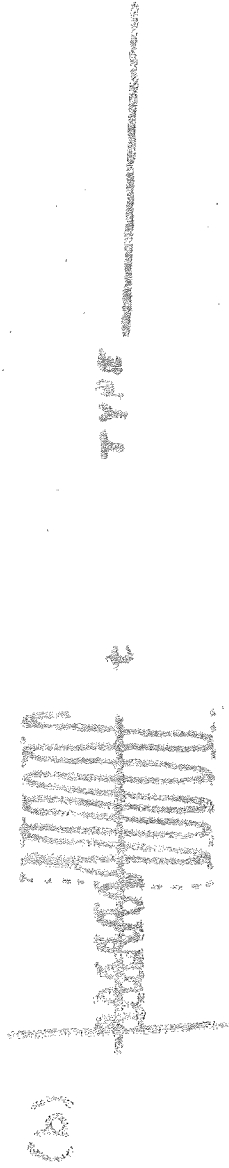


100 (2)

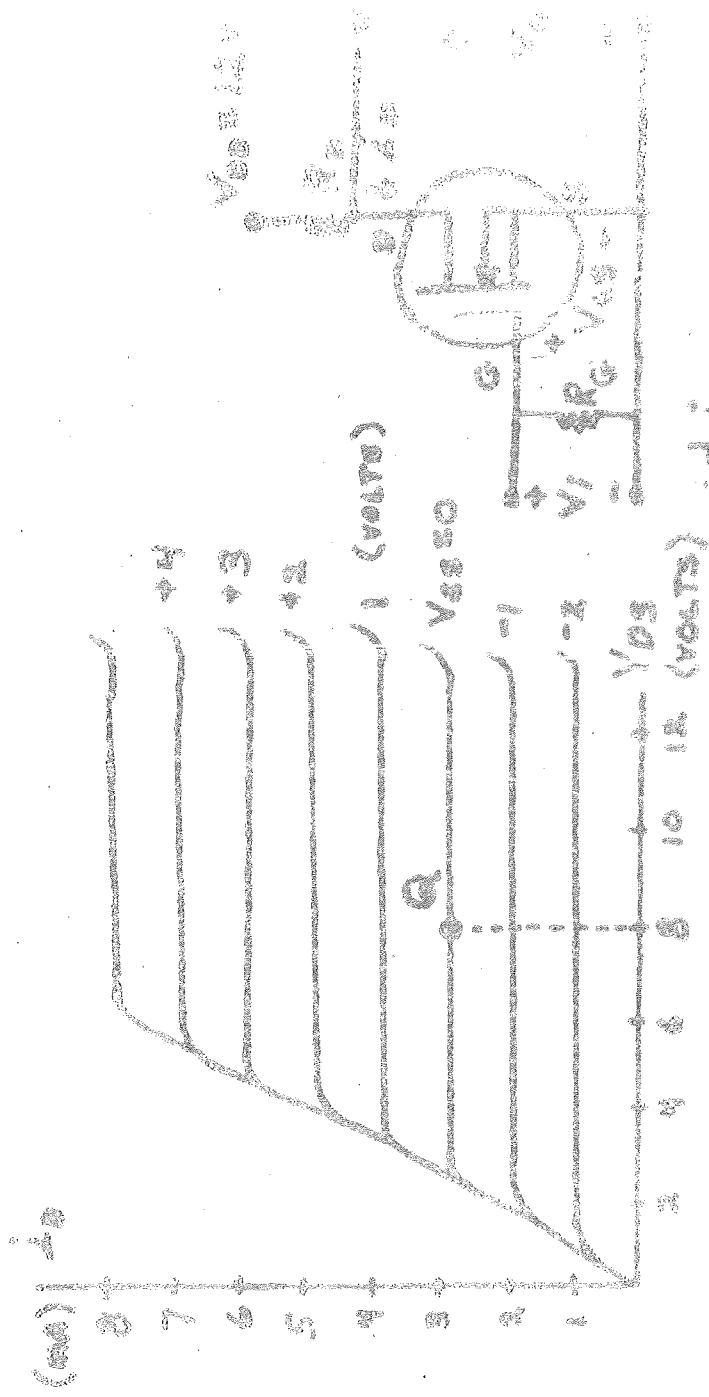

- (a) DETERMINE THE GAIN $G = \frac{dI_D}{dV_{GS}}$ OF THIS DE MOSFET CIRCUIT. [USE ONLY TWO POINTS TO DETERMINE THE LINE ON THE I_D VS. V_{GS} CURVE, CONFINE ANALYSIS TO THE LINEAR PORTION OF THE TRANSISTOR CHARACTERISTICS.]
- (b) SKETCH THE LOAD LINE ON THE ABOVE I_D VS. V_{DS} CURVE USING THE QUIESCENT POINT SHOWN.


(H) 20/

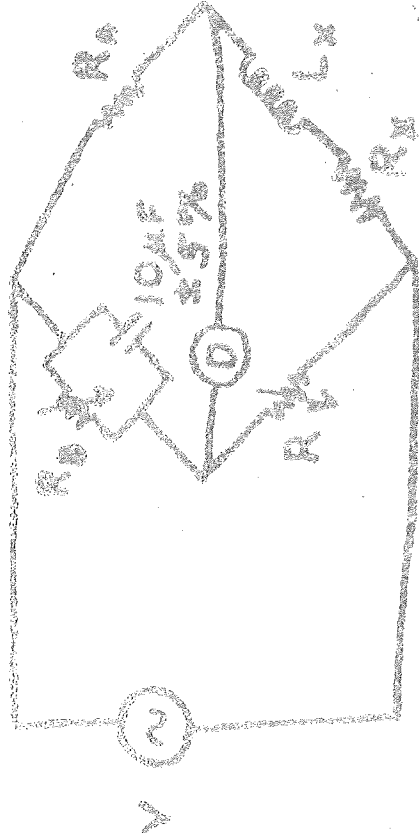

THIS MAXIMUM
BRIDGE BALANCE
WHEN $R_B = 100 \Omega$
 $\pm 2\%$ AND
 $R = 1000 \Omega \pm 2\%$
IF WE KNOW THAT
 R_A LIES SOMEWHERE
BETWEEN 99Ω AND
 101Ω , FIND L_x
AND R_x AND THEIR
CORRESPONDING TOLERANCES IN $\pm (\quad)\%$.
USE THE USUAL APPROXIMATIONS.

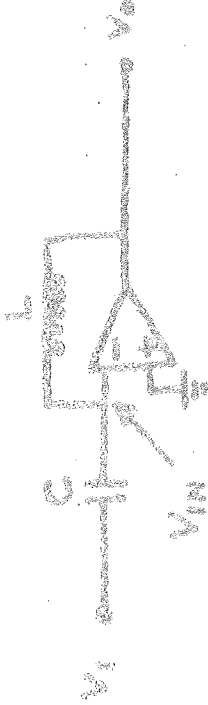(5) 20/

DETERMINE $V_o(t)$ AS A FUNCTION OF $V_i(t)$ IN THE FOLLOWING OP-AMP CIRCUIT:



ASSUME THE OP AMP HAS INFINITE INPUT IMPEDANCE (i.e., ZERO INPUT CURRENT) AND THAT


$$\frac{d^2 V_o}{dt^2} \approx V_{in} \approx 0$$

EE 2034 TEST 02 SOLUTIONS (100 MARKS)

(1) 1V, 2V, 3V, 4V, 5V, 6V, 7V, 8V, 9V, 10V, 11V, 12V


(2) (a) 0.9mA, (b) 0.9mA, (c) 0.9mA, (d) 0.9mA, (e) 0.9mA

(3)

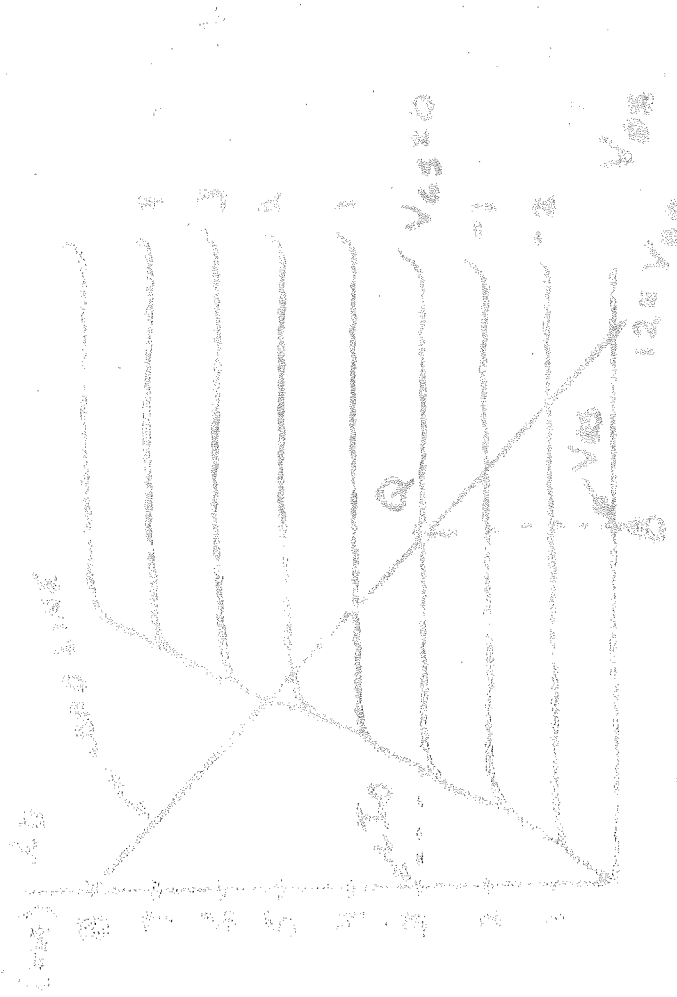

(a) $V_{GS} = 12V$ AND I_Q DETERMINING LOAD LINE

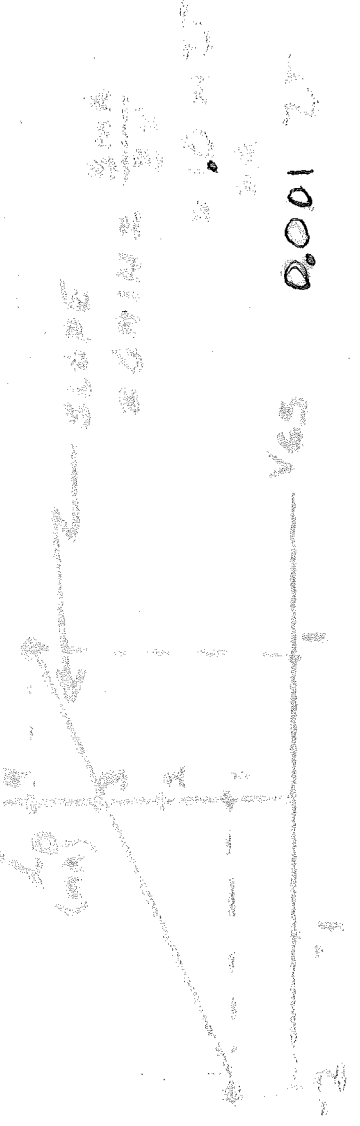(b) (a) $V_{GS} = 1V$, (b) $V_{GS} = 2V$, (c) $V_{GS} = 3V$, (d) $V_{GS} = 4V$, (e) $V_{GS} = 5V$



0.001 2V

(17) $R_A = 400\Omega \ll R_2 = 10^3\Omega \Rightarrow R_2 \approx 1000\Omega$ (10000)
 WE SHOWED IN HOMEWORK #5, PROBLEM 2, THAT

$$R_2 \approx R R_A / R_0 \quad \text{AND} \quad L_x = C_0 R R_A$$

$$R_2 = \frac{(10^3)(10^3)}{(10^2)} = \frac{(1 \pm 0.05)(0.2 \pm 0.02)}{(1 \pm 0.05)}$$


$$= 1000\Omega \quad [(1 \pm 0.02)(1 \pm 0.02)(1 \pm 0.01)]$$

$$= 1000\Omega \quad [(1 \pm 0.05) = 1000\Omega \pm 5\%]$$

$$L_x = (10^{-5})(10^3)(10^3) [(1 \pm 0.05)(1 \pm 0.02)(1 \pm 0.01)]$$

$$= 1 \mu\text{H} \pm 7\%$$

(18)

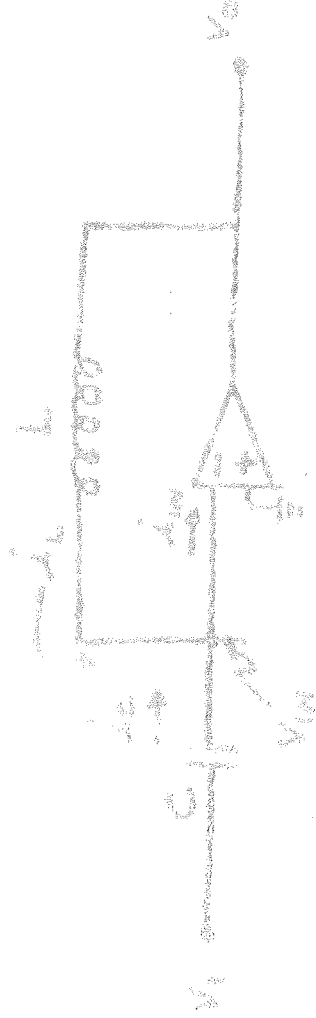

SUMMING CURRENTS AT V_{IN} WITH $i_{IN} = 0$:

$$i_C - i_L = 0 = C \frac{d(V_i - V_{IN})}{dt} + \frac{1}{L} \int^t (V_o - V_{IN}) dt$$

$$\text{OR } \int^t (V_o - V_{IN}) dt = -LC \frac{d(V_i - V_{IN})}{dt}$$

DIFFERENTIATING:

$$V_o - V_{IN} = -LC \left[\frac{d^2 V_i}{dt^2} - \frac{d^2 V_{IN}}{dt^2} \right]$$

ASSUMING $V_{IN} \approx d^2 V_{IN}/dt^2 \approx 0$ GIVES:

$$V_o = -LC \frac{d^2 V_i}{dt^2} \leftarrow \text{"DOUBLE DIFFERENTIATION"}$$

(NAME)

TEST 3

EE 234
BOB MAIR
4/26/77

INSTRUCTIONS

- WORK ALL 5 PROBLEMS. DO YOUR WORK ON THE PAGES IN THIS BOOKLE
- BUDGET YOUR TIME CAREFULLY
- EACH PROBLEM IS WORTH 20 PTS. (TOTAL = 100 POINTS)
- TEST IS OPEN BOOK, OPEN NOTE

-BEST OF LUCK

P. NO	TOTAL	OUT OF	
1		20	
2		20	
3		20	
4		20	
5		20	
TOTAL			100

"WISDOM IS THE
PRINCIPAL THING
THEREFORE, BE
WISDOM AND WE
ALL THY GETTING
GET UNDERSTAN

PROV. 4

(1) YOU RUN A FIELD WITH CIL WELLS A, B, AND C. EACH WELL IS FITTED WITH A SMOKE DETECTOR WHICH PUTS OUT A LOGIC "1" IF THERE WELLS ON FIRE. OTHERWISE, IT'S LOGIC ZERO.

(a) SUPPOSE YOU WANTED A SINGLE RED "LIGHT" TO GO ON WHEN TWO OR MORE OF YOUR WELLS IS ON FIRE. ASSIGNING A LOGIC TO THIS LIGHT BEING ON, COMPUTE THE CORRESPONDING TRUTH TABLE.

(b) FROM YOUR TRUTH TABLE, DESIGN A LOGIC CIRCUIT TO LITE YOUR LITE USING THE SMOKE DETECTOR SIGNAL LEVELS AS INPUTS.

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

(a) Using the "AMERICAN STANDARD CODE FOR INFORMATION EXCHANGE" ON PAGES 5-8 TO 5-11 OF VINE'S BOOK, WRITE THE CODE FOR THE MESSAGE:

I LIKE LEE

AFTER EACH LETTER (OR SPACE), PUT AN EVEN ONES PARITY BIT FOR THAT CODED LETTER (OR SPACE). USE THE SPACES BELOW FOR YOUR CODE:

(b) LET P_e BE THE PROBABILITY OF RECEIVING THE CODE EXACTLY AS IT WAS SENT AND P_{BE} THE PROBABILITY A BIT IS SENT OVER A CHANNEL WITH NO ERROR. WHAT IS P_e FOR $P_{BE} = 0.99$? FOR $P_{BE} = 0.999$? FOR $P_{BE} = 0.9999$?

(c) WHAT MUST P_{BE} BE IF $P_e = 0.95$? (CARRY P_e TO AT LEAST FIVE PLACES).

(3) IN CLASS, WE DEVELOPED THE BOOLEAN LOGIC FOR A TWO AND A THREE WAY LIGHT SWITCH. HERE, WE CONSIDER A FOUR WAY LIGHT SWITCH WITH SWITCHES A, B, C, AND D.


(a) DETERMINE THE TRUTH TABLE FOR THIS SYSTEMS ASSUME AS A STARTING POINT, THE IF $(ABCD) = (0,0,0,0)$, THEN OUR LIGHT IS OFF ($L=0$).

(b) FROM (a), WRITE THE BOOLEAN FUNCTION FOR L (YOU NEED NOT SIMPLY MER IMPLEMENT).

TRUTH TABLE:

A	B	C	D	L
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

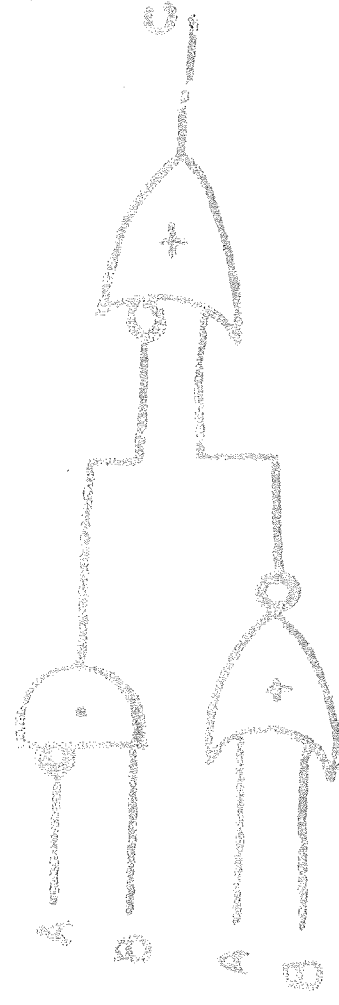(4) CONSIDER THE FOLLOWING LOGIC CIRCUIT.



- (a) COMPUTE THE TRUTH TABLE FOR THE OUTPUT, C, GIVEN THE INPUT A, B
- (b) WRITE THE BOOLEAN FUNCTION F(A, C) IN TERMS OF A AND B.


A	B	C
0	0	—
0	1	—
1	0	—
1	1	—

(5)

WE WISH TO SEND AN ARBITRARY ELEVEN BIT WORD OVER A BINARY SYMMETRIC CHANNEL (P) WITH $p_0 = p_1 = 1/2$. WE WISH TO HAVE A PROBABILITY OF CORRECT DETECTION OF 90%. COMPUTE THE REQUIRED VALUE OF CORRECTLY SENDING AN INDIVIDUAL BIT, P, FOR THE FOLLOWING TWO CASES.

- (a) WE SEND THE ELEVEN BIT MESSAGE DIRECTLY WITH NO CODING.
- (b) WE SEND THE ELEVEN BIT MESSAGE IN A SINGLE BIT ERROR CORRECTION MAPPING CODE. (FOUR PARITY BITS FOR A TOTAL OF FIFTEEN BITS). YOU MAY FIND THE FOLLOWING GRAPH HELPFUL.

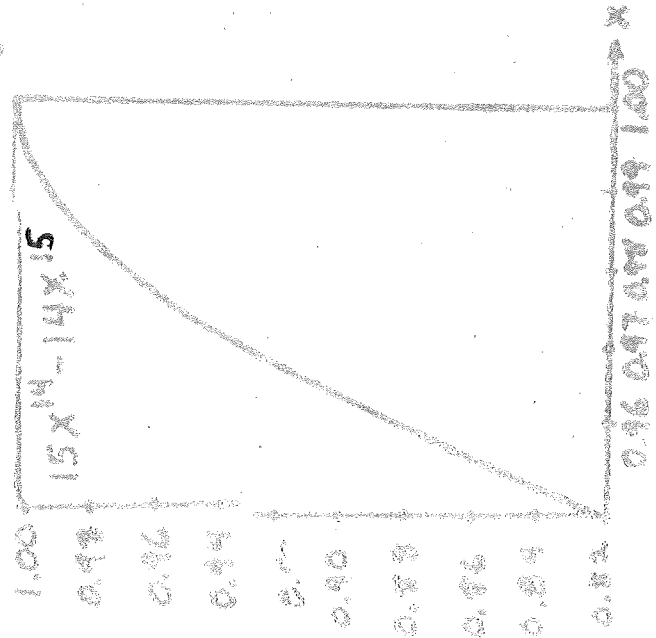(c) WHICH OF THE TWO SCHEMES REQUIRES THE LESS NOISY CHANNEL?




TEST # 3 (SOLUTIONS) by AKKAR

(1) (a) ANY TIME THERE ARE TWO OR MORE "1"'S, IN A, B, & C, WE WANT OUR LIGHT TO GO ON:

A	B	C	$\frac{L}{1}$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

↑
{ TRUTH TABLE

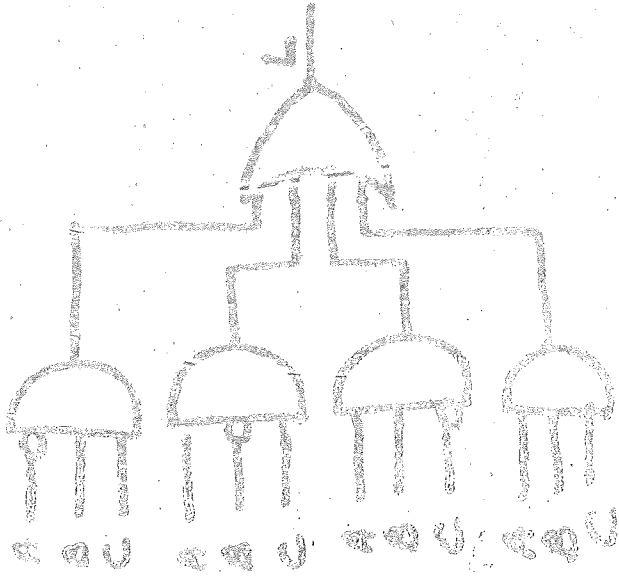(b) FROM OUR TRUTH TABLE:
 $L = \bar{A}BC + A\bar{B}C + AB\bar{C} + ABC$
 THUS, A SCHEME WOULD BE:



NOTE: IN NO WAY IS THIS THE OPTIMAL IMPLEMENTATION. CAN YOU REduce THE NUMBER OF REQUIRED GATES?

QUESTION: What are the probabilities of the following events?

(a) $P(A \cup B) = P(A) + P(B) - P(A \cap B) = 0.3 + 0.4 - 0.1 = 0.6$

(b) $P(A \cap B) = P(A) \cdot P(B) = 0.3 \cdot 0.4 = 0.12$

(c) $P(A \cap B \cap C) = P(A) \cdot P(B) \cdot P(C) = 0.3 \cdot 0.4 \cdot 0.5 = 0.06$

(d) $P(A \cup B \cup C) = P(A) + P(B) + P(C) - P(A \cap B) - P(A \cap C) - P(B \cap C) + P(A \cap B \cap C)$


$= 0.3 + 0.4 + 0.5 - 0.1 - 0.15 - 0.2 + 0.06 = 0.81$

(3) (a)

	A	B	C	L
1	0	0	0	0
2	0	0	1	0
3	0	1	0	0
4	0	1	1	0
5	1	0	0	0
6	1	0	1	0
7	1	1	0	0
8	1	1	1	0

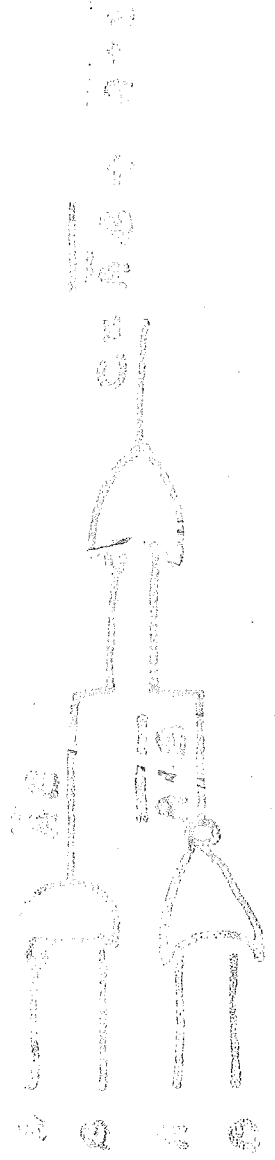(b) $P(A \cup B \cup C) = P(A) + P(B) + P(C) - P(A \cap B) - P(A \cap C) - P(B \cap C) + P(A \cap B \cap C)$

$= 0.3 + 0.4 + 0.5 - 0.1 - 0.15 - 0.2 + 0.06 = 0.81$



(a) $A=0, B=0 \Rightarrow \bar{A}B = 1 \cdot 0 = 0$

$\bar{A} + B = 0 + 0 = 0$

$C = 0 + 0 = 0$

$A=0, B=1 \Rightarrow \bar{A}B = 1 \cdot 1 = 1$

$\bar{A} + B = 0 + 1 = 1$

$C = 1 + 0 = 1$

$A=1, B=0 \Rightarrow \bar{A}B = 0 \cdot 0 = 0$

$\bar{A} + B = 1 + 0 = 1$

$C = 1 + 0 = 1$

$A=1, B=1 \Rightarrow \bar{A}B = 0 \cdot 1 = 0$

$\bar{A} + B = 1 + 1 = 1$

$C = 1 + 0 = 1$

TRUTH TABLE IS

A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

(b) From truth table, $C = \bar{A}B + A + \bar{A}$

or, From truth table, $C = \bar{A}B + 1 + \bar{A}$

$C = \bar{A}B + 1 + \bar{A}$

or $C = \bar{A} + \bar{A}B + A + \bar{A}$

(All the terms are connected here)

(1) $10^2 = 100$ $10^3 = 1000$ $10^4 = 10000$ $10^5 = 100000$
 (2) $10^6 = 1000000$ $10^7 = 10000000$ $10^8 = 100000000$
 (3) $10^9 = 1000000000$ $10^{10} = 10000000000$ $10^{11} = 100000000000$
 (4) $10^{12} = 1000000000000$ $10^{13} = 10000000000000$ $10^{14} = 100000000000000$
 (5) $10^{15} = 1000000000000000$ $10^{16} = 10000000000000000$ $10^{17} = 100000000000000000$
 (6) $10^{18} = 1000000000000000000$ $10^{19} = 10000000000000000000$ $10^{20} = 100000000000000000000$



(1) $10^0 = 1$ $10^1 = 10$ $10^2 = 100$ $10^3 = 1000$ $10^4 = 10000$ $10^5 = 100000$
 (2) $10^6 = 1000000$ $10^7 = 10000000$ $10^8 = 100000000$ $10^9 = 1000000000$ $10^{10} = 10000000000$
 (3) $10^{11} = 100000000000$ $10^{12} = 1000000000000$ $10^{13} = 10000000000000$ $10^{14} = 100000000000000$ $10^{15} = 1000000000000000$
 (4) $10^{16} = 10000000000000000$ $10^{17} = 100000000000000000$ $10^{18} = 1000000000000000000$ $10^{19} = 10000000000000000000$ $10^{20} = 100000000000000000000$

NAME

FORMAT

EE 234
800 MARKS
MAY 6, 1977

INSTRUCTIONS:

- I. THIS TEST IS DIVIDED INTO TWO SECTIONS:
- I. 100 TRUE-FALSE QUESTIONS (200 POINTS)
- II. FOUR PROBLEMS (250 POINTS EACH).
- THE TOTAL # OF POINTS IS 400.

"ALL WISDOM OF THIS WORLD IS FOOLISHNESS WITH GOD"

1 COR 3:19

SOME RELATIONS:

$e^{i\theta} = \cos \theta + j \sin \theta$ EULER

$R(t) = e^{-\lambda t}$ ← CONSTANT FAILURE RATE RELIABILITY

$\frac{1}{(s+a)(s+b)} = \frac{1}{(s+a)(b-a)} + \frac{1}{(s+b)(a-b)}$ ← PARTIAL FRACTIONS

$d[\ln(t)] = 1/t$

$d[e^{-at}] = -a e^{-at}$

Pr[k ERRORS IN n TRIALS EACH WITH PROBABILITY p] = $(1-p)^k p^n$

TRUE		200
FALSE		150
1		50
2		50
3		50
4		50

QUESTIONS

ANSWER EACH OF THE FOLLOWING QUESTIONS WITH A "Y" OR AN "N". ANSWER MARKS, LIKE "Y", WILL NOT BE GRADED. DO NOT GUESS. THERE WILL BE A PENALTY FOR WRONG ANSWERS. IF YOU DO NOT KNOW AN ANSWER, IT IS BEST TO LEAVE THE SPACE BLANK. (NO ANSWER IS "2. WRONG ANSWER IS -3. CORRECT ANSWER IS +3").

1. A DIODE IS A NONLINEAR DEVICE
2. THE VINN'S THEOREM CANNOT BE APPLIED TO
3. DIODE TYPE CIRCUIT ELEMENTS
4. KIRCHHOFF'S VOLTAGE AND CURRENT LAWS CANNOT BE APPLIED TO A DIODE-TYPE CIRCUIT
5. A REVERSE BIASED DIODE CONDUCTS
6. A RECTIFIER CAN TAKE A PERIODIC WAVEFORM OF ZERO AVERAGE VALUE TO GIVE ANOTHER PERIODIC WAVEFORM WITH NON-ZERO AVERAGE POWER
7. RECTIFIERS INCLUDE FULL AND HALF WAVE RECTIFIERS
8. A LOW RIPPLE FACTOR DENOTES A MORE "SQUAWKY" WAVEFORM
9. CAPACITIVE FILTERS ARE USED TO INCREASE THE RCTIVE FACTOR OF A RECTIFIED WAVEFORM
10. THE PFT IS MODULATED BY CONTROLLING THE SIZE OF THE CONDUCTING CHANNEL
11. DEPLETION MEANS DEPLETION EFFECT METAL OXIDE SEMICONDUCTOR FET PERFECT TRANSDUCER
12. IN NORMAL BJT USE, THE EMITTER JUNCTION IS REVERSE BIASED
13. THE LAPLACE TRANSFORM IS A LINEAR OPERATION
14. ALL LINEAR NON-CASUAL SYSTEMS ARE LINEAR
15. ALL KNOWN SYSTEMS ARE CAUSAL IN THE PHYSICAL WORLD
16. A LINEAR TIME-INVARIANT SYSTEM'S TRANSFER FUNCTION IS DEPENDANT ON THE SYSTEM INPUT
17. A BANDLIMITED SIGNAL HAS INFINITE BANDWIDTH
18. A SIGNAL OF BANDWIDTH 200HZ MUST BE SAMPLED AT LEAST AT A RATE OF 400 SAMPLES PER SECOND IF WE WISH TO LOSE NO INFORMATION
19. A FOURIER SERIES DECOMPOSES A PERIODIC WAVEFORM INTO ITS COMPONENT HARMONICS
20. "DTFT" DENOTES "MEDIAN TIME BETWEEN FAILURES"
21. THE TOTAL NUMBER OF A SYSTEM COMPOSED OF A NUMBER OF ELEMENTS CONNECTED IN SERIES IS SIMPLY THE SUM OF THE ELEMENTS' MTBF'S
22. THE RECTIFICATION CURVE IS A PLOT OF FAILURE RATE VS. TIME

24. PROBABILITY IS NOT A PROBABILISTIC MEASURE
25. AVAILABILITY IS THE RATIO BETWEEN MTBF & MTTR.
26. MTTR IS A MEASURE OF MAINTAINABILITY.
27. QUIESCENCE TRANSISTOR THE NO SIGNAL OPERATING POINT OF A TRANSISTOR CIRCUIT.
28. KIRCHHOFF'S LAWS CANNOT BE USED WHEN ANALYZING NONLINEAR TRANSISTOR CIRCUITS.
29. THE PARAMETERS OF A BJT ARE RELATIVELY INSENSITIVE TO AMBIENT TEMPERATURE.
30. BJT'S CAN EITHER BE NPN OR PNP.
31. A CRUDE BJT CAN BE MADE FROM TWO DIODES.
32. WHEATSTONE BRIDGES ARE USED FOR MEASURING RESISTANCES TO HI PRECISION.
33. A MAXWELL BRIDGE IS CAPABLE OF MEASURING TWO UNKNOWN COMPONENTS IN A SINGLE BALANCE OF THE BRIDGE.
34. AN IDEAL OPAMP HAS AN INPUT IMPEDANCE OF ∞
35. ANALOG COMPUTERS IN GENERAL ARE MORE EXACT THAN DIGITAL COMPUTERS.
36. OP AMPS CAN BE USED TO SUM VOLTAGES AND PERFORM VOLTAGE WAVEFORM INTEGRATION.
37. OP AMPS ARE GENERALLY SEMICONDUCTOR DEVICES.
38. AN UNMODULATED AM CARRIER IS SIMPLY A UNIFORM SQUARE WAVE.
39. THE AMPLITUDE ENVELOPE OF A MODULATED FM CARRIER VARIES WITH THE APPLIED SIGNAL.
40. WHEN WE SELECT AN AM OR FM STATION ON OUR RADIOS WE ARE SIMPLY SELECTING THE CARRIER FREQUENCY OF THAT STATION.
41. PAM IS THE DIGITAL EQUIVALENT OF AM.
42. PAM DENOTES "PHASE AMPLITUDE MODULATION".
43. PDM DENOTES "PHASE OR PLATION MODULATION".
44. MULTIPLEXING MEANS THE ACT OF SENDING TWO OR MORE SIGNALS OVER THE SAME CHANNEL.
45. PPM DENOTES "PULSE POSITION MODULATION".
46. ONLY ANALOG SIGNALS CAN BE MULTIPLEXED.
47. AN "A PRIORI" PROBABILITY MEANS A "BEFOREHAND" PROBABILITY.
48. THE PHRASE "I WILL BE HERE ON THUR" CONTAINS AN EXCLUSIVE OR.
49. EVENTS "A" AND "A'" PLACED AS INPUTS TO AN (INCLUSIVE) OR GATE WILL ALWAYS GIVE A LOGIC ZERO AS OUTPUT.

50. WITH A SINUSOID INPUT THE OUTPUT OF A BRIDGE CAPPER CIRCUIT HAS A ZERO D-C VALUE.
51. THE EXISTANCE OF A FEEDBACK CIRCUIT ASSURES THAT THE OUTPUT WILL NOT OSCILLATE.
52. LAPLACE TRANSFORMS CAN BE USED TO REDUCE THE CONVOLUTION OPERATION TO MULTIPLICATION.
53. THE FREQUENCY RESPONSE OF A LINEAR TIME INVARIANT SYSTEM CAN BE OBTAINED FROM THE SYSTEM'S TRANSFER FUNCTION.
54. THE BALANCING POINT OF ALL IMPEDANCE BRIDGES IS INDEPENDENT OF THE SOURCE FREQUENCY.
55. IN ORDER TO DOUBLE THE GAIN OF AN AMP, WE MUST MULTIPLY THE ACTUAL GAIN BY 20.
56. A BALANCED MAXWELL BRIDGE IS INDEPENDENT OF BOTH THE SOURCE FREQUENCY AND AMPLITUDE.
57. ALL IMPEDANCE BRIDGES CAN BE BALANCED.
58. A POSITIVE REACTANCE IS AN INDUCTIVE REACTANCE.
59. A GAIN OF 1 IS THE SAME THING AS A GAIN OF ZERO.
60. AN EIGHT-WAY LIGHT SWITCH CANNOT BE IMPLEMENTED USING ANY KNOWN TECHNIQUE.
61. AN EVEN ONE'S PARITY CODE IS AN ERROR DETECTION CODE AND NOT A CORRECTION CODE.
62. A HAMELING CODE IS AN ERROR CORRECTION CODE.
63. A HALE CODE PERFORMS BINARY ADDITION AND DIVIDES THE RESULT BY TWO (IN BINARY).
64. TWO SWITCHES IN PARALLEL CAN BE USED AS AN AND GATE.
65. IF MASS IS TAKEN AS THE MECHANICAL DUAL OF CAPACITANCE, THEN COMPLIANCE IS THE MECHANICAL DUAL OF INDUCTANCE.
66. IF THE VELOCITY OF A CHARGE MOVING IN A UNIFORM MAGNETIC FIELD IS PARALLEL TO THAT FIELD, THERE IS NO RESULTING FORCE ON THE CHARGE.
67. THERE IS FORCE ON A CURRENT CARRYING WIRE IN A FIELD.
68. HAMMING, THE ORIGINATOR OF THE HAMMING CODE, ALSO ORIGINATED HAMMING EGGS.
69. A BIASED TRANSISTOR IS A BISCOTE TRANSISTOR.
70. AN ELECTROMAGNET PRODUCES A FIELD.
71. THE FORCE RESULTING FROM MOTION OF A CHARGE IN A FIELD IS PERPENDICULAR TO THE PLANE DEFINED BY THE VELOCITY DIRECTION AND THE UNIFORM FIELD DIRECTION.
72. ONE CAN MAKE A MOTOR BY APPROPRIATELY USING THE PROPERTIES OF A MAGNETIC FIELD. SUCH IS NOT THE CASE FOR AN ELECTRIC FIELD.
73. IN RANDOM MOVEMENT, THE RESULTING TORQUE ON THE NEEDLE IS PROPORTIONAL TO THE APPLIED INSTANTANEOUS TORQUE.

- 74. IF WE PASS A SQUARE WAVE OF FREQUENCY 50 KHZ THROUGH A LOW PASS FILTER, THAT ONLY PASSES FREQUENCIES UP TO 45 KHZ, THE OUTPUT WILL BE A SINUSOID RIDING ON A D-C BIAS TERM. A SINUSOID RIDING ON A D-C BIAS TERM IS AT 50 KHZ, WE WILL HAVE ONLY A D-C TERM IN THE OUTPUT. WE WILL HAVE ONLY A D-C TERM IN THE SIGNAL. THE VOLTAGE MAY ONLY BE A SIGNAL IN OUR CODE. NOISE IS TO CHANGE A CODE'S TO BER'S IN OUR CODE. THEN, ACCORDING TO THE SAME LINE THEORY, HIGH FREQUENCIES ARE DISTORTED. ONE WAY TO INCREASE RELIABILITY IS REDUNDANCY. CHANNEL NOISE IS A PRODUCT OF NATURAL TRENDS. EFFECTS OF WHICH CANNOT BE REDUCED BY MAN'S CLEVERNESS.
- 81. ALL TRANSISTOR'S ARE FET'S
- 82. ALL FET'S ARE TRANSISTORS
- 83. AN INDUCTOR IS A DIFFICULT COMPONENT TO INCLUDE ON AN INTEGRATED CIRCUIT CHIP.
- 84. WHEN WE MODEL A MECHANICAL CIRCUIT, LAPLACE TRANSFORMS CANNOT BE USED IN THE SOLUTION.
- 85. A DIODE IS A TIME-VARIANT ELECTRONIC COMPONENT.
- 86. A SWITCH BUFFER IS A TIME-VARIANT SYSTEM.
- 87. A SWITCHING CODE CAN DETECT AN ERROR IN A PARITY BIT.
- 88. LOGIC CIRCUITS CAN BE DESIGNED DIRECTLY FROM THE TRUTH TABLE.
- 89. THE TYPES OF GATES ARE AND AND OR AND NOT.
- 90. WE MAY FABRICATE A NOT GATE BY CONNECTING THE TWO INPUT TERMINALS OF AN AND GATE.
- 91. EXCEEDING 100% MODULATION IN AM CAUSES DISTORTION.
- 92. AN IDEAL DIODE IS EITHER A SHORT OR AN OPEN CIRCUIT.
- 93. ALTHOUGH NECESSARY FOR OPERATION, GATES ON A DC MACHINE DO NOT CONDUCT ANY CURRENT.
- 94. ONE WAY TO INCREASE THE FREQUENCY OF AN INDUCTOR IS TO INCREASE THE NUMBER OF POLES.
- 95. A D/A CONVERTER CONVERTS A DIGITAL INPUT INTO AN AM MODULATED SIGNAL.
- 96. SLIP RINGS ROTATE.
- 97. SPLIT SLIP RINGS CAN ROTATE.
- 98. SPLIT SLIP RINGS STOP ON SPLITTING SLIPS.
- 99. WATER FLOWS ON OIL.
- 100. THIS IS THE LAST TRUE-FALSE QUESTION ON THIS TEST.

EXTRA CREDIT:

101. THE ANSWER TO THIS QUESTION IS FALSE.

PART II

1. A SINGLE PROTOTYPE MACHINE IS PUT ON TEST FOR 1100 HRS. IN THAT TIME, THERE WERE 2 FAILURES. THE TIMES TO REPAIR THE MACHINE FROM THESE TWO FAILURES WERE 60 HRS AND 40 HRS. WE ASSUME THAT, WHILE OPERATING, THE MACHINE EXPERIENCES A CONSTANT FAILURE RATE.

(a) WHAT IS THE MACHINE'S MTBF?

(b) " " " FAILURE RATE?

(c) " " " MTTR?

(d) WHAT IS THE PROBABILITY THE MACHINE WILL HAVE NO FAILURES IN 200 HRS. OF USE?

(e) IN 500 HRS OF USE?

(f) WHAT LENGTH OF TIME COULD WE USE THE MACHINE AND HAVE A 50-50 (i.e. 50%) CHANCE OF IT'S NOT FAILING?

2. AT A RECEIVER, YOU RECEIVE THE FOLLOWING 15 BIT STRING OF BITS WHICH YOU KNOW IS AN 11 BIT NAMING CODE WITH FOUR PARITY BITS. (ASSUME EVEN ONS PARITY).
- (a) HAS THERE BEEN AN ERROR IN TRANSMITTING THE CODE? HOW DO YOU KNOW?
- (b) ASSUMING ONLY ONE BIT ERROR WAS MADE, CORRECT THIS CODE.

RECEIVED CODE:

1 0 1 0 1 1 0 1 1 1 0 1 0 1 0 1


13 14 15 16 17 18 19 20 21 22 23 24 25 26 27

- (c) ASSUME WE RECEIVED THIS CODE OVER A BINARY SYMMETRIC CHANNEL BEARING IN MIND YOUR ANSWER IN (a), WHAT IS THE PROBABILITY OUR CORRECTED CODE IN THE CODE SENT? THAT IS, COMPUTE:

$P_{e|1}$ BIT ERROR / AN ERROR HAS OCCURRED]

ASSUME $p_1 = p_0 = \frac{1}{2}$ AND $p = q = 0.99$.

3.

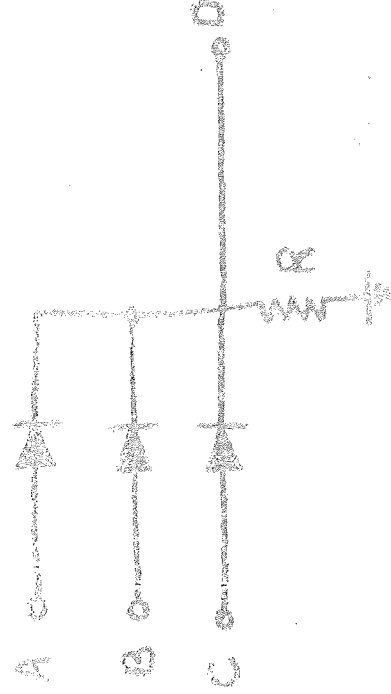


69

IN THE ABOVE LOGIC CIRCUIT, A, B, AND C ARE AT A LOGIC ZERO WHEN THERE IS NO APPLIED VOLTAGE AND AT A LOGIC ONE WHEN 5 VOLTS IS APPLIED. THE SAME IS TRUE FOR THE GATE OUTPUT, D.

(a) IN THE SPACE PROVIDED BELOW, DETERMINE THE TRUTH TABLE FOR THIS GATE.

(b) WHAT TYPE OF LOGIC GATE IS THIS?

A	B	C	D
0	0	0	_____
0	0	1	_____
0	1	0	_____
0	1	1	_____
1	0	0	_____
1	0	1	_____
1	1	0	_____
1	1	1	_____

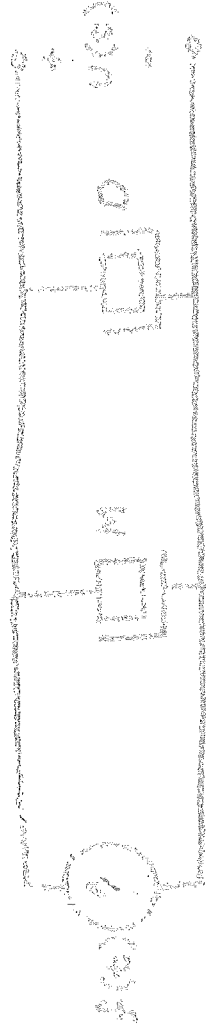

50/ CONSIDER THE ABOVE MECHANICAL CIRCUIT. A MASS M IS SUBJECTED TO AN APPLIED FORCE, $f(t)$. $f(t)$ DENOTES MECHANICAL RESISTANCE. ASSUME $f(t) = f_0 u(t)$ WHERE $u(t)$ IS THE UNIT STEP FUNCTION AND f_0 IS CONSTANT. FURTHER ASSUME ZERO INITIAL CONDITIONS (I.E., THE INITIAL VELOCITY IS ZERO).

(a) FIND THE RELATIONSHIP FOR THE VELOCITY, $U(t)$, (IN TERMS OF M, D , AND f_0) AS A FUNCTION OF TIME.

(b) GIVEN $M = 5 \text{ kg}$, $D = 1 \frac{\text{NT-SEC}}{\text{M}}$, AND $f_0 = 30 \text{ NT}$, HOW LONG WILL IT TAKE THE MASS TO ACHIEVE A VELOCITY OF 10 METERS/SEC? (c) IN TERMS OF f_0 AND M , WHAT IS THE SPEED, $U(t)$, IN STEADY STATE (AFTER A LONG TIME)?

WHAT IS THE STEADY STATE VALUE OF $U(t)$ FOR THE PARAMETERS GIVEN IN (b)? (d) DETERMINE THE REQUIRED FORCE, f_0 , THAT IS REQUIRED TO ACHIEVE A VELOCITY OF 100 METER/SEC IN 10 SECONDS. USE

$$D = 1 \frac{\text{NT-SEC}}{\text{M}} \quad \text{AND} \quad M = 5 \text{ kg.}$$

EE 234 FINAL SOLUTIONS by Marks! (Mar 2017)

1. T	26. T	51. F	76. F
2. T	27. T	52. T	77. F
3. F	28. F	53. T	78. T
4. F	29. F	54. F	79. T
5. T	30. T	55. F	80. F
6. T	31. T	56. T	81. F
7. F	32. T	57. F	82. T
8. F	33. T	58. T	83. T
9. T	34. F	59. T	84. F
10. T	35. F	60. F	85. F
11. F	36. T	61. T	86. T
12. F	37. T	62. T	87. T
13. T	38. F	63. F	88. T
14. T	39. F	64. F	89. F (NG)
15. T	40. T	65. T	90. F
16. F	41. T	66. T	91. T
17. F	42. F	67. T	92. T
18. T	43. F	68. F (NG)	93. F
19. T	44. T	69. F (NG)	94. F
20. F	45. T	70. T	95. F
21. F	46. F	71. T	96. T
22. T	47. T	72. F	97. T
23. T	48. T	73. F	98. F (NG)
24. F	49. T	74. T	99. F
25. F	50. F	75. T	100. F (NG)

(NG) Not Graded - AUTOMATIC CREDIT

$0.5 = e^{-t/500}$
 $\frac{t}{500} = \ln 2$
 $t = 500 \ln 2$
 $= 347 \text{ HRS}$

1. MACHINE ON TIME = 1000 HRS
 MACHINE REPAIR TIME = 100 HRS
 # FAILURES = 2

(a) $\text{MTBF} = \frac{1000 \text{ HRS}}{2 \text{ FAILURES}} = 500 \text{ HRS}$

(b) $\lambda = \frac{1}{\text{MTBF}} = 0.002 \text{ FAILURES/HRS}$

(c) $\text{MTR} = \frac{100}{2} = 50 \text{ HRS}$

(d) $R = e^{-\lambda/\text{MTR}} \Rightarrow R(200) = e^{-\frac{500}{500}} = 0.67 \Rightarrow 67\%$

$R(500) = e^{-500/500} = \frac{1}{e} \Rightarrow 37\%$

2. 1 0 1 0 1 0 1 1 1 0 1 0 1 0 1
 15 14 13 12 11 10 9 8 7 6 5 4 3 2 1
 $P_3 \quad P_2 \quad P_1 \quad P_0$

(1) OUR RECEIVED PARITY BITS ARE
 $P_3 P_2 P_1 P_0 = 1001$
 ASSUMING CORRECT CODE, OUR P_0 PARITY
 BIT SHOULD BE

1 3 5 7 9 11 13 15
 P_0 1 1 1 1 1 1 1
 7 ONES $\Rightarrow P_0 = 1$

FOR P_1 :

3 6 7 10 11 14 15
 P_1 1 0 1 0 1 0 1
 4 ONES $\Rightarrow P_1 = 0$

FOR P_2 :

4 5 6 7 12 13 14 15
 P_2 1 0 1 0 1 0 1
 4 ONES $\Rightarrow P_2 = 0$

FOR P_3 :

9 10 11 12 13 14 15
 P_3 1 0 1 0 1 0 1
 4 ONES $\Rightarrow P_3 = 0$

RECEIVED: $P_3 P_2 P_1 P_0 = 1001$
 SHOULD BE $\frac{1001}{0001}$

DIFFERENCE: 1000 \Rightarrow ERROR IN BIN 8.

(2) THE CODE HAD TO BE WRONG SOMEWHERE BECAUSE THE PARITY BITS DIDN'T CHECK.

$$(c) P[\text{1.5 UNIT ERROR / AN ERROR HAS OCCURRED}] \\ = \frac{P[\text{1.5 UNIT ERROR AND AN ERROR HAS OCCURRED}]}{P[\text{AN ERROR HAS OCCURRED}]}$$

$$P_0[\text{1.5 UNIT ERROR AND AN ERROR}] = \\ = P_0[\text{1.5 UNIT ERROR}] = 15 p^{14} (1-p)$$

$$P_0[\text{AN ERROR HAS OCCURRED}] = 0.1303$$

$$= 1 - P_0[\text{NO ERROR HAS OCCURRED}]$$

$$= 1 - p^{15} = 0.1399$$


$$\text{SO } P_0[\text{1.5 UNIT ER / AN ERROR}] = \frac{0.1303}{0.1399} = 0.9312$$

THIS IS AN OR GATE SINCE ANY TIME A B OR C IS ONE FORWARD BIASED BY THE APPLIED VOLTAGE ALL OF THE VOLTAGE APPEARS ACROSS THE RESISTOR. (SEE P. 366 ON SMITH, FIG. 10.1) SOA TRUTH TABLE IS:

A	B	C	D
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

YOUR LAB GRADE	TOTAL % FIRM	GRADE IN CLASS	YOUR FINAL GRADE IN REGR.

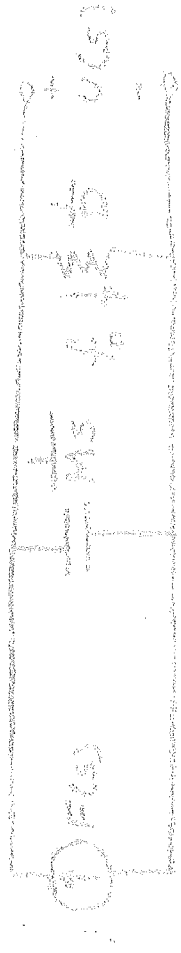4. FIRST, TRANSLATS CIRCUIT INTO LAPLACE DOMAIN



(c) BY CURRENT DIVIDER:

$$f_D = \frac{1/s}{1/s + 1/Ms} F(s) = \frac{D F(s)}{D + Ms}$$

$$\text{AND } U(s) = D \cdot f_D = \frac{D F(s)}{D + Ms}$$

$$\text{NOW } f(t) = f_0 \mu(t) \Rightarrow F(s) = \frac{f_0}{s} \Rightarrow U(s) = \frac{f_0}{s} \Rightarrow U(s) = \frac{f_0}{s} \text{ (STOPS)}$$

$$U(s) = \frac{f_0/s}{s(1/10 + s)} = \frac{f_0}{s} \left(\frac{1/10}{s} - \frac{1/10}{s + 0.1/M} \right) \quad \left(\leftarrow \begin{matrix} \text{PARTIAL} \\ \text{FRACTION} \end{matrix} \right)$$

$$= \frac{f_0}{D} \frac{1}{s} - \frac{f_0}{D} \frac{1}{s + 0.1/M}$$

INVERSE LAPLACING:

$$u(t) = \frac{f_0}{D} \mu(t) - \frac{f_0}{D} e^{-t/10} \mu(t)$$

$$= \frac{f_0}{D} (1 - e^{-t/10}) \mu(t)$$

$$(b) 10 = \frac{30}{1} (1 - e^{-t/30})$$

$$e^{-t/30} = 2/3 \Rightarrow t = 30 \ln \frac{3}{2} = 12.16$$

$$(c) u(t) = \frac{f_0}{D} (1 - e^{-t/40}) \mu(t)$$

$$\Rightarrow u(\infty) = f_0/D = \frac{30}{1} = 30 \text{ m/sec}$$

$$(d) u = \frac{f_0}{D} (1 - e^{-tD/M})$$


$$\Rightarrow f_0 = \frac{u D}{1 - e^{-tD/M}} = \frac{(100)(1)}{1 - e^{-10/10}}$$

$$= 352.8 \text{ NEWTONS}$$


marks

Frequency Response Time Constant and Fourier Series.

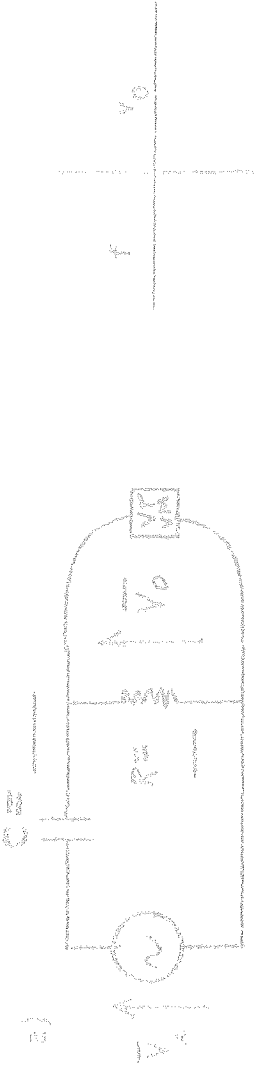
1. Frequency response. For the circuit shown, measure V_o using a c.r.t. oscilloscope. Input signal set at 2 volts, and vary the frequency from 20 Hz to 3 kHz. Be sure to include the half power point (cut-off frequency) as one of the measurements.



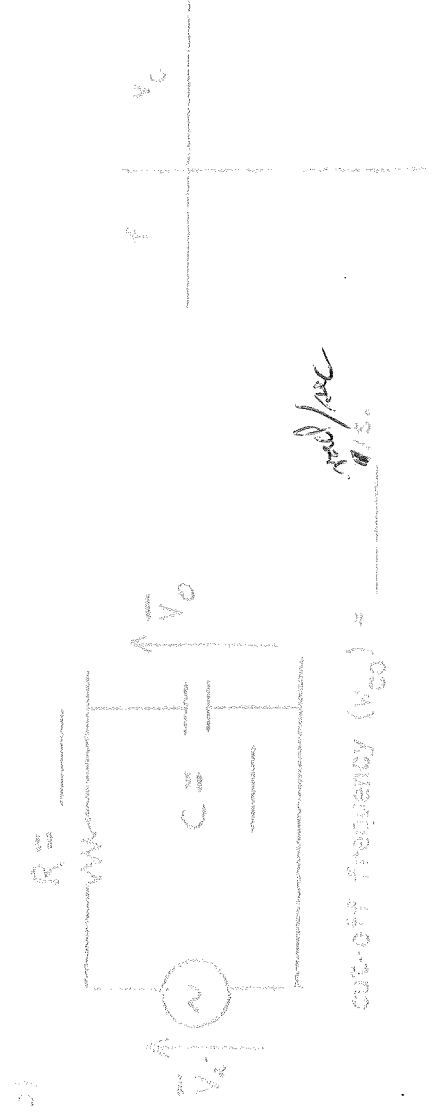cut-off frequency (ω_{CO}) = $\frac{V_o}{V_i}$




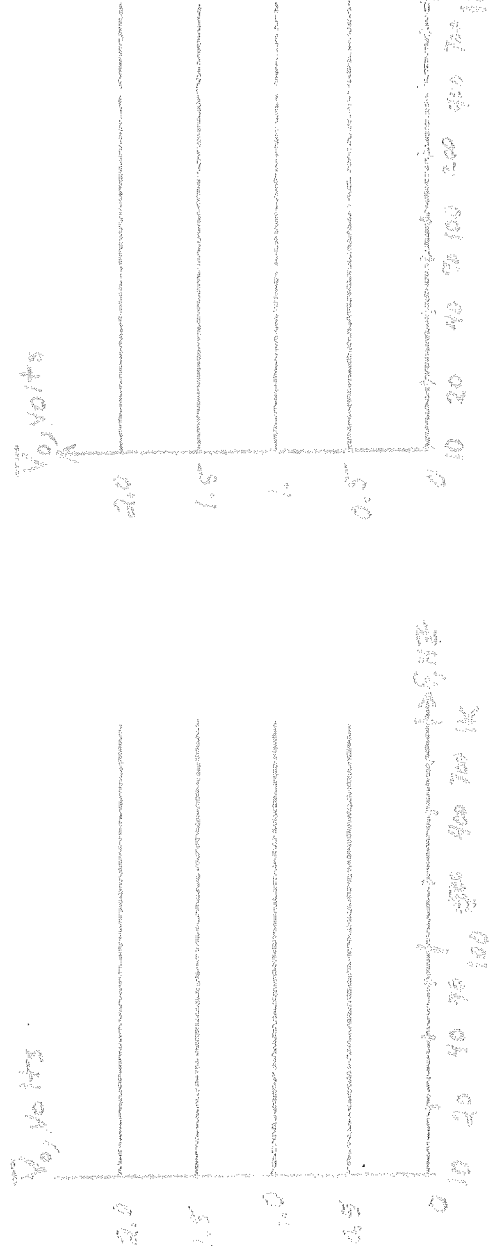cut-off frequency (ω_{CO}) = $\frac{V_o}{V_i}$



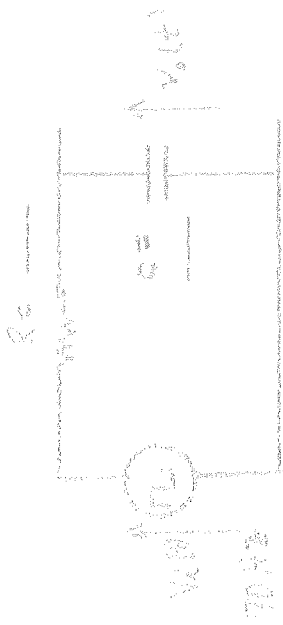2) RC circuit


Connect a square wave signal with the frequency 100 Hz and amplitude 10 V to the input of an RC circuit. Record the output voltage $V_o(t)$ and compare it with a 100 Hz square wave. Then switch the horizontal display axis from Normal to Trig. Record the waveforms below and calculate the time constant.




Time constant (τ_c) =

$\tau_c =$

τ_c (from part 1(a)) =

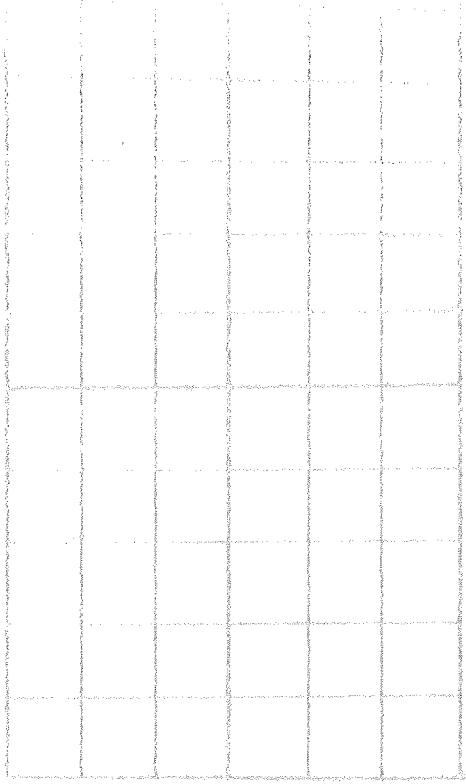

3) Fourier Series

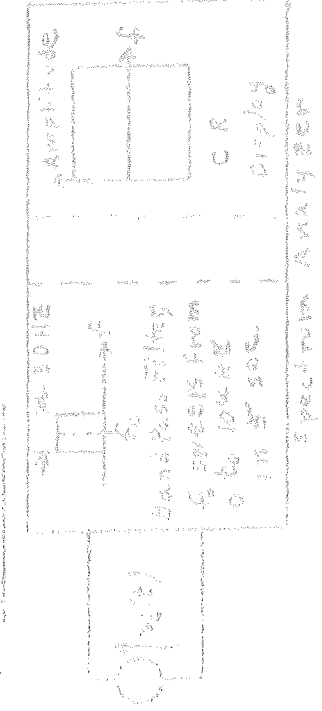

A 1 kHz square wave signal is applied to the input of an HP 35301 Spectrum Analyzer, which displays the harmonics of the signal vs. frequency.

Record the amplitude and frequency of each harmonic. Repeat for the triangular and sinusoidal waves.

Wave

	amplitude						
square							

triangular

	amplitude						
triangular							

sinusoidal

	amplitude						
sinusoidal							

Marks

Q. No. 13 of 3
Question 1 (100%) and 100% Satisfaction



Q. Write a short experiment to measure the current and voltage gain of a common emitter and the voltage gain of a JFET amplifier. Use the following data to calculate the gain.

Table 1: Common emitter JFET

Table 2: JFET amplifier



Table 3: JFET amplifier

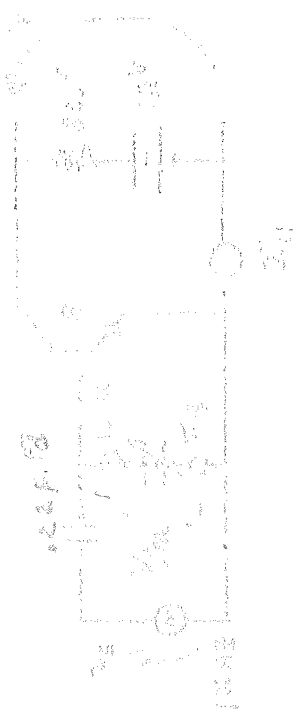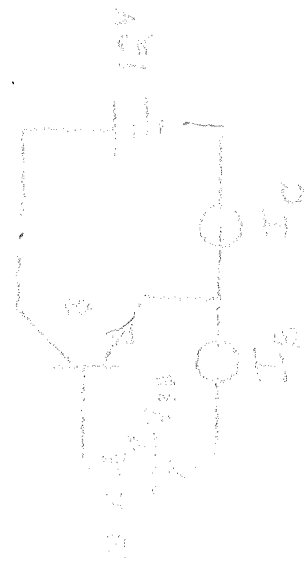

(1)

(2)

Q. Write the circuit of Fig. 10.1 and find the following data:

- 1. The current gain of the JFET amplifier.
- 2. The voltage gain of the JFET amplifier.
- 3. The current gain of the JFET amplifier.
- 4. The voltage gain of the JFET amplifier.

Q. Write the circuit



1. Connect the above circuit with the following values: $V_S = 0$, $R_D = 0$. Measure I_D for each of the following values of V_{GS} (volts): 0, 0.5, 1, 0.
2. Set V_{GS} to 2 volts and R_D to 3 k ohms. Connect a CRO to the output and gradually increase V_S until V_D appears distorted. Reduce the input until distortion is eliminated. Measure V_D and V_{I_n} (peak to peak) with the CRO.

Report

- Part A (1). a) Calculate the d.c. beta (current gain) for $I_g = 0.2$ ma.
 b) Calculate the a.c. current gain (a.c. beta) as follows:

$$\beta = \frac{\Delta I_C}{\Delta I_B} \quad (V_{CE} \text{ constant}).$$

Use the .2 to .4 change for ΔI_B .

A (2). Calculate the voltage gain.

- B (1). The amount or control that the gate voltage has over the drain current is measured by the change in I_D per volt change in V_{GS} . This is called g_m (mhos) and is expressed as

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}} \quad (\text{constant } V_{DS}).$$

Calculate g_m using data for V_{GS} change from 0.5 to 1 volt.

B (2). Calculate the voltage gain.

Marks

EE 234 (4)

Recording Instruments

The purpose of the laboratory is to demonstrate:

1. The basic ideas of operation of the most commonly used recording instruments,
2. Ways to calibrate recording instruments,
3. Frequency limitations of instruments,
4. Sensitivity of the instruments and noise effects at high sensitivity positions of the instruments.

Equipment:

1. Strip chart recording
2. X-Y plotter
3. Function generator
4. D.C. Power Supply

Lab Procedure

A. X-Y plotter

Connect the function generation (sine wave) to the X-Y plotter. Set the function generator frequency to 0.1 Hz, and the plotter sensitivity to 1 volt/division. Increase the generator output until the recorder output produces 5 inches of deflection (peak to peak).

1. Keep the generator voltage constant (use a CRO or a digital voltmeter to measure it). Plot a curve of deflection vs. frequency (frequency response curve), using frequencies of 0.1, 1, 3, 4, and 5 Hz, or until the half power point is found.
2. Replace the generator with d.c. source. Increase the d.c. voltage to get 1 inch of deflection. Calibrate the recorder. (Note that this is a d.c. amplifier). Use this reading for calculating sensitivity.
3. Remove the source from the input to the plotter. Set the sensitivity to maximum. Touch the input terminals with the fingers. Note the results.
4. Set the function generator to produce a ramp at .1 Hz. Use the plotter to get a graph of this voltage vs. time. Use a 1 V/division sensitivity setting.
5. Repeat for triangle and square wave.

Strip Chart Recorder

1. Set the input of the recorder to the 5 volt range. Connect the function generator to the recorder and set the generator amplitude to produce a peak-to-peak deflection of 3 inches. Set the chart speed to 3 inches/minute. Note the type of marking pen used. Does it differ from the X-Y plotter pen?
2. Repeat steps 1 through 5 of part A, for the strip chart recorder.

Project:

1. Describe a galvanometer type recorder.
2. For the X-Y plotter, describe the mechanism and associated circuits used to move the pen in the X direction. What is the maximum speed that the pen will move?
3. Plot a curve of maximum deflection vs. frequency for the X-Y plotter and strip-chart recorder.
4. Describe a capillary ink writing system and a heated stylus system.
5. Define sensitivity and calculate it for the strip-chart recorder and X-Y plotter.

References:

Principles of Modern Instrumentation - Spitzer, Howarth
Guide to Electronic Measurements and Laboratory - Stanley Wolf
Practical Measurements and Instrumentation - Oliver and Page

Marka

741 op-amp

741 op-amp

These experiments will provide an introduction to integrated circuit operational amplifiers (IC op-amps). Today op-amps are used in a wide range of analog signal processing including audio amplification, wave shaping, servo and process control, instrumentation and also in many non-linear applications such as comparators, analog to digital and digital to analog converters and non-linear function operators. We will be concerned with the use of an op-amp as an amplifier, a summer, and an inverter.

In this experiment you will be using type 741 op-amps. They have a gain of about 200,000 open circuited and a bandwidth of about 1 MHz. For unity gain. The 741 is an integrated circuit, meaning that the op-amp is implemented by transistors, resistors, diodes or deposited on a single chip of silicon using chemical (in this instance it is silicon).


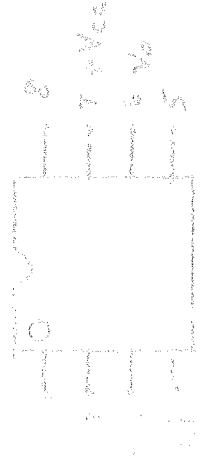


Fig. 1.1 Pinout (741 pin)

The 741 has two inputs: an inverting input and a non-inverting input.

Power Supplies

In order to achieve the ability to produce both positive and negative voltages the op-amp requires both +V_{cc} and -V_{cc} supplies. The 741 will operate on supply voltages of from 10V to 22V. It will be able for our work. The two power supplies are connected in series and need not be disconnected (though they should be disconnected if you are changing circuits) during the experiment. The power connections will not be shown on subsequent diagrams.

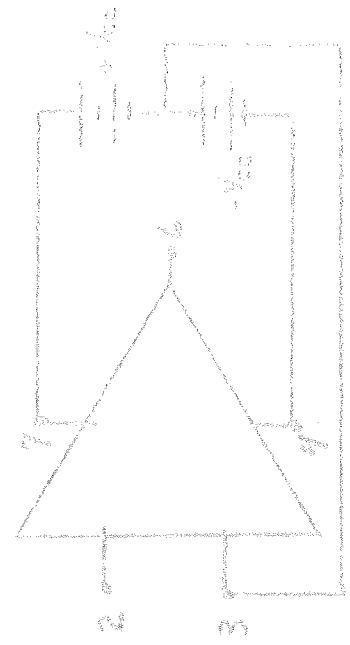

Scope Triggering


No observe the inversion of the input signal by the op-amp it will be necessary (on a one channel scope) to synchronize the scope trigger from some reference - usually the output of the signal generator. This is done by connecting the scope trigger input to the ungrounded side of the signal generator and putting the scope trigger source control on ext + or - and the trigger coupling control on AC or DC - and then adjusting the trigger level control. The lab instructor will review this with the class before beginning the experiment.

If a two channel scope is available, connect the amplifier input to one channel, and the output to the other, and observe the inversion.

Amplifiers

A. Inverting Amplifier

Connect the op-amp as shown below:

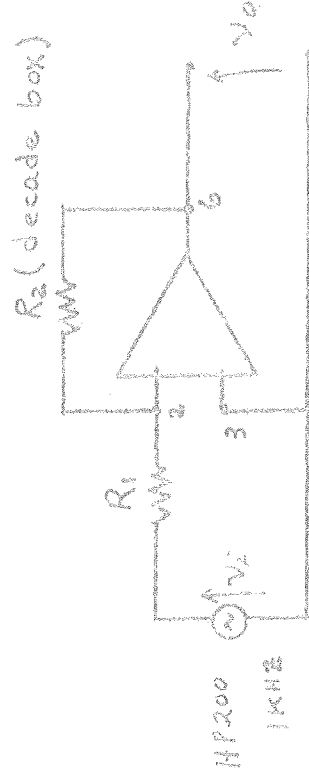

a) Use 5K ohms for R_1 , and set R_2 to give theoretical gains of 10, 20, 40 and 80. Set the input signal to give about 12 volts peak-to-peak for v_o . Adjust the input to eliminate distortion. Measure the gain in each case, using the CRO as a voltmeter.

Q1. How does the measured gain compare with the theoretical gain?
b) With the x80 theoretical gain setting, increase the signal input until you observe clipping on both the upper and lower portions of the output. Measure the voltage difference between the upper and lower clipping points on the output. The clipping is caused by the op-amp reaching its maximum and minimum output voltages (the saturation voltages), which are determined by the power supply voltages. A gain of x100 does not mean that the output will be 100 times the input


1) Now, reduce the amplitude of v_1 until the saturation level is 0.

2) $R_{in} = 100$ and $v_{in} = 1$ in our op-amp would not give 100x out, rather,

(1 sec - because it inverts).

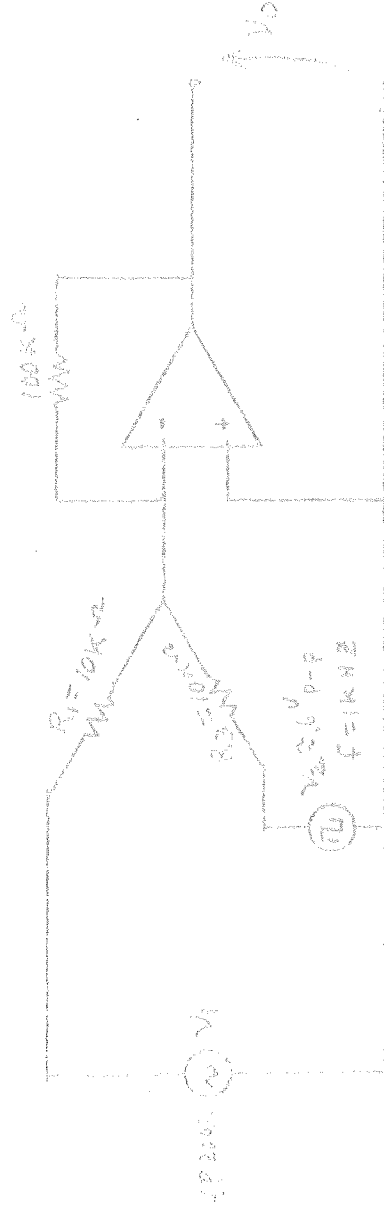3) Sumner

With the op-amp connected as a x10 amplifier ($R_1 = 10K$, $R_2 = 100K$) connect v_1 to the - input terminal (also known as the "summing point") and connect the output of the square wave generator to it as shown.




Adjust the square wave generator so v_2 is 0.6 V p to p. Observe v_1 with the scope synched to the square wave and sketch the waveform. Now connect the H-P oscillator, set its freq. to 4kHz and slowly increase its amplitude to about 1/2 the amplitude of v_2 and sketch v_1 . Slowly change the frequency of v_1 until a steady pattern results in v_0 .

4) Sketch the output with both generators connected. Is it the sum of the two inputs?

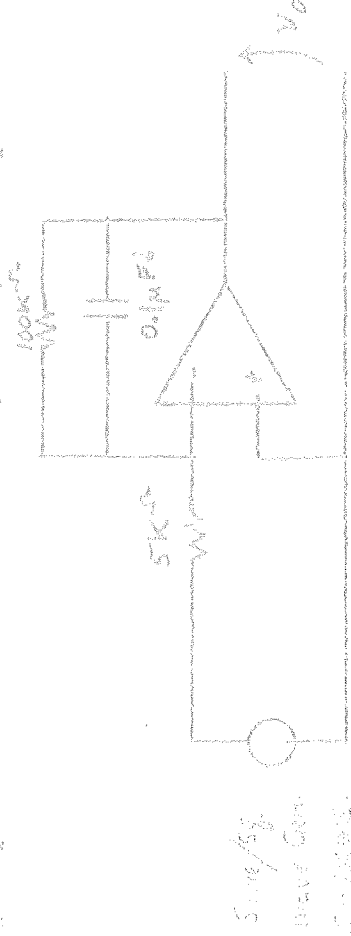5) Integrator

For integration a capacitor is added in the feedback loop, as shown below. The 100K resistor is present for d.c. stabilization of the op-amp and is not considered, here, as a part of the feedback loop.



- 1) Construct the circuit as shown. See the generator for a square wave output, $f = 1\text{kHz}$, $V_{in} = 5\text{V}$, $p = 50\%$. Observe the output.
- 2) Sketch output waveform - what sort of wave is this? Is it the integral of the input? Explain?
- 3) Switch the generator to sine wave output, increase the output maximum. Observe the output V_o . Use oscilloscope for the output. What output does the integrator produce if the input is a sine wave? Did this circuit really integrate? Explain.

The first part of the report is a general introduction to the subject of the study. It discusses the importance of the problem and the objectives of the research. The second part is a literature review, which examines the work of other researchers in the field. This is followed by a description of the experimental method used in the study. The results of the experiment are then presented, and a discussion is given of the implications of the findings. Finally, a conclusion is drawn from the study, and suggestions are made for further research.

The first part of the report is a general introduction to the subject of the study. It discusses the importance of the problem and the objectives of the research. The second part is a literature review, which examines the work of other researchers in the field. This is followed by a description of the experimental method used in the study. The results of the experiment are then presented, and a discussion is given of the implications of the findings. Finally, a conclusion is drawn from the study, and suggestions are made for further research.

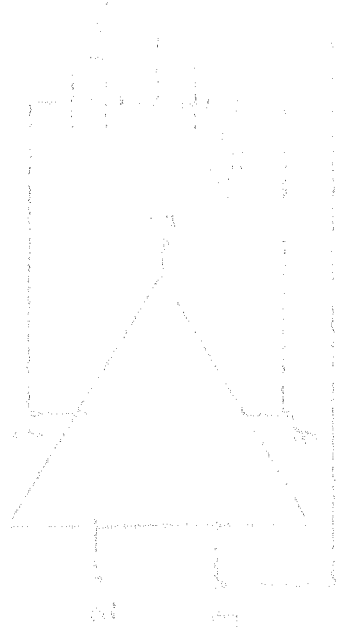


Figure 1: Schematic diagram of the mechanical system.


The first part of the report is a general introduction to the subject of the study. It discusses the importance of the problem and the objectives of the research. The second part is a literature review, which examines the work of other researchers in the field. This is followed by a description of the experimental method used in the study. The results of the experiment are then presented, and a discussion is given of the implications of the findings. Finally, a conclusion is drawn from the study, and suggestions are made for further research.

the power supply. The common emitter amplifier is an inverting amplifier, and the common collector amplifier is a non-inverting amplifier. The common emitter amplifier has a voltage gain of approximately 100, and the common collector amplifier has a voltage gain of approximately 1. The common emitter amplifier has a high input impedance, and the common collector amplifier has a low input impedance. The common emitter amplifier has a low output impedance, and the common collector amplifier has a high output impedance. The common emitter amplifier is used for voltage amplification, and the common collector amplifier is used for current amplification and buffering.

The common emitter amplifier is available. Protect the amplifier from damage and the circuit, and the output to the circuit, and observe the output waveform.

Common Emitter Amplifier

The circuit is shown below:

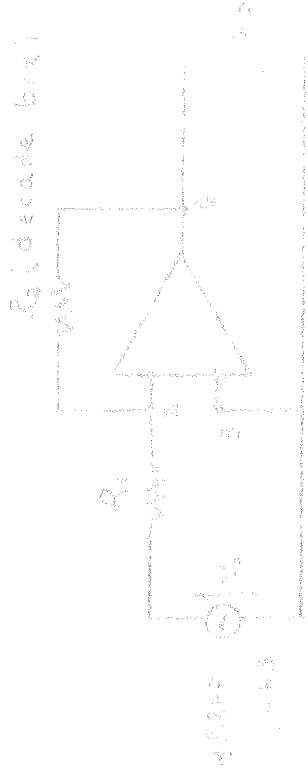


The circuit is shown below. The circuit is a common emitter amplifier. The input signal V_{in} is connected to the base of the transistor. The base is biased by a voltage divider consisting of resistors R_1 and R_2 connected to a 5V supply. The emitter is connected to ground. The collector is connected to a 10V supply through a resistor R_3 . The output signal V_{out} is taken from the collector. The circuit is labeled 'Common Emitter Amplifier'.

The measured gain of the common emitter amplifier is approximately 100. The measured gain is lower than the theoretical gain because of clipping. Clipping occurs when the output signal reaches the supply rails. The clipping is caused by the power supply voltages. The clipping is caused by the power supply voltages. The clipping is caused by the power supply voltages. The clipping is caused by the power supply voltages.

the output of the integrator is fed back to the input of the integrator.

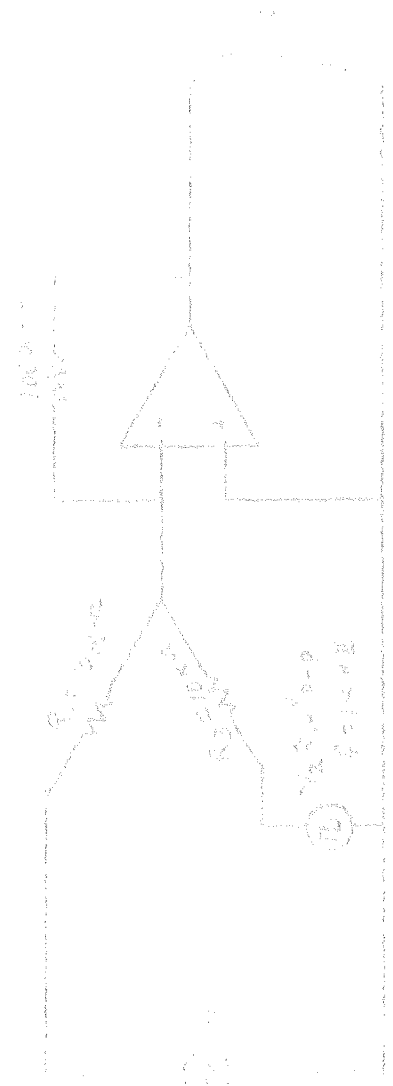The output of the integrator is a square wave. The amplitude of the square wave is determined by the feedback network. The frequency of the square wave is determined by the RC network.




When the square wave generator so V_2 is 10V, the output V_0 will be 10V. When the square wave is 0V, the output V_0 will be 0V. The output V_0 is a square wave. The amplitude of the square wave is 10V. The frequency of the square wave is 100Hz. The output V_0 is a square wave. The amplitude of the square wave is 10V. The frequency of the square wave is 100Hz.

When the square wave generator so V_2 is 10V, the output V_0 will be 10V. When the square wave is 0V, the output V_0 will be 0V. The output V_0 is a square wave. The amplitude of the square wave is 10V. The frequency of the square wave is 100Hz.

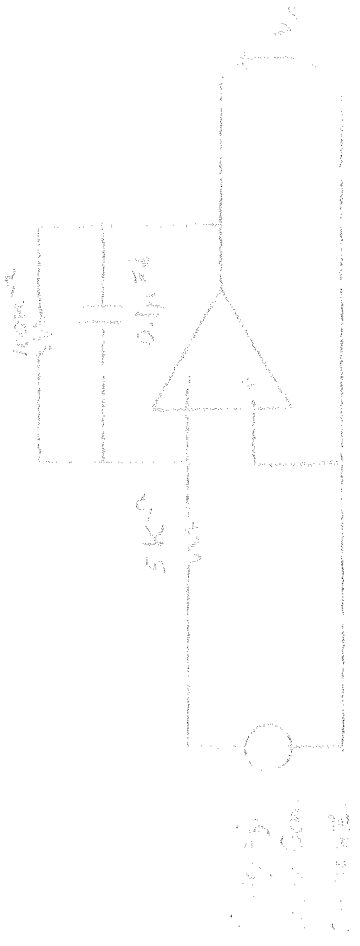2.2. Integrator

The integrator is added in the feedback loop. The output of the integrator is a square wave. The amplitude of the square wave is 10V. The frequency of the square wave is 100Hz. The output V_0 is a square wave. The amplitude of the square wave is 10V. The frequency of the square wave is 100Hz.



CILFIELD AUTOMATION SIMULATION

May 9, 1975

By Mark Carpenter

OILFIELD AUTOMATION SIMULATION

This program is a dynamic simulation of an oilfield to be utilized as a teaching aid in the understanding of digital control systems. The complete systems dynamics are incorporated in the program so that the user may write a control program for the field.

Designation of Program Variables

The following is a list of matrix variables, their dimensions, and usage in the program.

- Q(A) Well
- Q(K)=J
- P(A) Well Status P(K)=1 then Well K is on
 P(K)=0 then Well K is off
- X(A) Output of well in a fractional number
- Y(A) Input of a well in a fractional number
- W(K) Manifold Status W(K)=1 means Well K feeds Separator 1
 W(K)=2 means Well K feeds Separator 2
- Z(A) Complement of $W(K)-1$
- B(6) Total tank capacities for the two separators, two oil holding tanks, and two water holding tanks
- L(14) Various valves in the oilfield

C(14) Pump capacities of the pumps

B(2) Water outlet levels in the two separators

F(2) Oil outlet levels in the two separators

T(6) Total fluid volume in the six tanks

O(2) Oil volume in the two separators

X(2) Water volume in the two separators

The letter T designates the sample time in hours, and T9 is a counter to keep up with the total time period accumulated. Also used in the program are O1, O2, O3, O4, I1, I2, I3, I4, S5, S6, S7, S8, W1, W2, X, and K6. Care should be taken in the writing of the control program to prevent an overlapping of variables.

The Oilfield

The oilfield (Figure 1) has four wells, two separators, two oil holding tanks, and two water holding tanks. The valves are designated by X and are numbered. The pump locations are marked with a V and have the same subscript number as the valves at that location. For instance, C(6), or pump number 6, is located at valve L(6), where at valve number 9, L(9), there is no pump.

T(1) and T(2) are Separator 1 and Separator 2, T(3) and T(4) are the water holding tanks, and T(5) and T(6) are the oil holding tanks.

The entire control scheme centers around the two separators. Figure 2 shows a separator and various outlet locations.

Since the tanks are cylindrical, the volume is directly proportional to the height of the fluid. The main program sets $F(K)$ at 50% and $E(K)$ at 33.3% of the total tank height or volume. $I(K)$ is the water level of the tank and $T(K)$ is the total fluid level in the tank.

The control program will contain $X(K)$, $F(K)$, $T(K)$, $I(K)$, and $O(K)$ as fractional portions of the total tank capacity, $S(K)$.

The Control Program

The control program will be interfaced with the main program so that the main program will record accumulations in the tank and the control program will control the flows into and out of these tanks. Figure 3 shows a flow chart of the relationship between the main and control programs.

When the program is initially started, it goes through the dynamics first and then to the control program. The control program should monitor the tanks and make appropriate valve status changes. After the control operations are completed, the main program will transfer to the system dynamics, and the tank accumulations will again be calculated with the new valve statuses.

Inputs by the Operator

The following questions will be asked to the operator when the program is initially started:

1. Is Well 1-4 ON or OFF
2. Does Val: 1-4 Feed Separator 1 or Separator 2
3. What are the tank capacities in barrels
4. What are the Pump Capacities in GPM (the program will convert it to barrels/hour)
5. What is the valve status of V(9) and V(10) (water holding tank manifold)
6. What is your sample time in minutes (the program will convert it to hours)

These values will be asked only once during the program. The sample time will determine how often the control loop will monitor the various tank and interface levels.

The System Dynamics

The system dynamics are simple rate and accumulation equations whose dimensions are barrels and hours. The change in accumulation is calculated by multiplying the difference of the input and output by the sample time. A number of if statements are used to prevent the mathematical equations from exceeding the system's physical limitations. For instance, the total fluid volume cannot exceed a tank volume. The program will terminate anytime a tank overflows, water gets in the oil tank, or oil gets in the water tank.

Print Out

The main program will print once each sample time. The total accumulated time, the volumes of fluid in all the tanks,

and the outflow level. The two capacities of the pipes are given as input. The outflow level is determined by the operation should be performed from the control program.

Here I would like to explain the control program.

1. The variables $W(X)$ and $I(X)$ are the only variables that the control program should alter. All other variables can be compared with a control variable, but they should not be changed.
2. The control program will see the sample time in minutes, not minutes.
3. The fluid volume $V(X)$, interface level $I(X)$, and volume $Q(X)$, will be given as a fractional part of the total tank capacity $B(X)$.
4. The water outlet level and oil outlet level $W(X)$ and $S(X)$ respectively, are also in a fractional form of the total tank size.
5. The control program should be written from statements 2000 to 8999. Statements 1-10 can be used to count the counters.
6. The last statement in a control program should be a Remark statement. Any time the program needs to be transferred to the main program, send it to your last statement. The main program will pick it up as the following.

Conclusion

The program is set up to do in the working of digital control systems. The program has the potential of determining how about the operation of digital control systems, from the amount of understanding derived from the program is proportional to the amount of time and effort put in by the operator.

A group of Chemical Engineering students wrote the first control program for the system. Two students in particular, Gerald Dreyfus and James Simpson, did exceptional work, and their control programs aided in the final polishing of the main program.

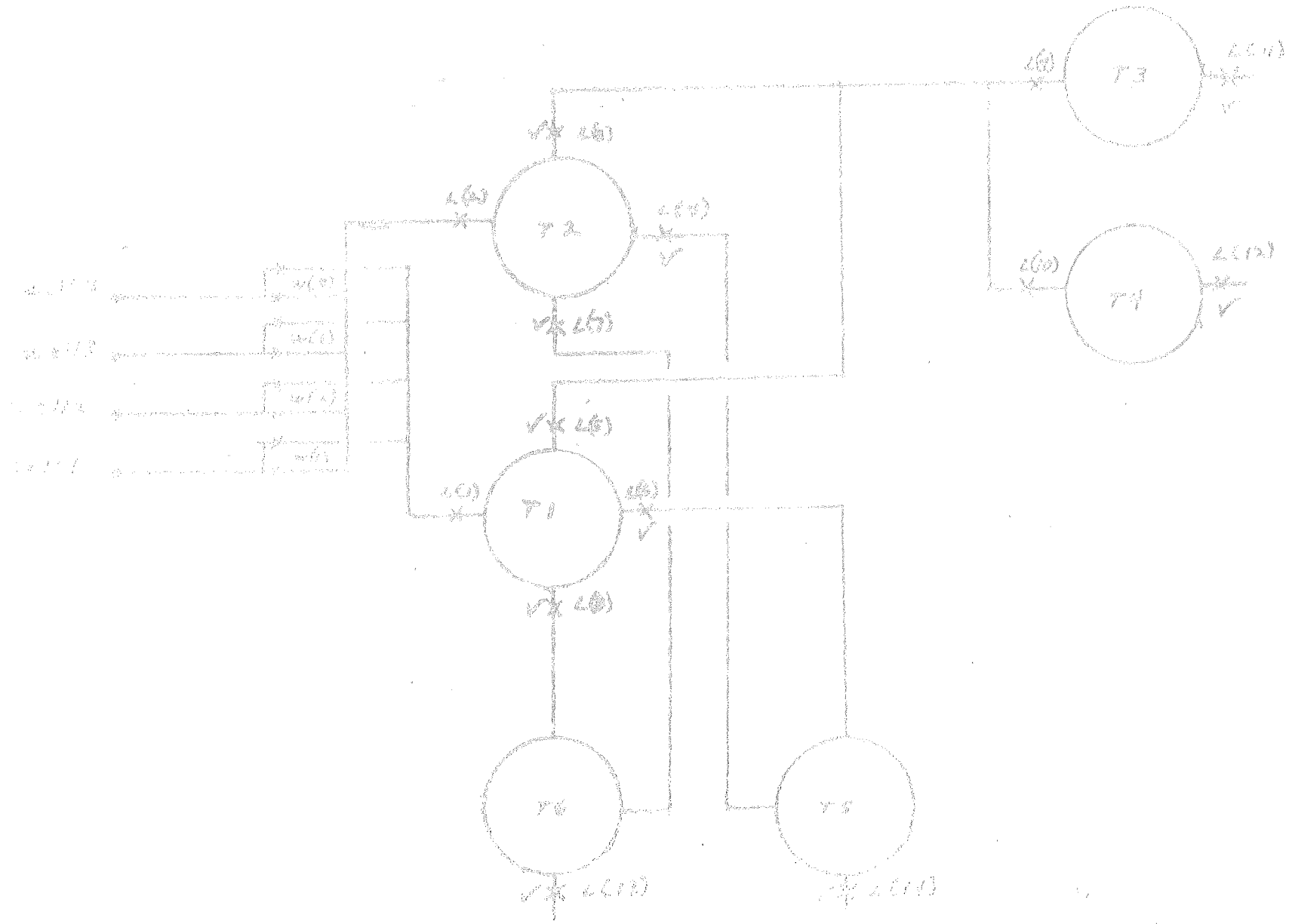


FIGURE 1. SIMPLIFIED MODEL.

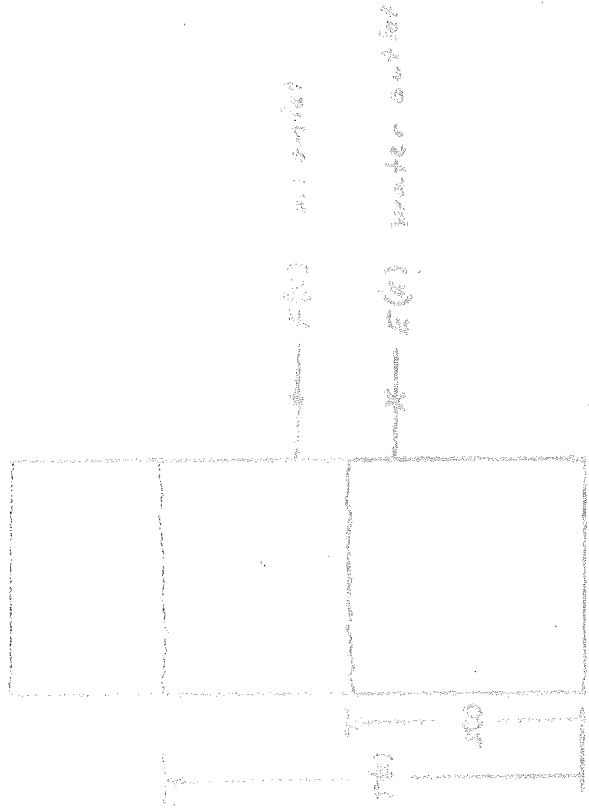


FIGURE 2
A SEPARATOR

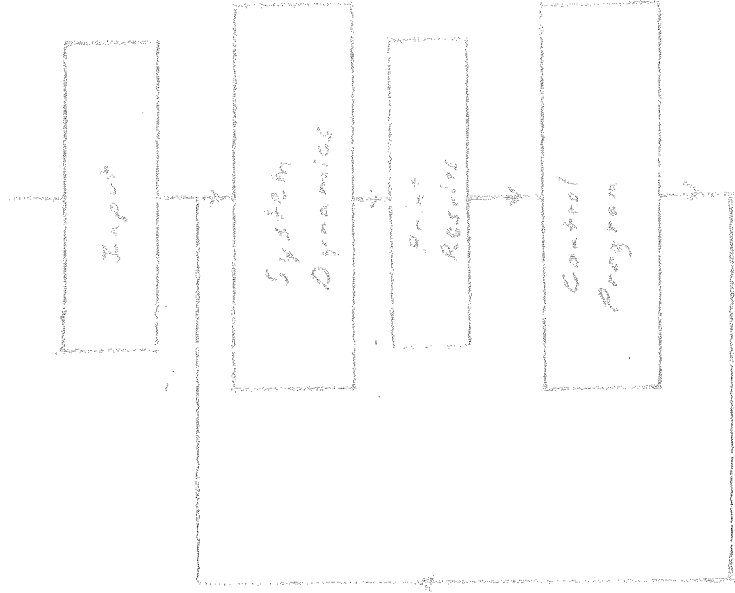


FIGURE 3
PROGRAM FLOW CHART

4 A's
 5 B's
 10 C's
 5 D's
 4 W's
 1 I

SEMESTER SESSION 19.....19.....
 SUBJECT EE 234
 SECTION..... CLASS PERIOD..... ROOM.....
 ASSISTANT.....

SPRING
 1977

HW = 1070
 ΣT = 4070
 F = 3090
 L = 2070

NAMES	MONTH DATE	TESTS			ΣT	HOMEWORK									ΣHW	ΣT	F	L	FINAL GRADES			
		#1	#2	#3		#1	#2	#3	#4	#5	#6	#7	#8	#9								
1		41	90	100	231	10	-	-	11E	25	27	29	80	52	234	231	294	91	79	B	10	
2		85	91	100	276	12	-	33	28	30	-	80	50	233+20	276	339	94	89	B	4		
3		69	94	98	261	10	-	27	23	30	26	20	80	48	264	261	284	87	82	B	8	
4		78	83	100	273	14	27	33	18E	28	23	21	80	47	291	273	350	89	90	B	2	
5		38	DROPPED			-	13	10	32	DROPPED			-	-	-	-	-	-	25-	-	A	2
6		83	91	100	274	9	29	40	29E	27	15	21	80	47	297	274	293	87	86	B	6	
7		64	52	37	-	10	12	14	-	26	-	-	42	50	154+20+50	153	208	87	61	B	20	
8		75	96	92	263	7	21	25	23	23	25	25	80	44	273	263	343	89	88	B	5	
9		53	81	95	229	12	-	23	22E	23	15	22	40	50	207+20	229	245	88	74	C	17	
10		58	DROPPED			-	17	23	34	DROPPED			-	-	-	-	-	25-	-	C	17	
11		68	97	94	259	10	8	-	-	-	24	-	-	-	42+20	259	292	86	76	C	16	
12		66	88	100	254	12	23	29	23	27	23	10	80	37	264	254	221	92	78	C	19	
13		82	92	100	294	-	23	33	24	23	24	26	60	50	263+20	294	370	81	93	C	1	
14		54	94	76	224	18	13	32	29	24	29	25	80	47	297	224	296	88	80	C	9	
15		65	90	95	250	7	-	30	22	28	8	15	75	45	241+20	250	255	85	78	C	12	
16		37	63	84	184	7	-	23	-	26	-	-	40	40	129	184	184	80	59	C	23	
17		32	77	79	188	7	-	19	-	-	-	-	42	38	106+20	188	201	74	59	D	23	
18		47	72	(95)	188	11	6	34	19	-	24	23	80	50	117	I 247	I 214	I 360	I 68	I 81	D	1
19		44	DROPPED			-	14	23	27	DROPPED			-	-	-	-	-	-	25-	-	I	1
20		43	73	86	-	6	-	-	-	25	10	13	80	48	182+20	202	289	70	69	I	19	
21		54	95	100	249	10	16	28	23E	27	20	-	20	48	192	249	301	83	79	C	10	
22		61	63	39	-	7	-	12	-	26	-	-	42	40	127+20	163	241	74	60	C	20	
23		81	91	92	264	16	-	-	10	-	21	7	80	44	55+20	264	310	85	78	C	12	
24		69	84	64	217	12	25	34	23	30	29	22	80	44	299	217	311	78	78	C	12	
25		72	97	100	269	14	12	25	28E	30	28	-	80	48	265	269	369	89	90	C	2	
26		DROPPED			-	5	DROPPED			DROPPED			-	-	-	-	-	-	15-	-	A	1
27		57	69	72	198	2	-	-	15	-	-	-	-	-	17+20	198	226	79	60	W	20	
28		69	83	74	226	-	-	31	17	26	29	23	-	45	171	226	265	73	70	D	18	
29		78	84	98	250	16	14	33	18	19	28	22	60	50	260	260	306	92	85	C	7	
		MAXIMUM →			100	100	100	300	20	30	40	30	30	60	50	320	300	400	100		B	24

90-100: 11	100%: 9	0.450-0.500 → 1	FINAL GRADE	HP-25	PROGRAM	(L)	X
80-90: 7	90-100: 15	0.4 - 0.45 → 5	(ΣH.W.)	(ΣT)	A	STOD: 400	RCLD
70-80: 2	80-90: 3	0.35 - 0.4 → 10	ENT. 11 X	ENT	X	RIS	+
60-70: 3	70-80: 4	0.3 - 0.35 → 1	300	STOD	300	RCLD (F): 13	STOD
	60-70: 1			RIS		ENT: X	RIS
	50-60: 0						
	40-50: 0						
	30-40: 2						

1. THE GRADE I EXPECT TO RECEIVE IN THIS COURSE: A B C D F
2. THE GRADE I FEEL I SHOULD GET IN THIS COURSE: A B C D F
3. THE THING I LIKED BEST ABOUT THIS COURSE:

4. THE THING I LIKED LEAST ABOUT THIS COURSE:

5. THE NEATEST THING I LEARNED IN THIS COURSE:

6. THE TOPIC COVERED IN THIS COURSE WHICH I STILL DON'T QUITE UNDERSTAND:

7. IF I HAD IT ALL TO DO OVER, I WOULD (a) STILL REMAIN IN THIS SECTION (b) SWITCH TO AN OTHER SECTION (c) PUT OFF TAKING THE COURSE (d) DROP OUT OF SCHOOL AND SELL VACUUM CLEANERS.
8. THE COORDINATION BETWEEN LAB AND LECTURES WAS (a) EXCELLENT (b) GOOD (c) FAIR (d) POOR (e) NONEXISTANT
9. THE LECTURES WERE PRESENTED (a) EXCELLENTLY (b) PRETTY GOOD (c) FAIR (d) POOR
10. MY GRADE FOR THE INSTRUCTOR IS: A B C D F
11. THE QUIZES GIVEN WERE REPRESENTATIVE OF THE MATERIAL COVERED (a) AGREE (b) DISAGREE
12. THE HOMEWORK HELPED ME TO BETTER UNDERSTAND THE MATERIAL (a) AGREED (b) DISAGREE.
13. BOB MARKS IS A SWELL FELLOW AND AN ALL-AROUND NICE GUY (a) AGREE (b) DISAGREE.
14. I FEEL THIS COURSE WILL HELP ME IN MY CAREER (a) A LOT (b) A LITTLE (c) NOT AT ALL (d) IN A NEGATIVE SENSE

COMMENTS:

1.

1. A

2. A

3. EASY

4. LAB

5. OP AMPS

6. Fourier SERIES

7. A

8. E

9. A

10. A

11. A

12. A

13. A

14. A

W333
2222
4444
3333
5555
6666
7777
8888
9999
0000
1111
2222
3333
4444
5555
6666
7777
8888
9999
0000
1111
2222
3333
4444
5555
6666
7777
8888
9999
0000



1. C

2. C

3. NOT MUCH (Empty box)

4. LAB

5.

6. UNACQUAINTED

7. a.

8. D

9. A

10. A

11. A

12. A

13. A

14. C

- 1) A
- 2) B
- 3) The instructor and that's about all.
- 4) The lab
- 5) None
- 6) Linear system theory
- 7) a
- 8) b
- 9) b
- 10) A
- 11) a
- 12) a
- 13) a
- 14) C

10/10

1 - C

2 - C

3 - it is NOT my major

4 - LAB

5 -

6 - FOURIER - SAMPLING

7 - D

8 - B

9 - A

10 - A

11 - A

12 - A

13 - A

14 - B

1. A

2. A

3. BOOLEAN STUFF & CODING

4. ABSTRACTS OF EE

5. HAMMING CODE

6. ELECTRO-MECHANICS

7. A

8. D

9. B

10. B (on spelling)

11. A

12. A

13. A

14. B

15. HOUR TESTS SHOULD BE LIMITED TO 1 HOUR

1. C
2. C
3. It only meets twice a week.
4. Too many topics and I really don't know much about anything.
5. Discussion of far out wild EE material
6. Electro mechanics
7. A
8. D
9. B
10. B
11. A
12. A
13. A
14. C



1. A
2. A
3. Subject covered are general enough
4. (except Fourier Transform series I'll never see anywhere else)
not even in math. Probably same with electromech systems
5. Hamming codes, modulation
6. Fourier Series, transforms
7. A
8. E
9. C
10. B
11. A
12. A
13. A
14. A or B



(1) A

(2) A

(3) Sampling theorem and Multiplexing, Modulation

(4) Fourier Series, Part

* should count first to more than 2nd and 3rd tabs.

(5) Binary channels and coding

(6) Fourier series

(7) stay in this section A)

(8) E) non existent

(9) A)

(10) A)

(11) A)

(12) A)

(13) A)

(14) C)


1. C
2. C
3. Modulation
4. Homework
5. Boolean logic
6. OP-AMPS
7. a
8. c
9. b
10. A
11. a
12. b
13. a
14. b

1. B
2. A → B
3. ~~GOOD~~ DON'T HAVE TO STUDY ALL THE TIME
4. ~~GOOD~~ LAB
5. HOW LUCKY I ^{AM} ~~WAS~~ TO NOT BE AN EE MAJOR
6. ELECTO-MECHANICS + DIODES & RECTIFIERS
7. STAY IN THIS SECTION
8. PIS-POOR
9. PRETTY GOOD
10. B⁺
11. Agree
12. Agree
13. C
14. a little (b)

COMPUTER PROGRAM ASSIGNMENT WAS STUPID & A LOT OF
NEEDLESS WORK & WORRY.

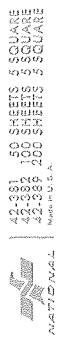- 1) A
- 2) A
- 3) informal atmosphere
- 4) Lab & tests
- 5) Impedance bridges
- 6) Fourier Series
- 7) remain in this section
- 8) nonexistent
- 9) B) Pretty good
- 10) B⁺
- 11) A
- 12) A
- 13) A
- 14) ~~very little~~ C

- ① B
- ② B
- ③ Boolean logic
- ④ Laplace transform, Fourier series
- ⑤ modulation
- ⑥ Impedance bridges
- ⑦ A
- ⑧ C
- ⑨ B
- ⑩ A
- ⑪ A
- ⑫ B
- ⑬ A
- ⑭ B



1 C-B

2 B

3 fun

4 LAB

5

6 Linear System

7 B

8 B

9 C

10 B

11 A

12 A

13 A

14 B

1. A

2. A

3. lectures are interesting

4. -

5. Sampling theorem

6. FOURIER SERIES

7. A

8. B

9. A

10. A

11. A

12. A

13. A

14. B

TEACHER EVALUATION

1. A
2. A
3. NOT TOO MUCH HOMEWORK
4. Lab
5. small idea of how computers work
6. FET & BJT circuits
7. (A)
8. (B)
9. (A)
10. A
11. A
12. YES (A)
13. A
14. (B)
15. NO PROGRAM

①

C

②

B-

③

Linear system theory, coding & binary channels
Op. amp

④

SAMPLING THEOREM, FOURIER SERIES

⑤

Everything

⑥

Electro-mechanics

⑦

a)

⑧

C) FOR

⑨

B) GOOD

10)

B-

11)

A) agree to a certain extent

12)

A) agree

13)

A)

14)

A) a lot

1. C
2. B
3. ~~NO TRICKS~~ NO TRICKS ON EXAMS OR H.W.
4. NA
5. USE OF BASIC PROGRAMMING
6. SAMPLING THEORY
7. a) REMAIN
8. c) POOR
9. b) GOOD
- 10.
11. a) AGREE
12. a) AGREE
13. ONLY STRIVE MAINLY CAN SAY THAT
14. C

1. D
 2. F
 3. WANNER TAUGHT
 4. DON'T ENJOY STUDYING EE
 5. BOOLEAN ALGEBRA
 6. SAMPLING
 7. A
 8. D
 9. B
 10. A
 11. A
 12. A
 13. A
 14. C
-

HELP!

EVALUATION

1. C
2. D
3. trip to Power Plant
4. Lab
5. how a three way light switch work
(~~the~~ pathway to hell is paved with good intentions)
6. Fourier series
7. A
8. E
9. A
10. A
11. A agree
12. agree when I get the solution.
13. well maybe but then maybe not
14. B

- 1) C
- 2) C
- 3) Last 2 tests
- 4) Lab
- 5) Hamming ~~coding~~ code & how it works.
- 6) Electro Mechanics & fourier series, Laplace transforms
- 7) (A)
- 8) (E) and below
- 9) (B) \rightarrow a little fast
- 10) (A)
- 11) (A)
- 12) ~~AB~~ (A)
- 13) (A)
- 14) (B) \rightarrow teaches discipline (only kidding)

1. B

2. B

3. It's nothing like anything I've ever seen before
I enjoyed the last part best - for the 3rd test binary #'s cut

4. lab

5. ~~They that I don't understand~~ Coding -

6. IA PDS & Fourier theory

7. A

8. E

9. A

10. A

11. A

12. A

13. A.

14. C